 




# XORAM MEMORY CELLS

Design and power consumption  
L. Fontini – A. Stabile

# ASSOCIATIVE MEMORY CELLS GOALS





# BLOCK ARCHITECTURE — AM07A

The 18-bit word line blocks have been piled up to compose and array of **18 × 64 bits**


**Buffers** placed at the top of the array

The **shift registers** is used to write and read the memory bank just for prototype characterization; in the new chip there will be different logic

  **Single cell area** is  $1.17 \mu\text{m} \times 0.98 \mu\text{m}$ , and the block area is  $6925 \mu\text{m}^2$  : **factor 3** w.r.t. old cell designed at 65 nm




# THE XORAM CELL

 

Based on XORAM CELL instead of NAND and NOR function.


 
Is made of a 6T SRAM cell connected to a 6T-XOR gate



10T XORAM + 18 input NOR
  
# BLOCK DESIGN




- **Bit Lines** propagation: top to bottom
- **Write-lines** propagation: left to right
- **Flip-Flop** at the end of each layer enabled by an **EN** signal
- Logic **NOR** tree integrated into the layer



# SOME STORY

Version	XORAM version	Technology	TOP2 size ( $\mu\text{m}^2$ )	Consumption (fJ/comp/bit)	BL cap. (fF/line)
<b>AM05a</b>	v3	65nm		Selective Precharge	
<b>AM06</b>	v4	65nm	21075	0.76	0.027
<b>AM07a</b>	v5	28nm	6925	0.53	0.0235
<b>AM07b</b>	v6	28nm	5202	0.13	0.0167

# DESIGN PROGRESS

   


# POWER SAVE METHODS

## Minimization of parasitics

- 70% of dynamic power consumption is due to **propagation of bitline data**
- Block layout has been designed aiming at **minimizing bitline RC parasitic**
- Bitline wires have been designed in the **first metal layer (M1)**
- Bitline capacitance: 18 fF at CMOS 28 nm w.r.t 27 fF at CMOS 65 nm
 
## Clockless circuit

- enable is given on the 18<sup>th</sup> bitline



# OPTIMIZE BUFFER W/L AND # OF ROWS

Given 6 different worst cases:

- TT: 0.9 V, 27 °C
- SS: 0.81 V, 0 °C
- ...

Given a fix  $t_{prop}(BL, BL_{out})=218ps$   $\psi = \frac{t_{prop}(BL, BL_{out})}{n}$ ;  $n \in \{16, 32, 64, 128, 256\}$   $\psi = 218 ps/64$

W/L should be change with the # of rows within the macro block.

Each macro block have Buffers on the top

We extract RC parasitics for 5 different row blocks:

- 16,32,64,128,256

**Find the optimum solution that minimize the power consumption for each 5 different row block, W/L and worst cases**

# SIMULATIONS

Tuning the  $W/L$  and the stades of BL and SL buffers

Parametric simulation by changing the  $W/L$  and the  $C(\text{load})$

Comparing the result with simulations:

If the minum point of the table is the same we demonstrate a strong correlation between the  $C(\text{load})$  and the power consumption

# CONCLUSIONS

DONE:

- ✓ Design of 28nm XORAM cell
- ✓ Optimization of BL capacitance
- ✓ Power consumption minimization
- ✓ Area reduction

TO DO:

- BL buffer design
- Cell characterization

