

BESIII



CGEM ASIC Details

Chongyang Leng

14th April, 2016 Turin

BESIII CGEM FEE/DAQ/Trigger Workshop

Outline

- Design pros of the Frontend ASIC
- Structure of the Frontend ASIC
- Charge measurement
- Time measurement
- Layout of the chip and post simulations

Front-end ASIC


➤ Sensor parameters

- Input charge : 1fC to 50 fC
- Sensor capacitance : up to 100pF
- Signal width : 50 ns to 100 ns

➤ ASIC Requirements


- Data Rate : 60KHz (with safety factor of 4)
- Power consumption per channel : < 10mW
- Time jitter : < 5ns
- ENC noise : < 1000e

Channel Structure

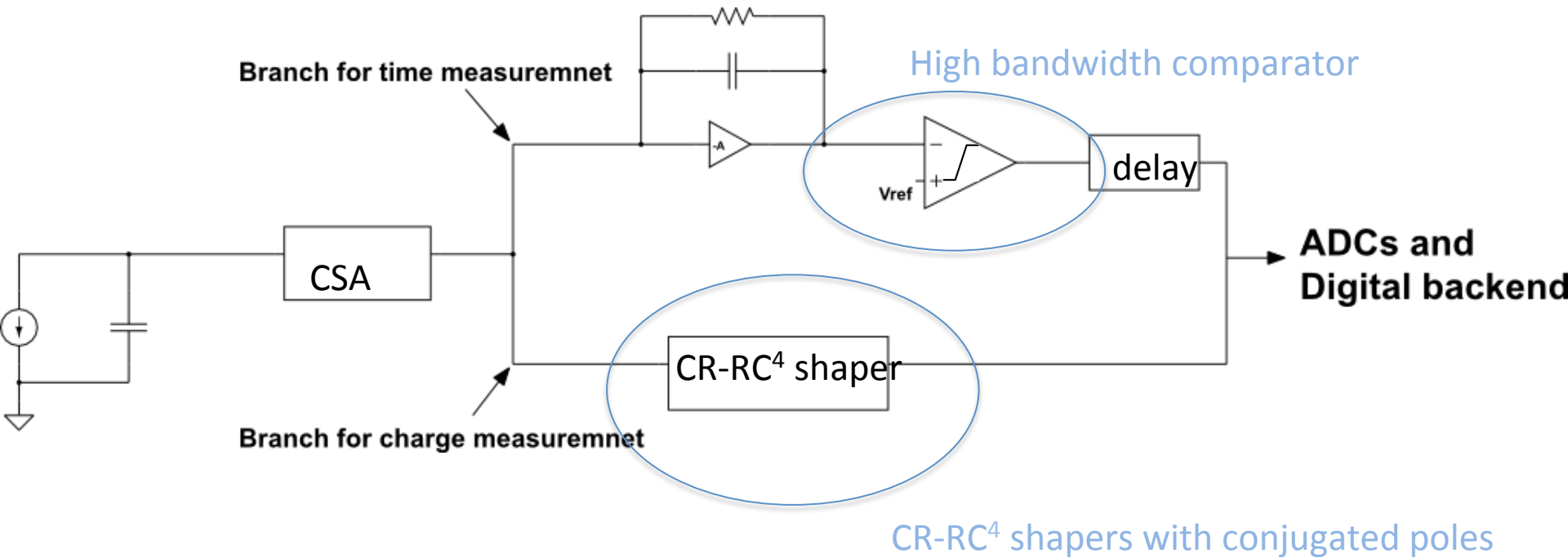


Preamplifier Implementation

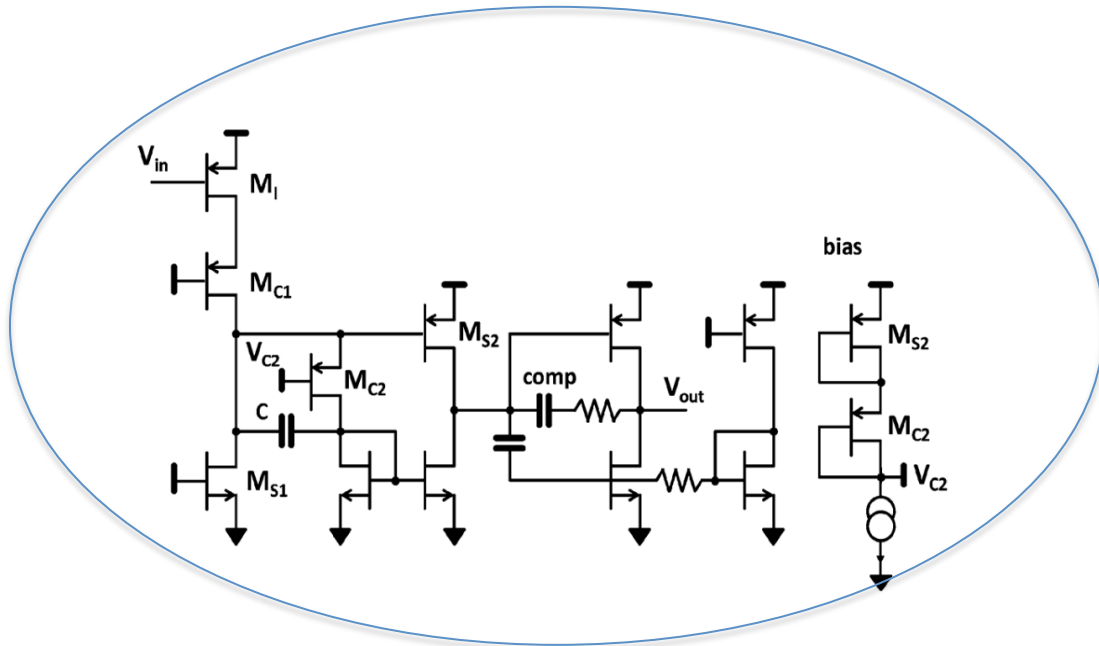A low noise charge sensitive amplifier strategy




Charge Sensitive Amplifier

 Current mode feedback structure, to get precise duplicated input signals for both branches






Charge measurement

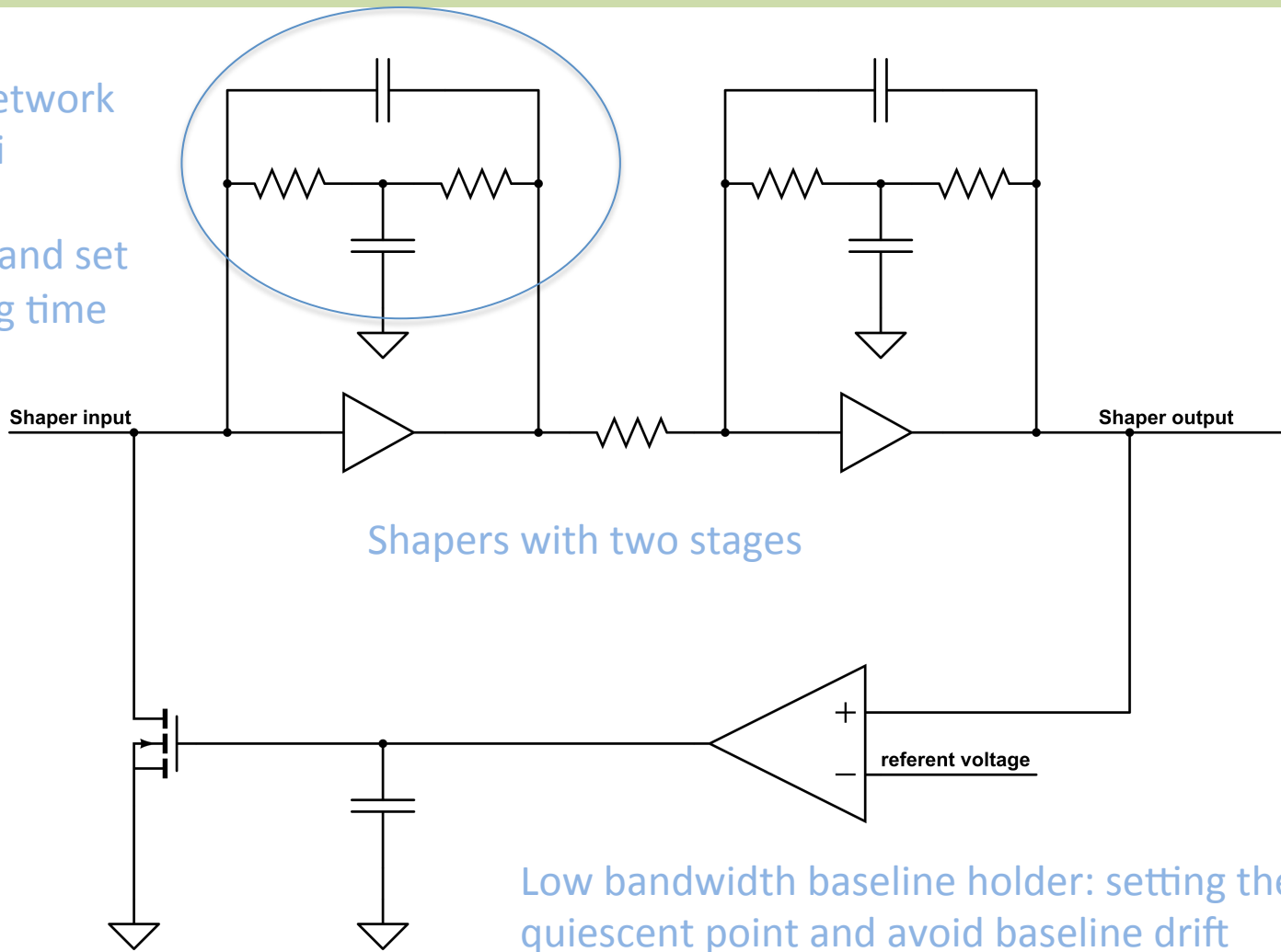T-bridge network
to get semi
Gaussian
waveform and set
the peaking time
to $\sim 200\text{ns}$




Performance and Results

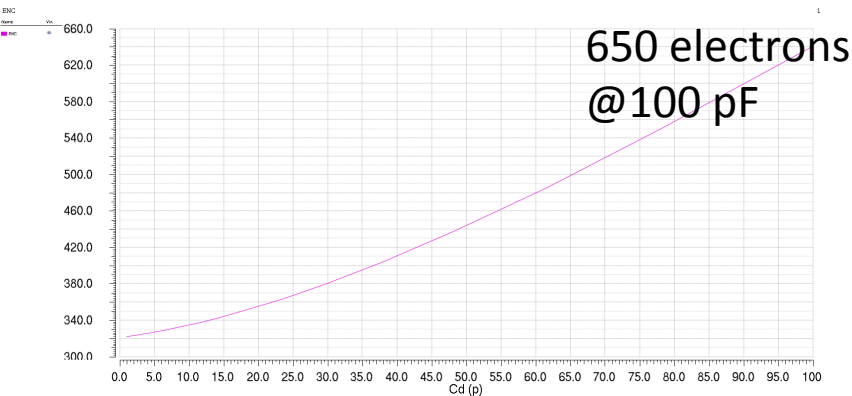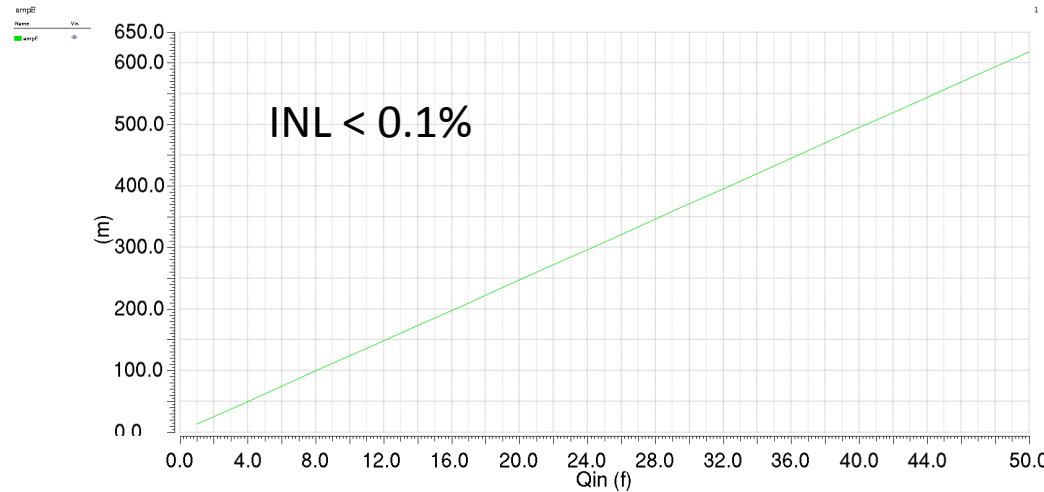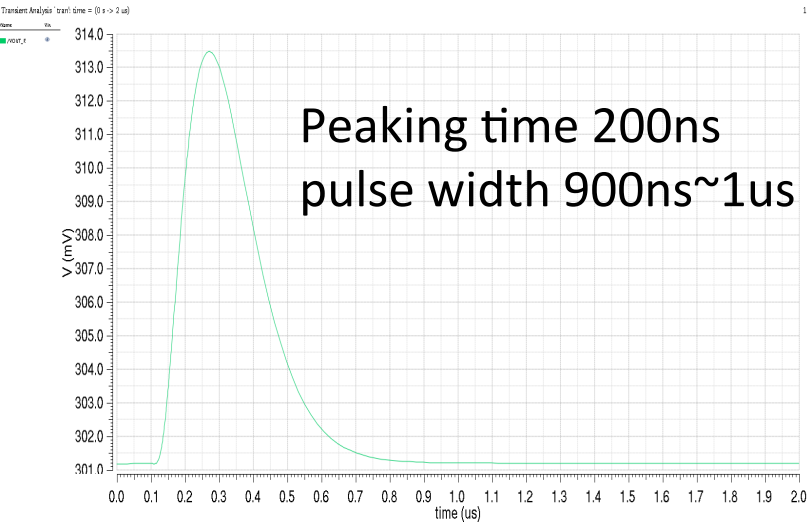

- Detector capacitance up to 100pF
- ENC: <700 e @peaking time =200ns,
- Power consumption per channel \approx 5mW
- Full signal pulse width < 1us
- Non-linearity = 0.08% (1fC to 50fC)
- Noise ratio \approx 3.6 e/pF
- Gain \approx 12mV/fC

Timing Jitter Measurement

 


Observing the output of the discriminator in the transient noise simulation (100 runs), we can get the time jitter by the plot or by empirical formula.

Timing Jitter Measurement

Transient Response

Wed Nov 25 15:00:22 2015



Name ...n
/VOUT_T
/FE_OUT

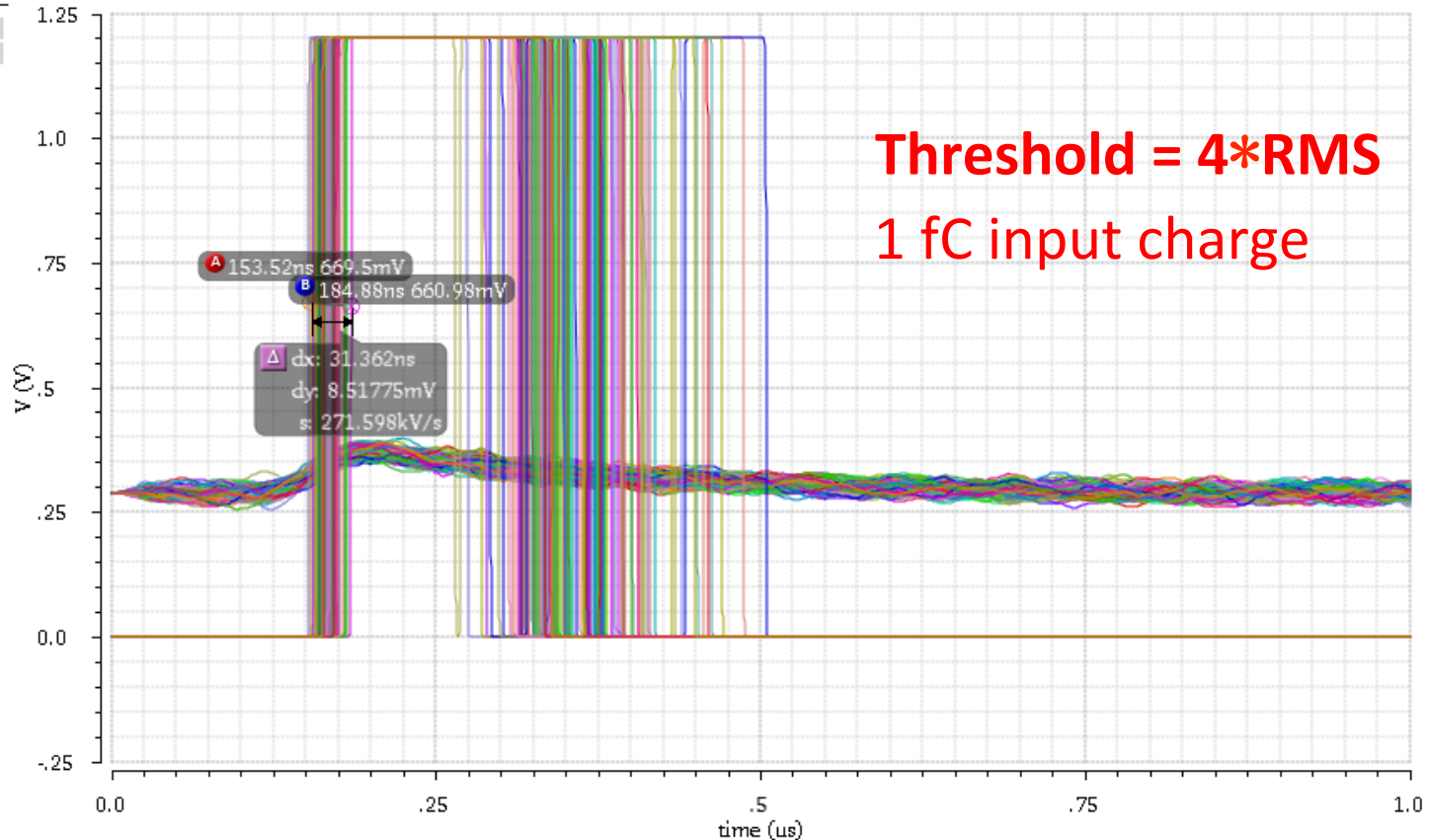

Jitter Simulation: Calculated by equation refers to Maximum slope

\Rightarrow jitter = rmsNoise/slope \approx 5.5ns

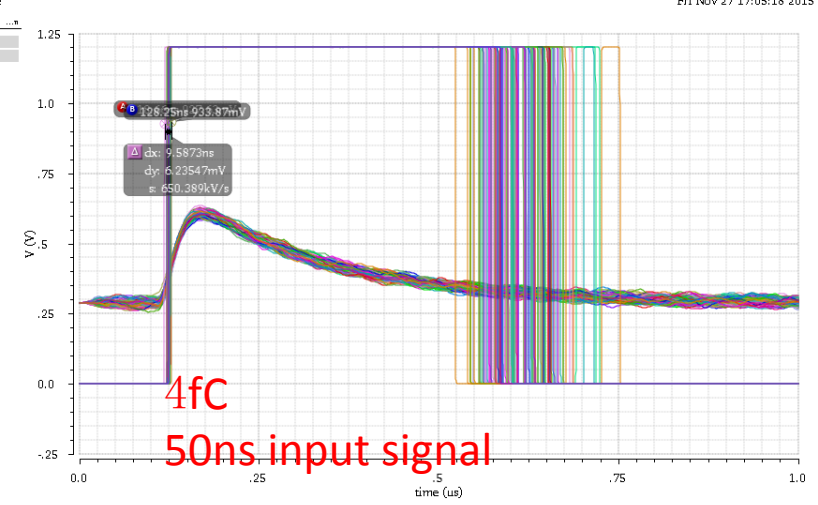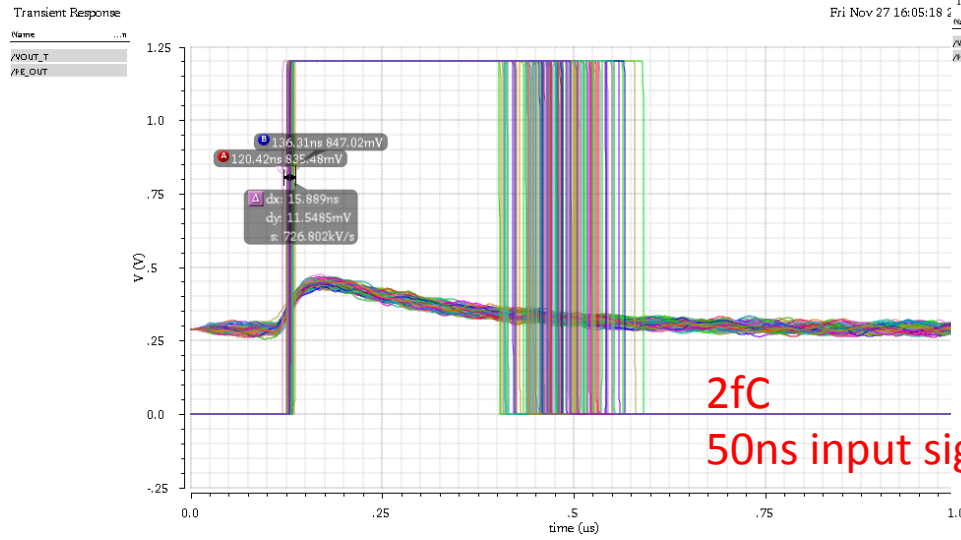
\Rightarrow From output of discriminator: jitter = dx/6 = 5.2ns



Input= 2fC jitter= 15.8ns/6 = 2.63 ns

Input= 4fC jitter=9.6ns/6= 1.6ns

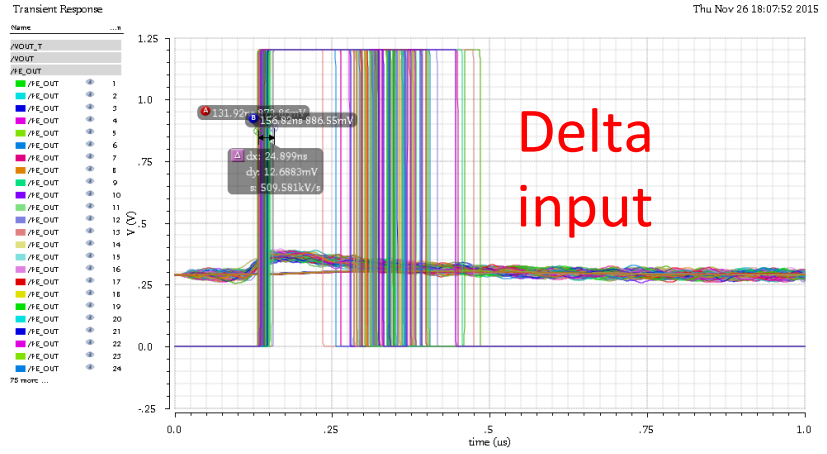Timing jitter will be exactly the reciprocal of input charge. If we will not always have input signal as small as 1fC, the jitter performance would be better.




Concerning the FEE itself(delta input signal) Peaking time = 65 ns
jitter = 24.8ns/6 = 4.2ns

Faster output also leads to less time jitter.



Layout

 


Layout of one single channel. Size $72\mu\text{m} * 1350\mu\text{m}$.


Parasitic problems in post-layout simulations:

- Parasitic resistance
 - > Noise increased from the input parasitic resistance
- Parasitic capacitance
 - > introducing small feedback capacitors in the loop and then oscillation in system
- Resistance and inductance introduced by the power grid
 - > Amplitude deterioration
- Crosstalk between neighboring channels

Post simulations

 


Output of the Charge sensitive amplifier

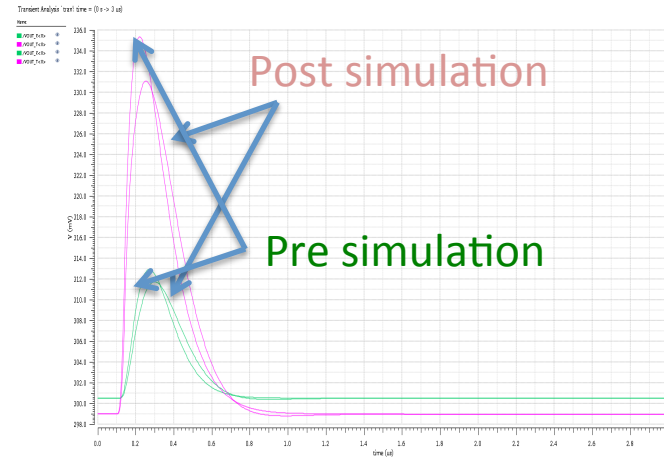



Output of the shaper(Charge and time branch)

	Pre-Simulation	Post-Simulation
ENC noise/e	640	698
Timing jitter/ns	5.5	6.0
Output amplitude/ mV	12.3	11.0
Pulse width/ns	830	910
Linearity	< 0.1%	<0.1%

Post simulations

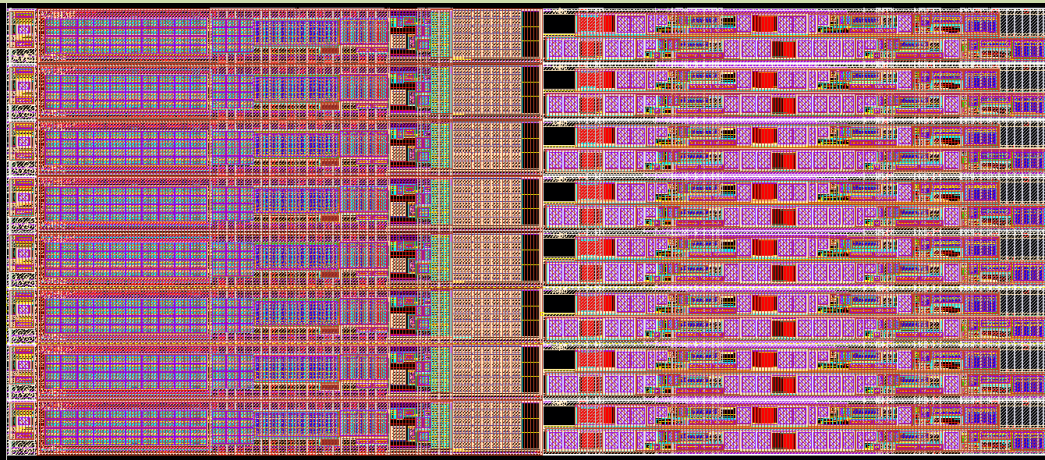

Simulations with 8 channels

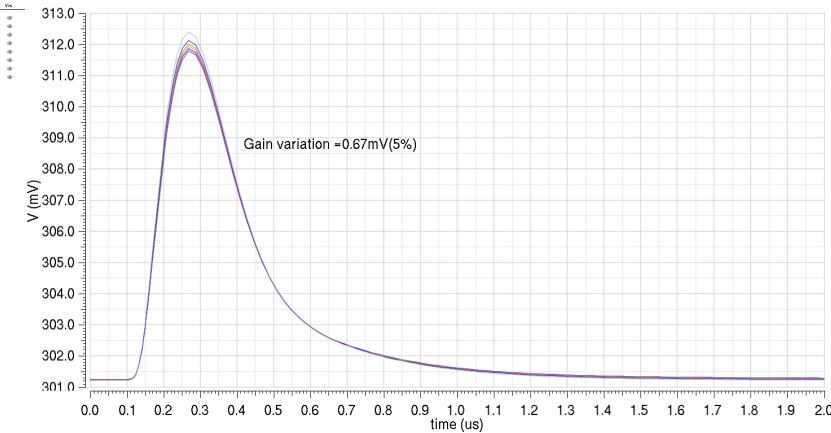 

Crosstalk results. Simulated with 50 fC input charge and 2nH inductor(Considering the power bonding)

Gain Variation: about 5% between channels. This will be better after power grid applied.

Summarys

- ◆ 64 channel layout ready
- ◆ Layout of bias cells undertaking
- ◆ Post simulation results : ENC noise, time jitter 10% larger than pre simulation. Output Gain 10% decreased. Power consumption , output width(data rate) and linearity not effected much.
- ◆ Small modification on going before integrated with back-end



THANK YOU!