

Front-End electronics optimization for time tagging with Ultra-Fast Silicon Detectors

Workshop on pico-second timing detectors for high energy physics and applications

Turin,
May 16th 2018

Federico Fausti
On behalf of the **UFSD** collaboration



Outline

❖ Introduction

- Ultra-Fast Silicon Sensors
- Front-end electronics for timing applications

❖ Preamplifier choice

❖ Fast TIAs for UFSD coupling


❖ The TOFFEE example

- Limits
- Possible improvements

❖ FE optimization approach


❖ Summary

Introduction: Ultra-Fast Silicon Sensors

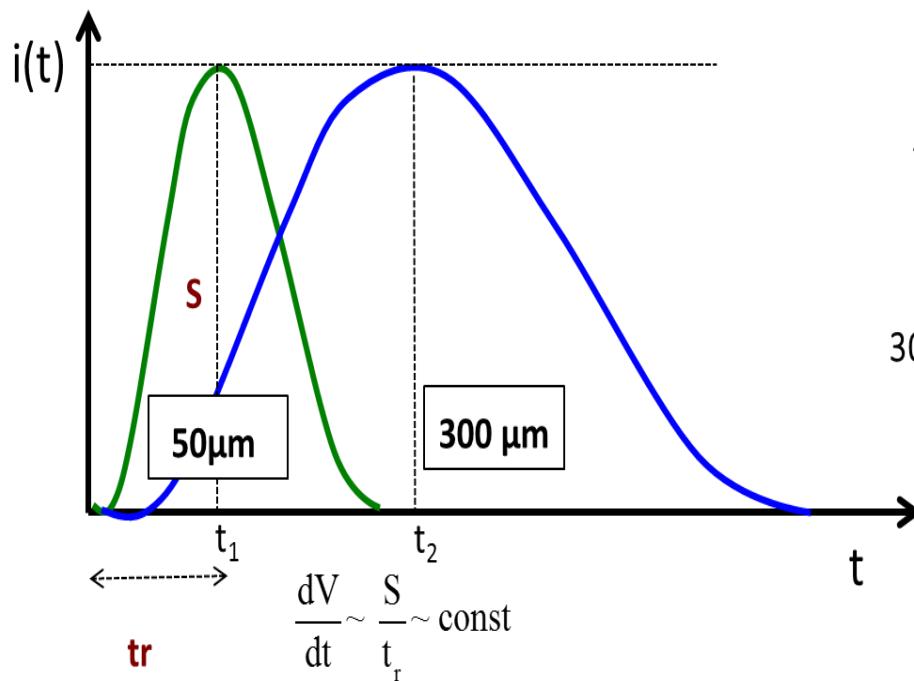


The maximum value depends
only on the gain value

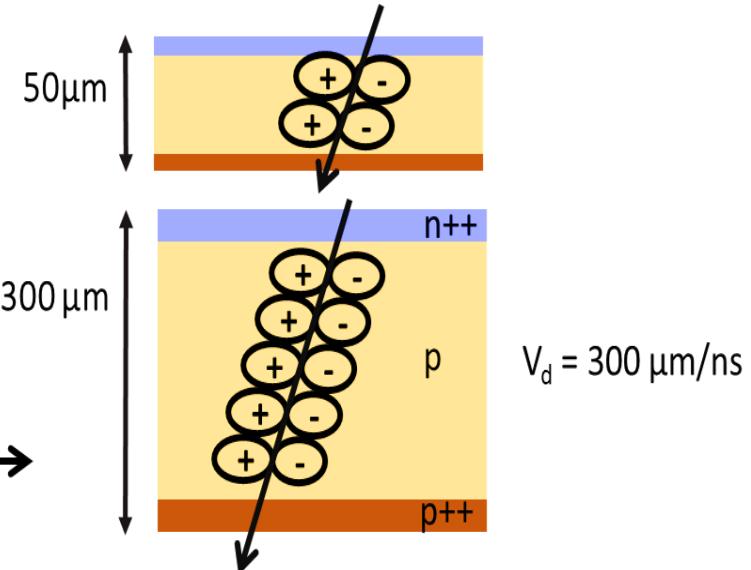The rise time depends only on
the sensor thickness $\sim 1/d$




Thick detectors have longer signals, not higher signals

$$\frac{dV}{dt} \propto \frac{G}{d}$$

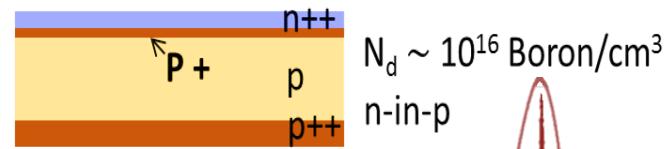


Introduction: Ultra-Fast Silicon Sensors

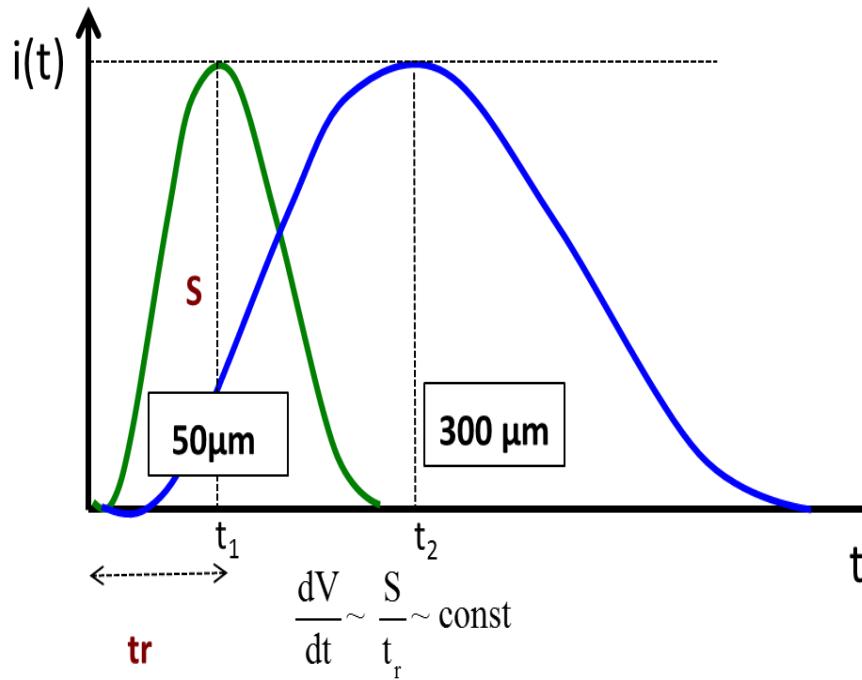


The maximum value depends
only on the gain value

$$\frac{dV}{dt} \propto \frac{G}{d}$$

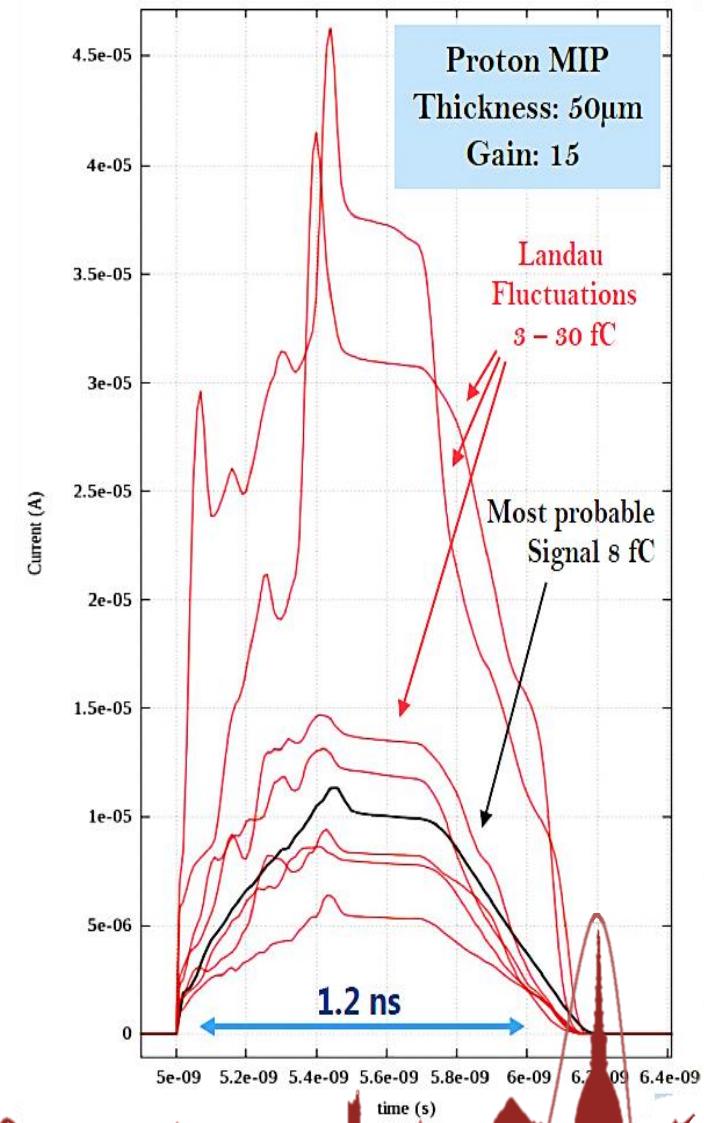The rise time depends only on
the sensor thickness $\sim 1/d$



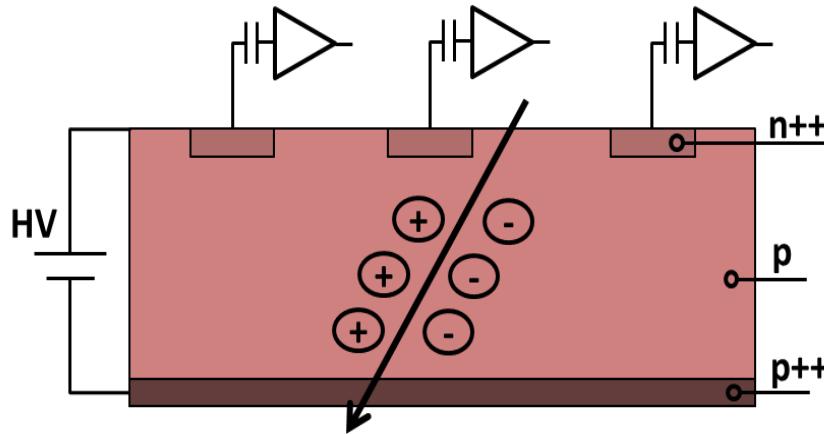
Introduction: Front-end electronics for timing



Intrinsic Landau noise sets a pre-front-end limit:
 $\sigma_{Landau\ Noise} \sim 20\ ps.$

The electronics design goal is then fixed by this number

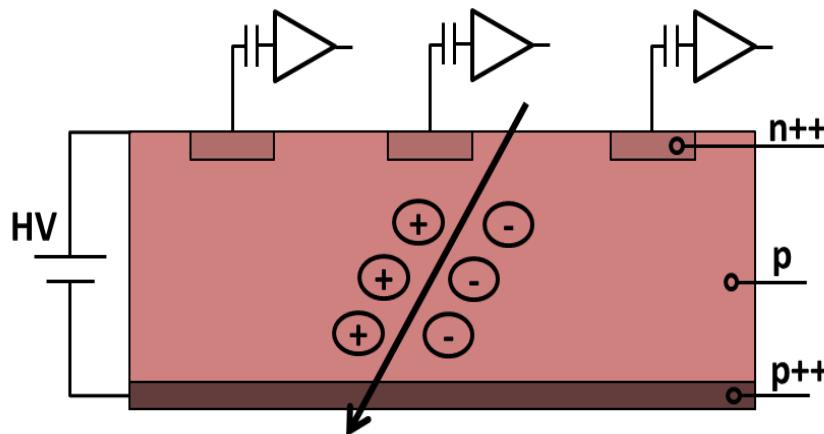
Introduction: Front-end electronics for timing




Intrinsic Landau noise sets a pre-front-end limit:
 $\sigma_{Landau\ Noise} \sim 20\ ps.$

$$\sigma_t^2 = \left(\frac{t_{rise}}{S/N} \right)^2 + \left(\left[\frac{t_{rise} V_{th}}{S} \right]_{RMS} \right)^2 + \left(\frac{TDC_{bin}}{\sqrt{12}} \right)^2$$

jitter time walk TDC

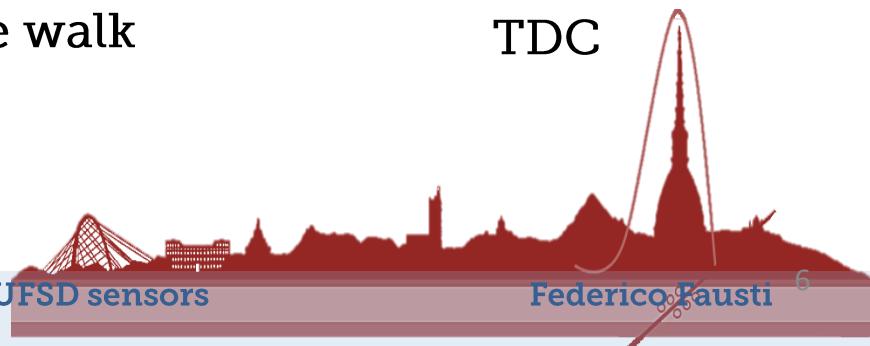

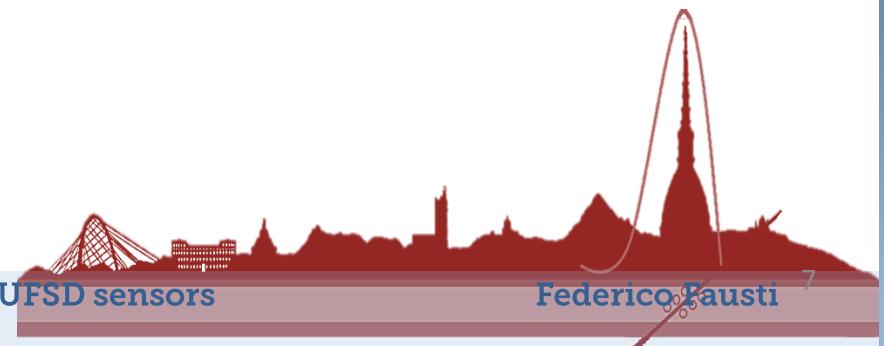Introduction: Front-end electronics for timing




Introduction: Front-end electronics for timing

$$\left(\frac{t_{rise}}{S/N} \right)^2$$


jitter
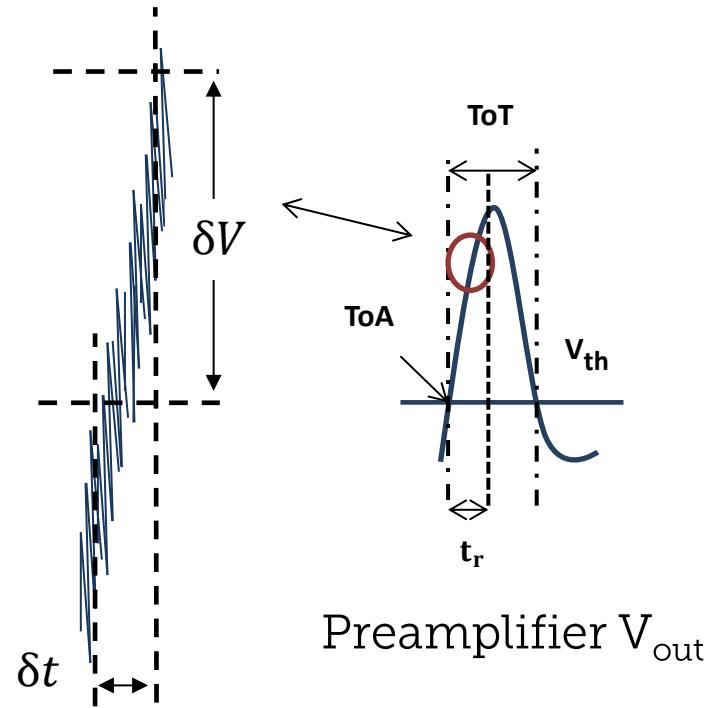
$$\sigma_t^j = \frac{N}{dV/dt} = \frac{t_r}{S/N}$$



Preamplifier V_{out}

Fast TIA for UFSD coupling

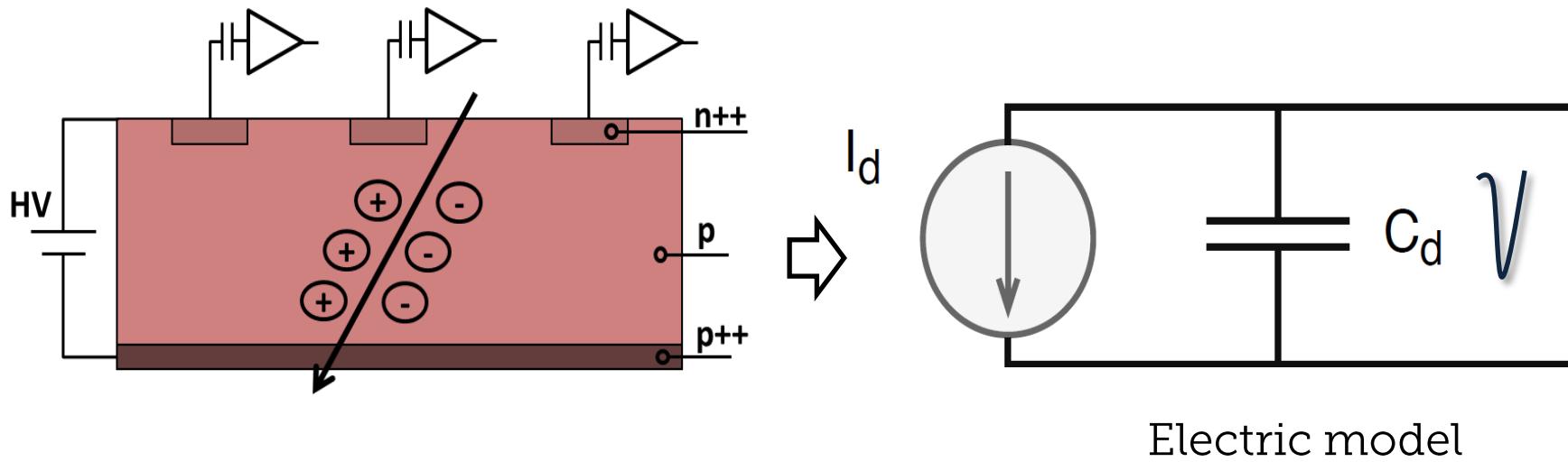


Fast TIA for UFSD coupling

Input	Output	Gain	Type
v_i	v_o	$A_v = v_o/v_i$	Voltage
i_i	i_o	$A_i = i_o/i_i$	Current
v_i	i_o	$A_g = i_o/v_i$	Transconductance
i_i	v_o	$A_r = v_i/i_o$	Transimpedance


Fast TIA for UFSD coupling

Input	Output	Gain	Type
v_i	v_o	$A_v = v_o/v_i$	Voltage
i_i	i_o	$A_i = i_o/i_i$	Current
v_i	i_o	$A_g = i_o/v_i$	Transconductance
i_i	v_o	$A_r = v_i/i_o$	Transimpedance

Fast TIA for UFSD coupling

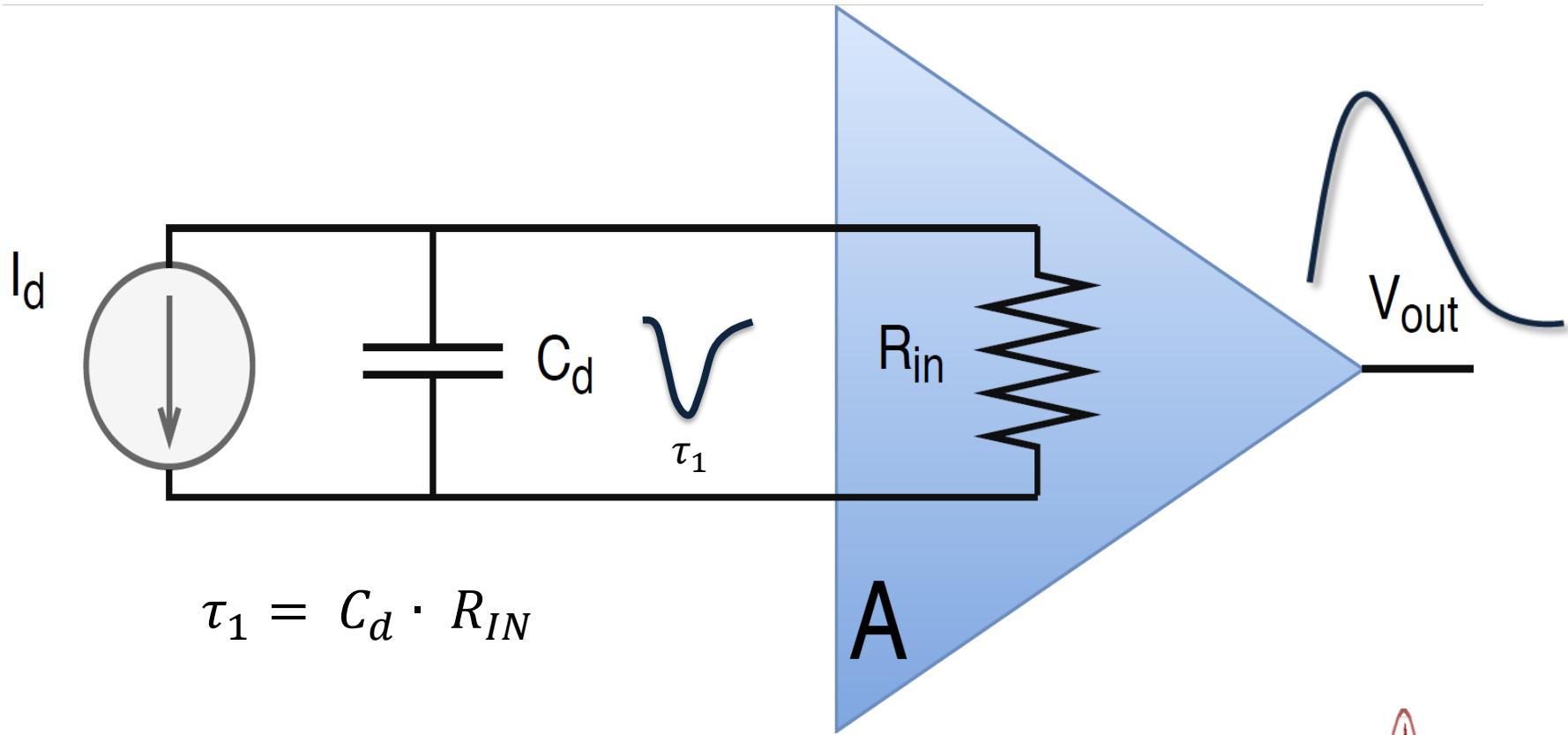


Fast TIA for UFSD coupling

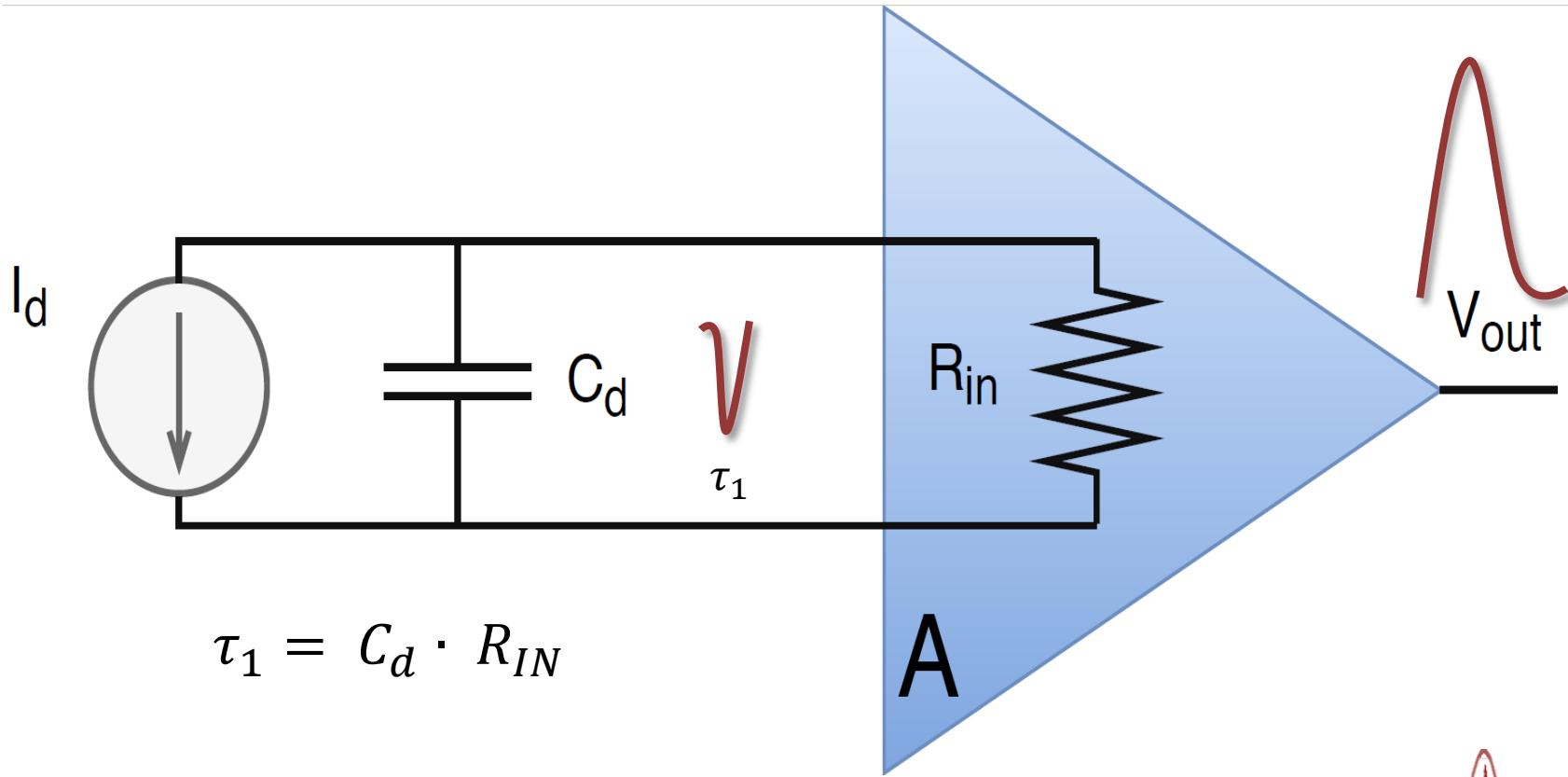


Fast TIA for UFSD coupling

Capacitive feedback Resistive feedback Broad-Band Regulated Common Gate


CSA

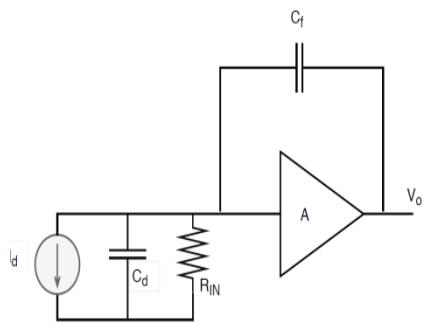


R_f -TIA

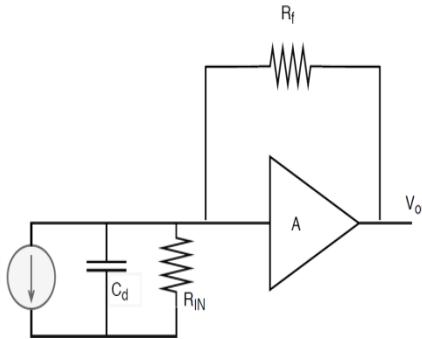

BB

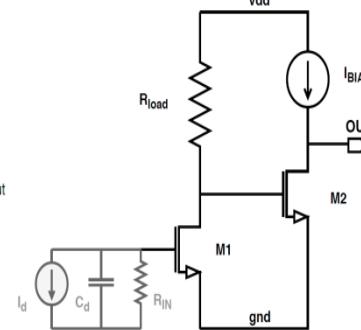

RCG

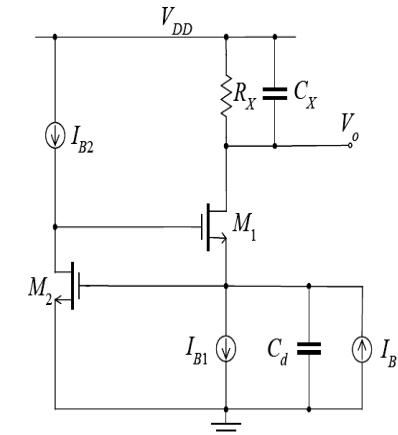

$$V_{out} = -1/C_f \int i(t)dt$$

$$V_{out} = -R_f i(t)$$

$$V_{out} = -(Z_{IN} i(t)) g_{m1} R_{load}$$

$$V_{out}(t) = \frac{Q_{in}}{C_f} \frac{\tau_1}{\tau_1 - \tau_2} \left(e^{-\frac{t}{\tau_1}} - e^{-\frac{t}{\tau_2}} \right)$$


 = Charge sensitive

 = Current sensitive

$$\tau_1 = \frac{C_d}{g_{m1} A} \quad \tau_2 = R_X C_X$$


Fast TIA for UFSD coupling

Current signal in a 50 μm sensor

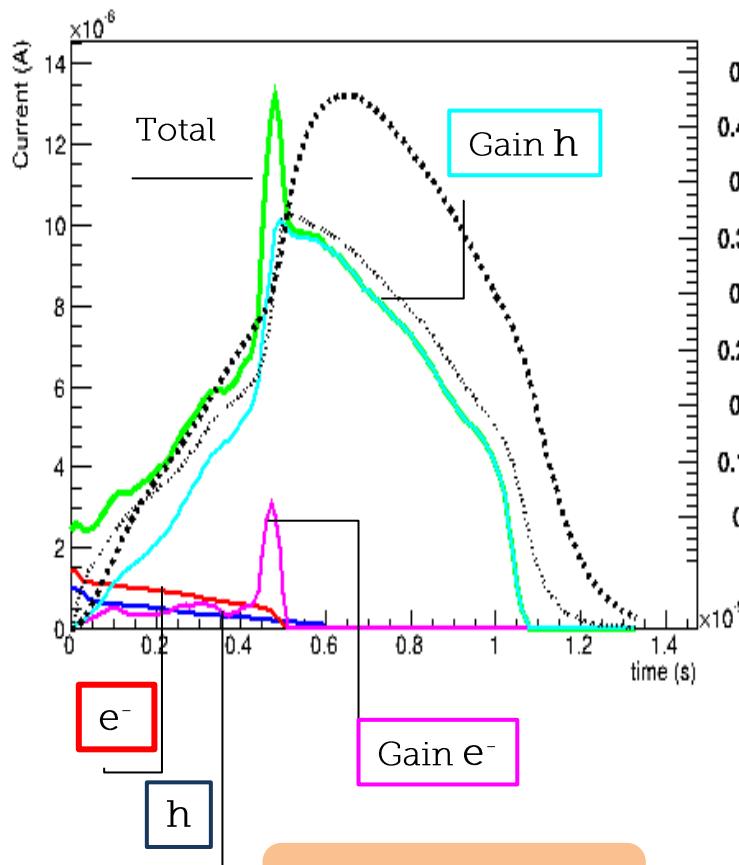

N. Cartiglia's talk

Front-end amplifier response

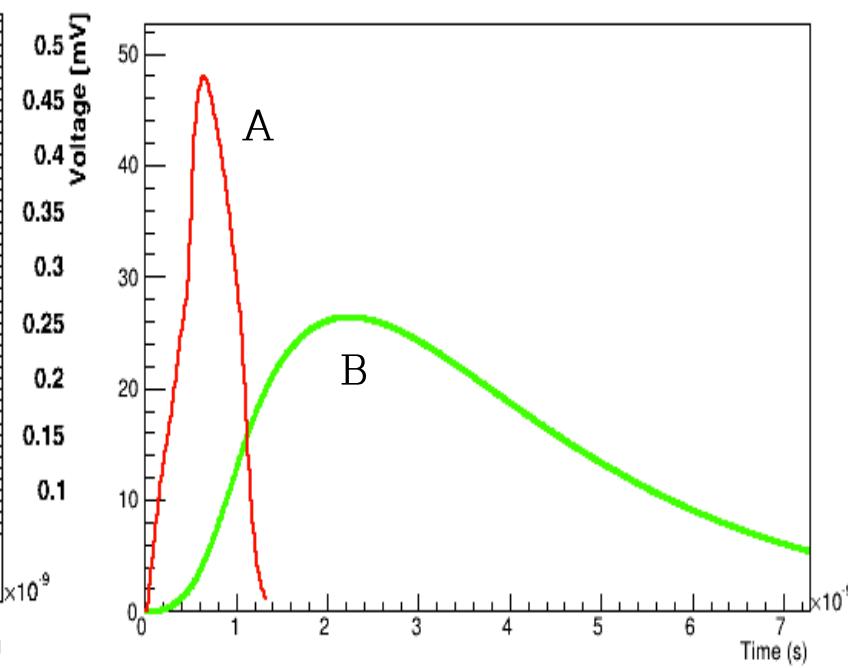


Current sensitive (A) → BB

Charge sensitive (B) → CSA

Fast TIA for UFSD coupling

Front-end amplifier response

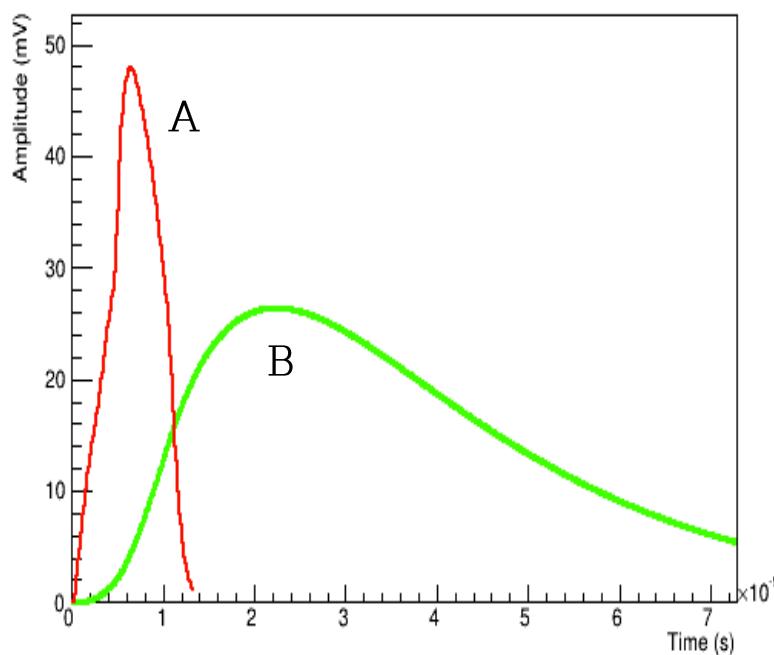

Current sensitive (A) → BB

Charge sensitive (B) → CSA


CSA

- $V_{out}/I_{in} = -1/j\omega C_f$
- Fine integration : $V_{out} = -Q/C_f$
- Lowest noise configuration
- Need R_f to discharge C_f



BB

- $V_{out}/I_{in} = -R_f$
- V_{out} profile follows I_{in}
- Sensitive to Landau bumps
- Need C_f for stability



The TOFFEE Example

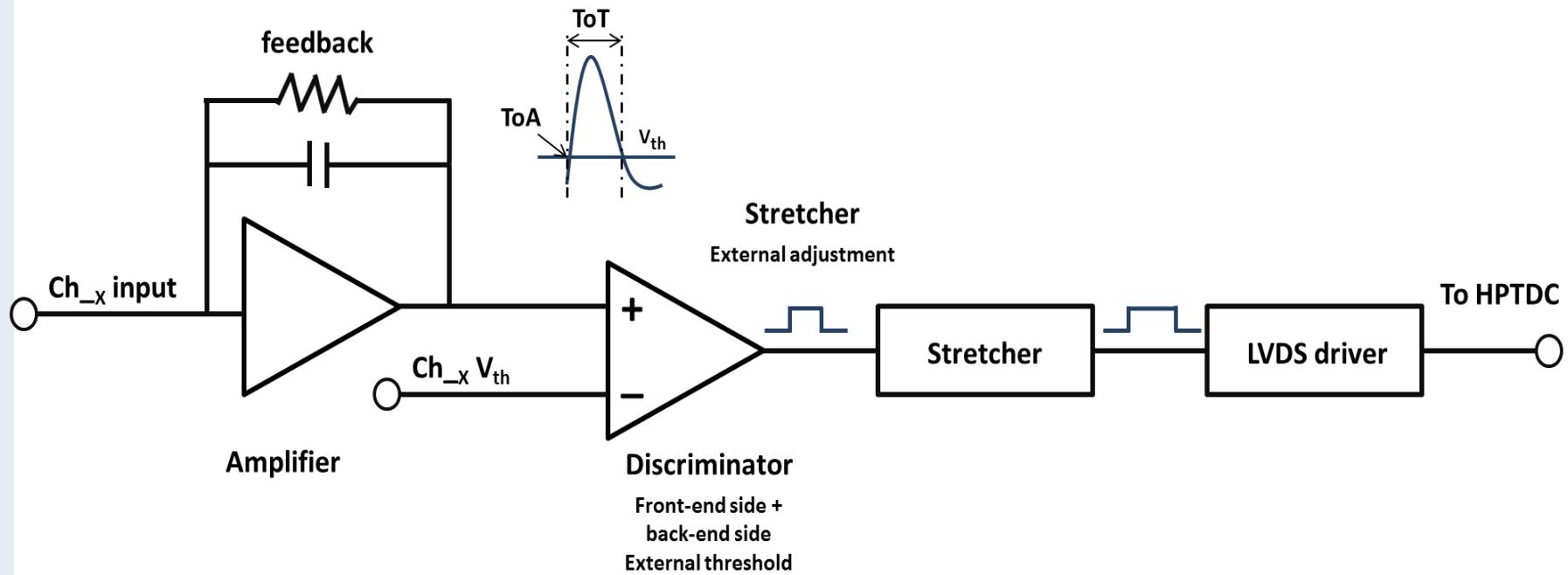

The TOFFEE Example

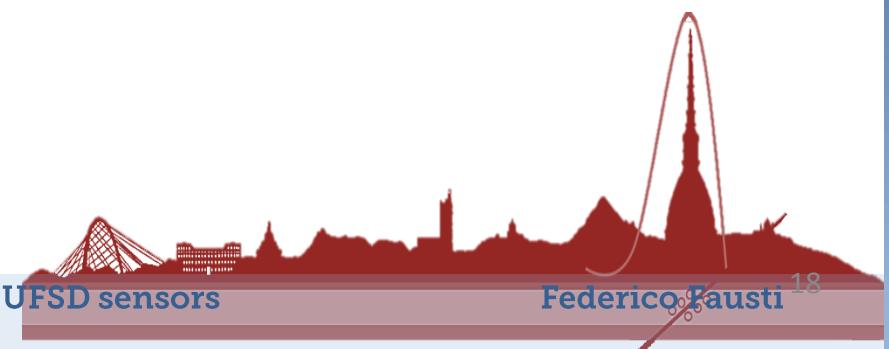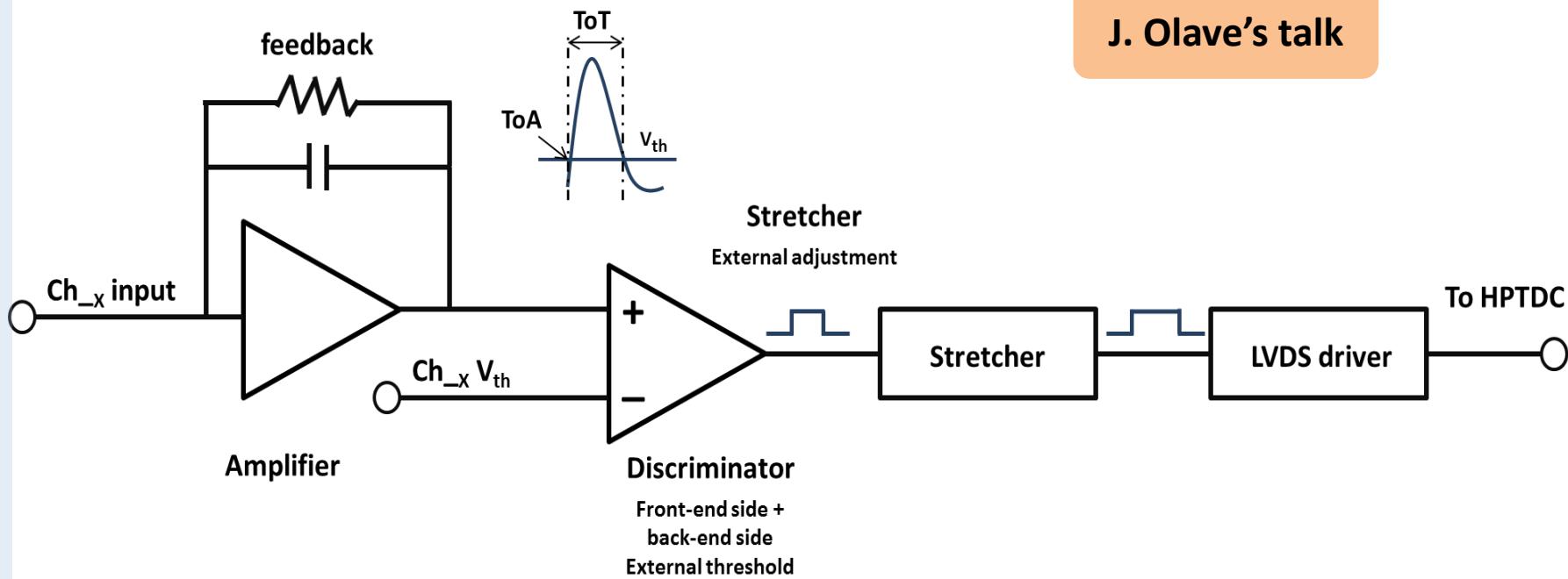

The TOFFEE Example: simulation outcomes

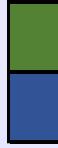 	BLOCK	JITTER [ps]			
CURRENT [mA]		2		12	
CHARGE [fC]		3	8	3	8
	Preamp	120	46	104	40
	Discriminator 1	132	47	106	39
	Discriminator 2	131	47	110	40
	Delay line	131	47	111	40
	LVDS	131	47	111	40
	Preamp	42	16	42	11
	Discriminator 1	52	17	53	12
	Discriminator 2	46	16	43	12
	Delay line	47	15	43	12
	LVDS	47	16	43	13

The TOFFEE Example: simulation outcomes

	BLOCK	JITTER [ps]			
CURRENT [mA]		2		12	
CHARGE [fC]		3	8	3	8
LAYOUT	Preamp	120	46	104	40
	Discriminator 1	132	47	106	39
	Discriminator 2	131	47	110	40
	Delay line	131	47	111	40
	LVDS	131	47	111	40
SCHEMATIC	Preamp	42	16	42	11
	Discriminator 1	52	17	53	12
	Discriminator 2	46	16	43	12
	Delay line	47	15	43	12
	LVDS	47	16	43	13

Front-end electronics optimization

Looking for a low-power, 20 ps Jitter VFE:

- Parasitics control → layout techniques

Front-end electronics optimization

Looking for a low-power, 20 ps Jitter VFE:

- Parasitics control → layout techniques
- Light architectures → minimum number of MOSFETs

Front-end electronics optimization

Looking for a low-power, 20 ps Jitter VFE:

- Parasitics control → layout techniques
- Light architectures → minimum number of MOSFETs
- Low power → small MOSFETs → less parasitics → faster transients

$$\text{Area} \propto I_{bias}$$

Front-end electronics optimization


Looking for a low-power, 20 ps Jitter VFE:

- Parasitics control → layout techniques
- Light architectures → minimum number of MOSFETs
- Low power → small MOSFETs → less parasitics → faster transients
- S/N optimization → larger g_m

Front-end electronics optimization

- S/N optimization → larger g_m

Example: the Broad-Band

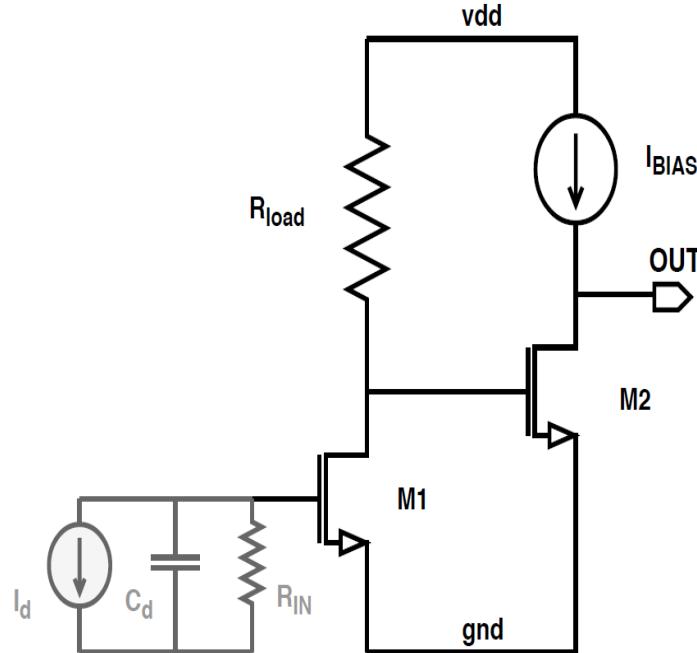

$$V_{out} = -(Z_{IN} i(t)) g_{m1} R_{load}$$


$$\sigma_t^J = \frac{t_r}{V_{out}/N}$$

$$\sigma_t^J = \frac{C_d}{Q_{in}} \sqrt{\frac{2KT}{g_{m1}}} t_d$$

Front-end electronics optimization

- S/N optimization → larger g_m

Example: the Broad-Band

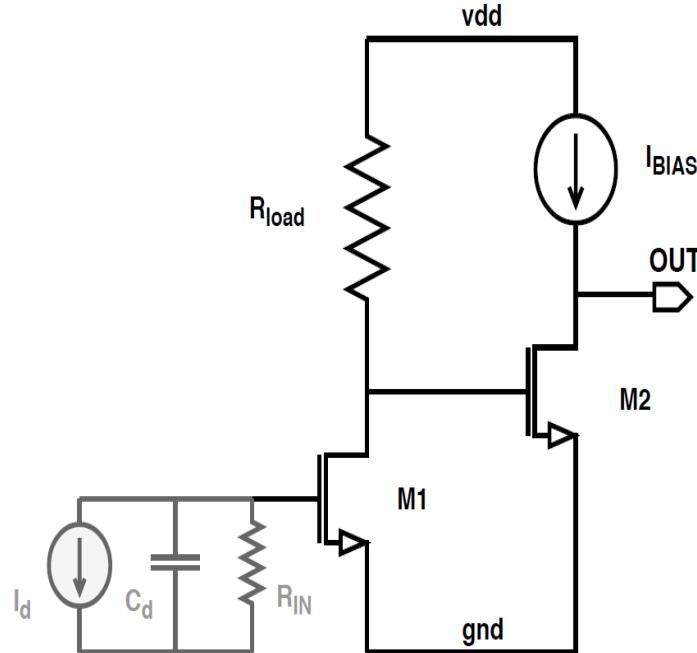

$$V_{out} = -(Z_{IN} i(t)) g_{m1} R_{load}$$

$$\sigma_t^J = \frac{t_r}{V_{out}/N}$$

$$\sigma_t^J = \frac{C_d}{Q_{in}} \sqrt{\frac{2KT}{g_{m1}}} t_d$$

Front-end electronics optimization

Looking for a low-power, 20 ps Jitter VFE:

- Parasitics control → layout techniques
- Light architectures → minimum number of MOSFETs
- Low power → small MOSFETs → less parasitics → faster transients
- S/N optimization → larger g_m
- Different technology nodes comparison → g_m scaling effect

Front-end electronics optimization



Looking for a low-power, 20 ps Jitter VFE:

- Parasitics control → layout techniques
- Light architectures → minimum number of MOSFETs
- Low power → small MOSFETs → less parasitics → faster transients
- S/N optimization → larger g_m
- Different technology nodes comparison → g_m scaling effect

- 350 nm
- 110 nm
- 65 nm
- 28 nm

Front-end electronics optimization

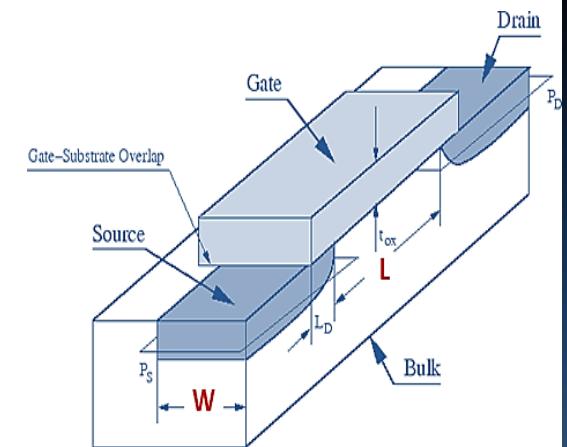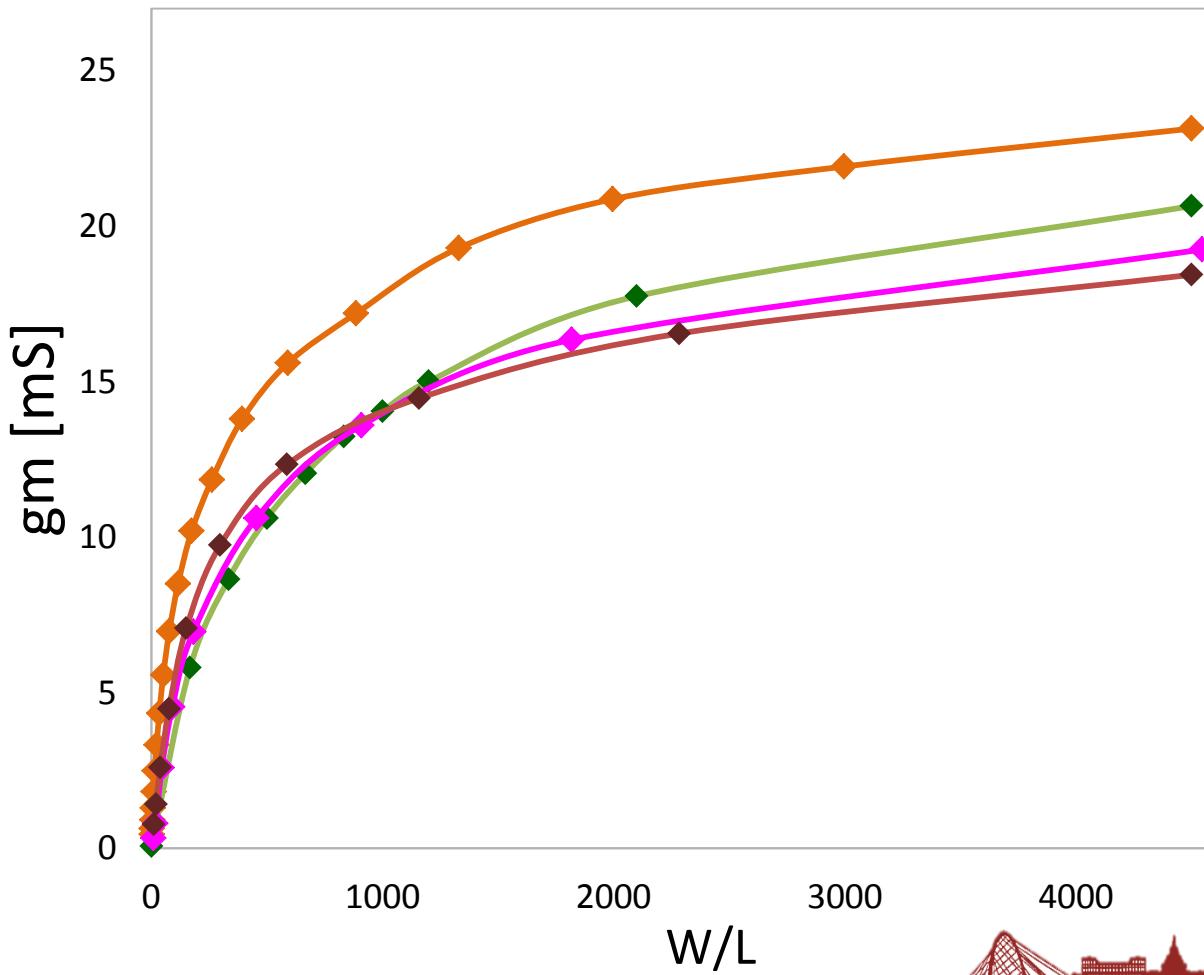NMOS scaling effect: g_m vs $\frac{W}{L}$



— 110nm

— 350nm



— 28nm

— 65nm

$$gm = \frac{\partial V_{GS}}{\partial I_{DS}} |V_{DS} = \text{const}$$

Front-end electronics optimization

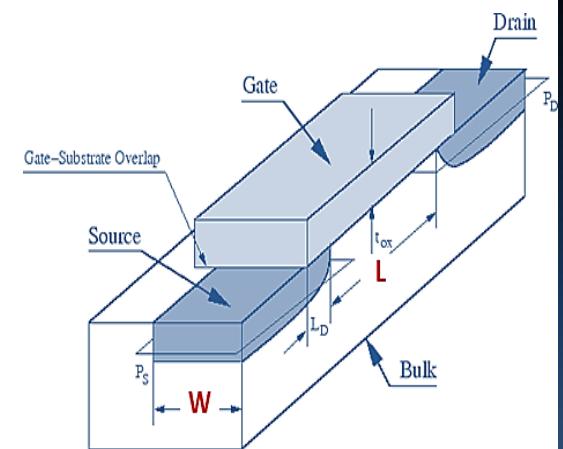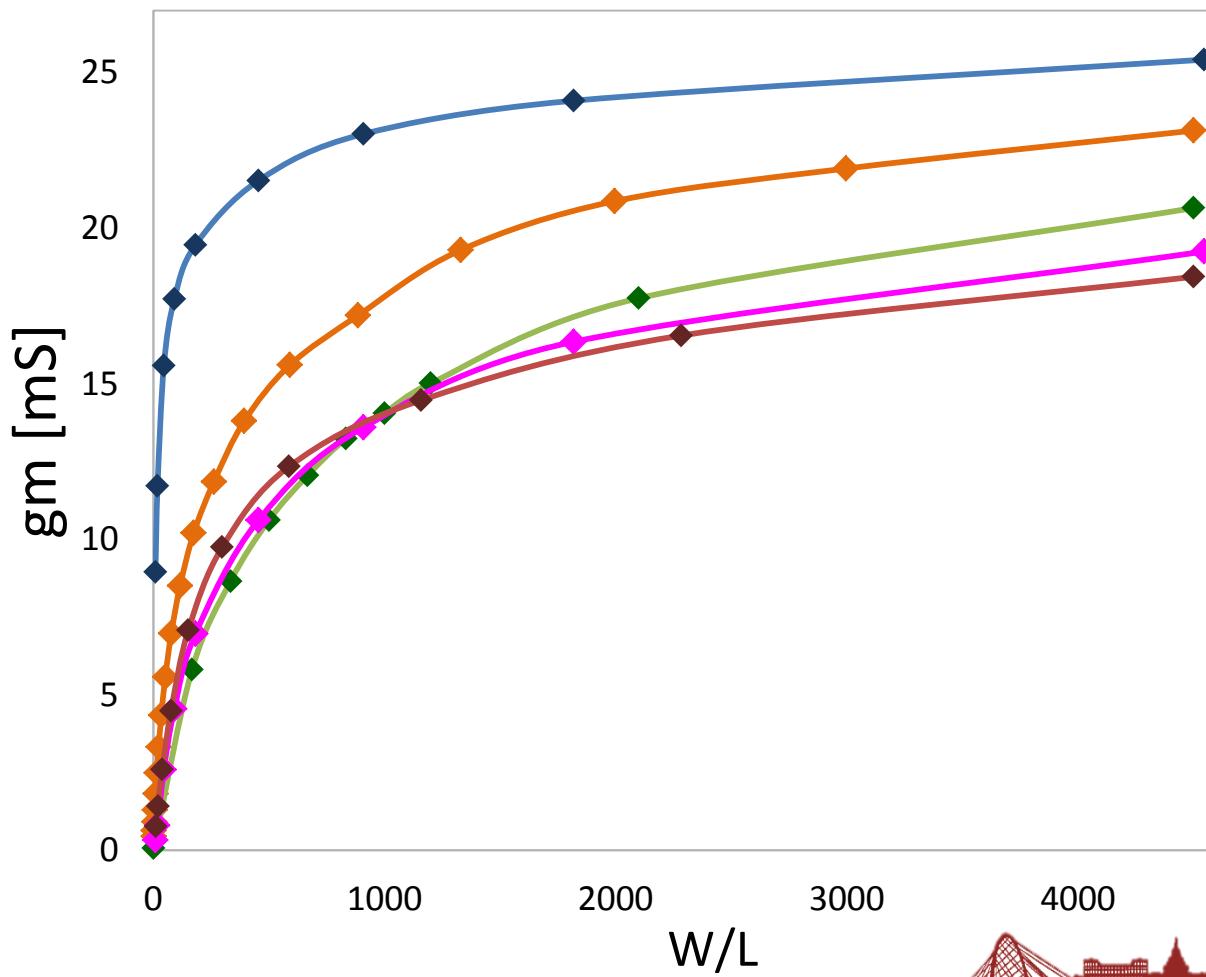NMOS scaling effect: g_m vs $\frac{W}{L}$



110nm_RF

110nm $gm = \frac{\partial V_{GS}}{\partial I_{DS}} |V_{DS} = const$

350nm

28nm

65nm



Front-end electronics optimization

Looking for a low-power, 20 ps Jitter VFE:

- Parasitics control → layout techniques
- Light architectures → minimum number of MOSFETs
- Low power → small MOSFETs → less parasitics → faster transients
- S/N optimization → larger gm
- Different technology nodes comparison → g_m scaling effect
- MOSFETs characterization for timing (RVT, LVT, HVT, RF...)

Front-end electronics optimization

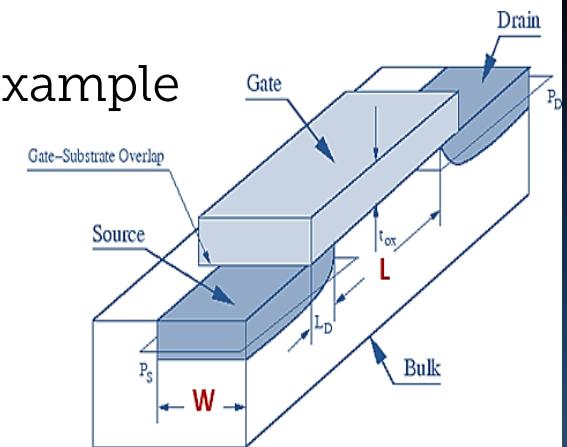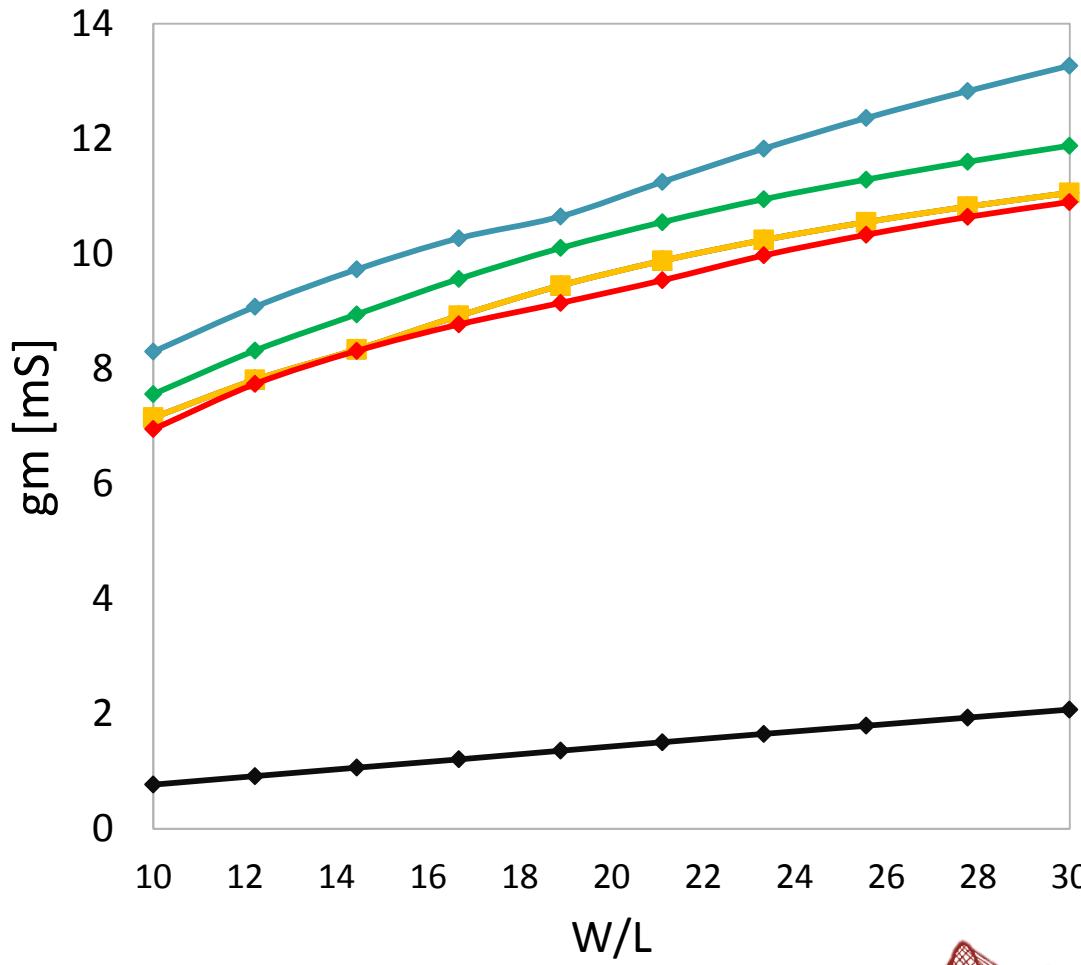MOSFETs characterization for timing: the 65 nm example



standard

RF

RF_a

RF_b

RF_25

RF_HVth

RF_LVth

$$gm = \frac{\partial V_{GS}}{\partial I_{DS}} |V_{DS} = \text{const}$$

Front-end electronics optimization


Looking for a low-power, 20 ps Jitter VFE:

- Parasitics control → layout techniques
- Light architectures → minimum number of MOSFETs
- Low power → small MOSFETs → less parasitics → faster transients
- S/N optimization → larger g_m
- Different technology nodes comparison → g_m scaling effect
- MOSFETs characterization for timing (RVT, LVT, HVT, RF...)
- Discriminator type → leading edge, CFD, both...

Outlook

VFE design strategy

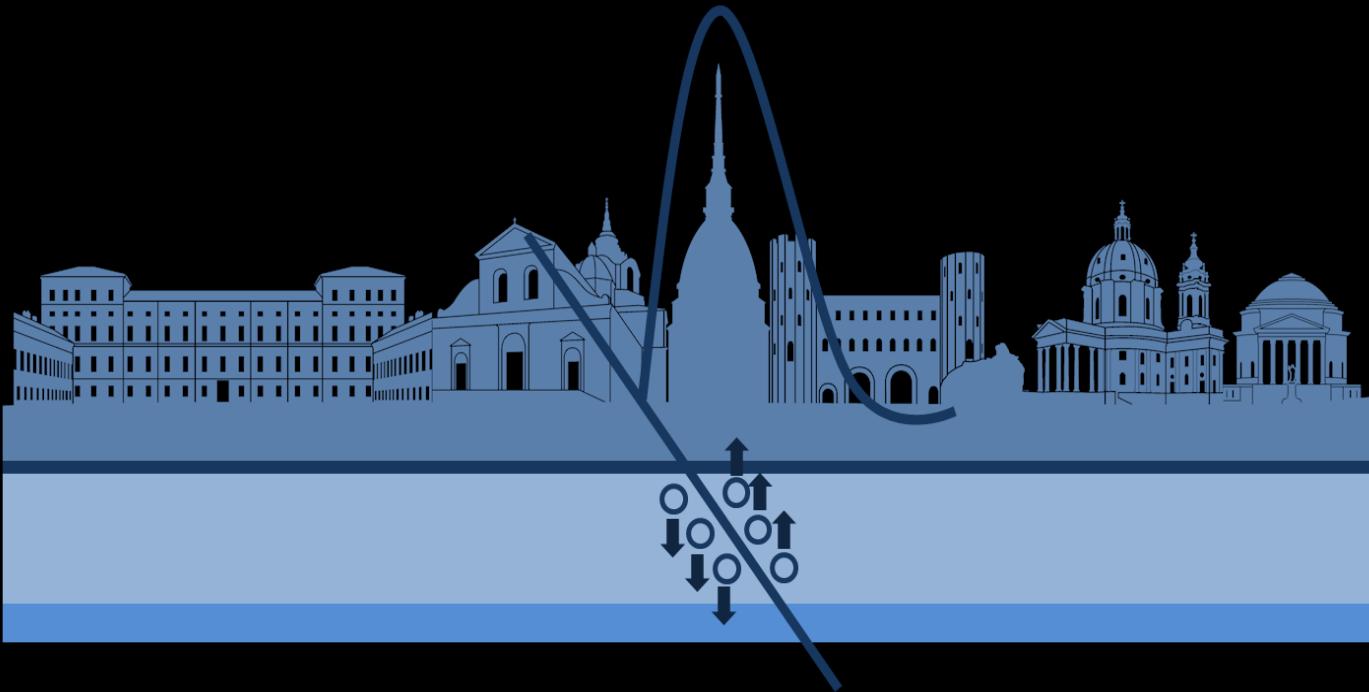- Device level characterization for timing applications
- Technology node choice
- Amplifier choice
- Multiple discriminator possibility
- Prototype development → test on silicon



Thanks for your attention


We kindly acknowledge the following funding agencies:

INFN – GruppoV
Horizon 2020 Grant URC 669529
Ministero degli Affari Esteri, Italy, MAE



Backup

UFSD: Weightfield2 signal profile

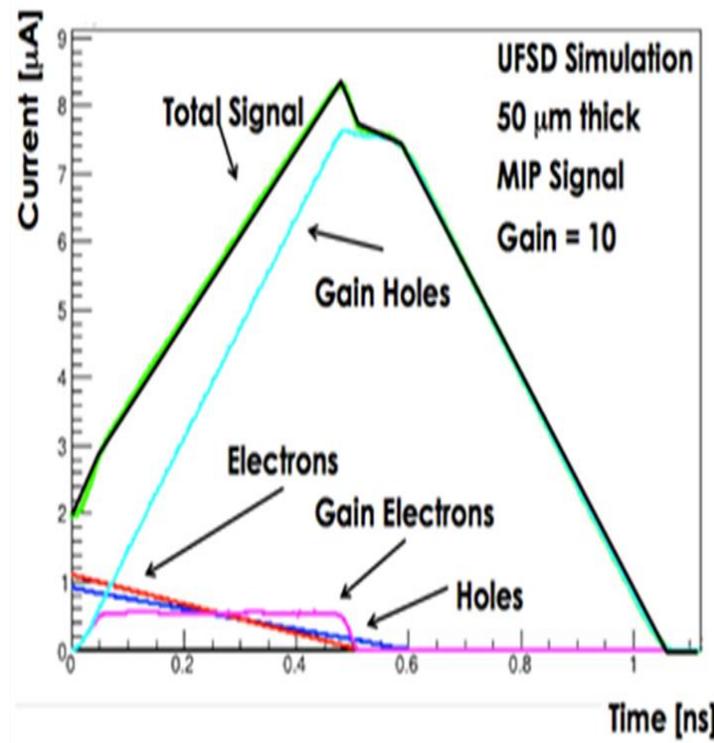

Prototype idea

16 channels VFE ASIC:

- 4 preampl. solutions
- x2 (redundancy)
- + RF MOSFETs

