 




EXCELENCIA
MARIA
DE MAEZTU

Institute of Cosmos
Sciences



SiPM readout circuits for Fast Timing

D. Gascon on behalf ICCUB-TECH
instrumentation section and
CIEMAT and CERN collaborators

*Picosecond Timing
Workshop
18/05/2018*

- I. Introduction**
- II. SiPM model
- III. FE circuits
- IV. ASICs for PET
- V. Avenues to fast timing

I. Introduction

- Many different ASICs
 - Many possible classifications as well !
- According the input impedance
 - Current mode versus voltage mode
- According the complexity / functionality
 - Pure analogue front-end
 - Section III
 - Mixed-mode including digitization and readout
 - Section IV
- According the application
 - Many applications: PET, LIDAR, vision, life-sciences, particle physics, astrophysics, etc
 - Fast timing is a must in many of them, e.g. TOFPET

Outlook

- I. Introduction
- II. SiPM model**
- III. FE circuits
- IV. ASICs for PET
- V. Avenues to fast timing


II. SiPM model

Vacuum Photomultipliers

$$G = 10^5 - 10^7$$

$$C_d \sim 10 \text{ pF}$$

$$L \sim 10 \text{ nH}$$


 


Silicon Photomultipliers

$$G = 10^5 - 10^7$$

$$C = 10 - 400 \text{ pF}$$

$$L = 1 - 10 \text{ nH}$$

  


II. SiPM model

Single cell model $\rightarrow (R_d || C_d) + (R_q || C_q)$

SiPM + load $\rightarrow (|| Z_{cell}) || C_{grid} + Z_{load}$


Signal = **slow** pulse (τ_d (rise), τ_{q-slow} (fall)) + **fast** pulse (τ_d (rise), τ_{q-fast} (fall))

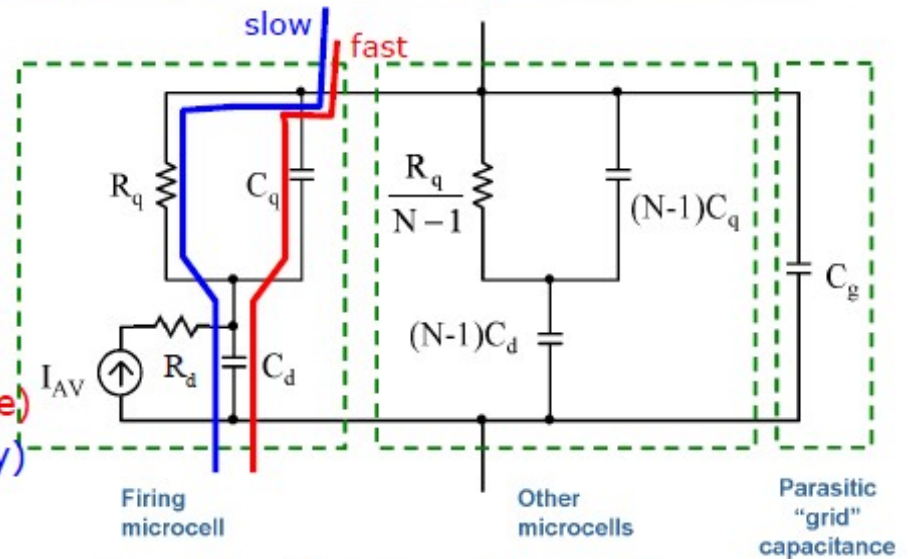- τ_d (rise) $\sim R_d (C_q + C_d)$
- τ_{q-fast} (fall) = $R_{load} C_{tot}$ (fast; parasitic spike)
- τ_{q-slow} (fall) = $R_q (C_q + C_d)$ (slow; cell recovery)



Pulse shape
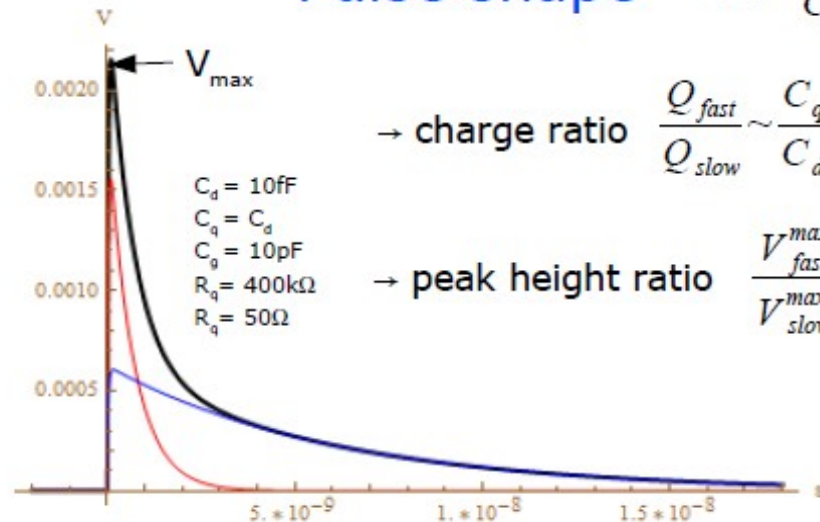
$$V(t) \approx \frac{Q}{C_q + C_d} \left(\frac{C_q}{C_{tot}} e^{\frac{-t}{\tau_{FAST}}} + \frac{R_{load}}{R_q} \frac{C_d}{C_q + C_d} e^{\frac{-t}{\tau_{SLOW}}} \right)$$



→ charge ratio $\frac{Q_{fast}}{Q_{slow}} \sim \frac{C_q}{C_d}$

→ peak height ratio $\frac{V_{fast}^{max}}{V_{slow}^{max}} \sim \frac{C_q^2 R_q}{C_d C_{tot} R_{load}}$

1) Peak V/I signal goes with C^{-1}

2) Peak I signal goes with R^{-1}


increasing with R_q and $1/R_{load}$
(and C_q of course)

Increasing C_q/C_d or/and R_q/R_{load}
→ spike enhancement
→ better timing

3) Fast vs slow component

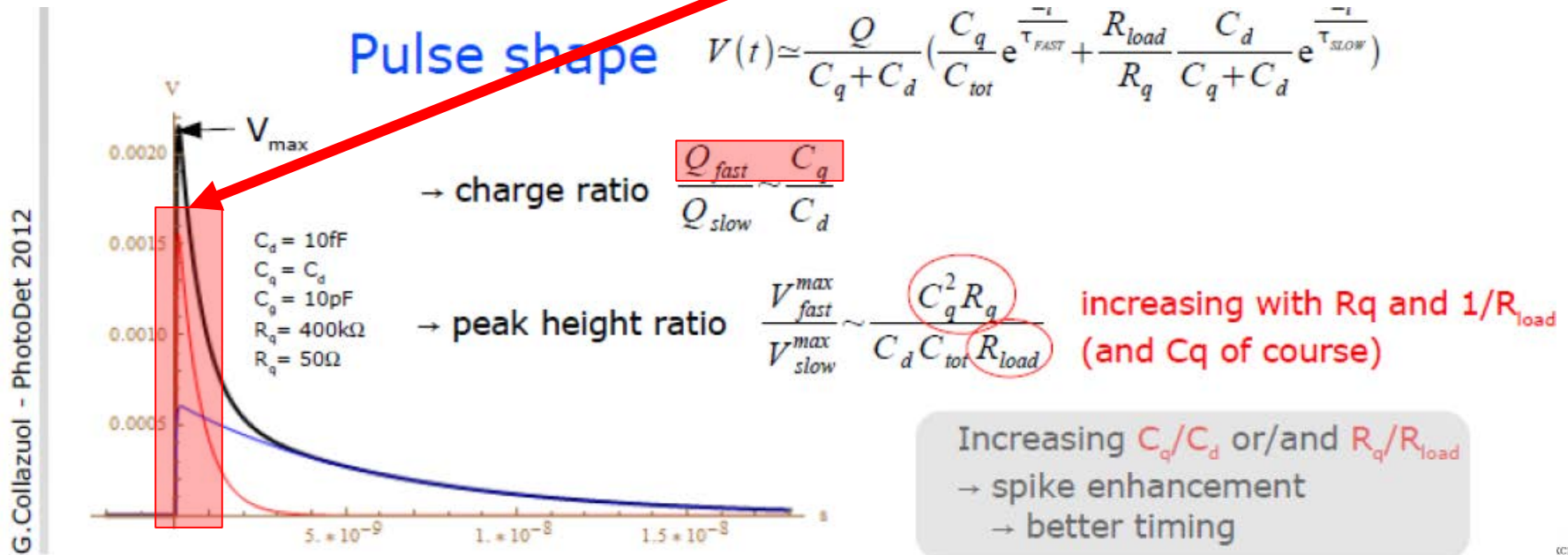II. SiPM model


- Front end electronics for SiPM is needed to:
 - Preamplify for SNR optimization
 - Even if “nominal” gain is in the order of 10^6 only a fraction of the charge is used for fast read-out systems
 - The “effective” gain for a fast system can be between 2 and 10 times lower than the nominal gain



- I. Introduction
- II. SiPM model
- III. FE circuits**
- IV. ASICs for PET
- V. Avenues to fast timing

 III. FE circuits: Pole-Zero cancellation


- Pole-Zero (PZ) cancellation of the SiPM recovery long time constant (τ_{slow})
- The PZ shaping has an effect in the signal to noise ratio (SNR)
 - A $\text{SNR} > 5$ is required for photopeak identification
 - Can be seen in 2 different ways:
 - 1) Attenuation of slow frequency components of the signal
 - 2) Increase of the input referred noise ($\text{ENC} = \text{Equivalent Noise Charge}$)



Simulation with a
model obtained from
3x3 mm device

II FE ASICs: effect of capacitance and shaping in noise

 
- Front end electronics for SiPM is needed to:
 - Low noise front end is required for large SiPMs
- SiPM capacitances range from 10s pF to more than several nF**



III. FE circuits: current versus voltage mode

- Typical photo-sensor front end circuit configurations:

Charge preamplifier

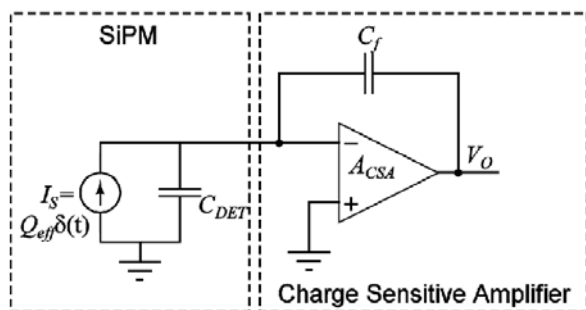

Voltage preamplifier

Current preamplifier

- ☐ Best noise performance
- ☐ Best with short signals
 - Long tails: pile-up!
 - Need to discharge C_f
- ☐ Best with small capacitance
 - $BW = C_f / C_{det} * GBW$, with $C_f \ll C_{det}$ typically...



- ☐ E.g. common-emitter/source configuration
- ☐ Large Z_{in} // Large Z_{out}
- ☐ Current conversion with R_{in}
- ☐ High power budget for high speed systems
- ☐ But can exploit RF technologies

- ☐ E.g. (super) common-base/gate
- ☐ Low Z_{in} // Large Z_{out}
- ☐ Current conversion with R_{in}
- ☐ Potential stability issues
- ☐ Best for high rate applications
- ☐ Good power/BW trade-off⁰

F. Ciciriello et al., "Time performance of voltage-mode vs current-mode readouts for SiPM's," */WASI/*, 2015

 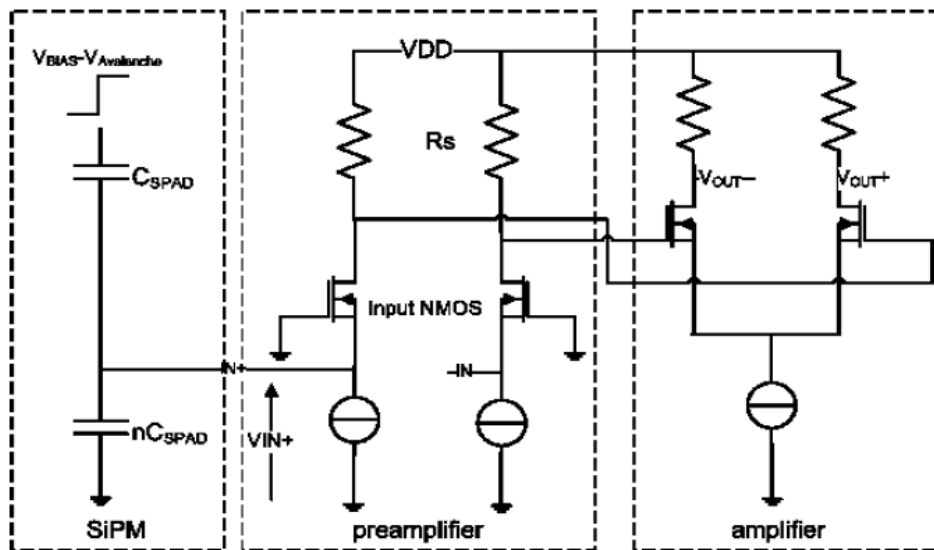III. FE circuits: NINO

- NINO: current mode, binary and quite generic
- Chip designed by CERN group for ALICE TOF RPCs but quite used for SiPM read-out
 - 8 channels amplifier and discriminator
 - Common grid current conveyor, high speed differential discriminator
 - High speed time measurement (10 ps),
 - $P_d = 25 \text{ mW/ch}$, Manufactured in IBM 0.25 μm



F. Anghinolfi, P. Jarron et al. NINO, NIM A, 2004, Vol. 533 page 183-187

III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Active summation to build large area detectors
- Why active summation?
 - Total noise for active and passive summation can be similar
 - But signal (peak) is much higher !
 - Provided that BW of summation is wide enough

Series noise < 2 nV/sqrt(Hz)
Parallel noise < 20 pA/sqrt(Hz)


7 x SiPM
6x6 mm² each



1 x PMT
18 mm diameter




 * 7x7mm² and some custom larger SiPMs exist




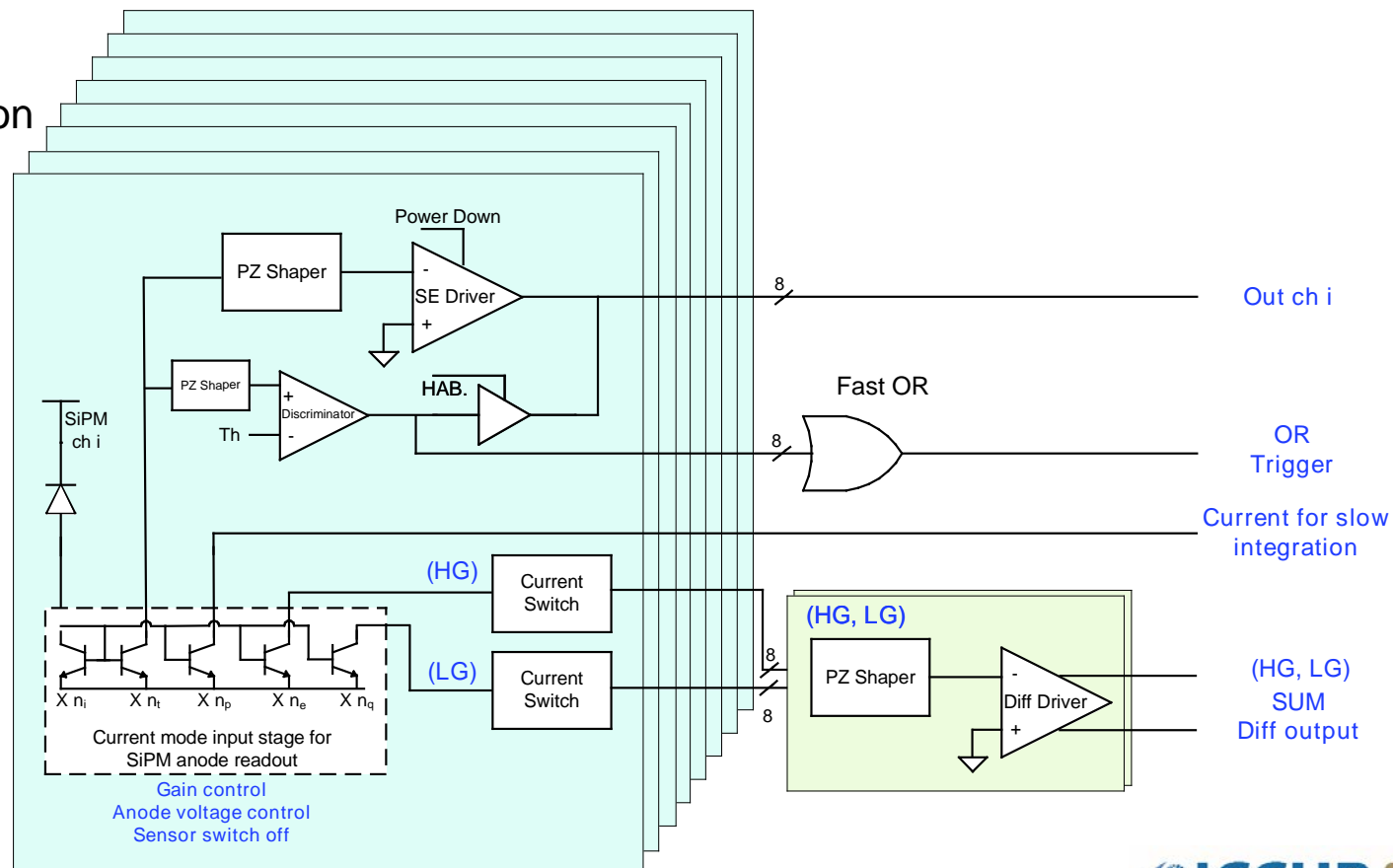III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC: current mode, analog (binary) and designed for astroparticle (CTA) but multipurpose
 - Amplification / impedance adaptation
 - Pole zero cancellation
 - Summation
 - Discrimination



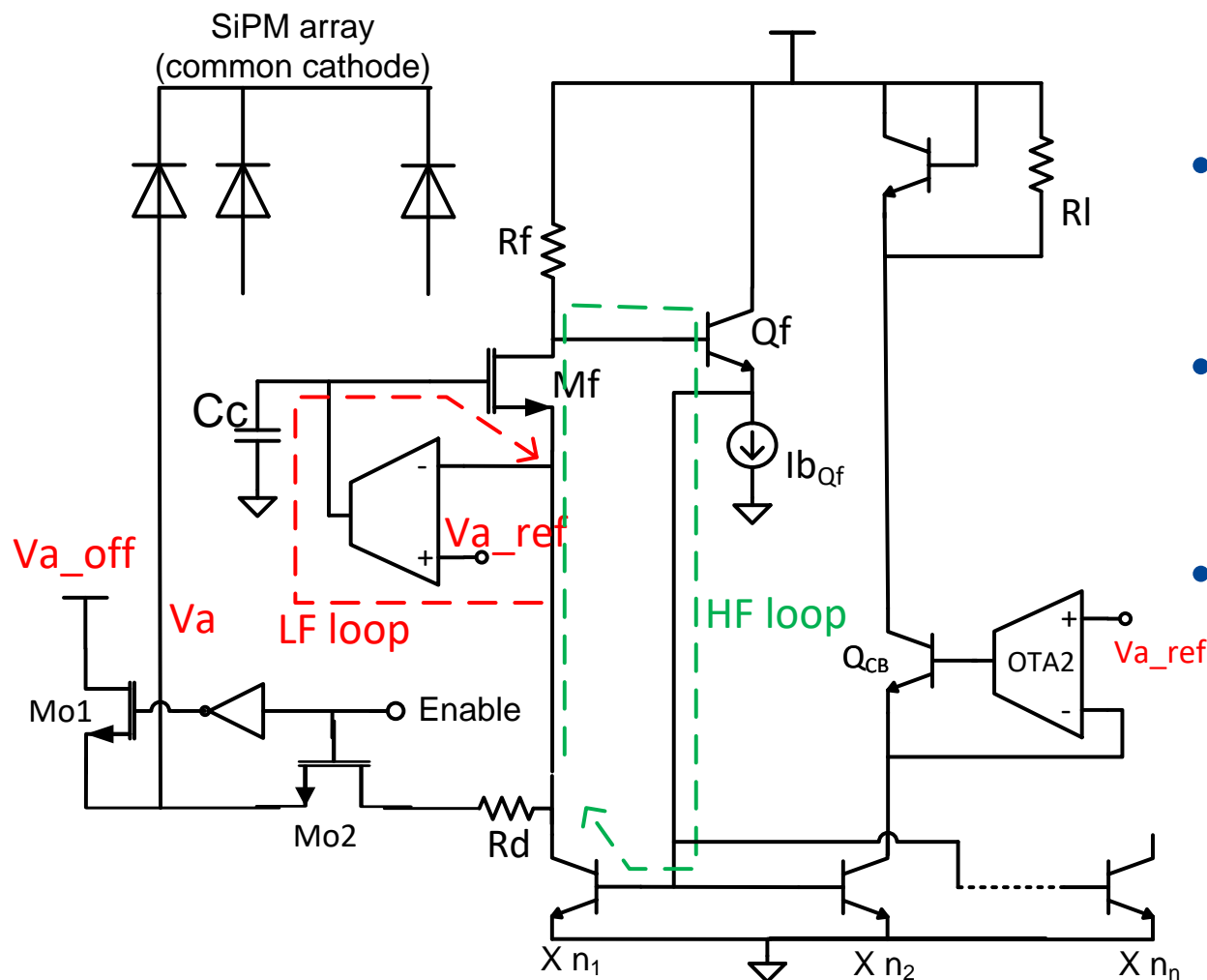III. FE circuits: MUSIC: Multipurpose SiPM RO chip




- Possible to disable each input reducing overvoltage by 4V
- Double feedback loop
 - Low input impedance
 - Anode voltage control
- High bandwidth

Series noise < 2 nV/sqrt(Hz)
Parallel noise < 20 pA/sqrt(Hz)

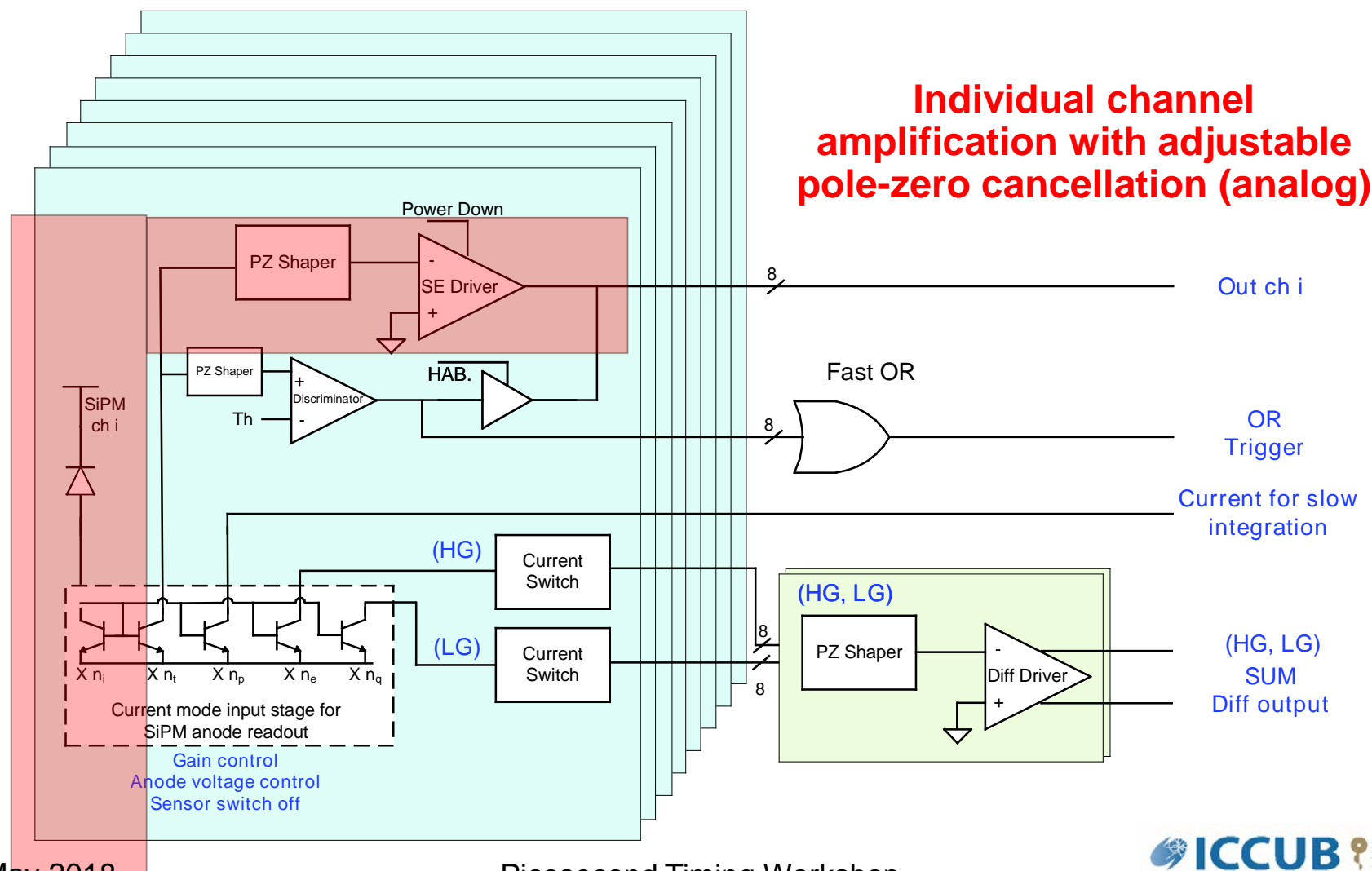
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC 8 ch ASIC integrates all those functionalities




III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Output for a LCT4 MPPC (3x3 mm²)

 

 
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Charge spectrum for a LCT4 MPPC (3x3 mm²)
- Pole-zero cancellation
- Excellent resolution with FWHM of 5 ns




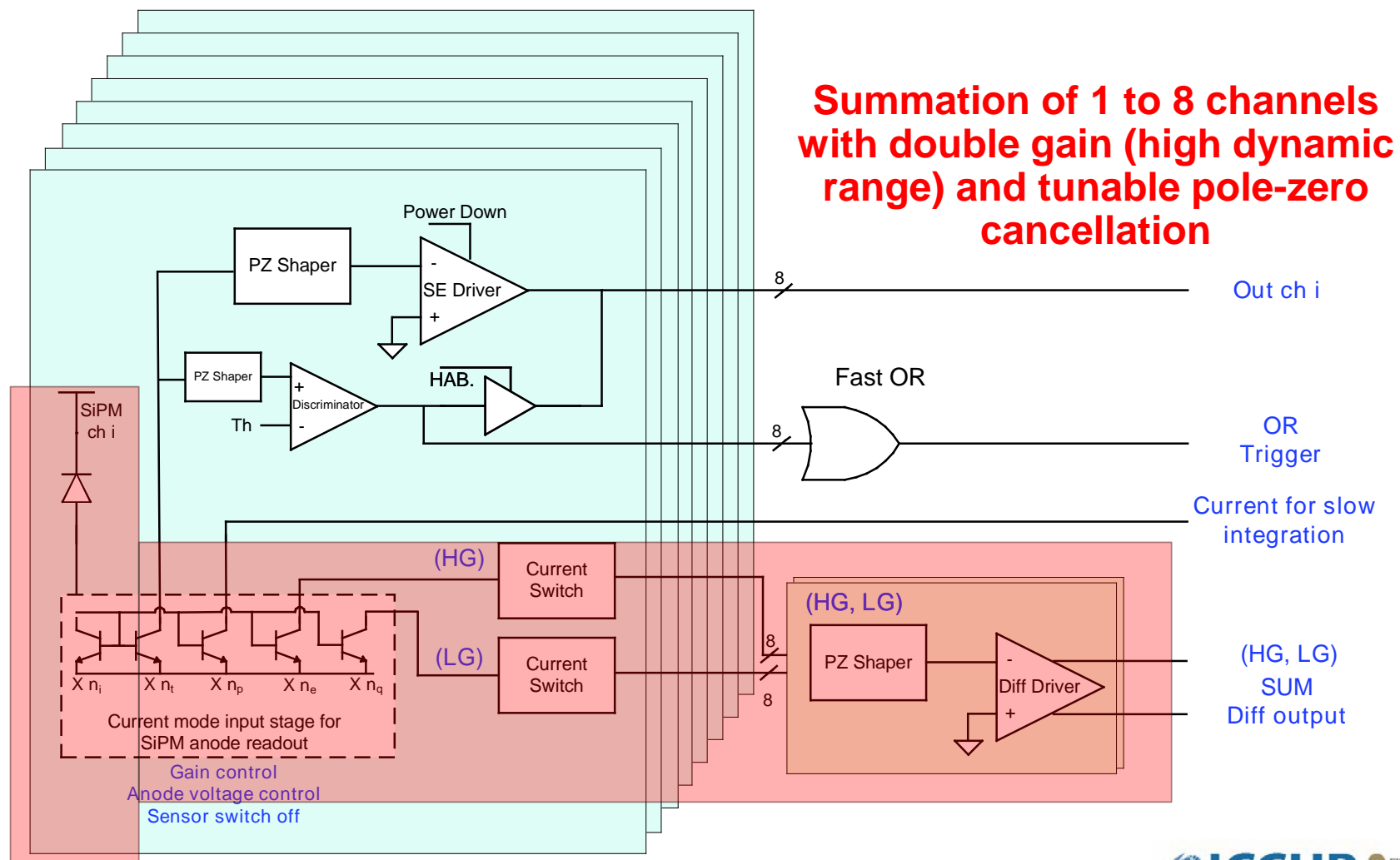
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC 8 ch ASIC integrates all those functionalities



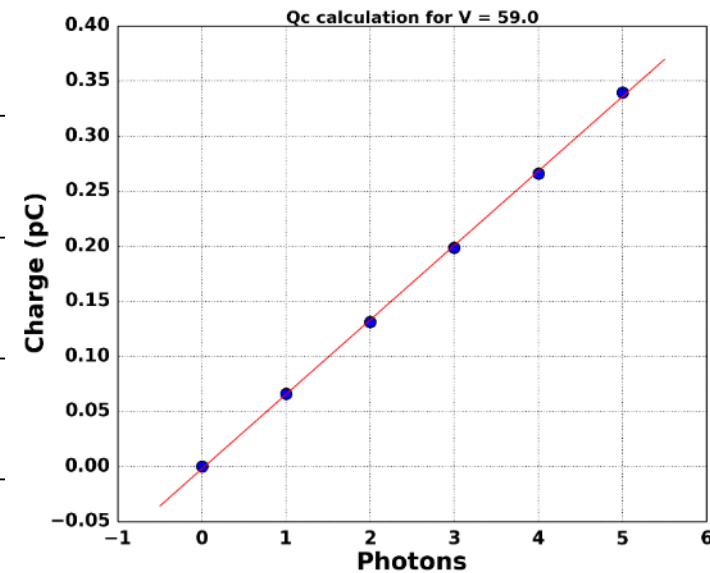
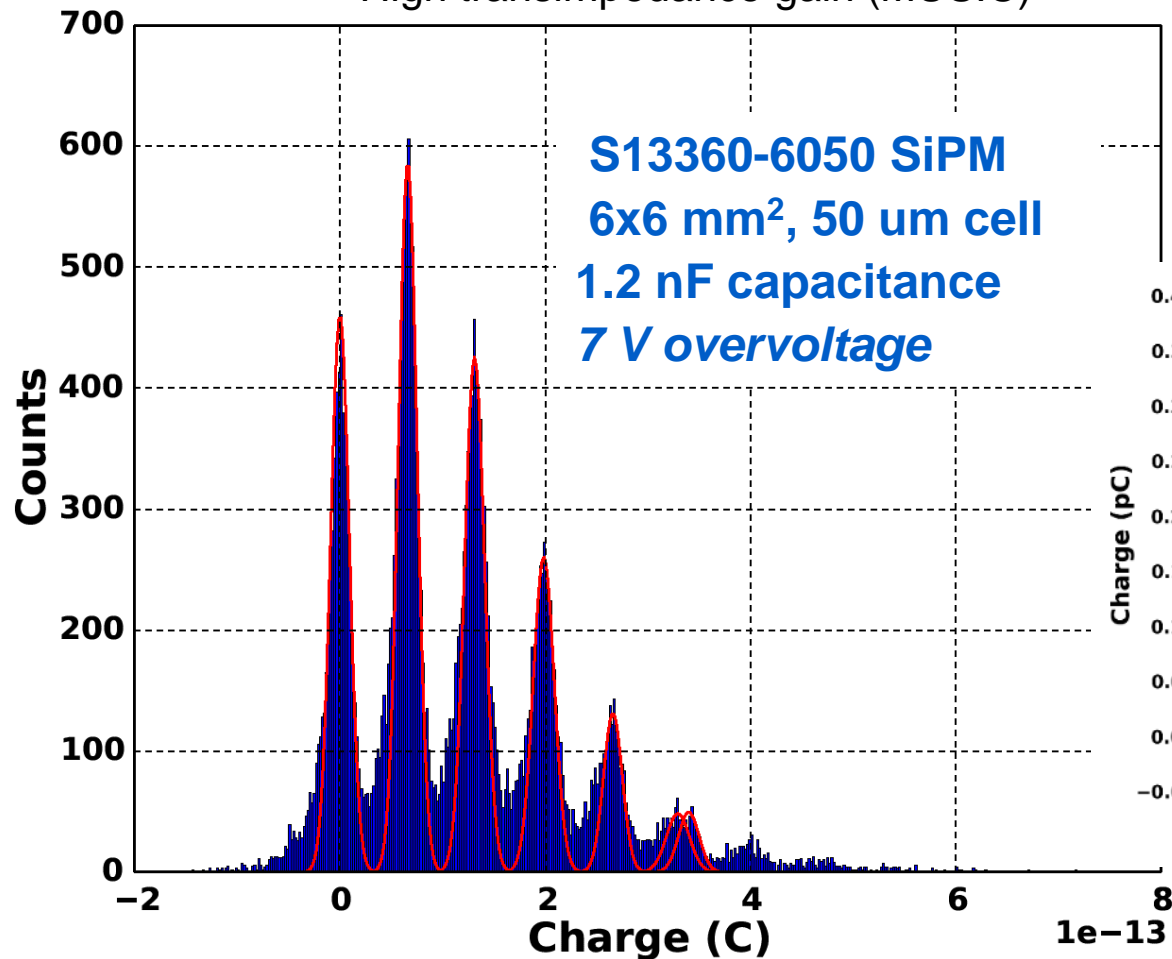
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC configuration: the adder takes only 1 channel
 - Pole-zero cancellation: trade-off between resolution and speed
 - High transimpedance gain (MUSIC)




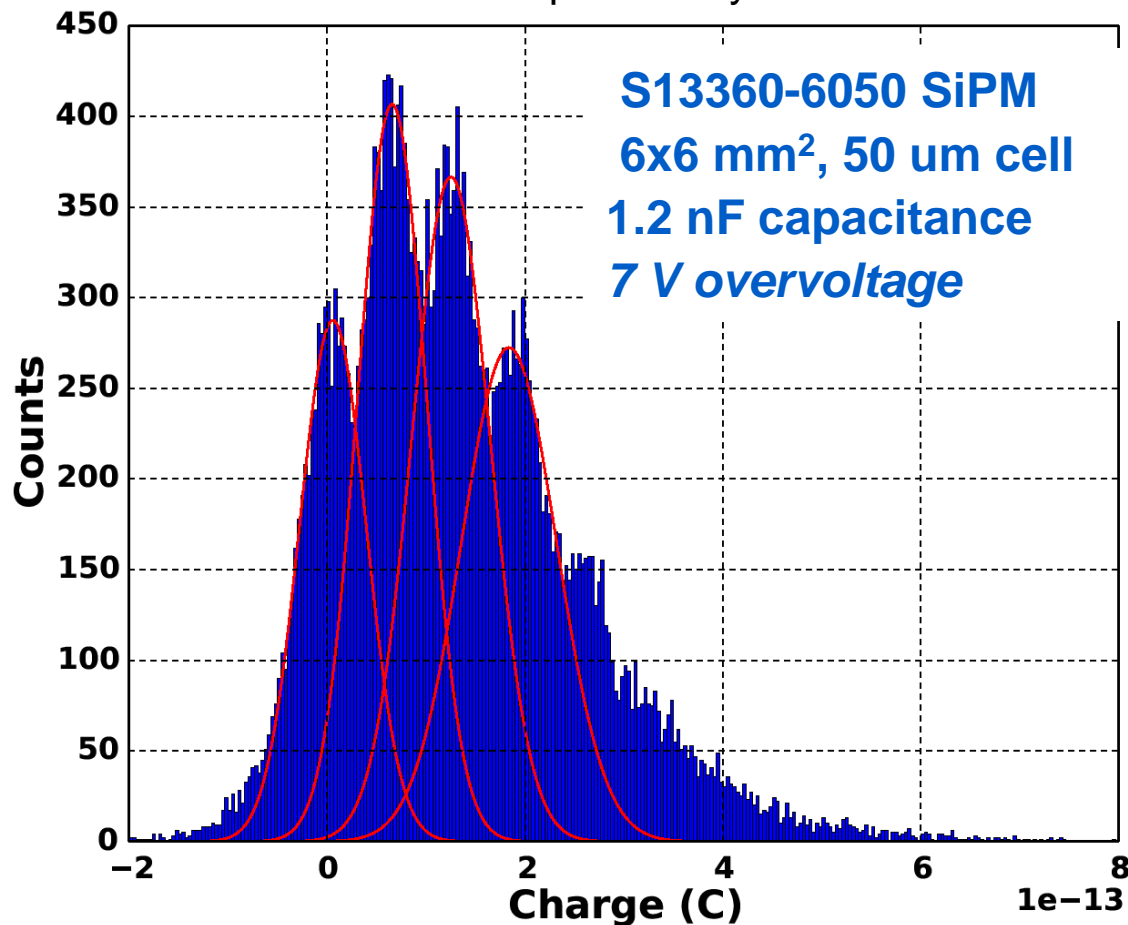 III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC configuration: the adder takes 7 channels
 - Noise is much higher ($\sqrt{7}$)
 - But pe (cell) peaks can still be identified
 - Channels have been equalized by MUSIC anode ctrl voltage




 1 x PMT \approx 7 x SiPM
18 mm diameter \approx 6x6 mm² each



- I. Introduction
- II. SiPM model
- III. FE circuits
- IV. ASICs for PET**
- V. Avenues to fast timing

IV. ASICs for PET: PETIROC

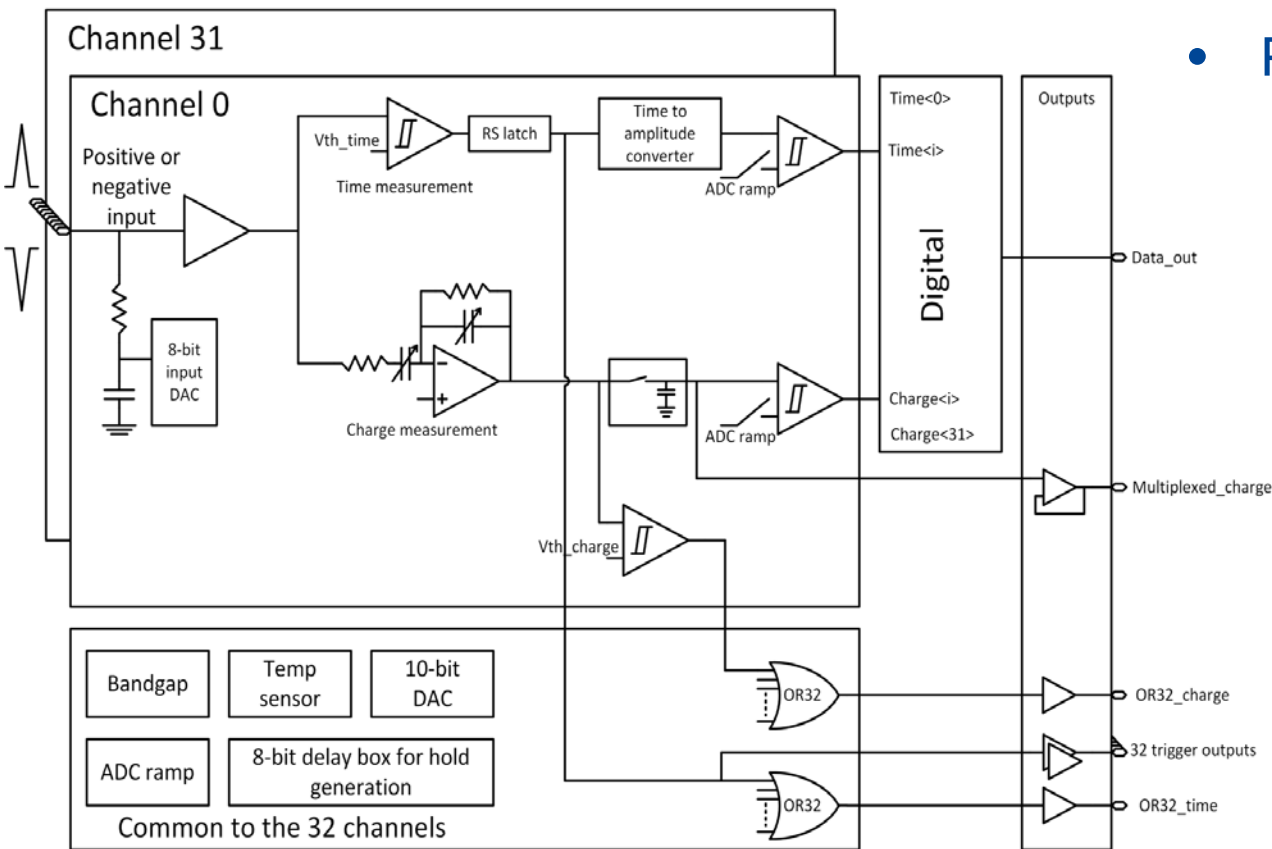

• PETIROC2:

- Voltage mode,
- Configurable: analogue, binary or digital
 - S&H + Wilkinson ADC
- For medical imaging (PET)
- Versatile: analog or digital
- But shaping time > 10 ns
- Max ev. rate is 40 KHz in digital mode
- Power:

<https://www.weeroc.com/fr/products/petiroc-2a>

Detector Read-Out	SiPM, SiPM array
Number of Channels	32
Signal Polarity	Positive or Negative
Sensitivity	Trigger on first photo-electron
Timing Resolution	~ 35 ps FWHM in analogue mode (2pe injected) - ~ 100 ps FWHM with internal TDC
Dynamic Range	3000 photo-electrons (10 ⁶ SiPM gain), Integral Non Linearity: 1% up to 2500 ph-e
Packaging & Dimension	TQFP208 – TFBGA353


IV. ASICs for PET: TOFPET

- Pre-amplifier: low input impedance current conveyor
- Two post-amplifiers (TIA) for time and energy measurements
- Three leading edge discriminators;
 - Very low threshold (1-5 p.e.) for optimum PET time resolution
 - multi-level event rejection

- Time to Amplitude Converter (TAC)
- Charge Integrator (CI)
 - configurable integration windows
 - linear amplitude measurement
 - TAC and Charge Integrator are quad-buffered
 - No dead-time due to Poisson fluctuations

- Two 10-bit ADCs per channel
 - Time and amplitude measurements
 - Optionally: Time-over-Threshold

 - TOFPET2: current mode, digital (linear ToT) and for medical imaging (PET)
 - Power: 8 mW/ch
 - Max rate 200 KHz/ch




J. Varela, "New results with TOFPET2", FAST, Ljubljana, Jan 2018


IV. ASICs for PET: STiC

- STiC: current mode, digital (linear ToT) and for medical imaging (PET)

STiC 2.1
[on test PCB]

 

STiC 3.0
[Chip layout]

 

Features:

STiC 2.1: 16 channels

STiC 3.0: 64 channels

Differential and
single-ended readout ...

Integrated TDC [ZITI, Fischer et al.]
and digital data processing ...

Timing and ToT-based
linearized energy measurement ...
[SPTR:180 ps; MPPC S10362-11-100]


SiPM bias tuning ...
[Tuning range: ~ 500 mV]

Serial interface for data
transmission and configuration ...

STiC — a mixed mode silicon photomultiplier readout ASIC for time-of-flight applications
T. Harion et al., 2014 JINST 9 C02003

 IV. ASICs for PET: FlexToT: linearized ToT RO chip

- Joint project with CIEMAT to develop a time-over-threshold ASIC for SiPM based PET
 - ICCUB: expertise on electronics and microelectronics design for detector FE
 - CIEMAT: expertise on PET and medical imaging instrumentation



FlexToT

16 channel

SiGe BiCMOS 0.35um

Aaustriamicrosystem

10 mm²

3.3 V (10 mW/ch)




QFN 64

IV. ASICs for PET: FlexToT: linearized ToT RO chip

• A Flexible ASIC for SiPM RO (PET, SPECT, Compton)


- Novel current mode input stage
- Time resolution for ToF
- Time over Threshold RO

▪ No ADC

 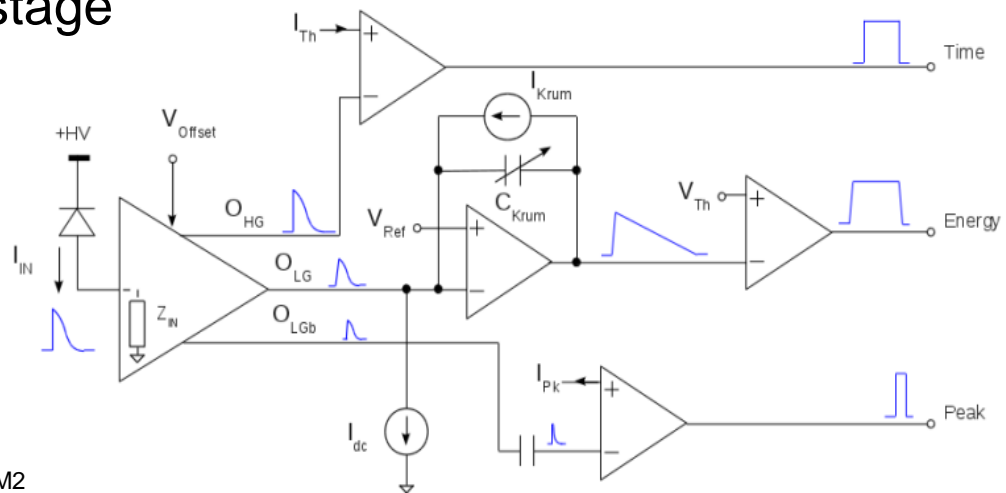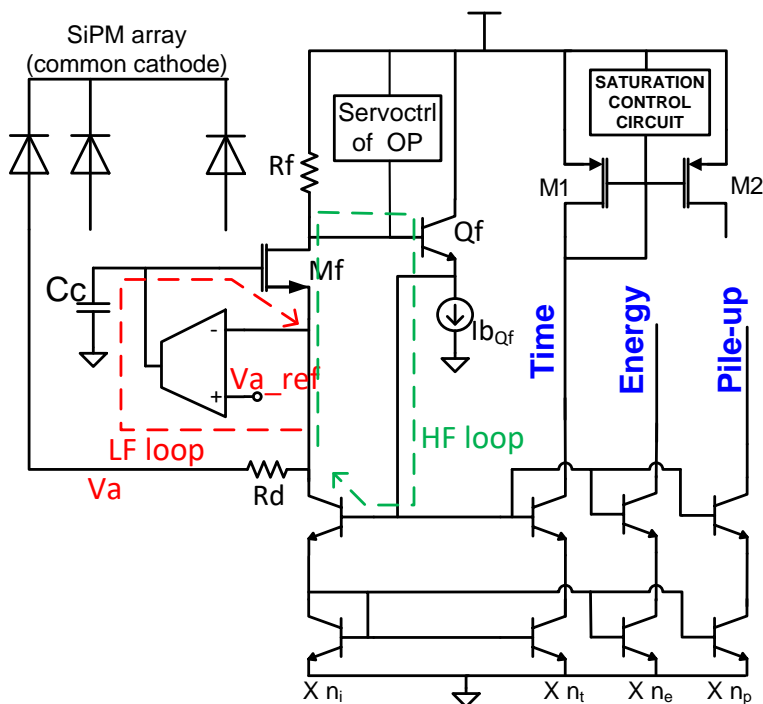

 IV. ASICs for PET: FlexToT: linearized ToT RO chip

- **Good linearity and uniformity**
 - With only comparator threshold offset equalization
- **Different operating ranges can be covered**





IV. ASICs for PET: FlexToT: linearized ToT RO chip

• Measured @ CERN:


- Single Photon Time resolution (SPTR)
- Coincidence Time Resolution (CTR)
- Supported by FAST COST ACTION
 - Many thanks to E. Auffray and S. Gundacker
- Similar results as for NINO but 3 times lower power consumption

Coincidence Time Resolution (CTR): 128 ps FWHM

  - 2x2x5 mm³ LSO:Ce,Ca crystals.
- Measurements performed in a black-box at 15 °C.
- Coincidences corresponding to 511 KeV photopeak ($\pm 3\sigma$).




SPTR=90ps

 

Jitter floor: 7 ps rms

 Coincidence Time Resolution (CTR) test bench setup



IV. ASICs for PET: FlexToT: linearized ToT RO chip



• Pisa University has developped a FPGA based TDC readout for FlexToT

- Based on Arria 10 FPGA
 - TDC: 38 ps resolution
- System CTR: 116 ps FWHM !
- Energy resolution: 8 % FWHM @ 511 KeV
- Dead time < 5ns: event rate > 1 MHz !



P. Catra,
G. Sportelli

2 LYSO xtals 3x3x5 mm³
NUV-SiPM

  


Timing distributions for different source positions

IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- A new version of the FlexToT has been recently developed.
 - A linear Time over Threshold with higher resolution (>8 bits)
 - Lower power consumption (about 3.5 mW/ch)
 - Different trigger levels and cluster trigger for monolithic crystals.
 - Different scintillator time constants.


HRFlexToT 180 nm CMOS

Characterization
during Q1 2018

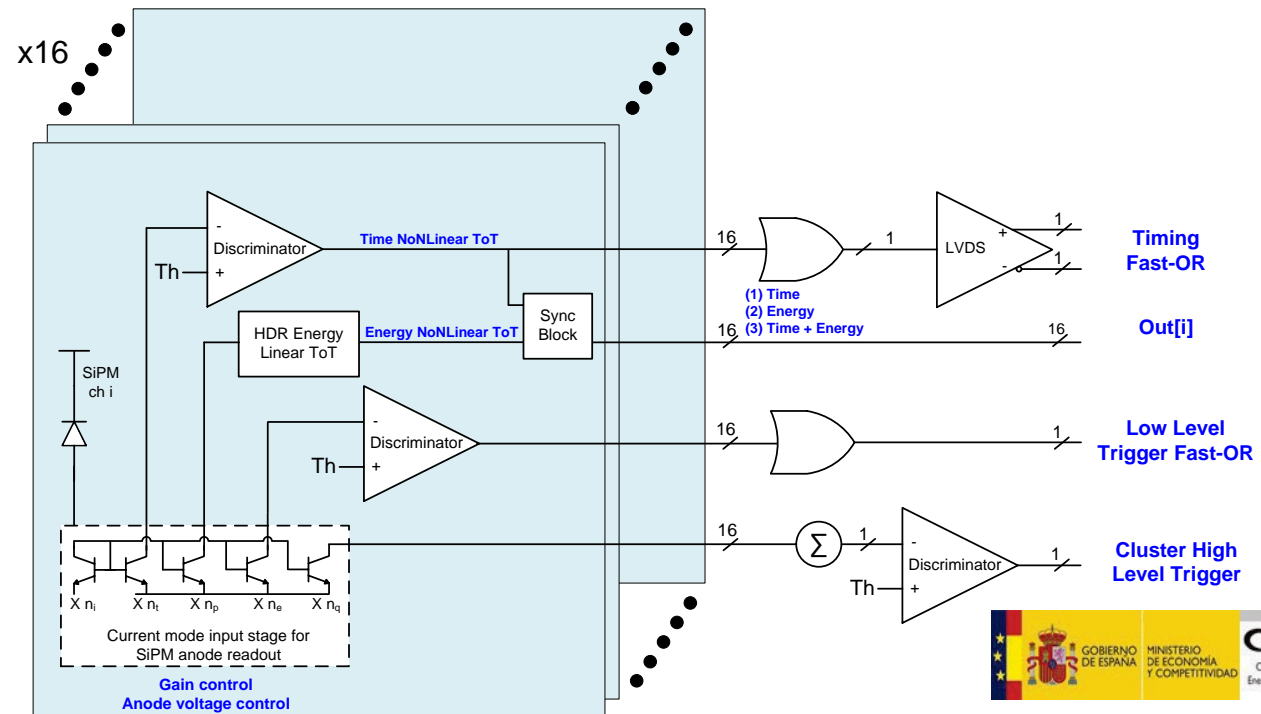

IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Preliminary results

 

- I. Introduction
- II. SiPM model
- III. FE circuits
- IV. ASICs for PET
- V. Avenues to fast timing**


V. Avenues for fast timing

- Disclaimer: I will not talk about “digital SiPMs”
- In the analog domain the FE circuit seems not to be the limitation for large area SiPMs ($> 2 \times 2 \text{ mm}^2$)
 - Best FE chips (PETIROC2A, TOFPET2, STIC, FlexToT and HRFlexToT) show similar results
 - SPTR for small SiPMs ($1 \times 1 \text{ mm}^2$): 40 ps sigma / 100 ps FWHM
 - SPTR for large SiPMs ($3 \times 3 \text{ mm}^2$): 85 ps sigma / 200 ps FWHM
 - CTR for small crystals ($2 \times 2 \times 3 \text{ mm}$) around 100 ps FWHM
 - CTR for large (realistic) crystals ($2 \times 2 \times 20 \text{ mm}$) around 200 ps FWHM
- These are results for pure analog chip/mode
 - Degradation when using on-chip TDCs
 - Limited resolution of the TDCs ($> 30 \text{ ps}$) due to power constraints
 - Noise coupled to the sensitive analog FEs



 V. Avenues for fast timing

- These results are for the best SiPMs
 - Some dependence on the SiPMs
 - But general conclusion remains...



Single photon time resolution of state of the art SiPMs

JINST, published: *October 21, 2016*

M.V. Nemallapudi, S. Gundacker, P. Lecoq and E. Auffray


doi:10.1088/1748-0221/11/10/P10016

V. Avenues for fast timing

- In order to improve CTR we need to progress in
 - Crystals: prompt light emission
 - Sensors: SPTR
 - In the the limit, the single SPAD SPTR: 20 ps FWHM ?
- A cost/power effective mixed-mode approach:
 - Use small SiPMs
 - Better SPTR
 - Low power input stage
 - Demonstrated with HRFlexToT chip
 - Fast analog summation
 - Demonstrated with MUSIC chip
 - Multi threshold comparators
 - Provides estimation of the time of arrival of several photons
 - High performance TDCs and synchronization
 - < 10 ps timing resolution demonstrated in 130 nm technology

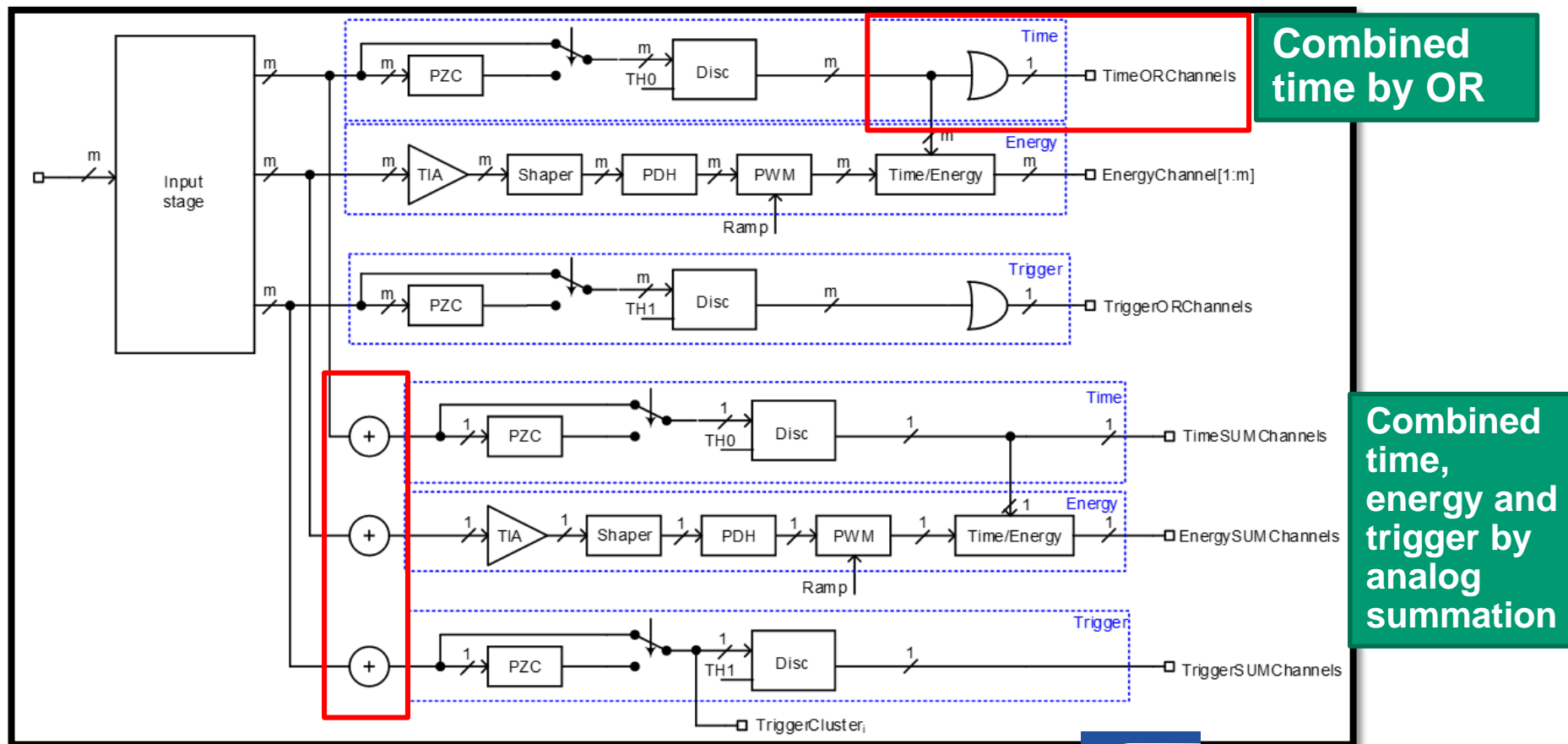V. Avenues for fast timing

- New ASIC in 65 nm being developed by ICCUB and CERN (FastIC)
 - Fast (2 GHz) and low power (< 1mW/input) summation
 - Compatible with picoTDC (3 ps time resolution)



Thanks a lot for your attention !!!

Questions ?

dgascon@fqa.ub.edu



Third Barcelona Techno Week Course on semiconductor detectors

Institute of Cosmos Sciences, Barcelona
From 2nd to 6th July 2018

About ▾ Program ▾ Sponsorship ▾ Registration Meeting Point Outreach Activities ▾ Techno Week Editions





Barcelona Techno Week

Barcelona Techno weeks are a series of meeting point events around a technological topic of interest for both academia and industry. They include comprehensive multidisciplinary keynote presentations by world experts that are combined with networking activities to foster collaboration among participants.

  III. FE circuits: NINO





- NINO: current mode, binary and quite generic
- Binary: usually connected to TDC for Time-Over-Threshold (ToT) energy
 - Simple discriminator: ToT is not linear
- Differential connection to the SiPM



F. Anghinolfi, P. Jarron et al. NINO, NIM A, 2004, Vol. 533 page 183-187

    
III. FE circuits: NINO

- Classical ToT is non-linear
 - Calibration is possible
 - But not perfect...
- It has an impact on energy resolution
 - Calibration is possible
 - But not perfect...



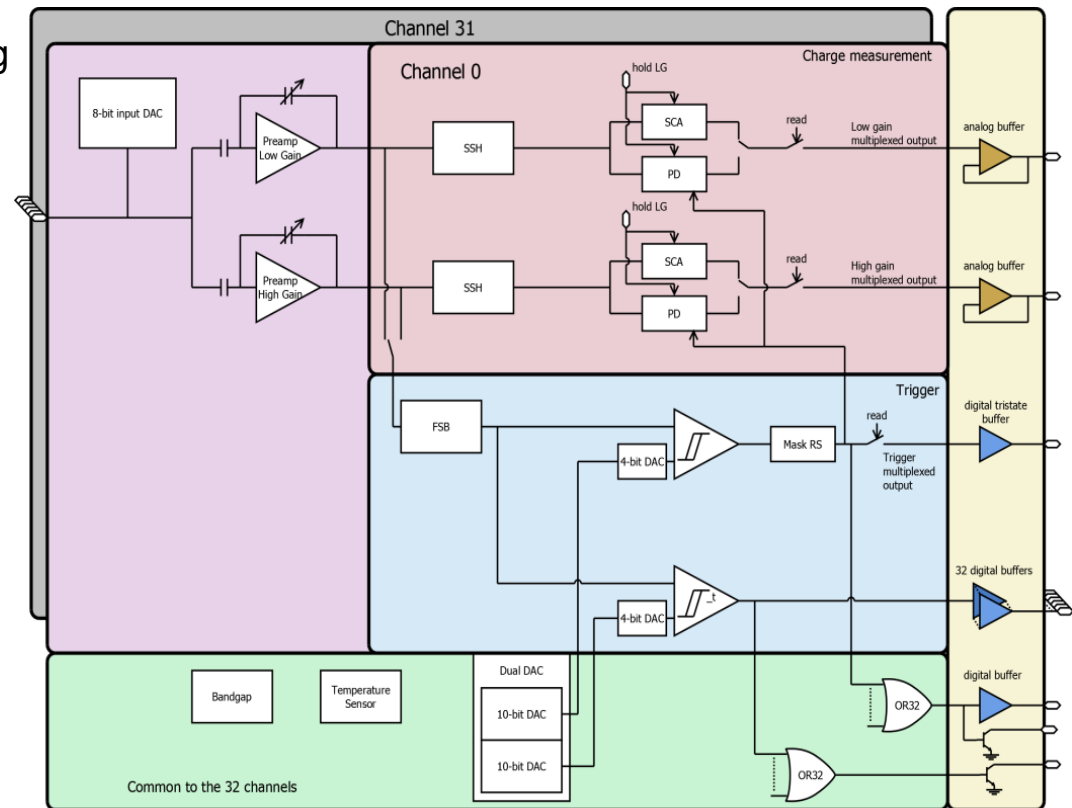III. FE circuits: CITIROC


- CITIROC: voltage mode, analogue and for CTA SSTs ASTRI camera
- Part of Omega/Weeroc family: CITIROC, PETIROC, PETIROC2, TRIROC, etc
- General ASIC
 - 32 channel, charge and trigger outting
 - 6.26mW/Ch. Power pulsed
- Front-end
 - Trigger
 - Fast shaper connected to either low or high gain preamp
 - Two discriminator : one for timing, one for event validation on energy
 - Energy measurement
 - 2 voltage preamplifier (10x gain difference) followed by shaper
 - Analogue memory : track and hold or peak detector
 - Analogue multiplexer
 - **Peaking time between 12.5 and 100 ns**
 - **Valid only for SSTs**



<https://www.weeroc.com/fr/products/citiroc-1a>



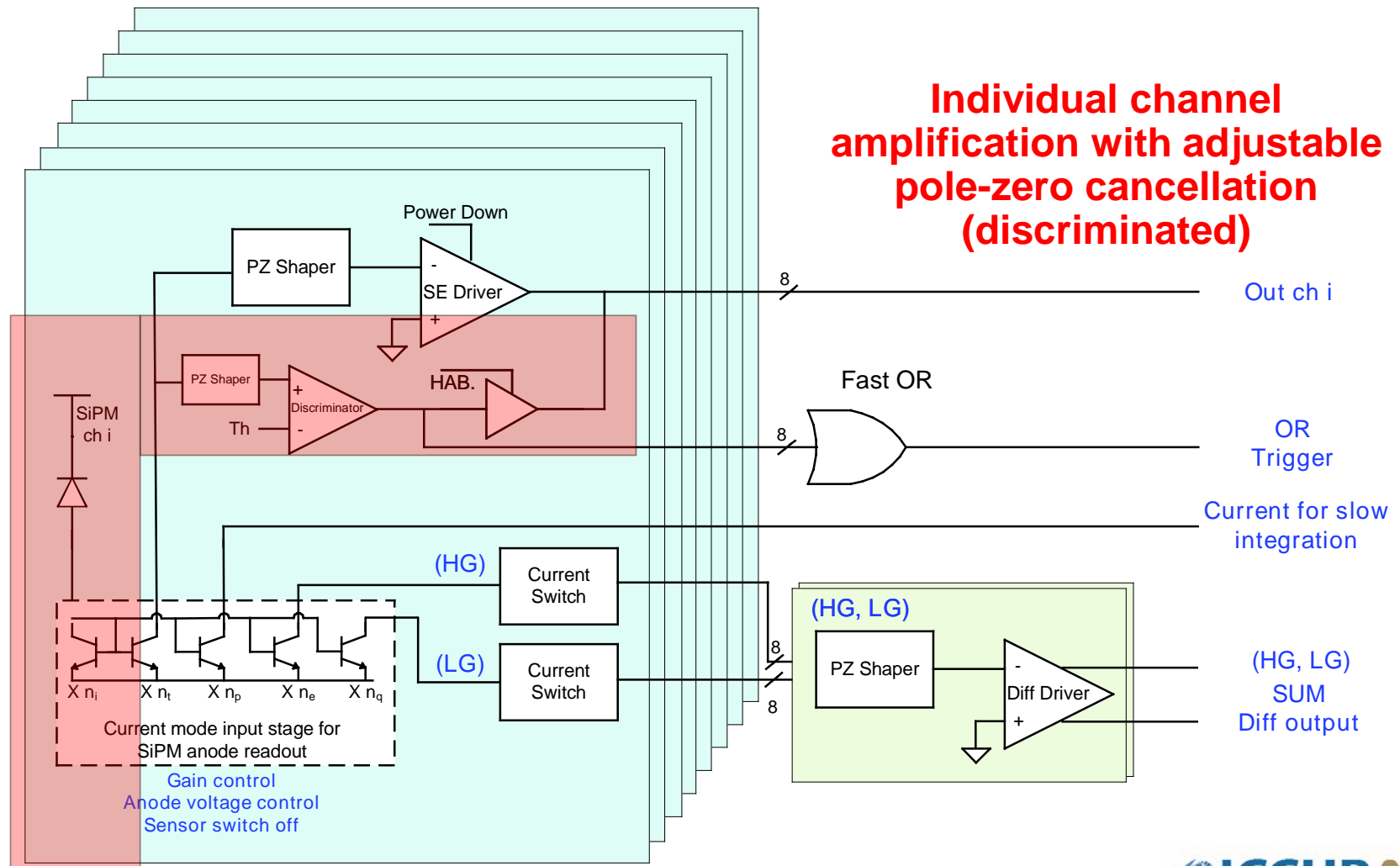
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- MUSIC 8 ch ASIC integrates all those functionalities



   
III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- Output for a LCT4 HPKK MPPC (3x3 mm²)
 - Picosecond laser
 - Pole-zero cancellation
 - Single Photon Time Resolution about 100 ps (@ 5V OV)



 III. FE circuits: MUSIC: Multipurpose SiPM RO chip

- SHIP experiment is a new general-purpose beam dump facility at the SPS (CERN) to search for hidden particles
 - Predicted by a very large number of recently elaborated models of Hidden
 - Dark matter, neutrino oscillations, and the origin of the full baryon asymmetry




SHIP

Search for Hidden Particles




- Reconstruction of the HNL decays in the final states: $\mu^- \pi^+$, $\mu^- \rho^+$ & $e^- \pi^+$

 Requires long decay volume, magnetic spectrometer, muon detector and electromagnetic calorimeter, preferably in surface building




- Long vacuum vessel, 5 m diameter, 50 m length
Background from active neutrino interactions becomes negligible at 0.01 mbar
- 10 m long magnetic spectrometer with 0.5 Tm dipole magnet and 4 low material tracking chambers

 
III. FE circuits: MUSIC: Multipurpose SiPM RO chip



Timing Detector in SHiP

 

 - For the TD of size 5 m x 10 m with a bar **100 cm x 6 cm x 1 cm**
 - 5 col x 182 row = 910 bars =>
 - 910 bars x 2 = 1820 ch =>
 - 1820 x 8 = 14560 SiPMs
- The resolution at 50 cm is ~140 ps => we can use with 1 m bar and 2-side readout to be within 100 ps.






5

   III. FE circuits: MUSIC: Multipurpose SiPM RO chip

Bar and sensors for ToF/ND280



- Bar: 230 cm x 6 cm x 1 cm
- Plastic material:
 - EJ200 (BC408) or EJ208(BC412)
 - Attenuation length ~ 4 m
 - 1.42 kg/bar
- Readout from both ends
 - 8 sensors of 6 mm x 6 mm
 - Example: S13360-6050PE



  III. FE circuits: MUSIC: Multipurpose SiPM RO chip

• Timing sub-detector test beam with MUSIC chip

- By Univ. Geneva & Univ. Zurich
- MUSIC in summation mode (8 $6 \times 6 \text{ mm}^2$ SiPMs)
 - Bar read-out at both ends
- 2.5 GeV/c muon beam at the CERN PS
- Readout with Wavecatcher
 - Fast analog memory (LAL & IRFU/CEA)




- Measurements with the 150 cm x 6 cm x 1 cm bar.
- Time resolution as measured by the SiPM arrays at both ends of the bar as a function of the interaction point along the bar.

© A. Kornezev (Univ. Geneva)

 III. FE circuits: MUSIC: Multipurpose SiPM RO chip


- Studying the possibility to develop a beam loss monitoring system based on scintillating fibers
 - Collaboration with Alba synchrotron General idea:
 - Fiber along the beam pipe or in selected regions
 - Losses are detected by a rate increase
 - With timing information, additional position information
 - Preliminary results: 20 cm resolution for a 2 m fiber of 1 mm diameter



IV. ASICs for PET: FlexToT: linearized ToT RO chip



• Spectroscopy with linear ToT

 


Outlook

- I. Introduction
- II. SiPM model
- III. FE circuits
- IV. Digitization**
- V. System-On-Chip (SoC)
- VI. Emerging technologies

III. Digitization: basic options


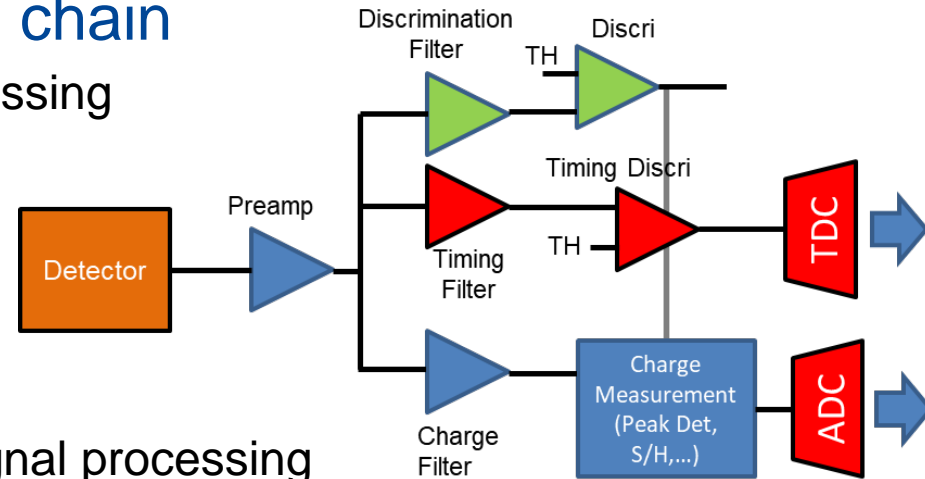
1) “Classical” signal processing chain

- Requires complex analogue processing
- Not so flexible
- Optimal in power for specific app.



  2) Digital signal processing


- Waveform sampling and digital signal processing
- Ideally one should sample at $f_s > 2 \times \text{signal BW}$ (x5)



E. Delagnes, “Precise Pulse Timing based on Ultra-Fast Waveform Digitizers”, IEEE NSS 2011

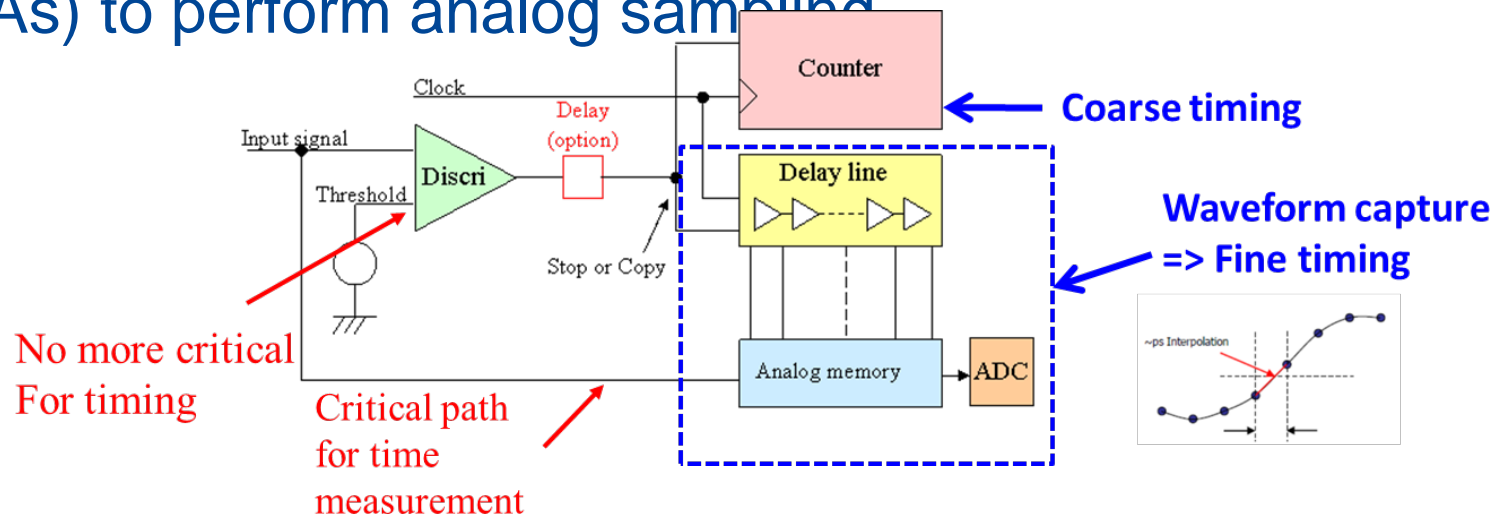III. Digitization: waveform sampling

- Very demanding sampling specs for IACTs
 - Dynamic range of about 12 bits (with several gains)
 - Analog BW > 300 MHz requires 1-2 GS/s
 - Power consumption and ADC cost !
 - Alternative: FlashCAM digitizes at much lower speed and tries to extract signal parameters by signal processing
 - But NSB will be there anyway, so energy threshold will be degraded...
- Many projects have been using Switch Capacitor Arrays (SCAs) to perform analog sampling




E. Delagnes, "Precise Pulse Timing based on Ultra-Fast Waveform Digitizers", IEEE NSS 2011

III. Digitization: waveform sampling

- SCAs sample the signal which is digitized at a lower speed



Switched Capacitor Array (Analog Memory)

 


III. Digitization: waveform sampling

 G. Varner Univ. Hawaii



TARGET 
CTA SCT and SST

Many chips for different projects
 Buffered and unbuffered
 Very deep arrays
 ADC on chip.
 Philosophy => pushing the
 limit of the SCA technology



Straw3 Labrador Labrador3 Target BLAB family

H. Frisch et al., Univ. Chicago



ps family


Goal: reach a 1ps precision !
 Pioneering R&D work
 130nm IBM
 18 GSPS, 256 samples, 6ch
 ADC on chip

Initiator of a
 networking
 activity on SCAs
 and ps-timing

S. Ritt, R. Dinapoli PSI



 Universal chip for many applications
 8 + 1 channels 1024 cells
 5GSPS, 950 MHz BW
 Low power consumption
 Short readout time
 Several possible modes of operation



DRS1 DRS2 DRS3 DRS4

DRS4
CTA LST

D. Breton IN2P3/LAL
 E. Delagnes CEA/Saclay



NECTAr
CTA MST-
NECTArCAM




ARS



MATAcq



SAM family

 


Nectar

More than 120.000 SCAs operating worldwide
 Buffered (f_{3dB} 400-500MHz) 3.2GSPS
 High dynamic range
 Robust (minimum calibration or ext. control)
 Conservative technologies
 Moderate depth 256-1024 cells/ 2ch
 On-chip ADC in the last chip

E. Delagnes, "Precise Pulse Timing based on Ultra-Fast Waveform Digitizers", IEEE NSS 2011

III. Digitization: waveform sampling

SAMPIC Waveform TDC

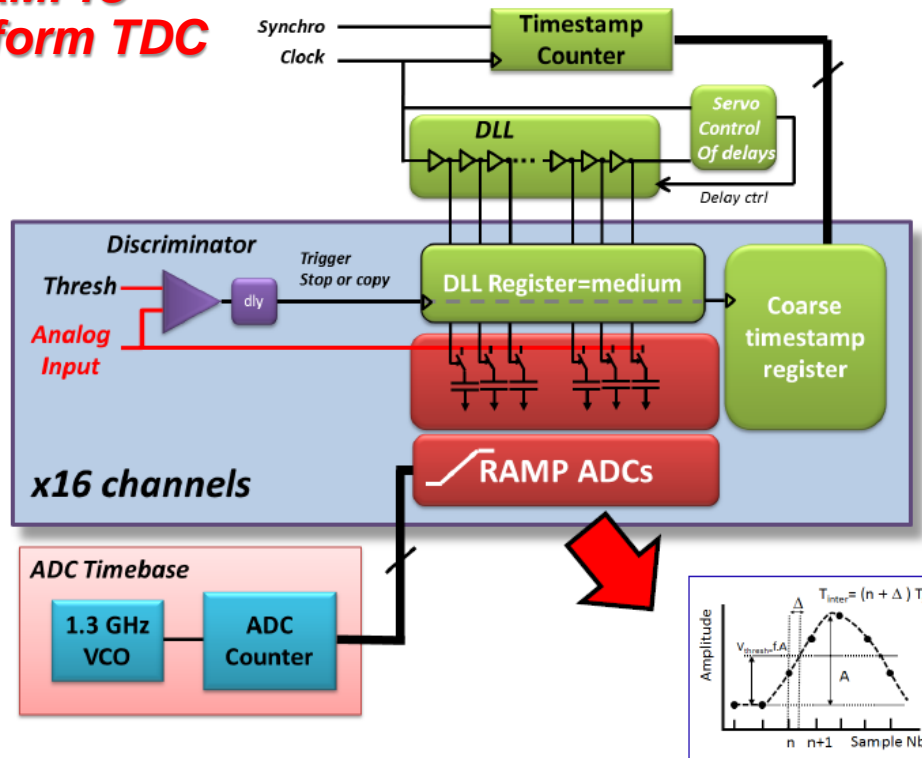

Global time = counter (~10ns) + DLL (~100ps) + waveform(~ps)

Waveform is available for extraction of other parameters (Q, A)

- **One Common 12-bit Gray Counter** (FClk up to 160MHz) for Coarse Timestamping.

- **One Common servo-controlled DLL:** (from 1.6 to 10.2 GHz) used for medium precision timing & analog sampling

- **16 independent WTDC channels each with :**

- ✓ 1 discriminator for self triggering
- ✓ Registers to store the timestamps
- ✓ 64-cell deep SCA analog memory
- ✓ One 11-bit ADC/ cell

(Total : $64 \times 16 = 1024$ on-chip ADCs)

- **One common 1.3 GHz oscillator + counter** used as timebase for all the **Wilkinson A to D converters**.

- **Read-Out interface**

- **SPI Link** for Slow Control configuration


III. Digitization: waveform sampling

SAMPIC Waveform TDC

SAMPIC_V1 PERFORMANCES


- Power consumption: **10mW/channel** →
- 3dB bandwidth > **1 GHz**
- Discriminator noise ~ **2 mV rms**
- Counting rate > **2Mevts/s** (full chip, full waveform),
up to > 10 Mevts/s with Region Of Interest (ROI)

Power
distribution

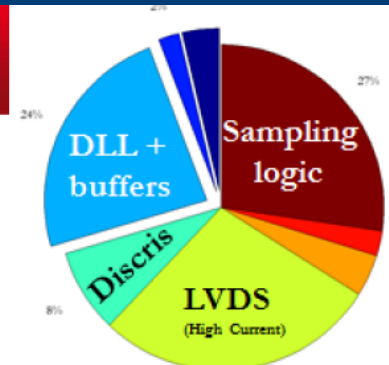


- Wilkinson ADC works with internal **1.3 GHz** clock

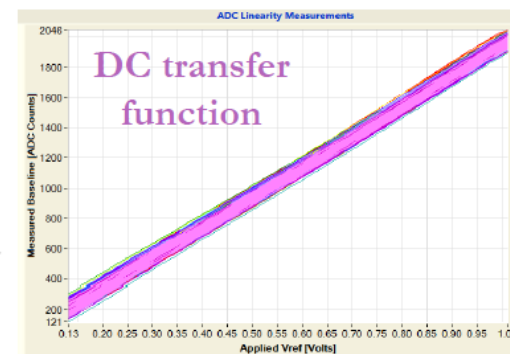- Dynamic range of **1V**
- Gain dispersion between cells ~ **1% rms**
- Non linearity < **1.4 %** peak to peak
- After correction of each cell (linear fit):
noise = **0.95 mV rms**



Ex: TDR @ 6.4 GS/s

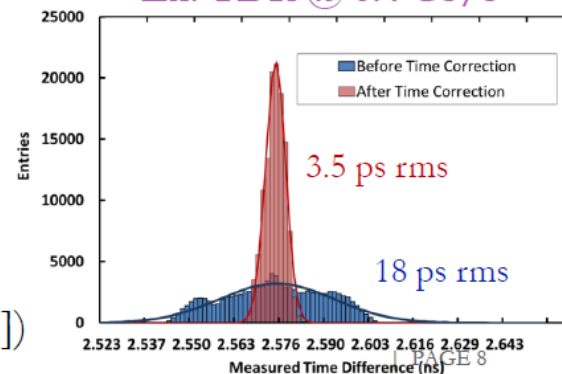


D. Breton, 4th FAST WG3/4/5 Meeting, Ljubljana, January7/8 2018

III. Digitization: waveform sampling

- CHEC camera is an interesting example of compact readout

CTA Application for TARGET

 

CHEC design for CTA


Gary S. Varner, 2nd Adv SiPM Workshop, Geneva, 2014

III. Digitization: waveform sampling


- Several iterations to have a functional chip: TARGET7

TARGET7 Specification Summary

16384	samples/chan (16-32us trig latency)
16	channels/TARGET ASIC
$\Sigma 4 \rightarrow 4$	Trigger channels (indep. Thr/Width)
~9-10	bits resolution (12-bits logging)
32	samples convert window (~32-64ns)
0.5-1	GSa/s
1	word (RAM) chan, sample readout
<10	us to convert 512 samples (at once)
>100	kHz sustained readout (multibuffer)

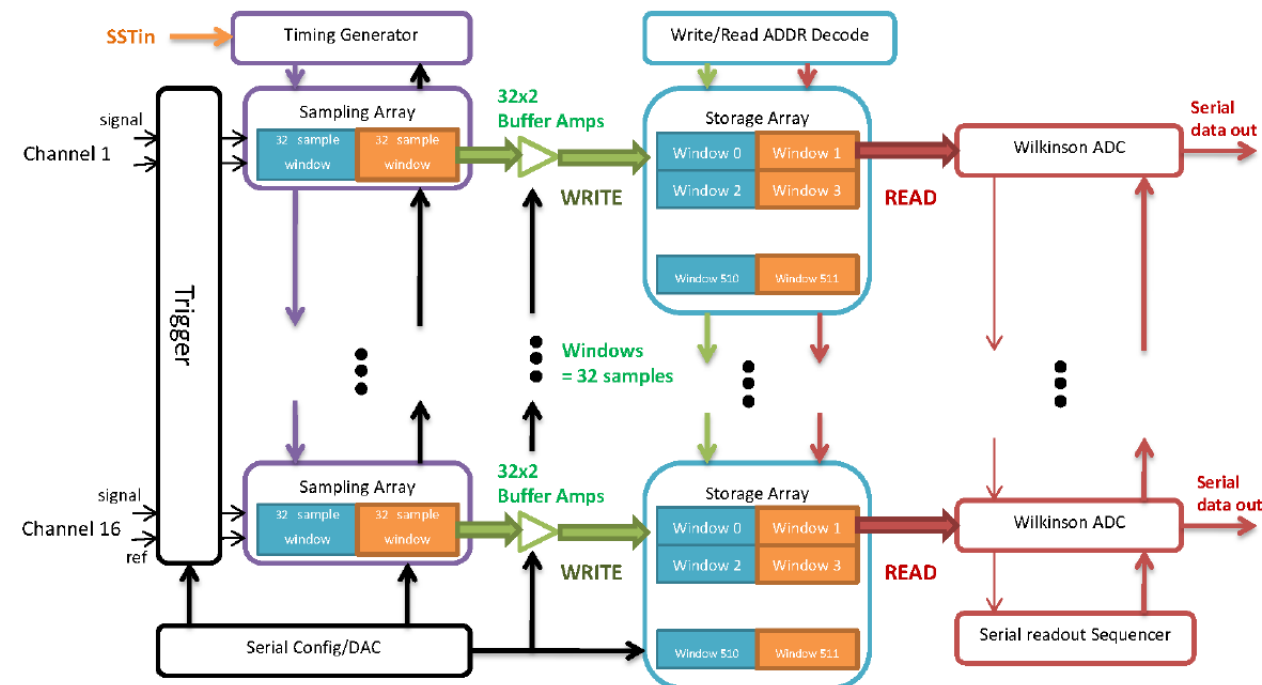

 Gary S. Varner, 2nd Adv SiPM Workshop, Geneva, 2014




Outlook

- I. Introduction
- II. SiPM model
- III. FE circuits
- IV. Digitization
- V. System-On-Chip (SoC)**
- VI. Emerging technologies

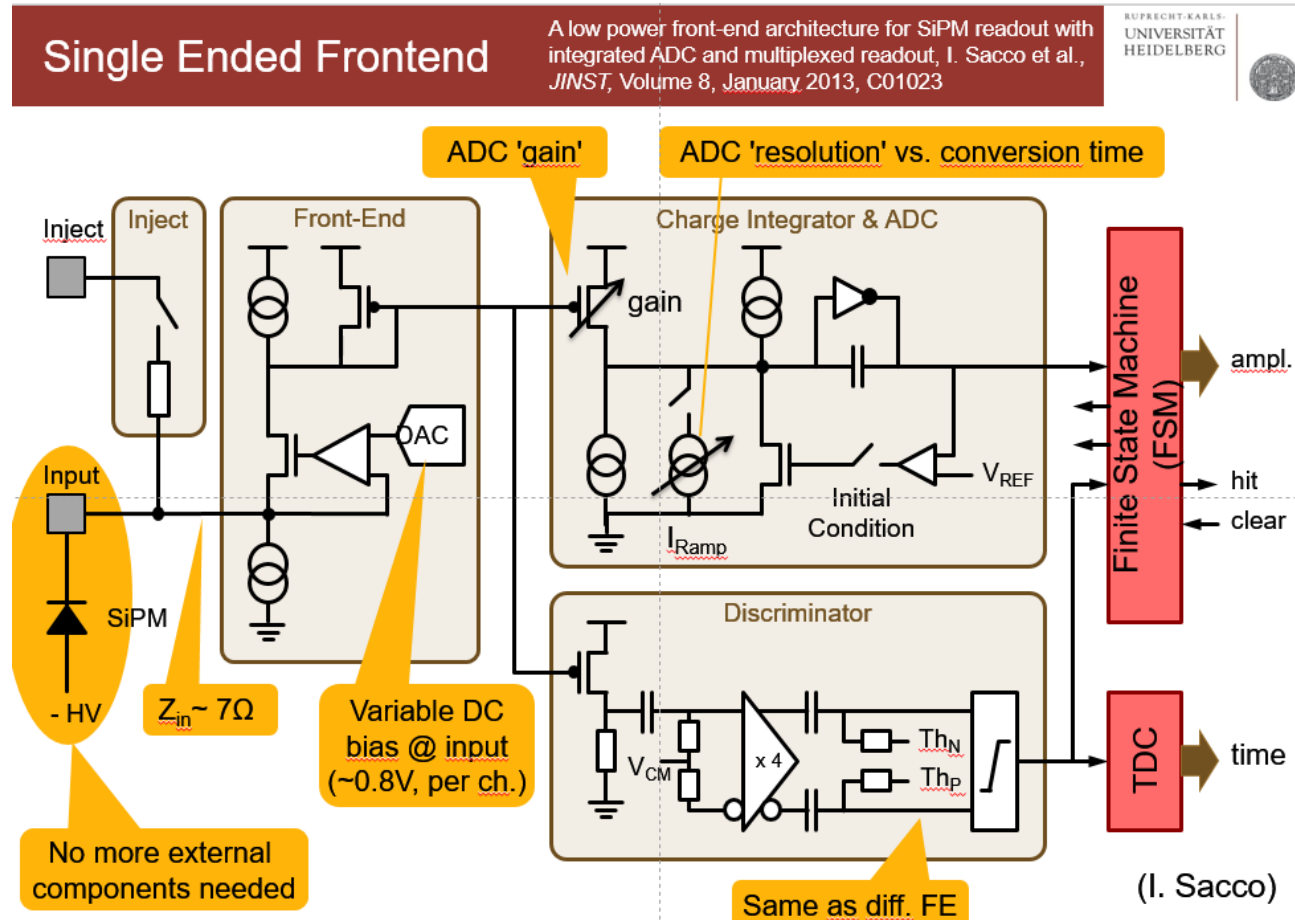IV. ASICs for PET: PETA


- PETA: current mode, charge (ADC) and time (TDC), for PET
 - Choice between Differential FE (both polarities, MRT immune) and Single Ended FE (low Z_{in} , DC bias adjustment, no external coupling parts)
 - Readout rates >200 kHz per channel (in all channels)
 - Power consumption ~30mW / channel



P. Fischer, Heidelberg University, The PETA Chip Family FAST Workshop, FBK 2016

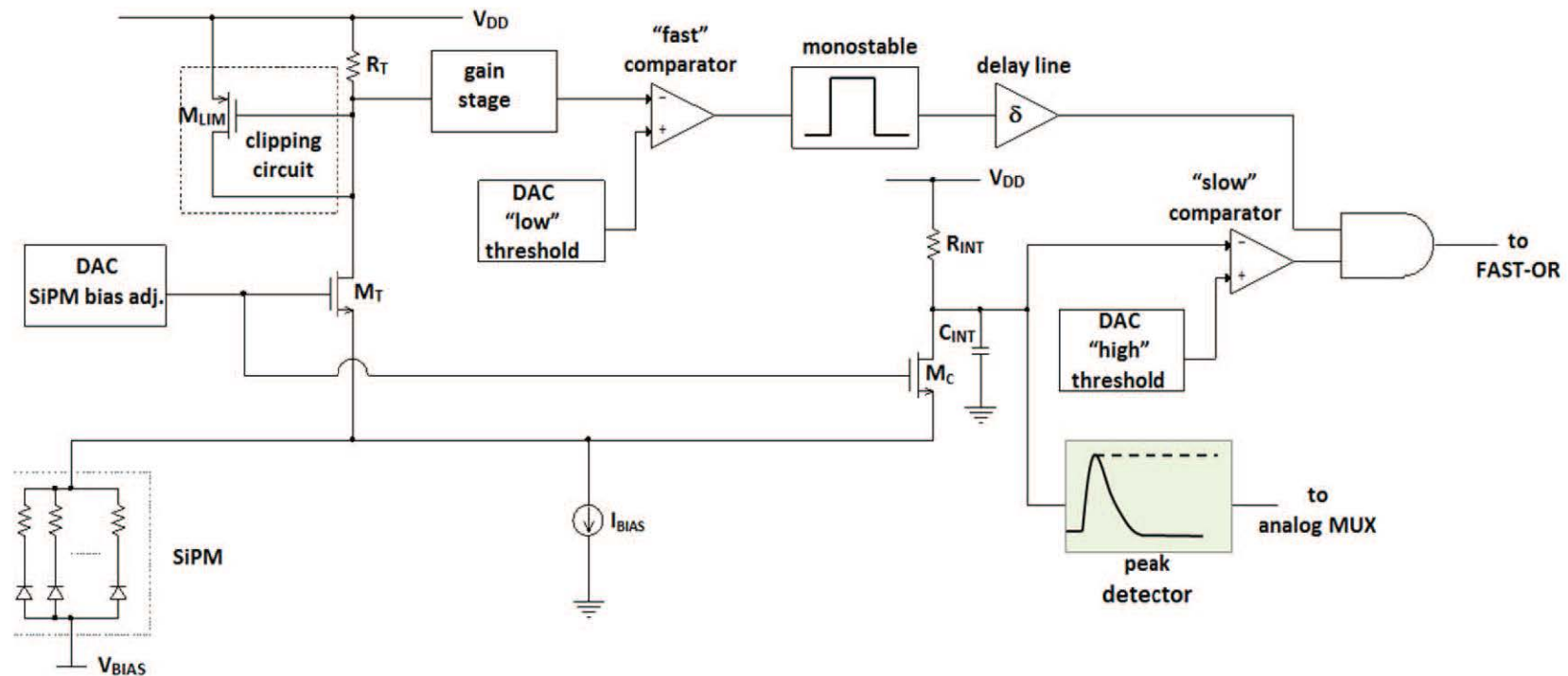IV. ASICs for PET: BASIC64

- BASIC64: current mode, digital (peak detector + ADC) and for PET
 - Power: 10 mW/ch
 - Max rate: 75 KHz/ch
 - No TDC for timing





C. Marzocca et al., "BASIC64: A new mixed-signal front-end ASIC for SiPM detectors," NSS 2016

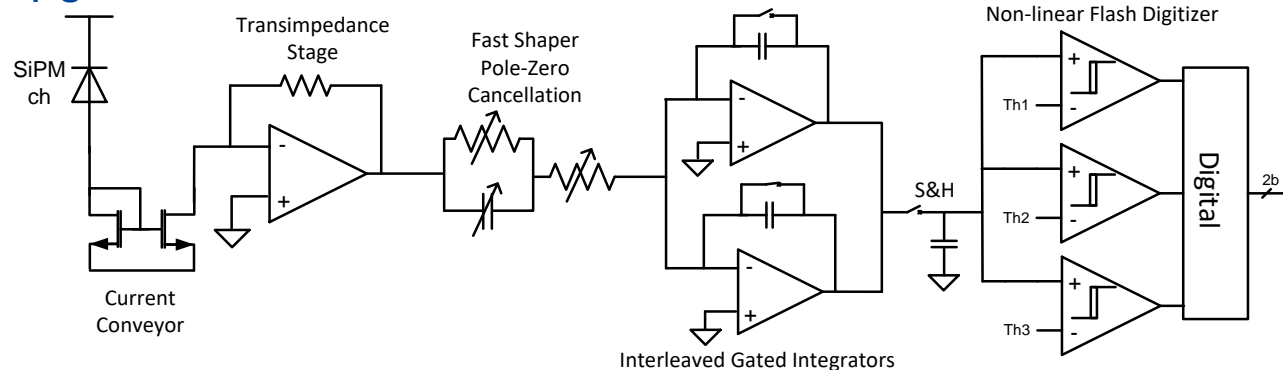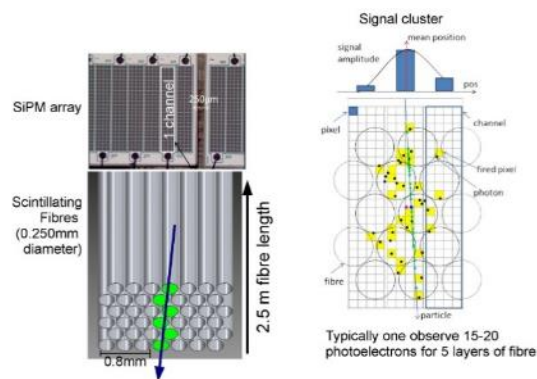IV. ASICs for PET: PACIFIC


Collaboration: ICCUB, Heidelberg, LPC-Clermont, IFIC-Valencia

- PACIFIC: A 64 ch ASIC for Scintillating Fiber Tracking in LHCb Upgrade



- Similar input current conveyor as in FlexToT
- Current conveyor with very low impedance input ($\approx 30\Omega$)
 - Adjustable gain / dynamic range
 - Input voltage adjustment
- Fast tunable shaper
 - Pole-zero cancellation to cancel slow SiPM time constant
 - A FWHM of 5 ns is achieved for single-cell signal
- Dual interleaved 25ns gated integrator
 - Almost no dead time
 - Average photo-statistical fluctuations
 - Maximize charge collection (25 ns integration)
- 2 bits 40MS/s flash non-linear ADC
- Power consumption < 8mW/channel @ 1.2 V


130 nm CMOS technology

 

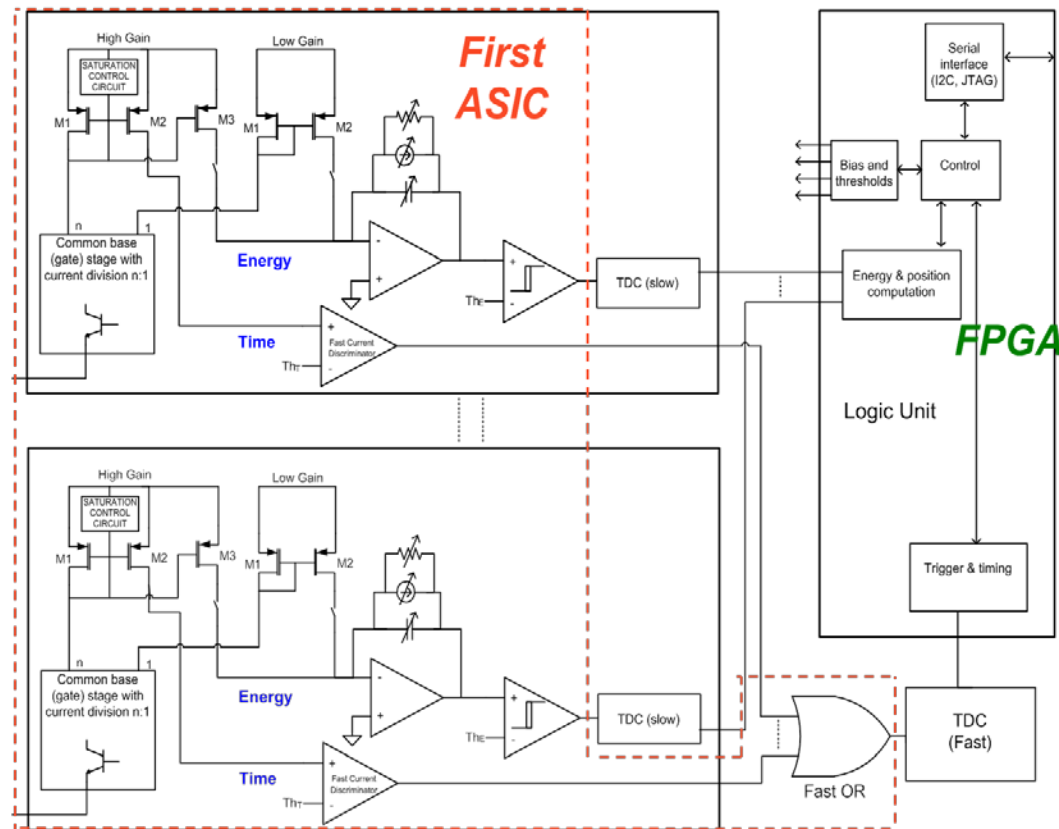IV. ASICs for PET: FlexToT: linearized ToT RO chip

• Why FlexToT is flexible?




- Different scintillator time constants
- Trading-off resolution versus rate
- Accurate analog processing directly connected to FPGA
 - TDCs and signal processing are in FPGA: reconfigurable !



IV. ASICs for PET: FlexToT: linearized ToT RO chip


- No linear ToT may degrade resolution
- Linear ToT is possible
 - Used in Medipix, Timepix, Dosepix ASICs family
 - Also proposed for PET
 - Tuneable feedback current (IFB)

▪ Rate vs resolution

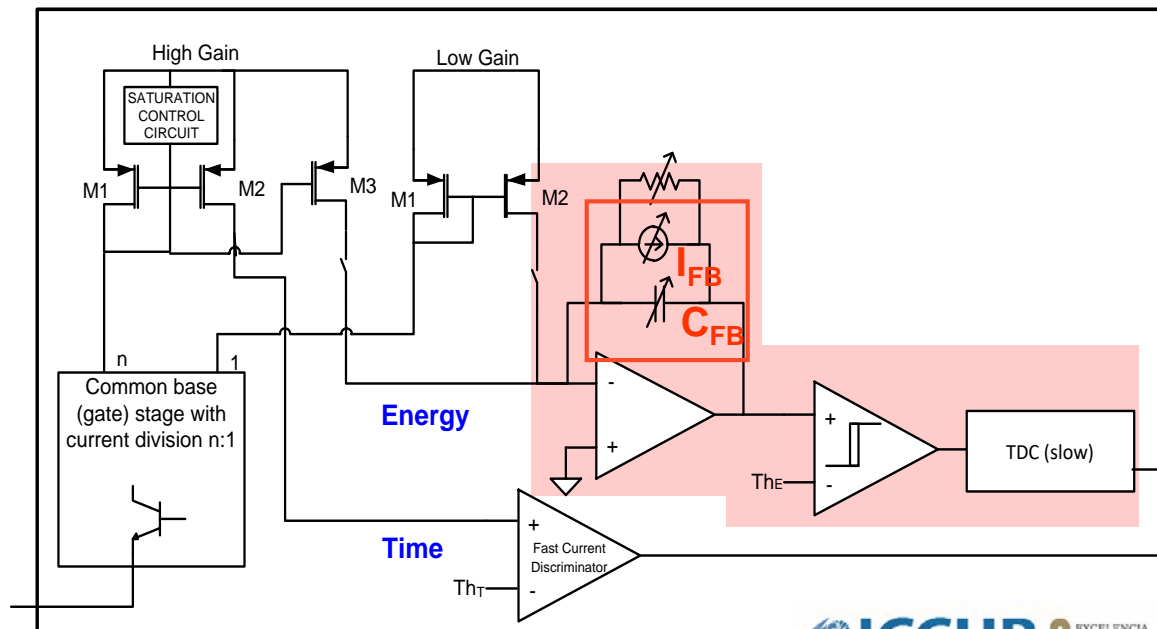  


IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Preliminary results

 

IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Preliminary results

 

IV. ASICs for PET: HRFlexToT: linearized ToT RO chip

- Preliminary results

