

Understanding the RD53 chip frontends

Including: “Never underestimate the joy people derive from hearing something they already know.” (E. Fermi)

*E.J. Schioppa
Lecce, April 2020*

RD53 specifications (2015)

Specification	Value	Comment or Test Conditions
Input polarity	Negative	
Interior pixel capacitance	<100 fF	this applies to most pixels
Edge pixel capacitance	<200 fF	see subsection on edge pixels
Interior pixel leakage current	<10 nA	
Edge* pixel leakage current	<20 nA	*see Sec. 5.2 for details
Min. stable threshold setting	600 e ⁻	With 50 fF load, 4 μA/pixel analog. For free running discriminated pixel. See Sec. 3.1
Min. charge above threshold resulting in <25 ns time walk	600 e ⁻	With 50 fF load, 4 μA/pixel analog. For free running discriminated pixel. See Sec. 3.1
Min. in-time threshold with free-running front end	1200 e ⁻	With 50 fF load, 4 μA/pixel analog. Simply the sum of the two above lines
Min. in-time threshold if using synchronous reset	750 e ⁻	With 50 fF load, 4 μA/pixel analog. See Sec. 3.1
Hit loss from in-pixel pileup	≤1%	at 75 kHz avg. hit rate. See Sec. 3.2
Recovery from saturation	<1 μs	See Sec. 3.2 for discussion
Trigger rate	1 MHz	

Trigger latency	12.5 μs	
Noise occupancy per pixel	< 10 ⁻⁶	50 fF load; in a 25 ns interval
Single pixel noise (ENC)	design-dependent	See Sec. 3.1
Radiation dose	500 Mrad	delivered at -15 C. Room T annealing only
Temperature range	-40C to +40C	
Current consumption, analog	4 μA/pixel	periphery consumption not included
Current consumption, digital	<4 μA/pixel	periphery consumption not included
Current consumption, Total	<500 mA/cm ²	Note this is 1 W/cm ² at 2 V input
SEU's affecting full chip	<0.05/hr/chip	in 1.5 GHz/cm ² particle flux
SEU's affecting single pixel	<100/hr/chip	in 1.5 GHz/cm ² particle flux
Charge scale shift	<2% / Mrad	change in mean with radiation
Threshold scale shift	<15 e ⁻ / Mrad	change in mean with radiation
Threshold dispersion	<60 e ⁻ / Mrad	added in quadrature
Charge meas. dispersion	<0.1 MIP/Mrad	added in quadrature

Critical performance specs (innermost layer)

Input capacitance

Johnson-Nyquist theorem*:
because of thermal noise, the charge
on a capacitance fluctuates with

$$\langle Q \rangle = 0 \quad \sqrt{\langle Q^2 \rangle} = \sqrt{kTC}$$

C	$\sqrt{\langle Q^2 \rangle}$
1 nF	12500
10 pF	1250
100 fF	125
1 fF	12.5

**one of the many specific cases of the fluctuation-dissipation theorem*


For a **single-sided** pn-junction:

$$C = \frac{\epsilon A}{W}$$



surface of the junction (pointing to A)
width of the depletion region (pointing to W)

For a **hybrid detector**:

 
$$\frac{1}{C_{tot}} = \frac{1}{C_{sensor}} + \frac{1}{C_{bb}} + \frac{1}{C_{ro}}$$




Charge sensitive amplifiers

  

On a longer
time scale


 


 The easiest way to
control the reset time



Now the circuit
is ready for a
new input

Leakage current

  

- In the depletion region, the only process that injects charge into the (reverse biased) junction is thermal generation
- The generation rate is something like

$$g = \frac{n_i}{\tau_g} \quad \leftarrow \text{temperature dependence (exponential...)}$$


- The leakage current density is (just by dimensions)

$$J_{leak} = -e \frac{n_i}{\tau_g} W$$

where (single sided pn-junction)

$$W = \sqrt{\frac{2e(V_{bi} + V_{bias})}{eN_{D/A}}}$$

The Krummenacher feedback circuit

 


F. Krummenacher, Pixel detectors with local intelligence: an IC designer point of view, NIM A305 (1991) 527-532

- Add a second feedback loop to a CSA
- The leakage current is forced to flow through M2, and not through the first loop

The RD53 linear frontend

Global DAC in the periphery

 


Single stage with
Krummenacher feedback

CSA:

- Low power (single stage)
- $Q_{max} = 30ke^-$
- Current conspn. = 4uA (most of the full FE)
- $I_k = 25nA$ @ high gain
→ ToT=400ns @ 30ke-
- High gain = 15mV/ke-
- Low gain = 7.5mV/ke-
- ENC = 87e- @ $C_{in}=50fF$

The RD53 linear frontend

 


Discriminator


- High speed (fast switching)
- Low power
- Current comparison
- Threshold dispersion:
 - 380 e- before tuning
 - ISSUE: this value is huge
 - 35 e- after tuning

The RD53 linear frontend

CSA forward gain stage

 


Threshold discriminator

 

The RD53 differential frontend

 Leakage current compensation (enabled/disabled globally)



Gain selector (global)

FE:

- Low power
- Small area
- Free running
- Purely analog
- $Th_{min} = 500e-$
- Current conspn. = 4uA
@ $C_{in} = 50fF$, $I_{leak} = 10nA$

Preamplifier:


- Low current
- Continuous reset
- Small fall-time dispersion → no local feedback current adjustment
- The LCC is not needed (no saturation) when $I_{leak} < 10nA$

11



- Additional amplification
- Only one branch can be adjusted at a time (Sel bit, the other branch is set to all 0 or all 1 globally)
- Optimized for low threshold
- Differential = small mismatch variations
- Good power supply rejection (?)

The RD53 differential frontend


 


Comparator



- ISSUE: Design bug → delay and ToT are not reliable for a sub-section of pixels
→ there exists a “good pixels mask” (for timing measurements)

Standard comparator with ToT counter (TDC)



The RD53 differential frontend

  

The RD53 differential frontend

  


The RD53 differential frontend

  


The RD53 differential frontend


Preamplifier

 

Pre-comparator

 

The RD53 synchronous frontend

 


Single stage with
Krummenacher feedback

AC coupling

CSA:

- $I_k = 10\text{nA} \rightarrow T_{OT} = 400\text{ns}$
@ 10ke-
- 2 possible gains (2.5 fF and 4 fF)

The RD53 synchronous frontend

 

Discriminator

- AC coupling removes the fluctuations from process mismatch
- Provides an additional gain (around x2)
- No adjustment bits → residual offset at output
- This is compensated by a latch circuit for auto-zeroing:
 - During LHC abort gaps, acquire 100ns baseline every 100us
 - Store the baseline value
 - Subtract baseline from signal
 - ISSUE: this induces noise on the power lines
- The latch can also be operated as ToT logic (working as a 800 MHz local oscillator)


Preamplifier




The diagram shows a two-stage CMOS op-amp. The first stage is a differential pair with NMOS transistors M1 and M2, and PMOS load transistors M3 and M4. The input is V_{in} and the output is V_{out} . A feedforward path is connected from the input to the output through a capacitor C_F . The second stage is a common-source stage with NMOS transistors M5 and M6, and PMOS load transistors M7 and M8. The input to the second stage is V_{out} and the output is V_{out2} . A feedforward path is connected from the input to the output through a capacitor C_C . The circuit is biased with V_{dd} and V_{ref} . The bias current I_{krum} is split into $I_{krum}/2$ and I_{krum} . The output current is I_{NMOS_FEED} and I_{PMOS_FEED} . The output voltage is V_{casN} .

The RD53 synchronous frontend


Discriminator

 

Latch (auto-zeroing circuit)

 

Calibration injection circuit

 

- Same for all frontend flavours
- Differential DC voltages, to reduce noise
- Linearity confirmed by measurements


Trigger

Triggering

- One trigger pulse allowed in each 40MHz BX_CLK cycle
- Two possibilities:
 - User-generated via the command decoder in the periphery
 - External
 - No internal self-trigger

Book keeping

 - Trigger pulse
 - periphery: new entry in the TT
 - matrix: store hits within (programmed) latency
- Pixels also receive TT row number (trigger ID)
- The TT entry has: trigger ID, tag (5 bits set by user + 2 bits from BC counter*), BCID (internal counter)
- The user can reset the BCID
- Readout is data driven (FIFO): empty the TT as fast as possible



***The trigger table (TT) is 32-words deep
(5 bits row number)***

* the trigger signal covers 4 BC

 


Figure 1.3: Schematic of preamplifier