


#### **EMC** front-end Electronics

Valerio Bocci

INFN sezione di Roma

M.Bizzarri, C. Cecchi, P. Lubrano, A. Papi, (INFN Perugia) G. Chiodi, R.Faccini, R. Lunadei, L. Recchia, D. Ruggieri (INFN Roma)
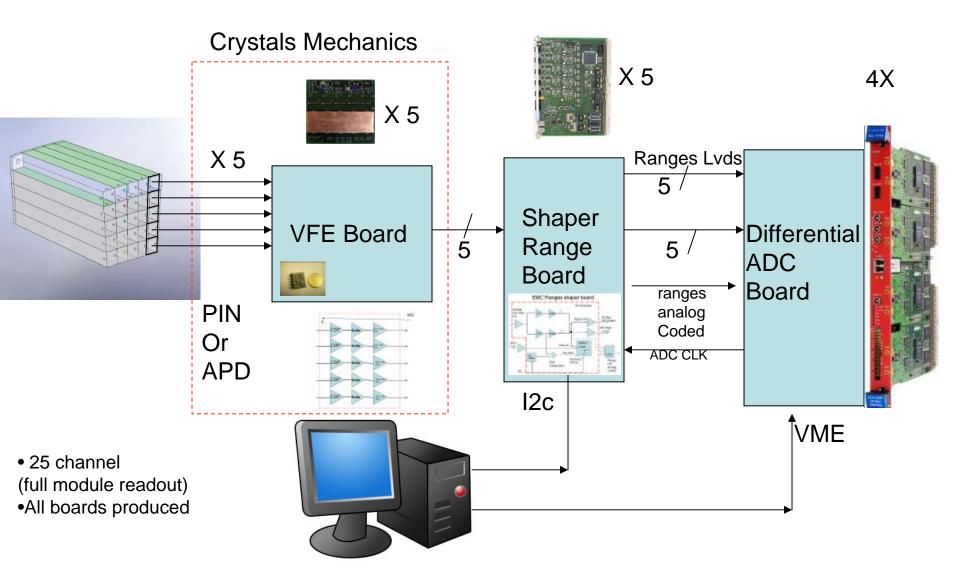
# Radout electronic for a 25 crystals tower




#### Very Front End Board

- •EMC VFE Board
- •5 CSP Channels
- Enable to mount: Cremat, Hamamatsu,


Home Made CSP

•HV distribution

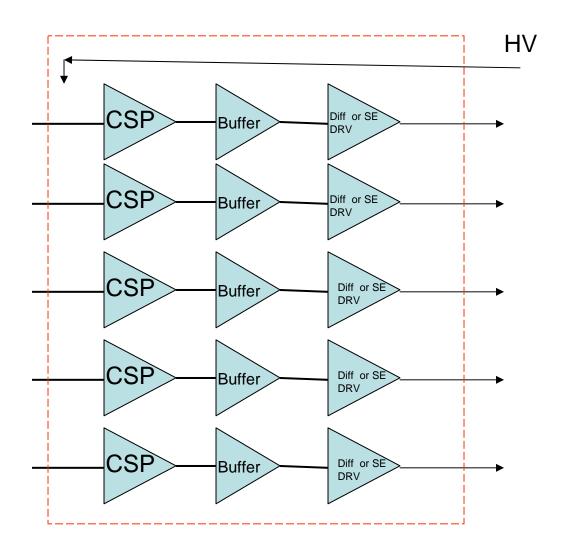
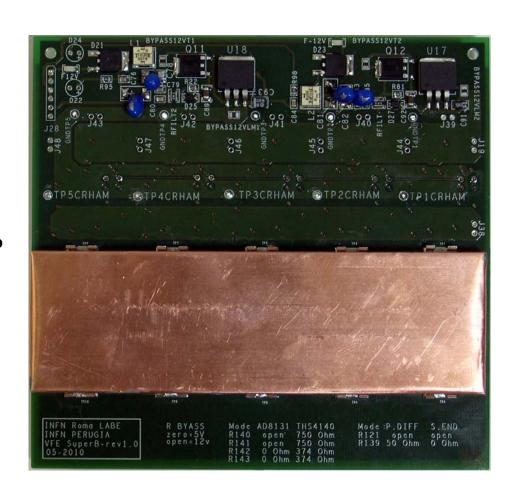
## Very Front End Board

- •EMC VFE Board
- •4 Layers
- •5 CSP Channels
- •Enable to mount:
- Cremat, Hamamatsu, Home Made CSP
- •HV distribution
- Mounted on crystals
- •Interface with EMC range Board




# Three Type of CSP under evaluation

Cremat 1.4 V/pC



- Availibility
- Perfomance
- •cost


Hamamatsu 1 V/pC

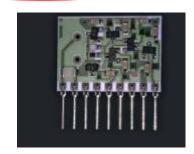

Homemade 1 V/pC




### **EMC** Ranges shaper board

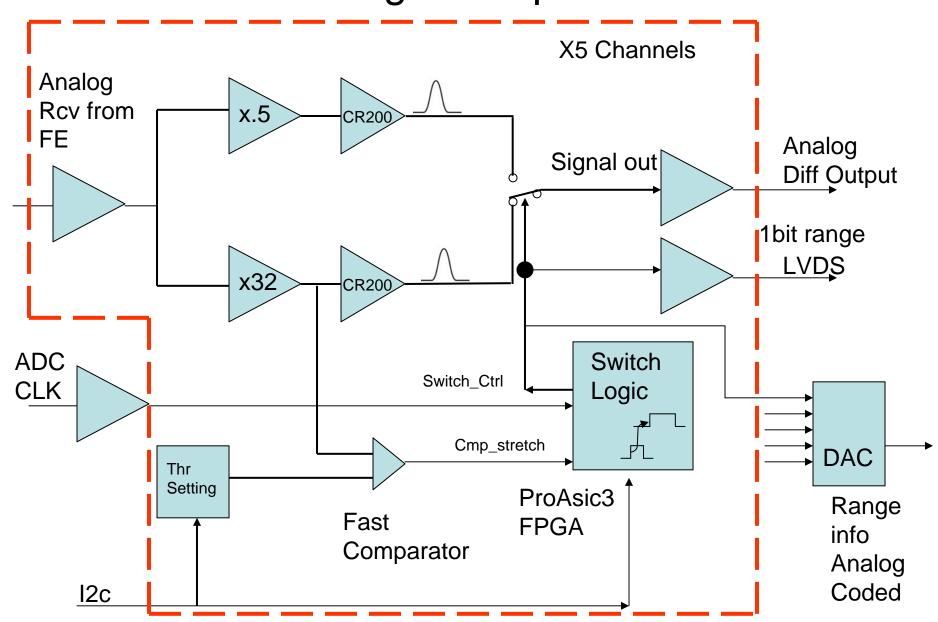
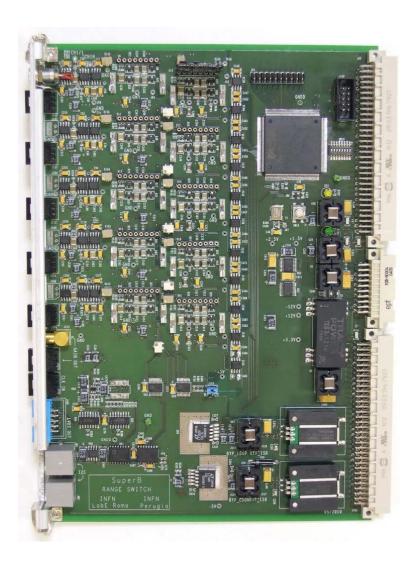
## **EMC** Range Board


- •EMC Range Board
- •8 Layers VME size
- •5 Channels Analog Differential input
- •5 Channles Analog Differtial output
- •1 Main clock input
- •Long line I2c control input
- Range info analog coded
- •Lvds output for Range bit





# EMC 5 Channel readout protoype (single ended ADC)


#### Crystals Mechanics

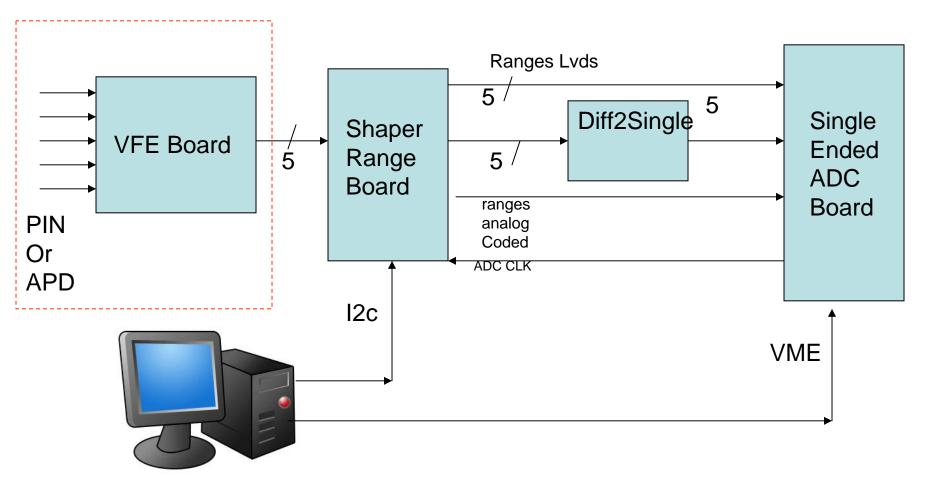

### Differential2Single ended Board

Utility board to convert differential signals to Single Ended signals.

Four layer PCB 5 channel

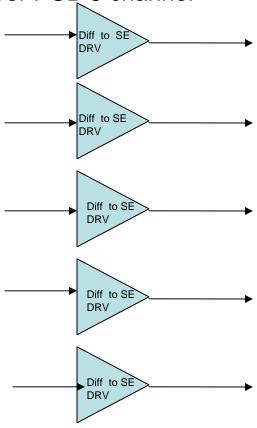



## BTF setup











# Front Panel Cabling

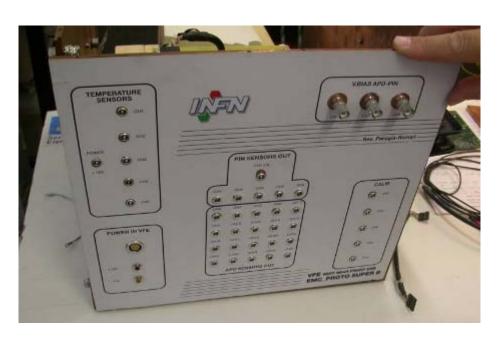



VFE inside the copper Box 1/2



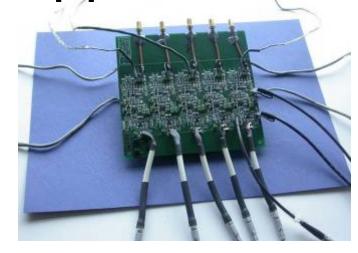





## VFE inside the copper Box 2/2



