

# Pixel analog part design in TIIMM for STRONG project

---

Weiping REN  
2020.06.05



# Contents

---

**01**

**STRONG strategy & requirements**

**02**

**TIIMM-0 Sensor introduction**

**03**

**TIIMM-1 Analog pixel studies**

**04**

**New pixel architecture with ADC**

**05**

**Conclusion**

## ■ The TIIMM

The TIIMM ( Tracking and Ions Identifications with Minimal Material budget ) project in STRONG aims to create a new class of instrument combining precision tracking and energy loss measurement in conditions where minimizing the crossed material is mandatory.

## ■ TIIMM expectations and status


- 1st prototype (TIIMM-1) in late 2020
- 2nd prototype (TIIMM-2) in 2021-2022
- Both are small size prototypes
- Status: preliminary prototype (TIIMM-0) submitted with MIMOSIS-1.

## Requirements for hadron physics

- Particles to be detected: protons to Oxygen ions (200-400 MeV/u) and consider proton close to 1 GeV
- Spatial resolution 5 to 10  $\mu\text{m}$
- Hit rate few kHz/cm<sup>2</sup> (in any case < MHz/cm<sup>2</sup>)
- Sensor surface area few cm<sup>2</sup> (2x2 or 1x3 probably OK)
- Power dissipation compatible with air cooling < 200 mW/cm<sup>2</sup>
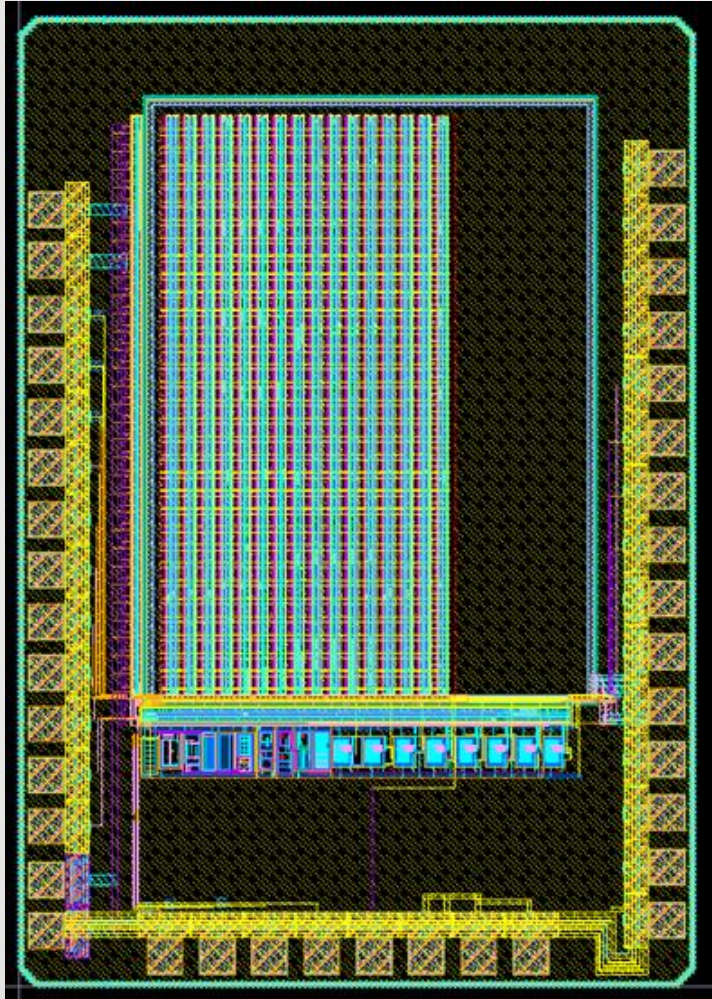
## Sensor specifications

- Signal charge assuming 25  $\mu\text{m}$  sensitive thickness: 500 e<sup>-</sup> to 500 000 e<sup>-</sup> (1-1000 dynamic ← to be confirmed)
- Digitization over 4 to 6 bits (4 will be probably not enough due to dynamic...)
- Pixel pitch 20 to 40  $\mu\text{m}$  (the smaller, probably the better)
- Frame rate 1-10 kHz  $\leftrightarrow$  integration time 100 to 1000  $\mu\text{s}$  (if  $T_{\text{int}} \sim \mu\text{s}$  possible, better)




TIIMM0 sensor layout

- **CMOS Monolithic Active Pixel Sensor**
- **Design in TowerJazz 180 nm process**
- **Submitted in March, 2020**
- **Chip area: 2.2 mm \* 1.5 mm**
- **Matrix: 32 (rows) \* 16 (columns)**  
*(the last column has the analog output for test)*
- **Pixel pitch: 40 μm**
- **Position and energy measurements**




# TIIMM-0 - Pixel structure

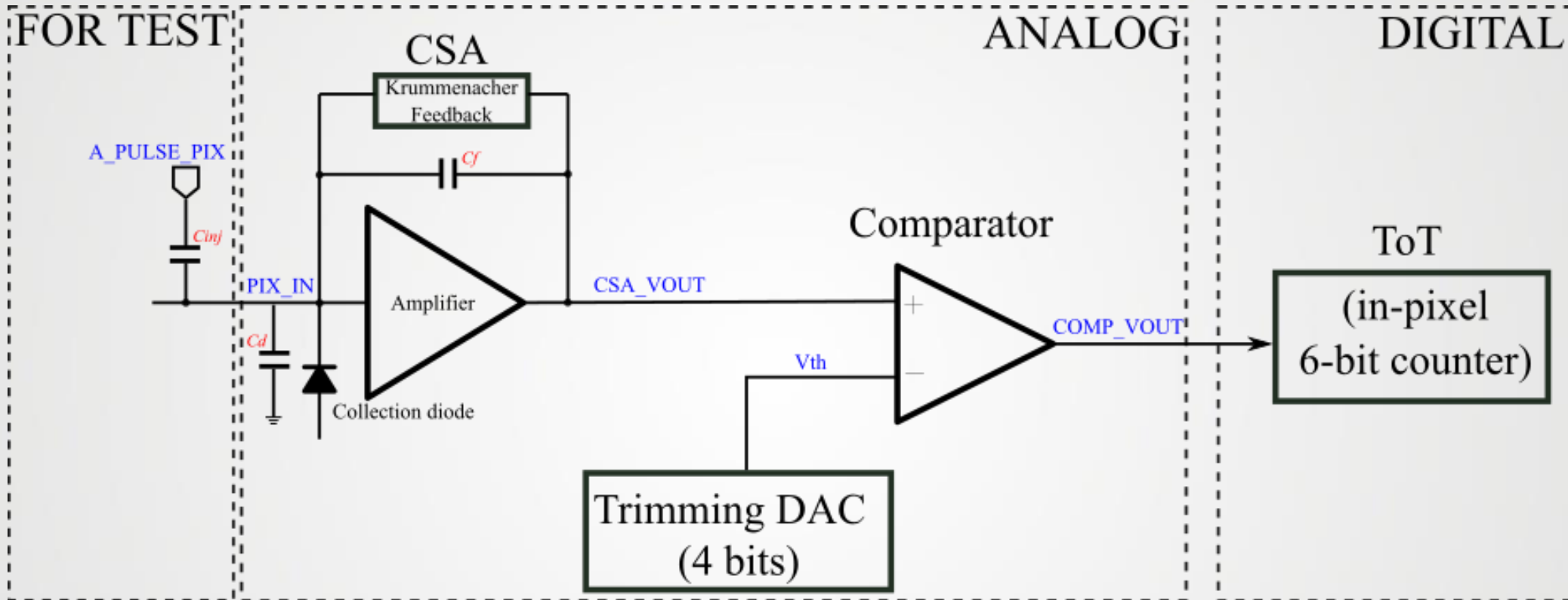

- **TOT (6 bits)** – 6 bits register in pixel
- **Trimming DAC (4 bits)** - for threshold adjustment
- **Possibility to mask pixels**

# TIIMM-0 - Pixel layout design

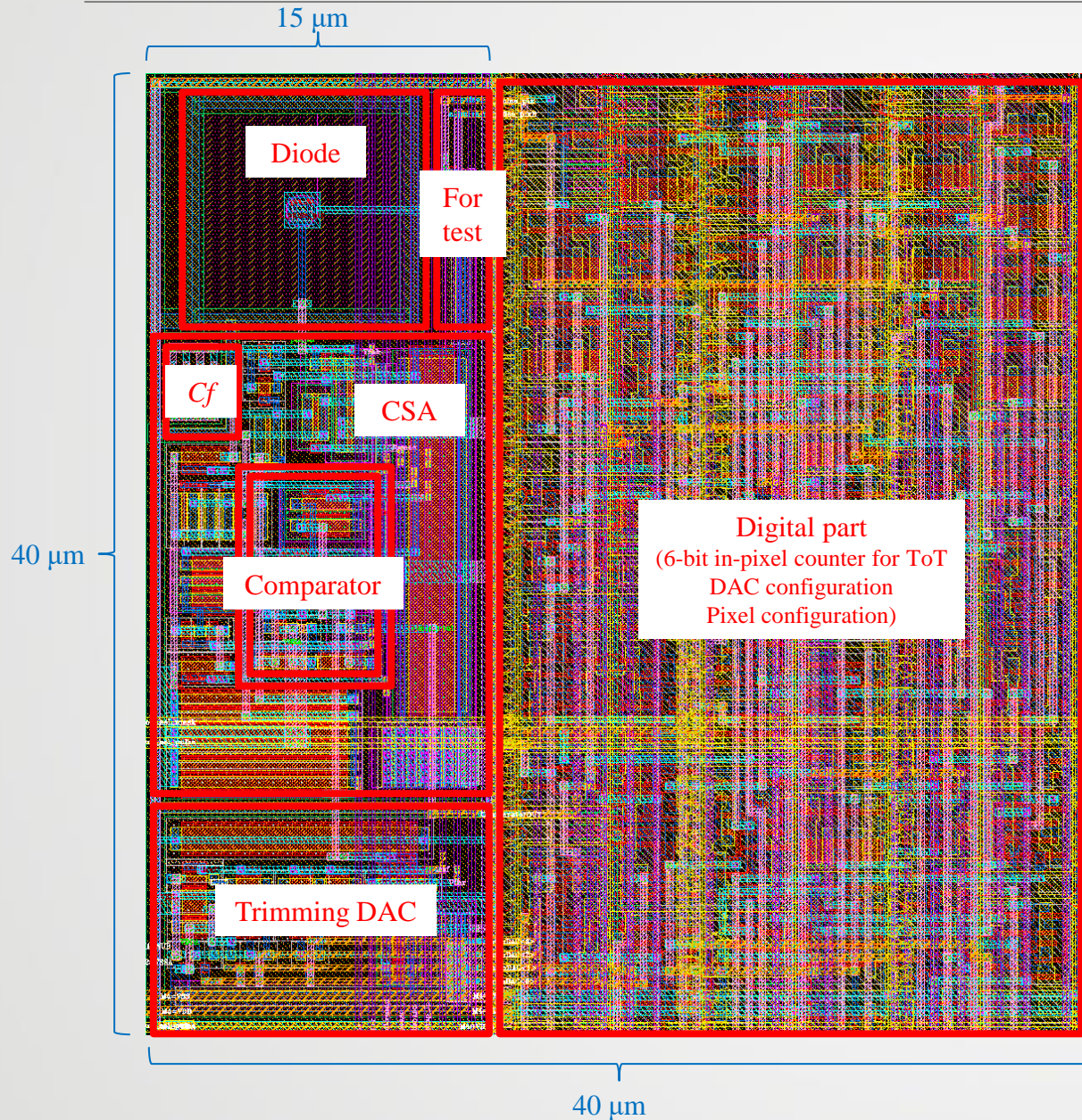


Pixel size: 40 μm \* 40 μm


Analog part: 40 μm \* 15 μm

Digital part: 40 μm \* 25 μm
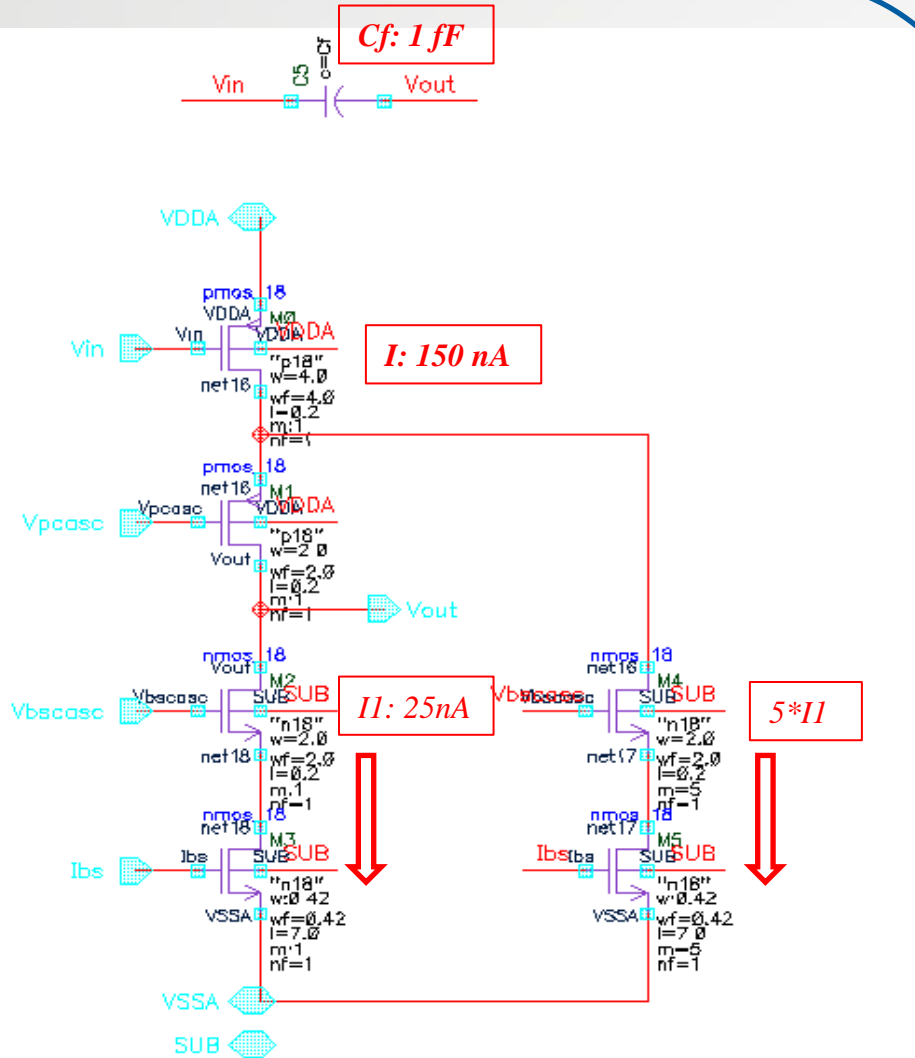
# TIIMM-0 - CSA with Krummenacher feedback



Amplifier


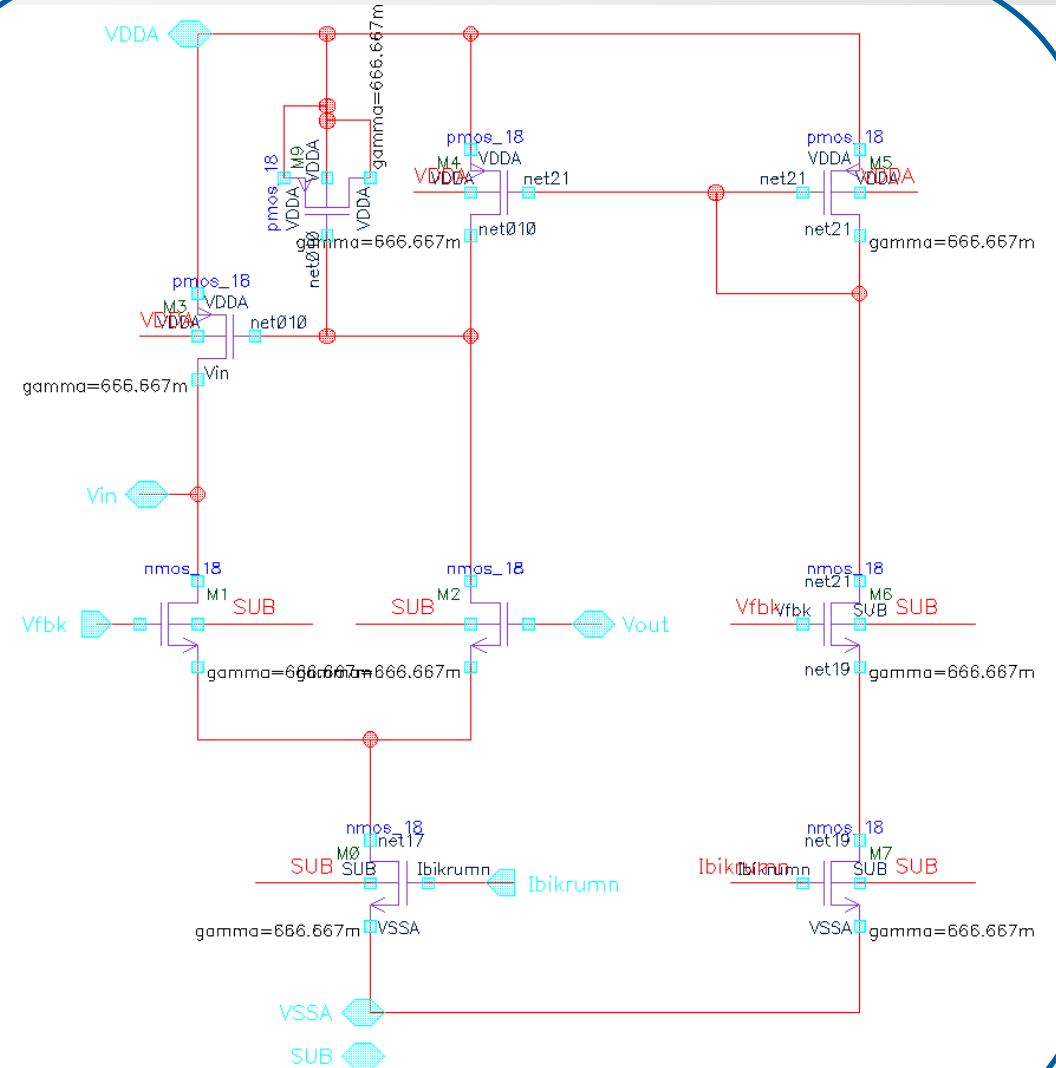


Krummenacher Feedback




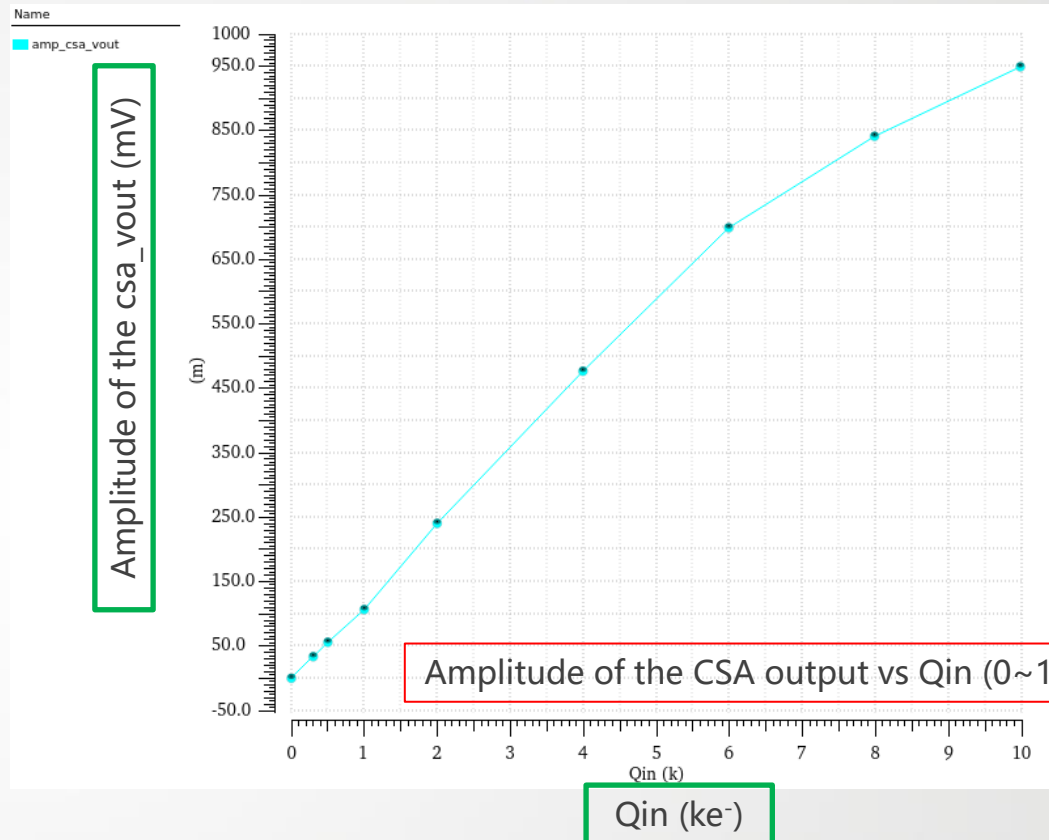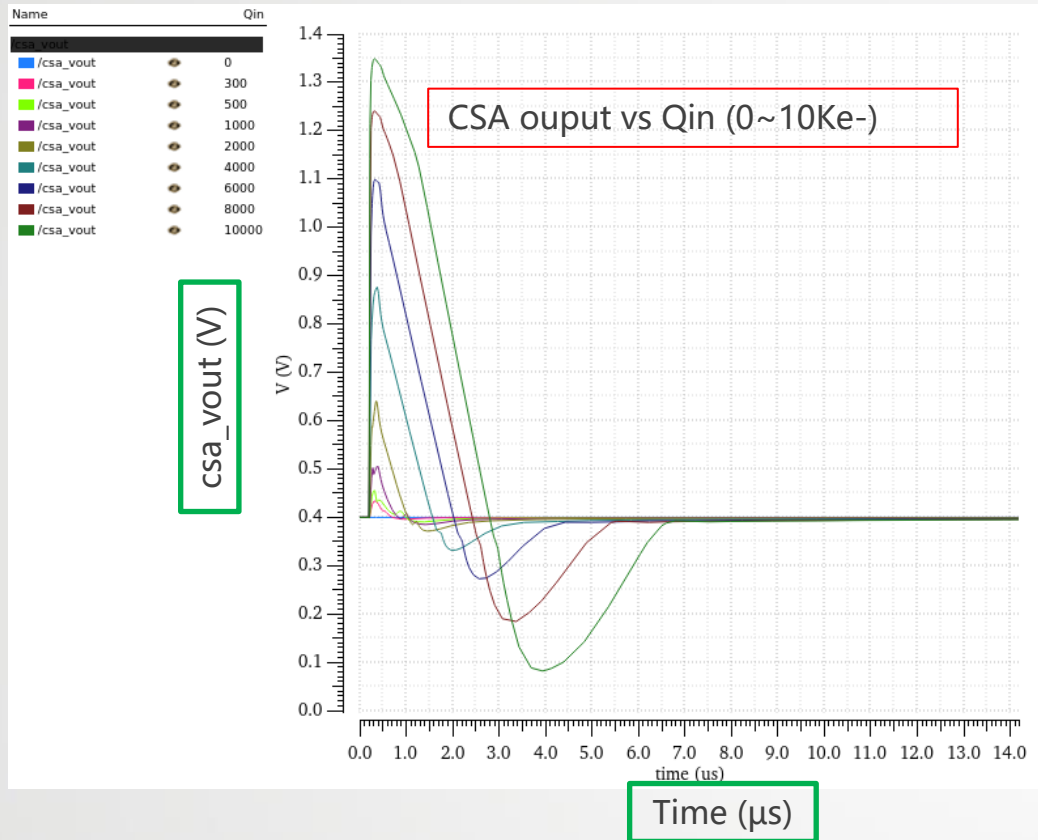
# TIIMM-0 - Simulation performance of CSA





- $C_f = 1\text{fF}$ ,  $C_d = 2\text{fF}$
- Gain about  $120\text{ mV/ke}^-$ ,  $\text{ENC} = 42\text{ e}^-$
- There is a overshoot problem in the CSA design.

## TIIMM-0 - Performance of CSA (corner simulation)

<b>Q<sub>in</sub>=500 e<sup>-</sup></b>	<b>NOM 27°C</b>	<b>FAST 0°C</b>	<b>SLOW 85°C</b>
CSA Power[nA]	146.8	150.2	149.9
ENC[e <sup>-</sup> ]	41.98	39.99	43.93
Amplitude of the CSA output[mV]	55.89	55.68	60.09
Baseline of the CSA output[mV]	399.7	399.8	399.3



# TIIMM-0 – Performance of the CSA (MC simulation|Mismatch)

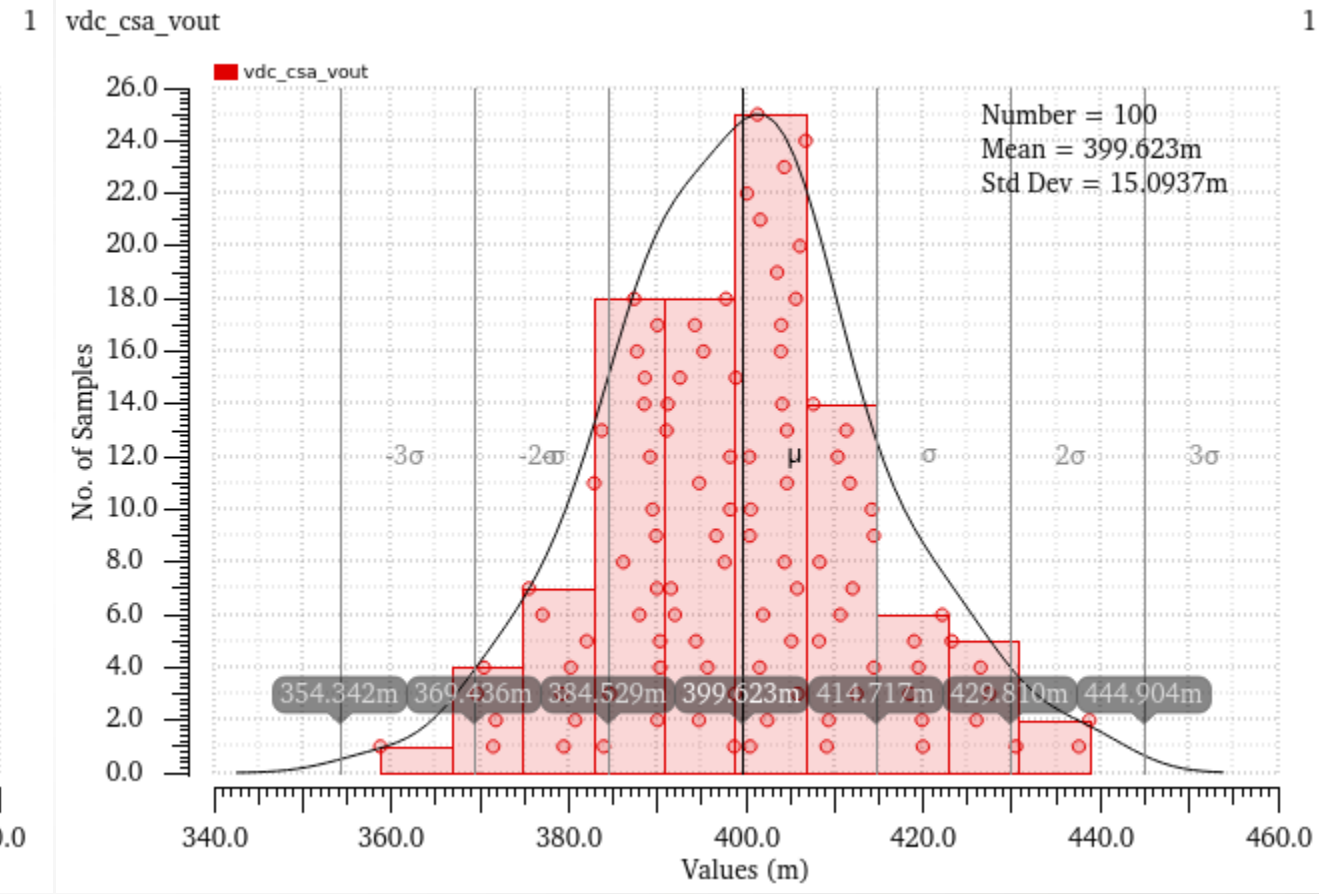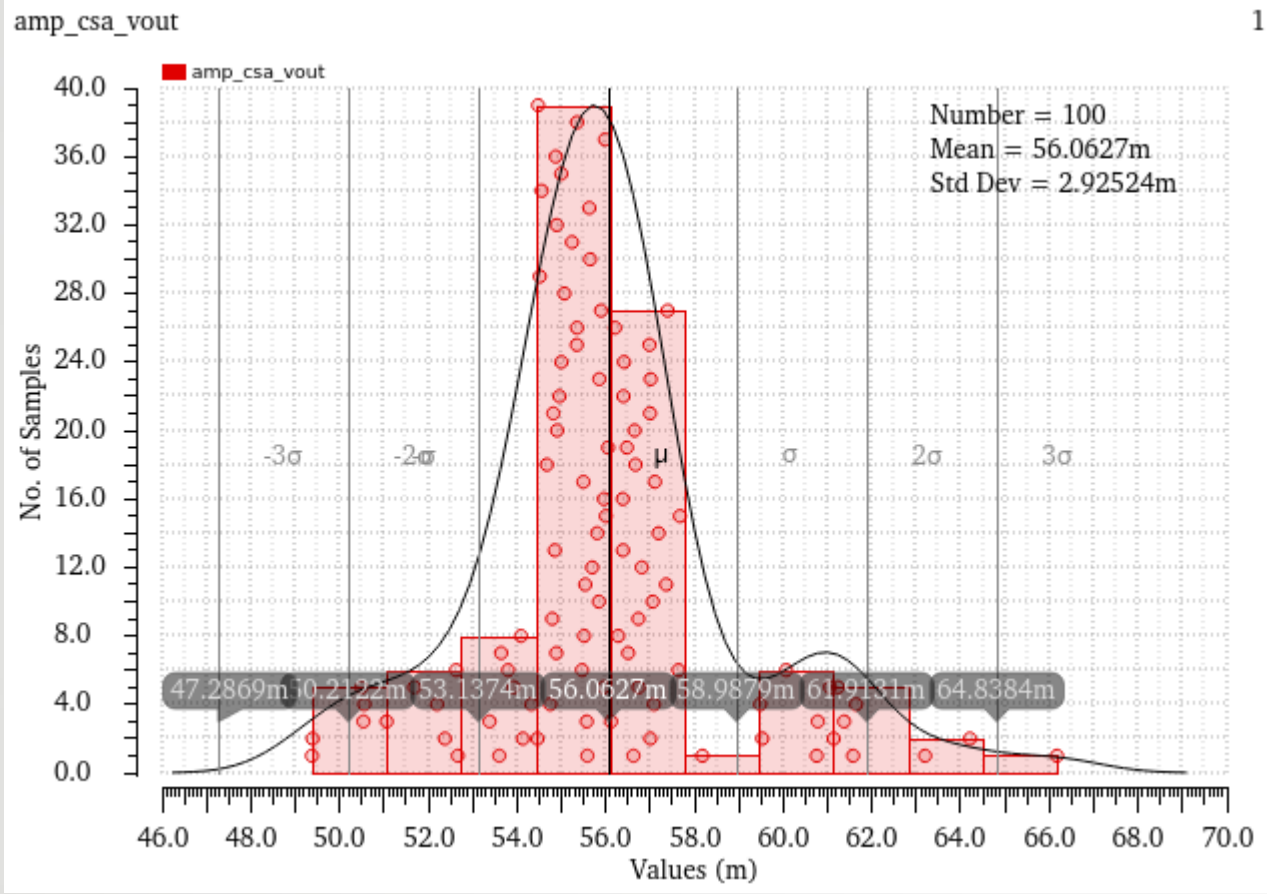


Monte Carlo simulation, spread of the amplitude of the CSA output (Qin=500 e-)


Monte Carlo simulation, CSA output baseline offset

■ Offset spread of the CSA  
Sigma: 15.09 mV  
Range: 359 mV ~ 440 mV

# TIIMM-0 – Performance of the CSA (MC simulation|Process)

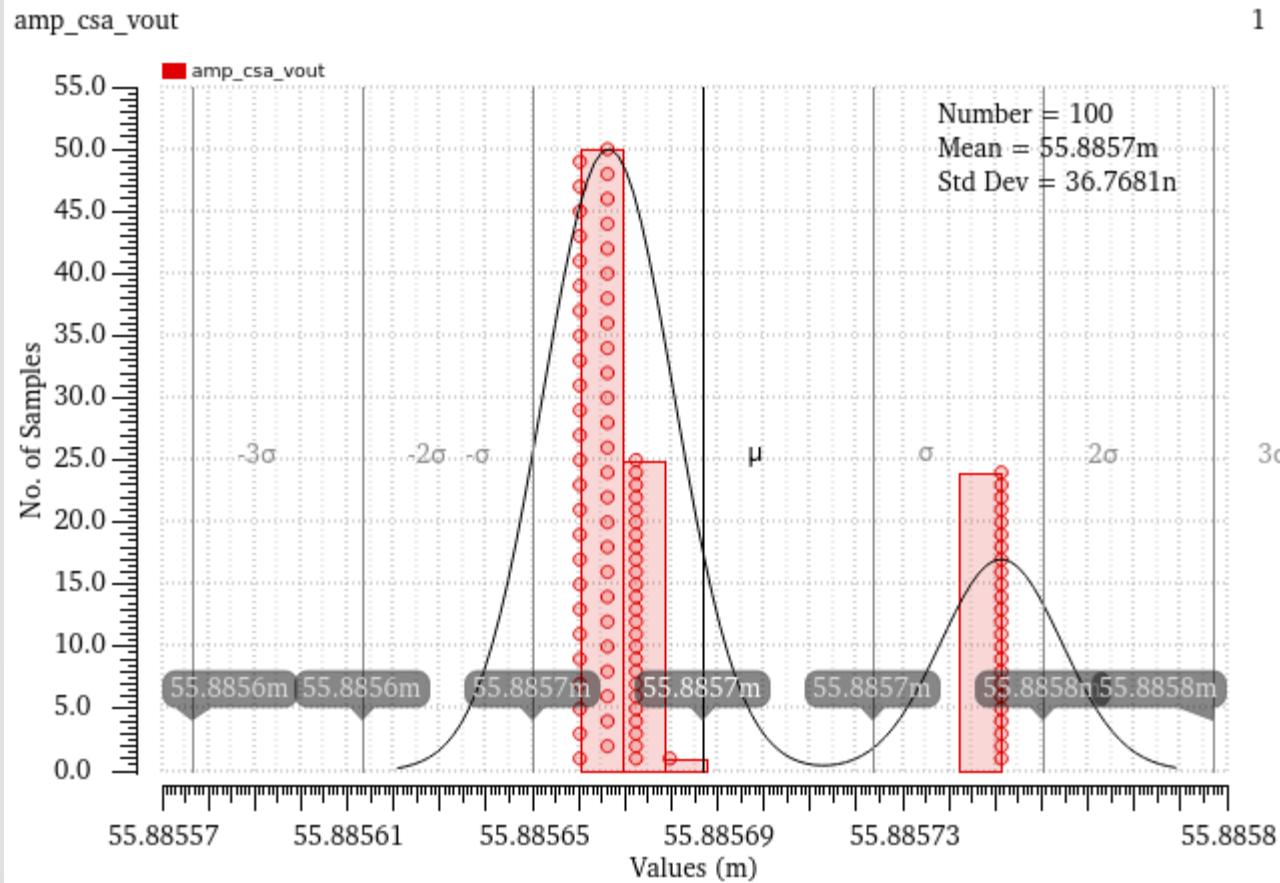


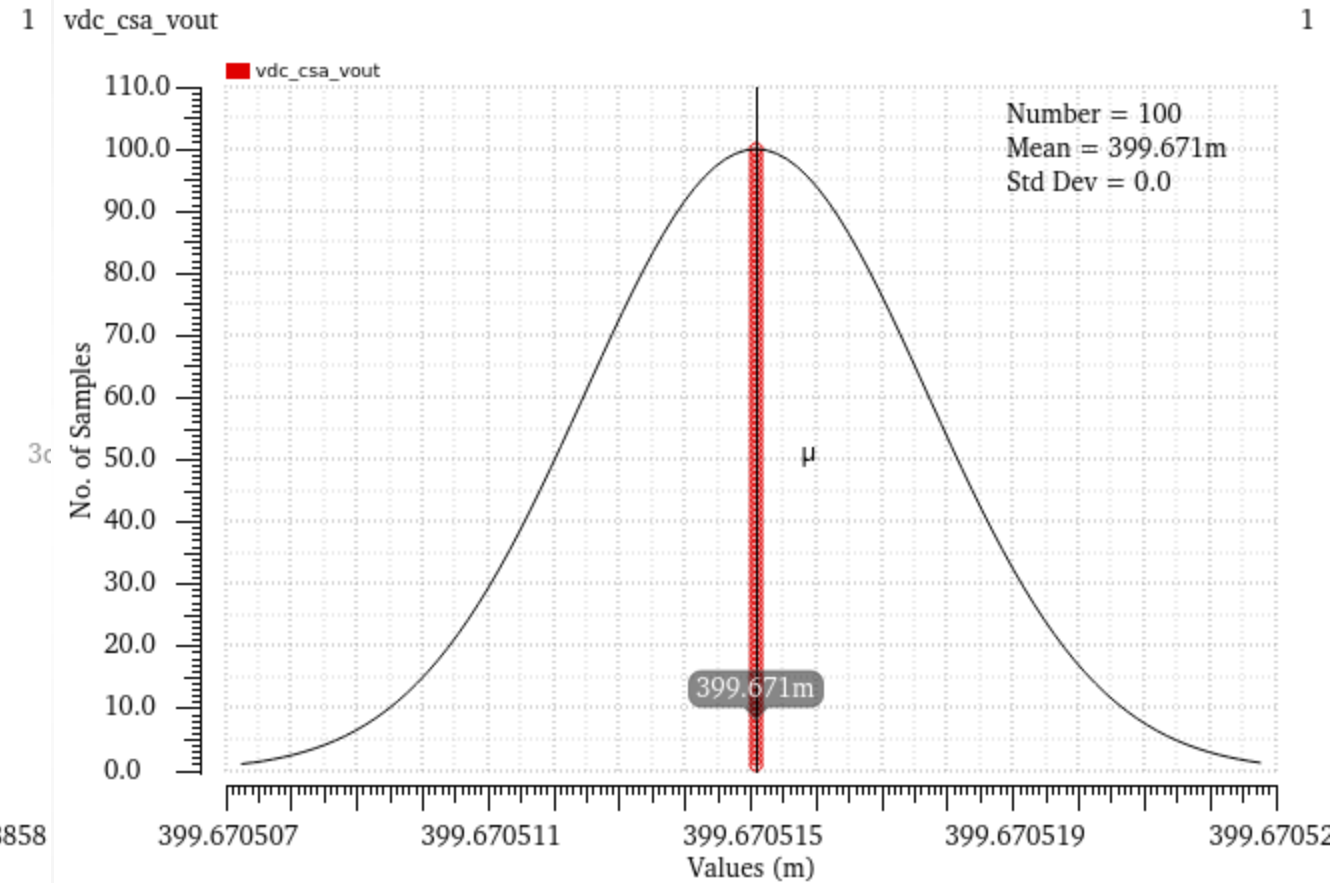Monte Carlo simulation, spread of the amplitude of the CSA output (Qin=500 e-)



Monte Carlo simulation, CSA output baseline offset

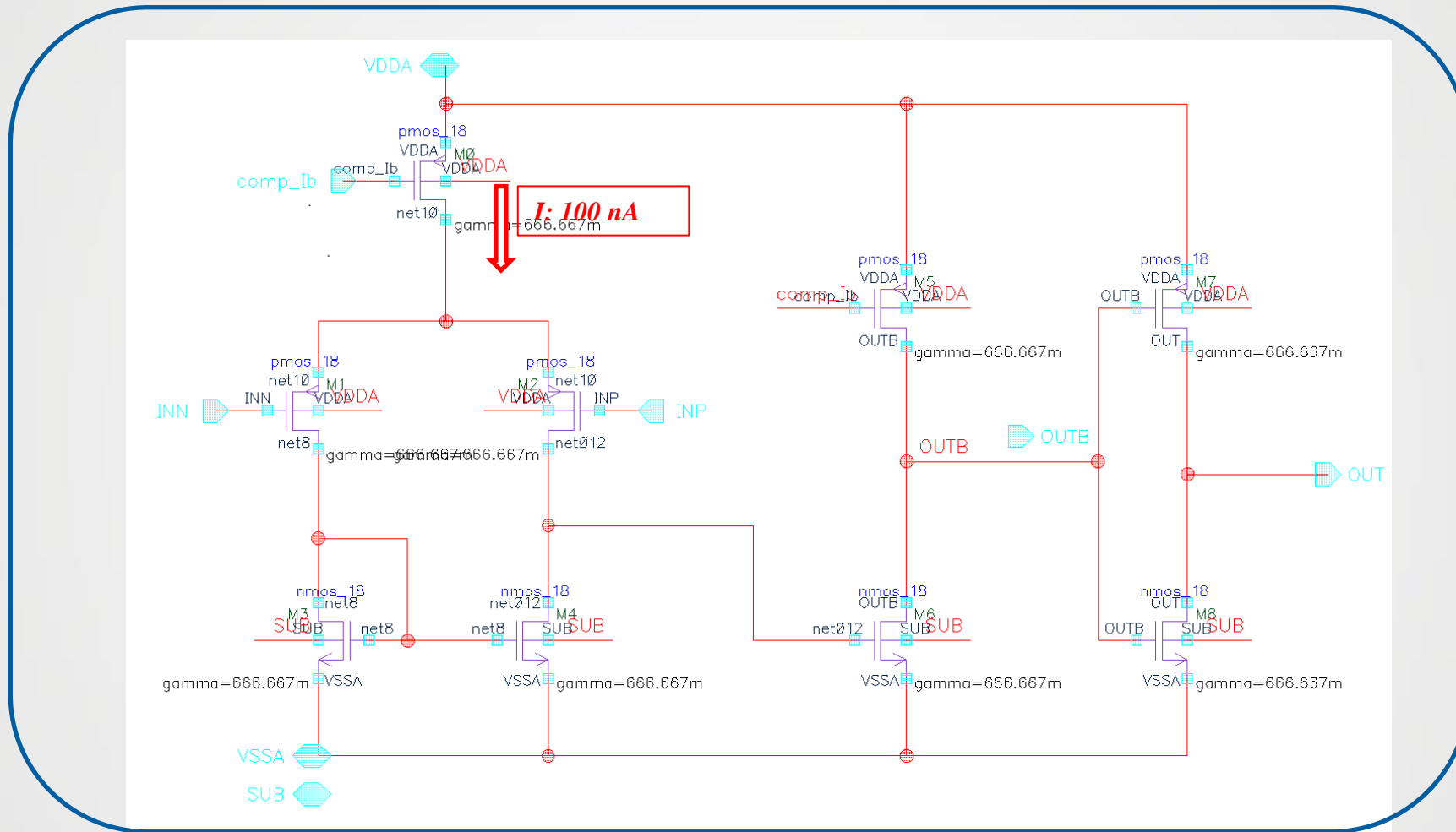
■ Offset spread of the CSA baseline  
Sigma: 0 mV



- The comparator is designed with a two stage amplifier and an inverter to form the digital signal.



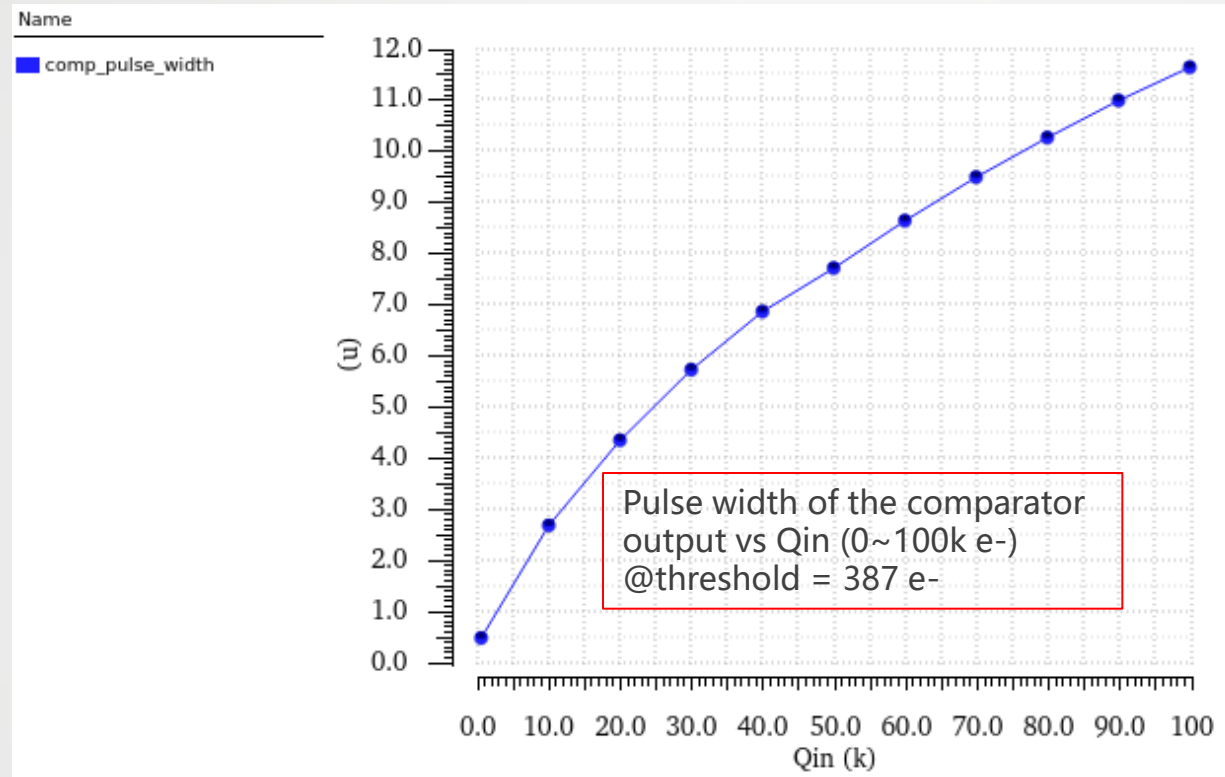
# TIIMM-0 - Pulse width vs Qin (0~100Ke-)



- The pulse width (0.5  $\mu\text{s}$ ~12  $\mu\text{s}$ ) increase with the Qin(from 0 to 100 Ke-).
- Threshold=387 e-.
- ToT output is not linear (at least at low Qin)  $\rightarrow$  calibration needed.


# TIIMM-0 – Trimming DAC

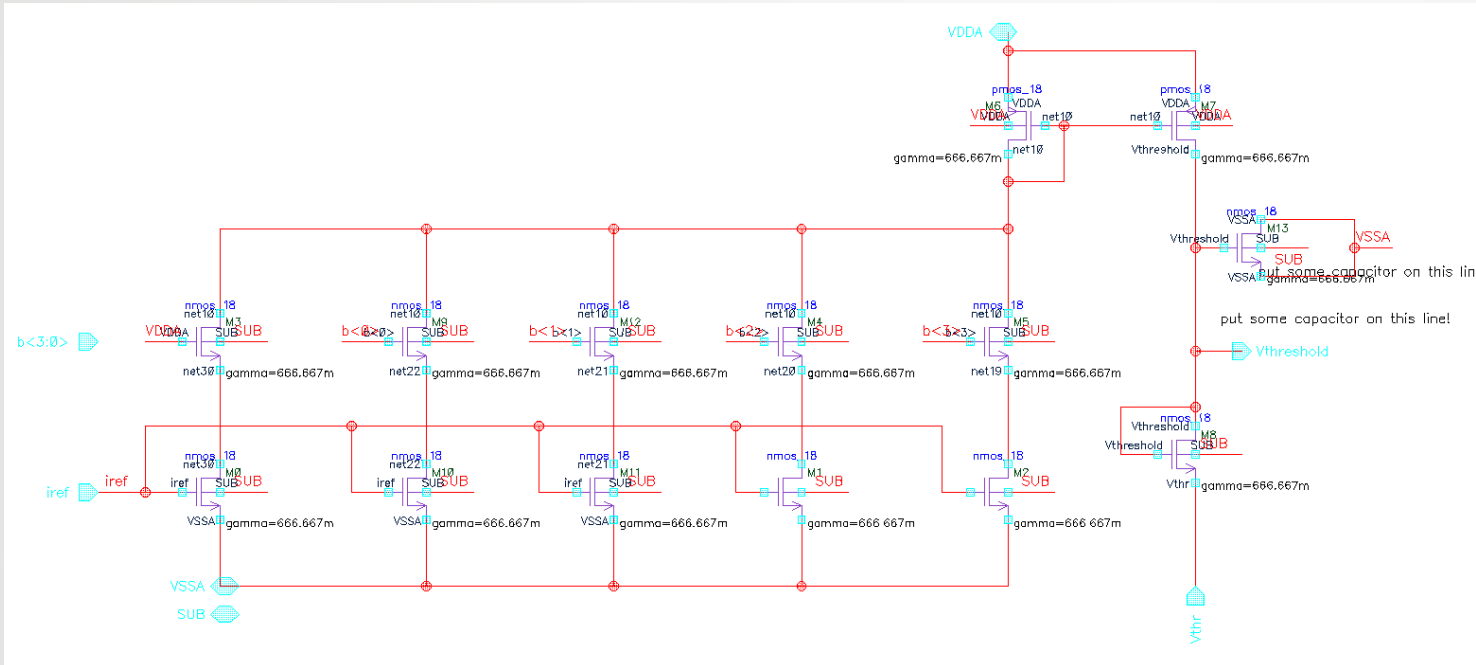

- The Trimming DAC provides the adjustable threshold for the Comparator to treat with the problem of the offset of the CSA
- 4 bits
- Range: 331 mV ~ 473.8 mV (cover the offset of the CSA)

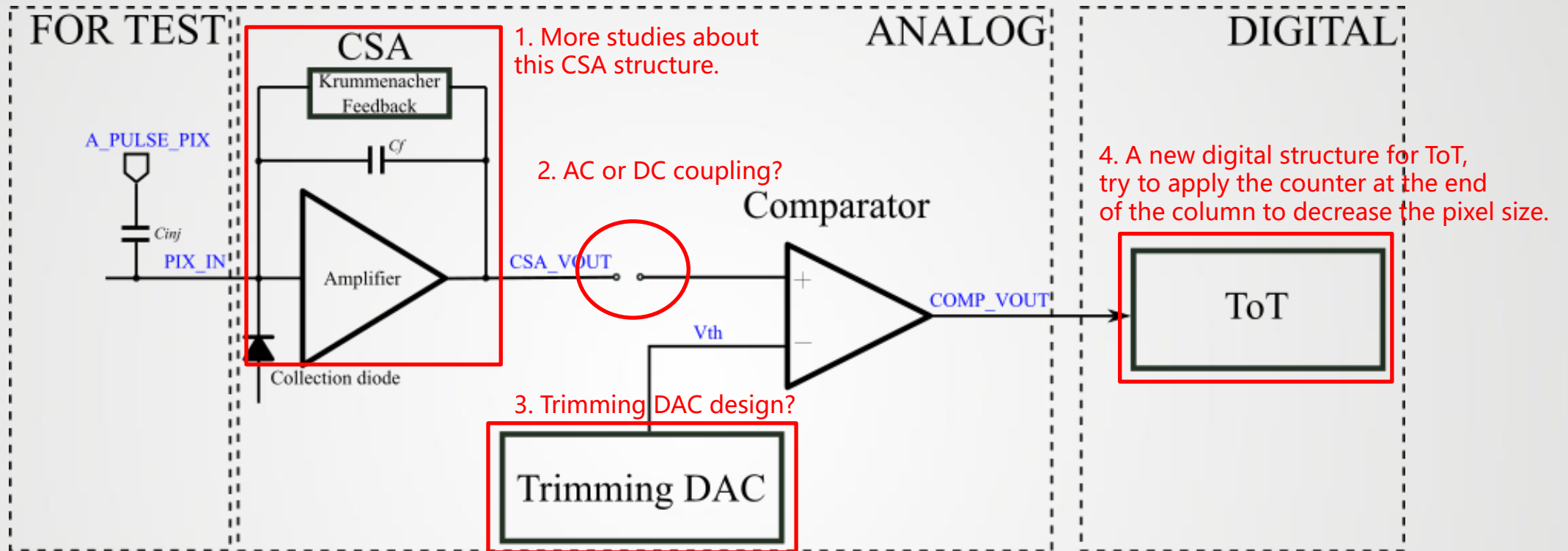
- $ENC = 42 e^- \rightarrow$  is that good enough for our project?
- ToT output is non-linear  $\rightarrow$  require calibration.
- Resolution on  $Q_{in}$  varies non-linearity with  $Q_{in} \rightarrow$  input to physics simulation for cross check.
- In this design, the trimming DAC can cover the offset range of the CSA. But it only has 4 bits. Its performance needs to be verified by chip test.








- In this design, we want to apply this **new architecture of amplifier**. This amplifier structure can get higher gain which can reduce the ENC.
- Due to the spread of the CSA output baseline is large, and it is common in pixel sensor. We are considering about using **AC coupling** between CSA and comparator or a **trimming DAC** with better performance to reduce the threshold dispersion.
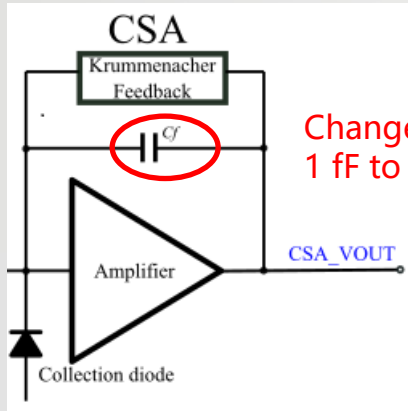
# TIIMM-1 - CSA with Krummenacher feedback





Change from 1 fF to 3 fF

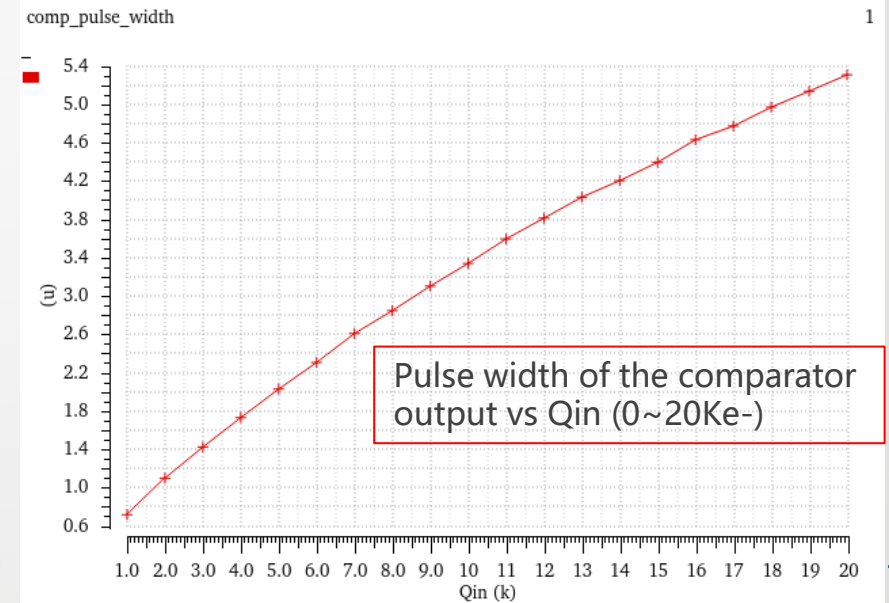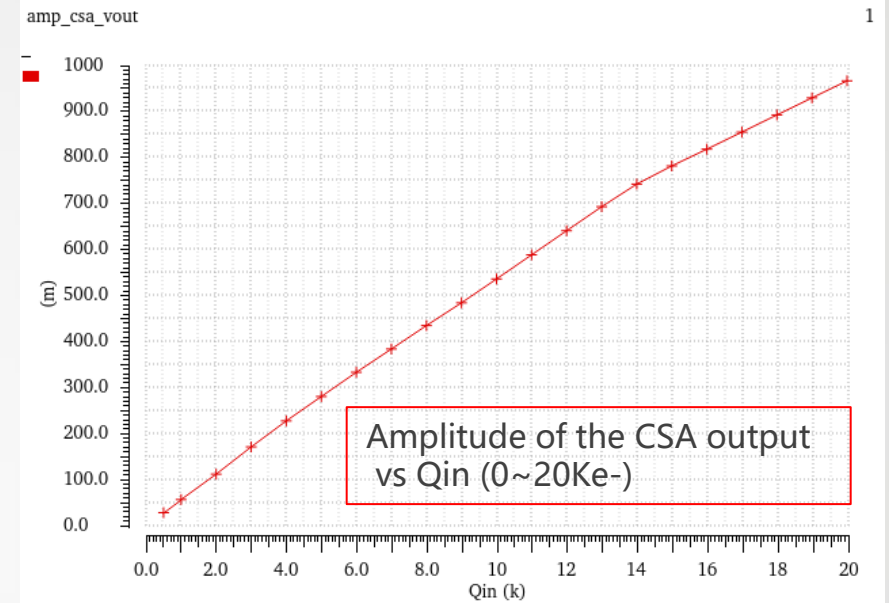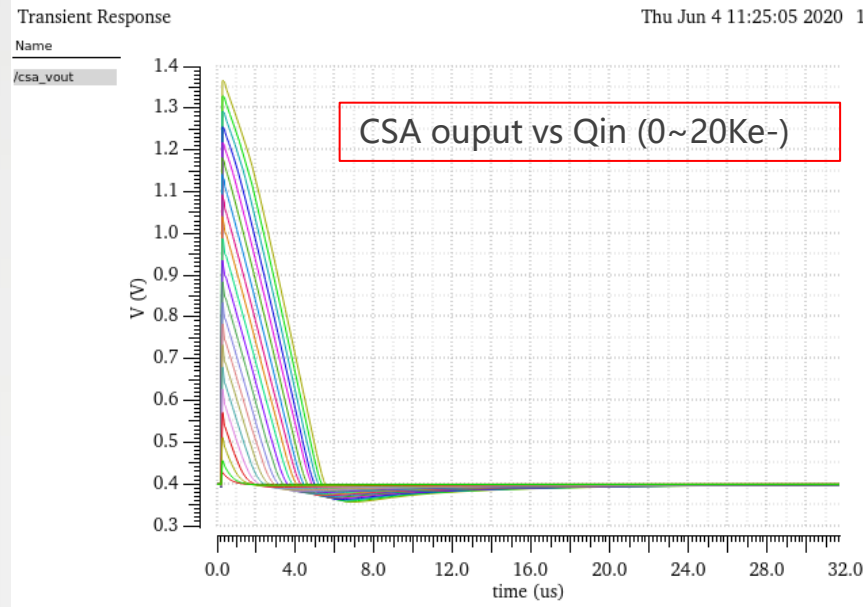

- $C_f=3$  fF(In TIIMM-0, it is set as 1fF)
- ENC=52 e-
- At charge range: 0~20k e-
  - 1) The overshoot problem of the CSA output improved a lot.
  - 2) The pulse width of the comparator shows a better linearity performance.

# TIIMM-1 - AC coupling

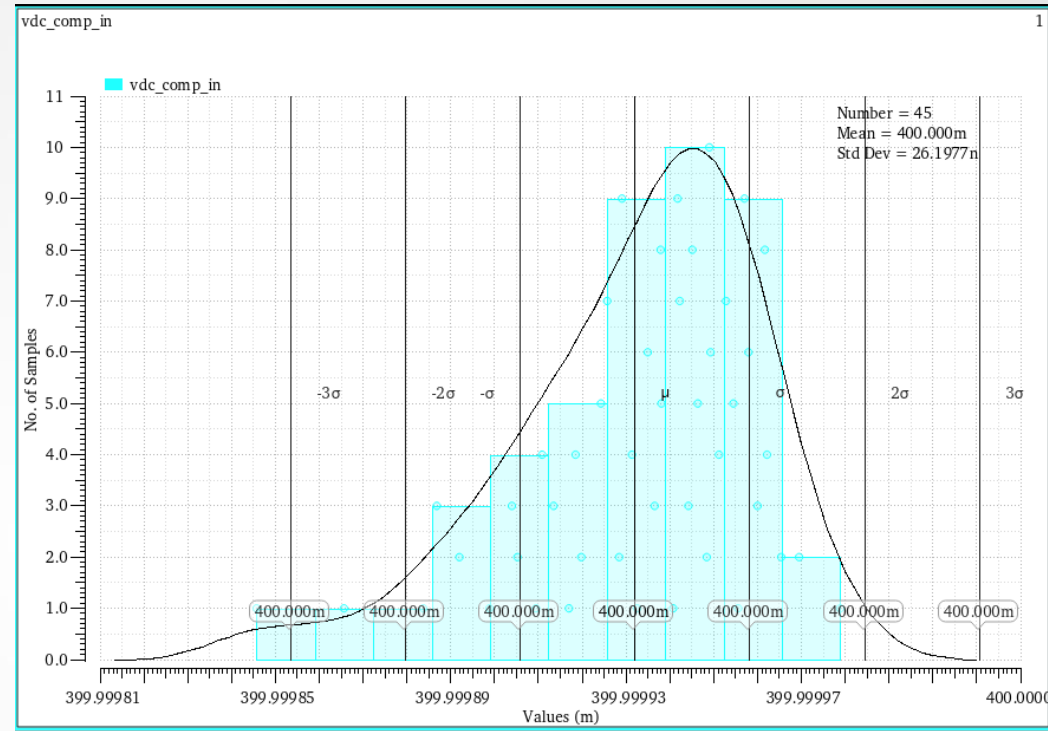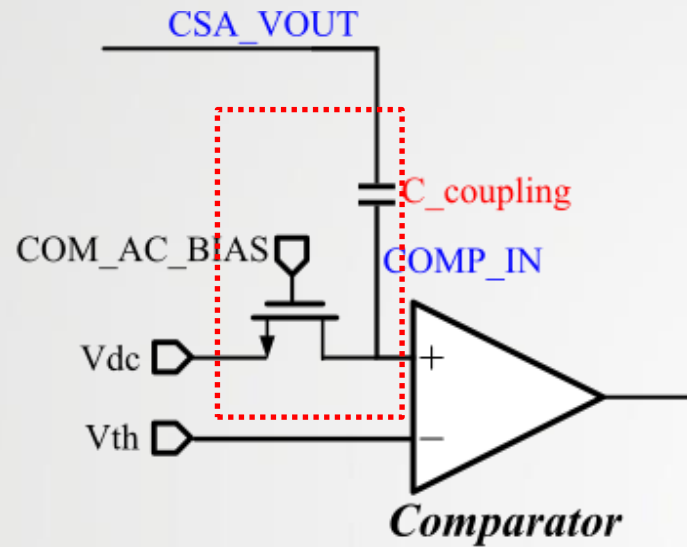

- Add capacitor between CSA and comparator to realize AC coupling (consuming an area for capacitor) . And the DC-level will be provided by a reference voltage  $V_{dc}$  through a NMOS transistor. The simulation shows that the spread of the COMP\_IN after the capacitor is  $\sigma = 26$  nV.
- But the comparator will still bring offset even though we use AC-coupling to eliminate the pixel-to-pixel baseline spread (threshold offset). Thus we still need a trimming DAC afterwards to reduce the offset of the comparator. AC-coupling + Trimming DAC (simple one, only used to reduce the offset of the comparator)
- Or DC-coupling + Trimming DAC (high performance)

# TIIMM-1 - Trimming DAC (reference paper)

## A multi-level offset trimming DAC

- 7-bit trim DAC for tuning  $I_{DAC}$  current
- Two different ways to control the tuning range (bit br or bit bb)
- Addition of an extra offset at the input from outSH\_ref line (bits bosf<0:1>)

## Performance

- Pixel-to-pixel baseline level spread before correction is about  $\sigma = 17$  mV rms. It is reduced to  $\sigma = 1.524$  mV rms (using only 7-bit trim DACs)


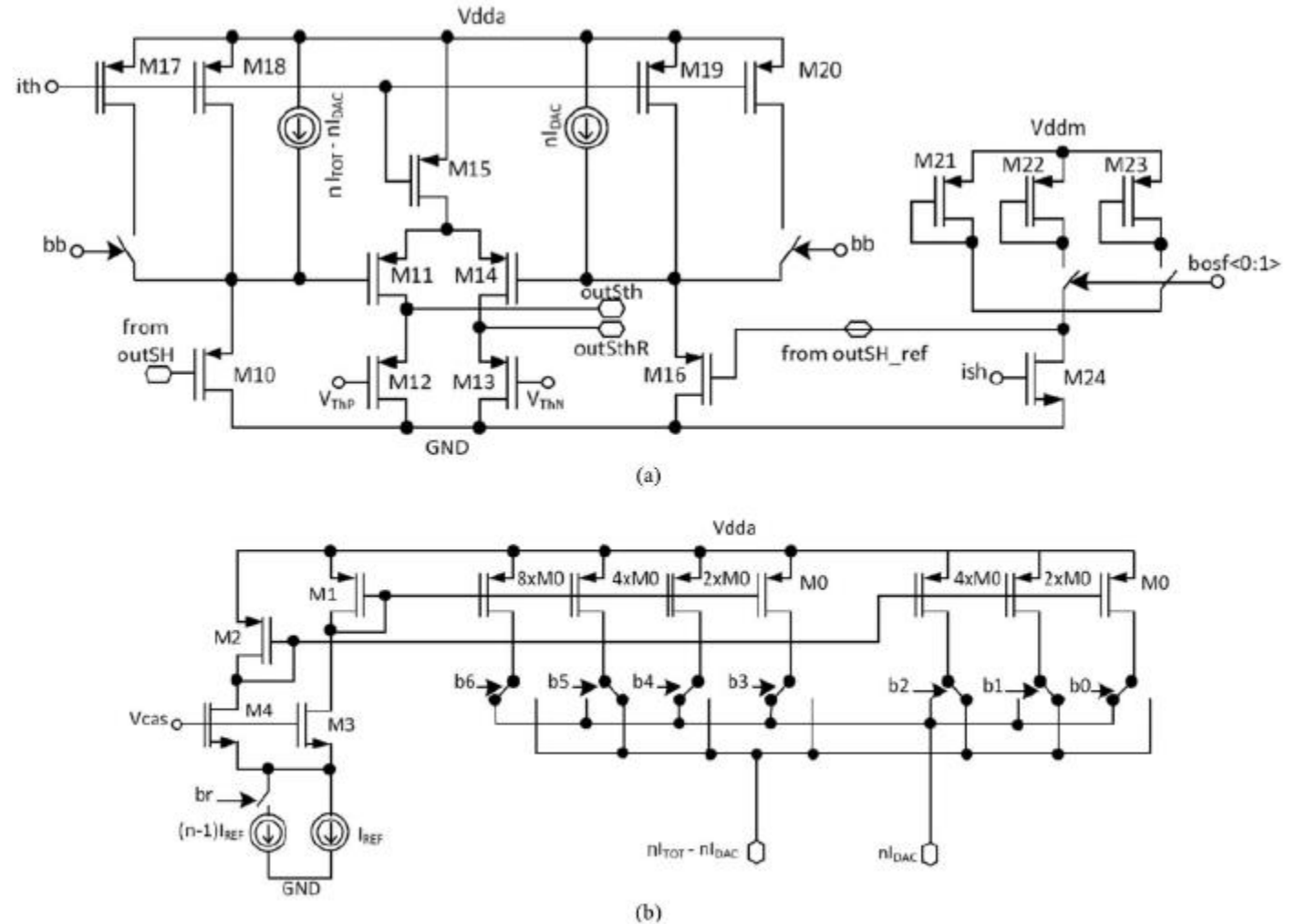


Fig. 7. (a) Circuit for applying the threshold voltage and offset correction-trim DAC is represented by two current sources, (b) simplified scheme of trim DAC ( $M0$  transistor dimensions are  $W_0/L_0 = 0.3 \mu\text{m}/2 \mu\text{m}$ ).

# ➤➤➤ New pixel architecture with ADC

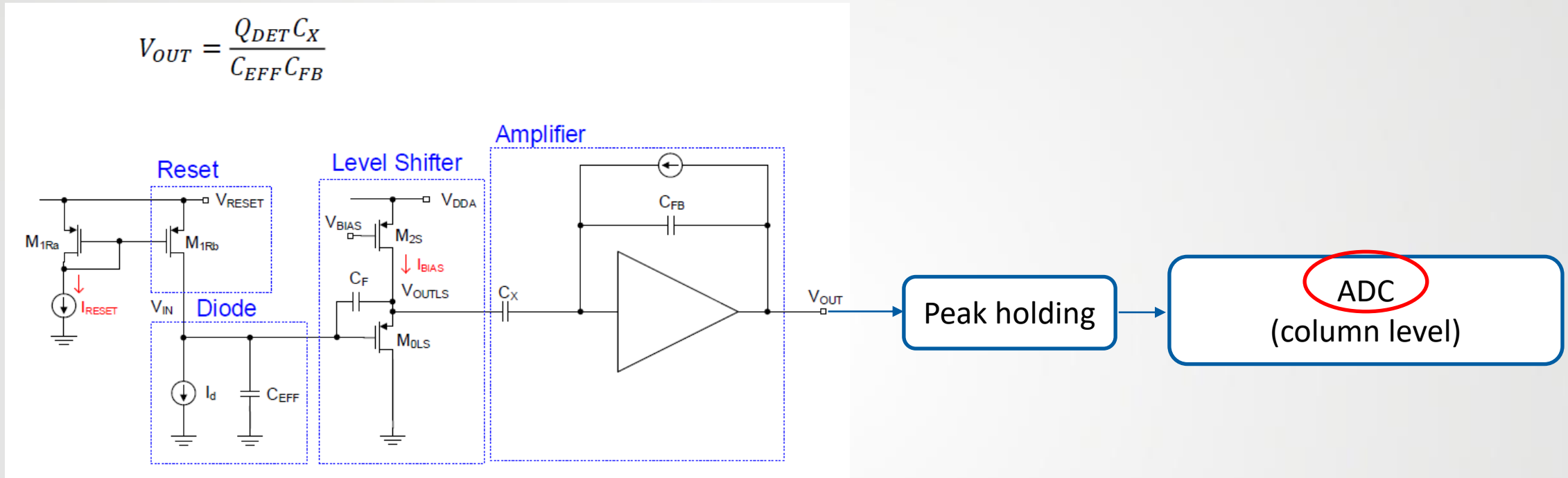

## ■ For the next prototype, if we will try the column ADC structure?

- Need peaking holding circuit in pixel.
- Reduce the area (In ToT structure, the register for ToT in the pixel consumes a large area)
- Column level, can get higher bits.
- The output amplitude of the Amplifier has better linearity vs input charge.
- The dynamic range is bound to be smaller with the ADC structure (unless we can switch the capacitance)



- The TIIMM-0 design has been summarized. The chip contains 32 rows and 16 columns with a pixel pitch of 40  $\mu\text{m}$ . A 6-bit ToT architecture has been applied for energy measurement.
- The ENC of the TIIMM-0 is 42  $e^-$ .
- The 4-bit Trimming DAC in TIIMM-0 provides the adjustable threshold for the Comparator to treat with the problem of the offset of the CSA. And the performance need to be verified through the chip test.
- In TIIMM-1, more studies about the amplifier were carried out.
- AC-coupling scheme between the CSA and comparator was proposed.
- A multi-level trimming DAC to solve the offset problem with calibration was presented (reference).
- ADC solution seems more complex, not considered for the time being.

*The end*

---

Thanks!

# Predicting ToT values (TIIMM-0 proto)

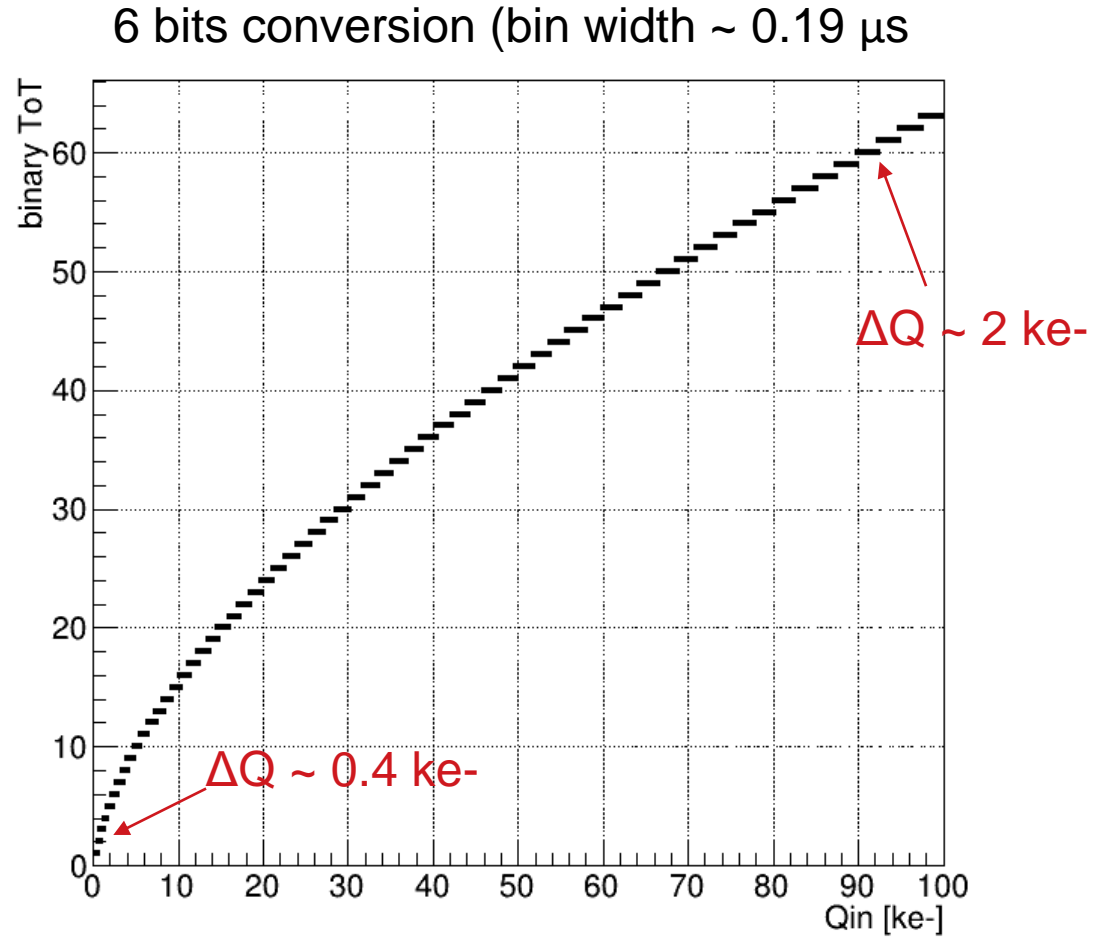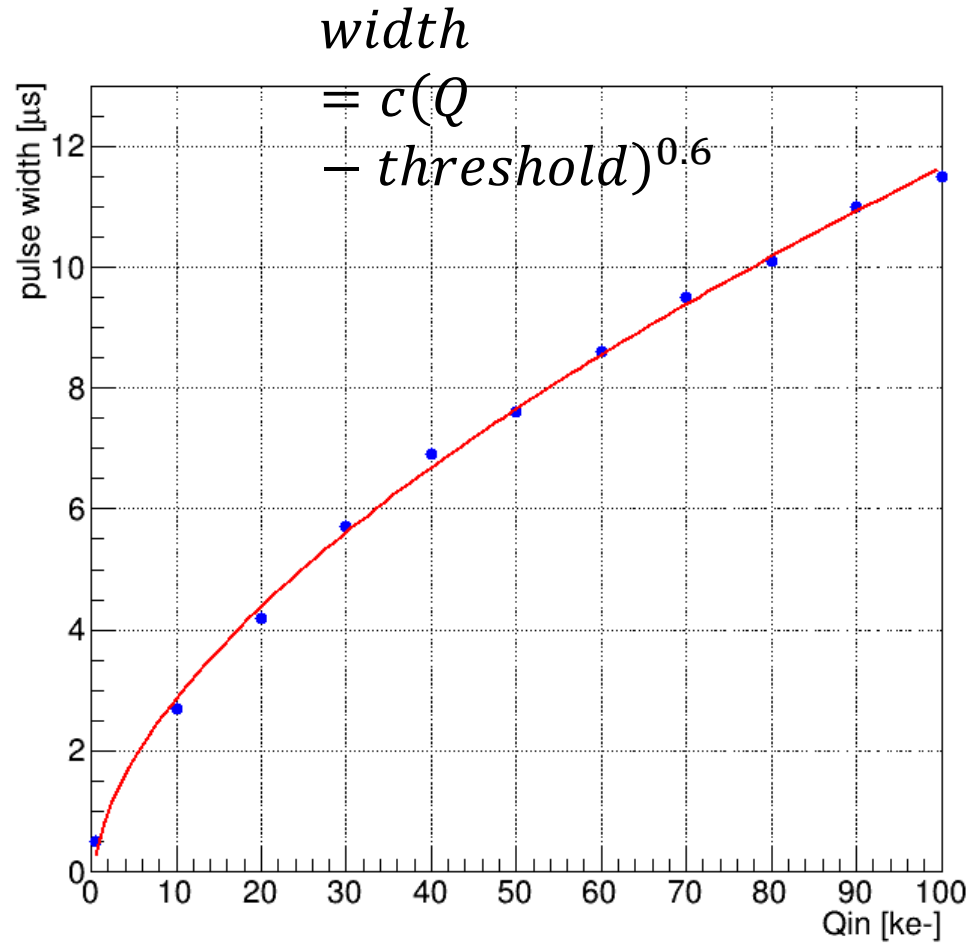

$\Delta Q$  = increase in  $Q$  to increment ToT by 1 digit