

# MAPS (Monolithic Active Pixel Sensor ) design: experience at INFN-LNF

*Eleuterio Spiriti*

( INFN LNF/Roma Tre )


1. A brief history:
  - Mimoroma1
  - Mimoroma2
  - Mimoroma3
2. Further studies for "Mimoroma4" (not built)
3. Solutions proposed
3. Simulation results: **mismatch, noise, S/N, power, area.**
4. Conclusions

# Mimoroma1: the first trial!

Pitch =  $17\mu\text{m}$   
4096 pixels


Pitch =  $34\mu\text{m}$   
1024 pixels

Test  
structures

 


- TSMC  $0.25\mu\text{m}$
- $8\mu\text{m}$  epi thickness
- gate all around design for radiation hardness
- different pixels architecture (different collecting diode number and dimensions)

Chip

 

# Mimoroma1: the first trial!


RUN 423: sub-matrix0 calibration peaks

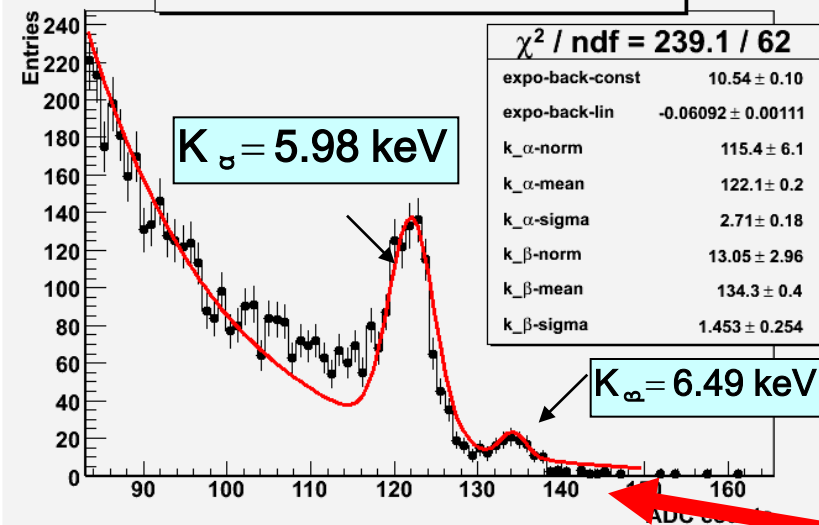


**mimoroma1 chip**  
( first? MAPS designed at INFN)

Fe55 X  
X ray  
source

Double alfa event  
large pitch (34  $\mu\text{m}$ )  
32 x 32 pixel

 


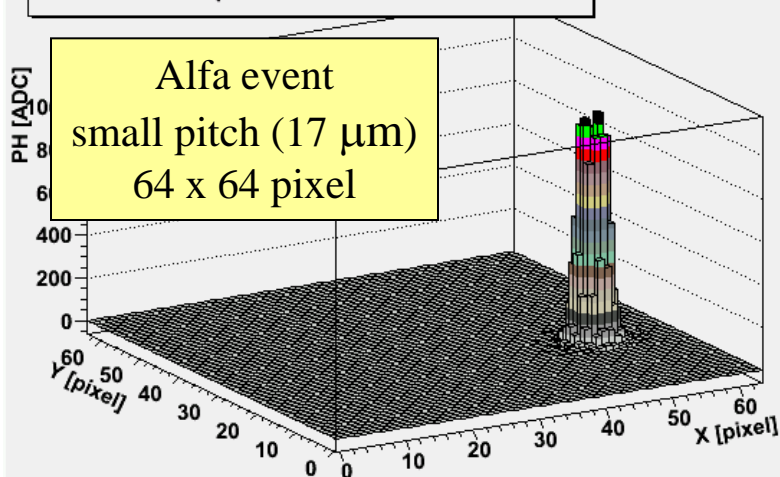Event 2766: Alpha event on the mixed matrix






 
# The Mimoroma2 example (**only NMOS architecture**)



## Pixel architecture


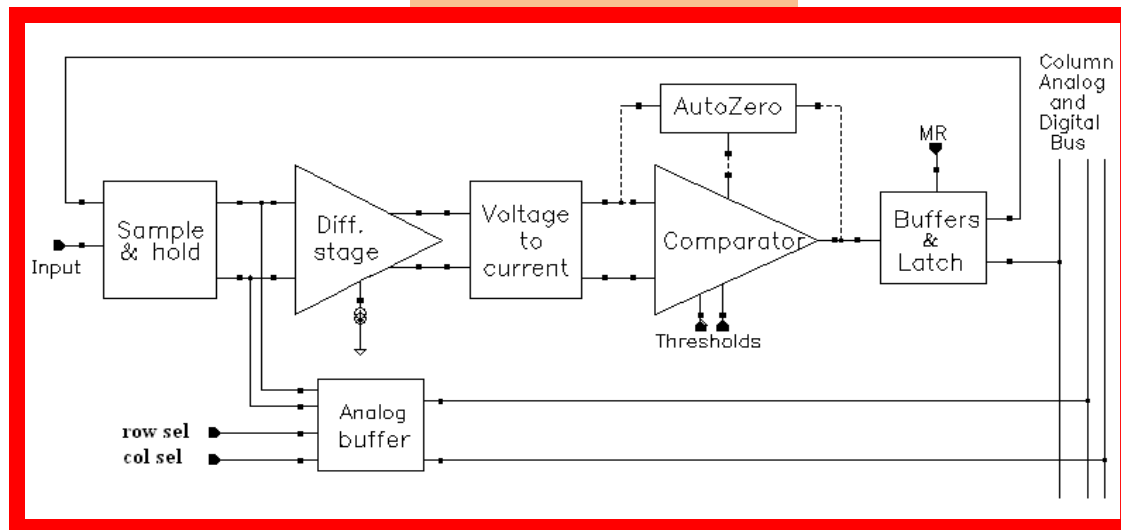


## Pixel layout

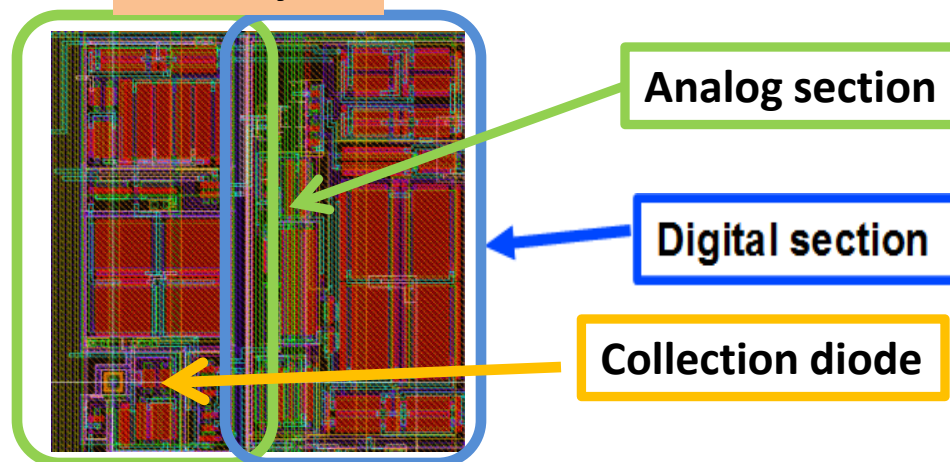


- STMicroelectronics CMOS 130nm
- Chip size: 2mm x 3mm
- 18 different arrays
- sparsified pixel size: 25 $\mu$ m x 25 $\mu$ m
  
# The Mimoroma2 example (only NMOS architecture)



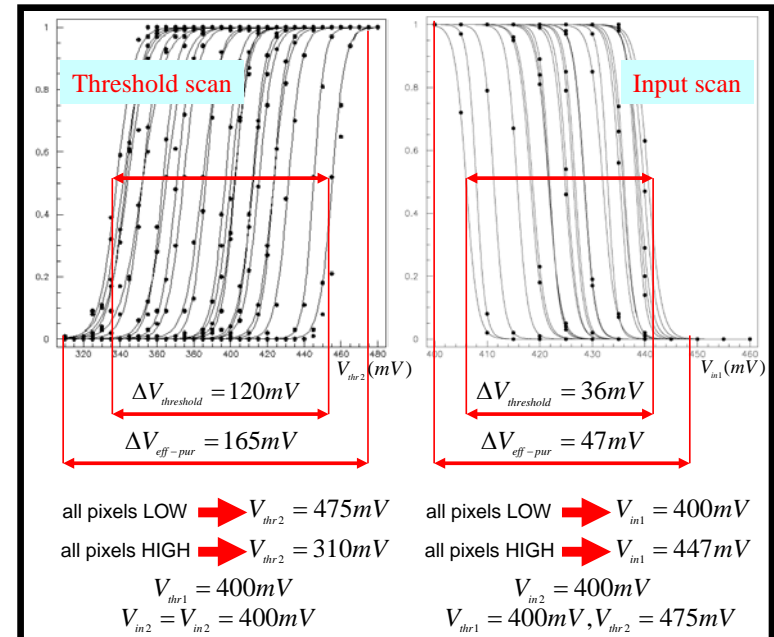**Discriminator threshold dispersion: only NMOS transistor used in the design.**


**Alpha particles detection:** Cluster reconstruction of two events produced by an alpha particle hit on the two 32x64 non-sparsified pixel matrices (HG and LG) by Americium 241 radioactive source.




# Mimoroma3: a jump into 3D technology (130nm Chartered, GlobalFoundries, Tezzaron)

## Input stage 3T configuration

## S&H stage configuration

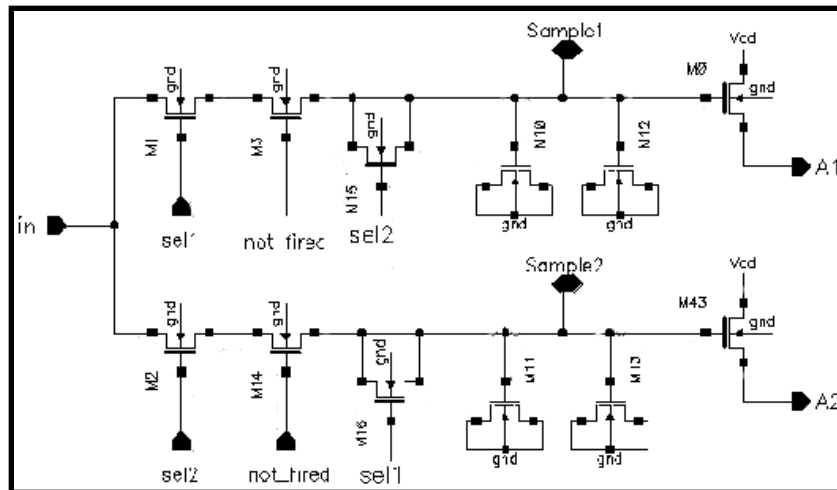
 
## Discriminator stage configuration Only NMOS configuration in mimoroma2 NMOS/PMOS used in mimoroma3



- A. Bulgheroni, E. Spiriti, J. Mlynarczyk, "Design and characterization of a Monolithic Active Pixel Sensor in 0.25 $\mu$ m Technology" Proceedings of the 10th ICATPP Conference. Held 8-12 October 2007, DOI: 10.1142/9789812819093\_0156
- J. Mlynarczyk, E. Spiriti, A. Bulgheroni, "Design of a monolithic active pixel sensor in ST 0.13 $\mu$ m technology," Proceedings of the 10th ICATPP Conference, Oct. 2007, pp. 999-1003.
- Mlynarczyk, J., Spiriti, E.; "On pixel signal processing for MAPS sparsified readout implemented in CMOS VLSI technology"; Signals and Electronic Systems, 2008. ICSES '08. International Conference on; DOI: 10.1109/ICSES.2008.4673359
- Spiriti, E., Mlynarczyk, J.; "Results of an on pixel sparsification architecture in a MAPS test chip in STM 130nm technology"; Nuclear Science Symposium Conference Record, 2008. NSS '08. IEEE; DOI: 10.1109/NSSMIC.2008.4774596





## Pixel layout area

Mimoroma3 ( Chartered 0.13 $\mu\text{m}$  )  $2*25\mu\text{m}*25\mu\text{m}=1250\mu\text{m}^2$

25 $\mu\text{m}$  x 25 $\mu\text{m}$  Digital Tier pixel

 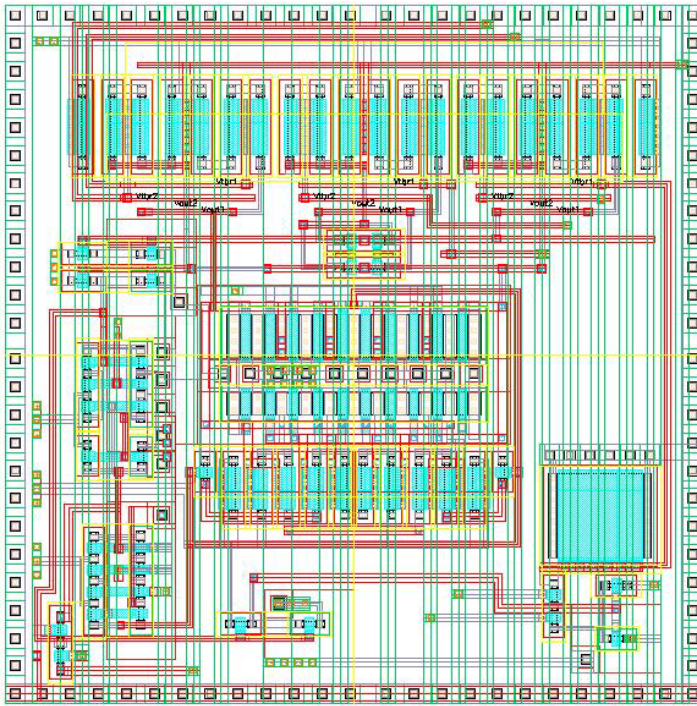25 $\mu\text{m}$  x 25 $\mu\text{m}$  Analog Tier pixel



Area estimation:

Mimoroma3  $\rightarrow \sum \text{MOS}(w \times l) \sim 270 \mu\text{m}^2$

90% S&H MOS capacitors

Mimoroma4  $\rightarrow \sum \text{MOS}(w \times l) \sim 135 \mu\text{m}^2$

85% S&H MOS capacitors

- 50  $\mu\text{m}$  pitch should be NO PROBLEM with 0.13  $\mu\text{m}$  and 0.18  $\mu\text{m}$  technologies
- 25  $\mu\text{m}$  pitch probably possible with 0.13  $\mu\text{m}$ , difficult/impossible with 0.18  $\mu\text{m}$ .

## Further studies for “mimoroma4” → modified mimoroma2/3 architecture only simulations shown from here on!

### Constrains

- In single particle application ( MIPs ) main constrain → rate (  $100\text{Mhits/s}\cdot\text{cm}^2$  )
- signal level → 500-1000 electrons
- if ADC how many bits, dynamic range?
- readout time?
- SDS Sparse Data Scan?

### Considerations/questions

- Digital readout only? → in-pixel discriminator (noise, mismatch, power, area)  
fast column/matrix(?) digital readout?  
only digital logic @ End of Column
- Analog readout only? → discriminator and/or ADC @ End of Column  
“slow” column/matrix(?) analog readout
- Both? → Fast digital and Analog readout ( speed factor 10-20)  
fast column/matrix readout  
fast column/matrix readout
- Discriminator → **level sensitive/latch type** ( integration time)(?)  
mismatch correction?
- In pixel analog pipeline? → How many stages deep? ( one minimum if Analog RO)
- End of Column readout




# Matrix readout architecture
 
## *Solution based on:*

- *in pixel discrimination*
- *in pixel analog memory*
- *column readout*
- *two column readout busses:*
  - *digital on/off ( fast )*
  - *analog (slow ) sparsified*

End of column digital  
( fast synchronous readout )  
+  
Sparsified ( slow ) analog/  
ADC readout




Data  
out



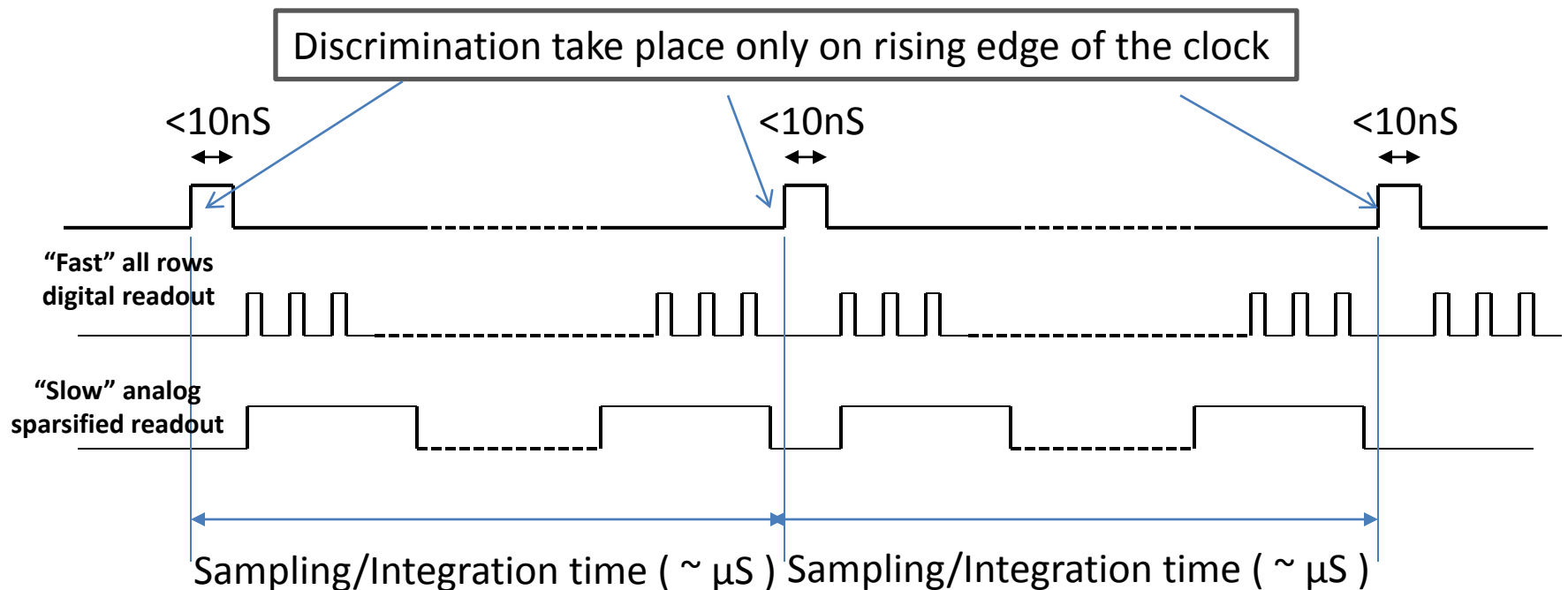
## Achitecture: timing!

- Sample & Hold and discriminator sampling @ Integration Time period
- All digital outputs of a column are readout in the integration time (rolling shutter)
- All analog output over threshold are readout in the integration time (token passing) with one level deep analog pipeline ( data lost if “high” occupancy )
- Time resolution defined by Integration Time ( time stamp resolution )



# Pixel architecture

 

## Analog section

- Fully differential ( CDS comes naturally ) configuration
- Switching technique ( fast, small, low power )
- Autozero to compensate mismatch
- Analog signals available (  $dE/dx$  possible )
- Discriminator in pixel  $\rightarrow$  sparse data scan
- Sample & hold/discriminator control in rolling shutter mode
- Input from 3T scheme or any integration front-end!!
- 3D coupling to "sensor" layer with or without FE possible

## Digital section

Simulation shows that further gain ( differential stage ) Is NOT needed!



## Architecture manageable rates and readout times.

Rates for the 2 options: **25  $\mu\text{m}$  or 50  $\mu\text{m}$  pitch:**

### A - 25 $\mu\text{m}$ pitch

400x400 matrix - 10x10 mm<sup>2</sup> - 160000 pixel

**100 Mhits/s\*cm<sup>2</sup>** - 1 Mhits/s\*mm<sup>2</sup> - 625 hits/s\*pixel

$\lambda = 250.0 \cdot 10^3$  hits per second per column in average

T = Column scanning time = 9ns\*400=3.6  $\mu\text{s}$

average number of hits to readout per column per scanning time =  $\lambda \cdot T$

$\lambda \cdot T = 250.0 \cdot 10^3 \cdot 3.6 \cdot 10^{-6} = \mathbf{0.9 \text{ hits/column} \cdot \text{scanning time}}$

### B - 50 $\mu\text{m}$ pitch

200x200 matrix - 10x10 mm<sup>2</sup> - 40000 pixel


**100 Mhits/s\*cm<sup>2</sup>** - 1 Mhits/s\*mm<sup>2</sup> - 2500 hits/s\*pixel

$\lambda = 500.0 \cdot 10^3$  hit per second per column in average

T = Column scanning time = 9ns\*200=1.8  $\mu\text{s}$

$\lambda \cdot T = 500.0 \cdot 10^3 \cdot 1.8 \cdot 10^{-6} = \mathbf{0.9 \text{ hits/column} \cdot \text{scanning time}}$
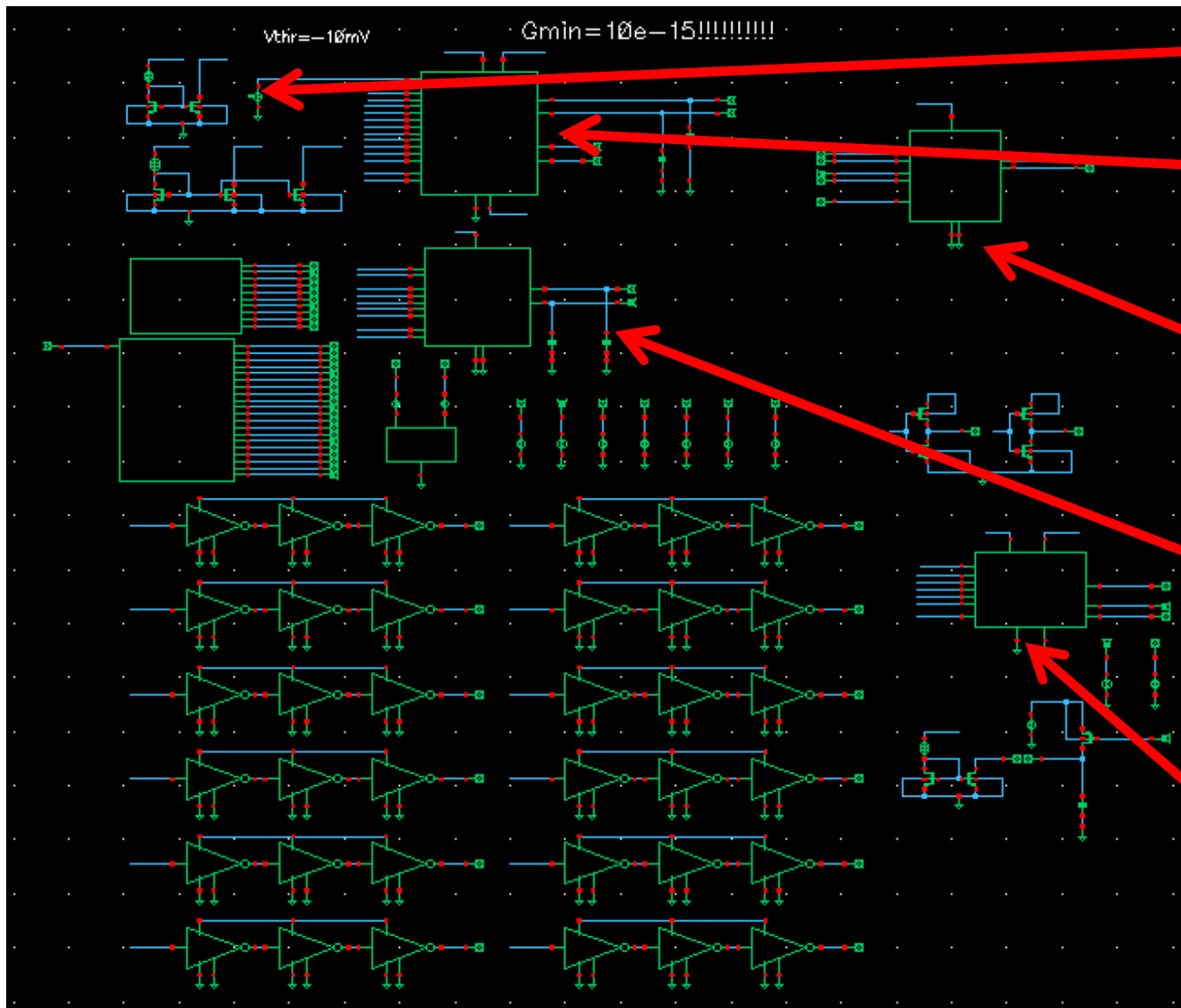
# Block schematic of the pixel ( GlobalFoundries 0.13 $\mu\text{m}$ , q2v3 )



**Current pulse  
injection**

**3T FE + S&H  
Analog block**

**edge sensitive  
discriminator  
block**




**mismatch  
compensation  
block**

**digital  
output block**
   
# In pixel discriminator MonteCarlo transient noise simulation

Switched capacitor circuit simulation quite tricky:

- Transient noise Monte Carlo simulation needed
- Input threshold reference voltage stair applied after dispersion correction signal stabilization
- Discriminator output counted on each stair step for threshold scan evaluation



Simulation at 100ns  
Integration time.



Simulated 160  $\mu$ s in **~80 min**  
simulation time on a core of a  
quad CPU/quad core Intel(R)  
Xeon(R) E5520 @ 2.27GHz


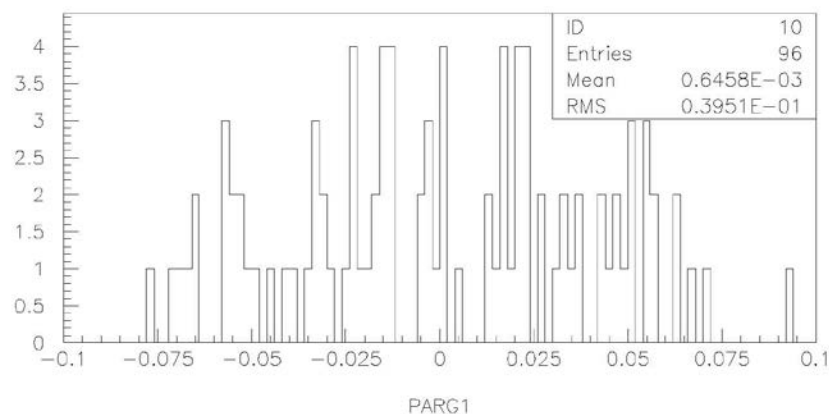 
# Discriminator threshold dispersion simulation with correction circuit switched off/on



Mismatch correction circuit **off**:

- x-scale  $\pm 100$  mV
- offset RMS = 39 mV



Mismatch correction circuit **on**:

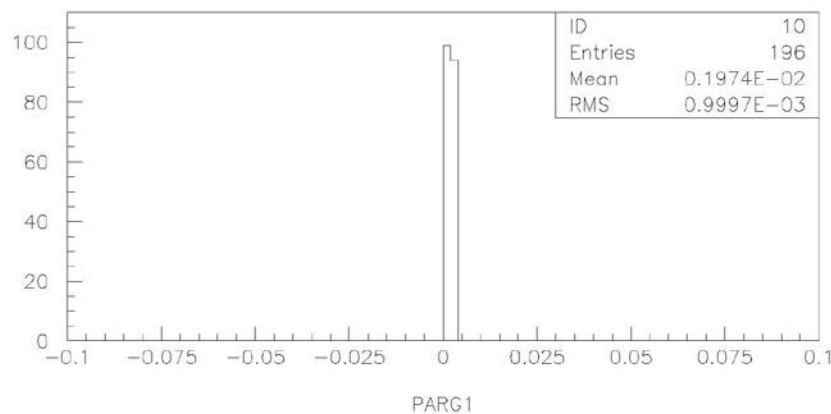
 
- x-scale  $\pm 100$  mV
- **offset RMS reduced by 2 orders of magnitude**


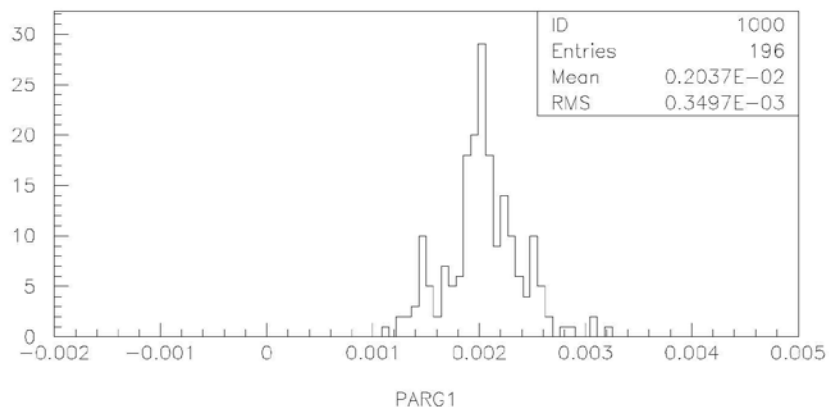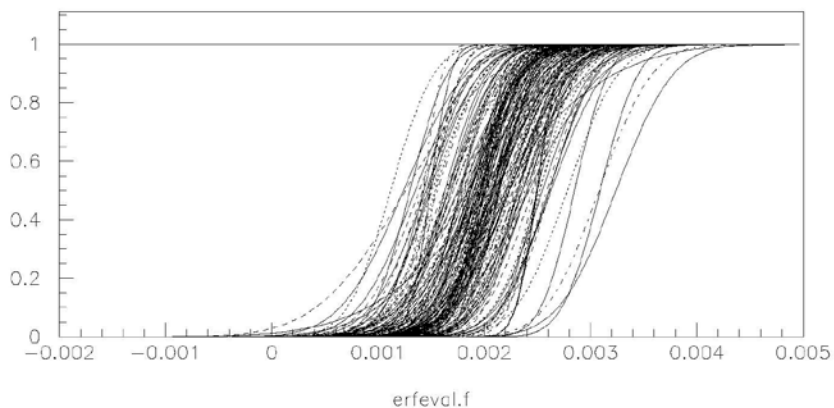
# Discriminator/full pixel threshold dispersion with correction circuit on



Mismatch correction circuit **on**,  
discriminator circuit simulation:

- x-scale (+5 mV, -2 mV)
- offset RMS = **0.35 mV**




Mismatch correction circuit **on**,  
**FULL PIXEL** circuit simulation:

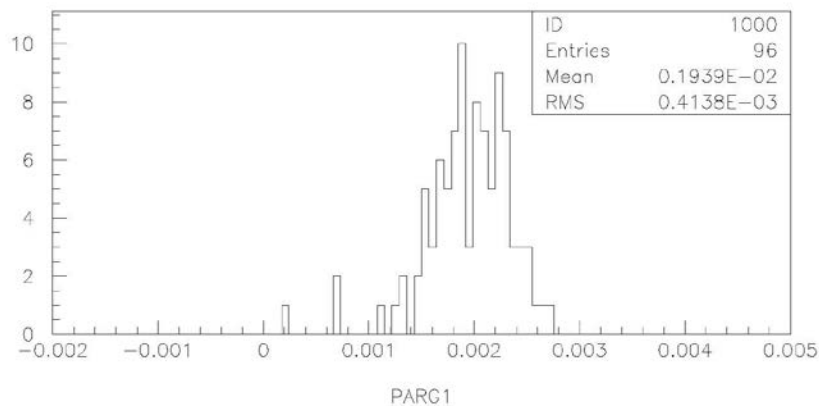 - x-scale (+5 mV, -2 mV)
- offset RMS = **0.41 mV**




# Pixel analog signal response/"calibration"

 
## Parametric transient noise simulation (no MonteCarlo)



0.137mV/electron

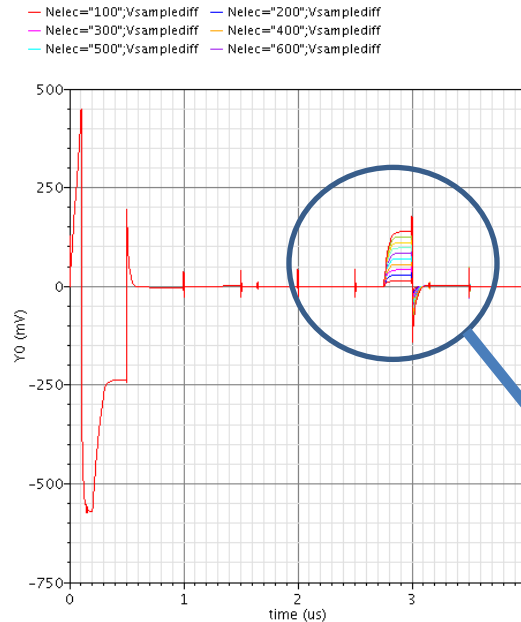

 1 electron charge = 16pA for 10nS  
Scan 100 e  $\rightarrow$  1000 e in 10 steps  
Current pulse on a collecting diode of  $3\mu\text{m} \times 3\mu\text{m}$  area






# Full pixel ( 3T configuration FE ) signal to noise ratio

Differential input signal to discriminator

**100 transient noise simulations**

 

Sample of baseline

Sample of signal



**Noise RMS=0.85 mV →**

**→ 0.85 mV / (0.137 mV/electron) →**

**→ 6.2 e ????!!!!**


**Residual mismatch noise to be added!**

  **$\text{Sqrt}(0.85^2 + 0.41^2) = 0.94 \rightarrow 6.9 \text{ e } ????!!!!$**



500 e injected pulse ~ 70 mV
 
# Pixel power consumption @ different integration times ( 500nS $\rightarrow$ 5 $\mu$ S )



Analog layer  $\sim 1\mu$ W

Discriminator:  
 $1\mu$ W  $\rightarrow$  200nW

Offset compensation:  
 $2.25\text{nW} \rightarrow 0.25\text{ nW} ???$

## Possible approach for **column readout** from Static RAM designs ( brief bibliography sketch )

SRAM technology bibliography examples:

- H. Nambu, K. Kanetani, K. Yamasaki, K Higea, M. Usami, T. Kusunoki, K. Yamaguchi, and N. Homma,  
“A 1.8ns Access, 550MHz 4.5Mb CMOS SRAM”  
in *IEEE Intern. Solid-State Circuits Conference Digest of Technical Papers*. Ieee, Feb. 1998, pp. 360-361.
- T. Uetake, Y. Maki, T. Nakadai, K. Yoshida, M. Susuki, and R. Nanjo,  
“A 1.0ns Access 770MHz 36Kb SRAM Macro”  
in *1999 Symp. On VLSI Circuits Digest of Technical Papers*, New York, June 1999, IEEE, pp. 109-110
- H. Nambu, K. Kanetani, K. Yamasaki, K Higea, M. Usami, TY. Fujimura, K. Ando, T. Kusunoki,  
K. Yamaguchi, and N. Homma,  
“A 1.8ns Access, 550MHz 4.5Mb CMOS SRAM”  
*IEEE Journal of Solid-State Circuits*, vol.33, no. 11, pp. 1650-1657, Nov. 1998.


Fast column readout is possible.

## End of Column **digital readout** ( bitline bus parasitics included )

128 pixel ( only output logic ) column.  
Signal collecting line  
parasitic resistance and  
Capacitance included!

VHDL-AMS  
Test bench

End of Column  
digital readout

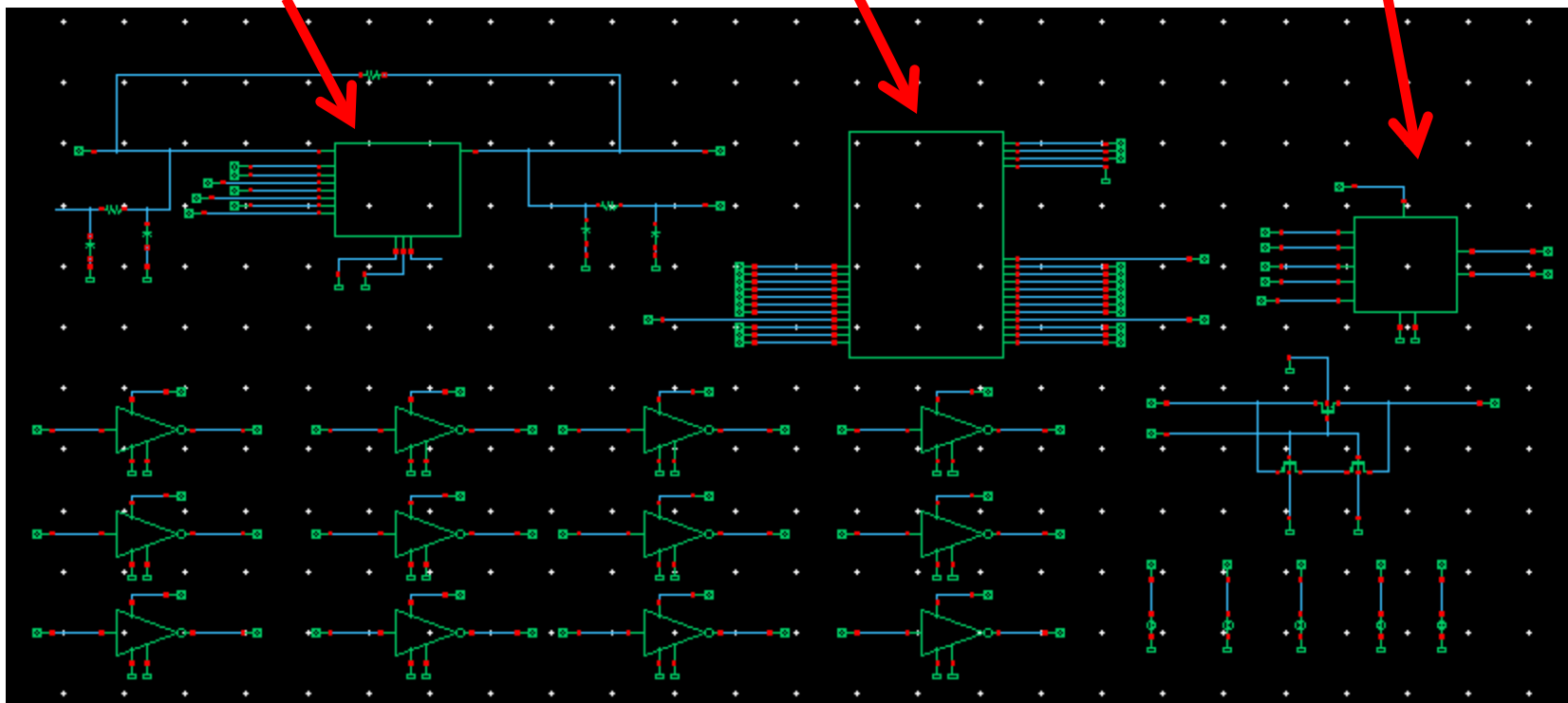

## Column input pattern to be readout

22




# Column readout timing simulation

Read out of first 16 bits.  
Pattern AAF0 correctly reproduced!

Read out time = 9 ns  
 $9 \text{ ns} \rightarrow \sim 111 \text{ MHz}$   
Can be improved!

 Transient noise  
Simulation  
( no MonteCarlo )  
Low frequency noise  
effect!



**Static RAMS usually work with a signal also 10 times lower!!**

## Power consumption summary (**NO OPTIMIZATION AT ALL**)

**Pixel power consumption summary (pitch 25  $\mu\text{m}$ ) = 335.2 -> 201.6 mW/cm\*2**

Integration time	500 nS	5 $\mu\text{s}$
Analog layer	1.093 $\mu\text{W}$	1.070 $\mu\text{W}$
Discriminator	1 $\mu\text{W}$	190 nW
Offset compensation	2.25 nW	0.25 nW

**No  
power  
cut**

**End of Column digital readout power consumption summary ( 111MHz )**

# Column	1	400 column => 1 cm 25 $\mu\text{m}$ pitch
EC readout	36.7 $\mu\text{W}$	14.68 mW
Bitline	10.8 $\mu\text{W}$	4.32 mW
Pixel output buffers	6.7 $\mu\text{W}$ *	2.68 mW

**\* All  
output  
buffers  
in the  
column**

**End of columnn analog readout power consumption to be evaluated.  
Order of magnitude lower than the analog one due to the  
sparsified readout!**

## Conclusions:

**What, if any, of this work  
could be useful in  
the framework of the ALICE ITS  
upgrade project?**

- known-how?**
- ideas?**
- experience in testing?**