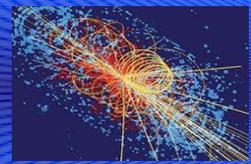




FAST FRONT-END ELECTRONICS

Part I: Fast sampling circuits

Angelo Rivetti – INFN Sezione di Torino



■ Front-end electronics

- Circuits reading a signal from a detector and sending data out after some preliminary elaboration;
- Multi-channel systems implemented in the form of custom VLSI circuits.

■ Fast:


- Circuits capable of sampling rates > 1 GHz.
- Circuits capable of events rate > 100 kHz.

■ Today topics:



- Very fast sampling and digitization circuits;
- Examples from the open literature.


■ Tomorrow topics :

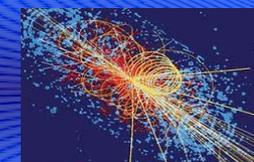- High event-rate and low power circuits;
- Case studies based on direct experience.



Imaging Cherenkov Telescope Arrays

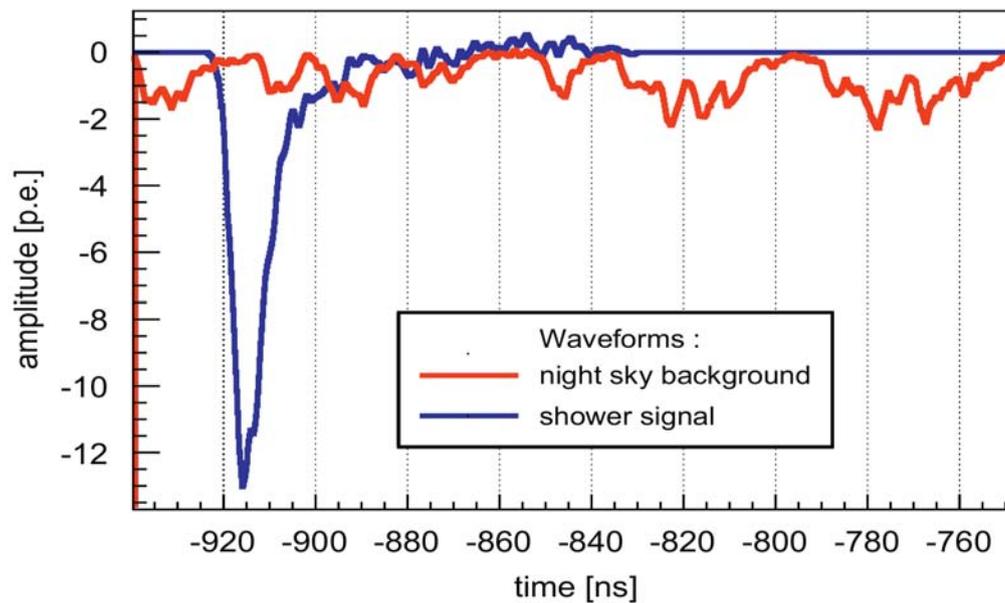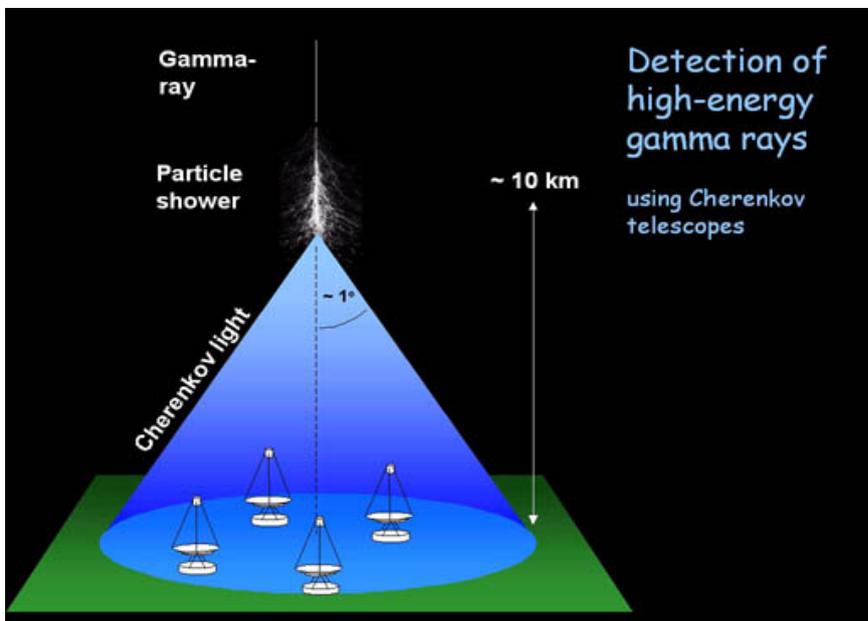

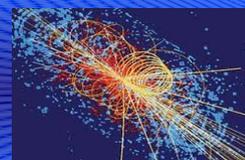

#1. UHE event will induce an e/ γ shower:



Askaryan effect


In electron-gamma shower in matter, there will be 20% more electrons than positrons.

Compton scattering: $\gamma + e^-_{(at\ rest)} \rightarrow \gamma + e^-$


Positron annihilation: $e^+ + e^-_{(at\ rest)} \rightarrow \gamma + \gamma$
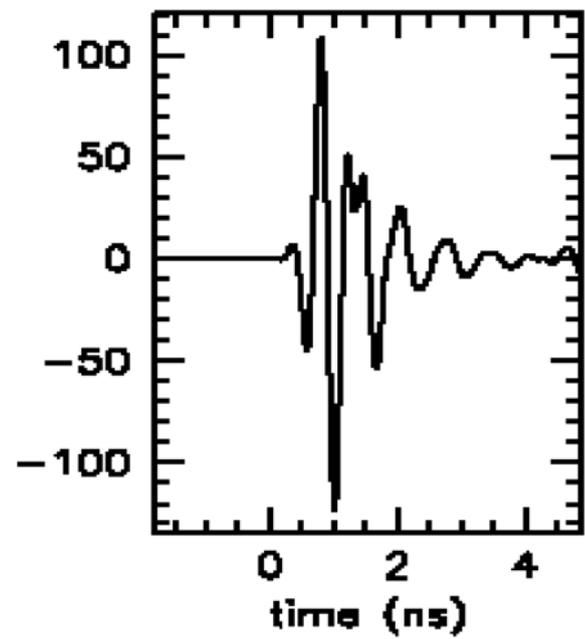
#2. Excess charge moving faster than c/n in matter emit **Cherenkov Radiation**



$\lambda \gg R_{Moliere}$ (microwaves), coherent $\Rightarrow P \propto N^2$




The “ideal” front-end

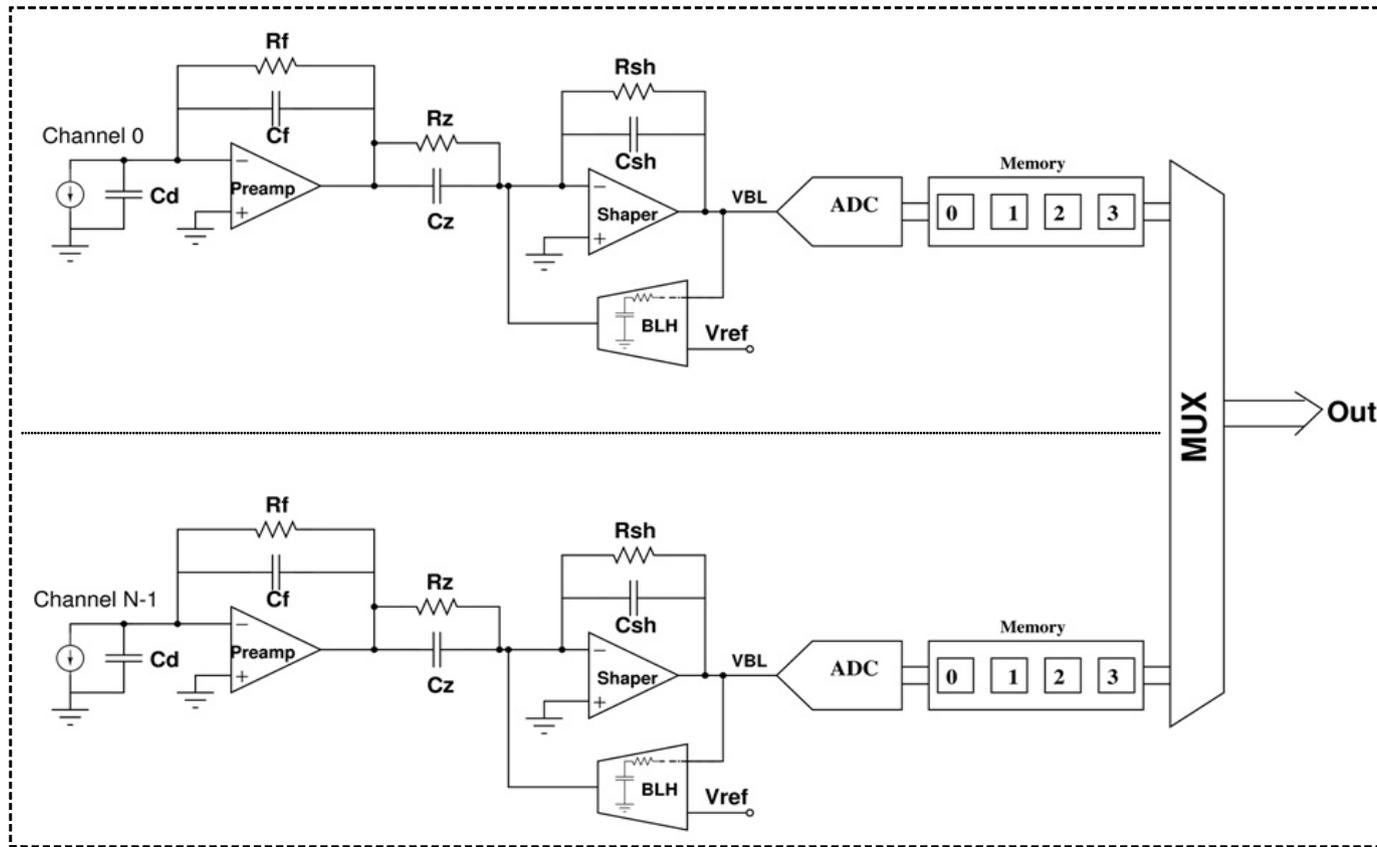

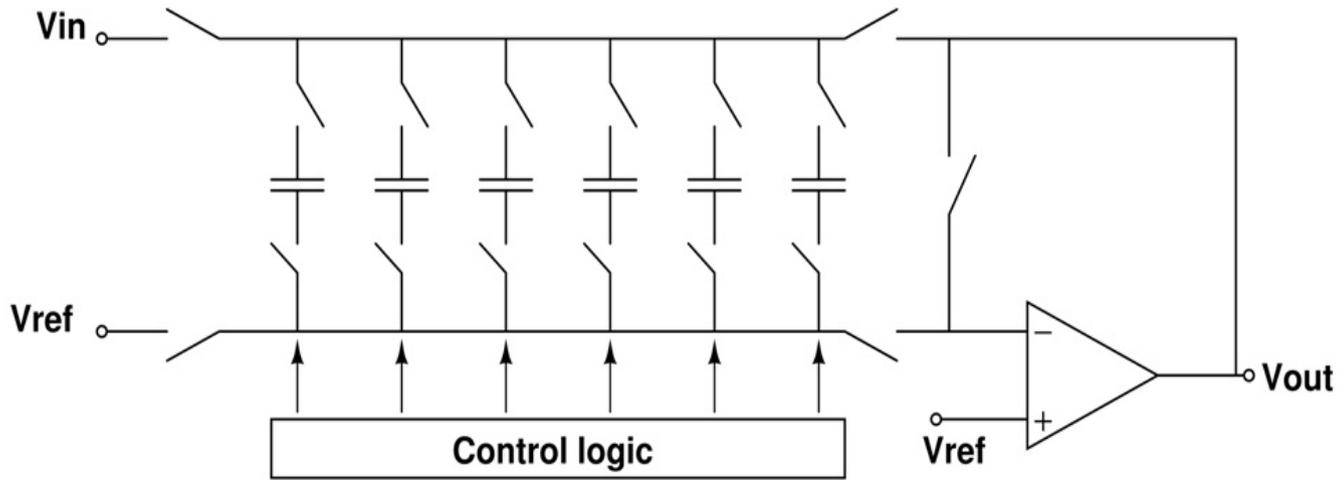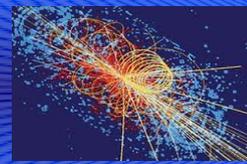- **Early digitization** immediately after the front-end amplifier;
- Transfer also the information to the back-end and do the signal selection on FPGA, where selection algorithms can be easily **changed/upgraded**.
- Transmission bandwidth required for a 64 channel chip sampling continuously at 100 MHz and 8bit resolution: 51.2 Gbit/sec...






a)

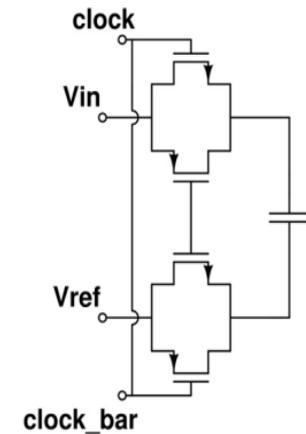

b)

- Decoupling sampling and digitization/transmission....
- **Sampling** the analog voltage on a **capacitor**.
- Sampling is fast and cheap: **fast transients** can be captured and **digitized** only if needed;
- More segments can be used to allow **arrival time derandomization**.
- AM can be combined **slower on chip ADCs** or with powerful state-of-the art commercial components **located off-chip**.
- Timing circuit often implemented with shift registers

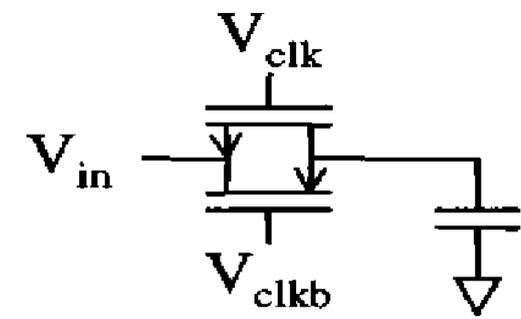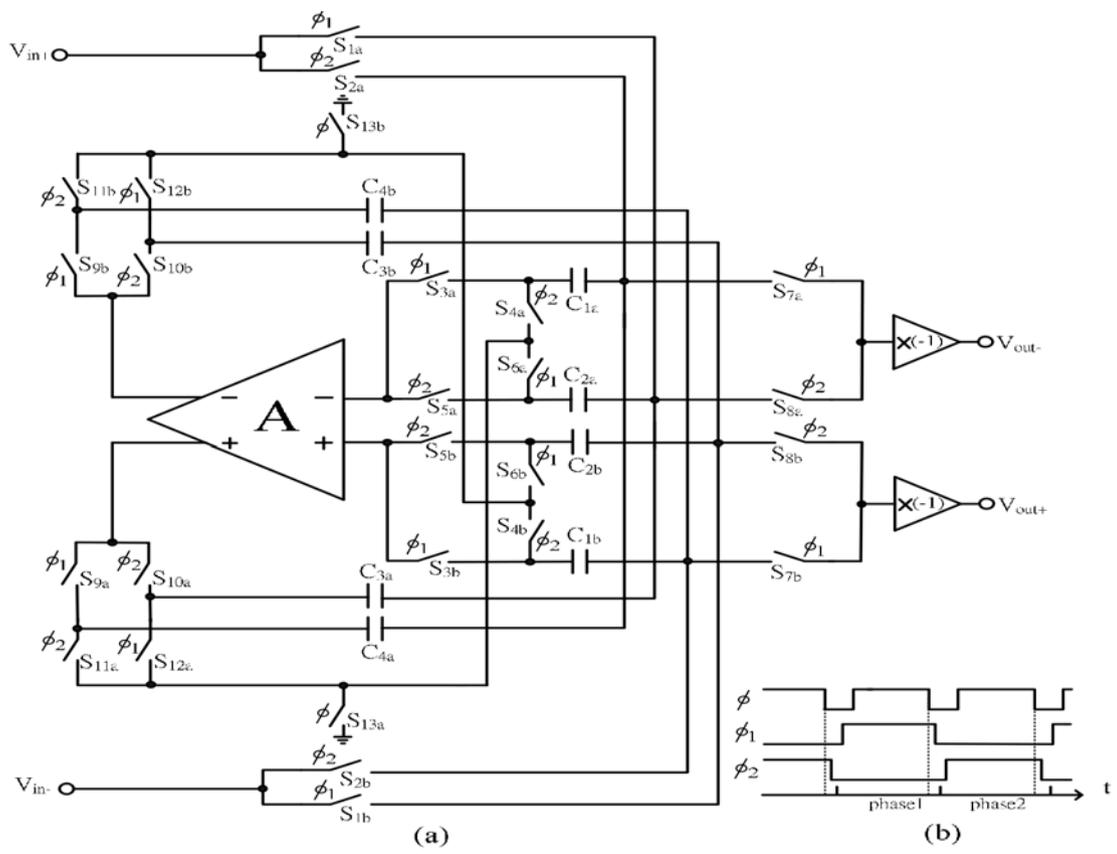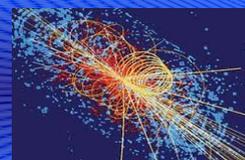Popular since the early days of ASICs in particle physics




Typical sampling cells in an analogue memory for HEP


T. S. Lee et al., Proceedings of IEEE ISCAS 2005

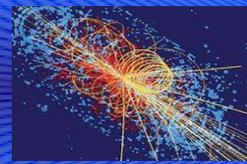6.7 mV, 10 bit **linearity**.

- In detector applications we need **large dynamic range** but requirements on **linearity** are less stringent (**1%** is usually already a good figure);
- **Complexity** of sampling/digitization circuitry tends to **grow** exponentially with linearity requirements...






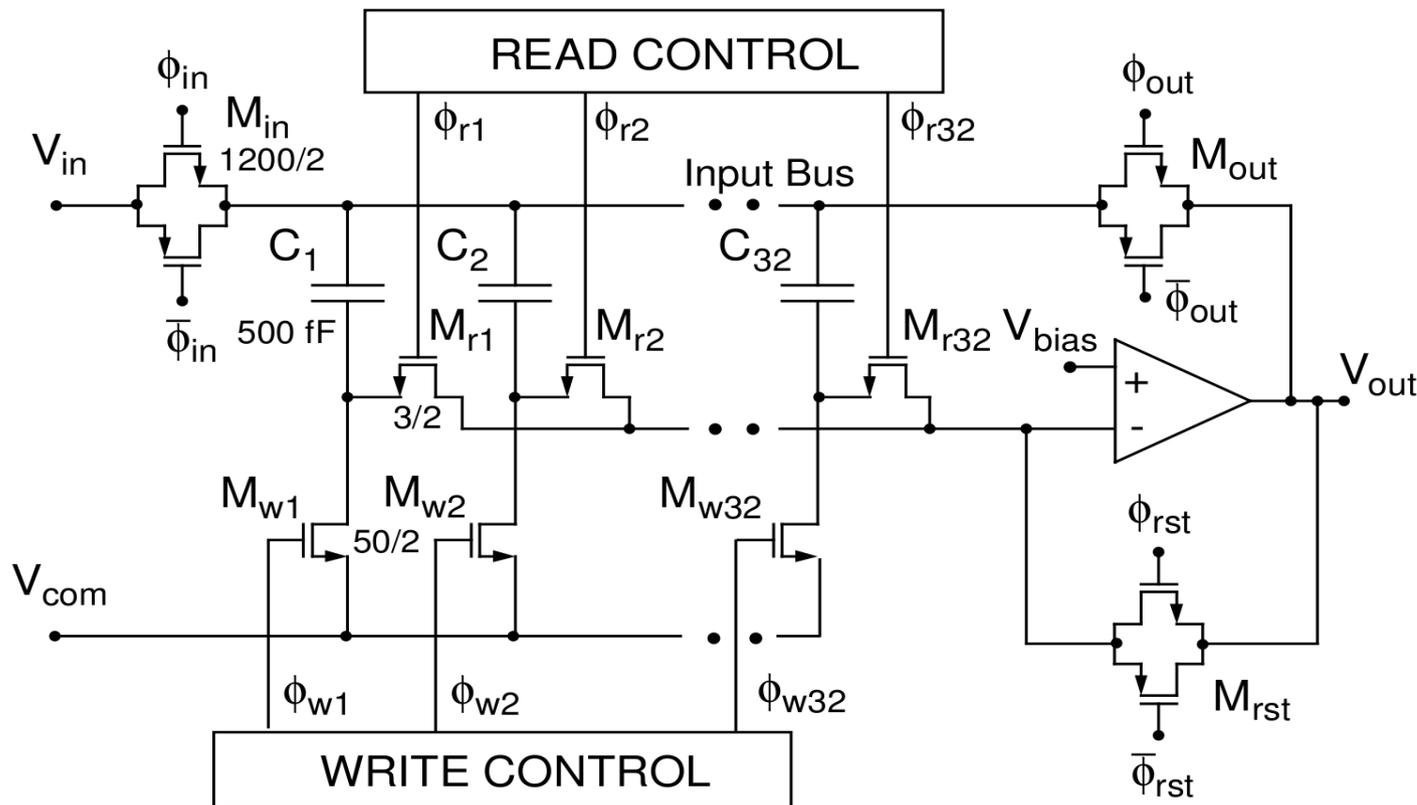“A 700-MHz Switched-Capacitor Analog Waveform Sampling Circuit”
 G. Haller and B. Wooley, JSSC, April 1994.




- Replacing the shift register with a **delay line** to control the write pointer;
- Distance between sampling times defined by **delays of digital gates** instead of clock;
- Technology: 2 μm , 5 V with poly-poly capacitors.

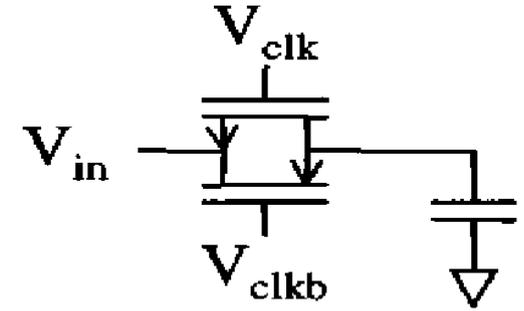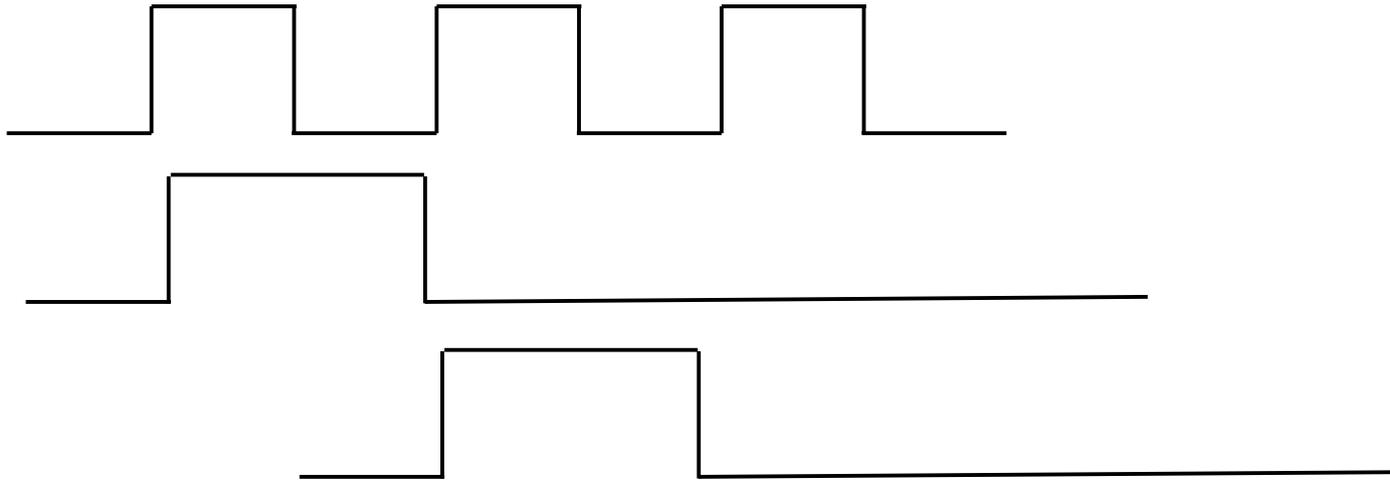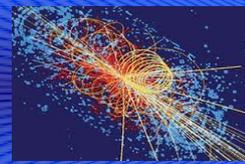700 MHz sampling rate with 2 mW of power per channel!



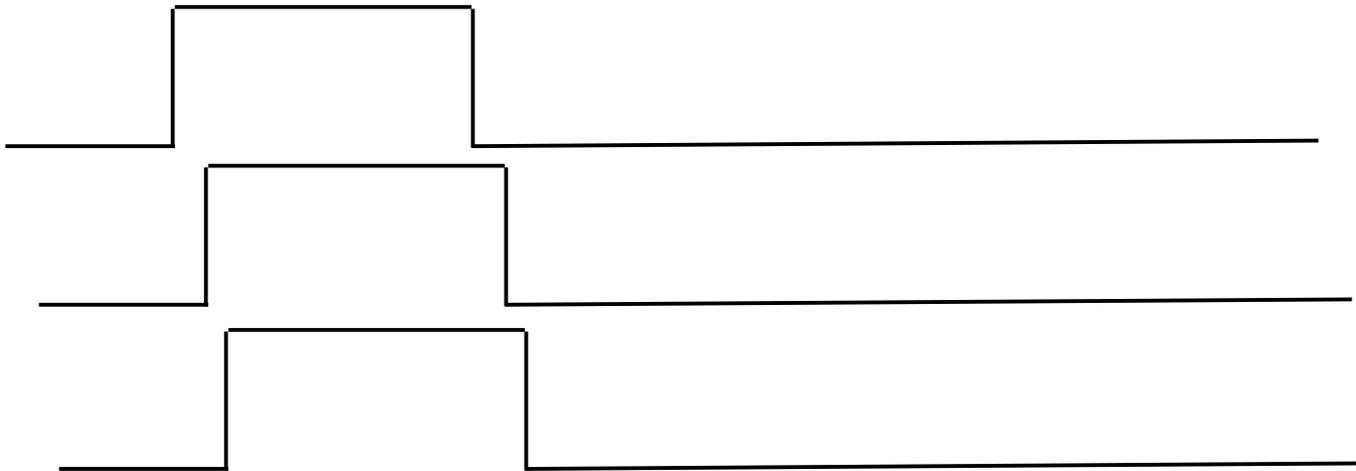
a) Shift registers: time between samples= T_{clock}



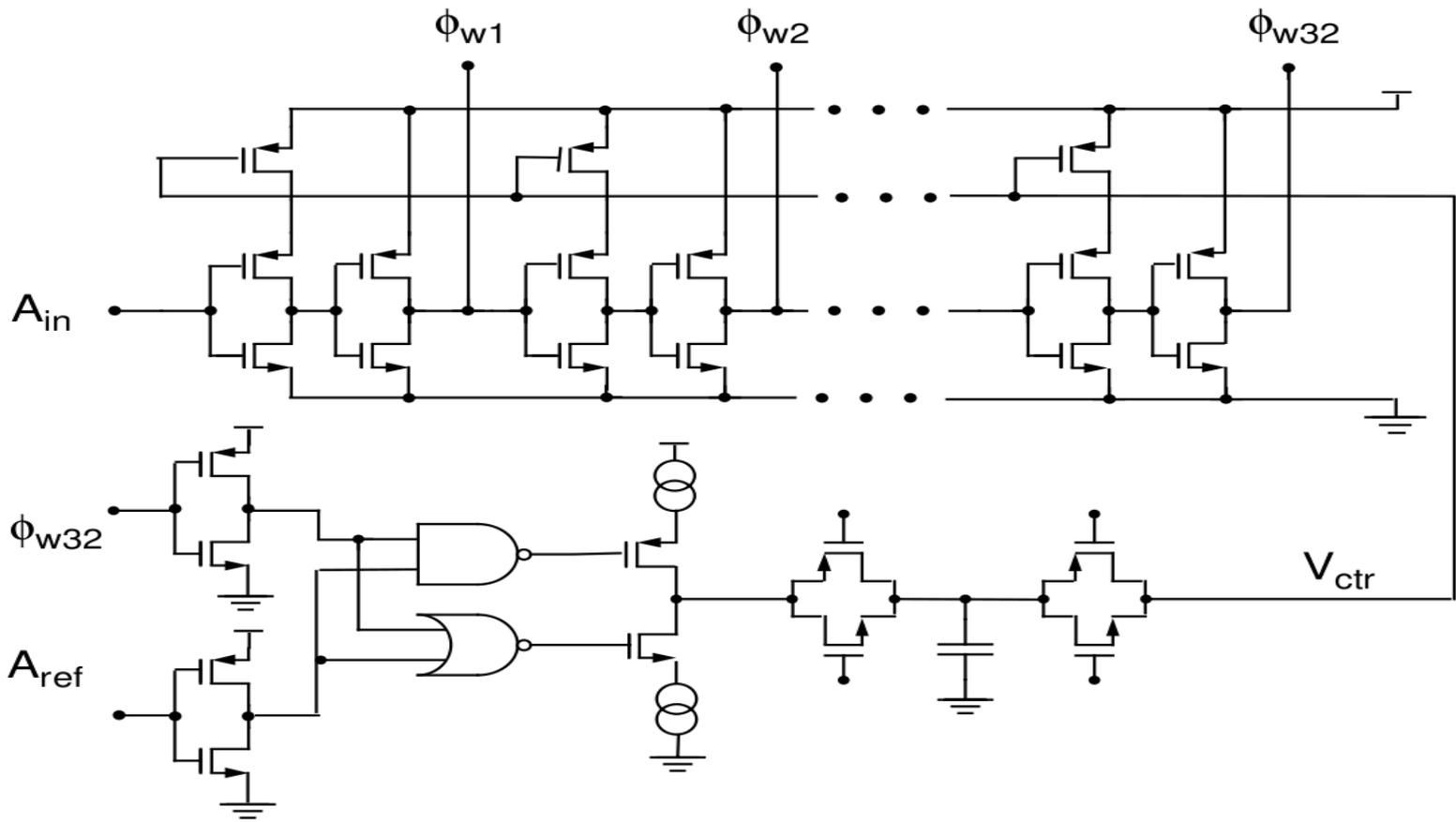a) Delay line: time between samples= T_{delay}



“A 700-MHz Switched-Capacitor Analog Waveform Sampling Circuit”
 G. Haller and B. Wooley, JSSC, April 1994.



- Issues with delay lines: uniformity between timing sampling, changing with temperature...
- Chain of starved inverter with feed-back




Analog memories in deep submicron: perspectives





- Deep submicron CMOS technologies offer very fast digital gates.
- Typical gate delay is **50 ps** for a **130 nm** process.
- Potential for sampling speed in the order of **20 GHz** or more.
- Read-out/digitization speed will be of course much slower...
- Capture of **very fast transient** and possibility of applying powerful DSP processing offline or online with FPGAs.
- **Amplitude** and good (100 ps...) **time resolution** in one shot.

But...

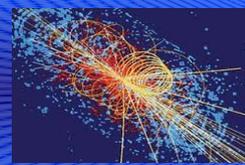
- Deep submicron CMOS technologies operate with low supply voltages
 - From **3.3 V** in 0.35 μm to **1 V** in 90 nm.
 - Need of almost rail-to-rail operation to have acceptable dynamic range.
- Poly-to-poly capacitors not available in deep submicron. Need to find alternatives.



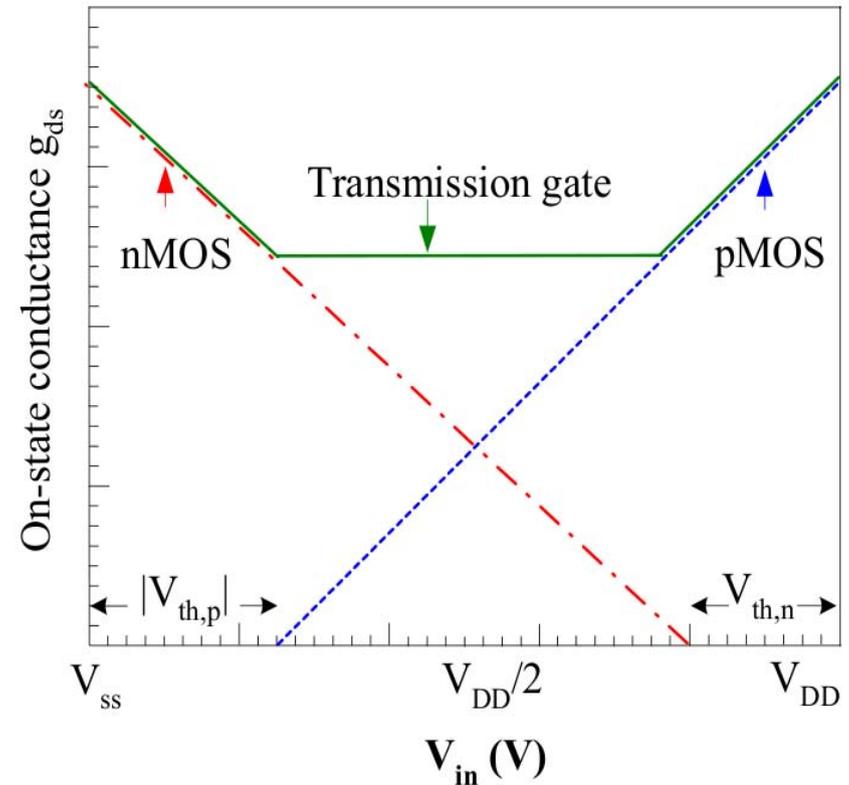
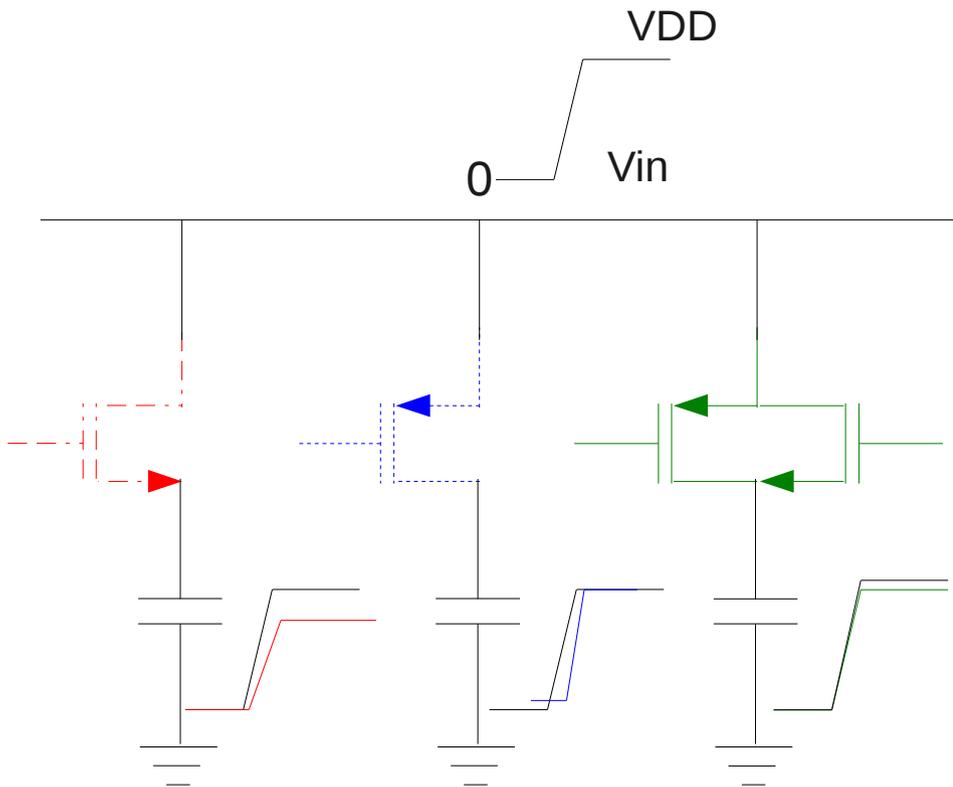
- Use of CMOS switches in the signal path for reasonable dynamic range;
- Even in this case keeping a **conductive path** can be challenging.



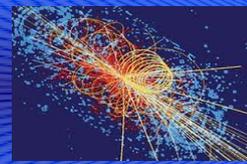- Non uniform switch resistance across the signal path leads to **harmonic distortion**.




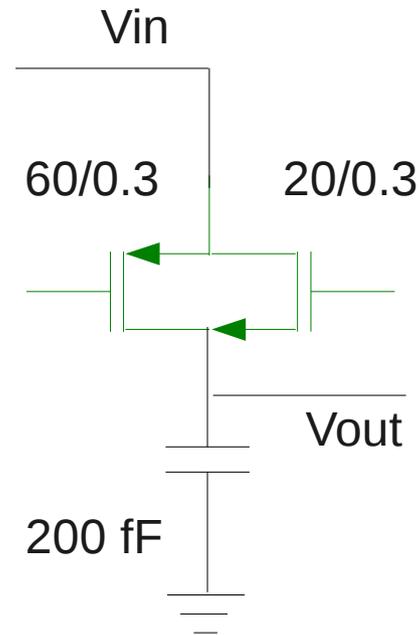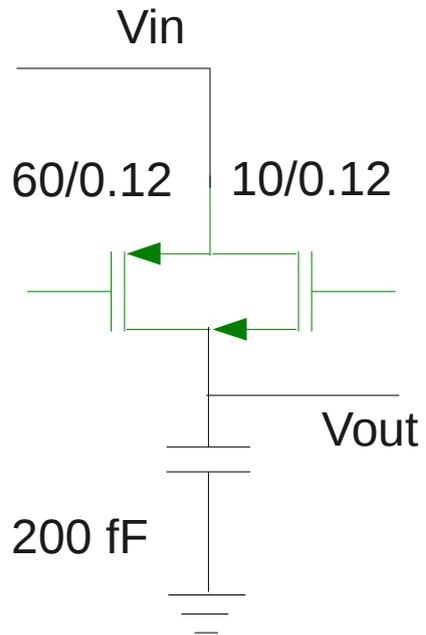- Two different set of switches considered with same W and different L ;
- Bandwidth measured as a function of the input dc level;
- Simulation with typical mean condition @ 27 C.






Example of bandwidth performance

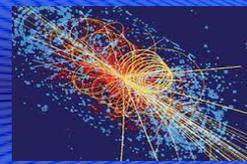


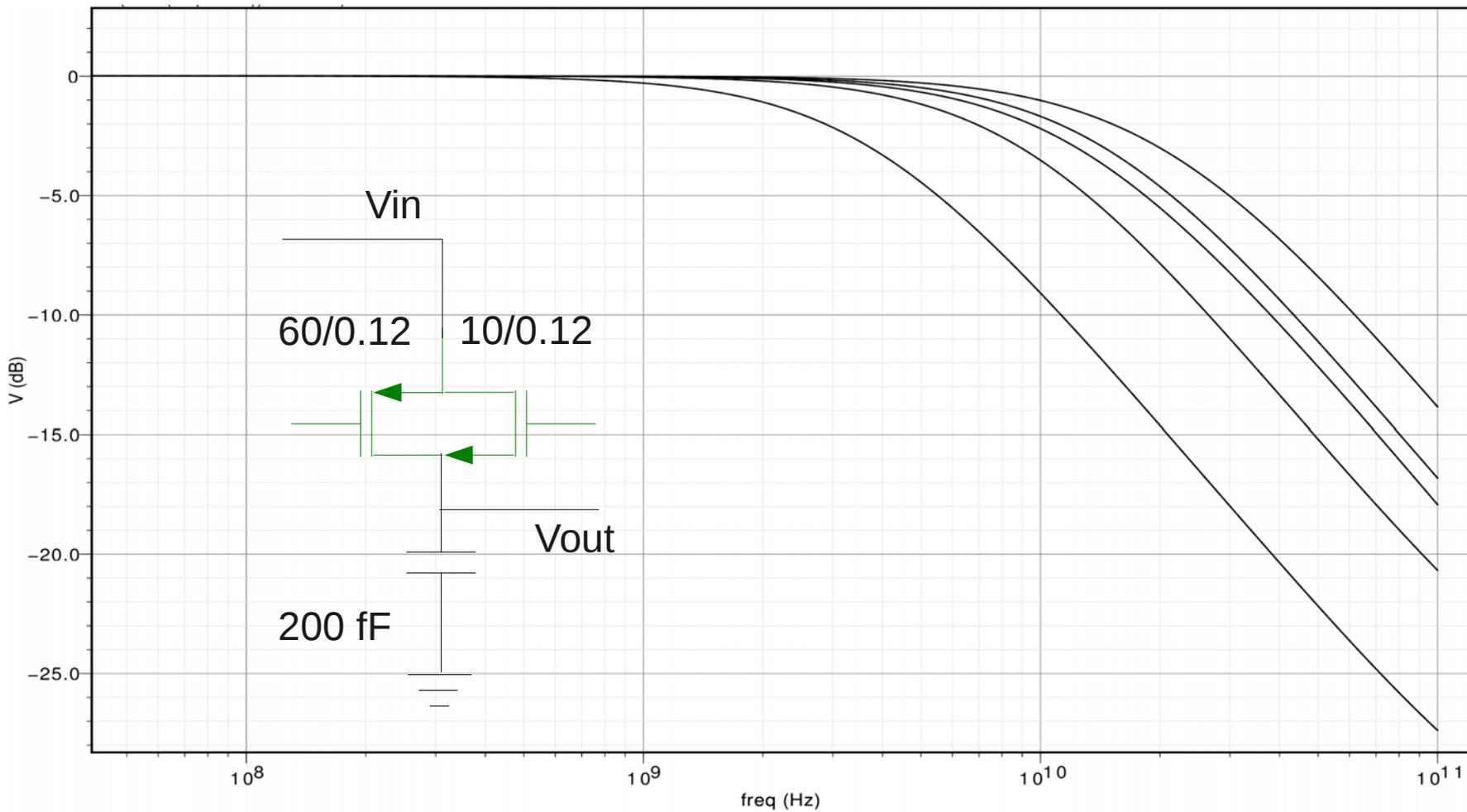- With simple CMOS switches huge bandwidth variation as a function of signal level.
- Worst point: **0.6 V** (middle of dynamic range) => BW= **3.76 GHz**
- Best point **0 V** (NMOS in full conduction) => BW = **20.6 GHz**.










Comparison of different switch size

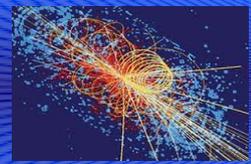

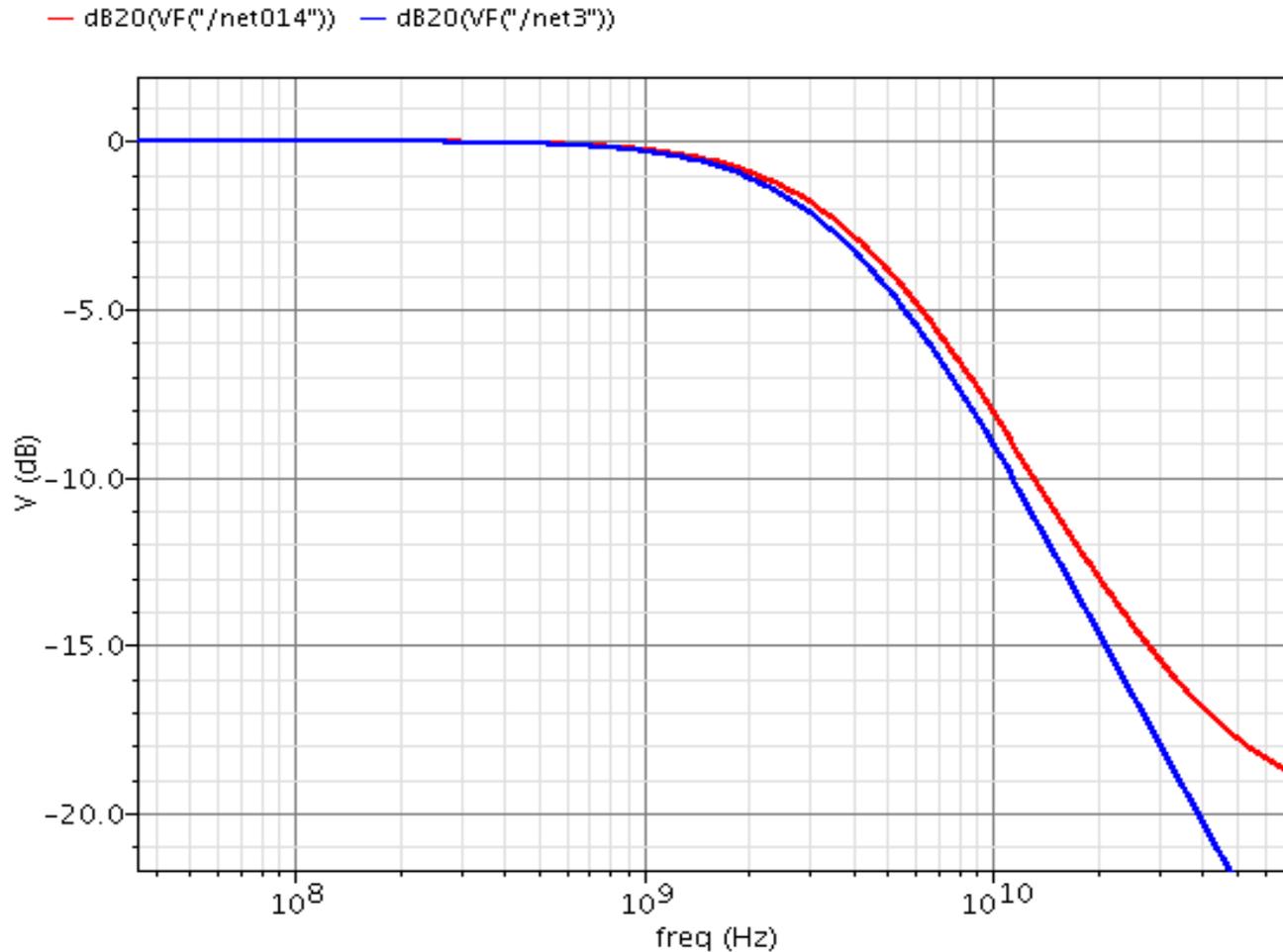
- **Red curve:** switch size 20/0.3 for NMOS and 60/0.3 for PMOS: bandwidth 4.2 GHz.
- **Blue curve:** switch size 20/0.12 for NMOS and 60/0.12 for PMOS: bandwidth 3.7 GHz.



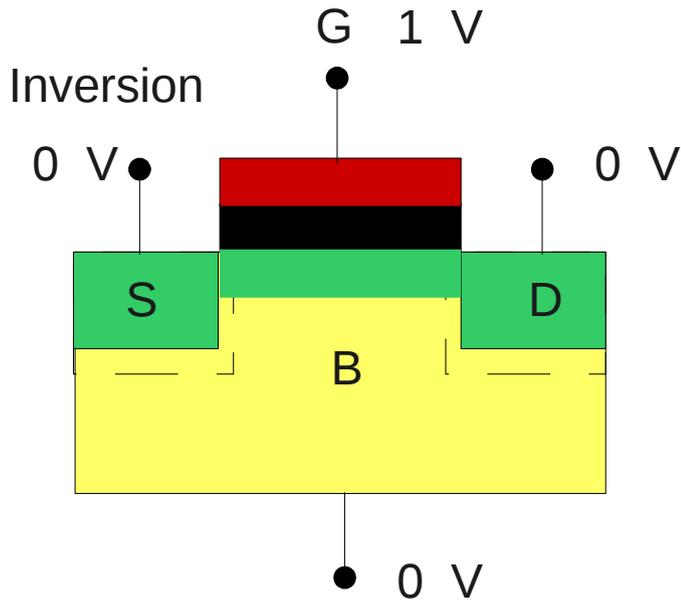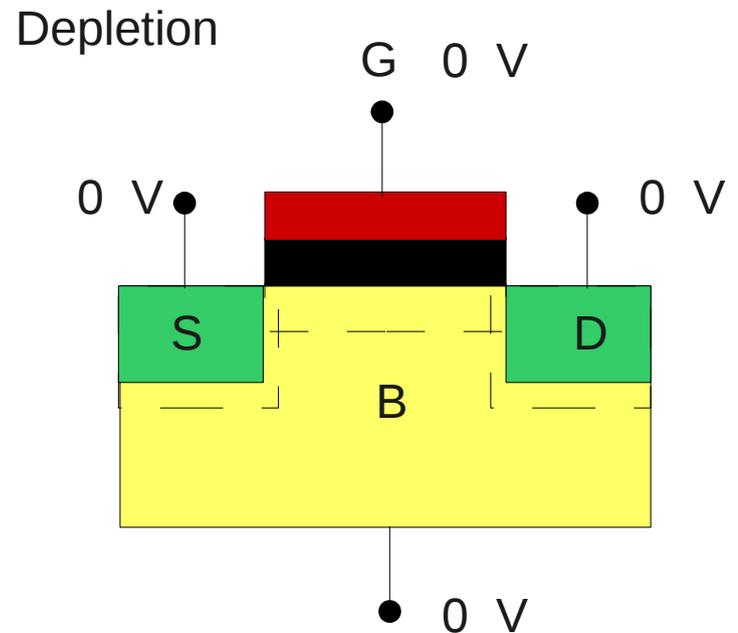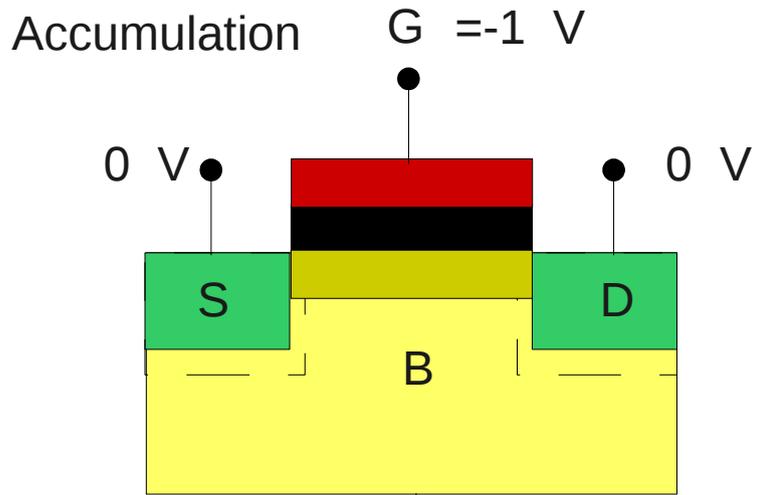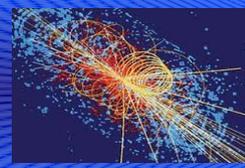Longer switches conduct better than minimum length one: reverse short channel effect





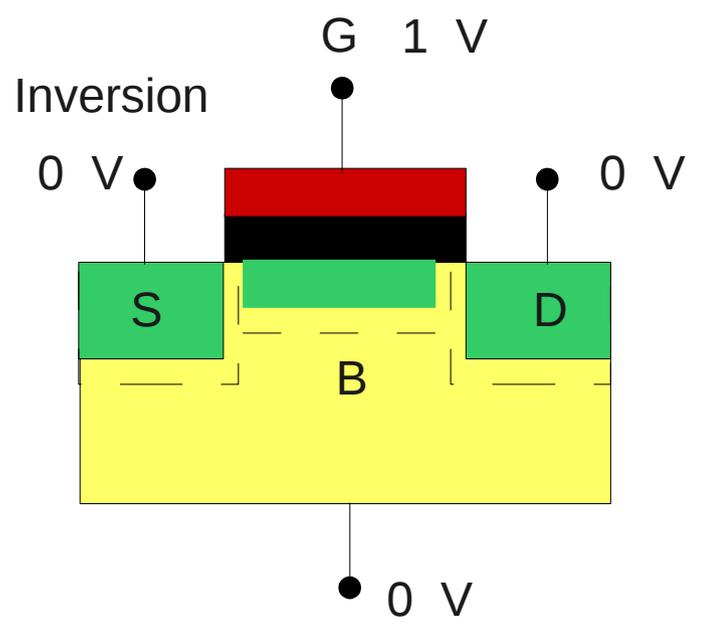
Switch on resistance: $R_{on} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$



- The gate voltage needs to maintain also the **depletion region**.
- For short channel device source and drain **depletion regions protrude** significantly in the channel.
- For the **same charge** store on the gate, **more carriers** can be attracted in the channel, since the depletion region is partially supported by source/drain

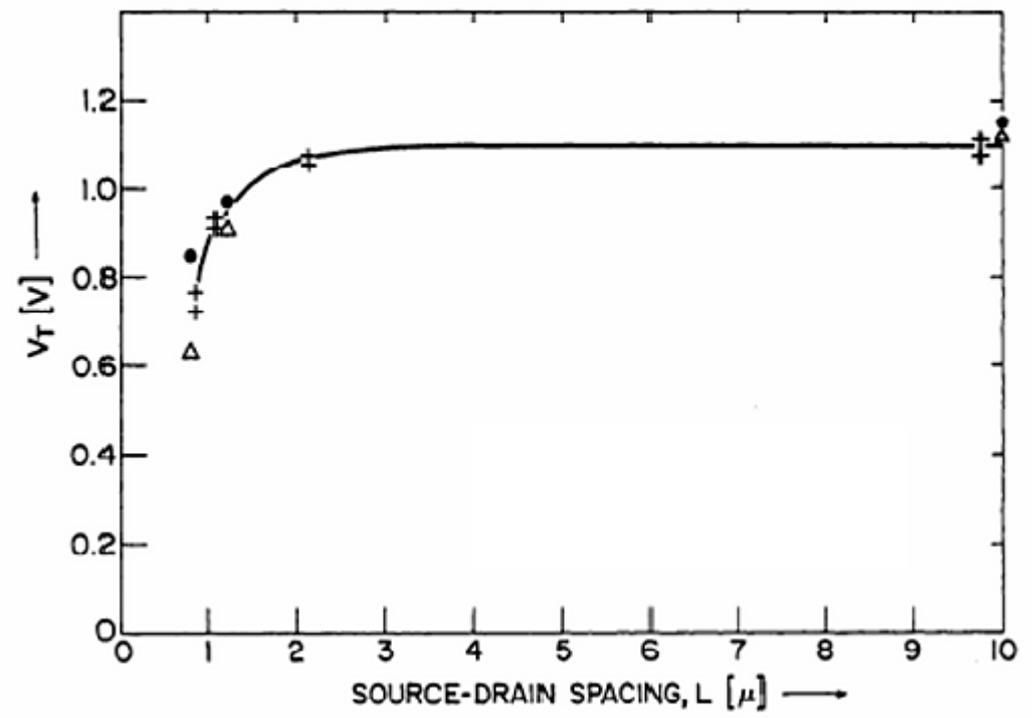
Example of traditional short channel effect: threshold is **lower** as channel length is **decreased**.



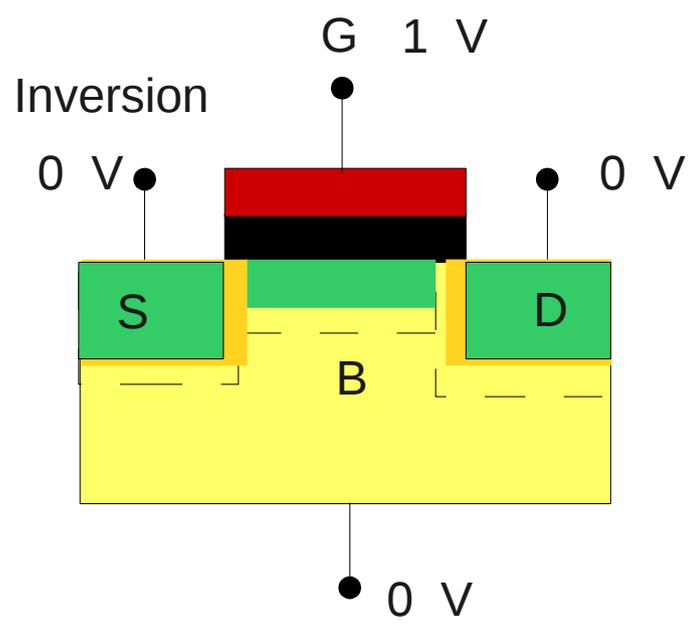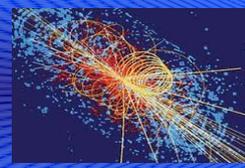


- To prevent excessive extension of the source-drain depletion region into the regions around the electrodes receive a stronger substrate doping (**halo doping**).
- When the channel is very short the two regions tend to **overlap**, the local substrate doping in the channel region is increased and the **threshold voltage increases**.
- Another reason to keep **away from minimum length** devices in analog design!

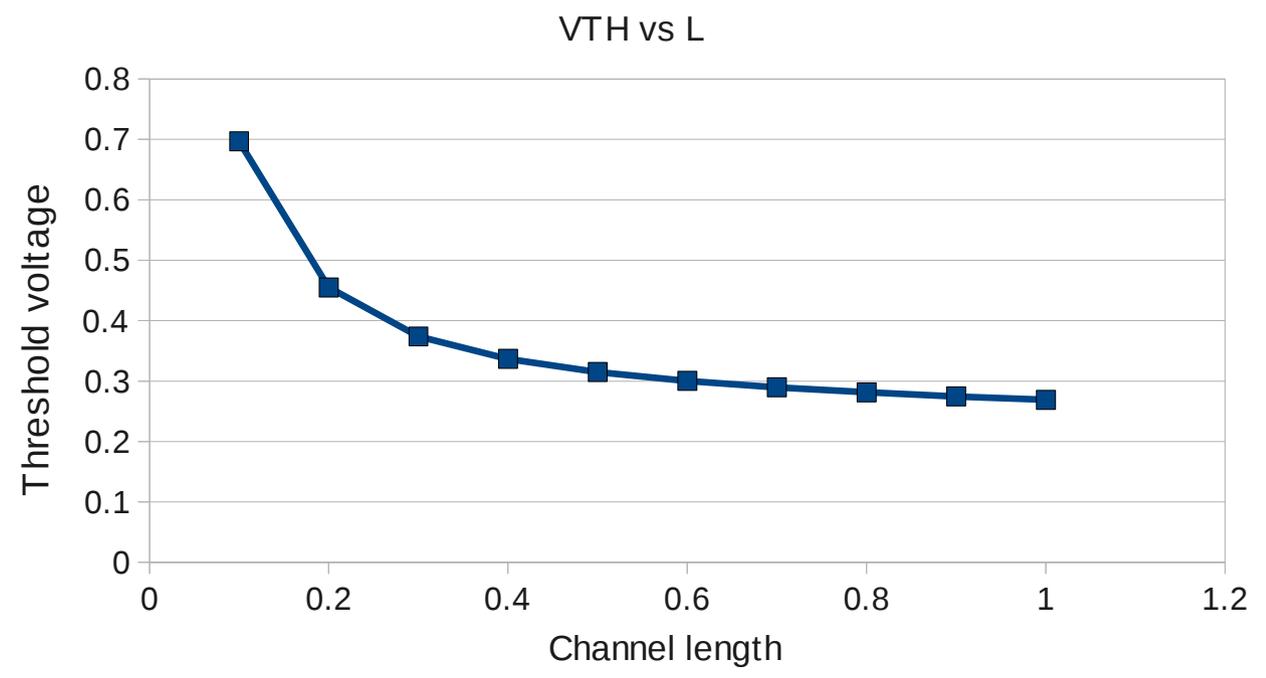Reverse short channel effect: simulated **threshold variation** as a function of **channel length** in a 90 nm CMOS process.





Which capacitor for storage?

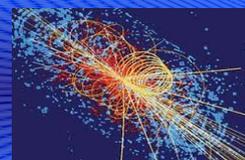

- **Poly-poly capacitors** in general not available **beyond 0.35 μm CMOS**.
- Alternatives: **MOS capacitors, metal-insulator-metal, vertical capacitors**.
- MOS capacitors in analogue memories in DST:

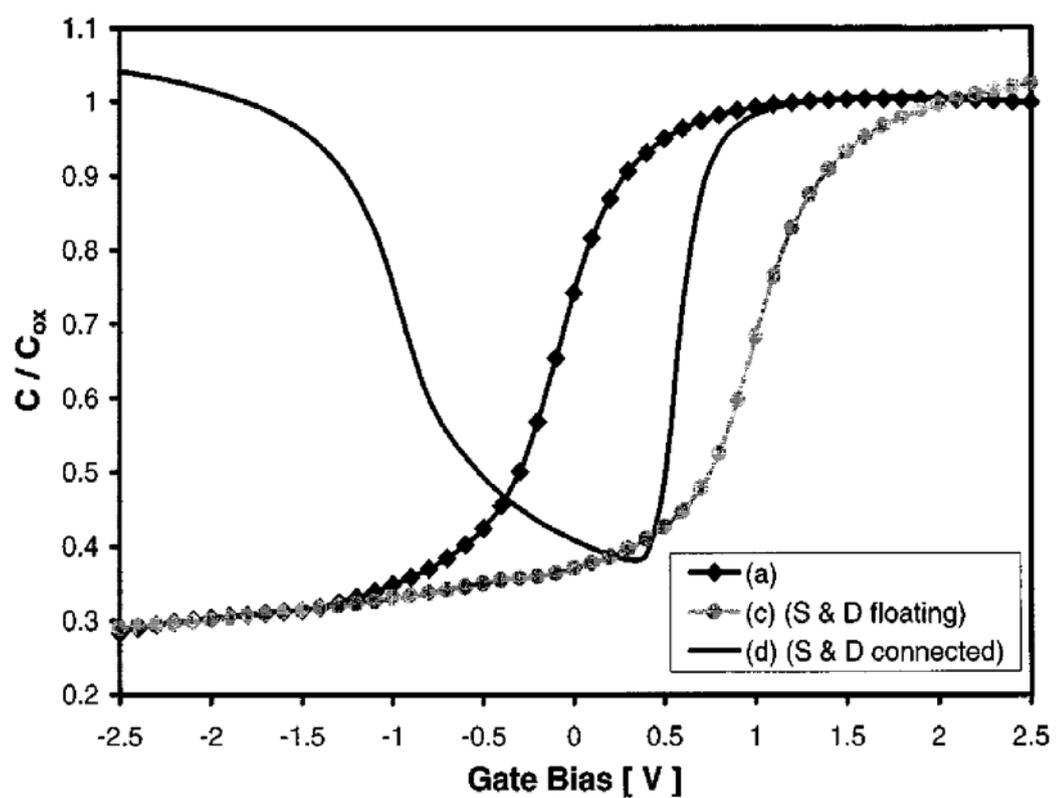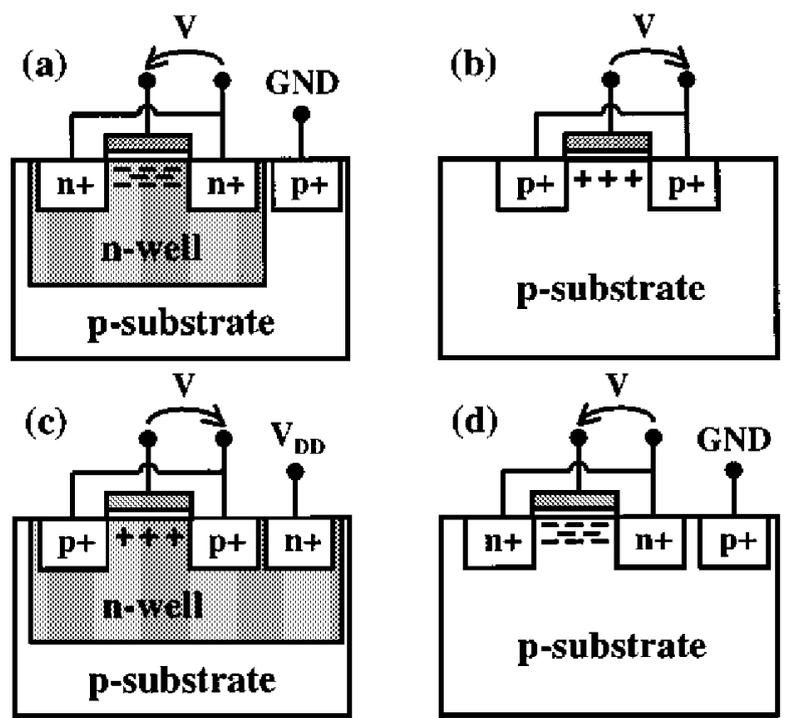
G. Anelli, F. Anghinolfi and A. Rivetti: "A Large Dynamic Range Radiation Tolerant Analog Memory in a Quarter Micron CMOS Technology", *IEEE TNS*, vol. 48, no. 3, June 2001.




- **MOS structures** offer **high specific capacitance**, good for keeping the stored values for long times (but gate leakage might be an issue in very scaled processes).



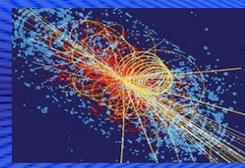Which capacitor for high sampling speed (1) ?




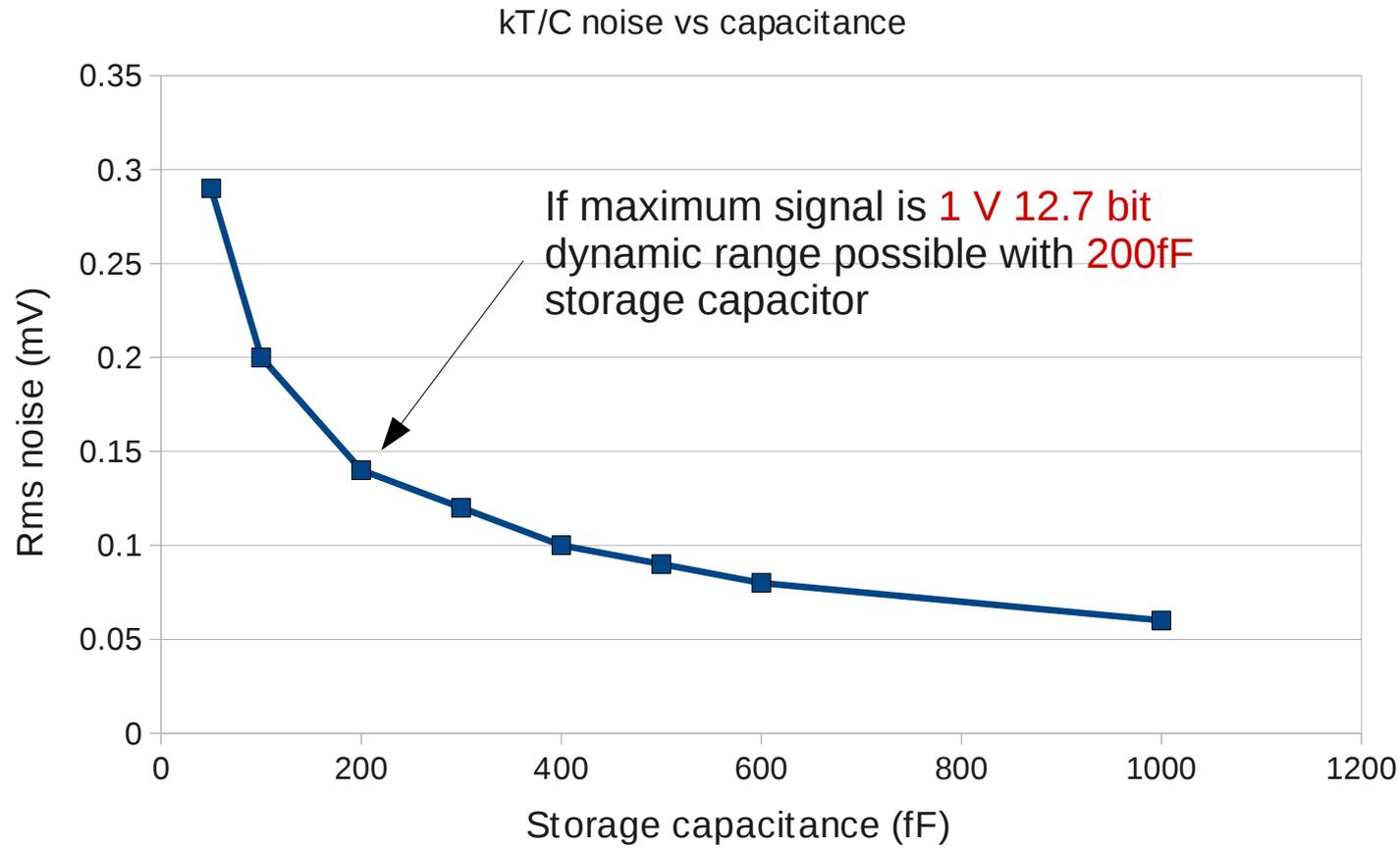- High input bandwidths require **small and fast** capacitors.
- What about **kT/C** noise?





Major concerns in using small capacitors come from leakage and charge injection


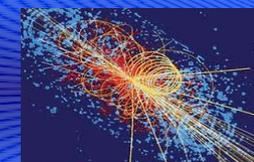
Which capacitor for high sampling speed (2) ?



- In deep sub-micron technologies (from **0.25 μm and beyond**) highly linear capacitors are obtained by sandwiching **two dedicated metal layers**.
- Specific capacitance may range from **0.5 $\text{fF}/\mu\text{m}^2$ to 2 $\text{fF}/\mu\text{m}^2$** .
- However, deep sub-micron technologies impose severe **pattern density rules** for each layer used in chip fabrication (diffusions, poly, metals...)
- To guarantee adequate inter-layer dielectric flatness after chemical-mechanical polishing each pattern should fill the area within a given range.
- This can be a serious issue for front-end chips, which usually implies regular **repetition of many channels** which tend to overfill selected areas.


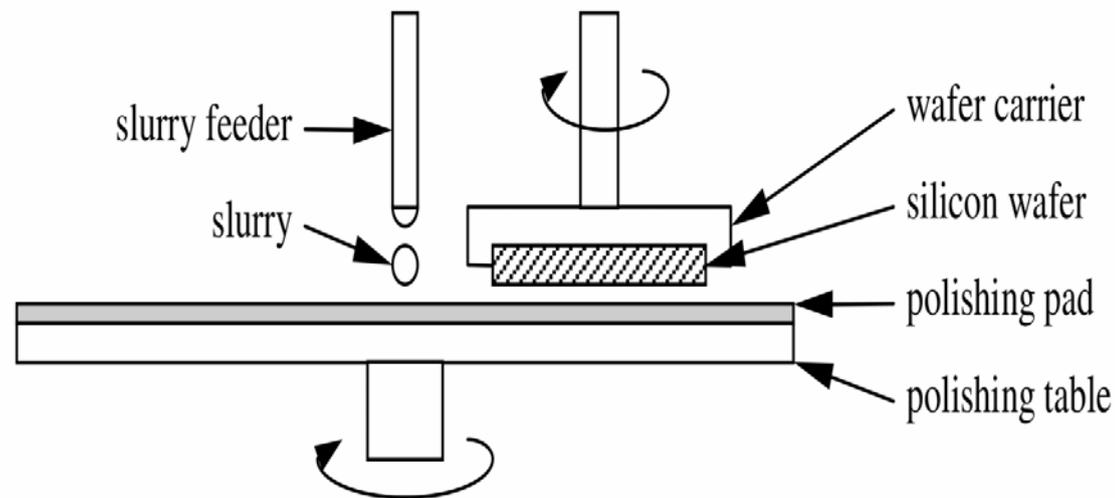
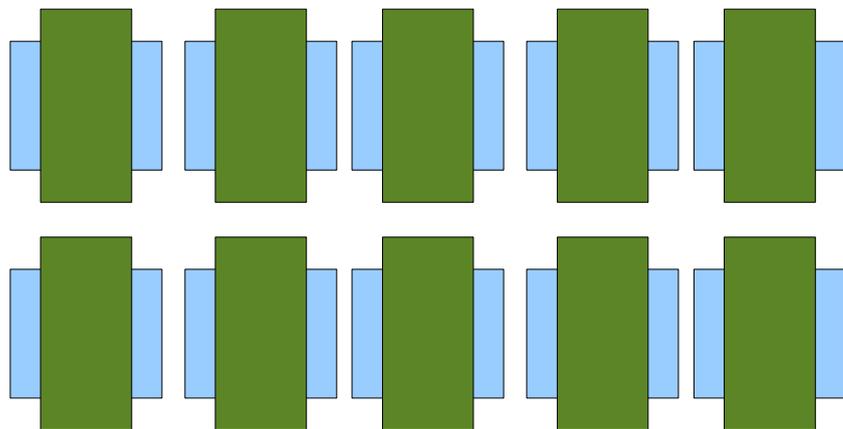


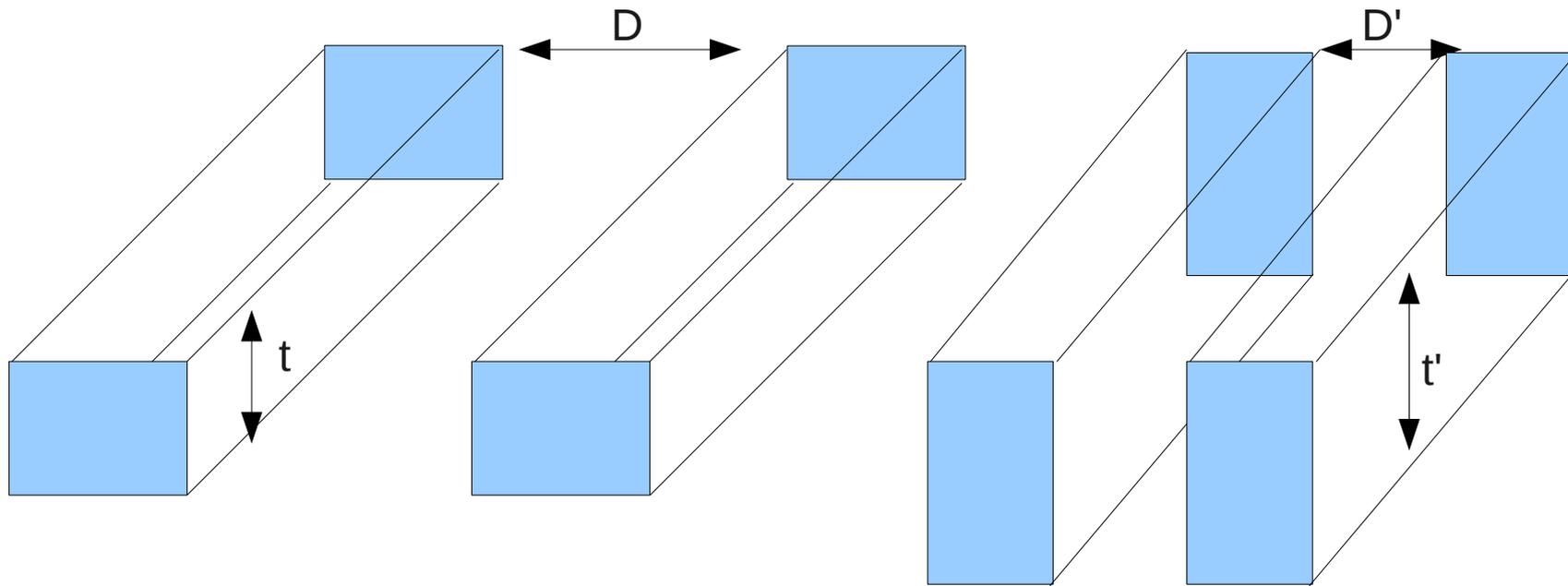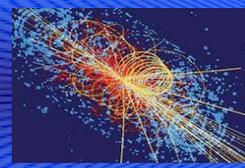Which capacitor for high sampling speed (3) ?




- Scaling requires also **finer pitch interconnects** and narrower lines;
- Vertical dimension grows to keep resistance acceptable;
- Vertical capacitance also grows, so **RC delays** are approximately constant;
- Many metal layers available. Stacking yield reasonable capacitance. ($0.5 - 1 \text{ fF}/\mu\text{m}^2$).

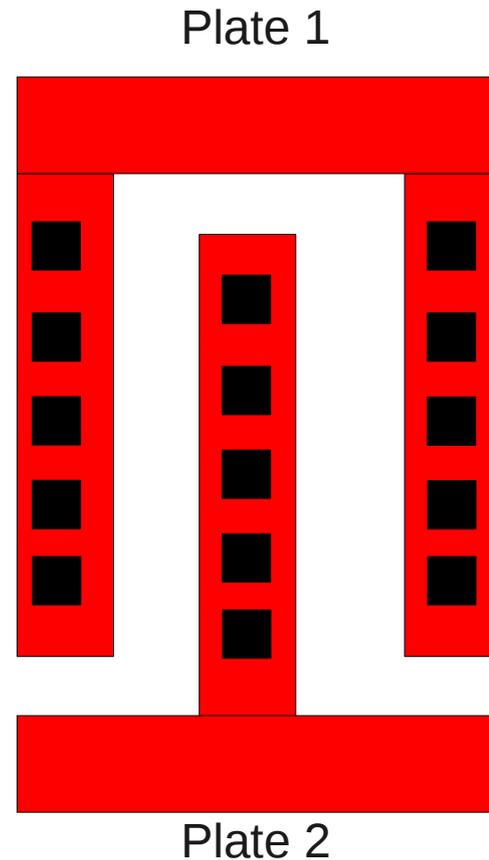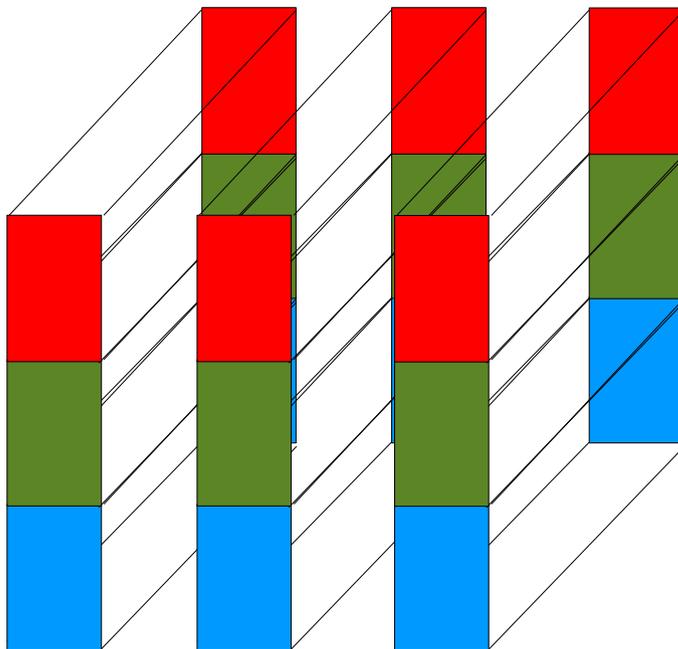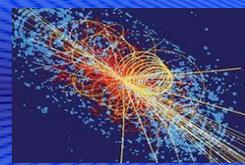Which capacitor for high sampling speed (4) ?




- Vertical capacitors used **native metal**, no extra mask required (cost);
- Capacitance density reasonable;
- Metal coverage can be **more than 50%**;
- There is no a “top” and “bottom” plate: both **equally sensitive to parasitic** capacitance.

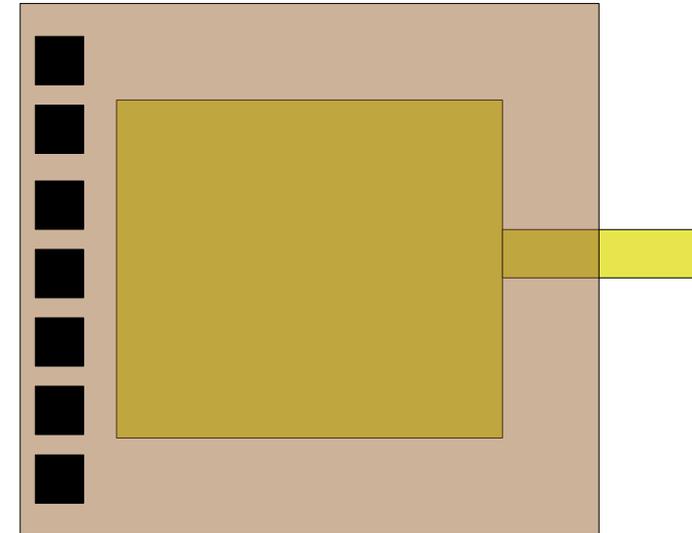Which capacitor for high sampling speed (5) ?



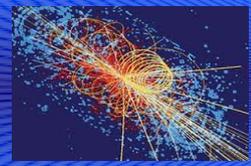- Other possibility: “sandwich capacitor”
- Possibility to minimize the parasitic capacitance of one plate;
- As good as the vertical one from the point of view of metal coverage...
- In general, use the one which has been modeled by the foundry (if any!).



- A lot of developments on high-speed waveform recorder/digitizer has been made in the framework of High Energy Astrophysics experiments (ICE cube, H.E.S.S, ANTARES, ANITA, AMANDA...)
- Main purpose: capture of fast transient signal from silicon photomultipliers.
- Developments also in the nuclear/particle physics community (MEG experiment at PSI).
- High sampling speed achieved also in non deep-submicron technologies
- However there is a general trend toward 0.25 μm and also 130 nm processes:
- Main motivation for scaling: increase the speed of the analog-to-digital conversion and reduced dead-time.
- In general, high speed waveform digitizers are characterized by:
 - Modest channel number (< 10)
 - Fairly high power consumption (40-150 mW/ch)
 - High dynamic range (12 bits or more)



“Waveform Digitization with Programmable Windowed Real-Time Trigger Capability”

→ 2 Gs/sec. with 2 GHz bandwidth and on chip ADCs, 0.25 μm CMOS.

W. Huang, S. W. Chiang and S. Kleinfelder, IEEE NSS Conference Record 2009, N13-50

“Design and Performance of the 6GHz Waveform Digitizing Chip DRS4”

→ 6 Gs/sec., 40 mW/ch, 850 MHz analog bandwidth, external ADC, 0.25 μm CMOS.

S. Ritt, IEEE NSS Conference Record 2008, N11-8

“The large analog bandwidth recorder and digitizer with ordered readout (LABRADOR) ASIC”

→ 3.7 Gs/sec. with 1 GHz bandwidth and on chip ADCs, 0.25 μm CMOS

G. S. Varner et al, NIMA (583) pp. 447-460.


“A 20 Gs/s sampling ASIC in 130 nm CMOS Technology”

→ Target: 20 Gs/sec with on board ADCs.

J. F. Genat et al., TWEPP 2010, Aachen, Germany

online: [http://indico.cern.ch/materialDisplay.py?](http://indico.cern.ch/materialDisplay.py?contribId=26&sessionId=15&materialId=slides&confId=83060)

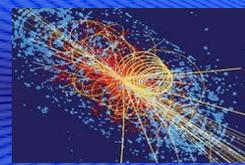[contribId=26&sessionId=15&materialId=slides&confId=83060](http://indico.cern.ch/materialDisplay.py?contribId=26&sessionId=15&materialId=slides&confId=83060)




W. Huang, S. W. Chiang and S. Kleinfelder, I
 →IEEE NSS Conference Record 2009, N13-50

TABLE I. ATWD CHIP PARAMETERS


Parameter	Value
Technology	0.25 um, 5-metal CMOS
Die size	4.9 x 2.7 mm
Prototype package	84-pin LCC (76 active pins)
PLL reference clock frequency	~28 – 33 MHz
PLL output frequency	0.9 – 1.05 GHz
Sample clock rate	1.8 – 2.1 GHz
Phase Noise	< -100 dBc/Hz at 1MHz offset
Number of sample points stored	1 Channel of 128 samples
Storage capacitor -3dB bandwidth	~2.2 GHz at $\leq 1V$, ~1GHz at 1.5V
Input signal range	0.0 – 1.7 V
Comparator gain and bandwidth	60 dB , 100MHz (-3dB)
Trigger decision speed	~7 ns
Fixed pattern noise	12.9 mV, RMS
Temporal noise, all sources	~0.625 mV, RMS

ATWD chip

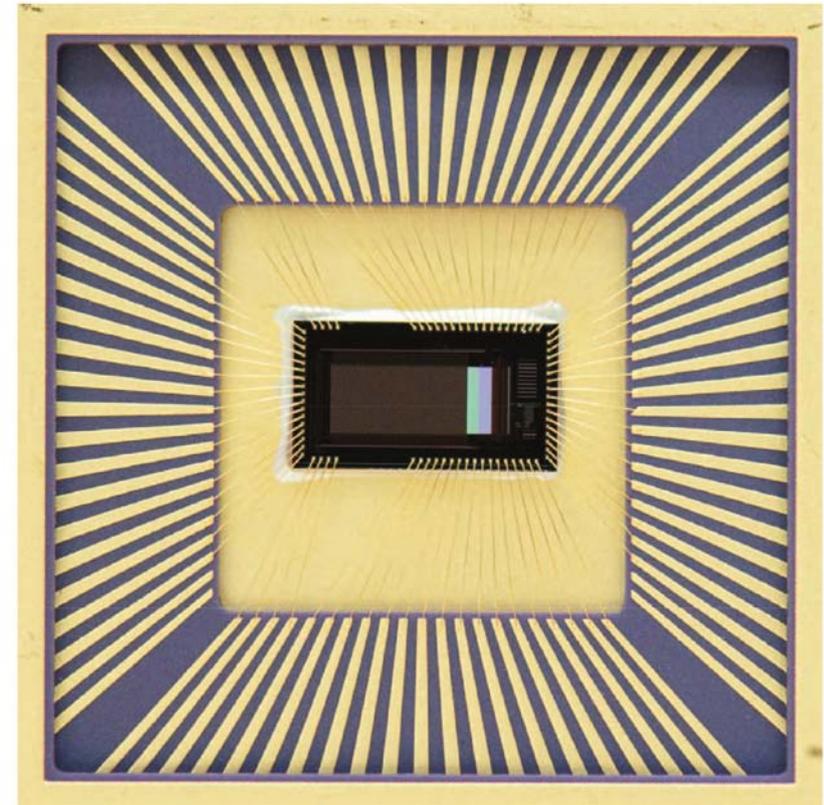




Fast sampling: design example (2)

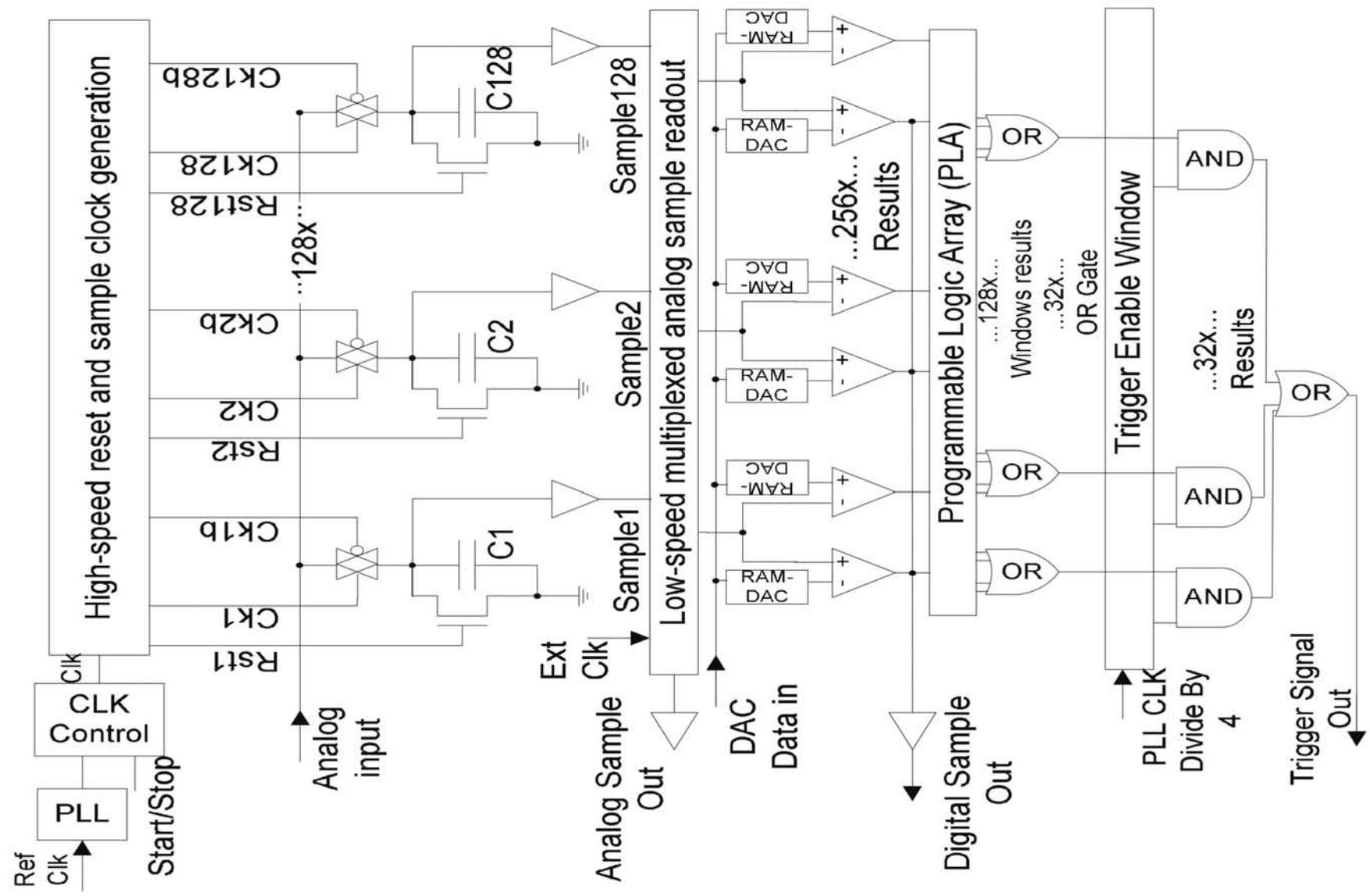







Fast sampling: design example (3)

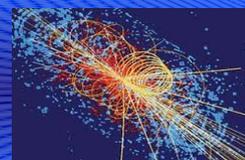

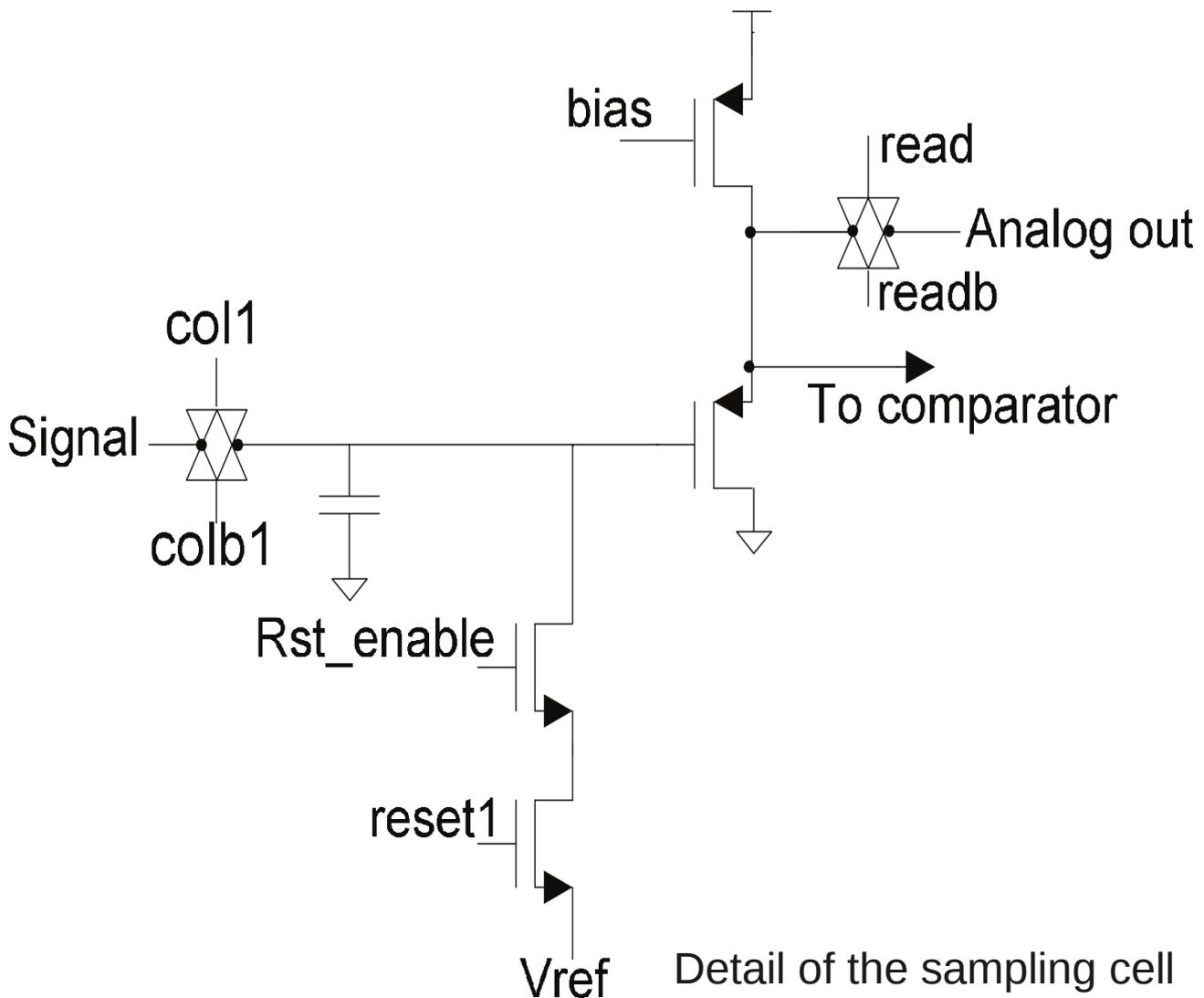W. Huang, S. W. Chiang and S. Kleinfelder, IEEE NSS Conference Record 2009, N13-50




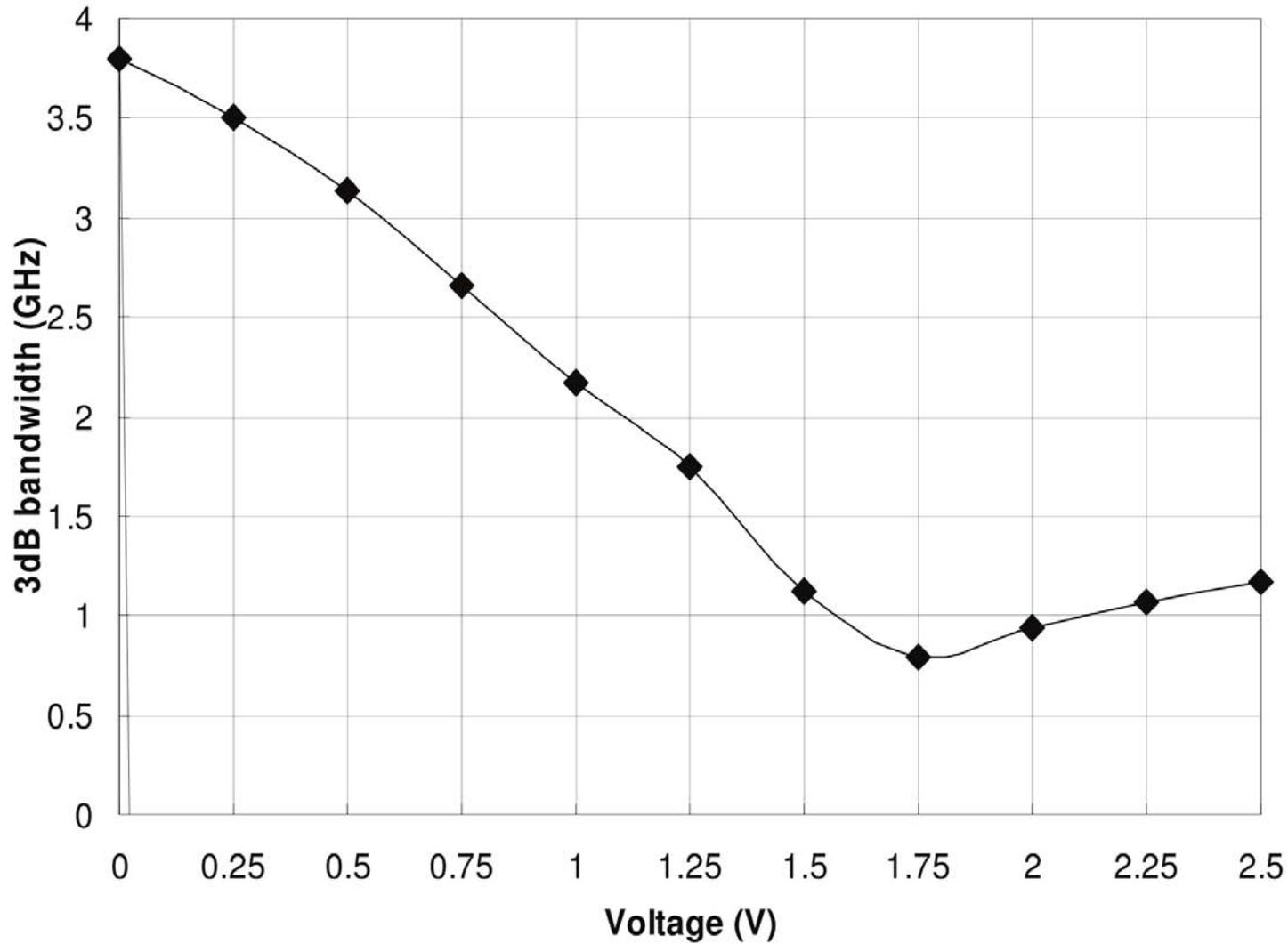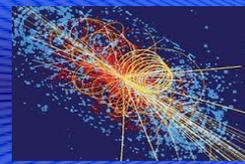

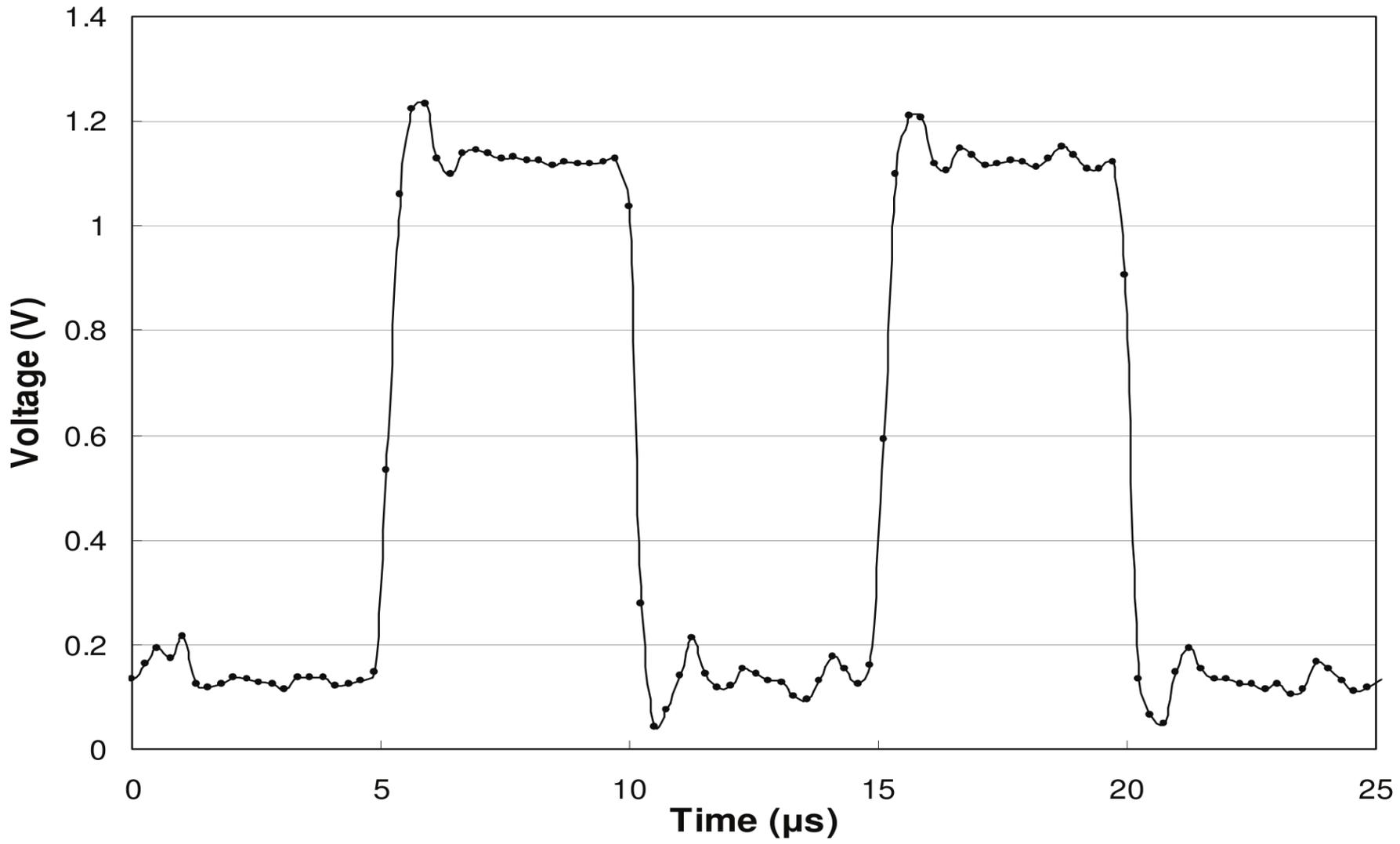





Fast sampling: design example (5)

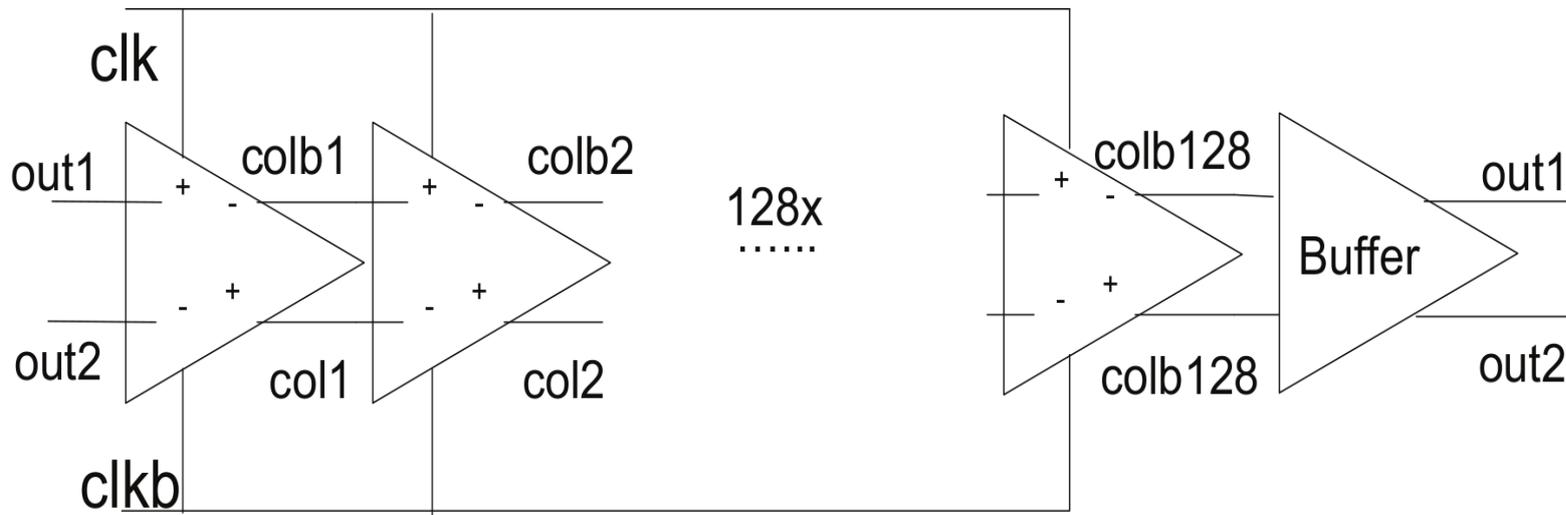

High speed sampling achieved by:

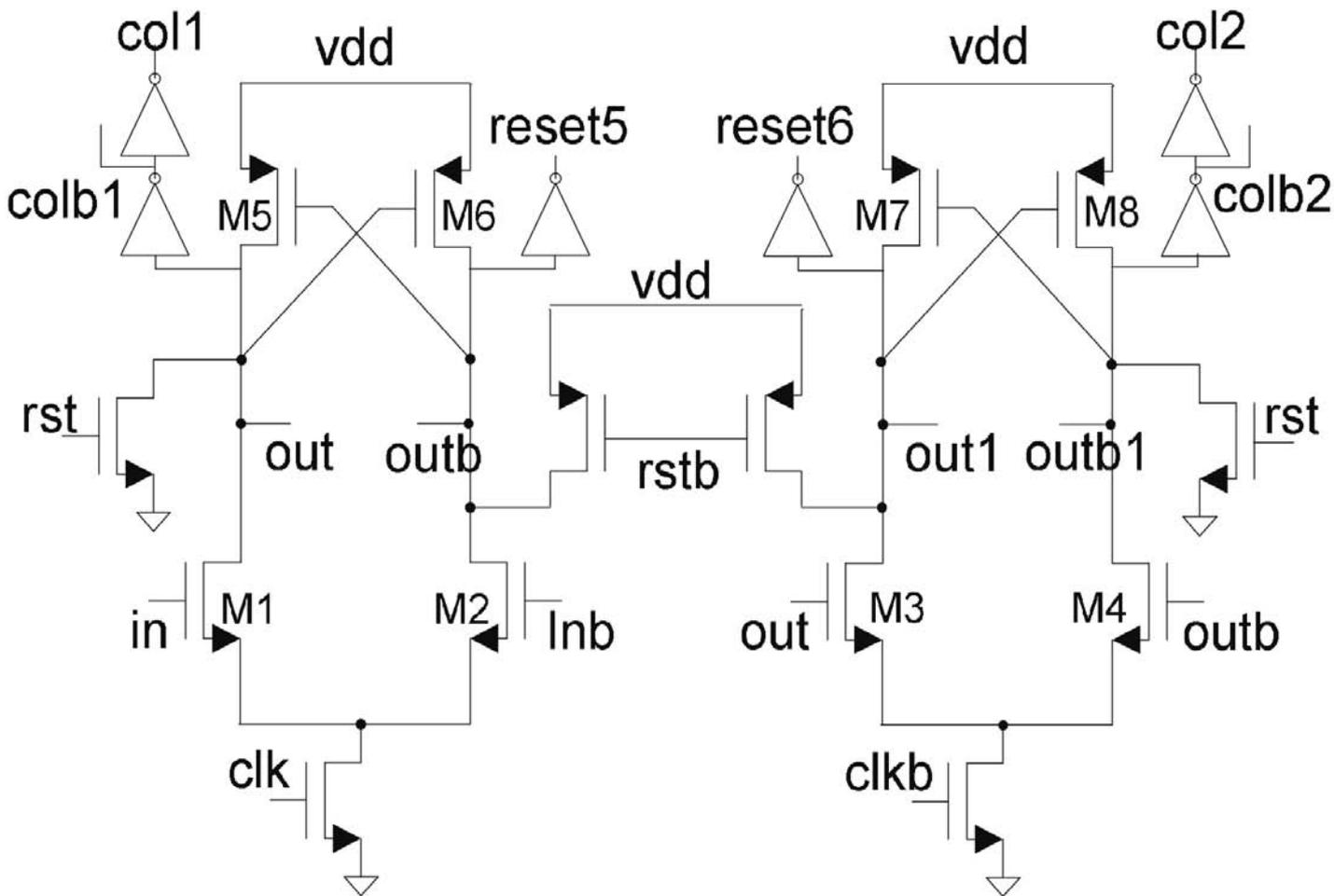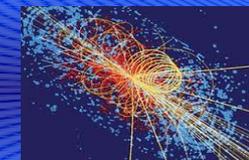- Multiplying external low clock frequency with an on **chip PLL**;
- Using a fast shift registers with custom **differential** master-slave **flip-flops**;
- Sampling on **both clock edges** of the high speed clock.



- High speed differential flip flop for the sampling register.
- Digitization is done on chip with an array of 128 Wilkinson ADC working in parallel.



New waveform sampler in 0.13 μm CMOS



Waveform Sampler ASIC specs

Channels 4 + 1 test

Sampling rate 10-15 GS/s

Analog Bandwidth 1-2GHz

Self and External trigger

Dynamic range 800mV

Sampling window 400ps-800ps (or 8 delay cells)

DLL Timing generator Internal phase comparator and charge pump, external LP filter

DC Input impedance $\frac{1}{2}$ 50 Ω internal, $\frac{1}{2}$ external

Conversion clock Adjustable 500MHz 1GHz internal ring oscillator.


Maximum conversion time 8 μs .

Read clock 40 MHz. Readout time (4-channel) 4 x 256 x 25ns=25.6 μs

Power 40mW/channel

Power supply 1.2V

Process IBM 8RF-DM (130nm CMOS)

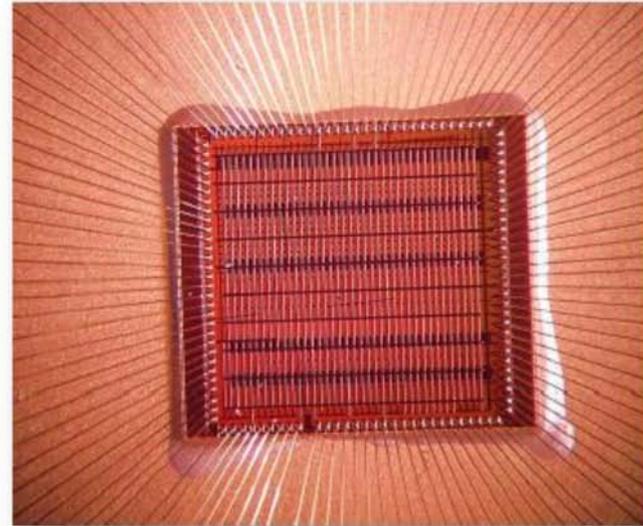



NECTAr: New electronics for the Cherenkov Telescope Array


S. Vorobiov^{a,*}, J. Bolmont^b, P. Corona^b, E. Delagnes^c, F. Feinstein^a, D. Gascón^d, J.-F. Glicenstein^c, C.L. Naumann^b, P. Nayman^b, A. Sanuy^d, F. Toussanel^b, P. Vincent^b

^a LPTA, Université Montpellier II & IN2P3/CNRS, Montpellier, France

^b LPNHE, Université Paris VI & IN2P3/CNRS, Paris, France

^c IRFU/DSM/CEA, Saclay, Gif-sur-Yvette, France

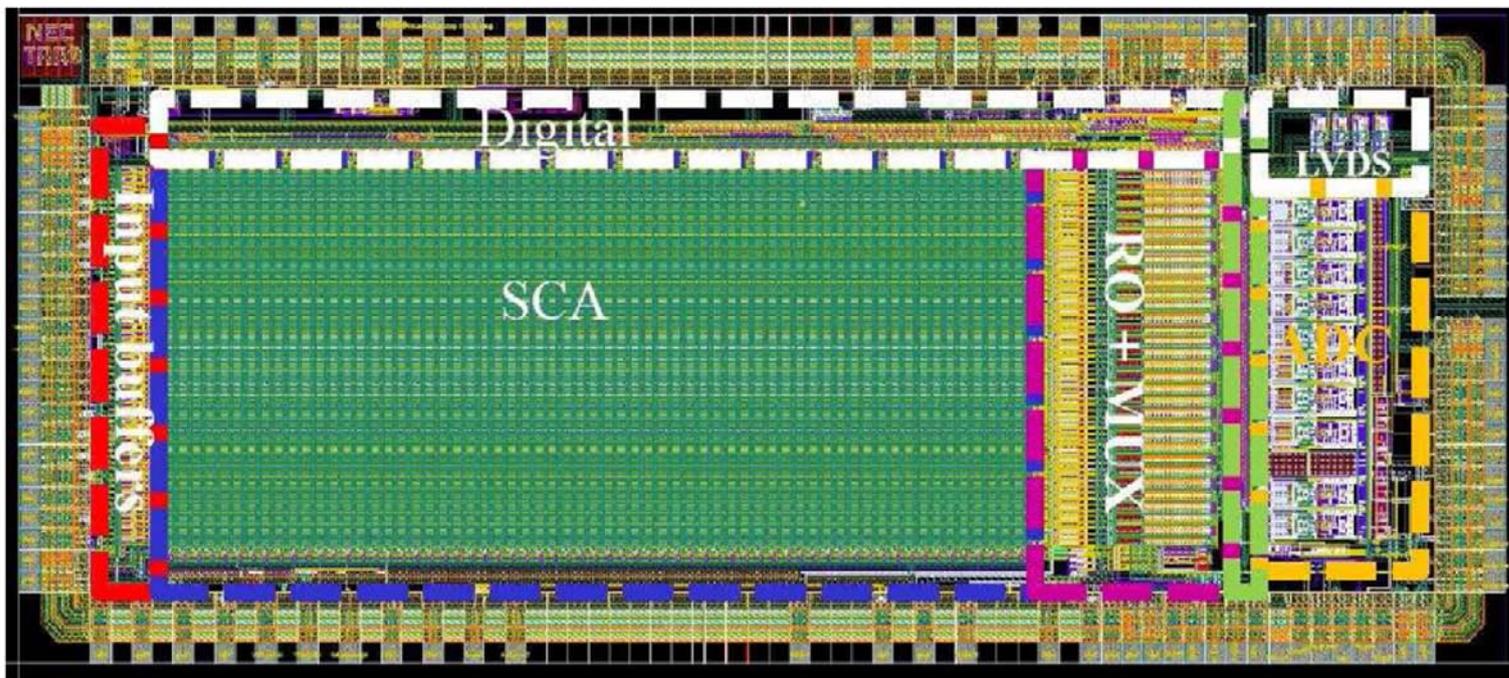^d ICC-UB, Universitat Barcelona, Barcelona, Spain





NECTAr chip specifications

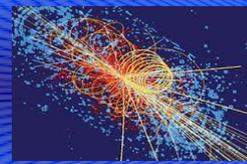


Table 1


Expected NECTAr0 chip performances.

Parameter	Value
Power consumption	300 mW
Maximal signal	2 V
Sampling frequency	0.4–3.2 GHz
Analog bandwidth	0.3–0.5 GHz
Memory depth	1024 samples
Readout freq. (16 samples)	> 800 kHz
Dynamic range	~ 12 bits
Integral nonlinearity	< 1%
Crosstalk	< 0.3%
Sampling jitter	< 15 ps rms
Number of channels	2 differential ch.
Total noise	0.65 mV rms


High speed digitization is achieved with a shared 12 bit, 25 Ms/sec. ADC.



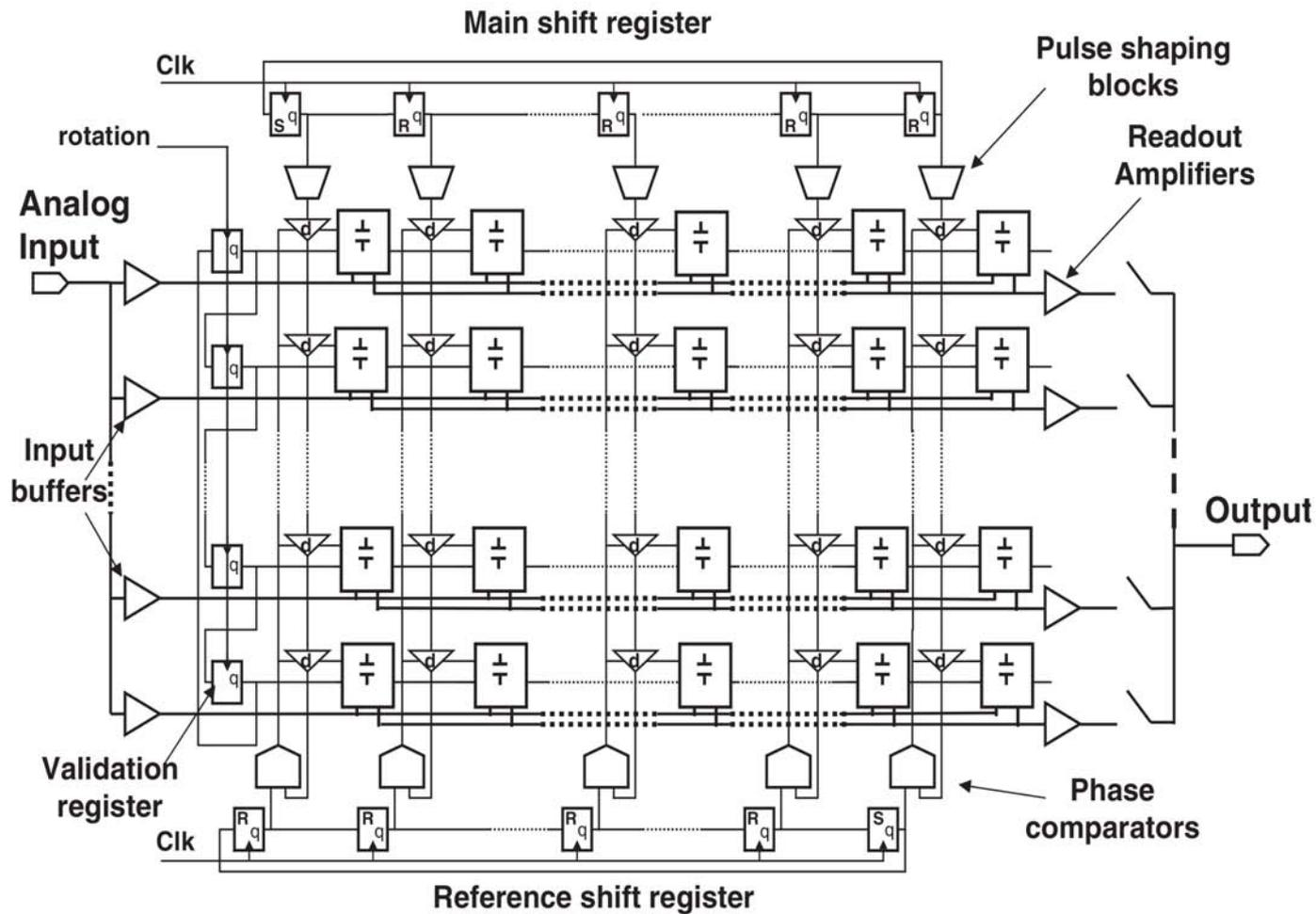E. Delagnes et al. / Nuclear Instruments and Methods in Physics Research A 567 (2006) 21–26



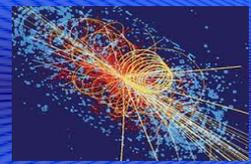- Memory cells are arranged in a 16 x 16 matrix
- Samples is $1/f_s$ along the columns and $16/f_s$ along the row.



- The full digitization of the signal allows not only the straightforward amplitude measurement, but also timing extraction.
- To achieve very precise time measurement several corrections on the data can be needed.
- However such corrections could be nicely implemented on FPGA.
- Fast waveform sampling does not require TDC.

A nice example:

Nuclear Instruments and Methods in Physics Research A 602 (2009) 438–445

Sub-10 ps monolithic and low-power photodetector readout

L.L. Ruckman, G.S. Varner *

Department of Physics and Astronomy, University of Hawaii, 2505 Correa Road, Honolulu, HI 96822, USA

Testing method: split the same signal in two digitizing channels and measure the time difference.

Test done with the BLAB1 (Buffered LABRADOR) chip described in:


Nuclear Instruments and Methods in Physics Research A 591 (2008) 534–545



Timing with high speed waveform samplers (2)




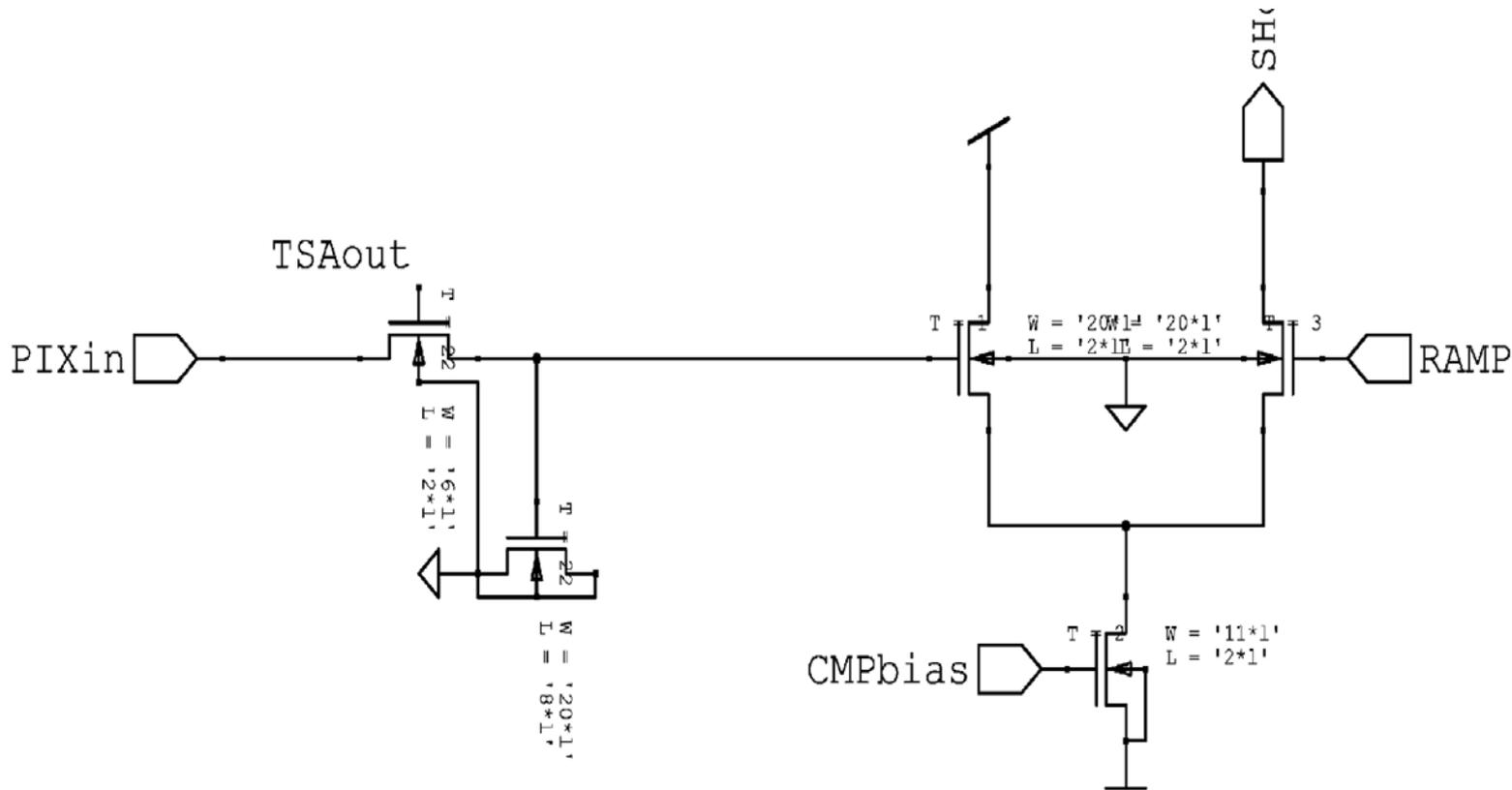- One of the peculiarity of the BLAB1 chip is its small sampling capacitor (only 14 fF).
- However kT/C noise is still ok! (0.54 mV rms)





BLAB1 sampling cell

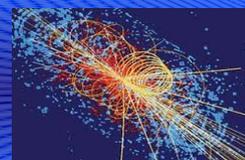- One comparator per cell
- External capacitor for ramp generation
- External counter for the wilkinson ADC.



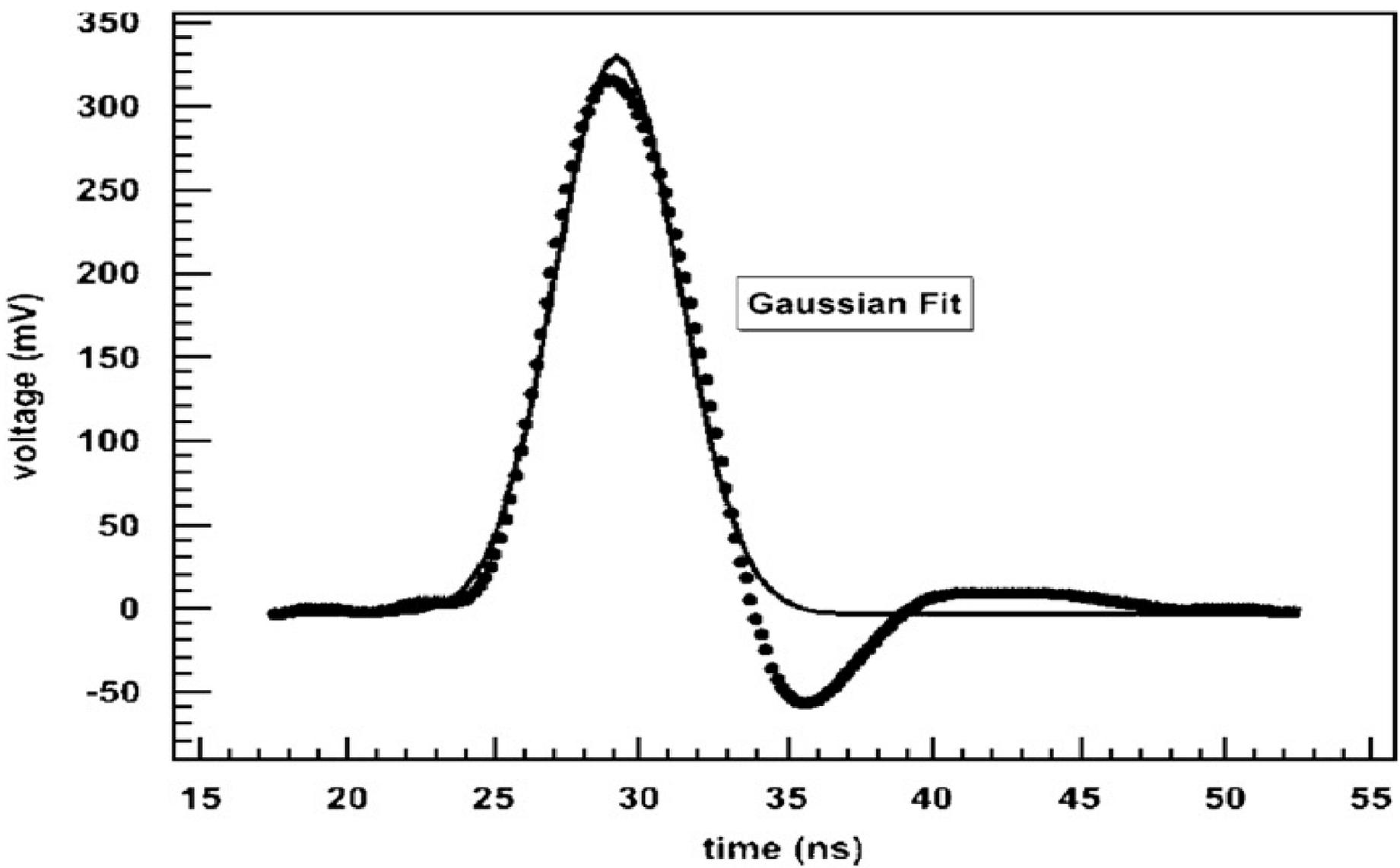→ Photodetector pulse recorded by the ASIC



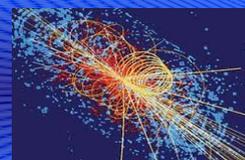

→ Raw timing between two channels...Already quite good (76 ps rms)



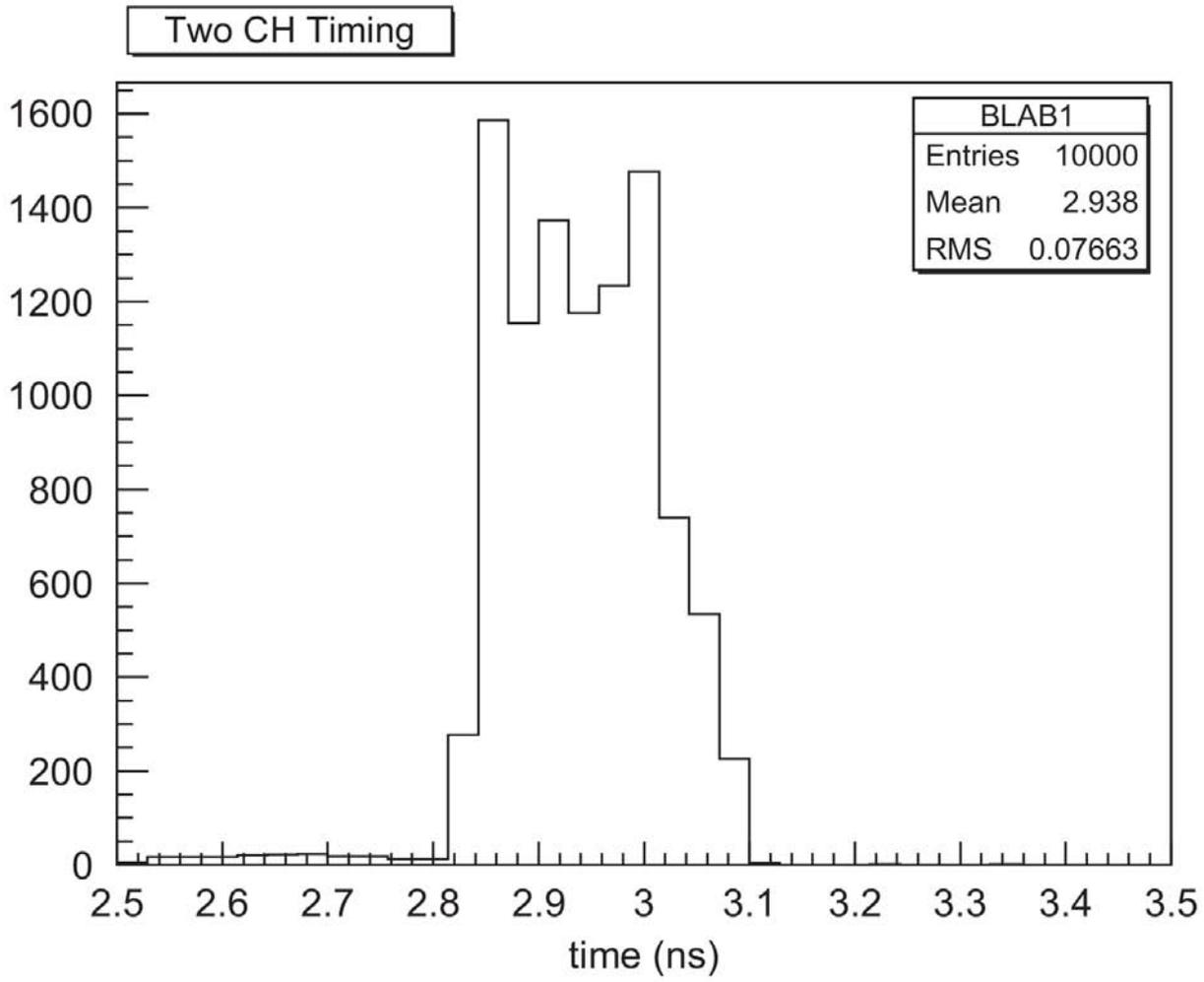


Fig. 13. Raw timing performance after simple timebase correction.

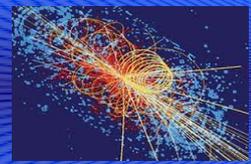


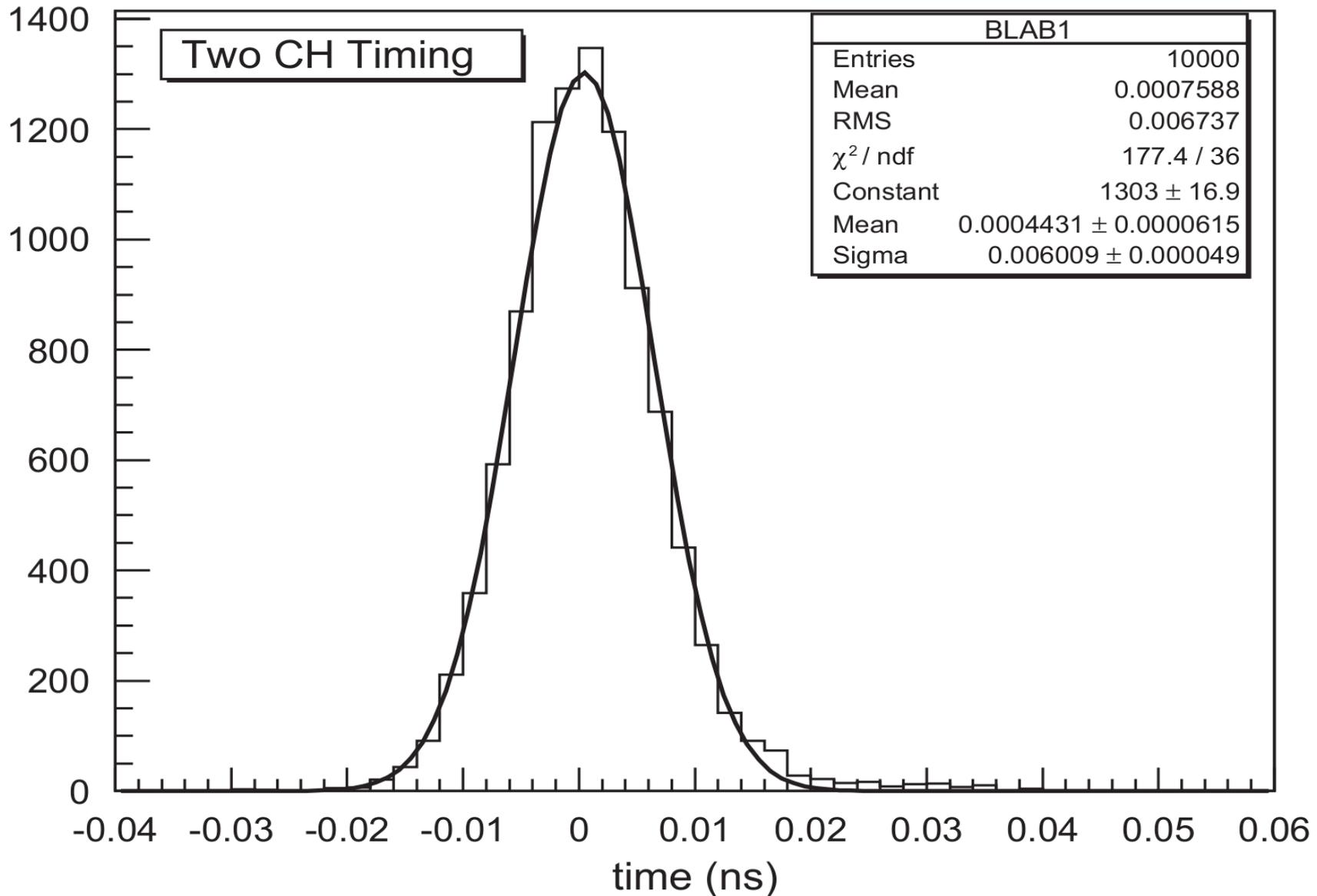→ Timing after calibration refinement: 6.7 ps.







- Basically, (almost) all the chips seen so far employ Wilkinson ADC for conversion
- However, driven by consumer applications and favored by the evolution of CMOS technology the performance of ADC converter are improving at an impressive speed
- ADC figure of merit: $P/(2^{\text{ENOB}} \text{ min (fs, 2ERBW)})$, with P=power consumption, fs=sampling frequency, ENOB=effective number of bits.
- State of the art 10 year ago: 9.4 ENOB, 40 Ms/sec, 50 mW, FoM=1.85 pJ/step
- In general not feasible to integrate the ADC after the preamplifier, so analog memories were needed also at relatively low sampling speed (like 40 Ms/sec of the LHC front-ends)

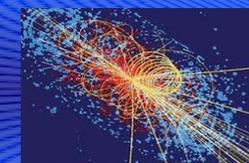

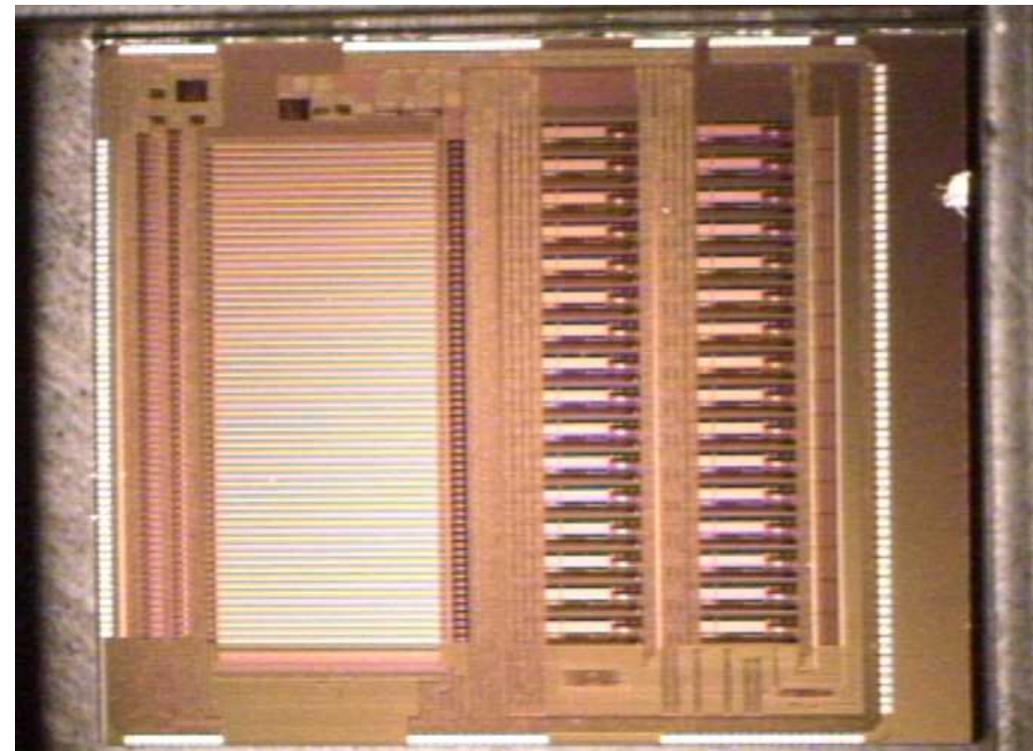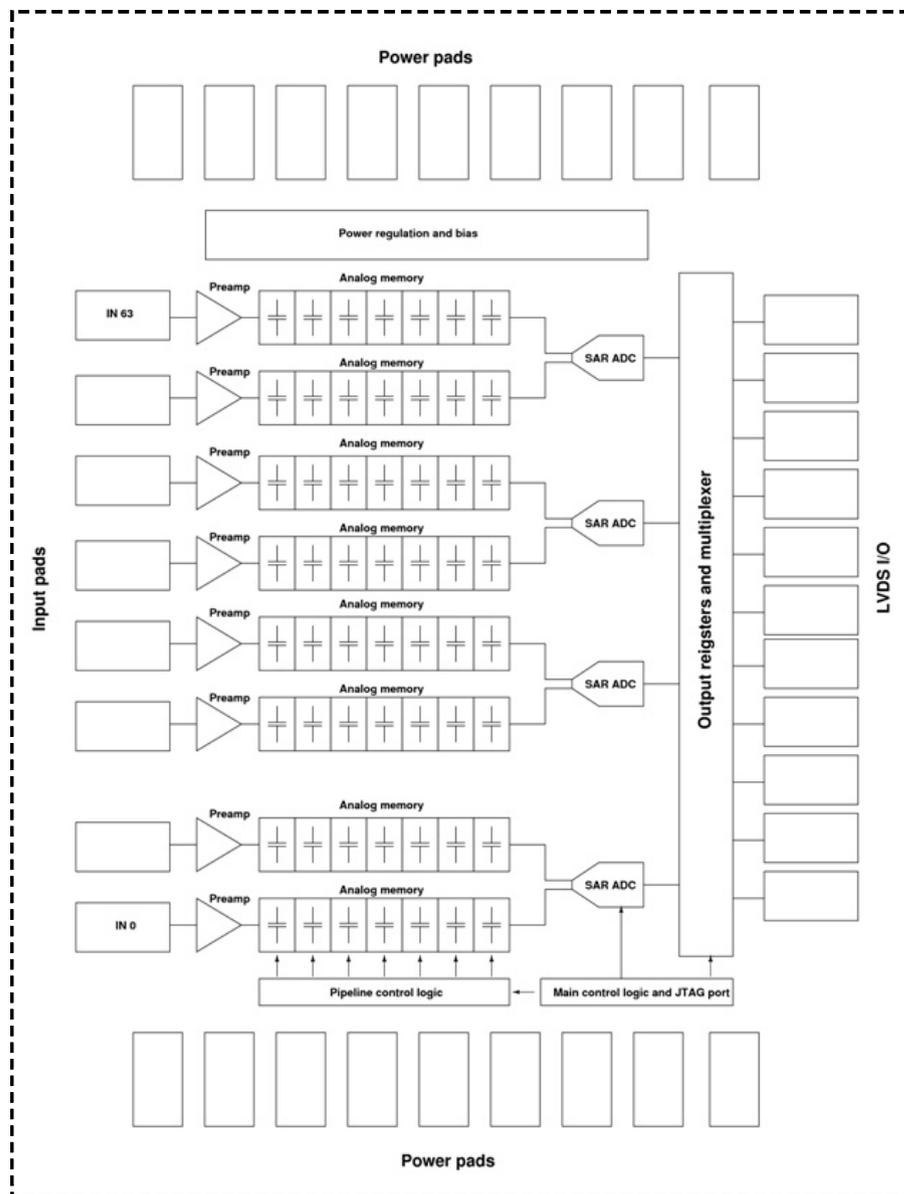■ Preamplifier, Analog Storage and Conversion from Analog to Digital (PASCAL)





1 cm

CMOS 0.25 μm
 Sampling frequency 40 MHz.
 Digitization < 1 ms
 32 10 bit SAR ADC in two rows



10 years old SAR ADC

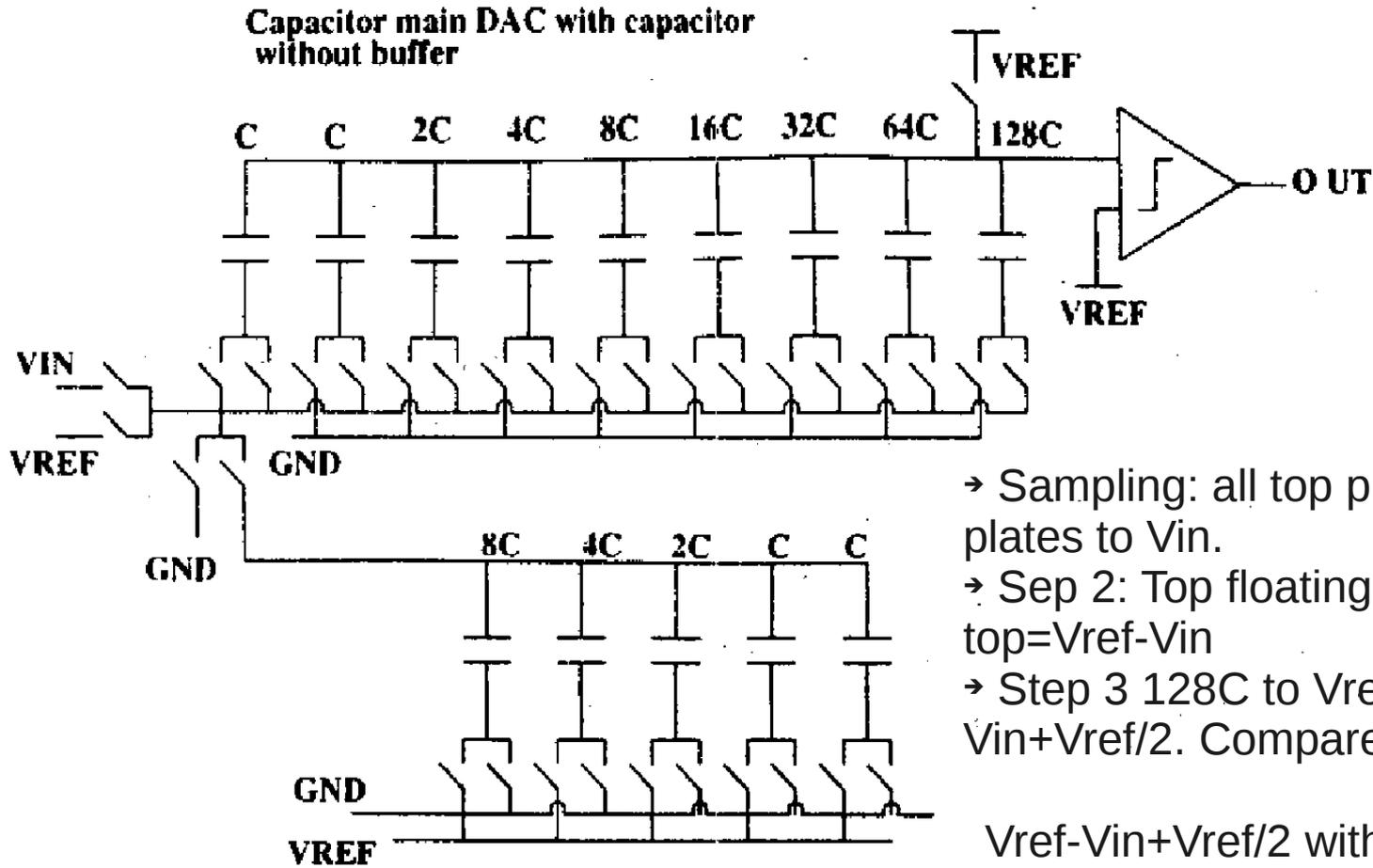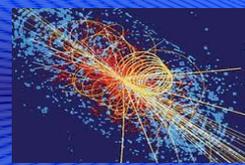

- Sampling: all top plates to Vref, all bottom plates to Vin.
- Sep 2: Top floating, bottom to gnd. Voltage on top= $V_{ref}-V_{in}$
- Step 3 128C to Vref, voltage on top= $V_{ref}-V_{in}+V_{ref}/2$. Compare:

$V_{ref}-V_{in}+V_{ref}/2$ with V_{ref} , equivalent to testing: $-V_{in}+V_{ref}/2 < 0$. If yes, switch 64 C to Vref. If no switch 64C to Vref and return 128C to GND, and so on...

40 MHz clock
 10 clock cycles for conversion + 2 for sampling
 9.1 ENOB at 3.2 Ms/sec, 3 mW, 1.85 pJ/step



A 9.4-bit, 50-MS/s, 1.44-mW Pipelined ADC Using Dynamic Source Follower Residue Amplification

Jason Hu, Noam Dolev, and Boris Murmann, *Member, IEEE*

N stage in cascade.

First stage: compare V_{in} to V_{ref}


If $V_{in} > V_{ref}$, $V_{out} = 2(V_{in} - V_{ref})$ Bit=1


If $V_{in} < V_{ref}$, $V_{out} = 2V_{in}$, Bit=0

Then second stage takes over...

Unfortunately not as simple to implement in practice...


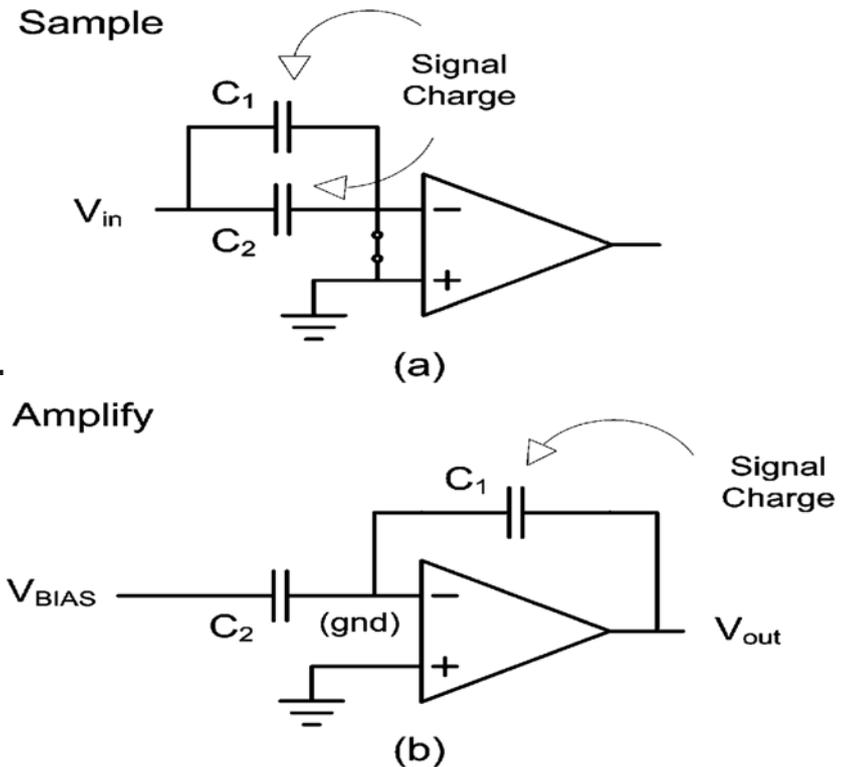
Key point: op-amp used in 2X multiplications require power.



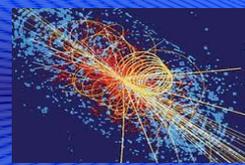


A 9.4-bit, 50-MS/s, 1.44-mW Pipelined ADC Using Dynamic Source Follower Residue Amplification

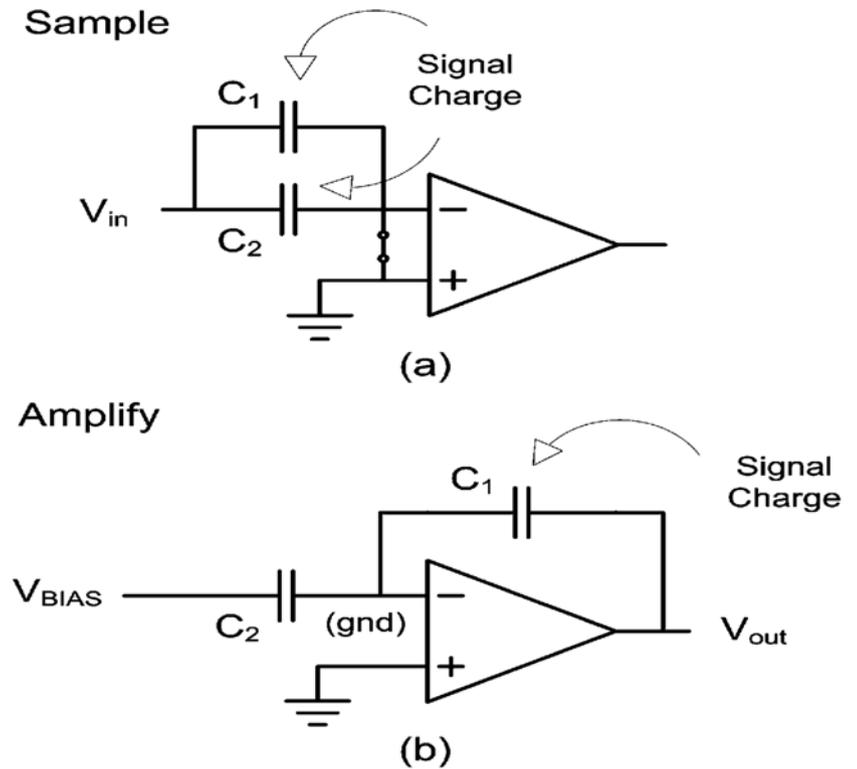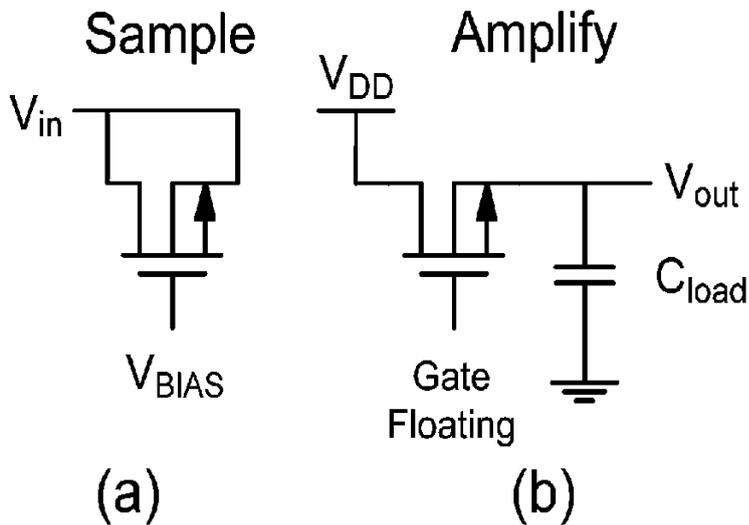
Jason Hu, Noam Dolev, and Boris Murmann, *Member, IEEE*



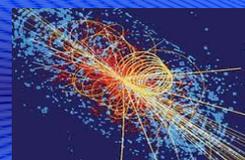How to replace an op-amp....
FoM 115 fJ/step, 90 nm CMOS




Sample

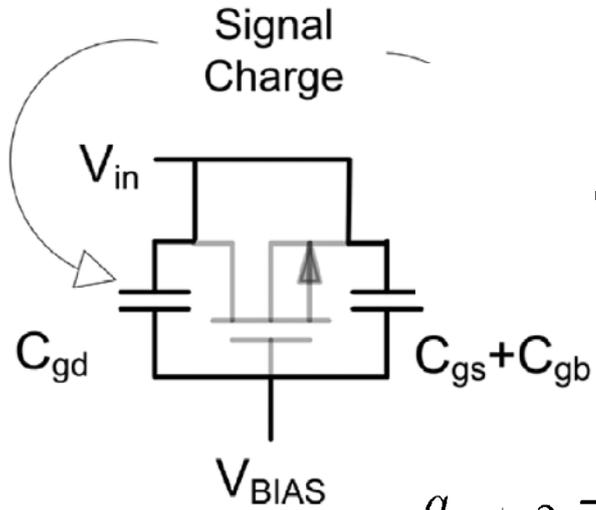



$$q_{\text{gate1}} = -(C_{\text{gs}} + C_{\text{gd}} + C_{\text{gb}})v_{\text{in}}$$

$$q_{\text{gate2}} = C'_{\text{gd}}v_{\text{gd}} = C'_{\text{gd}}v_{\text{g}} = C'_{\text{gd}}(v_{\text{out}} + v_{\text{gs}}) \cong C'_{\text{gd}}v_{\text{out}}$$


Amplify

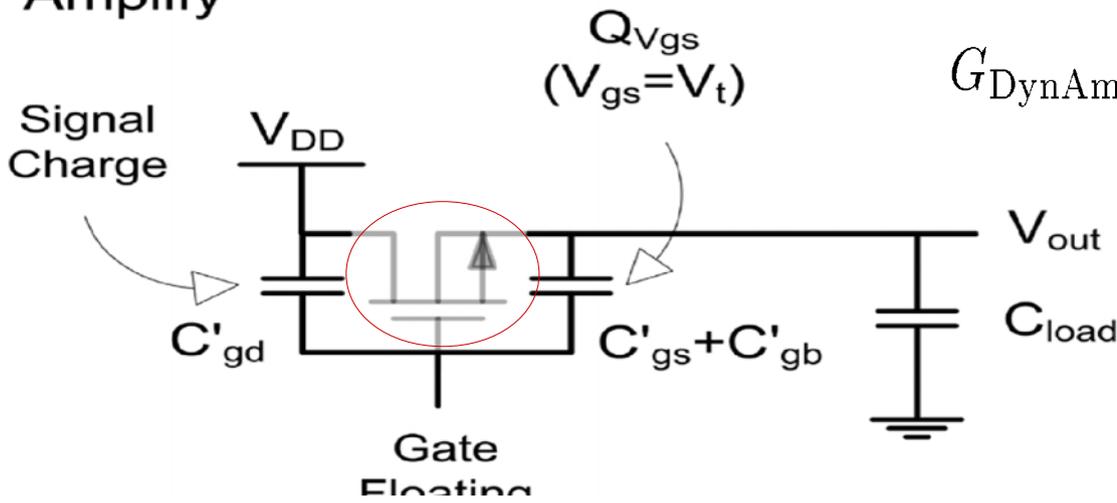
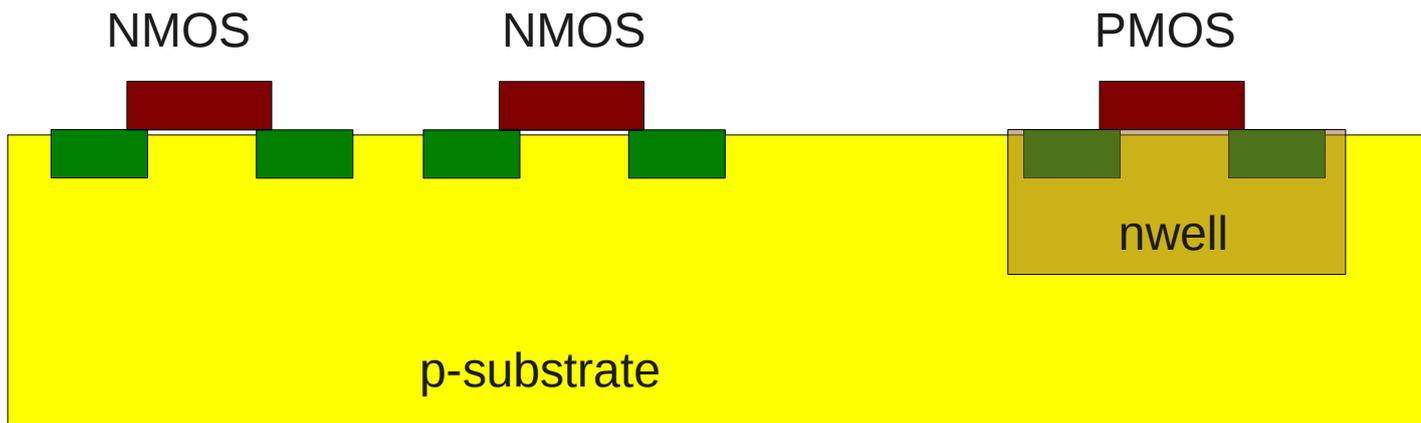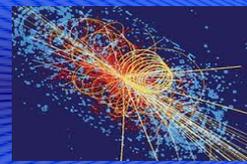
$$G_{\text{DynAmp}} = \frac{v_{\text{out}}}{v_{\text{in}}} \cong -\frac{C_{\text{gs}} + C_{\text{gd}} + C_{\text{gb}}}{C'_{\text{gd}}}$$



Standard nwell process

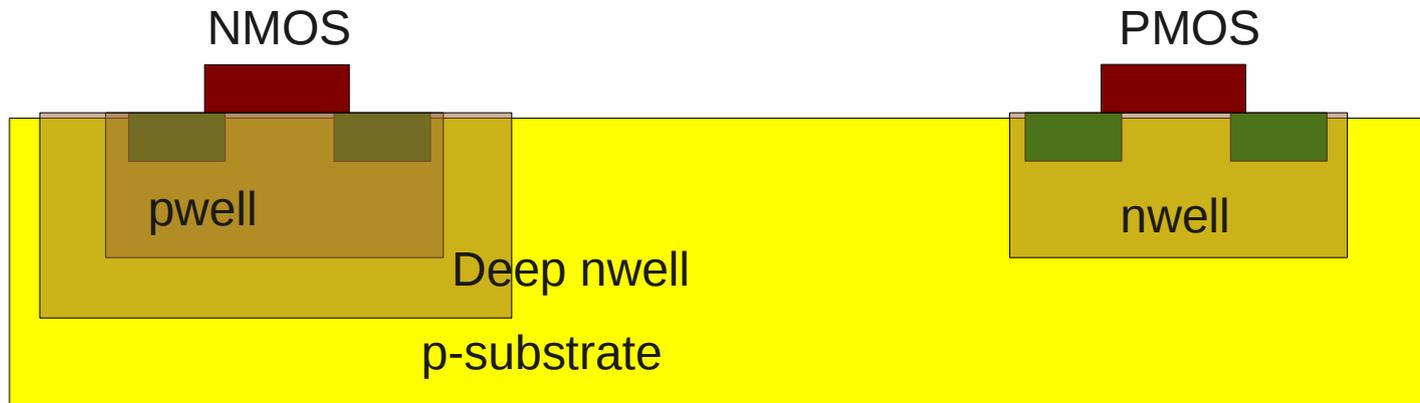

Triple well possible in very deep submicron processes (0.13 μm and beyond)




- Very exciting developments have been done and are in progress in the field of fast waveform digitizers for application in detector read-out;
- At the same time impressive progresses are achieved both in industry and academia in the field of fast and low power ADC;
- Very fast front-end electronics can greatly benefit from deep submicron technology: benefit in increase of sampling frequency and even greater with the decrease of conversion time (and hence dead-time) due to the use of novel fast ADCs;
- With ADC achieving 40-50 Ms/sec and few mW, analog memory is on the other hand being phased-out from medium speed application (50-100 Ms/sec...);
- But: very deep submicron technologies are expensive and ADC design is a very complex business!



FAST FRONT-END ELECTRONICS

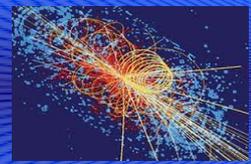
Angelo Rivetti – INFN Sezione di Torino
PARTII: Low Power Circuits for High Data Rates



- When the data rate per channel is high (>100 kHz) full waveform sampling and digitization may become impractical.
- Alternative: transfer the minimum of information by pre-processing in the analogue domain;
- Amplitude extraction with peak detectors;
- Timing extraction with TDC.
- Pure binary systems.






Amplitude and Time Measurements



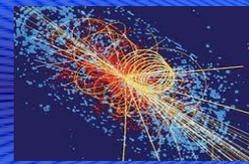


Amplitude and Time Measurement ASIC with Analog Derandomization

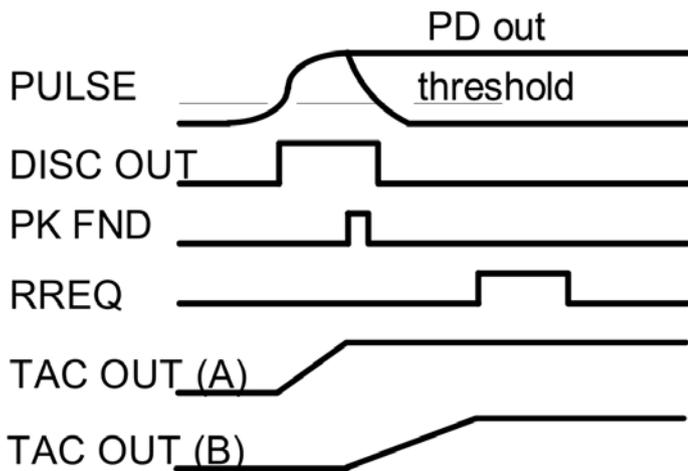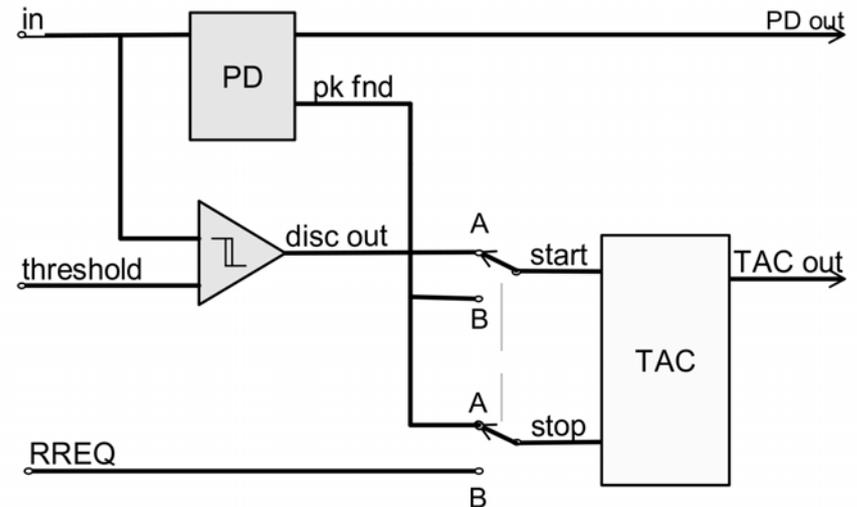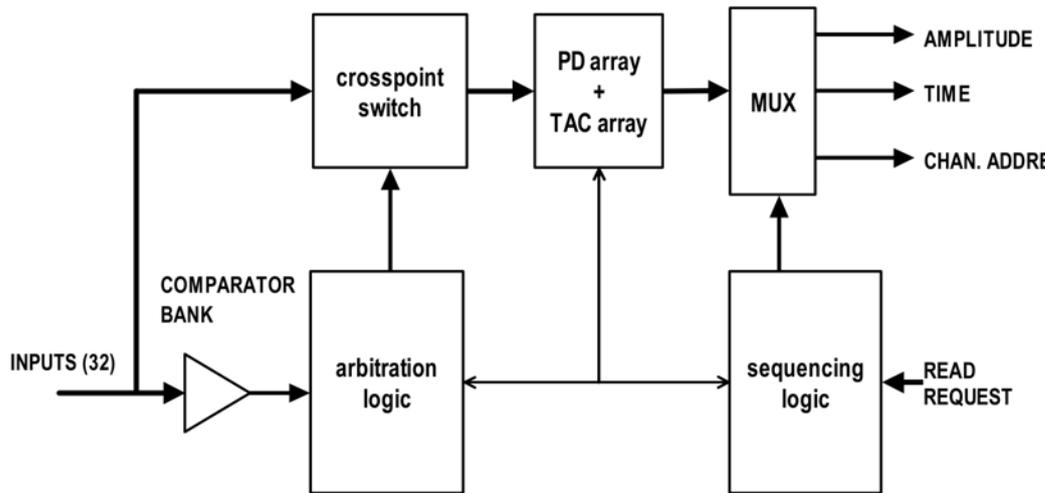G. De Geronimo, P. O'Connor, A. Kandasamy
IEEE NSS-MIC 2002 Conference record






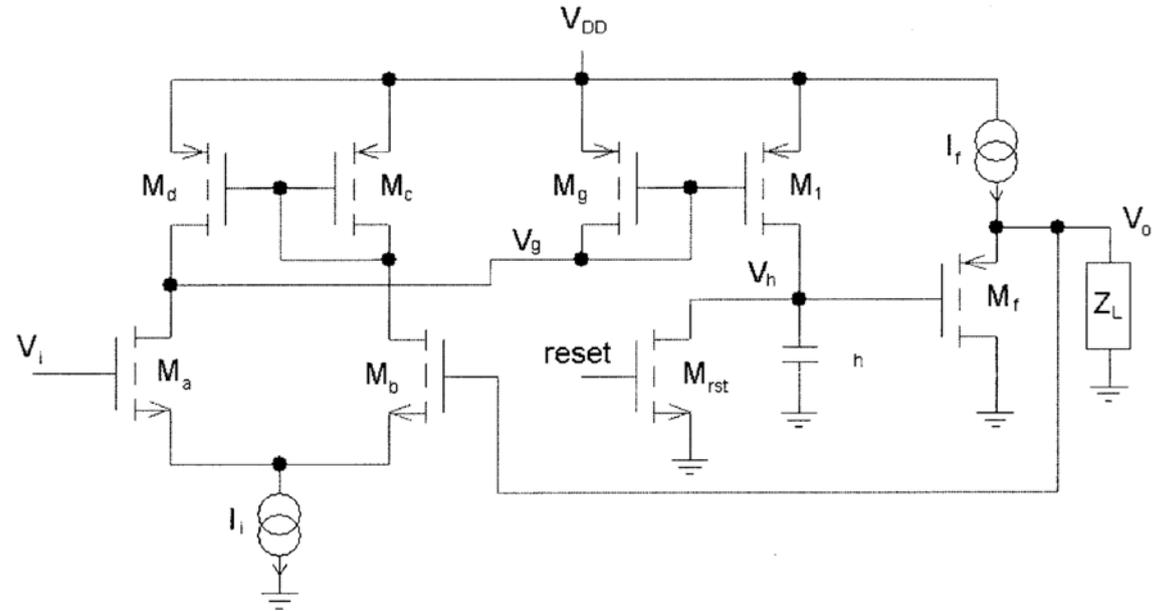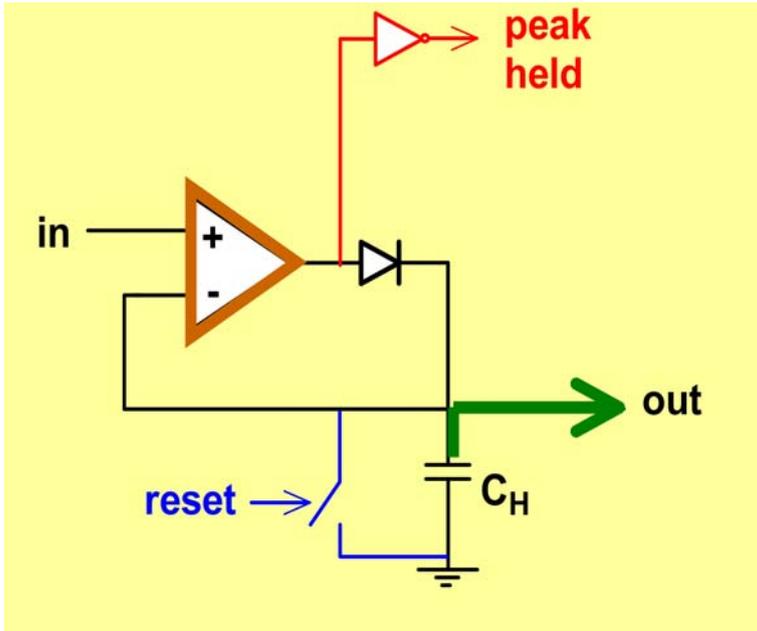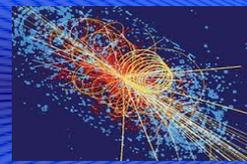- The arbitration logic route the analog signal to one of the **8 analog processing** units.
- Each processing unit consists of a **Peak Detector**, a **main TAC** used for timing and a secondary TAC used to set a time-out for the PD.
- The analog outputs of the PD and TAC are multiplexed on one output and digitized by an **external ADC**.
- Max rate: **1.6 MHz with 2.2 mW/ch.**



- Principle: **introduce a unidirectional element** in the feed-back loop of an opamp.
- The voltage on C_H follows the input till to the peak and then stays constant.

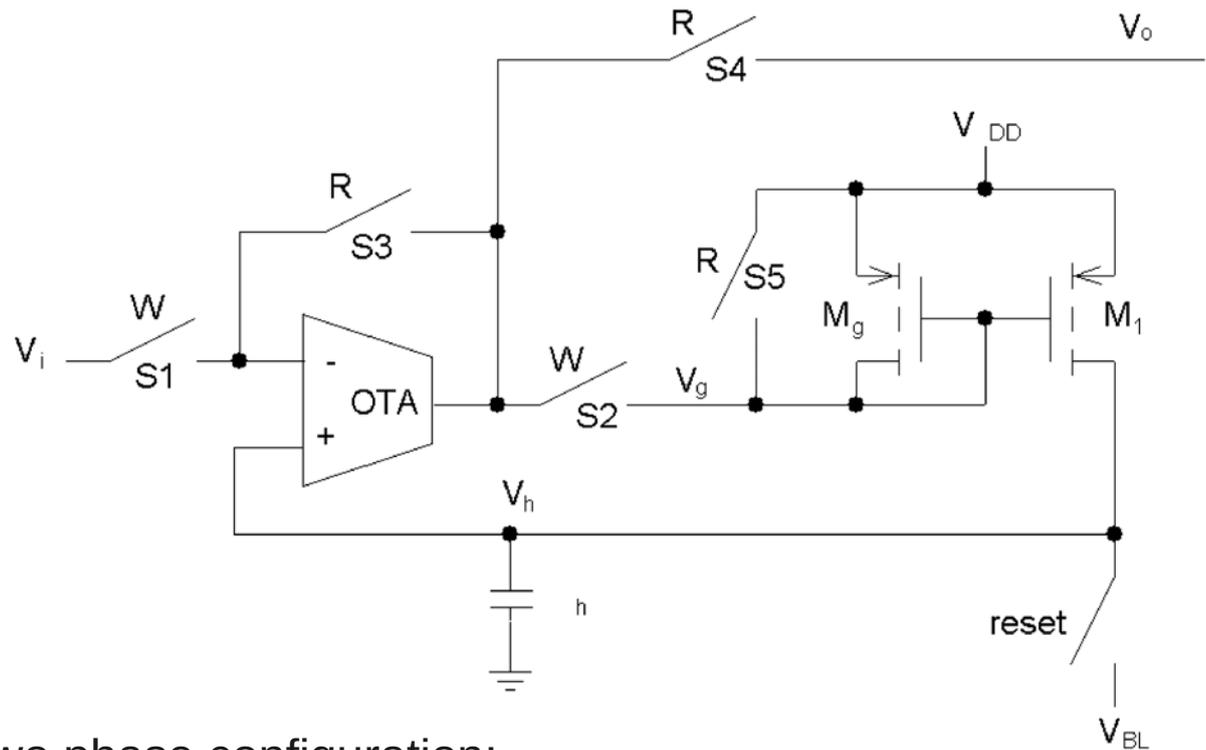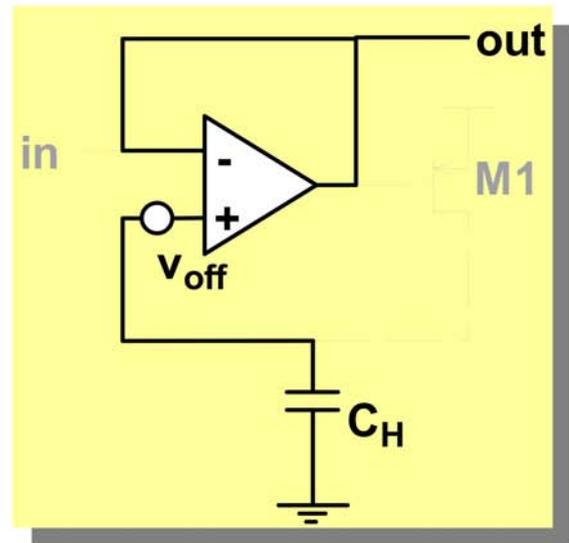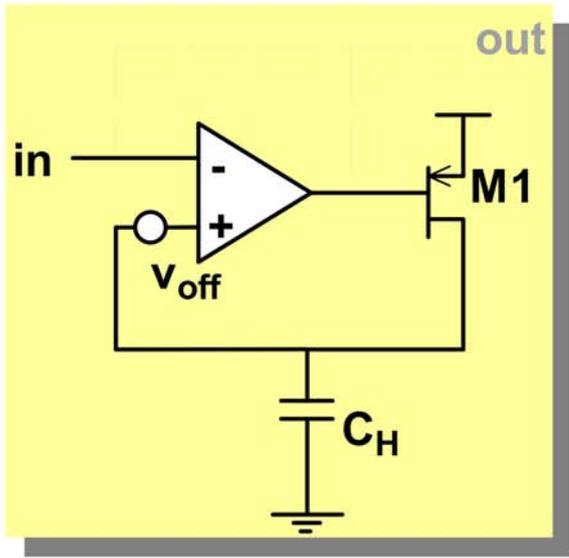
- Single phase peak detector in CMOS
 - Simpler
 - Suffers from op-amp errors





- Two phase configuration:
 - Write phase=**conventional peak detectors**:
 - Read phase=**op-amp used as buffer**. Op amp errors cancel

G. De Geronimo, P. O'Connor, A. Kandasamy:
 "Analog CMOS peak detect and hold circuits. Part I. Analysis of the classical configuration"
 "Analog CMOS peak detect and hold circuits. Part II. The two phase offset free and derandomizing configuration".



Time to Amplitude Converters

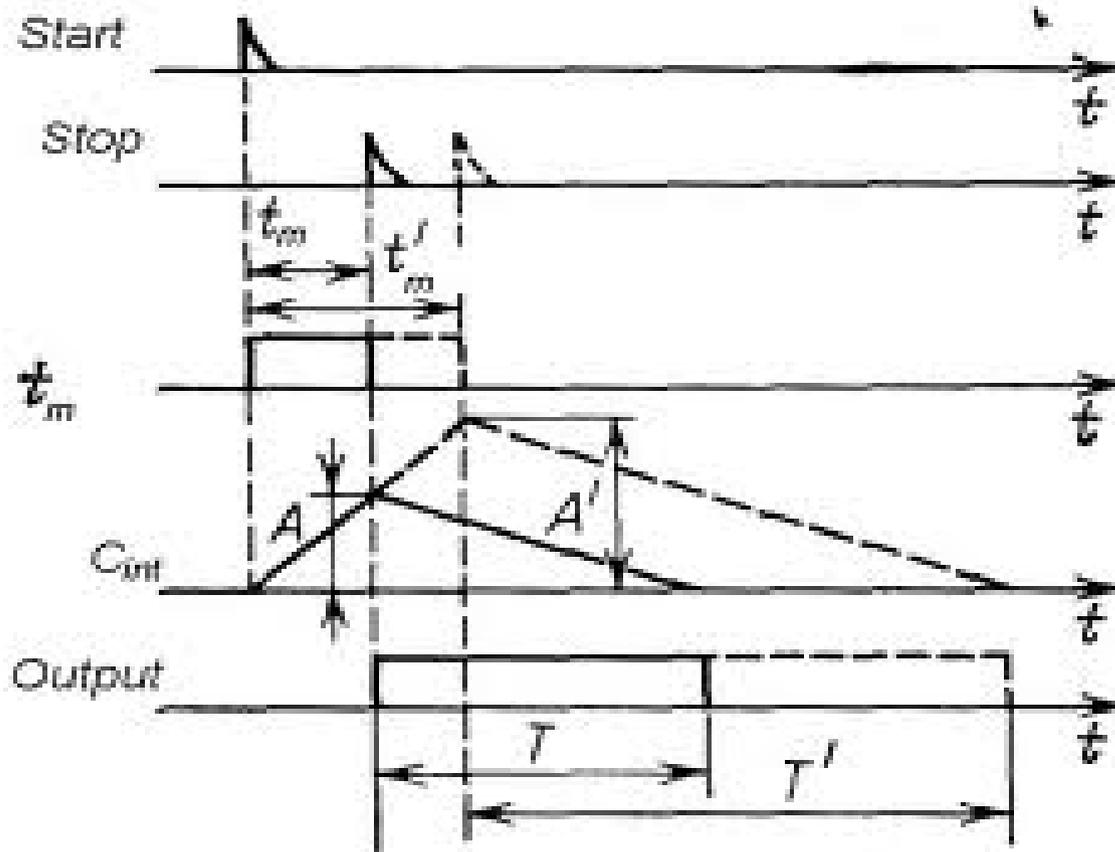

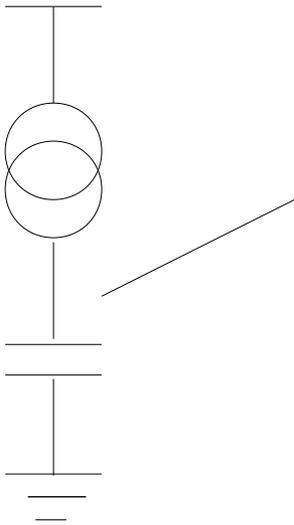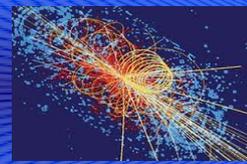- Principle: charge a capacitor with a constant current source.
- The resulting voltage is proportional to the time difference between the start and the stop pulse.
- Quite an old technique, but still in use, especially for high resolution...



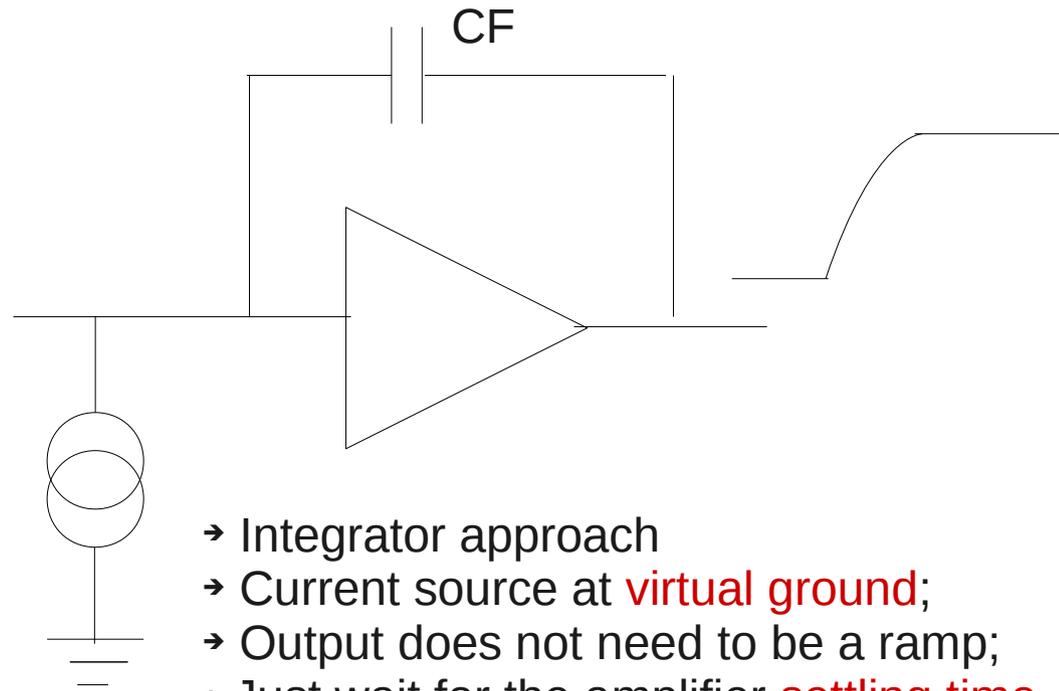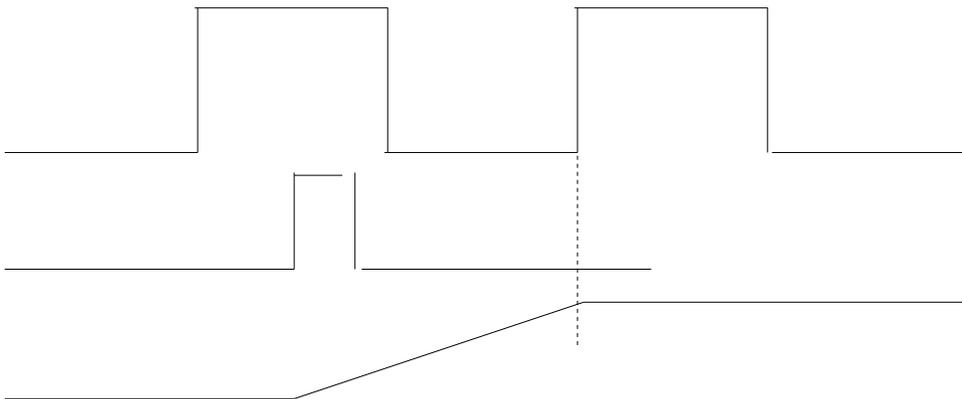- Direct capacitor charge:
 - Mostly used with **discrete implementation** or when the capacitor is external.
 - Current source experience significant voltage **variations across** its terminal,




- Integrator approach
- Current source at **virtual ground**;
- Output does not need to be a ramp;
- Just wait for the amplifier **settling time**.

- TAC as **analog interpolators**
 - A digital counter counts the clock pulses.
 - The TAC interpolates the time between the signal of interest and a suitable clock edge.



Digitizing the the voltage

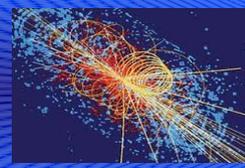




2008 International Conference on Design & Technology of Integrated Systems in Nanoscale Era

High Precision Time-to-Amplitude Converter for Diffuse Optical Tomography Applications

Moez Kanoun, Yves Bérubé-Lauzière, Réjean Fontaine
Department of Electrical and Computer Engineering
Université de Sherbrooke, Sherbrooke, Québec, Canada, J1K 2R1
{Moez.Kanoun}, {Yves.Berube-Lauziere}, {Rejean.Fontaine}@USherbrooke.ca



■ In principle, any ADC can do the job

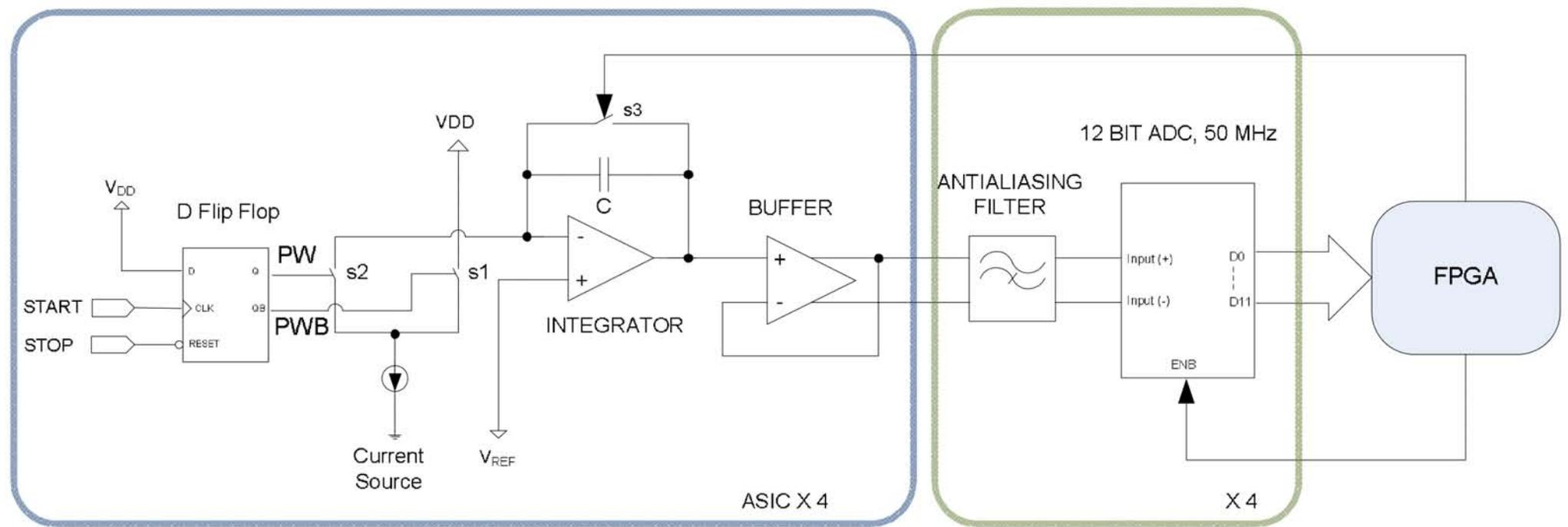


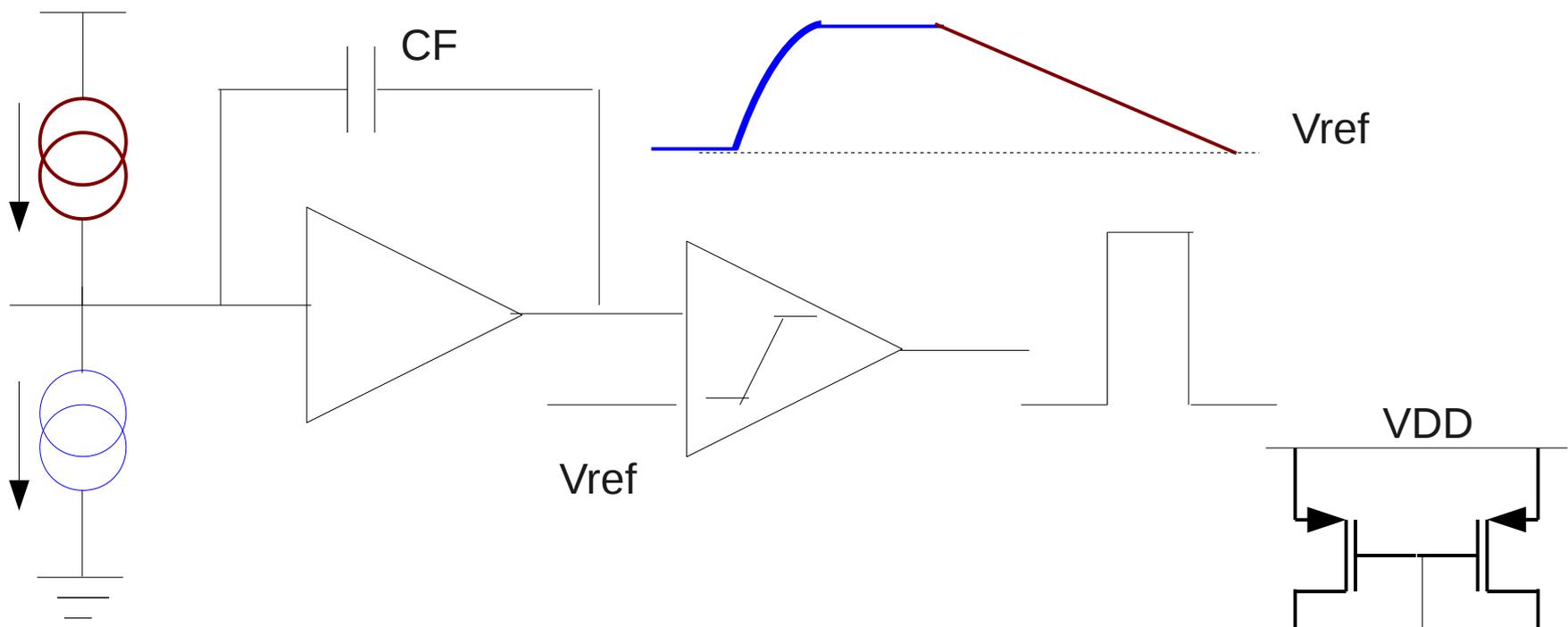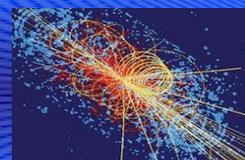

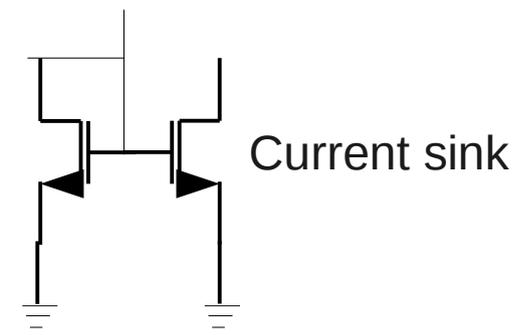
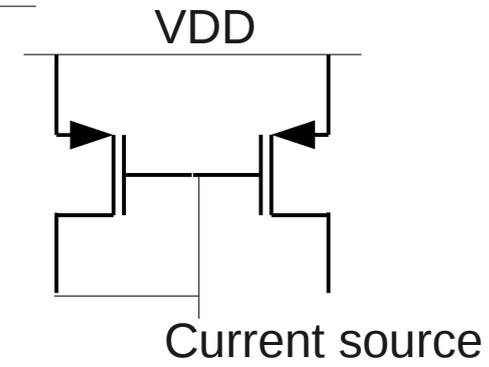
- Example: Main clock to be interpolated: **25 ns**
- 8 bit resolution=97.5 ps time bin=> rms resolution: 28.5 ps.
- Counter running at 40 MHz => Ratio between currents **256**.
- Dead-time: **6.4 μs**.
- Power can be as low as **0.1 mW** or less.

■ Issues: Speed, ratio between currents, current source implementation



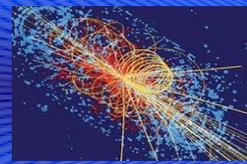

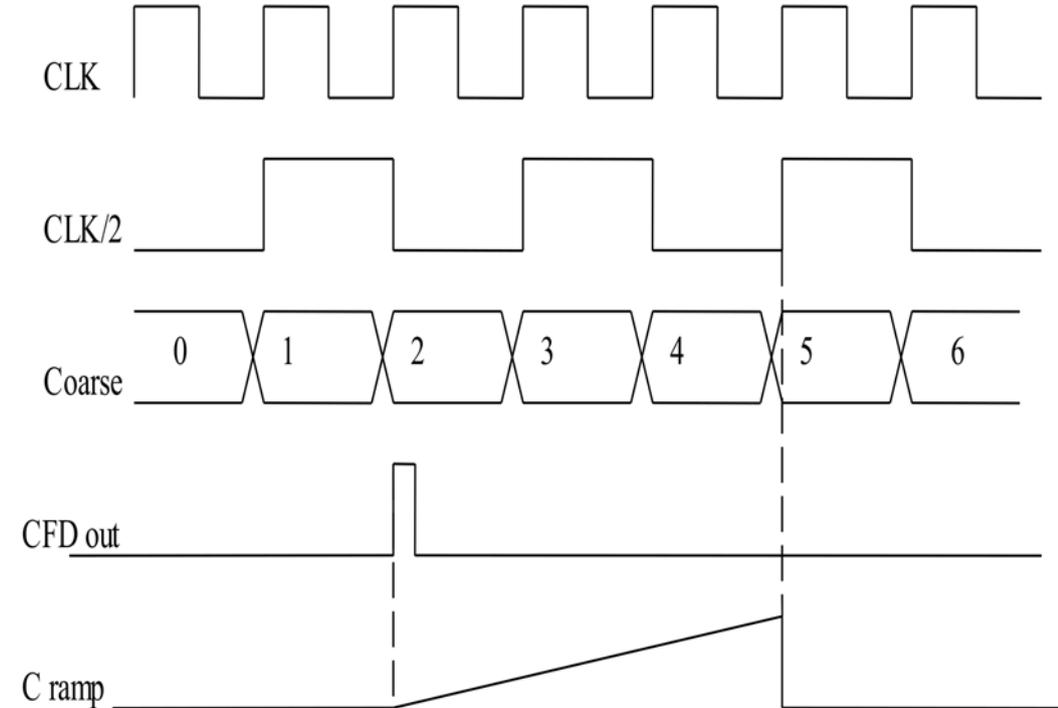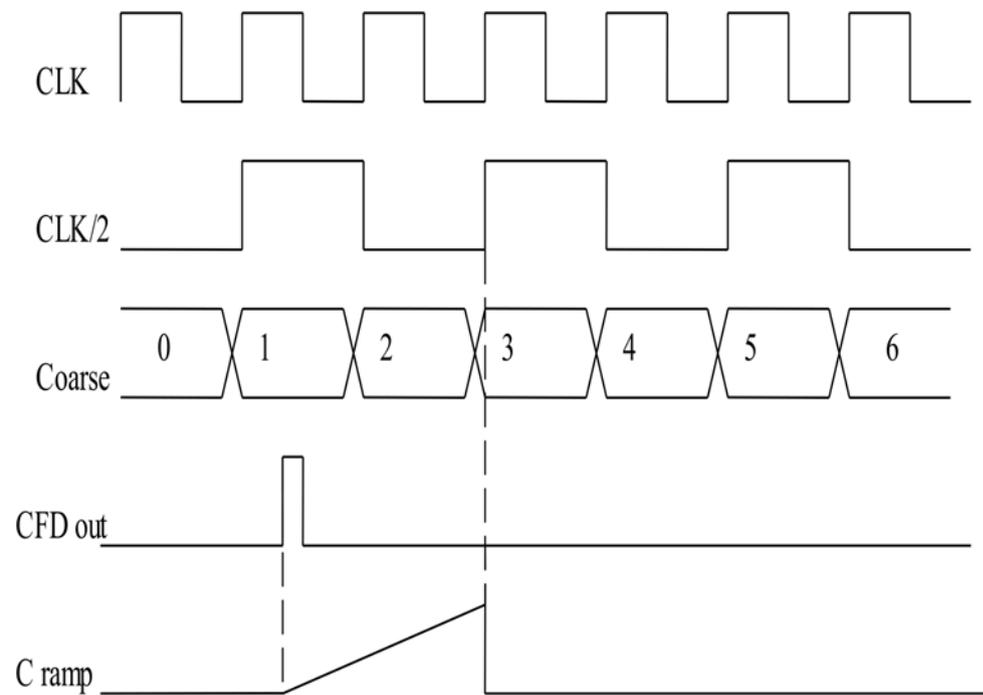
- Increase the conversion **clock!**
- This also reduces the ratio between **current sources**
- For instance, 160 MHz clock yields 4x reduction: from 256 to 64
- Still keep the full scale at 25 ns. Why?





- Introduce offset to avoid sudden “**switch-on, switch-off**”.
- Use **over-ranging** to correct for potential ambiguities



- Precharge C_F to V_{ref} and discharge it when the pulse arrive.
- Transfer the voltage on C_{out} .
- Recharge C_{out} back to V_{ref} : currents have the same polarity
- $C_{out}=4*C_F$, current source ration scales further by 4x, from 64 to 16.
- Design **becomes compact**
- Range to interpolate: 18.75 ns, 192 counts, dead time **1.2 μ s, 830 kHz.**
- Better than 99% 8.3kHz, assuming Poisson incoming rate => Buffering.




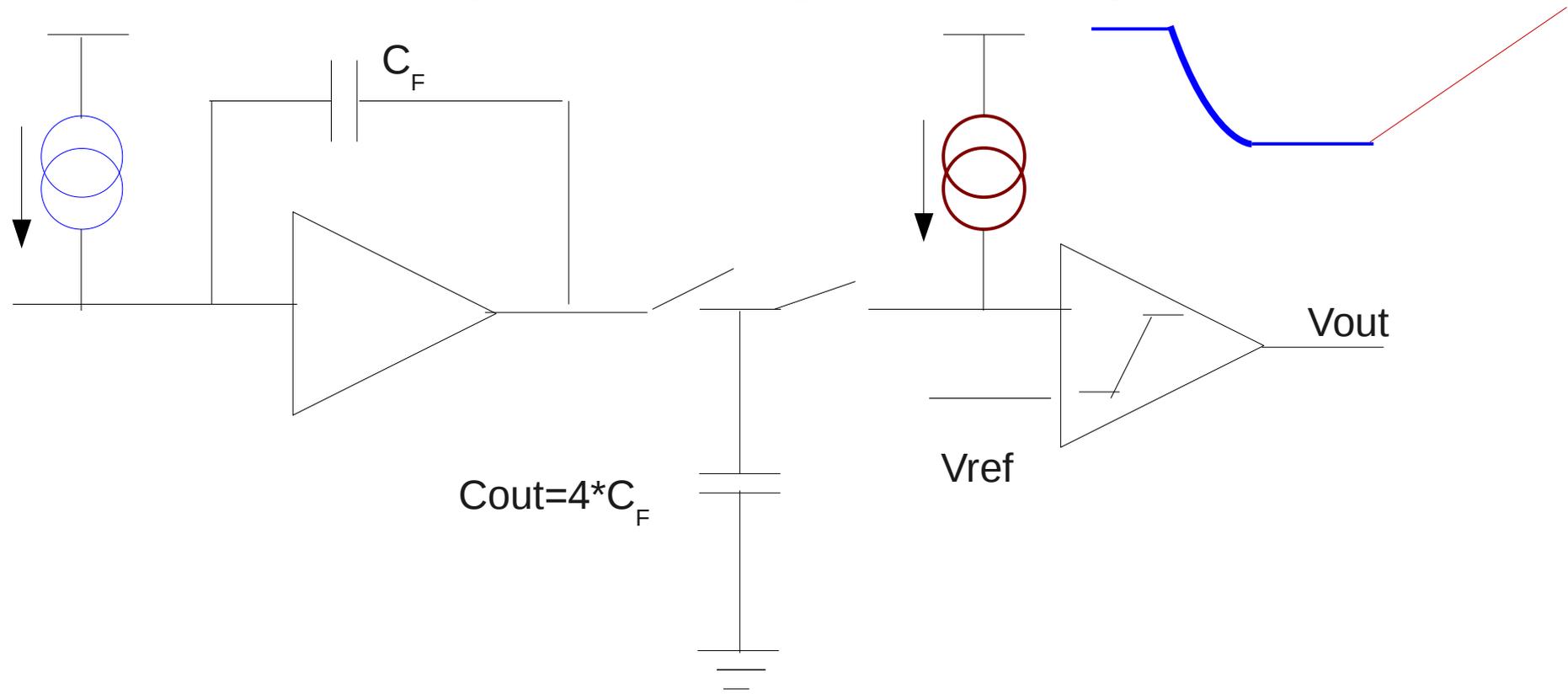


Chip prototype with 105 TDCs

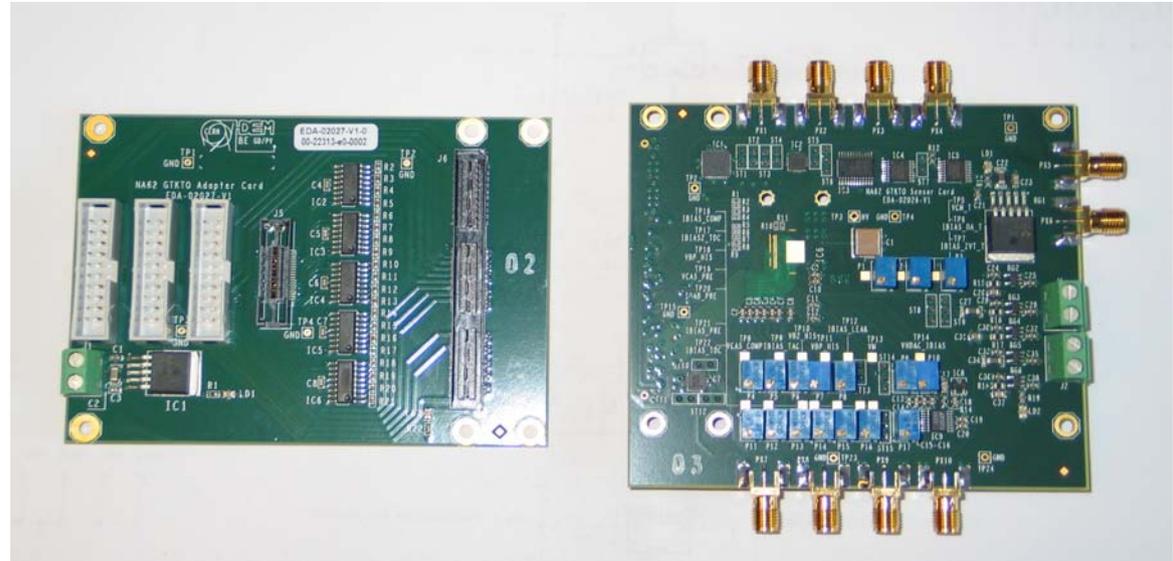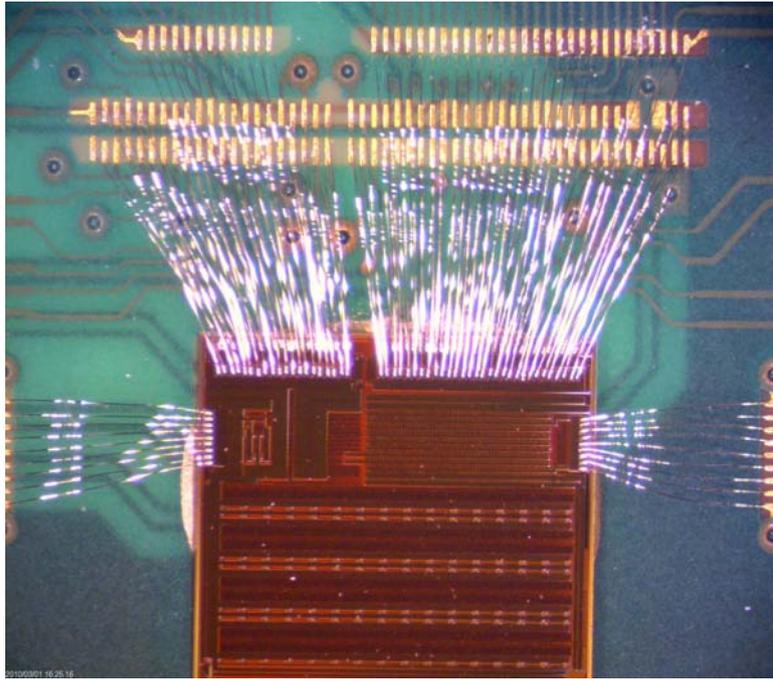

- Developed in the R&D for the NA62 Gigatracker.
- Each channel is $300\ \mu\text{m} \times 300\ \mu\text{m}$.
- In each channel: preamplifier+constant fraction discriminator+4-buffer TDC
- Power: 2.5 mW/ch

TDC performance

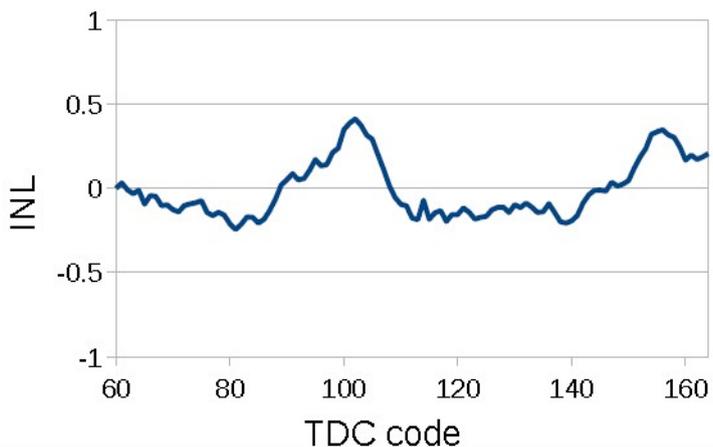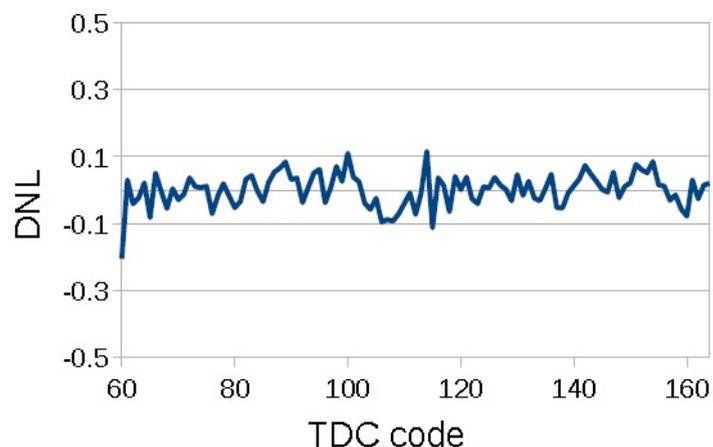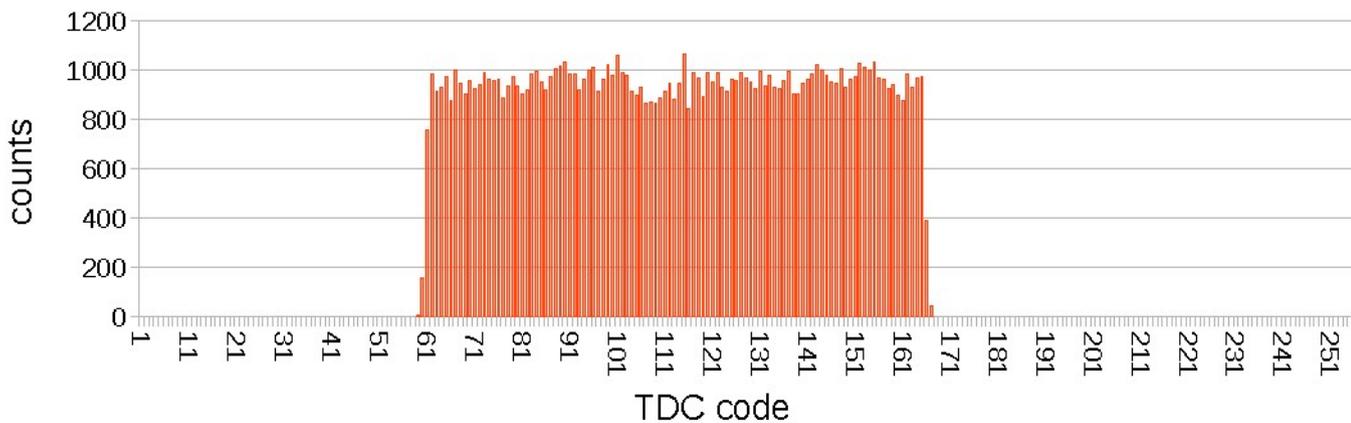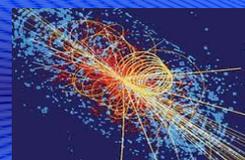



10^5 random test pulses to the 7-bit TDC: $N_{th} = 10^5 / 2^7$

$$-0.5 < DNL(i) = \frac{N_{EXP}(i) - N_{th}(i)}{N_{th}(i)} < 0.5$$

$$-1 < INL(i) = \sum_{i=1}^k DNL(i) < 1$$



TDC performance

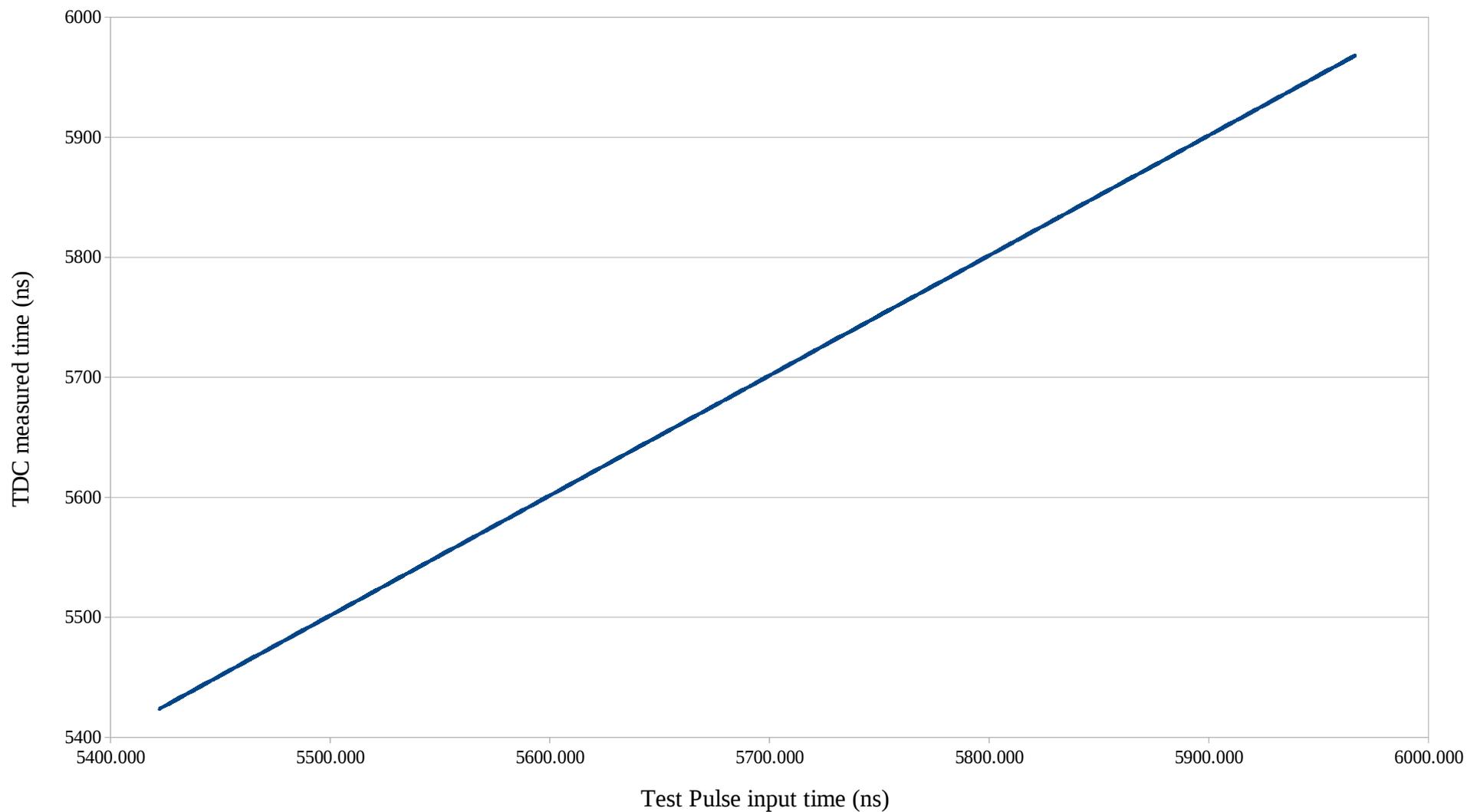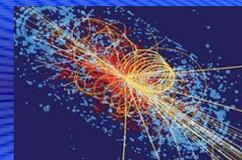



Fast binary front-end for multi-anode PMT





- Development of a fast binary read-out chip for Compass at CERN;
- Chip designed to replace an older ASIC (MAD4) in the RICH upgrade;
- MAD4: 0.8 μm BiCMOS chip developed by INFN-Padova for CMS muon drift tubes.
- User requirements:
 - Full compatibility with the existing read-out electronics;
 - Reduced gain for MPT and same gain of the MAD4 for other applications;
 - Threshold adjustable channel by channel;
 - Maximum hit rate > 5 MHz/channel;
 - Power consumption < 30 mW/channel;
 - Technology: standard 0.35 μm CMOS.



CMAD design choices




- Work with very low threshold to minimize time walk while using a simple leading edge discriminator:
 - Low noise front-end amplifier:
 - Minimal threshold dispersion.
- Maximize linear operation to allow quick recovery from overdrive;
 - Rail-to-rail output stage before discriminator.
- Keep maximum flexibility:
 - Programmable front-end amplifier
 - “Digital shaper” to guarantee either an output pulse of fixed duration or a pulse width modulated by amplitude to allow Time over Threshold operation.
- Design for 10 Mhz/channel operation to have good safety margin.

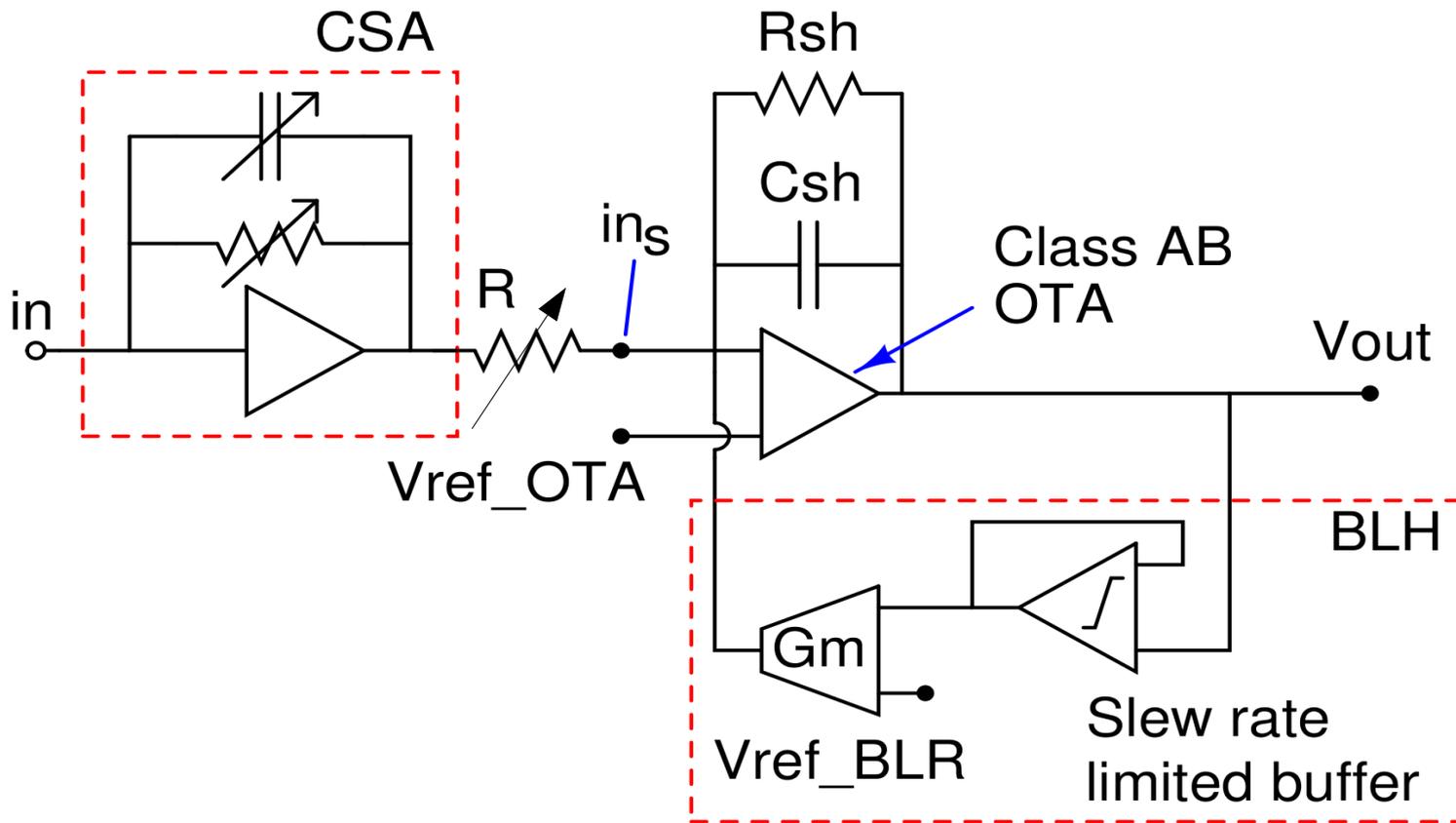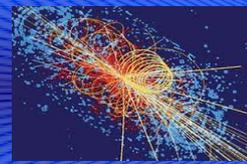


■ Moderate input capacitance (< 20 pF):

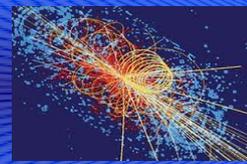
- Input stage: transimpedance amplifier with resistive and capacitive feed-back
- Programmable resistance and capacitance in the first stage feed-back
- Programmable coupling resistance between the stages



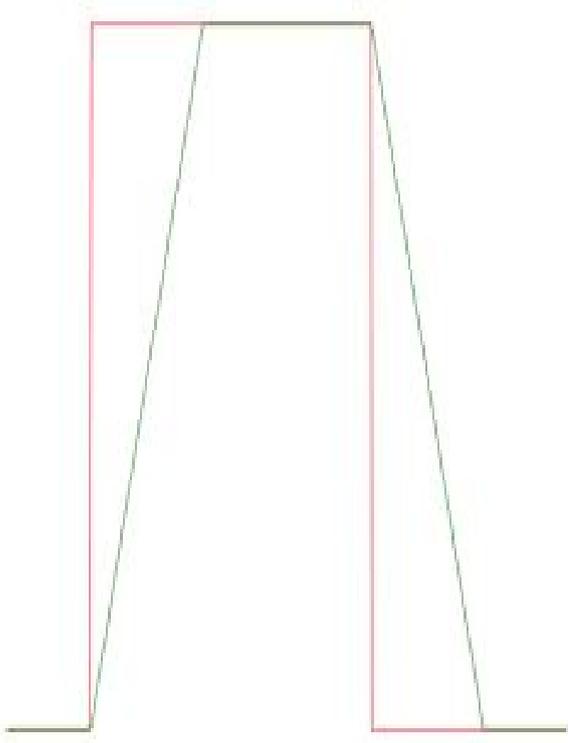- Inverting configuration: input is at virtual ground
- High output swing in however needed to maximize the dynamic range
- High slew rate to avoid pulse distortion




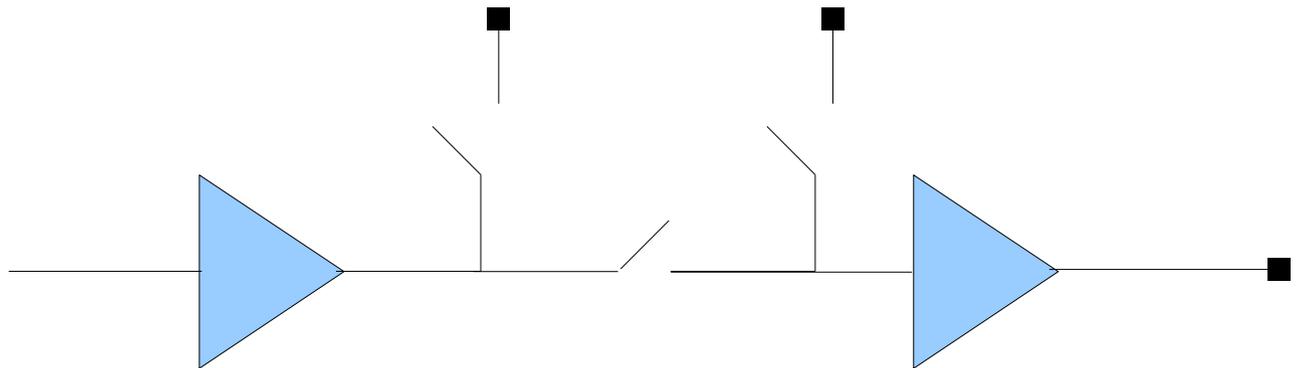- Slew rate= I_{out}/C_{load}
- Output capacitance modest (<0.5 pF), but need of observing directly the output for testing/debugging purposes.
- Not to distort a sinusoid input $SR > 2\pi f V_p$







Slew rate limitations in pulse amplifier

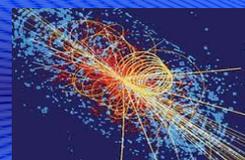


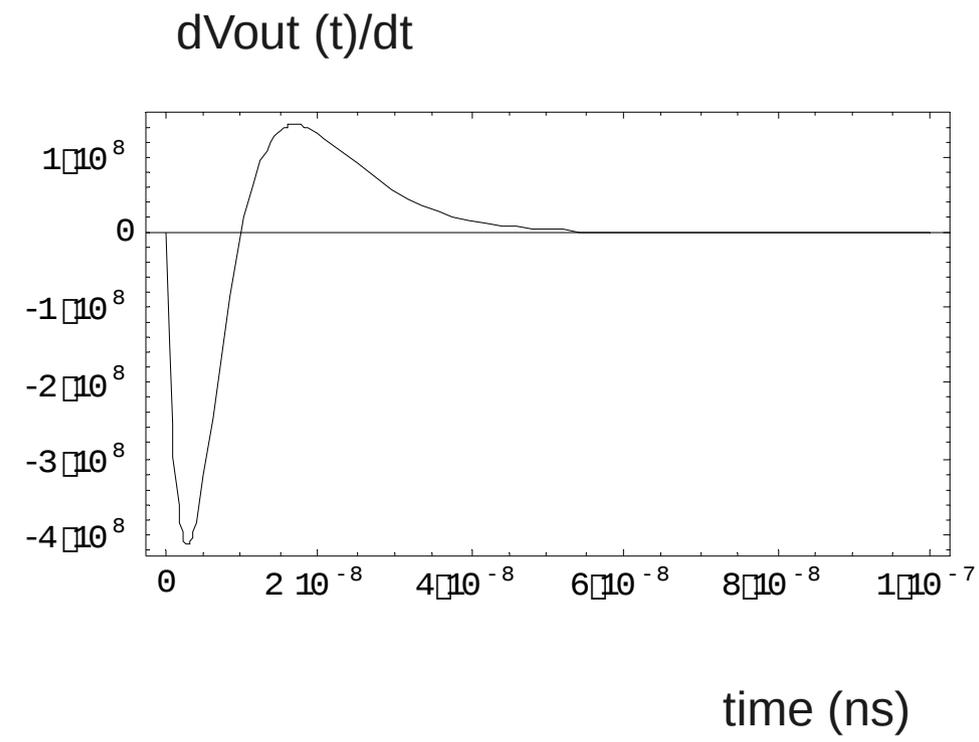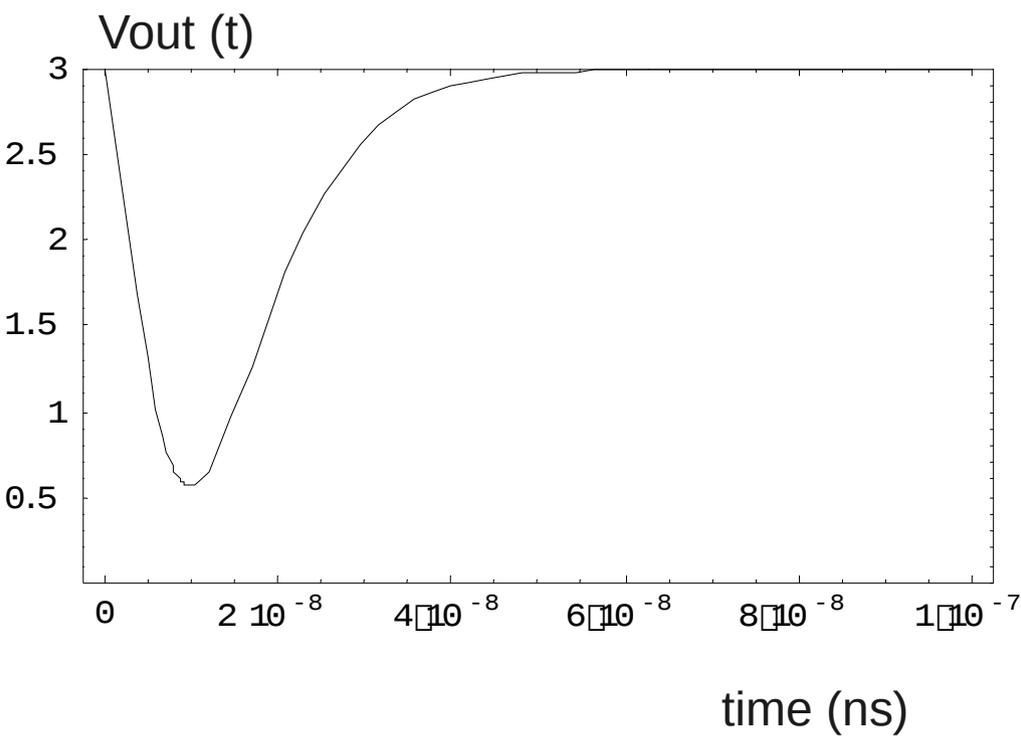- For fast semi-gaussian shaping slew rate requirements are quite demanding
- Ex: 2.5 V at 10 ns peaking time requires SR of 400 V/ μ s
- For a class A amplifier and 10 pF bias current of 4 mA.





Second stage based on a class AB OTA with rail to rail output

Class AB output stage

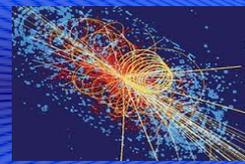


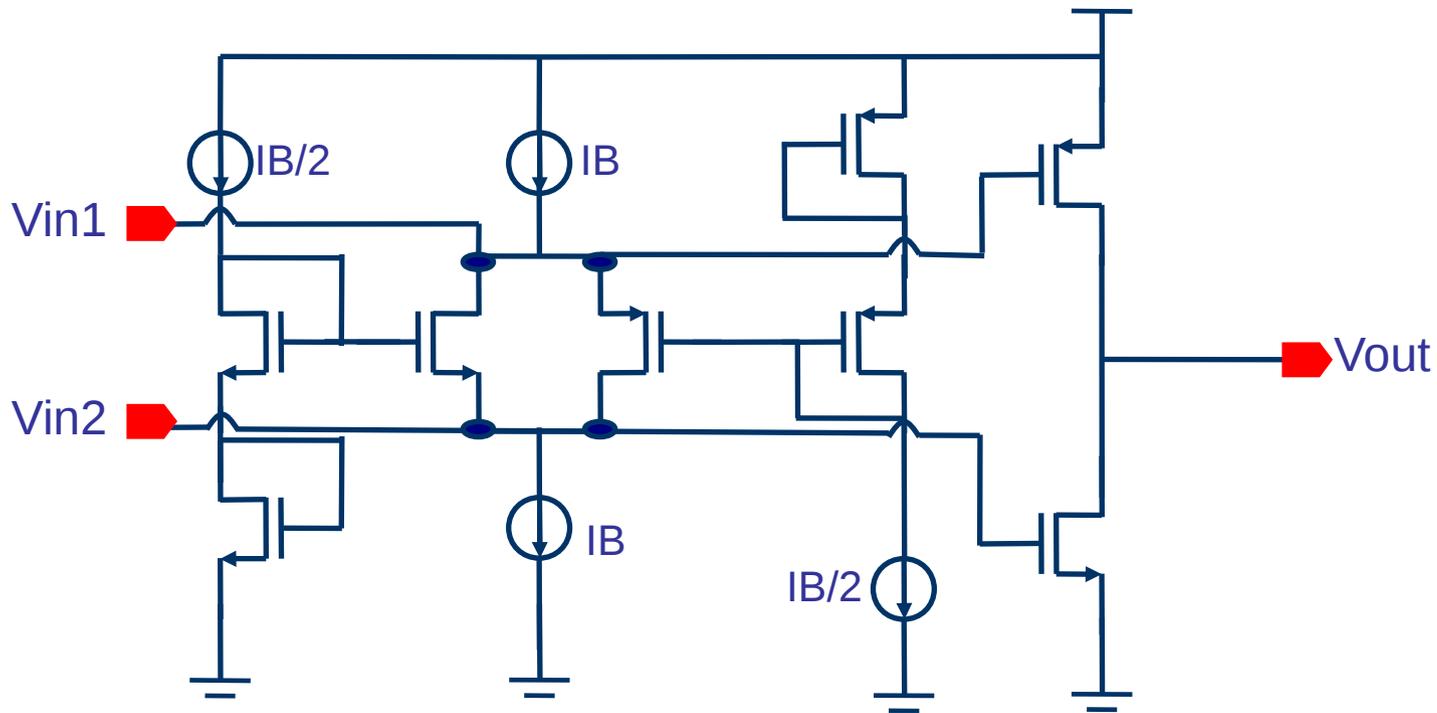- Output is an inverter;
- The bias circuit set the quiescent current I_q ;
- The minimum current for the “non active” transistor is $0.3 \cdot I_q$;
- The maximum current is $\gg I_q$.




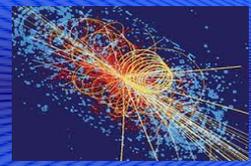

- An operational transconductance amplifier (Gm-stage) is inserted in feed-back around the shaper;
- The stage sink current to bring the DC output to the reference voltage to V_{ref_BLR} ;
- Bandwidth of the Gm stage must be small otherwise also signal are clipped!
- Large time constant can be implemented with small capacitor by starving Gm.
- The DC output voltage can be locked to the desired reference value

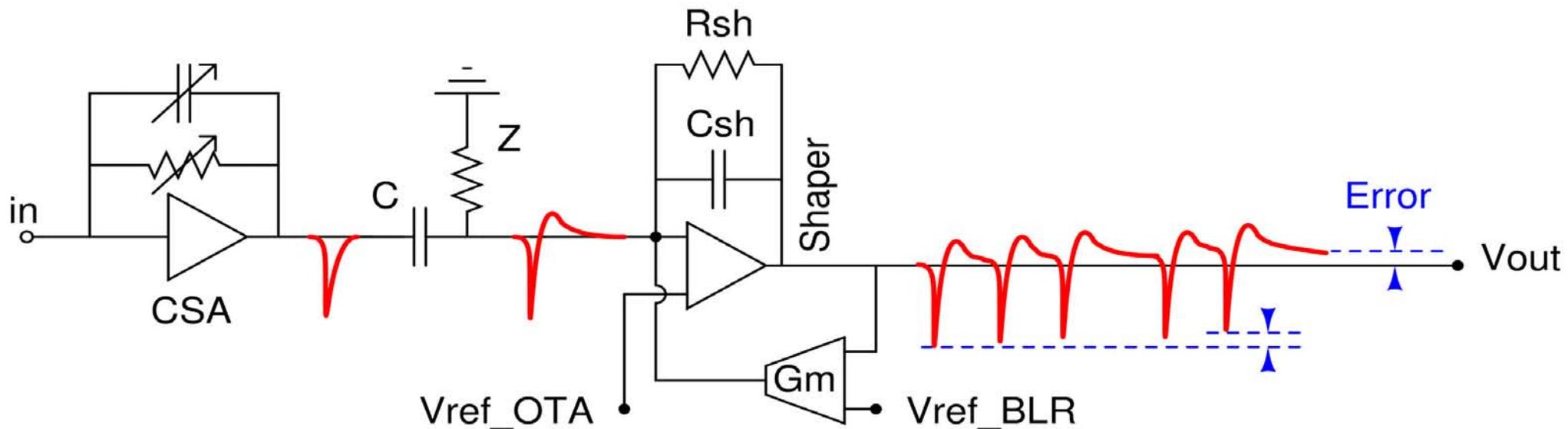

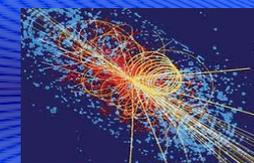It is an ac coupling, so it can be subjected to rate-dependent baseline drift!



- A non-linearity must be inserted in the chain, so that fast signals are severely clipped;
- Slew rate limitations are very well suited to this purpose.
- So a slew-rate limited buffer must be inserted in the baseline controlling chain.


IEEE TRANSACTIONS ON NUCLEAR SCIENCE, VOL. 47, NO. 3, JUNE 2000

A CMOS Baseline Holder (BLH) for Readout ASICs¹

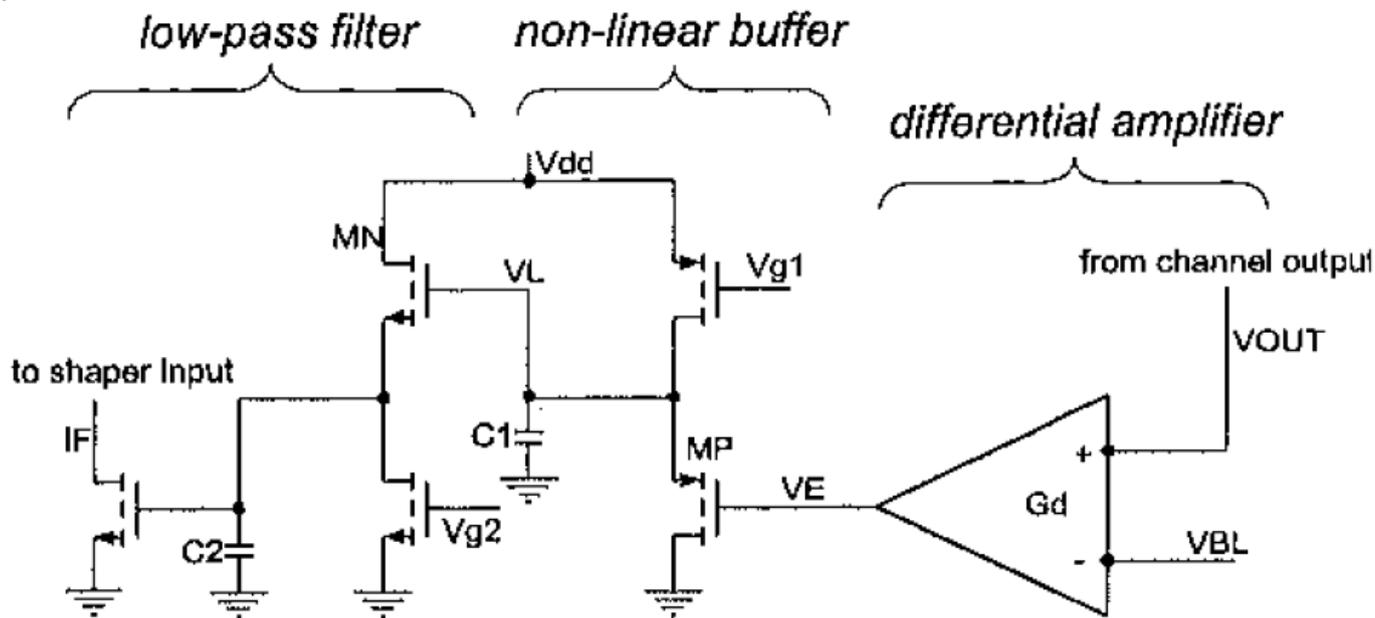G. De Geronimo², P. O'Connor² and J. Grosholz³


²Brookhaven National Laboratory, Instrumentation Division, Bldg 535B, Upton, NY 11973, USA

³cV Products, Div. of II-VI Inc., 373 Saxonburg Blvd., Saxonburg, PA16056, USA






SR limitations with unity gain buffer

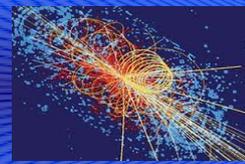


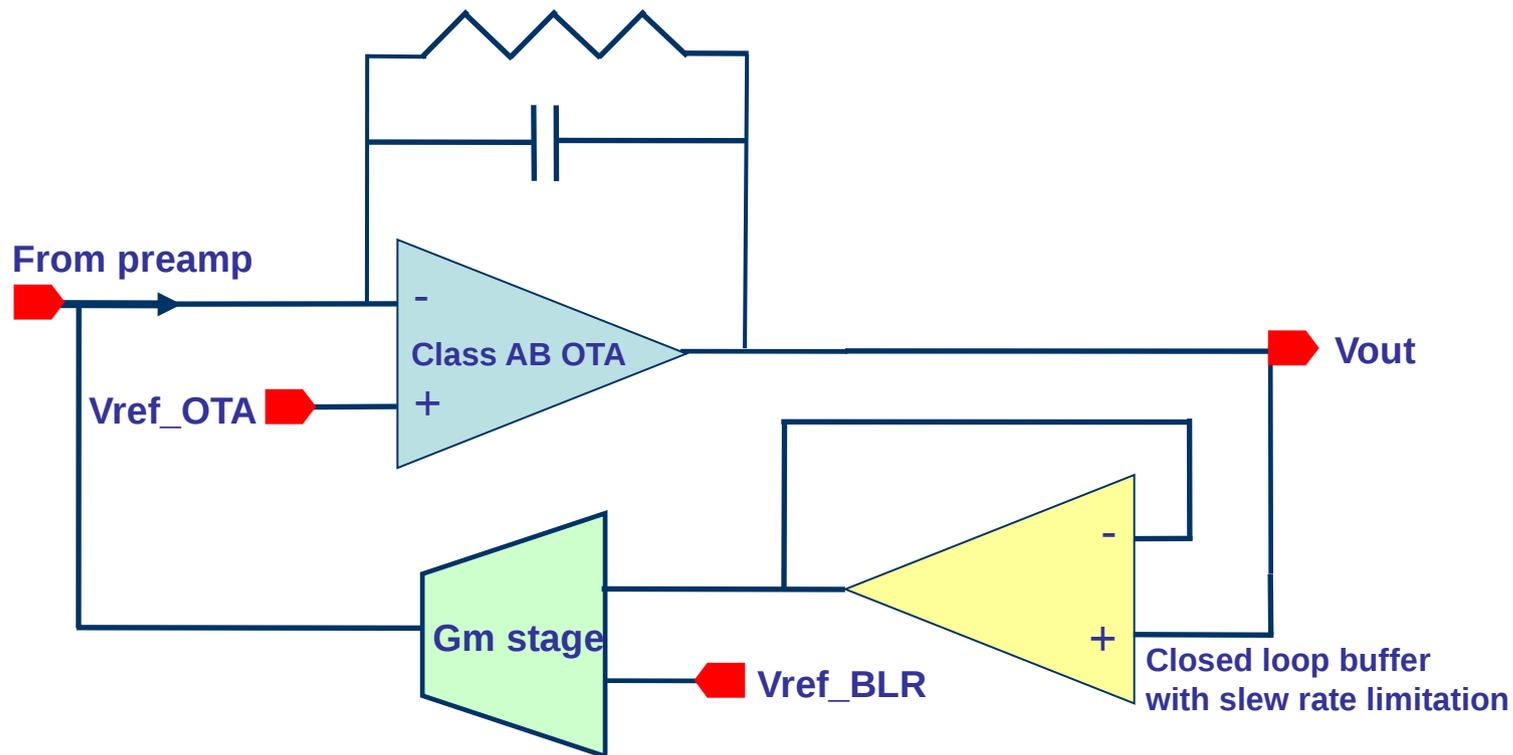- A voltage follower is used with high-bandwidth e strong slew rate limitation;
- The unity-gain feedback gives an high frequency pole which does not interfere with the compensation.






Effect of slew-rate limitation

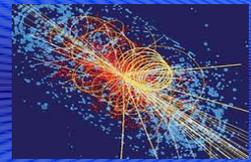


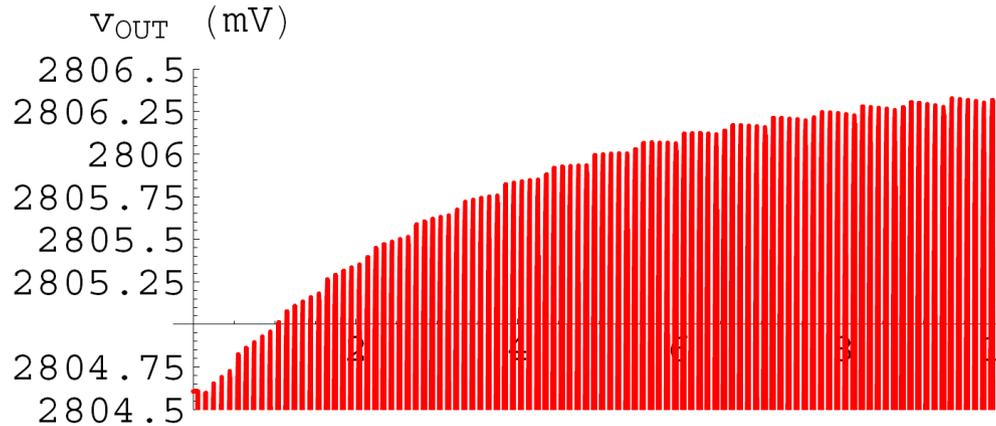Spice simulations with and without SR-limited buffer



With 10 MHz, 2.7 V pulse the baseline drift is $< 1\text{mV}$

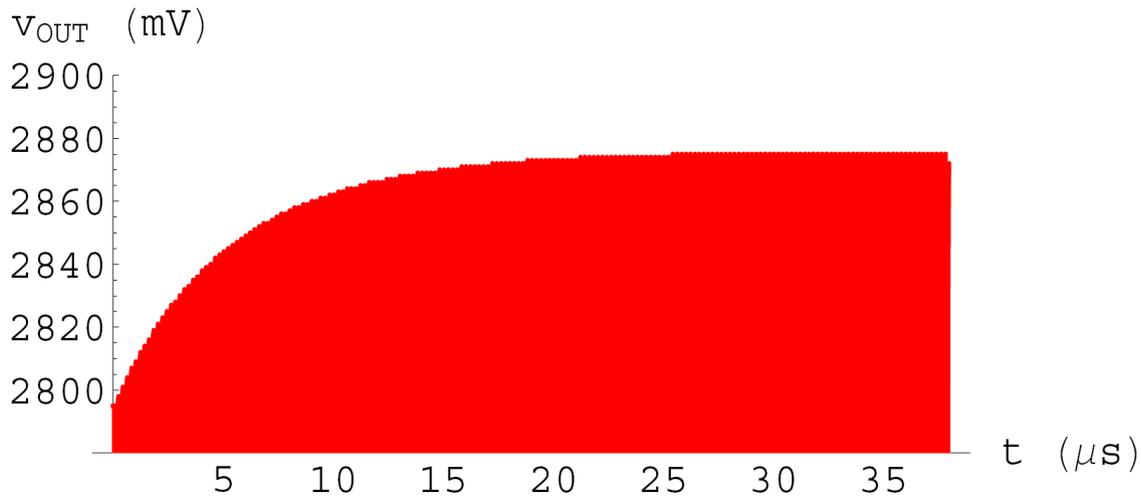This is a very pessimistic assumption. For practical cases baseline fluctuation will be kept in the noise






SR-limited buffer schematic




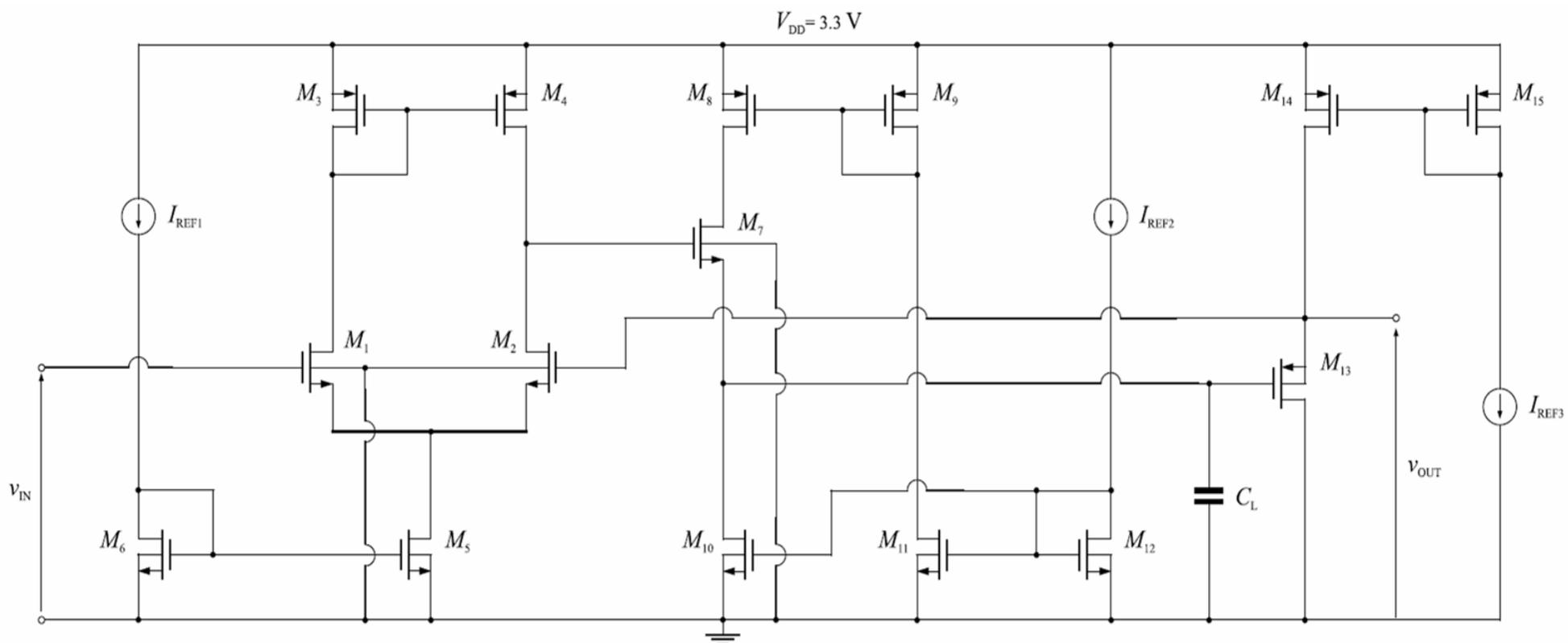CL must be protected by charge injection from the past preamplifier output via the parasitics of M1 and M2.






Comparator schematic

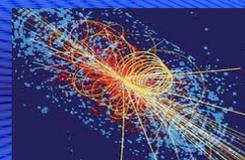

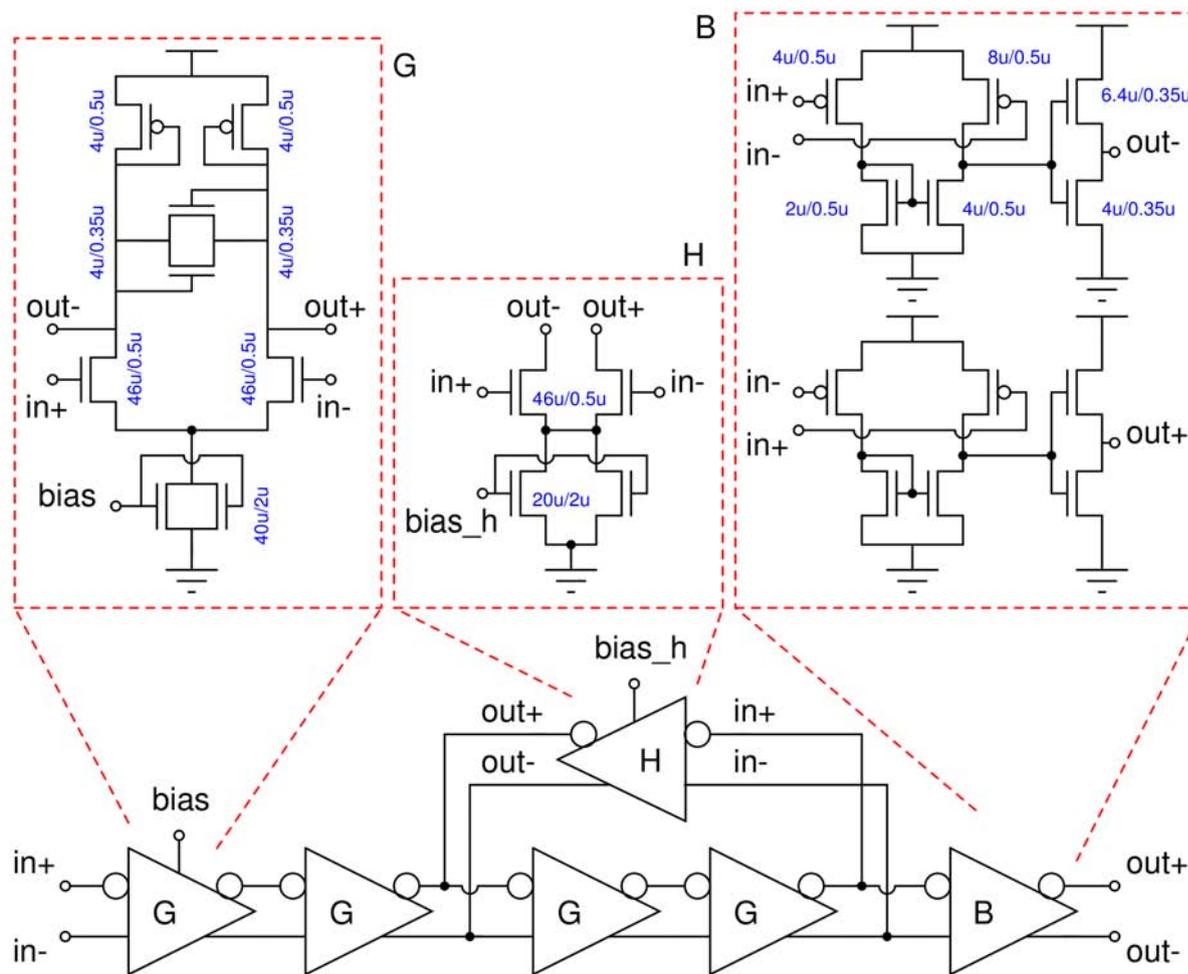
- Cascade of fully differential chain with hysteresis;
- Generation of CMOS levels only in the last stage;
- Small devices for high speed=offset.



DAC schematic




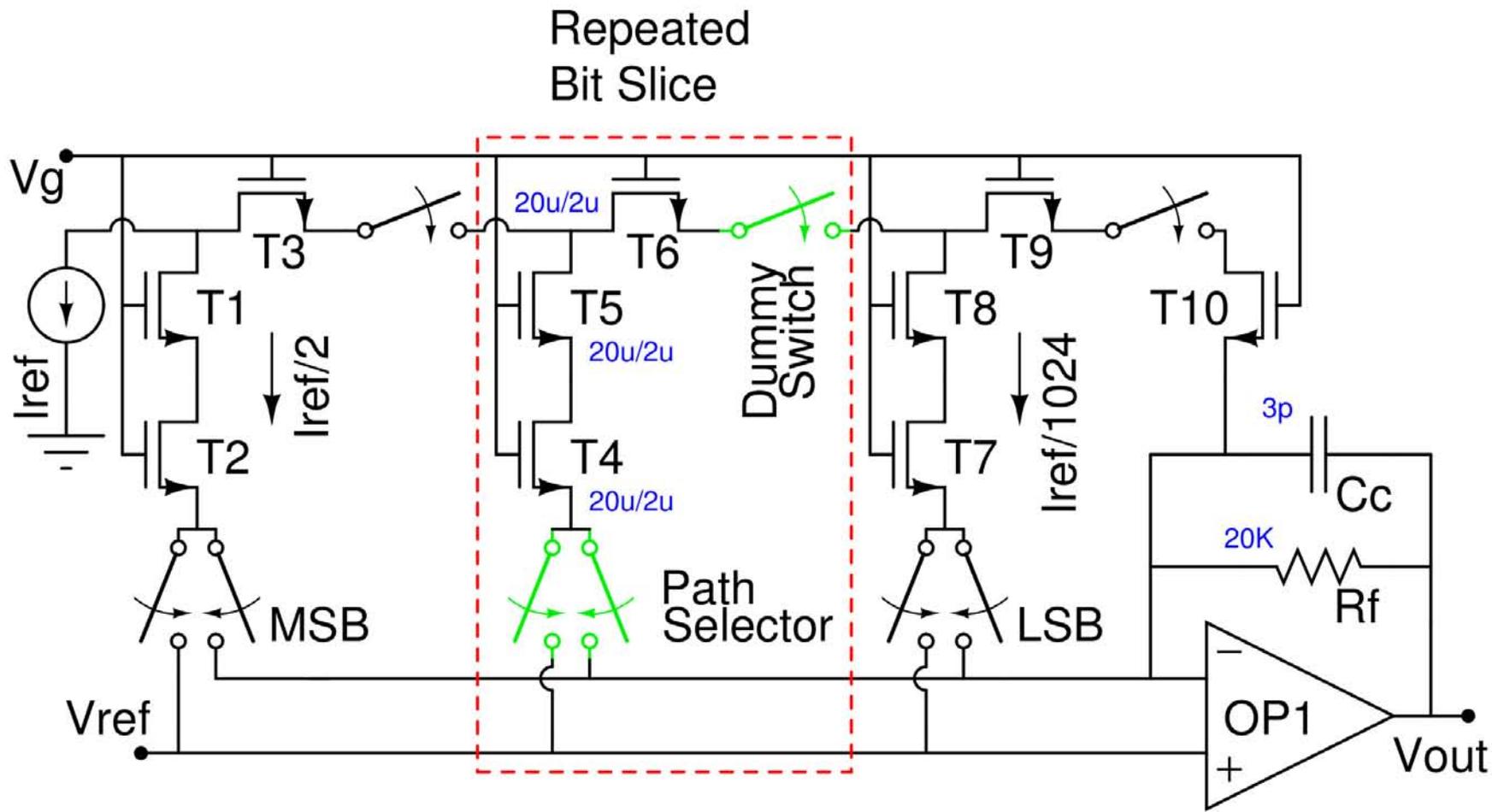- Current division by mean of equal slices;
- Size grows linearly with the number of bits;
- Two DACs per channel: one for baselines and one for thresholds.






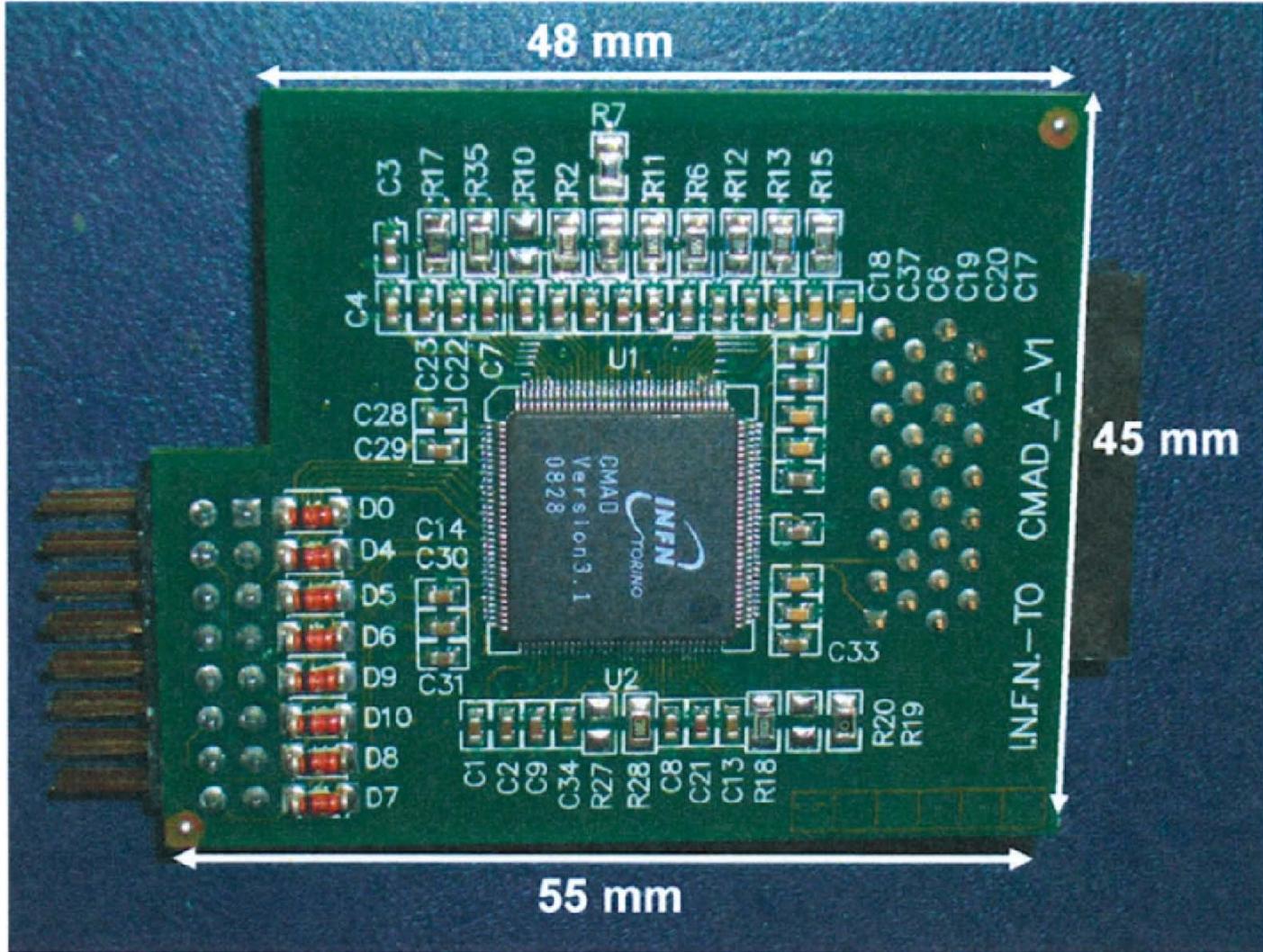
■ Test board used in data taking in the experiment



Gain settings

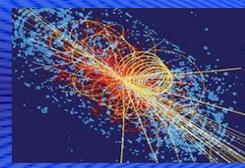

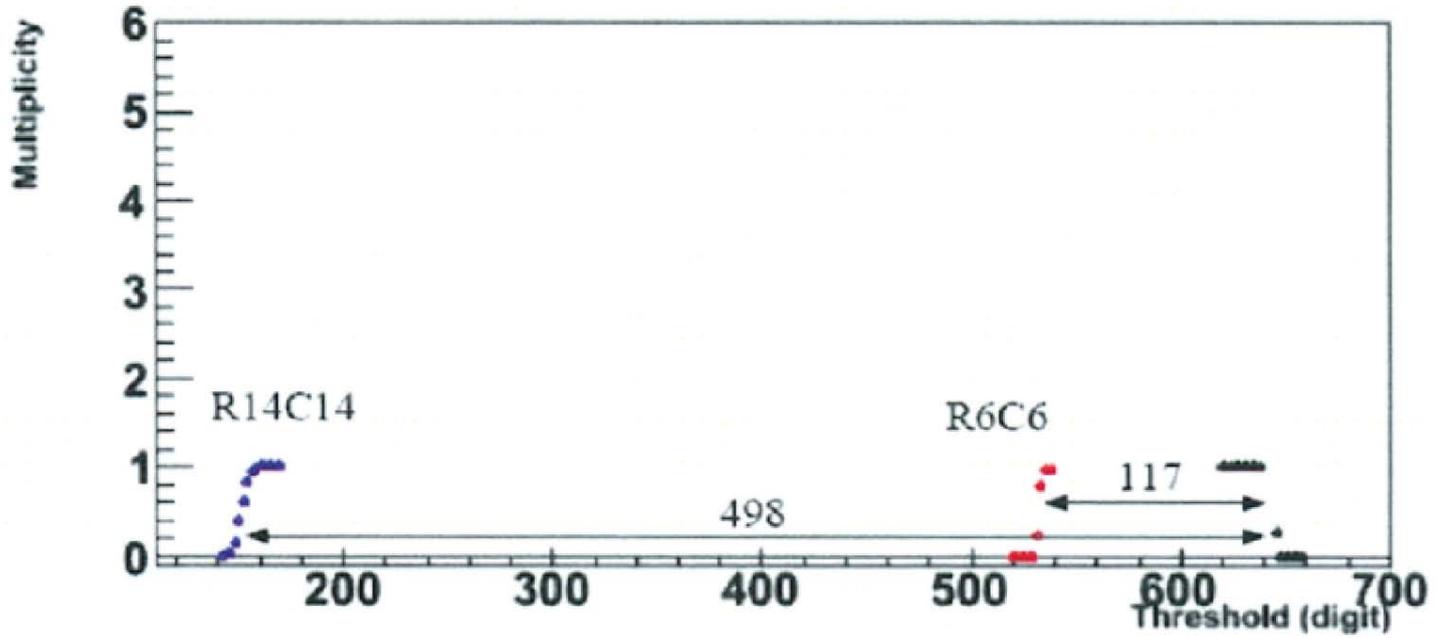
- Threshold scan with the same input signal and two different gain settings



Threshold equalization



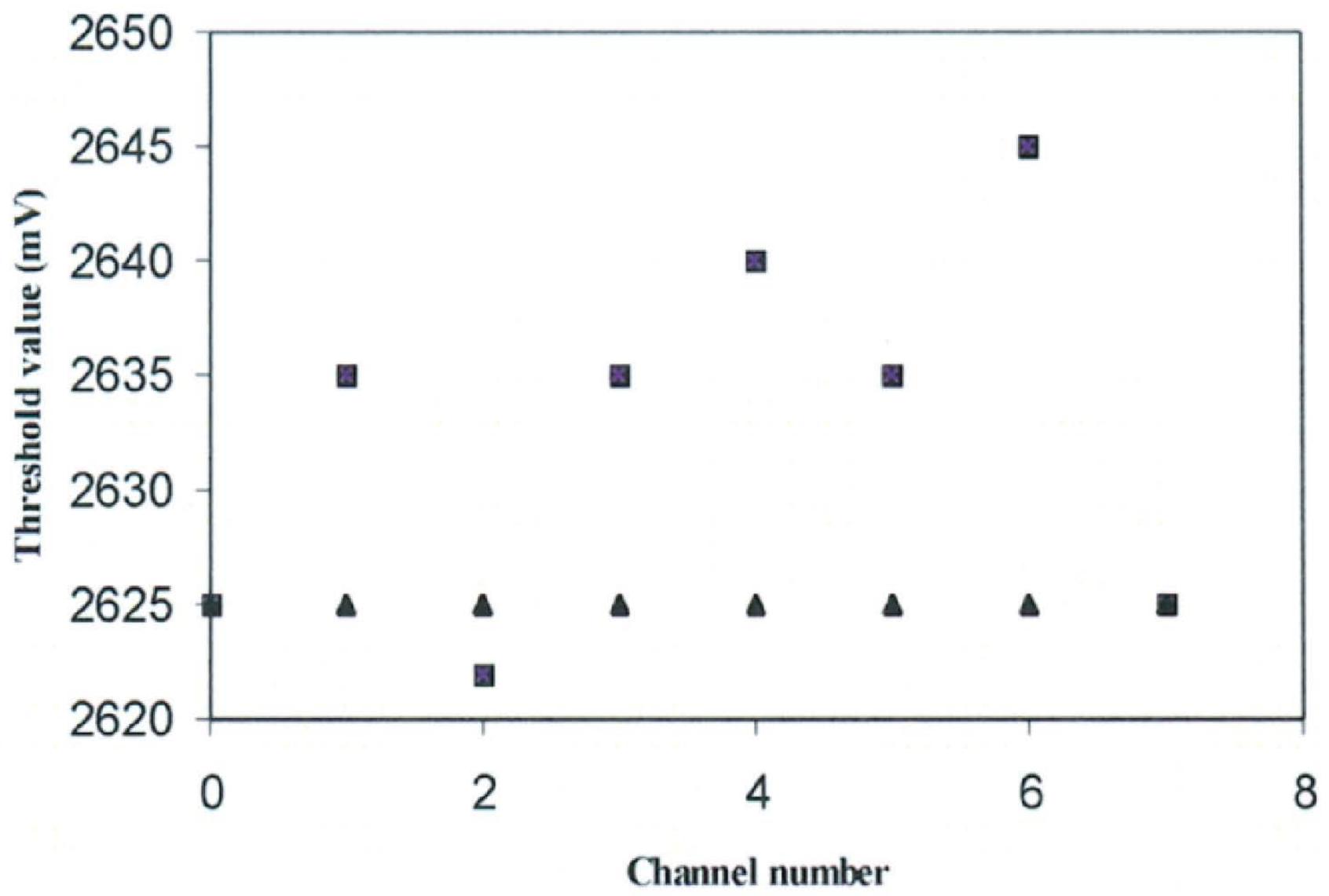
■ Threshold residual dispersion less than 0.5 mV (200 electrons for the max gain)





■ Efficiency vs rate

■ Measurements done with PMTs

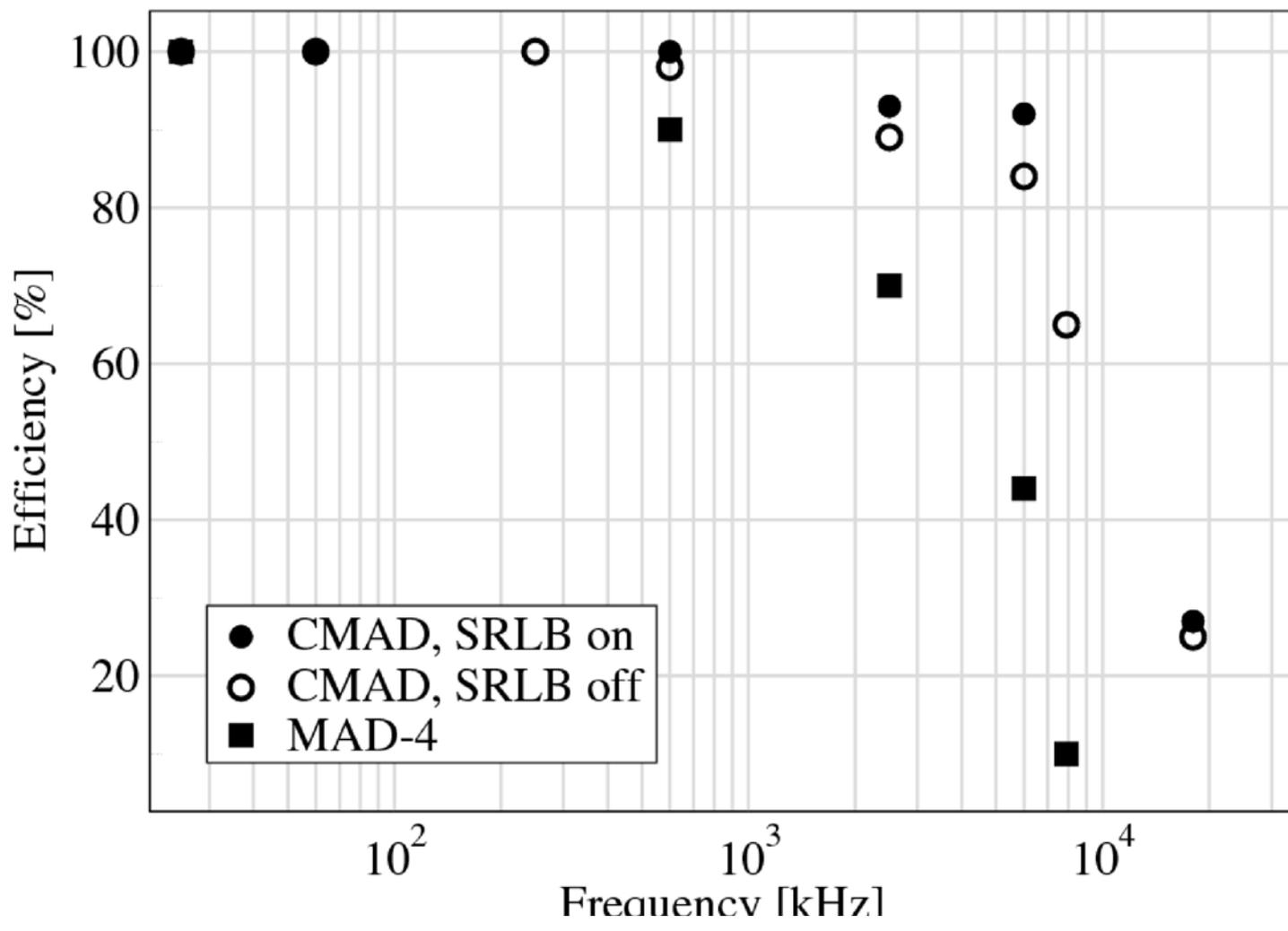





Integrating digital and analog



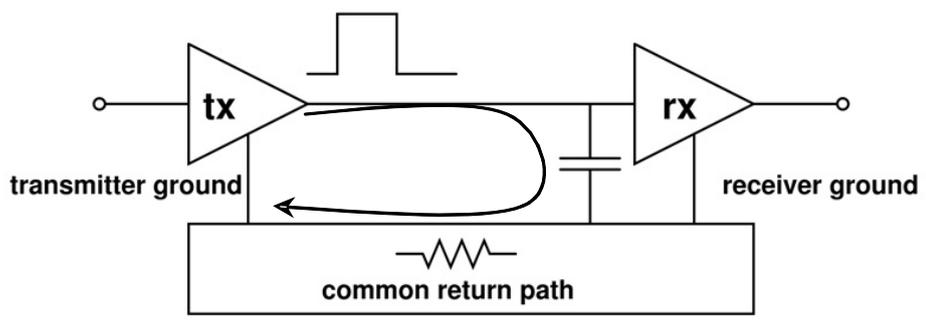- ...can be very dangerous!!
- $1.2 \text{ V} \times 1 \text{ fF} = 1 \text{ fC} = 6250 \text{ electrons...}$
- Amplifiers input must be very well isolated from the digital part
- Coupling can easily occur through the I/O
- Use of differential signalling on chip mandatory....





a)

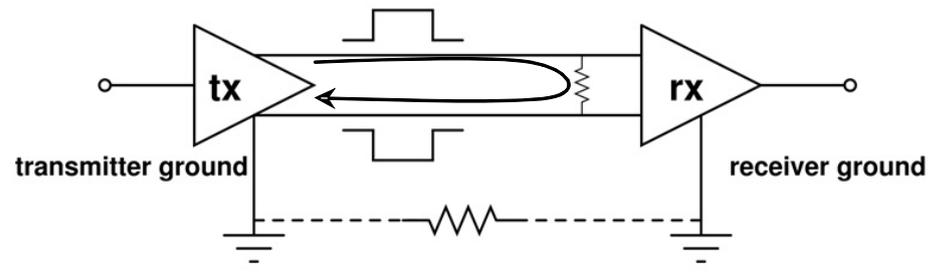

b)

Internal digital coupling

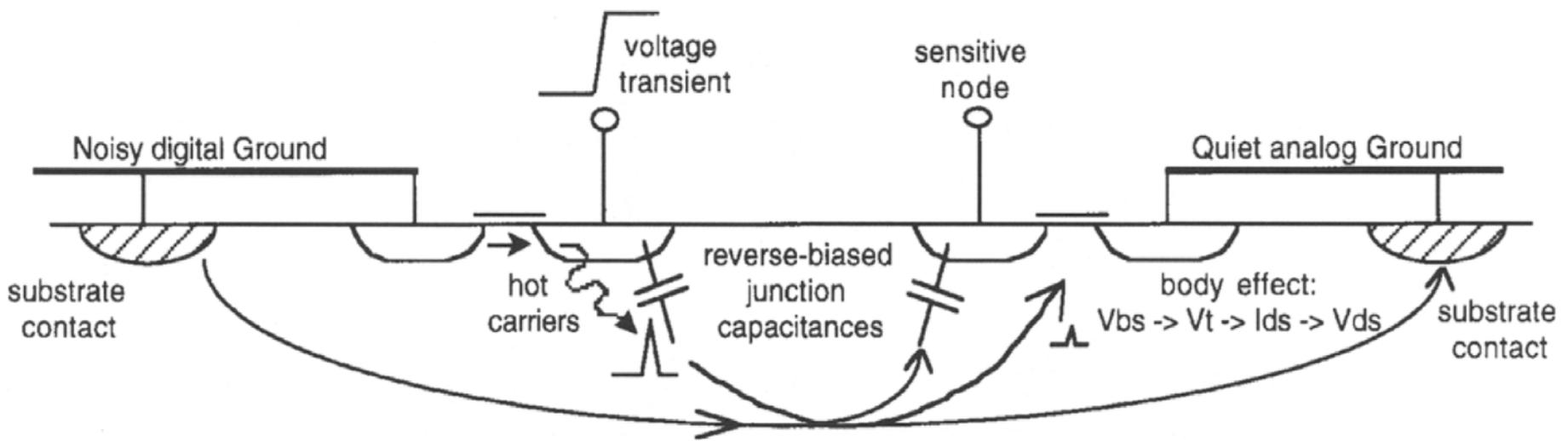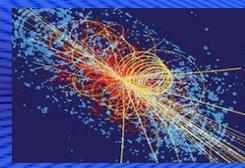



Homogeneous wafer





epi-wafer




Which signals are more dangerous?

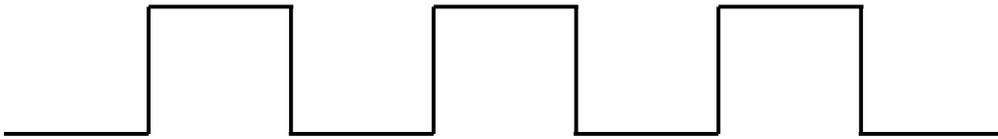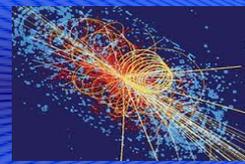


(De)-coupling

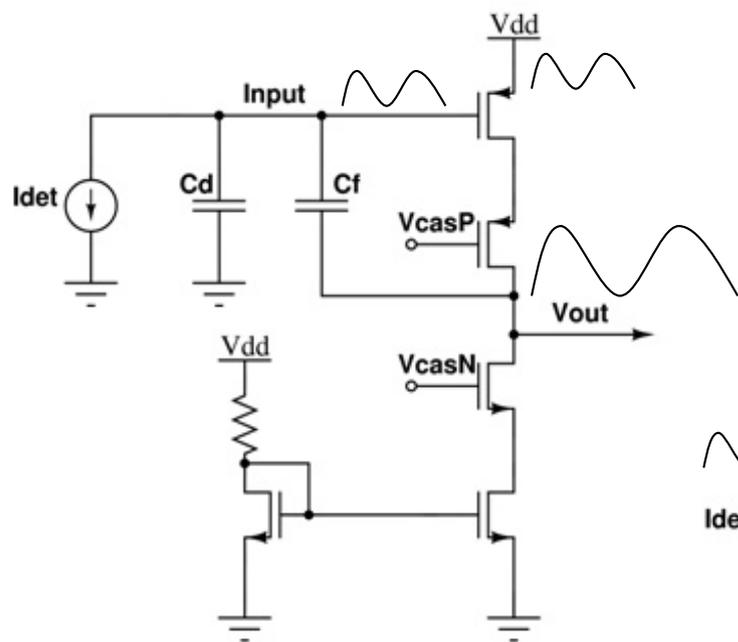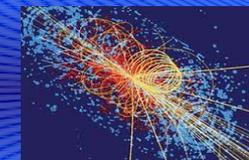



a)

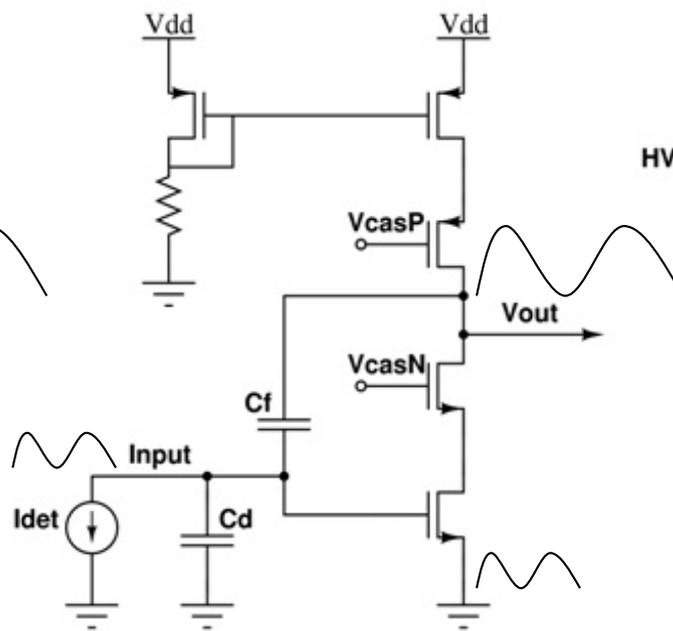


b)

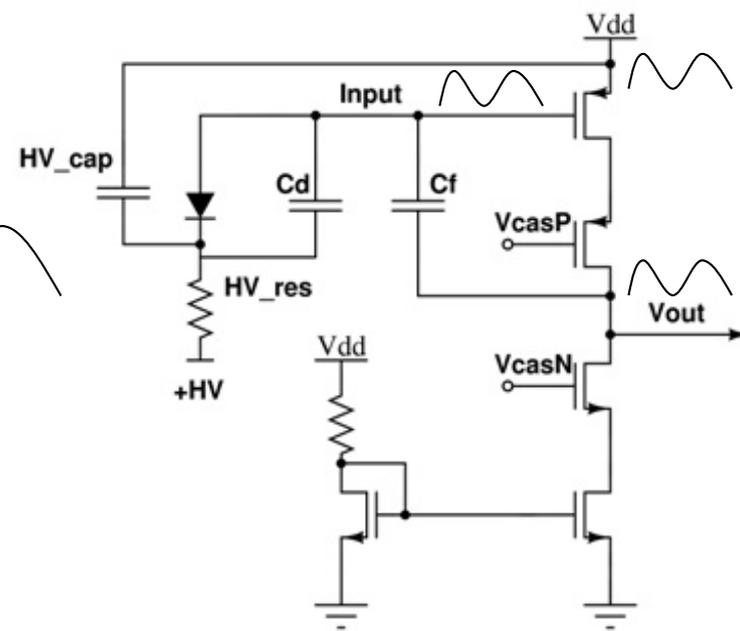


c)

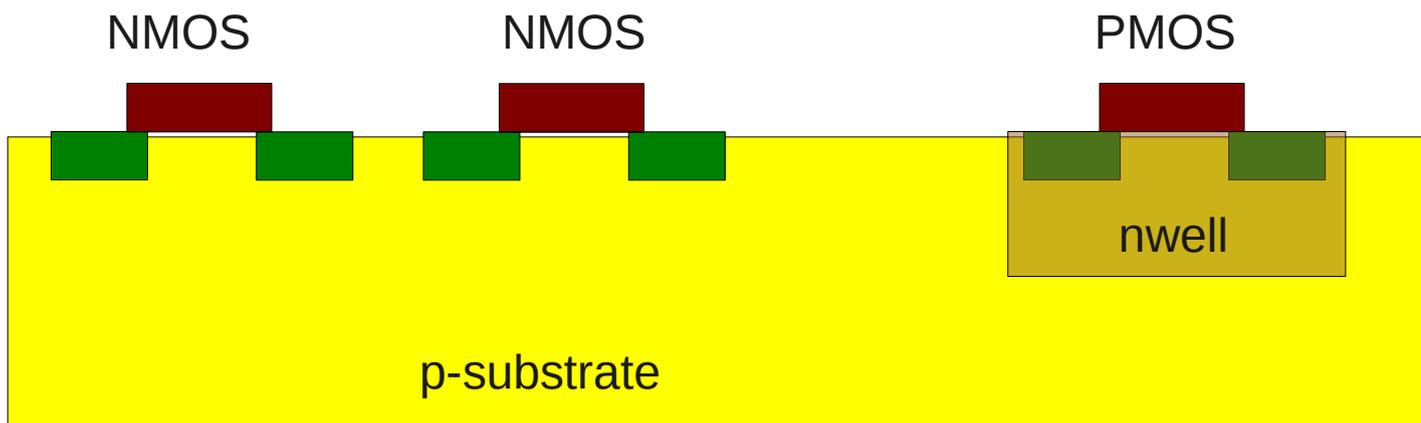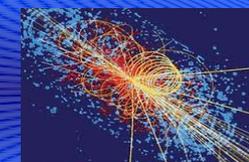

Standard nwell process

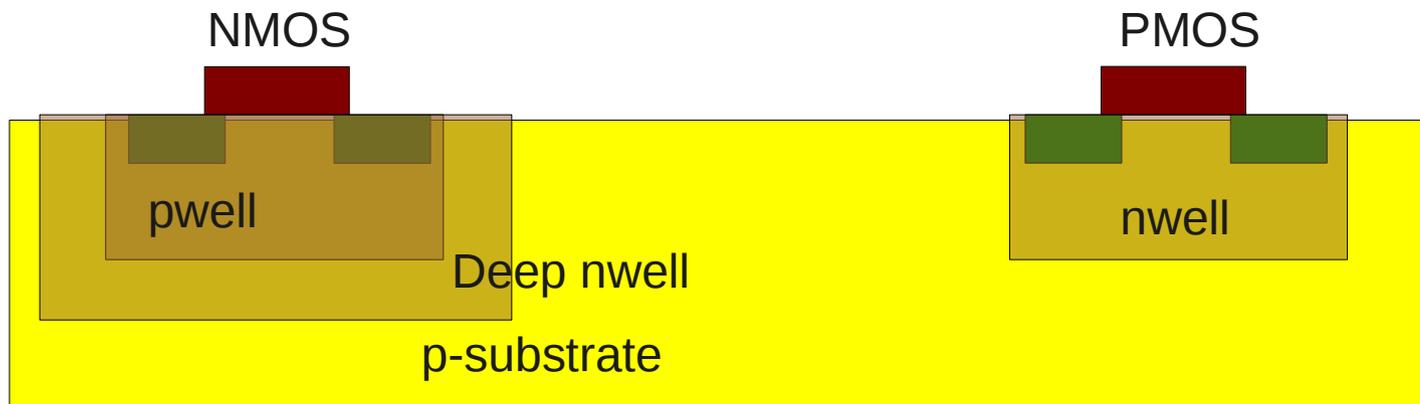

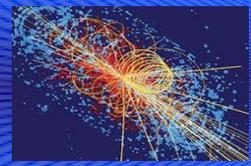Triple well possible in very deep submicron processes (0.13 μm and beyond)



PRESSMEDDELANDE
Press release

5 October 2010

The Nobel Prize in Physics 2010

The Royal Swedish Academy of Sciences has decided to award the Nobel Prize in Physics for 2010 to

Andre Geim

University of Manchester, UK

and

Konstantin Novoselov

University of Manchester, UK




“for groundbreaking experiments regarding the two-dimensional material graphene”

Graphene – the perfect atomic lattice

A thin flake of ordinary carbon, just one atom thick, lies behind this year’s Nobel Prize in Physics.

Andre Geim and Konstantin Novoselov have shown that carbon in such a flat form has exceptional properties that originate from the remarkable world of quantum physics.

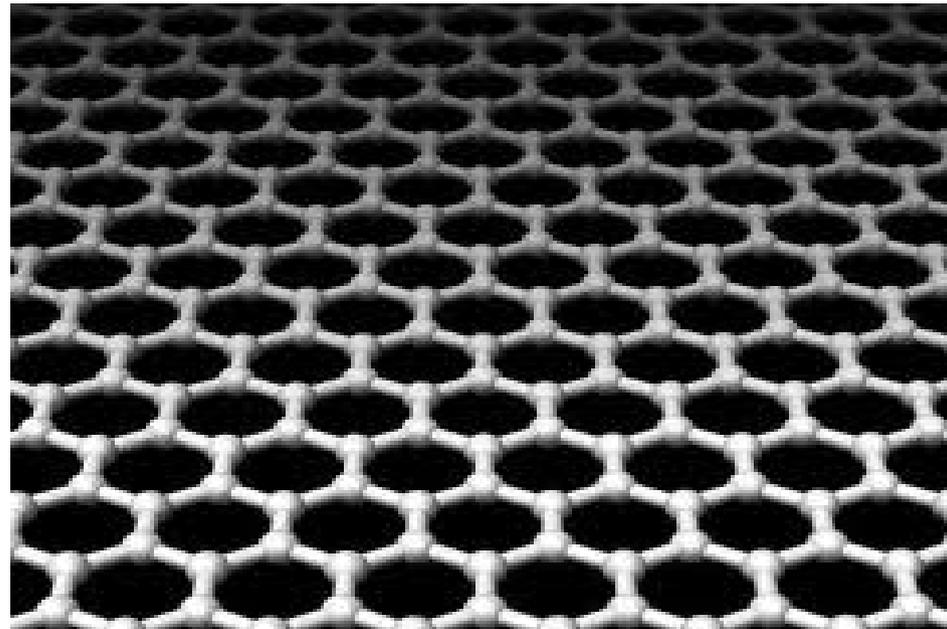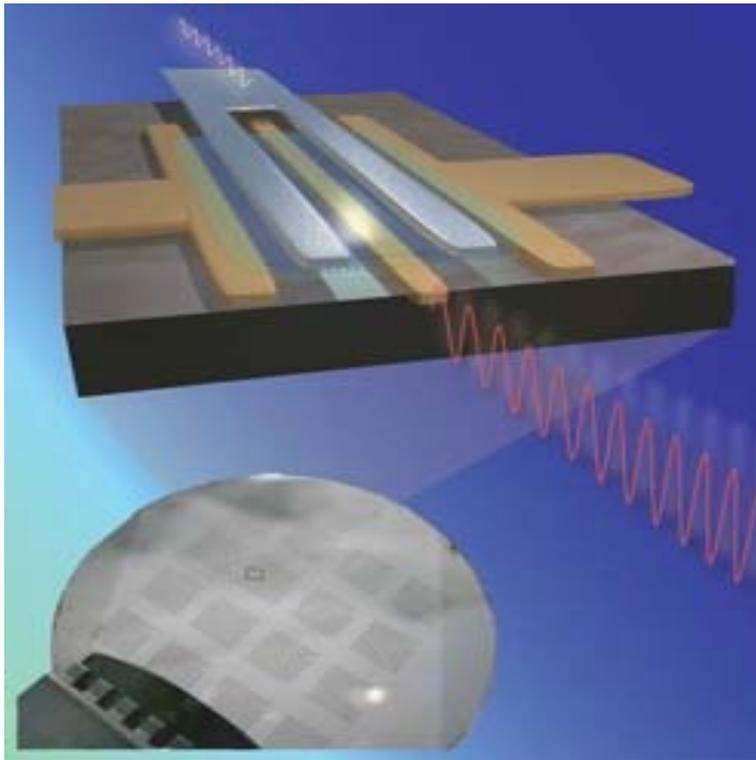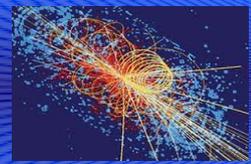When mixed into plastics, graphene can turn them into conductors of electricity while making them more heat resistant and mechanically robust. This resilience can be utilised in new super strong materials, which are also thin, elastic and lightweight. In the future, satellites, airplanes, and cars could be manufactured out of the new



- Maximum theoretical mobility: $200000 \text{ cm}^2/\text{V s}$ (1350 of Si)
- In practice 40.000 achieved. FT of 100 GHz demonstrated with 240 nm gate
- Symmetry between electrons and holes
- Still in its infancy....
- End of CMOS scaling around 2020, so CMOS still a good baseline choice for future detectors!