

FALAPHEL: Drivers

Gabriele Ciarpi

INFN Pisa

17/01/2021

Drivers





- 25 Gb/s driver in 28 nm HPC for SiPh Ring Resonator
- 12.5 Gb/s CML driver in 28 nm HPC+ for SERDES
- 12.5 GHz clock receiver in 28 nm HPC+ for SERDES
- 25 Gb/s driver in 28 nm HPC+ for SiPh Ring Resonator

25 Gb/s Driver for RR in HPC-28 nm



Old design submitted in December 2020, testing board designed in 2021, first tests performed in October 2021.

  Driver for SiPh Ring Resonator device able to sustain 25 Gb/s




Layout of the 25 Gb/s driver in 28 nm


High-speed Board Design



 
Great effort into the modeling of the SiPh devices but also into the testing board design



High-speed board with 2.92 mm connectors

 

 
Board etch to reduce the bonding wire length (bonding capability should be improved)




Electro-magnetic simulations

First Electrical Measurements-1

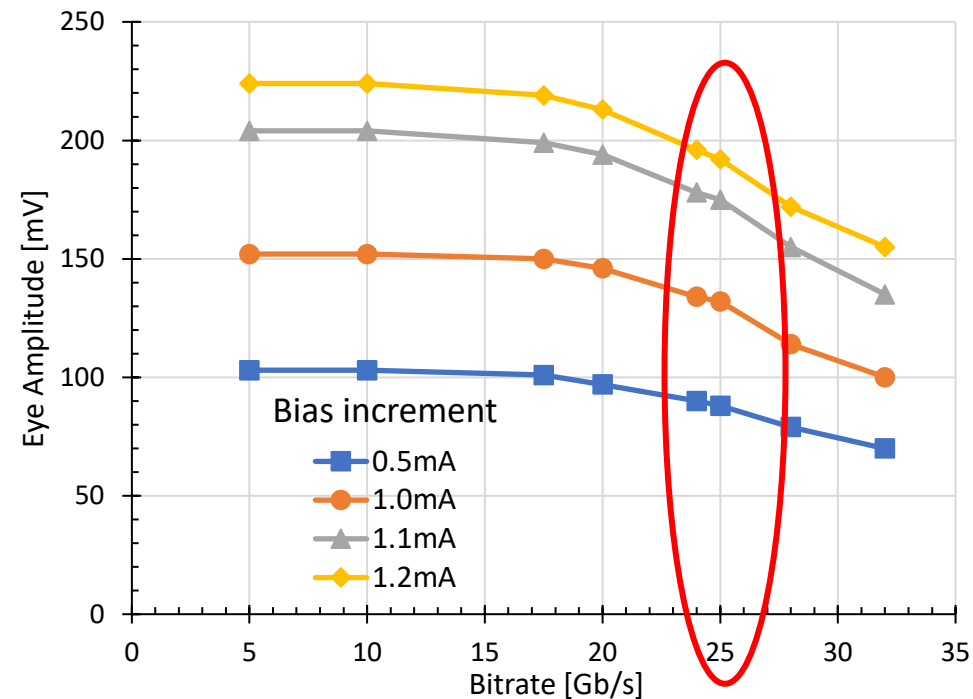Electrical measurements of the HPC 28 nm driver




 Voltage amplitude divided by a 4 factor (2 for load and 2 for Balun)




The first measurements on the 28 nm driver shown its ability to operate up 25 Gb/s

First Electrical Measurements-2

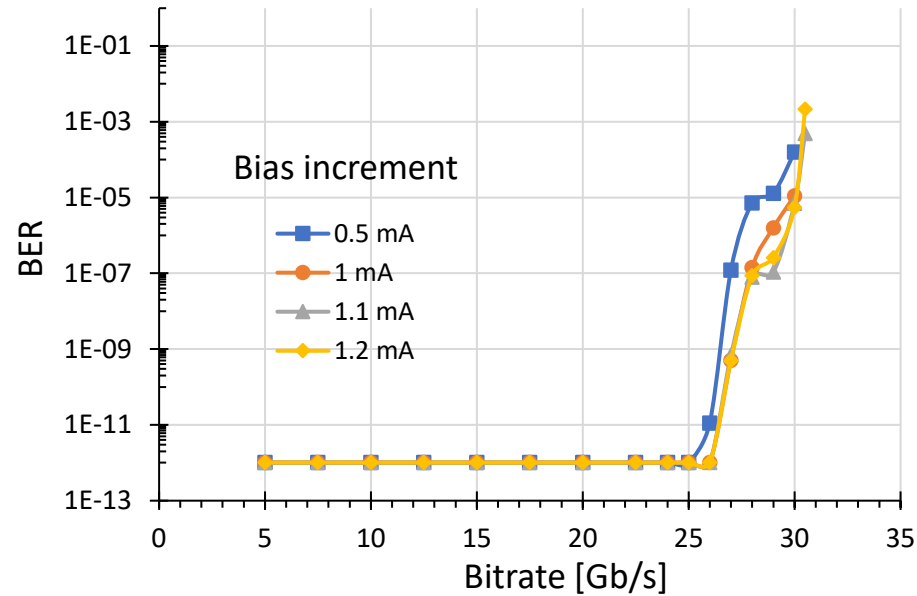


The electrical BER measurements on the HPC 28 nm driver show a value lower than 10⁻¹² up to 25 Gb/s

 What about radiation? Working in progress...



12.5 Gb/s CML driver in 28 nm HPC+

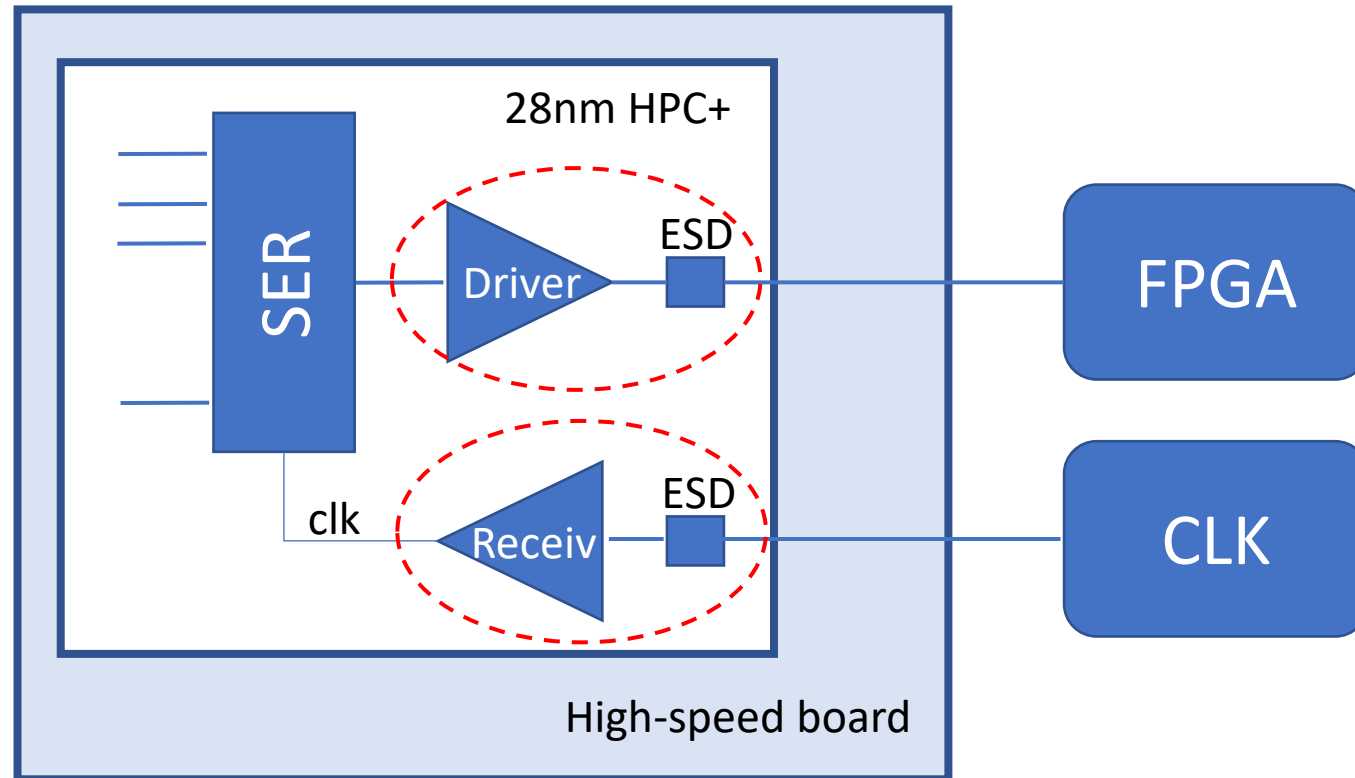



Followed approach:

Translate the previous 25 Gb/s driver to the HPC+ technology and check its operability

High-speed ESD in HPC+



  Translate the custom ESD protections designed in HPC to the HPC+ technology



In-house

- 1 kV HBM ESD with low capacitance (160-200 fF)
- Low resistance Power clamps

The HPC+ technology held by INFN has its own PADs and ESDs for power and low speed (Guido)



- High-speed ESD only where it is required

Note: Power clamps in HPC have some problems

12.5 Gb/s CML driver in 28 nm HPC+




Same driver's structure of HPC

  

There is still work to be done

- Maximum input capacitance?
- Remove the active peaking?
- Translate into INFN tech

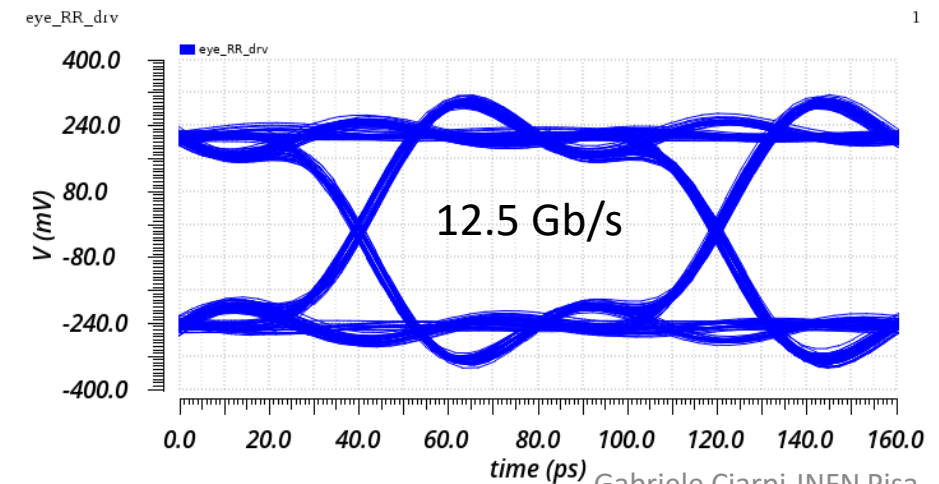Simulation of the output signals considering the FPGA loading




12.5 GHz clock receiver in 28 nm HPC+




Working in progress...

25 Gb/s driver in 28 nm HPC+

HPC driver results

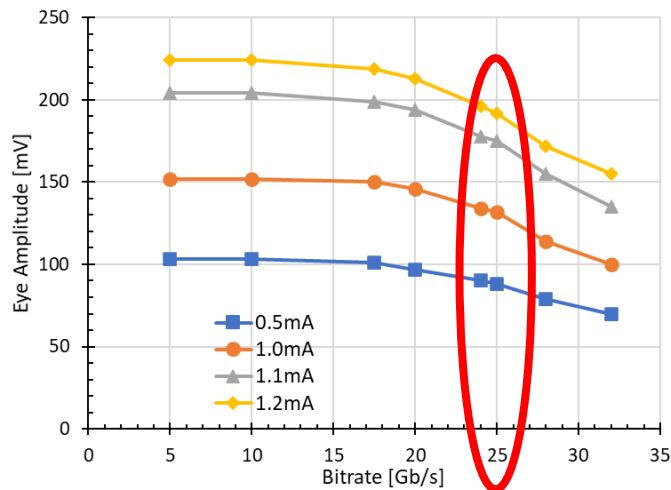

 How can we improve the driver bandwidth?
Which is the main limitation of driver bandwidth?




- Inductive peaking
 - Custom Low Cap
 - Short Wires
 - Ring Resonator
- 3D?




???

Other bandwidth extension techs

 

Inductive peaking

BWER ≈ 1.72

 


T-coil peaking

BWER ≈ 4.1

Custom design of T-coil transformer:

 - First simulations of TSMC library inductors did not match the tech results (10% discrepancy in L and 55% discrepancy in Q)
- Now simulations match technology devices (less 10% discrepancy to be refined)
- Many TSMC inductors show a resonant frequency below 10-20 GHz
- Work in progress...



Next points



- Close the 12.5 Gb/s HPC+ driver for the SERDES
- Design the 12.5 GHz HPC+ receiver for the clock of the SERDES
- Design the 25 Gb/s HPC+ driver for the RR with T-coil and RR model (submission: 3° quarter 2022)
- Expose the 25 Gb/s HPC driver to TID e SEE
- Connect the 25 Gb/s HPC driver to SiPh RR and test them

Thanks for the attention