



# Front-end Electronics for Nuclear Physics

Riccardo Introzzi

by Physics Department - INFN PoliTO

November 6, 2010



# Signals in Nuclear Physics



- 1 Detector Overview
  - Particle Detectors
  - Detector Signals
  - Detector Examples



# Signal Acquisition

- 2 Signal Acquisition
  - Nyquist Theorem
  - DAQ
  - Basic Front-end
  
- 3 Functional Blocks
  - PreAmp
  - Anti-aliasing
  - S/H
  - ADC
  - Multiplexer
  
- 4 Fast Transient Acquisition
  - Analog Memory
  - Fast Sampling
  - Fast Switches



# Signal Acquisition

- 2 Signal Acquisition
  - Nyquist Theorem
  - DAQ
  - Basic Front-end
  
- 3 Functional Blocks
  - PreAmp
  - Anti-aliasing
  - S/H
  - ADC
  - Multiplexer
  
- 4 Fast Transient Acquisition
  - Analog Memory
  - Fast Sampling
  - Fast Switches





# Signal Acquisition

- 2 Signal Acquisition
  - Nyquist Theorem
  - DAQ
  - Basic Front-end
  
- 3 Functional Blocks
  - PreAmp
  - Anti-aliasing
  - S/H
  - ADC
  - Multiplexer
  
- 4 Fast Transient Acquisition
  - Analog Memory
  - Fast Sampling
  - Fast Switches



# Fast Circuits for Data Acquisition



## 5 Fast Signal Acquisition

- 6 Shaper
  - Pulse integrator
  - PD
  - PHA

- 7 Discriminator
  - CFD

- 8 Time Measurement
  - TAC
  - TDC
  - Mean Timer



# Fast Circuits for Data Acquisition



## 5 Fast Signal Acquisition

### 6 Shaper

- Pulse integrator
- PD
- PHA

### 7 Discriminator

- CFD

### 8 Time Measurement

- TAC
- TDC
- Mean Timer



# Fast Circuits for Data Acquisition



## 5 Fast Signal Acquisition

### 6 Shaper

- Pulse integrator
- PD
- PHA

### 7 Discriminator

- CFD

### 8 Time Measurement

- TAC
- TDC
- Mean Timer



# Fast Circuits for Data Acquisition



- 5 Fast Signal Acquisition
- 6 Shaper
  - Pulse integrator
  - PD
  - PHA
- 7 Discriminator
  - CFD
- 8 Time Measurement
  - TAC
  - TDC
  - Mean Timer





# Part I

## Signals in Particle Physics



# Detector Types (1)



## Ionizing radiation detectors:

- Gas chambers
  - Ionization chambers
  - Proportional Counters - HV: charge multiplication, (1 keV, 100 keV)
  - Geiger Counters - fixed-size pulses: no energy information
- Scintillators with Photo Multiplier Tubes (PMT)
  - NaI(Tl) - 6% energy resolution, (10 keV, 10 GeV), 1  $\mu$ s pulses
  - Plastic - poorer resolution, 10 ns pulses
  - Liquid 'cocktails' - mixed with radioisotopes
- Solid State detectors - @ 77 K
  - Si(Li) - (1 keV, 50 keV), 2.5% energy resolution
  - Ge(Li) - (10 keV, 10 MeV), 0.14% energy resolution
  - High Purity Germanium Detectors (HPGe) - Intrinsic semiconductor



# Detector Types (1)



Ionizing radiation detectors:

- Gas chambers
  - Ionization chambers
  - Proportional Counters - HV: charge multiplication, (1 keV, 100 keV)
  - Geiger Counters - fixed-size pulses: no energy information
- Scintillators with Photo Multiplier Tubes (PMT)
  - NaI(Tl) - 6% energy resolution, (10 keV, 10 GeV), 1  $\mu$ s pulses
  - Plastic - poorer resolution, 10 ns pulses
  - Liquid 'cocktails' - mixed with radioisotopes
- Solid State detectors - @ 77 K
  - Si(Li) - (1 keV, 50 keV), 2.5% energy resolution
  - Ge(Li) - (10 keV, 10 MeV), 0.14% energy resolution
  - High Purity Germanium Detectors (HPGe) - Intrinsic semiconductor





# Detector Types (1)



Ionizing radiation detectors:

- Gas chambers
  - Ionization chambers
  - Proportional Counters - HV: charge multiplication, (1 keV, 100 keV)
  - Geiger Counters - fixed-size pulses: no energy information
- Scintillators with Photo Multiplier Tubes (PMT)
  - NaI(Tl) - 6% energy resolution, (10 keV, 10 GeV), 1  $\mu$ s pulses
  - Plastic - poorer resolution, 10 ns pulses
  - Liquid 'cocktails' - mixed with radioisotopes
- Solid State detectors - @ 77 K
  - Si(Li) - (1 keV, 50 keV), 2.5% energy resolution
  - Ge(Li) - (10 keV, 10 MeV), 0.14% energy resolution
  - High Purity Germanium Detectors (HPGe) - Intrinsic semiconductor



# Detector Types (1)



Ionizing radiation detectors:

- Gas chambers
  - Ionization chambers
  - Proportional Counters - HV: charge multiplication, (1 keV, 100 keV)
  - Geiger Counters - fixed-size pulses: no energy information
- Scintillators with Photo Multiplier Tubes (PMT)
  - NaI(Tl) - 6% energy resolution, (10 keV, 10 GeV), 1  $\mu$ s pulses
  - Plastic - poorer resolution, 10 ns pulses
  - Liquid 'cocktails' - mixed with radioisotopes
- Solid State detectors - @ 77 K
  - Si(Li) - (1 keV, 50 keV), 2.5% energy resolution
  - Ge(Li) - (10 keV, 10 MeV), 0.14% energy resolution
  - High Purity Germanium Detectors (HPGe) - Intrinsic semiconductor



## Detector Types (2)

### Charged particle detectors:

- Surface-barrier detectors - @ 300 K, (1 MeV, 100 MeV), 0.2% energy resolution
  - Si(Li)
  - Ge(Li)
- Cherenkov detectors - Cherenkov 'light boom', above 1 GeV
- Ionization chambers - Ar, single or multi wire or plate electrodes
- Shower chambers - liquid Ar, 'calorimeters'
- Scintillators with UV PMT - gas or liquid, very fast
  - Ar
  - Xe
- Drift chambers - gas volume criss-crossed by wire arrays with applied voltage to drift out ions and track particle paths
  - Ar-ethane mixture - 0.2 mm spatial resolution



## Detector Types (2)

Charged particle detectors:

- Surface-barrier detectors - @ 300 K, (1 MeV, 100 MeV), 0.2% energy resolution
  - Si(Li)
  - Ge(Li)
- Cherenkov detectors - Cherenkov 'light boom', above 1 GeV
- Ionization chambers - Ar, single or multi wire or plate electrodes
- Shower chambers - liquid Ar, 'calorimeters'
- Scintillators with UV PMT - gas or liquid, very fast
  - Ar
  - Xe
- Drift chambers - gas volume criss-crossed by wire arrays with applied voltage to drift out ions and track particle paths
  - Ar-ethane mixture - 0.2 mm spatial resolution



## Detector Types (2)

Charged particle detectors:

- Surface-barrier detectors - @ 300 K, (1 MeV, 100 MeV), 0.2% energy resolution
  - Si(Li)
  - Ge(Li)
- Cherenkov detectors - Cherenkov 'light boom', above 1 GeV
- Ionization chambers - Ar, single or multi wire or plate electrodes
- Shower chambers - liquid Ar, 'calorimeters'
- Scintillators with UV PMT - gas or liquid, very fast
  - Ar
  - Xe
- Drift chambers - gas volume criss-crossed by wire arrays with applied voltage to drift out ions and track particle paths
  - Ar-ethane mixture - 0.2 mm spatial resolution



## Detector Types (2)

Charged particle detectors:

- Surface-barrier detectors - @ 300 K, (1 MeV, 100 MeV), 0.2% energy resolution
  - Si(Li)
  - Ge(Li)
- Cherenkov detectors - Cherenkov 'light boom', above 1 GeV
- Ionization chambers - Ar, single or multi wire or plate electrodes
- Shower chambers - liquid Ar, 'calorimeters'
- Scintillators with UV PMT - gas or liquid, very fast
  - Ar
  - Xe
- Drift chambers - gas volume criss-crossed by wire arrays with applied voltage to drift out ions and track particle paths
  - Ar-ethane mixture - 0.2 mm spatial resolution





## Detector Types (2)

Charged particle detectors:

- Surface-barrier detectors - @ 300 K, (1 MeV, 100 MeV), 0.2% energy resolution
  - Si(Li)
  - Ge(Li)
- Cherenkov detectors - Cherenkov 'light boom', above 1 GeV
- Ionization chambers - Ar, single or multi wire or plate electrodes
- Shower chambers - liquid Ar, 'calorimeters'
- Scintillators with UV PMT - gas or liquid, very fast
  - Ar
  - Xe
- Drift chambers - gas volume criss-crossed by wire arrays with applied voltage to drift out ions and track particle paths
  - Ar-ethane mixture - 0.2 mm spatial resolution





# Pulse Shape 1



In general a detection event causes a current burst

- fast voltage ramp (usually negative)
- slower exponential-like decay ( $\sim 5$  ns)

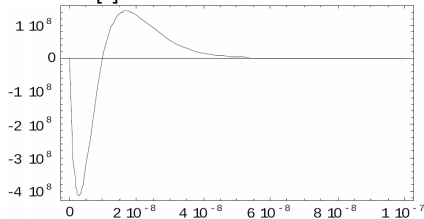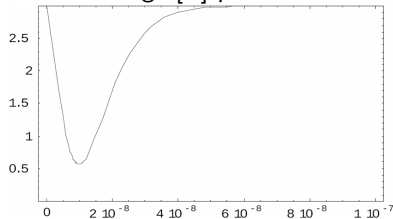Anode voltage [V] pulse in a PMT vs time [s]



## Pulse Shape 2

Quantity of interest may be related to

- collected charge number (e.g. energy spectroscopy in ionization chambers)
  - the integral of the pulse signal has to be derived
- maximum pulse voltage (e.g. energy spectroscopy in scintillators)
  - the maximum of voltage peak must be found
- pulse timing (e.g. Time of Flight (TOF) in Scintillators)
  - a characteristic time of the pulse shaping is needed
- detection of spatial position/s (e.g. drift chambers, TOF-walls)
  - many different channels are necessary and/or timing post-processing
- trajectory (e.g. particle recognition in drift chambers with magnetic field)
  - trajectory bending:  $R = p/(ZeB)$
  - heavy post-processing from multi-channel signals is required



## Pulse Shape 2

Quantity of interest may be related to

- collected charge number (e.g. energy spectroscopy in ionization chambers)
  - the integral of the pulse signal has to be derived
- maximum pulse voltage (e.g. energy spectroscopy in scintillators)
  - the maximum of voltage peak must be found
- pulse timing (e.g. Time of Flight (TOF) in Scintillators)
  - a characteristic time of the pulse shaping is needed
- detection of spatial position/s (e.g. drift chambers, TOF-walls)
  - many different channels are necessary and/or timing post-processing
- trajectory (e.g. particle recognition in drift chambers with magnetic field)
  - trajectory bending:  $R = p/(ZeB)$
  - heavy post-processing from multi-channel signals is required



## Pulse Shape 2

Quantity of interest may be related to

- collected charge number (e.g. energy spectroscopy in ionization chambers)
  - the integral of the pulse signal has to be derived
- maximum pulse voltage (e.g. energy spectroscopy in scintillators)
  - the maximum of voltage peak must be found
- pulse timing (e.g. Time of Flight (TOF) in Scintillators)
  - a characteristic time of the pulse shaping is needed
- detection of spatial position/s (e.g. drift chambers, TOF-walls)
  - many different channels are necessary and/or timing post-processing
- trajectory (e.g. particle recognition in drift chambers with magnetic field)
  - trajectory bending:  $R = p/(ZeB)$
  - heavy post-processing from multi-channel signals is required



## Pulse Shape 2

Quantity of interest may be related to

- collected charge number (e.g. energy spectroscopy in ionization chambers)
  - the integral of the pulse signal has to be derived
- maximum pulse voltage (e.g. energy spectroscopy in scintillators)
  - the maximum of voltage peak must be found
- pulse timing (e.g. Time of Flight (TOF) in Scintillators)
  - a characteristic time of the pulse shaping is needed
- detection of spatial position/s (e.g. drift chambers, TOF-walls)
  - many different channels are necessary and/or timing post-processing
- trajectory (e.g. particle recognition in drift chambers with magnetic field)
  - trajectory bending:  $R = p/(ZeB)$
  - heavy post-processing from multi-channel signals is required






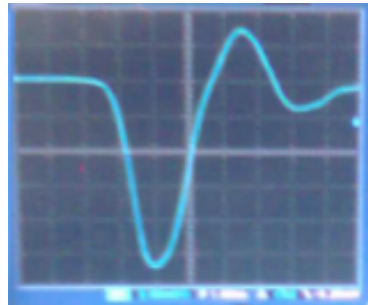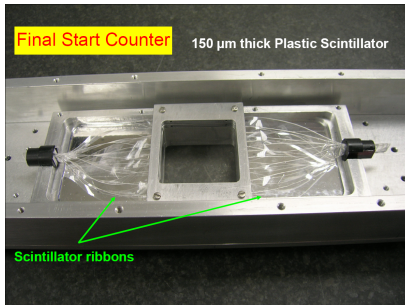
# Detector Examples 1





- Trigger detector based on a scintillator
  - The START pulse resolution is  $O(300 \text{ ps})$ , with long tails



# Detector Examples





## • Ionization Chamber

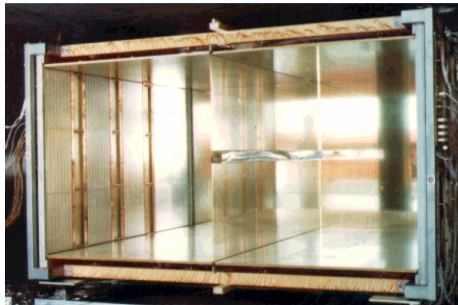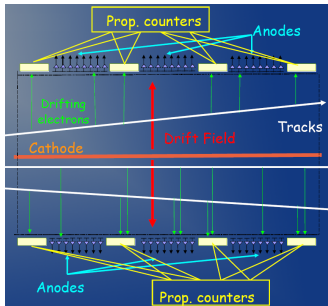
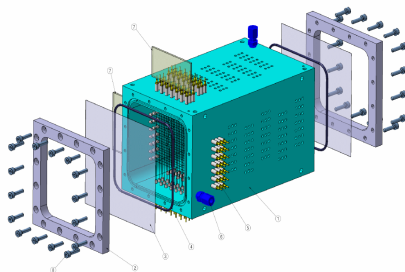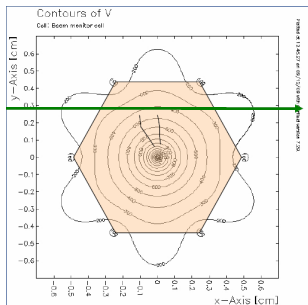
# Detector Examples





- Drift Chamber (very small one)
  - Hexagonal cell: 0.5 cm radius
  - Spatial resolution  $O(100-200) \mu\text{m}$



# Detector Examples




- Drift Chamber (very small one)

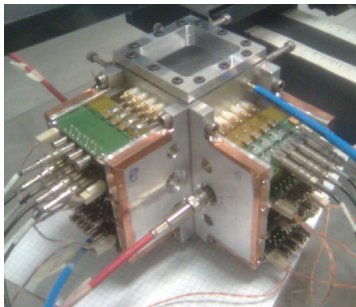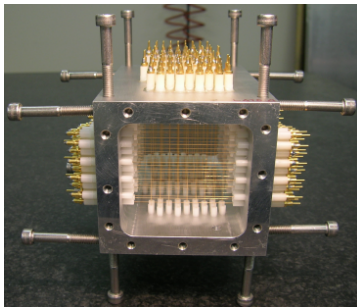
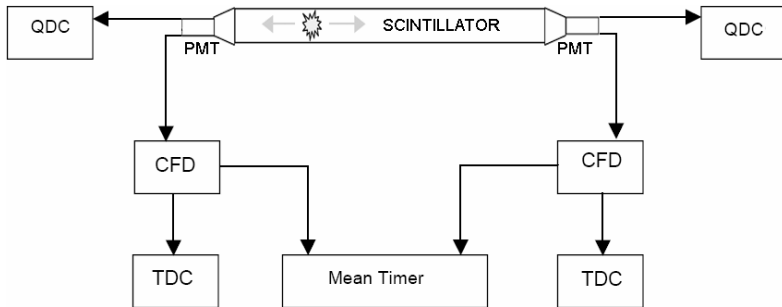
# Detector Examples





- TOF-wall
  - based on plastic scintillator
  - slabs are 1.10 m long, 2.5cm wide and 1 cm thick with a PMT at each edge



# Detector Examples



- TOF-wall

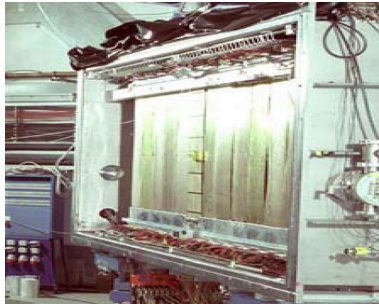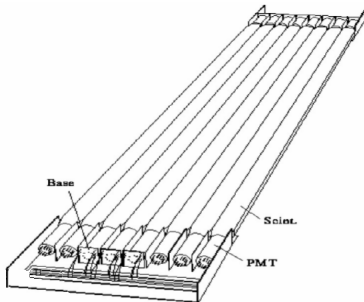



## Part II


# Signal Acquisition


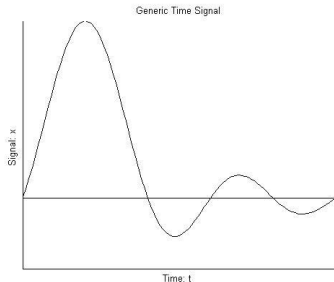
# Nyquist Theorem



- Consider a generic time signal  $x(t)$  which has to be sampled





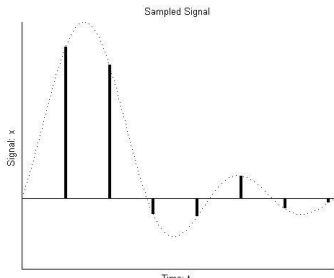
# Nyquist Theorem

- The sampled signal can be built multiplying by a  $\delta$  comb  $T$  spaced in time
  - $T$  is the sampling period



$$\begin{aligned}
 x_{\delta}(t) &= \sum_{i=-\infty}^{+\infty} T x(iT) \delta(t - iT) \\
 &= x(t) T \sum_{i=-\infty}^{+\infty} \delta(t - iT)
 \end{aligned}$$



# Nyquist Theorem

- Define  $\Delta(f)$  as the Fourier transform of the time  $\delta$  comb
  - the spectrum of a time  $\delta$  comb is a frequency  $\delta$  comb
  - $f_s = 1/T$  be the sampling frequency

$$\begin{aligned}\Delta(f) &= \mathcal{F} \left[ T \sum_{i=-\infty}^{+\infty} \delta(t - iT) \right] \\ &= \sum_{i=-\infty}^{+\infty} \delta(f - if_s)\end{aligned}$$

- Recall the Fourier transform of the product of two functions: convolution product ( $\star$ ) of the respective spectra


$$\begin{aligned}\mathcal{F}[z(t)y(t)] &= \int_{-\infty}^{+\infty} X(a)Y(f - a)da \\ &= X(f) \star Y(f)\end{aligned}$$


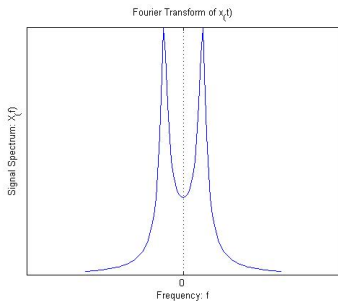
# Nyquist Theorem



- $X(f)$  be the Fourier transform of  $x(t)$



# Nyquist Theorem



- $X_\delta(f)$  be the Fourier transform of  $x_\delta(t)$
- $X_\delta(f)$  is the convolution product of  $X(f)$  and  $\Delta(f)$

$$\begin{aligned} X_\delta(t) &= X(f) \star \Delta(f) \\ &= \sum_{i=-\infty}^{+\infty} X(f - if_s) \end{aligned}$$



- The spectrum  $X_\delta(f)$  of the sampled signal is the sum of infinite replicas of the spectrum  $X(f)$  of the original signal shifted  $f_s$  away one from each other



# Nyquist Theorem


- The Nyquist rule grants the tails of successive replicas do not overlap
  - given the bandwidth extension  $B$  of the original spectrum and the sampling frequency  $f_s$

$$f_s \geq 2B$$

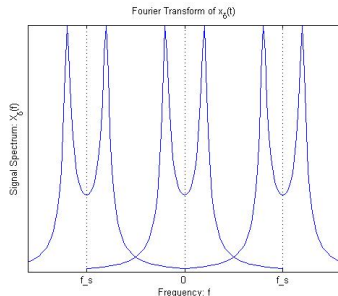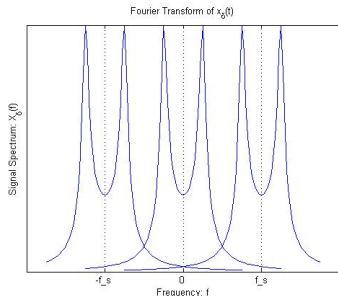

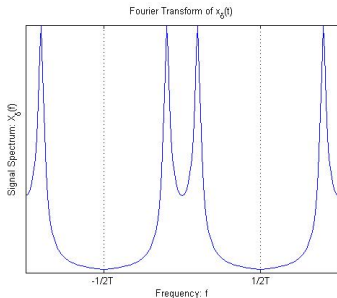
# Nyquist Theorem

- Low-pass filtering the base band replica the original signal can be reconstructed
- the task is ideally performed by the Nyquist interpolator: a rectangular low-pass filter
  - the Nyquist pass-band coincides with the bandwidth  $B$  of the original signal


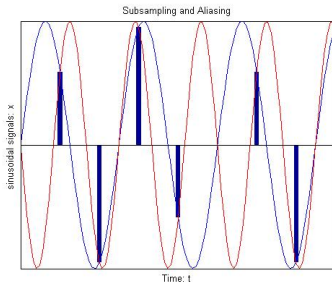
# Aliasing and Sub-sampling

- Aliasing is given by the spectrum replica tail overlapping: different harmonic lines of the original spectrum are indistinguishable
- It is evident when a given harmonic line is focused
  - in the example a 3 kHz sinusoid, sampled @ 8 kHz, shows ambiguity with a 2 kHz sinusoid



# Data Acquisition System



Analog-digital conversion involves two discretization processes:

- 1 sampling
  - continuous time  $\rightarrow$  discrete time
  - non perfect low-pass filtering for anti-aliasing
  - approximation by real interpolators (real low-pass filter, HW/SW)
- 2 discretization
  - continuous amplitude  $\rightarrow$  discrete amplitude
  - approximation given by the Least Significant Bit (LSB)





# Data Acquisition System



Analog-digital conversion involves two discretization processes:

- 1 sampling
  - continuous time  $\rightarrow$  discrete time
  - non perfect low-pass filtering for anti-aliasing
  - approximation by real interpolators (real low-pass filter, HW/SW)
- 2 discretization
  - continuous amplitude  $\rightarrow$  discrete amplitude
  - approximation given by the Least Significant Bit (LSB)



# Data Acquisition System




Analog-digital conversion involves two discretization processes:

- ① sampling
  - continuous time  $\rightarrow$  discrete time
  - non perfect low-pass filtering for anti-aliasing
  - approximation by real interpolators (real low-pass filter, HW/SW)
- ② discretization
  - continuous amplitude  $\rightarrow$  discrete amplitude
  - approximation given by the Least Significant Bit (LSB)


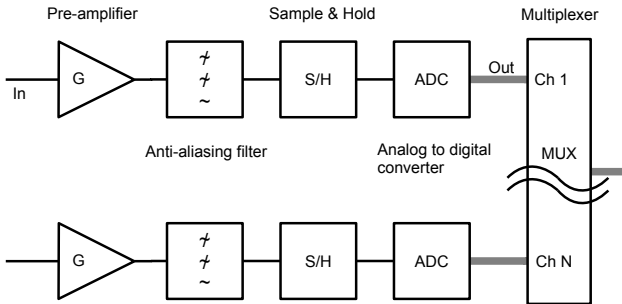
# Basic Front-end

- Pre-amplifier
- Anti-aliasing filter
- Sample & Hold (S/H)
- Analog to Digital Converter (ADC)
- Multiplexer (MUX)



# Pre-amplifier



## Features:



- first stage amplification:
  - maximizes Signal to Noise Ratio (SNR)
  - adapts voltage levels to the next measurement stage
- low output impedance, considerable current drive
  - buffers the input signal
  - sinks interference current injection: preserve SNR
- OpAmp configuration with SW-tunable feedback are common
  - differential input stage: common mode interference rejection
  - issues on bandwidth, stability and slew-rate require careful design
- pulse current integration is possible with capacitive feedback
  - charge summation is converted to voltage amplitude
  - drift due to input offset currents must be avoided


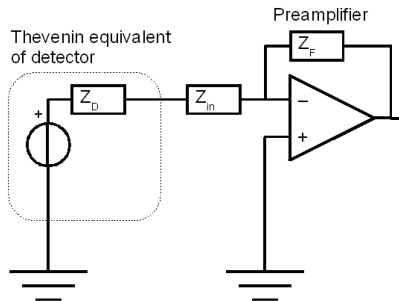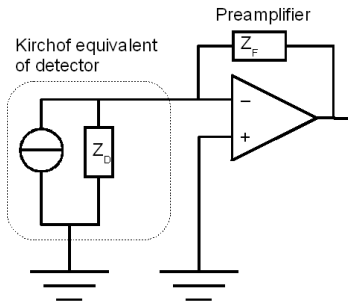
# Trans-impedance and Voltage amplifiers




- 1 trans-impedance amplifier for high source impedance
- 2 voltage amplifier for low source impedance


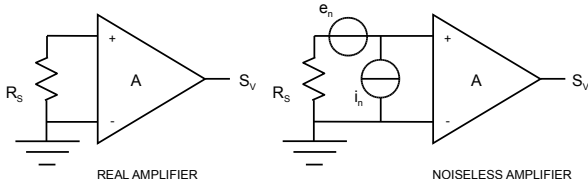
# Signal and Noise



Detectors usually provide very low-level output signals

- many source of noise and disturbance can overrun the signal
- careful design is needed especially for the first stage


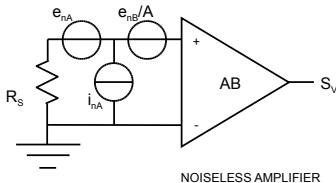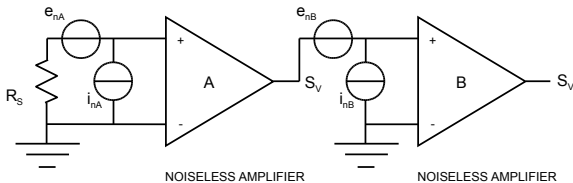
# Signal and Noise


- First stage equivalent noise remains at the input of the chain
- second stage contributes at the input only with its voltage equivalent noise, divided by the first stage gain


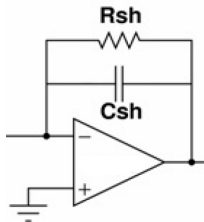
# Anti-aliasing Filter



- Low-pass filters are used to avoid aliasing effects
- filters can be implemented in amplifier feedback
- high order filters would be required to take advantage of the full ADC bandwidth
  - trade-off between high slope frequency cutoff and filter size and complexity
  - single pole feedback and OpAmp poles are exploited





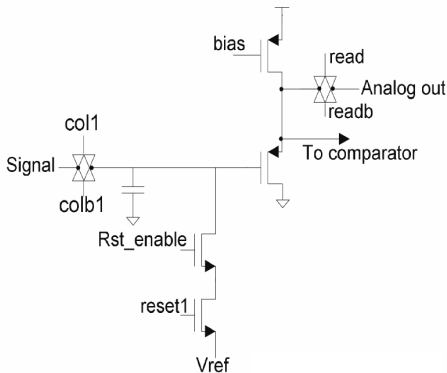
# Sample & Hold

Fast signals are sampled and then hold during A/D conversion time

- Capacitors as analog memory
  - droop issue: charge/discharge due to read-out  $I_{off}$
- CMOS Transmission gates as switching elements
  - signal feed-through issue: via  $C_{DS}$  of the switch



# Analog To Digital Converter (ADC)




- A/D Flash
- Successive Approximations Register (SAR)
- Double ramp A/D
- Source Follower Residue Amplification


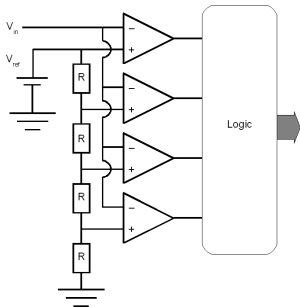
# ADFlash


- comparator array (one for each output bit)
- resistive reference scale
  - ratiometric (voltage divider), variable  $V_{ref}$
  - no missing code
  - high precision R needed
  - high power consumption (resistive scale)
- high speed (parallel computation)


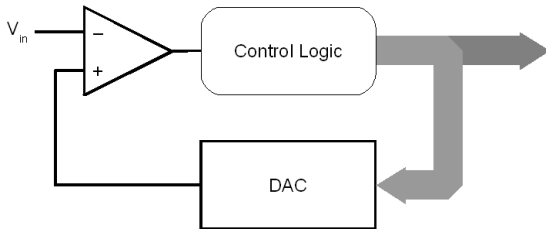
# SAR ADC



- single comparator
- feedback Digital to Analog Converter (DAC) provide voltage references
- logic controls successive approximations of the input signal
  - 1 up/down counter strategy
  - 2 bisection technique



# SAR ADC





Up/down counter

- “digital voltage follower”: 1 LSB fluctuation around the input
- long transient at start-up
- single step conversion once the signal is “locked”

Bisection technique

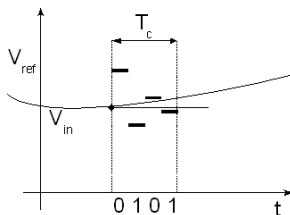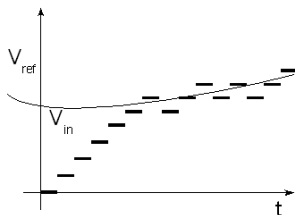- conversion time:  $T_c = N_{bit} T_{ck}$





# Source Follower Residue Amplification ADC



## State of the art ADC

- pipeline of  $N_{bit}$  identical stages
- simple working principle:
  - $bit_n = 1 \iff V_{in\ n} - V_{bit_n} > 0$
  - $V_{residue\ n} = V_{in} - V_{bit_n} bit_n$
  - $V_{out\ n} = 2V_{residue}$
- dynamic source follower
- 1 conversion at each pipeline step, just a delay of  $N_{bit}$  steps!

J. Hu, N. Dolev and B. Murmann:

*"A 9.4-bit, 50 Ms/s, 1.44 mW Pipelined ADC using Dynamic Source Follower Residue Amplification"*,

IEEE Journal of Solid State Circuits, **44** 4, 2009




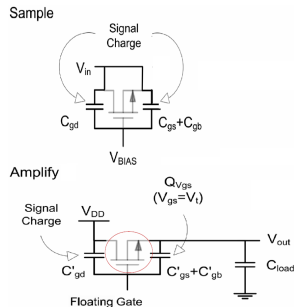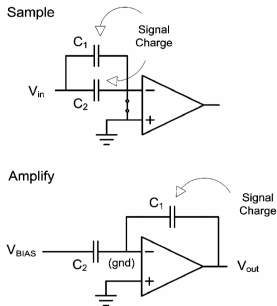
# Source Follower Residue Amplification ADC



Residue amplification implementation:


- 1 OpAmp based
  - cumbersome for power consumption
- 2 MOS based
  - exploits transistor characteristic capacitances





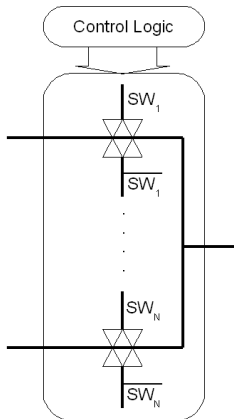
# Multiplexer

- Multiplexer (MUX) are switch array controlled by logic
  - transmission gate implementation in analog MUX - bidirectional
  - more switches can be on together (e.g. SAR DAC)





# Fast Transient Acquisition

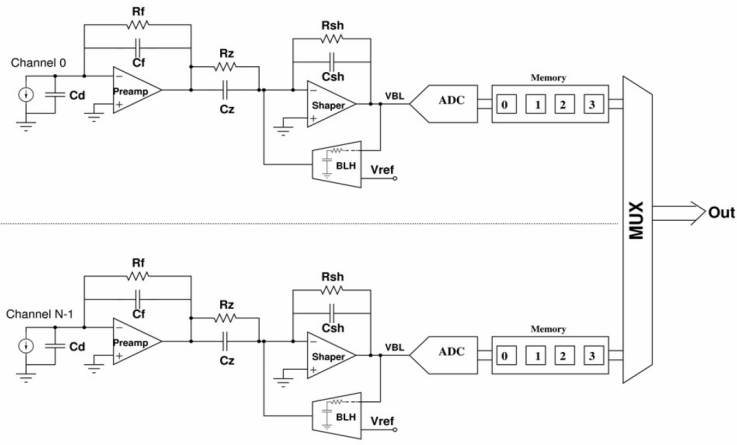
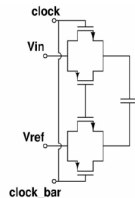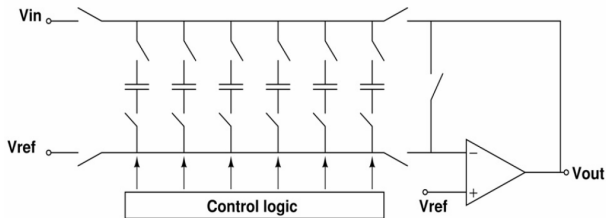
# Analog Memory




- Analog Memories: array of S/H cells
  - Dead Time → Pipeline


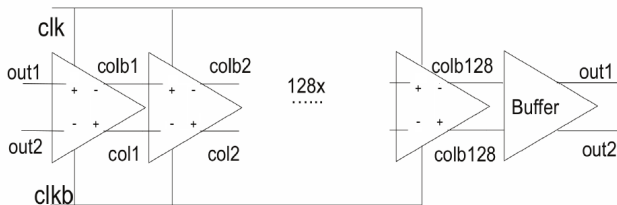
# Very Fast Control Logic





- sampling on both clock edges
- clock multiplication with local Phase Locked Loop (PLL)
- fast shift register with custom Flip/Flop
- delay line: logic gate propagation
  - Clock period variation with temperature


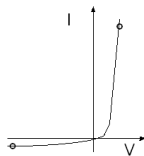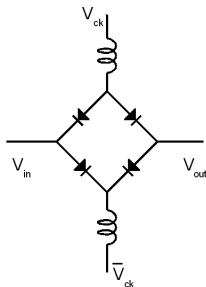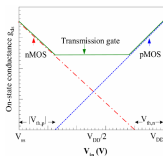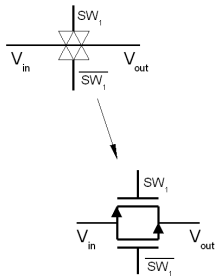
# Fast Switches



- CMOS transmission gate - low and constant conductance
- Diode bridge - very fast switching, inductors needed





## Part III

# Fast Data Acquisition



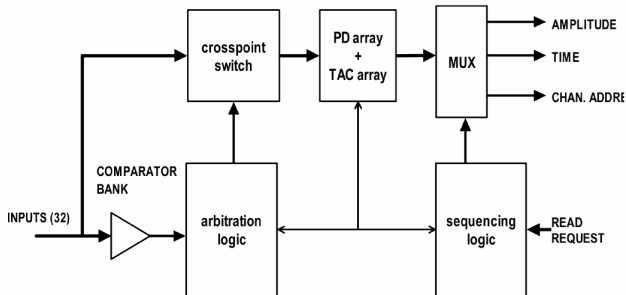
## Preliminary Considerations

Full digitization becomes impractical at high data rates (over 100 kHz)  
Only quantities of interest are gathered by pre-processing in the analog domain



- 1 pulse amplitude or area
- 2 timing detection
- 3 position detection



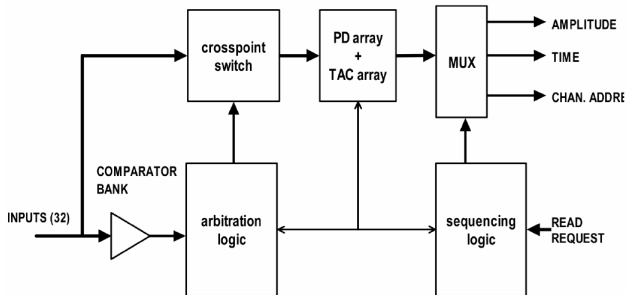
# Preliminary Considerations

Full digitization becomes impractical at high data rates (over 100 kHz)  
Only quantities of interest are gathered by pre-processing in the analog domain



- 1 pulse amplitude or area
- 2 timing detection
- 3 position detection





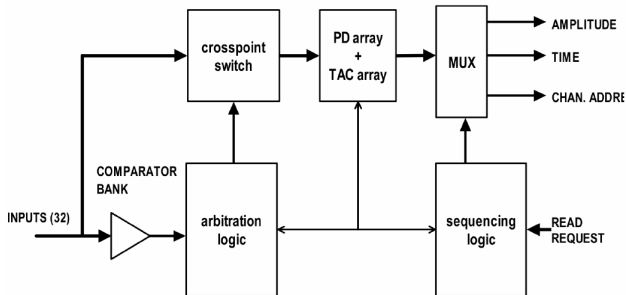
## Preliminary Considerations

Full digitization becomes impractical at high data rates (over 100 kHz)  
Only quantities of interest are gathered by pre-processing in the analog domain



- 1 pulse amplitude or area
- 2 timing detection
- 3 position detection



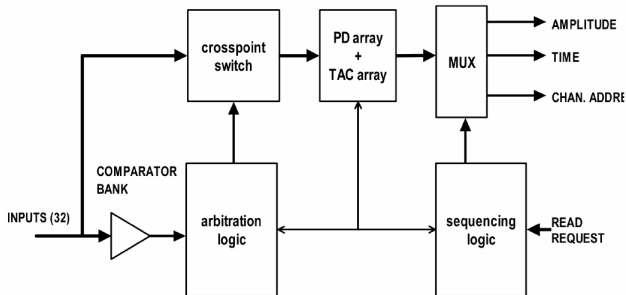
# Preliminary Considerations

Full digitization becomes impractical at high data rates (over 100 kHz)  
Only quantities of interest are gathered by pre-processing in the analog domain



- 1 pulse amplitude or area
- 2 timing detection
- 3 position detection



# Shaper




- Amplifier: see pre-amplifier in DAQ
- Pulse integrator: provides a signal proportional to the pulse area
  - Proportional Counters are based on integrators as detector read-out
- Pulse detector (PD): outputs the maximum of the peak with a peak detect flag signal
  - Pulse Height Analyzers (PHA) use PDs as detector read-out


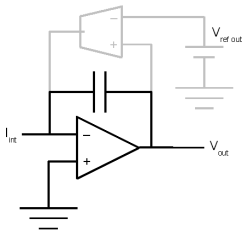
# Pulse integrator



- Exploits a capacitive feedback (i.e.  $\mathcal{F} [f \cdot dt] = \frac{1}{j\omega C}$ )
- OpAmp offset currents can give rise to output drifts
- An Operational Transconductance Amplifier (OTA) controls the DC output - Baseline Holder (BLH)



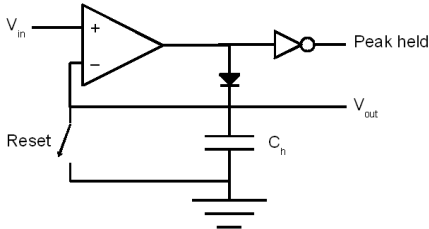
# Peak detector



Flags a peak detection and hold the peak maximum

- exploits unidirectional element
- a capacitor is charged up to the peak maximum and then holds the level





# Pulse Height Analyzer




- PDs coupled with ADCs allow to record the pulse height
- Pulse Height Analyzers (PHA) perform energy spectroscopy with a variety of detectors (e.g. proportional counters, scintillators, solid state detectors and surface barrier detectors)
  - based on a PD-ADC system driving a multichannel scale counter


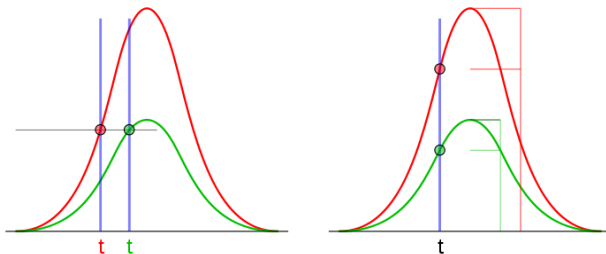
# Discriminator

- Often pulses occur with different amplitude and mostly the same shape
- Threshold comparators undergo time-walk errors
- Constant Fraction Discriminator (CFD) allow accurate timing






# Constant Fraction Discriminator
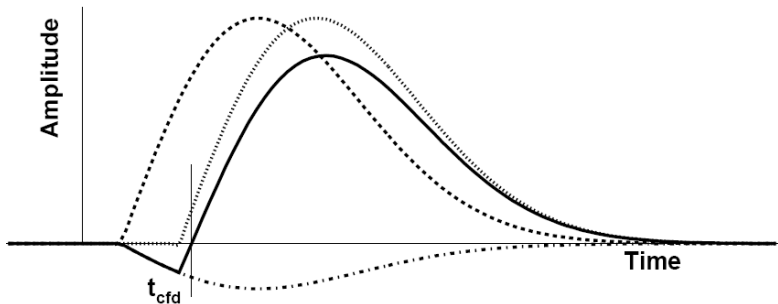
## Working principle


- split the input in two
- attenuate one
- delay the other
- feed them to a comparator
- the output triggers at a constant fraction of the peak height
  - e.g. 15% for peak rising-edge linearity in scintillator



# Constant Fraction Discriminator
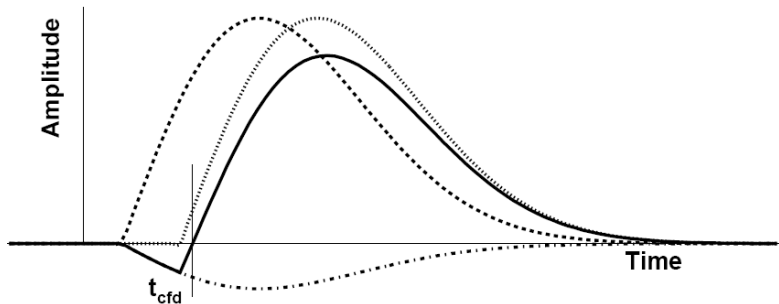
## Working principle


- split the input in two
- attenuate one
- delay the other
- feed them to a comparator
- the output triggers at a constant fraction of the peak height
  - e.g. 15% for peak rising-edge linearity in scintillator



# Constant Fraction Discriminator
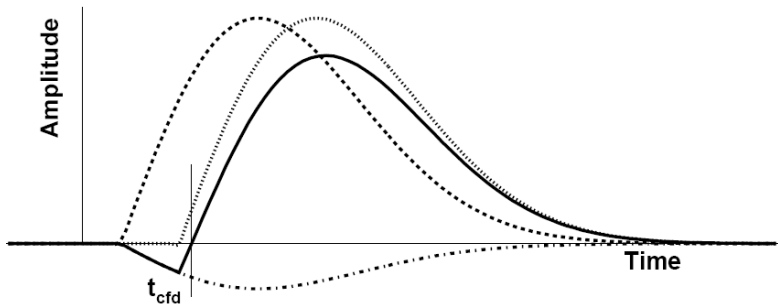
## Working principle


- split the input in two
- attenuate one
- delay the other
- feed them to a comparator
- the output triggers at a constant fraction of the peak height
  - e.g. 15% for peak rising-edge linearity in scintillator



# Constant Fraction Discriminator
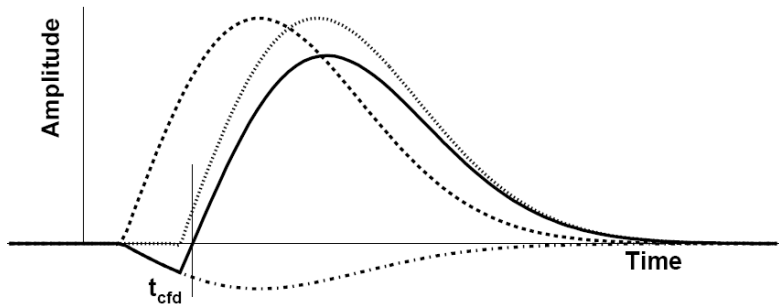
## Working principle


- split the input in two
- attenuate one
- delay the other
- feed them to a comparator
- the output triggers at a constant fraction of the peak height
  - e.g. 15% for peak rising-edge linearity in scintillator



# Constant Fraction Discriminator
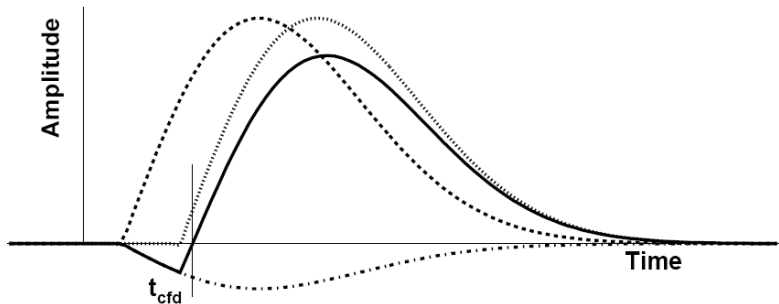
## Working principle


- split the input in two
- attenuate one
- delay the other
- feed them to a comparator
- the output triggers at a constant fraction of the peak height
  - e.g. 15% for peak rising-edge linearity in scintillator



# Constant Fraction Discriminator
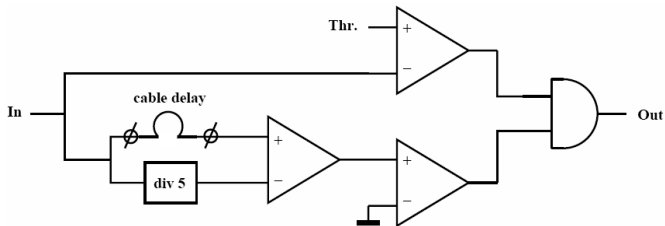
## Refined operation

- when the input is steady the two replicas are at the same level
- the comparator output fluctuates between the high and low logic levels
  - on average it should be midway - useful for calibration
- output enabled by a parallel threshold discriminator in proper conditions



# Time Measurement



Main functional circuits for time measurement:


- Time to Amplitude Converter (TAC)
- Time to Digital Converter (TDC)
- Mean Timer



# Time to Amplitude Converter
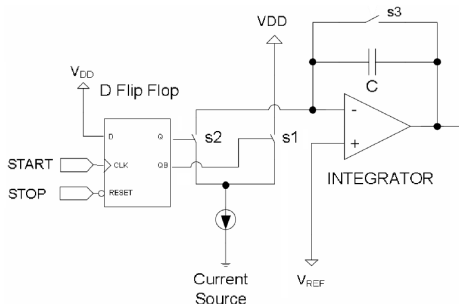
## Working principle

- a capacitor is charged at constant current between start and stop edges
- the resulting voltage is proportional to the start-stop interval
- TAC interpolates time between a pulse and a suitable clock edges
- high precision timing with respect to clock edges





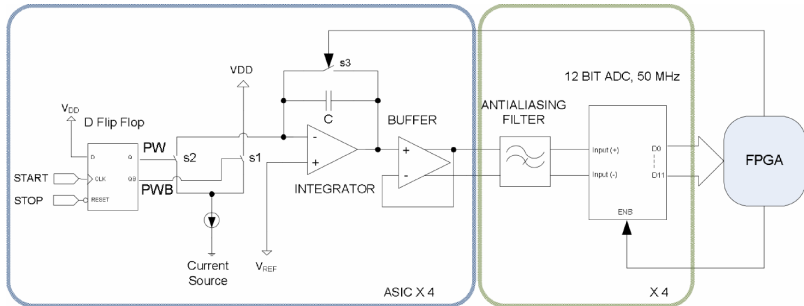
# Time to Digital Converter




- A TDC is simply made by coupling a TAC with an ADC


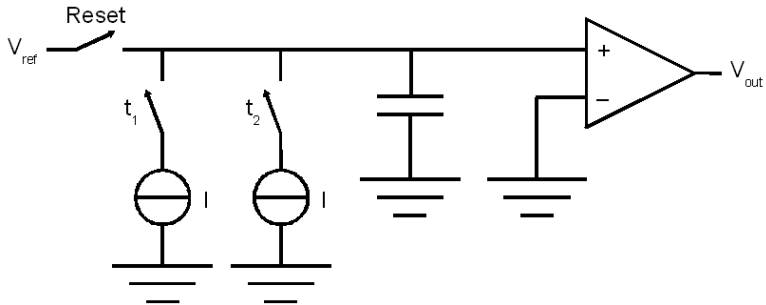
# Mean Timer



- Capacitor  $C$  is pre-charged at  $V_{ref}$
- each pulse starts a current generator at times  $t_1$  and  $t_2$
- the generators sink a charge  $I\Delta t$  from  $C$  till the comparator fires



# Mean Time

$V_C = 0 \rightarrow \Delta V = V_{ref}$  when the comparator fires

$$\Delta t_1 = t - t_1 \quad \Delta t_2 = t - t_2$$

$$\begin{aligned} -C\Delta V &= I\Delta t_1 + I\Delta t_2 \\ &= I(t - t_1 + t - t_2) \\ &= I(2t - (t_1 + t_2)) \end{aligned}$$

$$-\frac{C\Delta V}{I} = 2t - t_1 - t_2$$

- the output is fired at a time  $t$  given by the mean time of  $t_1$  and  $t_2$  plus a constant delay


$$t = \frac{t_1 + t_2}{2} + \frac{C|\Delta V|}{2I}$$



# Detector Examples



## • TOF-wall element

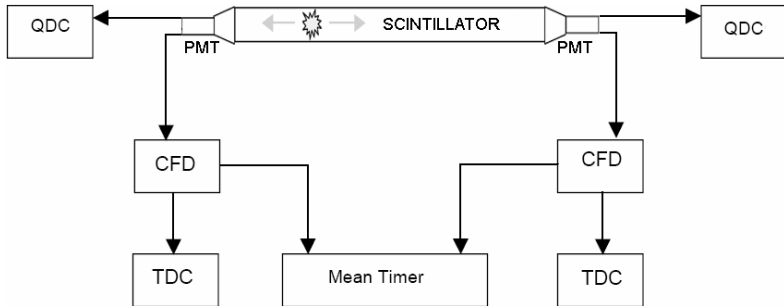

# Conclusions



## Radiation Physycs front-end electronics

- highly demanding requirements of fast analog processing
- most solutions are as simple as possible but smart!
- a number of functional blocks available for several detector types
- the ultimate speed performance limits are technology related (e.g. CMOS, parassitic elements, ...)
- what comes next to front-ends: a Huge data trasmission and processing task!



# THE END



Thanks for your attention

