



Power supply per Fisica delle Alte Energie: problematiche e soluzioni innovative

**B.Allongue¹, G.Blanchot¹, S.Busso², F.Faccio¹, C.Fuentes^{1,3},
P.Mattavelli², S.Michelis^{1,4}, S.Orlandi¹, G.Spiazzi²**

¹CERN - PH-ESE

²Dept. Information Engineering, Padova University, Italy

³UTFSM, Valparaiso, Chile

⁴EPFL, Lausanne



Outline




- Present power distribution architectures at LHC experiments
- Expected power supply requirements for the future LHC upgrade
- Serial powering
- Parallel powering: DC-DC converters based solution
 - DC-DC converter topologies for Point of Load (POL) converters
- Conclusions



Present Power Distribution Schemes in Trackers (ATLAS)



 Typical low-voltage power distribution in LHC trackers:
No on-detector conversion. Low-voltage (2.5-5V) required by electronics provided directly from off-detector. Sense wire necessary for PS to provide correct voltage to electronics. Cables get thinner when approaching the collision point (strict material budget).



In view of SLHC:


-Scheme not easily scalable to the larger currents expected (see next slides)



Present Power Distribution Schemes in Trackers (ATLAS)





 1A/channel (analog or digital), round-trip cables, and sense to nearest regulation





Example: LAr Calorimeter Power Supply

  




Example: LAr Calorimeter Power Supply



Total power: 3 kW

 

Output voltages:

$$V_{\text{out1}} = +6\text{V} - 100\text{A}$$

$$V_{\text{out2}} = +11\text{V} - 20\text{A}$$

$$V_{\text{out3}} = +7\text{V} - 160\text{A}$$

$$V_{\text{out4}} = +6\text{V} - 150\text{A}$$

$$V_{\text{out5}} = +4\text{V} - 130\text{A}$$


$$V_{\text{out6}} = -4\text{V} - 180\text{A}$$

$$V_{\text{out7}} = +7\text{V} - 15\text{A}$$

Low Drop-Out (LDO) regulators
on board



Example: CMS Power Supply Architectures

 


Source: S. Lusin, TWEPP '07



Why independent powering fails at SLHC ?



 - Don't get 5 or 10 times more cables in
- Power efficiency is too low (50% ATLAS SCT \Leftrightarrow ~15% SLHC)
- Cable material budget
- Packaging constraints



Source: M. Weber, TWEPP '07




Example: ATLAS Tracker



All ASICs will be manufactured in an advanced CMOS (or BiCMOS) process, 130nm generation or below. Here we consider only CMOS ASICs.

Detector module

 

Front-End readout ASIC

- $I_{\text{digital}} \geq I_{\text{analog}}$ (for instance, current projection for ATLAS Short Strip readout is $I_{\text{analog}} \sim 20\text{mA}$, $I_{\text{digital}} \sim 60\text{-}100\text{mA}$)
- 2 power domains: $V_{\text{an}}=1.2\text{V}$, $V_{\text{dig}}=0.9\text{-}0.8\text{V}$ (as low as possible)
- Clock gating might be used \Rightarrow switching load

Hybrid/Module controller

- Ensures communication (data, timing, trigger, etc.)
- Digital functions only
- It might require I/Os at 2.5V

Rod/stave



Other than the **rod/stave controller**, **optoelectronics components** will also have to be used, requiring an additional power domain (2.5-3V)

Source: S. Michelis, TWEPP '07



Example: ATLAS Tracker

Summary

- 3 Voltages to be provided to minimize power consumption:
 - 2.5V for optoelectronics and (maybe) control/communication ASICs
 - 1.2V for analog circuitry in FE ASICs
 - 0.8-0.9V for digital circuitry in FE ASICs. This domain uses most of the current!
- Digital current might be switching in time (to really minimize the power)

Power and Current in LHC/SLHC

- Projection based on current estimate for ATLAS upgrade
- Only accounting barrel detector, power from Readout ASICs only
- SCT is LHC ATLAS Silicon Tracker detector, to be replaced (grossly) by Short Strip layers in present upgrade layout

	N of layers	Min and Max R (cm)	Barrel length (cm)	N of chips	N of hybrids	Active power (KW)	Load current (KA)
SCT barrel	4	30, 51	153	25,000	2100	11.6	2.75 (@3.5-4V)
SLHC SS layers, barrel	3	38, 60	200	173,000	8600	16.2 (@0.9-1.2V) 20.3 (@1.2V)	17.2 (@0.9-1.2V)

Large waste of power
if $V_{an} = V_{dig} = 1.2V$

Large current increase
(Power on cables = RI^2)

Source: S. Michelis, TWEPP '07



Working Environment



- **High magnetic field** (up to 4T in CMS, 2T in ATLAS)
- **High level of radiation** inside the detectors:
 - LHC doses probably increased $\times 5 - 10$ so we can extrapolate to hundreds of Mrad in several Tracker location, decreasing to ten(s) in the outer Trackers



Power Distribution Schemes




- Serial Powering (SP)
 - Shunt regulators
- Parallel Powering (PP)
 - Inductor-based switching converters
 - Switched capacitor converters




Serial Powering



Powering schemes comparison

 
 
$$\text{Efficiency} := \eta := \frac{P_M}{P_M + P_C} = \frac{1}{1 + \frac{I_m R_c}{n V_m}} = \frac{1}{1 + \frac{x}{n}}$$




Example of efficiency plot vs. number of modules (n) and supply voltage (V) for $I_m = 2 \text{ A}$ $R_c = 3 \Omega$ for Serial Powering scheme

Source: G. Villani, TWEPP '07



Shunt Regulation in SP

 External shunt regulator + external power transistor




Source: G. Villani, TWEPP '07



Parallel Powering




Example of LAr calorimeter power supply

 

niPOL = Non-Isolated Point of Load Converters



Reduction of Cable Power Losses

 


Solution without converter: ↓ Power losses on cable = RI^2

Solution with converter: ↑ Power losses on cable = $R\left(\frac{I}{N}\right)^2 = \frac{RI^2}{N^2}$



 Proposed Power Distribution Scheme for ATLAS Trackers



Conversion stage 1 (ratio 4-5.5)

- Vin=10V => high-V technology
- Same ASIC development for analog and digital




Conversion stage 2 (ratio 2)

- Embedded in controller or readout ASIC
- Closely same converter for analog and digital (different current, hence different size of switching transistors): macros (IP blocks) in same technology



Implementation Example

 



Power supply for ATLAS Trackers



- The high magnetic field calls for coreless conversion stages
- Low-value air core inductors can be used with switching frequencies in the megahertz region
- Inductor-less conversion stages can also be used (switched capacitor converters)
- Switching noise is a big concern



Soft-switching is a must!




Different Converter Topologies (1/3)



 
1. Single phase synchronous buck converter

- ↑ Simple, small number of passive components
- ↓ Larger output ripple for same C_o
- ↓ RMS current limitation for inductor and output capacitance



 2. 4 phase interleaved synchronous buck converter

- ↑ Complete cancellation of output ripple for a conversion ratio of 4 (with small C_o)
- ↑ Smaller current in each inductor (compatible with available commercial inductors)
- ↓ Large number of passive components
- ↓ More complex control circuitry






Different Converter Topologies (2/3)



 
3. Two phase interleaved synchronous buck converter with integral voltage divider

- ↑ Complete cancellation of output ripple for a conversion ration of 4 (with small C_o)
- ↑ Simpler control and smaller number of passive components than 4 phase interleaved
- ↓ More components than the single-phase synchronous buck



 4. Multi-resonant buck converter

- ↑ Very small switching losses (zero voltage and zero current switching)
- ↓ To achieve resonance:
 - Current waveforms have high RMS value => large conduction losses => lower efficiency
 - Voltage waveforms have high peaks, possibly stressing the technology beyond max V_{dd}
- ↓ Different loads require complete re-tuning of converter parameters






Different Converter Topologies (3/3)



 5. switched capacitor voltage divider

- ↑ rather simple, limited number of passive components
- ↑ lack of inductor => good for radiated noise and for compact design
- ↓ No regulation of the output voltage, only integer division of the input voltage
- ↓ Efficiency decreases with conversion ratio (larger number of switches)
- ↑ Good solution for ratio = 2, for which high efficiency can be achieved







Single-phase Synchronous Buck Converter



Principle of operation

  



The 2^o order $L-C_o$ filter removes the switching frequency harmonics, making the output voltage DC component dominant



Single-phase Synchronous Buck Converter



- Hp: constant voltages

  

Inductor flux balance:




$$\bar{u}_L = 0 \quad \Rightarrow \quad (U_g - U_o)D - U_o(1 - D) = 0 \quad \Rightarrow \quad M = \frac{U_o}{U_g} = D$$



Single-phase Synchronous Buck Converter




- Quasi-square wave operation

   

High current ripple



Multiphase Interleaved Buck Converters

 


$N =$ phase number

Same drive signal
but phase shifted
by T_{sw}/N


- Reduced current level per phase
- Reduced output current ripple
- Reduced input current ripple
- Increased bandwidth ($F_{eq} = N F_{sw}$)



Multi-Phase Interleaved Converters

 

Example:
2 phases

 


➡ Ripple reduction
on output filter



Output Current Ripple Cancellation




Two phases

 

Input voltage

$D=0.5$ for the best cancellation effect



Four phases

 

$D=0.25, 0.5, 0.75$ for the best cancellation effect



Multi-Phase Interleaved Converters

  

Ripple reduction on input current



Multi-resonant buck converter



Example:

Input voltage:

$$U_g = 12V$$

Output voltage:

$$U_o = 3V$$

Output current:

$$I_o = 3A$$

Switching frequency:

$$f_s = 6.4MHz$$

Resonant inductance:



$$L_r = 100nH$$

Switch capacitance:

$$C_s = 3nF$$


Diode capacitance:

$$C_D = 9nF$$

  



 Two-Phase Interleaved Buck with Voltage Divider







Two-Phase Interleaved Buck with Voltage Divider



$D < 0.5$


 


$D > 0.5$

 





  Two-Phase Interleaved Buck with Voltage Divider: $D < 0.5$







  Two-Phase Interleaved Buck with Voltage Divider: $D < 0.5$







  Two-Phase Interleaved Buck with Voltage Divider: $D < 0.5$





  Two-Phase Interleaved Buck with Voltage Divider: $D < 0.5$





Steady-state analysis ($D < 0.5$)



- Inductor flux balance:

$$\bar{u}_{L1} = 0 \quad \Rightarrow \quad (U_{C1} - U_o)D - U_o(1-D) = 0 \quad \Rightarrow \quad U_{C1}D = U_o$$

$$\bar{u}_{L2} = 0 \quad \Rightarrow \quad (-U_{C1} + U_{in} - U_o)D - U_o(1-D) = 0 \quad \Rightarrow \quad (U_{in} - U_{C1})D = U_o$$

$$M = \frac{U_o}{U_{in}} = \frac{D}{2} \qquad \frac{U_{C1}}{U_{in}} = \frac{1}{2}$$

- Capacitor charge balance:

$$I_2D - I_1D = 0 \quad \Rightarrow \quad I_2 = I_1 \quad \Rightarrow \quad I_2 + I_1 = I_o \quad \Rightarrow \quad I_1 = I_2 = \frac{I_o}{2}$$



Two-Phase Interleaved Buck with Voltage Divider: $D < 0.5$



- “Natural” current sharing
- Optimal ripple cancellation for overall voltage conversion ratio equal to $\frac{1}{4}$
- Reduced switch voltage stress (one half of input voltage)



Two-Phase Interleaved Buck with Voltage Divider: $D > 0.5$



$$M = \frac{U_o}{U_g} = D^2 \quad \frac{U_{C1}}{U_g} = 1 - D$$



- Unequal average currents in the two phases
- Increased switch voltage stress (equal to the input voltage)



Two-Phase Interleaved Buck with Voltage Divider: $D < 0.5$



$D=0.37$

 
 




Two-Phase Interleaved Buck with Voltage Divider: $D > 0.5$



$D=0.63$

  





Switched-Capacitor Voltage Divider




Topology corresponding to

  $Q_1, Q_3 = \text{"on"};$
 $Q_2, Q_4 = \text{"off"}$



Topology corresponding to

 $Q_2, Q_4 = \text{"on"};$
 $Q_1, Q_3 = \text{"off"}$



$$R = 2R_{D\text{Son}} + R_{\text{ESR}x}$$



$$C_1 = C_2 = C$$



SCVD: Steady-State Analysis



  - Input voltage: $V_g = 3V$
- Output current: $I_o = 0.1A$
- Switching frequency: $f_s = 200kHz$
- MOSFET on resistance: $R_{DSon} = 100m\Omega$
- Filter capacitors: $C = 200nF$
- Charge transfer capacitor: $C_x = 10\mu F$






SCVD: Steady-State Analysis



 Converter efficiency as a function of output current total parasitic resistance $R = 2 \times R_{DSon}$ for four different output current values: $I_o = 0.1$ A (red curve); $I_o = 0.2$ A (blue curve); $I_o = 0.3$ A (green curve); $I_o = 0.4$ A (magenta curve) ($C = 200$ nF, $C_x = 10$ μ F)





2PIB-VD: Experimental Results at $f_s = 1\text{MHz}$



Input voltage: $U_g = 12\text{ V}$
Output voltage: $U_o = 2.5\text{ V}$
Nominal output power: $P_o = 7.5\text{ W}$
Nominal output current: $I_o = 3\text{ A}$



$C_{in} = 100\text{nF} + 10\mu\text{F}$	$C_o = 2 \times 47\text{nF} + 4 \times 2.2\ \mu\text{F}$	$C_1 = 2 \times 220\text{nF} (1206)$
$L_1 = 353\text{nH} - 90\text{m}\Omega$	$L_2 = 342\text{nH} - 86\text{m}\Omega$	$S_{1,4} = \text{IRF8915}$



2PIB-VD: Experimental Results at $f_s = 1\text{MHz}$



  Converter's main waveforms at nominal power: S_3 logical driving signal (Blue); output voltage ripple (yellow); S_3 Drain-to-Source voltage (red)





Single Buck Converter: Experimental Results at $f_s = 1\text{MHz}$



Input voltage: $U_g = 12\text{ V}$
Output voltage: $U_o = 2.5\text{ V}$
Nominal output power: $P_o = 7.5\text{ W}$
Nominal output current: $I_o = 3\text{ A}$

$C_{in} = 100\text{nF} + 10\mu\text{F}$	$C_o = 2 \times 47\text{nF} + 2 \times 47\mu\text{F} + 2 \times 10\mu\text{F}$
$L = 222\text{nH} - 64\text{m}\Omega$ (12L Coilcraft)	$Q_{1,2} = 2 \times \text{IRF8915}$

Lower Inductance
value

Parallel-connected
switches




Single Buck Converter: Experimental Results at $f_s = 1\text{MHz}$




Quasi-square wave operation

 Converter's main waveforms at nominal power: S_1 logical driving signal (Blue); output voltage ripple (yellow); S_3 Drain-to-Source voltage (red)





 Efficiency Comparison at $f_s = 1\text{MHz}$



Home-made L: 0.84mm wire diameter ($L = 220\text{nH}$, $50\text{m}\Omega$) wound on a plastic support ($\phi = 4.38\text{mm}$)



Experimental Results at $f_s = 2\text{MHz}$



2PIB-VD


$C_{in} = 100\text{nF} + 10\mu\text{F}$	$C_o = 2 \times 47\text{nF} + 4 \times 2.2\ \mu\text{F}$	$C_1 = 2 \times 470\text{nF}$ (1206)
$L_1 = 161\text{nH} - 58\text{m}\Omega$	$L_2 = 169\text{nH} - 63\text{m}\Omega$	$S_{1,4} = \text{IRF8915}$

Single buck

$C_{in} = 100\text{nF} + 10\mu\text{F}$	$C_o = 2 \times 47\text{nF} + 2 \times 47\mu\text{F} + 2 \times 10\mu\text{F}$
$L = 90\text{nH} - 30\text{m}\Omega$	$Q_{1,2} = 2 \times \text{IRF8915}$



 Efficiency Comparison @ $f_s = 2\text{MHz}$





Conclusions



Summary

- The present power supply architecture at LHC will no longer be sustainable in the future upgrades
- Distributed power supply architectures based on DC-DC converters are proposed
- High step-down ratio topologies are the key for increasing power distribution with the same cabling
- High conversion efficiency as well as low switching noise are mandatory

Future investigations

- Radiation tolerance components and technologies must be selected
- More intensive investigations on switching noise effects must be carried out