

# Modeling of JPA


*S. Pagano (+ collaborators in Salerno)*

*Dip. Fisica Univ. Salerno*

*INFN G.C. Salerno*

Aim: modelling of a JPA without simplifications of the nonlinear components

## Model by Claudio Gatti

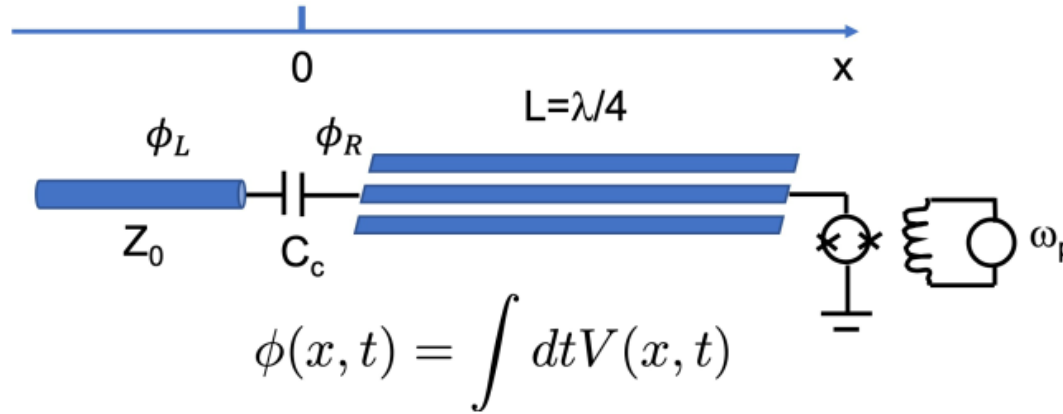

The Lagrangian density of the circuit in figure 1 is obtained by the sum of the capacitive energies minus the inductive energies:

$$\begin{aligned} \mathcal{L} = & \left( \frac{1}{2} C_L \dot{\phi}_L^2 - \frac{1}{2L_L} \phi_L'^2 \right) \sigma(-x) + \left( \frac{1}{2} C_R \dot{\phi}_R^2 - \frac{1}{2L_R} \phi_R'^2 \right) [\sigma(x) - \sigma(x - L)] \\ & + \left( \frac{1}{2} C_c (\dot{\phi}_L - \dot{\phi}_R) \right) \delta(x) + \left[ \frac{C_J}{2} \dot{\phi}_J^2 + E_J(\phi_{ext}) \cos \left( 2\pi \frac{\phi_J}{\phi_0} \right) \right] \delta(x - L) \end{aligned} \quad (1)$$

where  $\phi_{L,R}(x)$  is the flux variable defined as  $\phi(x) = \int^t dt' V(t')$  in the left (right) transmission line and  $C_{L,R}$  and  $L_{L,R}$  are their capacitances and inductances per unit length, and  $\phi_J = \phi_R(x = L)$ .  $\sigma(x)$  is the Heaviside (step) function. The (symmetric) SQUID Josephson energy is:

$$E_J(\phi_{ext}) = 2E_{0J} \cos \left( \pi \frac{\phi_{ext}}{\phi_0} \right) \quad (2)$$

where  $E_{0J}$  is the Josephson energy of the single junction.

## Wave equations for $\phi_L$ and $\phi_R$

$$\begin{aligned} \sigma(-x) \left[ C_L \ddot{\phi}_L - \frac{1}{L_L} \phi_L'' \right] + \delta(x) \left[ C_c (\ddot{\phi}_L - \ddot{\phi}_R) + \frac{1}{L_L} \phi_L' \right] &= 0(4) \\ [\sigma(x) - \sigma(x-L)] \left[ C_R \ddot{\phi}_R - \frac{1}{L_R} \phi_R'' \right] + \delta(x) \left[ -C_c (\ddot{\phi}_L - \ddot{\phi}_R) - \frac{1}{L_R} \phi_R' \right] + \\ \delta(x-L) \left[ C_J \ddot{\phi}_R + \frac{1}{L_R} \phi_R' + \frac{2\pi}{\phi_0} E_J(\phi_{ext}) \sin \left( 2\pi \frac{\phi_R}{\phi_0} \right) \right] &= 0 \end{aligned}$$

The solution is the sum of an outgoing and an incoming wave

$\phi(x, t) = \phi^{in}(t - x/v_p) + \phi^{out}(t + x/v_p)$  and  $v_p = 1/\sqrt{LC}$ . The other equations give the boundary conditions:

$$\begin{aligned} -\frac{1}{L_L} \phi_L' &= C_c (\ddot{\phi}_L - \ddot{\phi}_R) & (x=0) \\ -\frac{1}{L_R} \phi_R' &= C_c (\ddot{\phi}_L - \ddot{\phi}_R) & (x=0) \\ C_J \ddot{\phi}_R + \frac{1}{L_R} \phi_R' + \frac{2\pi}{\phi_0} E_J(\phi_{ext}) \sin \left( 2\pi \frac{\phi_R}{\phi_0} \right) &= 0 & (x=L) \end{aligned}$$

$\phi' = \frac{1}{v_p} (\dot{\phi}^{out} - \dot{\phi}^{in})$  *in and out fields.*

$\dot{\phi} = \dot{\phi}^{in} + \dot{\phi}^{out}$

$$2\ddot{\phi}_R^{in} + \frac{1}{CcZ_0} \dot{\phi}_R^{in} = \ddot{\phi}_L^{in} + \frac{1}{CcZ_0} \dot{\phi}_R^{out} \quad (x=0)$$

$$C_J \ddot{\phi}_J + \frac{1}{Z_0} \dot{\phi}_J + \frac{2\pi}{\phi_0} E_J(\phi_{ext}) \sin \left( 2\pi \frac{\phi_J}{\phi_0} \right) = \frac{2}{Z_0} \dot{\phi}_R^{in} \quad (x=L) \quad \phi_R^{in}(t, x=L) = \phi_R^{in}(t-L/v_p, x=0)$$


$$\begin{aligned} \phi_R^{out}(t, x=L) &= \phi_R^{out}(t+L/v_p, x=0) = \phi_J(t) - \phi_R^{in}(t, x=L) \\ &= \phi_J(t) - \phi_R^{in}(t-L/v_p, x=0) \end{aligned}$$

$$\phi_L^{out} = \phi_R^{out} - \phi_R^{in} + \phi_L^{in} \quad (x=0)$$

# Transient Analysis of Lossless Transmission Lines

Manuscript received July 7, 1967; revised September 8, 1967.

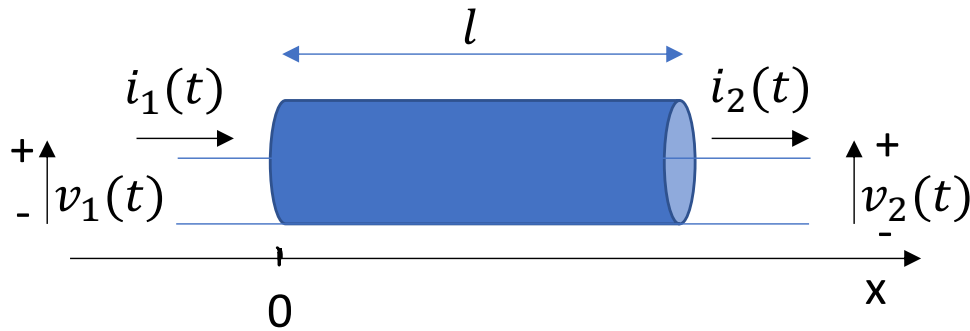F. H. BRANIN, JR.  
Systems Development Div. Lab.  
IBM Corporation  
Kingston, N. Y.



$$\tau = \sqrt{LC} \text{ } l \text{ line delay}$$

$$Z_0 = \sqrt{\frac{L}{C}} \text{ line impedance}$$

$$\Delta e = +Z_0 \Delta i \quad \Delta e = -Z_0 \Delta i$$

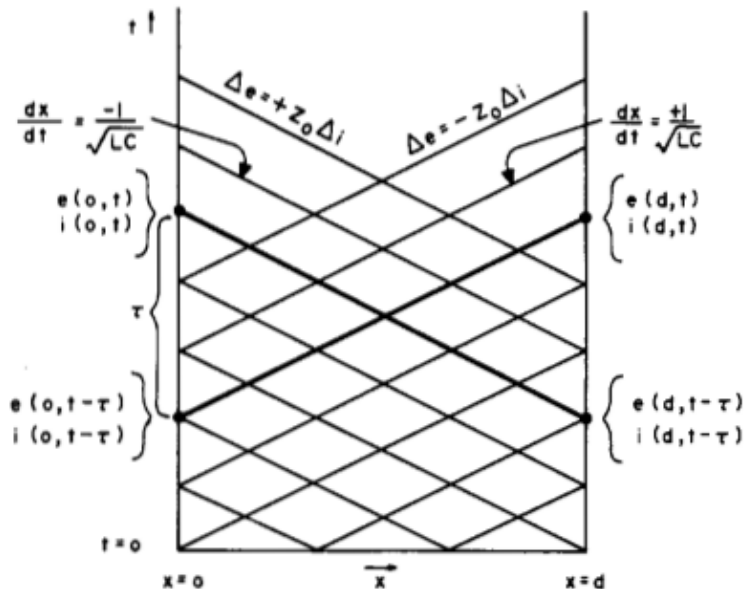


Fig. 1. Characteristic curves for a uniform transmission line.

$$v = v(x, t) \quad i = i(x, t)$$

$$\begin{aligned} L \frac{\partial i}{\partial t} + \frac{\partial v}{\partial x} &= 0 \\ C \frac{\partial v}{\partial t} + \frac{\partial i}{\partial x} &= 0 \end{aligned} \quad \longrightarrow \quad \begin{aligned} i_{tt} - \frac{1}{LC} i_{xx} &= 0 \\ v_{tt} - \frac{1}{LC} v_{xx} &= 0 \end{aligned}$$

The method of characteristics for solving these equations is based on a transformation in the  $x-t$  plane which accomplishes the conversion of (1) and (2) into a pair of ordinary differential equations. Each of these two ordinary differential equations holds true along a different family of characteristic curves in the  $x-t$  plane, one family corresponding to the forward or incident wave and the other to the backward or reflected wave. These two families of characteristic curves are, in effect, the basis for a new coordinate system instead of the canonical coordinates  $x = \text{constant}$  and  $t = \text{constant}$ .

$$dx/dt = 1/\sqrt{LC} \quad \text{and} \quad dx/dt = -1/\sqrt{LC}$$

$$\sqrt{\frac{L}{C}} di + \left( Ri + \sqrt{\frac{L}{C}} Ge \right) dx + de = 0 \quad (3)$$

which holds true only along the *forward* characteristics, defined as  $dx/dt = 1/\sqrt{LC}$ , and



$$-\sqrt{\frac{L}{C}} di + \left( Ri - \sqrt{\frac{L}{C}} Ge \right) dx + de = 0 \quad (4)$$

which holds true only along the *backward* characteristics, defined as  $dx/dt = -1/\sqrt{LC}$ .

# Transient Analysis of Lossless Transmission Lines

Manuscript received July 7, 1967; revised September 8, 1967.

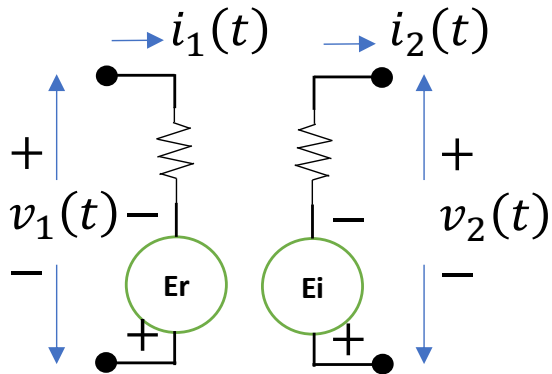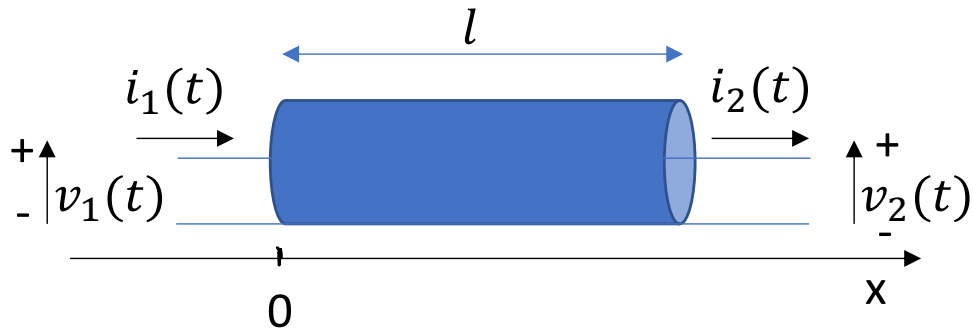F. H. BRANIN, JR.  
Systems Development Div. Lab.  
IBM Corporation  
Kingston, N. Y.



$$v = v(x, t) \quad i = i(x, t)$$

$$\tau = \sqrt{LC} l \text{ line delay}$$

$$Z_0 = \sqrt{\frac{L}{C}} \text{ line impedance}$$

$$v(l, t) = -Z_0 i(l, t) + [v(0, t - \tau) + Z_0 i(0, t - \tau)]$$

$$v(0, t) = +Z_0 i(0, t) + [v(l, t - \tau) - Z_0 i(l, t - \tau)]$$

$$v_2(t) = -Z_0 i_2(t) + [v_1(t - \tau) + Z_0 i_1(t - \tau)]$$




$$v_1(t) = +Z_0 i_1(t) + [v_2(t - \tau) - Z_0 i_2(t - \tau)]$$

$$v_2(t) = -Z_0 i_2(t) - E_i(t - \tau)$$

$$v_1(t) = +Z_0 i_1(t) - E_r(t - \tau)$$

$$E_i(t) = -[2v_1(t) + E_r(t - \tau)]$$

$$E_r(t) = -[2v_2(t) + E_i(t - \tau)]$$

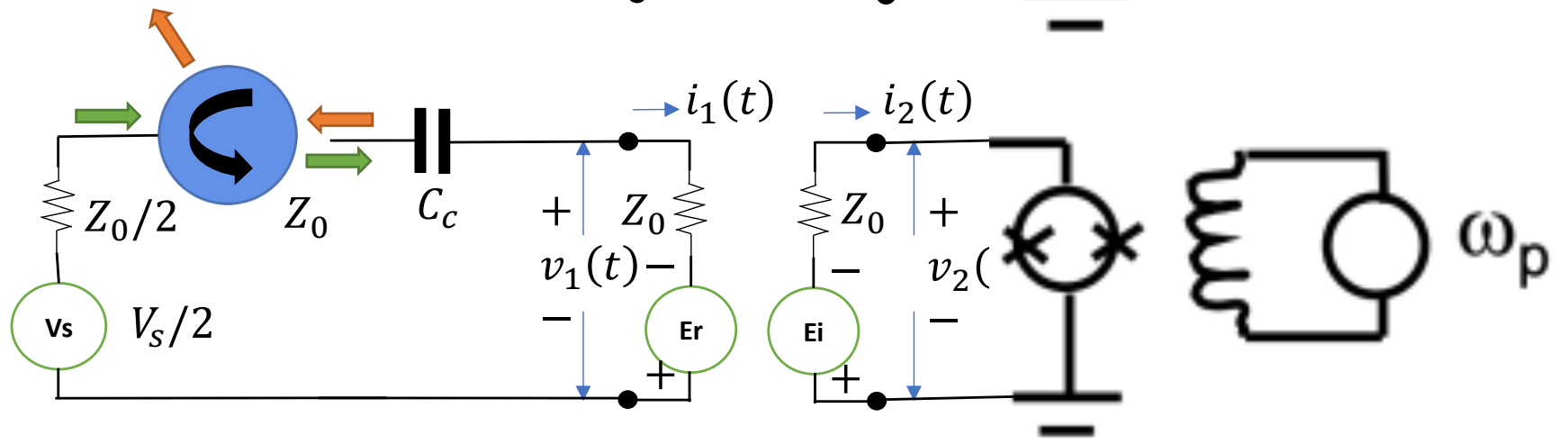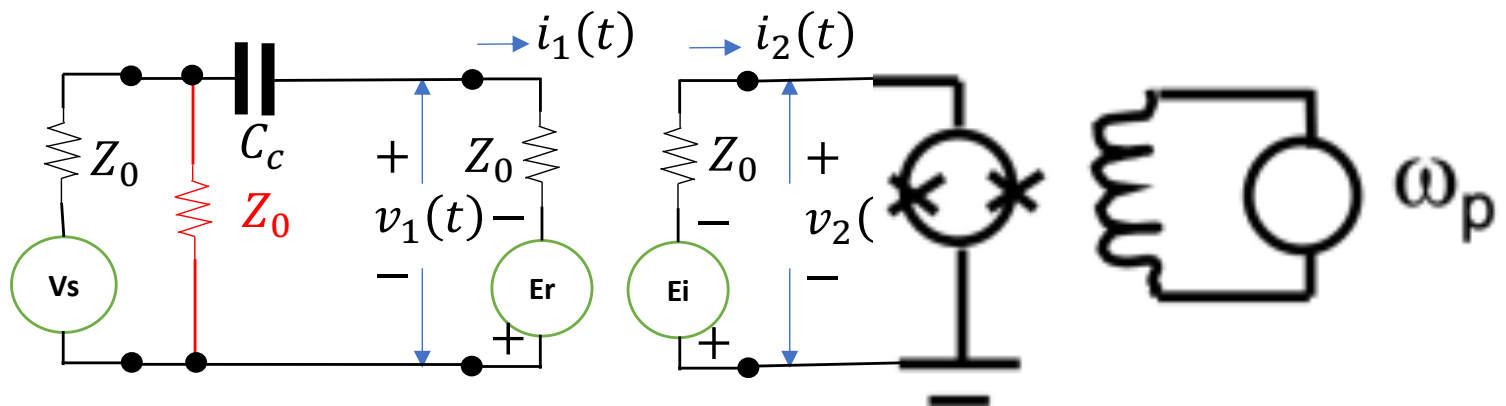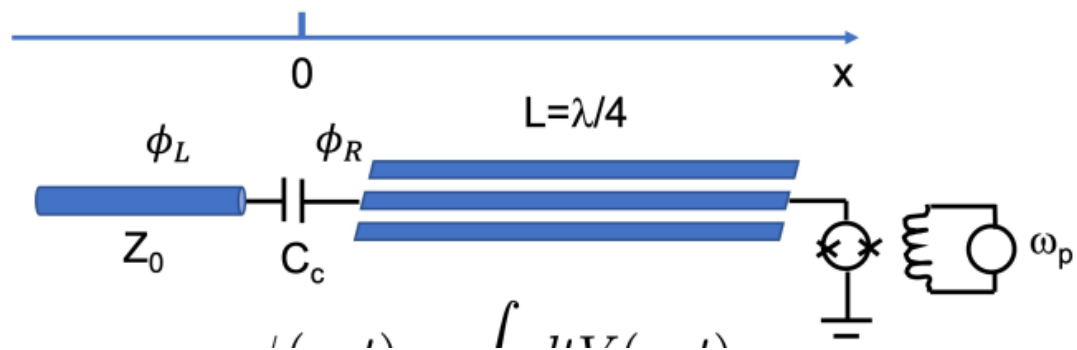

$$\dot{v}_1 = -\frac{1}{2 C_c Z_0} v_1 + \frac{1}{2} \dot{v}_a(t) - \frac{1}{2} \dot{E}_r(t - \tau) - \frac{1}{2 C_c Z_0} E_r(t - \tau)$$

$$\dot{v}_2 = -\left(\frac{1}{C_j Z_0} + \frac{1}{C_j R_j}\right) v_2 - \frac{I_j}{C_j} \cos\left(\pi \frac{\phi_{ext}}{\phi_0}\right) \sin \varphi - \frac{1}{C_j Z_0} E_i(t - \tau)$$

$$\dot{\varphi} = \frac{2e}{\hbar} v_2$$

where

$$v_s(t) = v_{rf} \sin \omega t$$

$$\dot{v}_s(t) = v_{rf} \omega \cos \omega t$$

$$\phi_{ext}(t) = \phi_{dc} + \phi_{ac} \cos \omega_p t$$

$$Z_0 = 50 \Omega; \quad \tau = \frac{T}{4} = \frac{\pi}{2 \omega_{ris}};$$

$I_j = 2I_{j0}$ ,  $C_j = 2C_{j0}$  and  $R_j = \frac{1}{2}R_{j0}$  are the SQUID critical current capacitance and resistance

We start with  $E_i$  and  $E_r$  set to zero

The values of  $E_i$  and  $E_r$  are updated during the integration according to:


$$E_i(t) = -[2v_1(t) + E_r(t - \tau)]$$

$$E_r(t) = -[2v_2(t) + E_i(t - \tau)]$$

For  $V_{out}$  we have to decide how to simulate the circulator:


Assuming that the reflected wave do not see the signal source, its component at the signal frequency will see an RC circuit
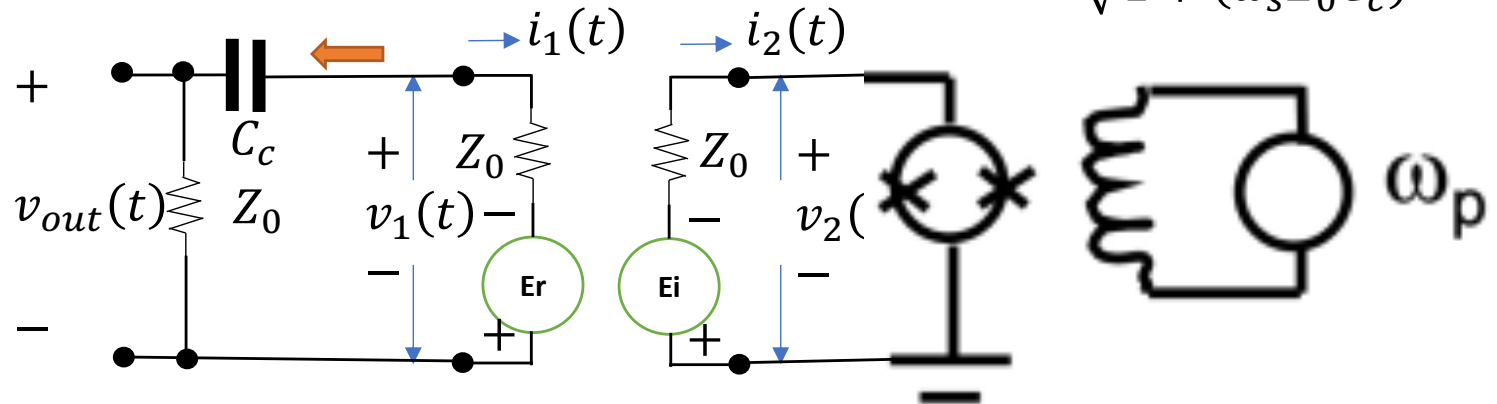
$$v_{out} = v_1 \frac{\omega_s Z_0 C_c}{\sqrt{1 + (\omega_s Z_0 C_c)^2}}$$



Alternatively, we can take the voltage at that the input of the coupling capacitor:

$$v_{out}(t) = V_s(t) - Z_0 i_1(t)$$

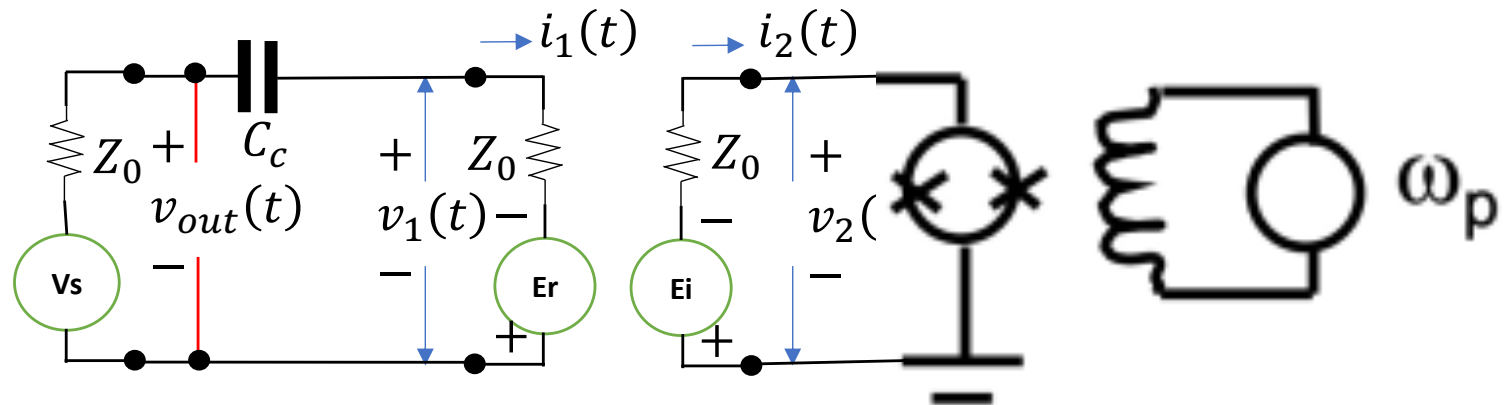



## Simulation results

As parameter values the experimental data from LNF are used:

Resonator Length 2.62mm

Substrate silicon  $\epsilon_{\text{eff}}=6.346$

Bare resonator frequency **11.3 GHz**

Impedance  **$Z_0=50 \text{ Ohm}$**

Coupling capacitor **14-18 fF**

$S=12 \text{ }\mu\text{m}$  e  $w=7 \text{ }\mu\text{m}$

SQUID Parameters:

Junction area 0.3-0.6  $\mu\text{m}^2$

Junction  **$I_c=0.47 \text{ }\mu\text{A}$**  (quella misurata)

Junction  **$C_j<0.5 \text{ pF}$**





Junction freq  $f_{jj} \gg 10 \text{ GHz}$

DC SQUID

Area 4x4  $\mu\text{m}^2$

$M=70 \text{ fH}$  (misurata)

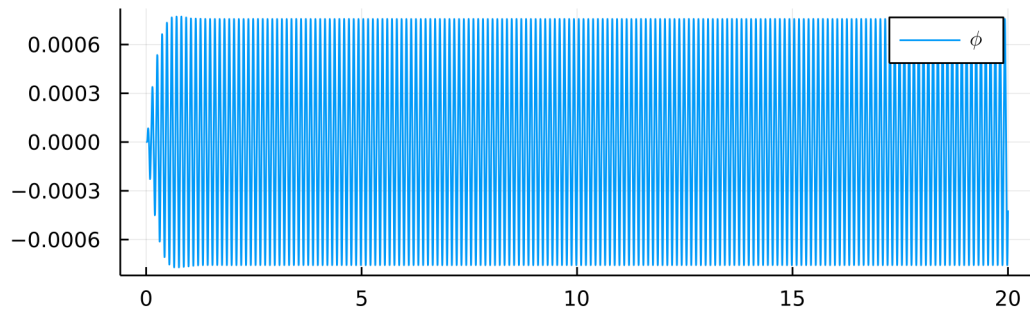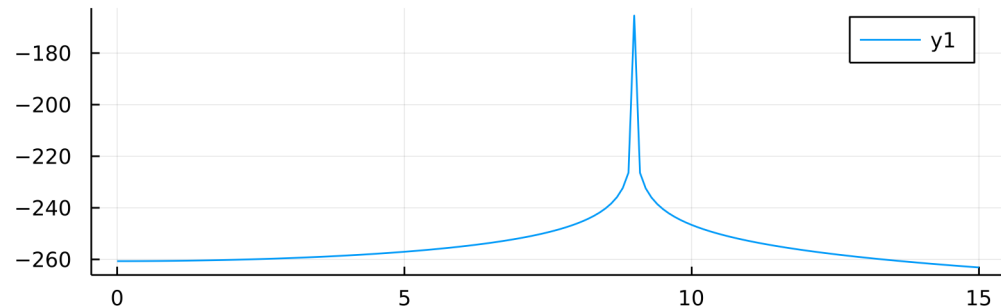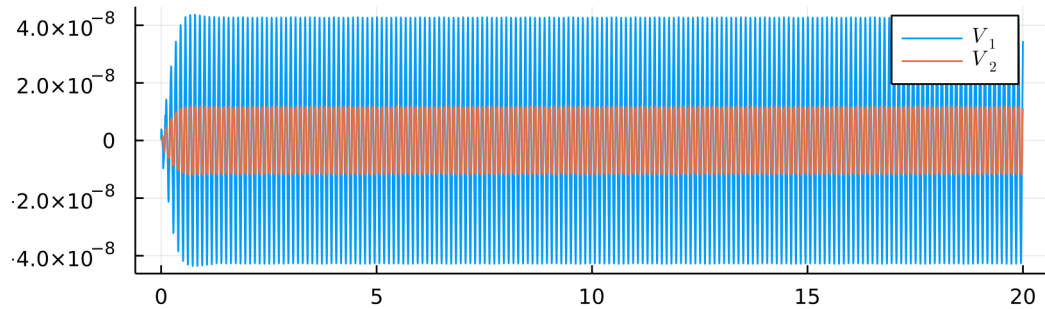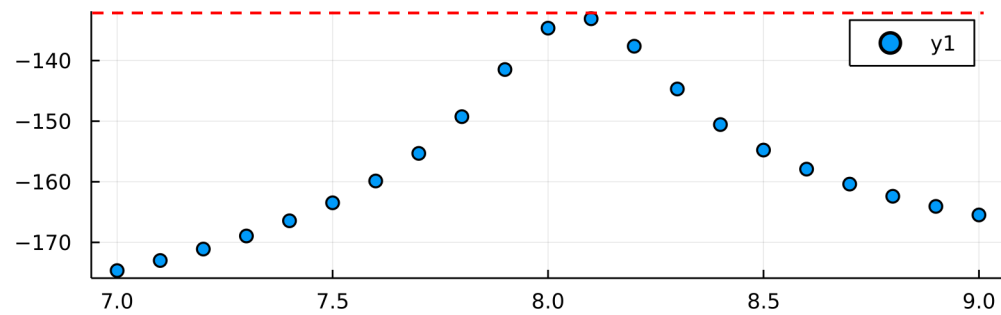The effects of the SQUID load depend strongly on the critical current



Scan of pump frequency with  $f_{\text{pump}} = 2 f_{\text{signal}}$

The effects of the SQUID load depend strongly on the critical current

A resonance occurs for  $f_{\text{signal}}$  near 8 GHz

$f_{\text{pump}} = 2 f_{\text{signal}}$

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   
 **$I_0 = 2.0 \text{ uA}$**   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$   
 $f_{\text{plasma}} = 110.24538380186623 \text{ GHz}$

$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.12 ps

input RF signal = 0.1 uV = -130.0 dBm



$f_{\text{start}} = 7.0 \text{ GHz}$   $f_{\text{end}} = 9.0 \text{ GHz}$   $f_{\text{step}} = 100.0 \text{ MHz}$

Magnetic flux amplitude **DC = 0.29**  $\Phi_0$  **RF = 0.15**  $\Phi_0$   
 $\Phi_0$  Frequency = 10.2 GHz

Integration time = 20.0 ns time step = 0.1 ps  
 integrating 200000 time steps with 221 lag steps

increase of dc flux bias

## Effect of dc flux bias

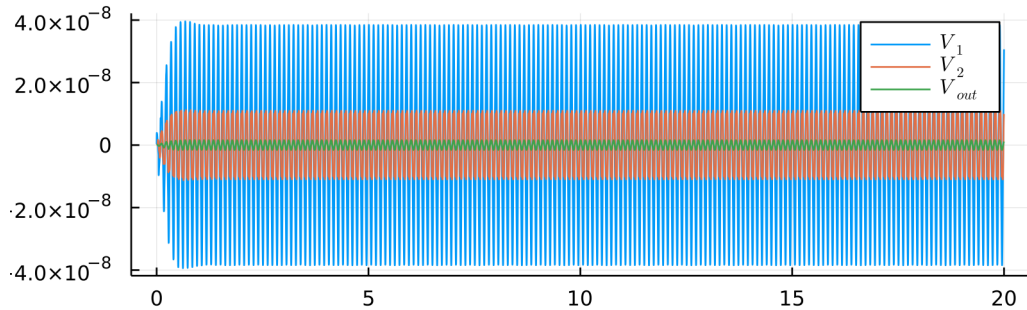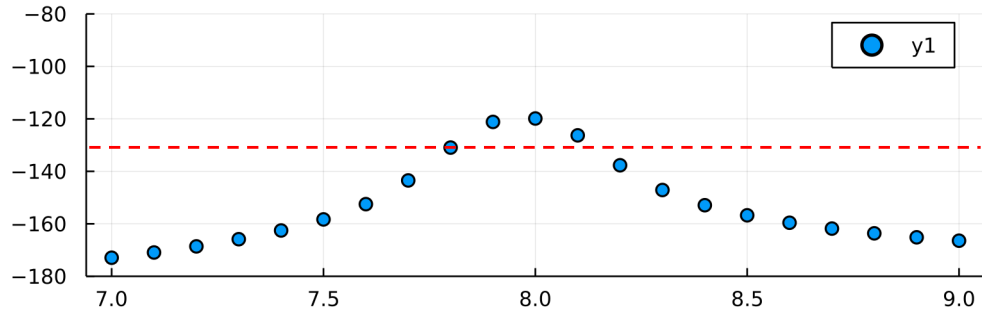

$f_{pump} = 2 f_{signal}$

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$

**$I_0 = 2.0 \text{ uA}$**   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$

$f_{plasma} = 110 \text{ GHz}$

$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.12 ps

input RF signal = 0.1 uV = -130.0 dBm



$f_{start} = 7.0 \text{ GHz}$   $f_{end} = 9.0 \text{ GHz}$   $f_{step} = 100.0 \text{ MHz}$

Magnetic flux amplitude **DC = 0.3  $\Phi_0$**  RF = 0.15  $\Phi_0$

Frequency = 10.2 GHz

Integration time = 20.0 ns time step = 0.1 ps

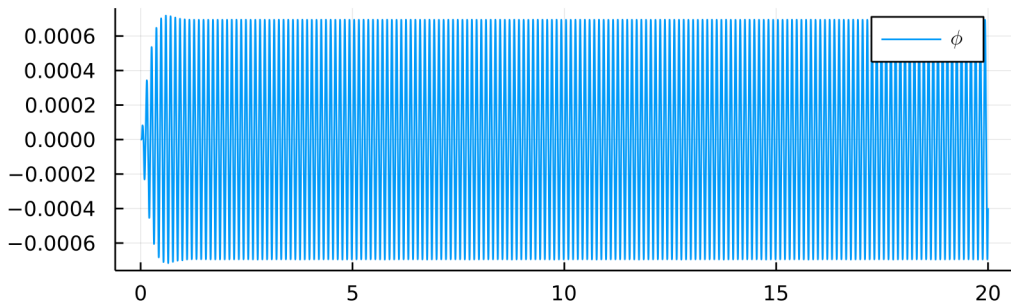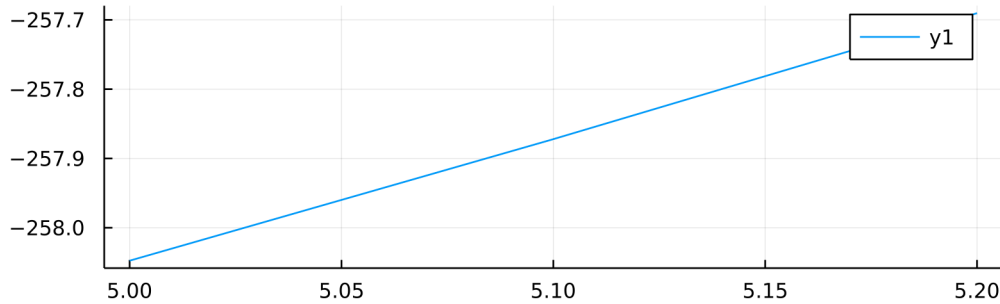integrating 200000 time steps with 221 lag steps



## Effect of dc flux bias

$I_c = 2 \mu\text{A}$

$f_{\text{pump}} = 2$   $f_{\text{signal}}$

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   
 $I_0 = 2.0 \mu\text{A}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$

$f_{\text{plasma}} = 110.24 \text{ GHz}$





$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.12 ps

input RF signal = 0.1  $\mu\text{V}$  = -130.0 dBm

$f_{\text{start}} = 7.0 \text{ GHz}$   $f_{\text{end}} = 9.0 \text{ GHz}$   $f_{\text{step}} = 100.0 \text{ MHz}$

Magnetic flux amplitude **DC** = 0.31  $\Phi_0$  RF = 0.15  $\Phi_0$   
Frequency = 10.2 GHz

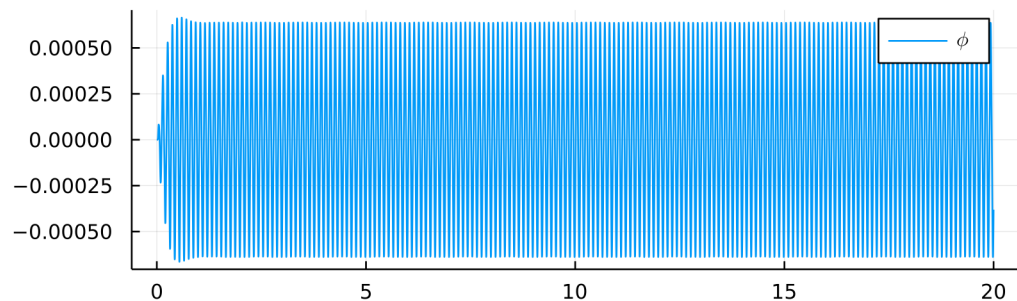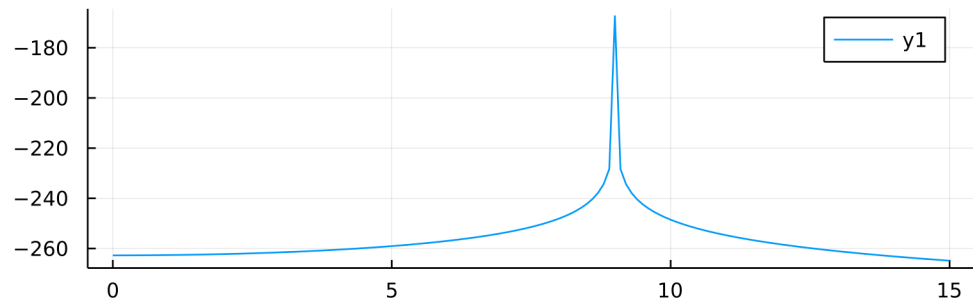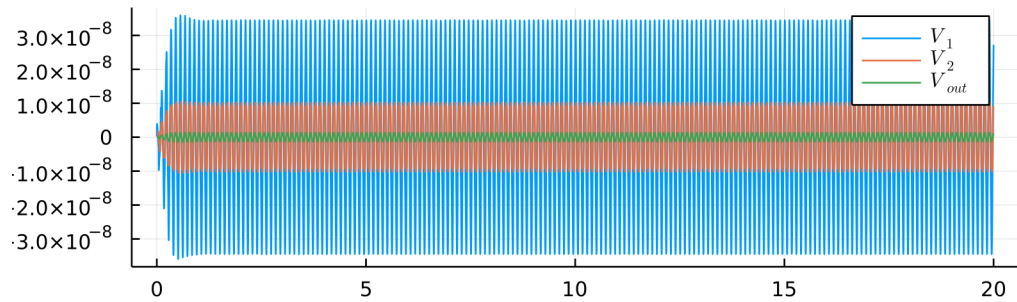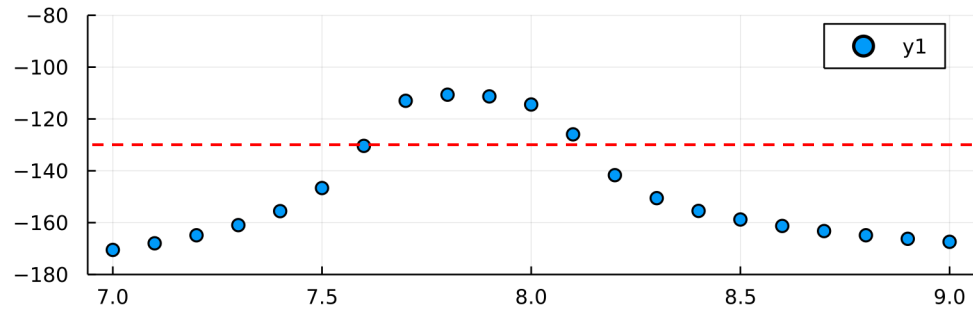Integration time = 20.0 ns time step = 0.1 ps  
integrating 200000 time steps with 221 lag steps



Now we reduce the SQUID critical current:  
 $I_c = 1 \mu\text{A}$

It is necessary more pump power

The resonance moves to lower frequency

$f_{\text{pump}} = 2 f_{\text{signal}}$

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   
 $I_0 = 1.0 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$   
 $f_{\text{plasma}} = 77.95 \text{ GHz}$





$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.12 ps

input RF signal = 0.1 uV = -130.0 dBm

$f_{\text{start}} = 5.0 \text{ GHz}$   $f_{\text{end}} = 7.0 \text{ GHz}$   $f_{\text{step}} = 100.0 \text{ MHz}$

Magnetic flux amplitude **DC = 0.33  $\Phi_{i0}$**  **RF = 0.25  $\Phi_{i0}$**   
Frequency = 10.2 GHz

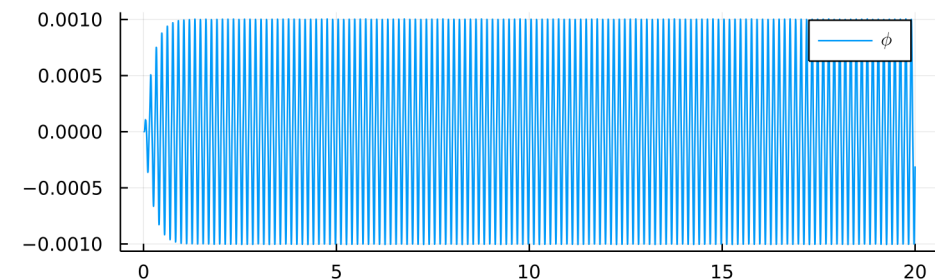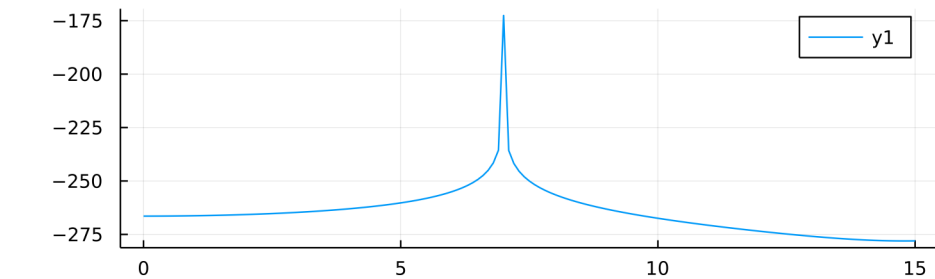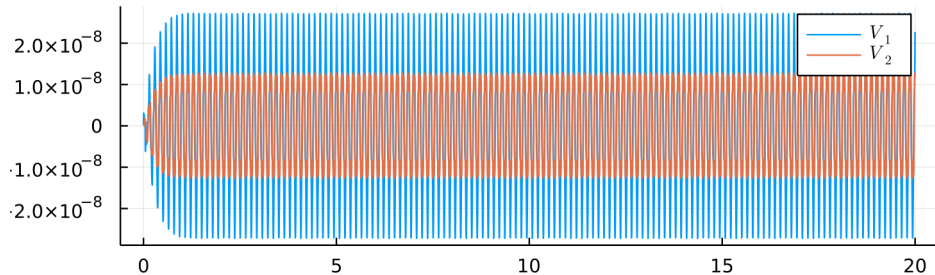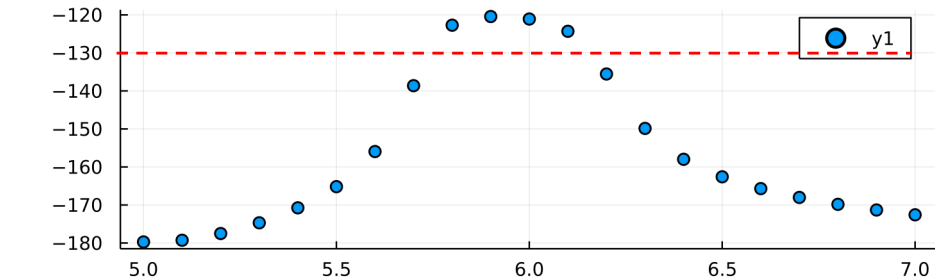Integration time = 20.0 ns time step = 0.1 ps  
integrating 200000 time steps with 221 lag steps



Reducing further the SQUID critical current:  
 $I_c = 0.5 \mu\text{A}$

More pump power is necessary

The resonance frequency is further reduced

$f_{\text{pump}} = 2 f_{\text{signal}}$

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   $I_0 = 0.5 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$

$f_{\text{plasma}} = 55.12 \text{ GHz}$

$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.12 ps





input RF signal = 0.1 uV = -130.0 dBm

$f_{\text{start}} = 2.5 \text{ GHz}$   $f_{\text{end}} = 4.5 \text{ GHz}$   $f_{\text{step}} = 100.0 \text{ MHz}$

Magnetic flux **amplitude DC = 0.33  $\Phi_0$**  **RF = 0.3  $\Phi_0$**   
Frequency = 10.2 GHz

Integration time = 20.0 ns time step = 0.1 ps

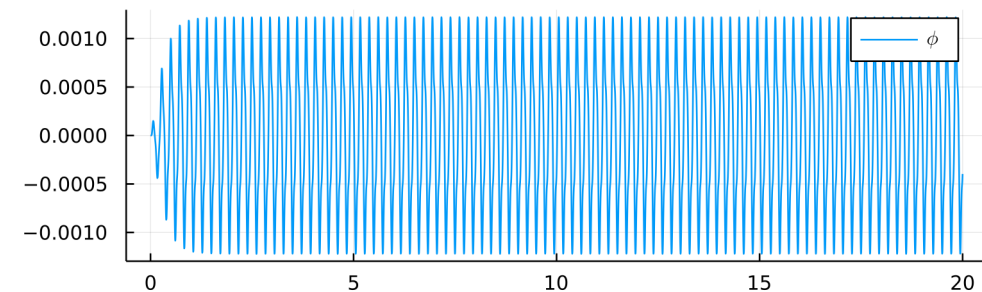
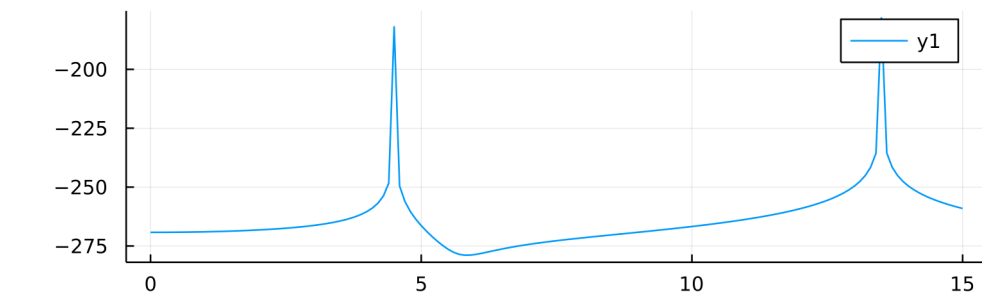
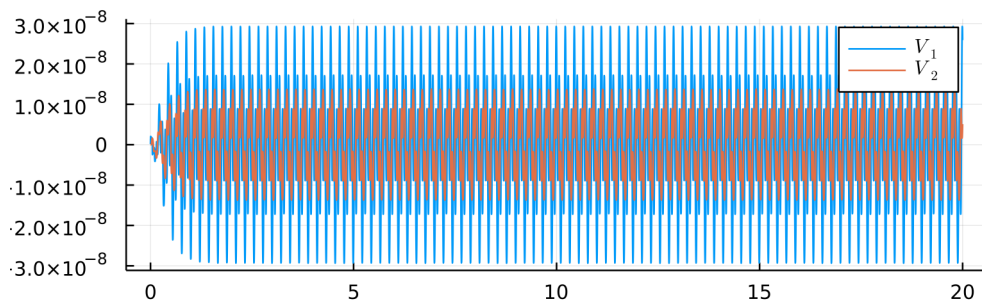
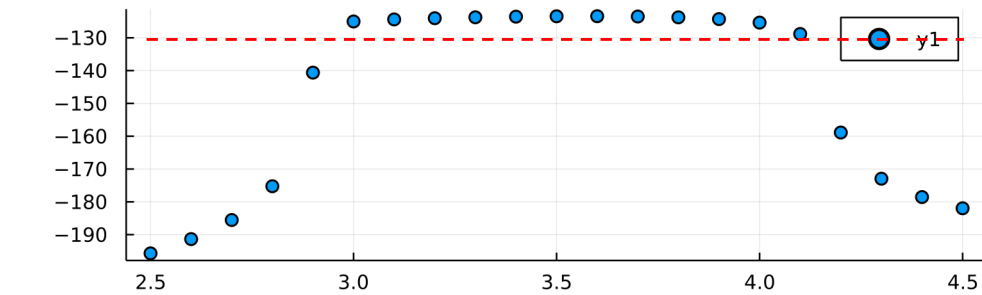
integrating 200000 time steps with 221 lag steps



Back to  $I_c=1\mu A$

Fix the pump frequency to 11.8 GHz  
and sweep the signal frequency

After 20 ns the system is not stationary

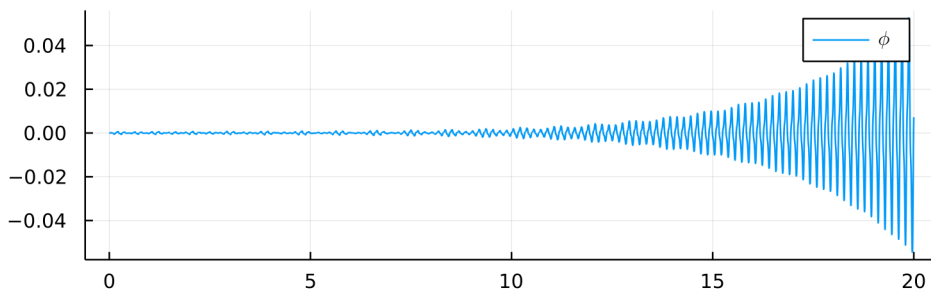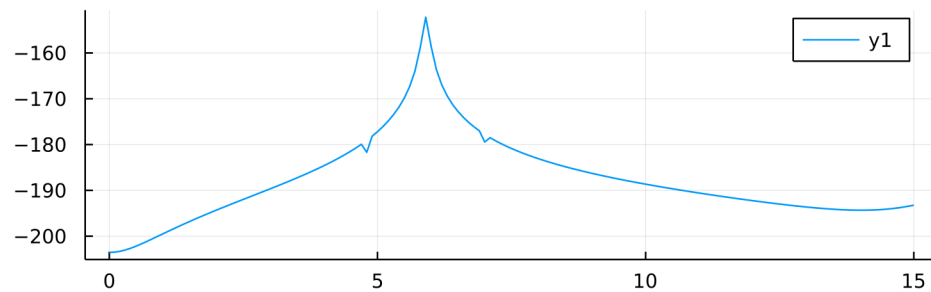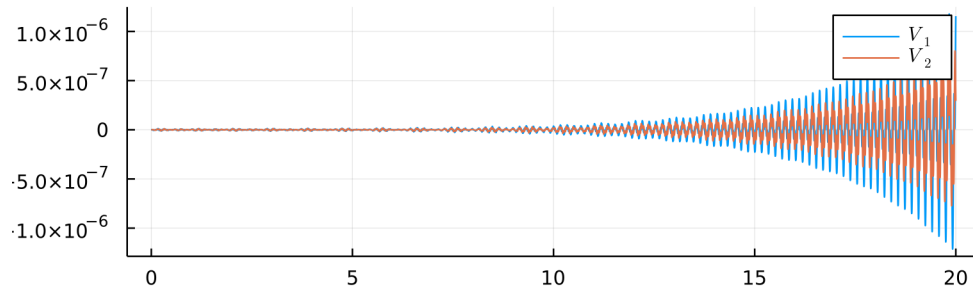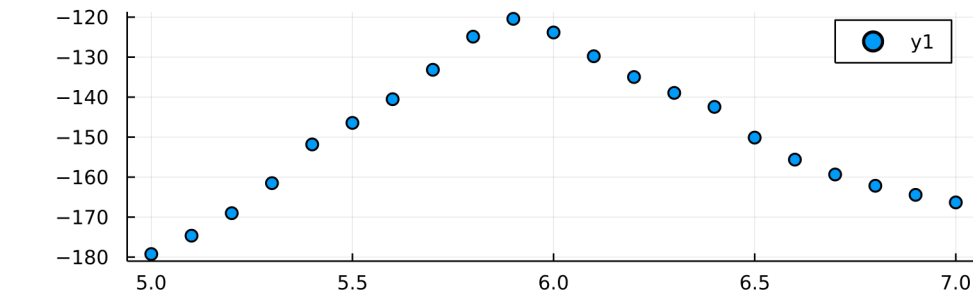

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   
 $I_0 = 1.0 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$   
 $F_{\text{plasma}} = 77.95 \text{ GHz}$





Lambda/4 Resonator frequency = 11.3 GHz Time delay = 22.12 ps  
input RF signal = 0.1 uV = -130.0 dBm

Fstart = 5.0 GHz Fend = 7.0 GHz Fstep = 100.0 MHz

Magnetic flux amplitude DC = 0.33  $\Phi_0$  RF = 0.25  $\Phi_0$   
Frequency = 11.8 GHz

**Integration time = 20.0 ns** time step = 0.1 ps  
integrating 200000 time steps with 221 lag steps

## Increase to 50 ns

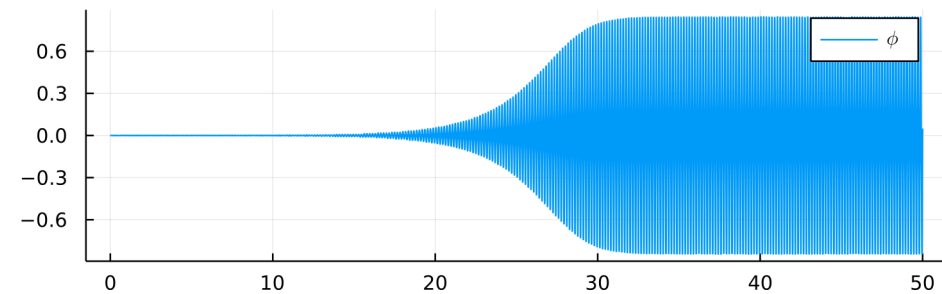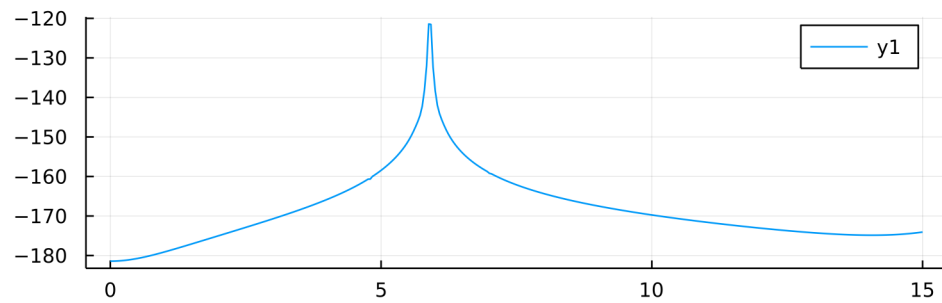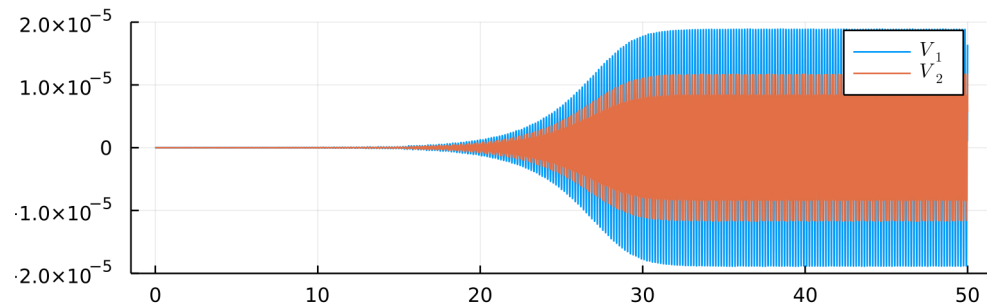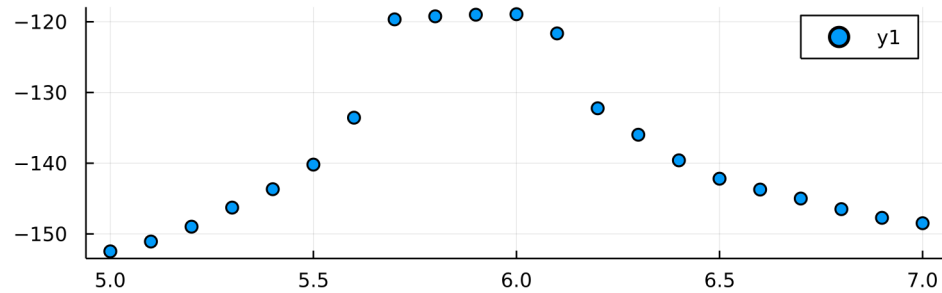

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   
 $I_0 = 1.0 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$

$F_{\text{plasma}} = 77.95 \text{ GHz}$

$\text{Lambda}/4 \text{ Resonator frequency} = 11.3 \text{ GHz}$   $\text{Time delay} = 22.12 \text{ ps}$   
 $\text{input RF signal} = 0.1 \text{ uV} = -130.0 \text{ dBm}$

$F_{\text{start}} = 5.0 \text{ GHz}$   $F_{\text{end}} = 7.0 \text{ GHz}$   $F_{\text{step}} = 100.0 \text{ MHz}$

$\text{Magnetic flux amplitude DC} = 0.33 \text{ Phi}_0$   $\text{RF} = 0.25 \text{ Phi}_0$   
 $\text{Frequency} = 11.8 \text{ GHz}$

$\text{Integration time} = 50.0 \text{ ns}$   $\text{time step} = 0.1 \text{ ps}$   
 $\text{integrating } 500000 \text{ time steps with } 221 \text{ lag steps}$



Lowering the signal does not change the result

The system is self oscillating, triggered by the signal

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   $I_0 = 1.0 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$

$F_{\text{plasma}} = 77.95 \text{ GHz}$

$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.12 ps

input RF signal = 0.01 uV = **-150.0 dBm**





$F_{\text{start}} = 5.0 \text{ GHz}$   $F_{\text{end}} = 7.0 \text{ GHz}$   $F_{\text{step}} = 100.0 \text{ MHz}$

Magnetic flux amplitude DC = 0.33  $\Phi_0$  RF = 0.25  $\Phi_0$

Frequency = 11.8 GHz









Integration time = 50.0 ns time step = 0.1 ps

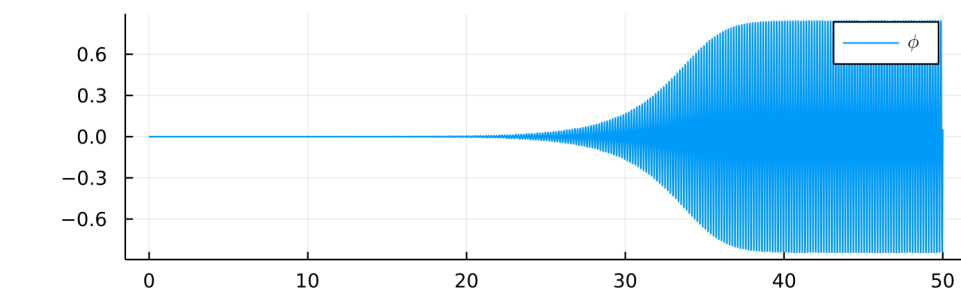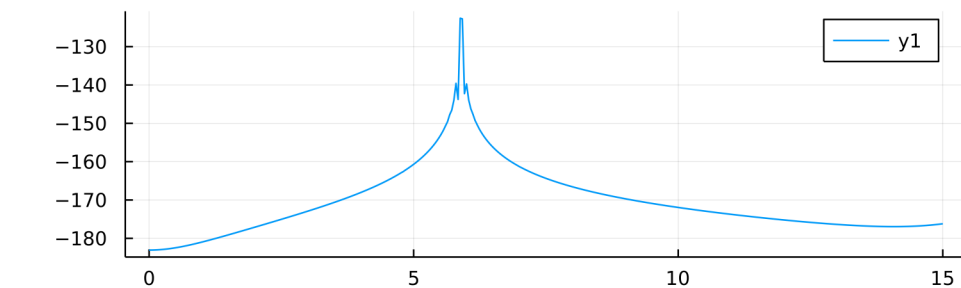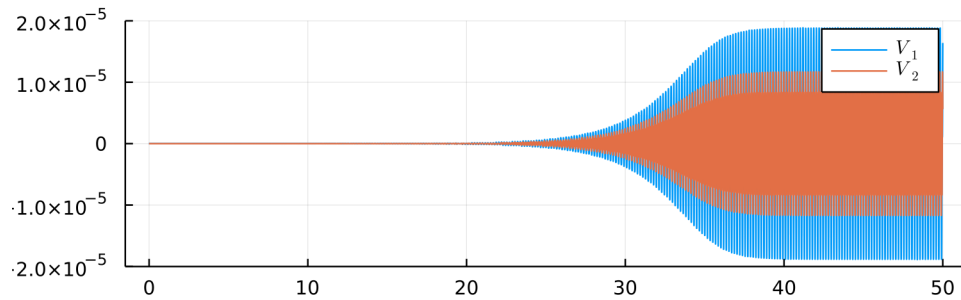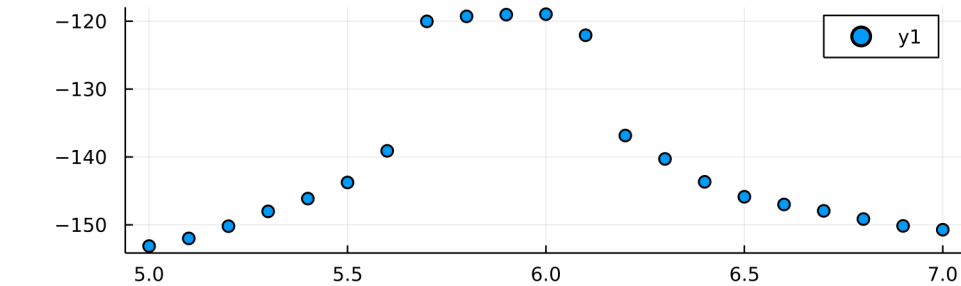integrating 500000 time steps with 221 lag steps



# Scan of different dc and rf amplitudes of magnetic flux

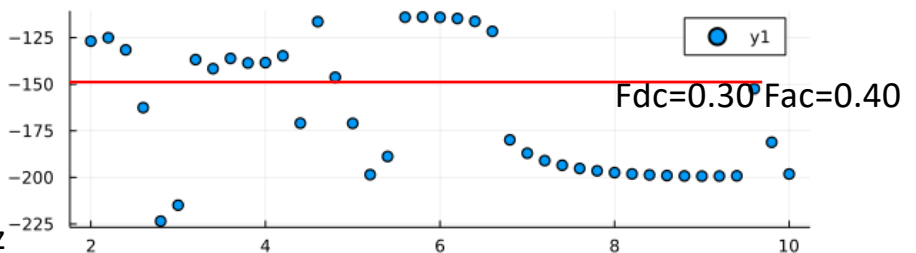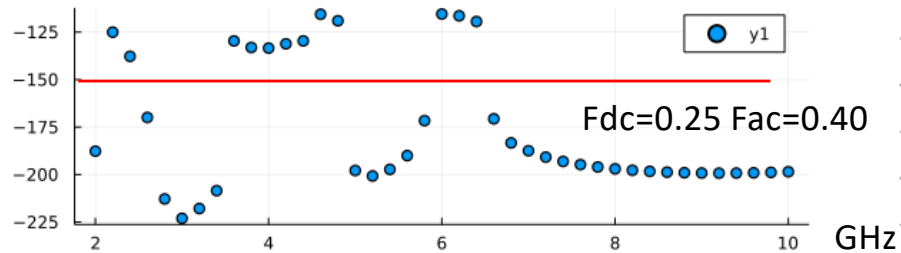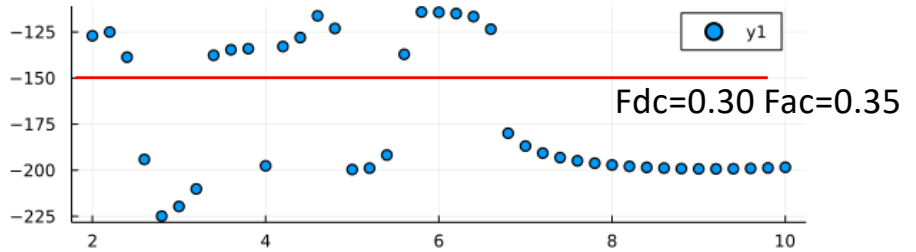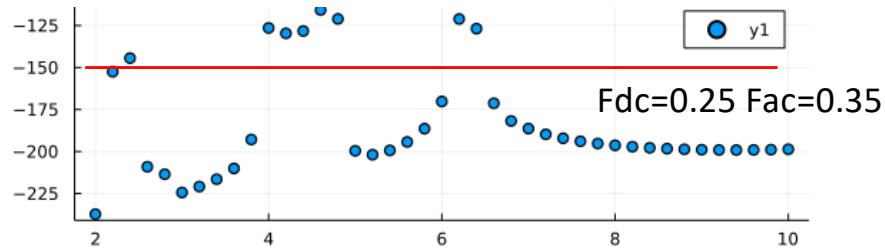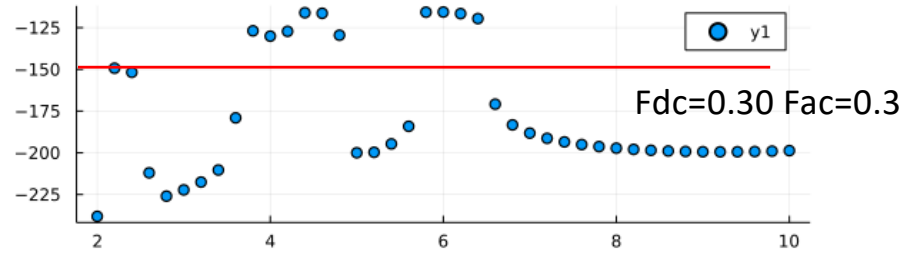
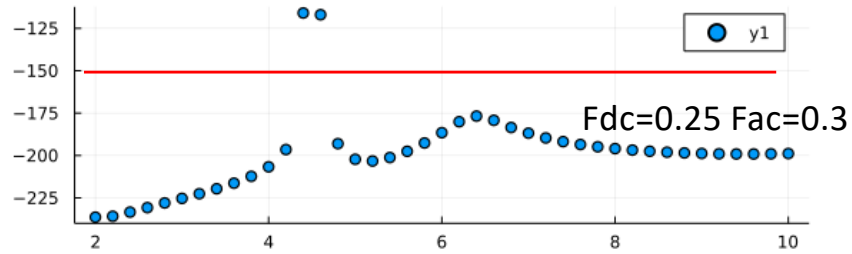
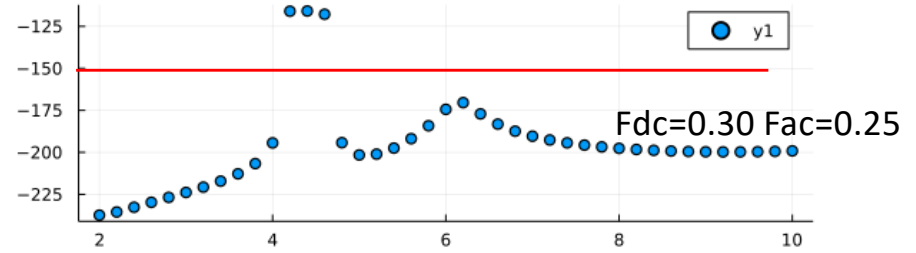
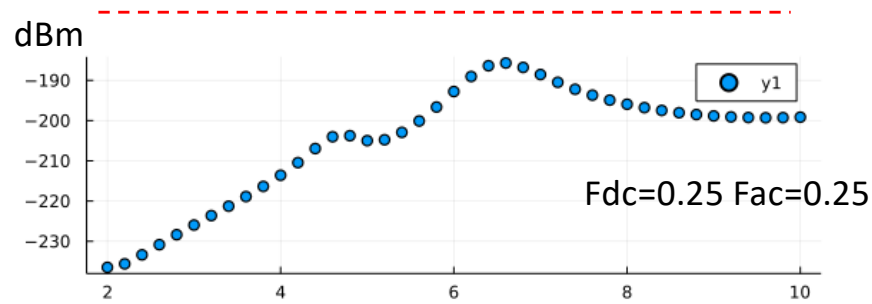
**F<sub>pump</sub> = 2 F<sub>signal</sub>   A<sub>signal</sub> = -150dBm**



GHz

## Effect of increasing the dc magnetic flux

$F_{dc} = 0.30$

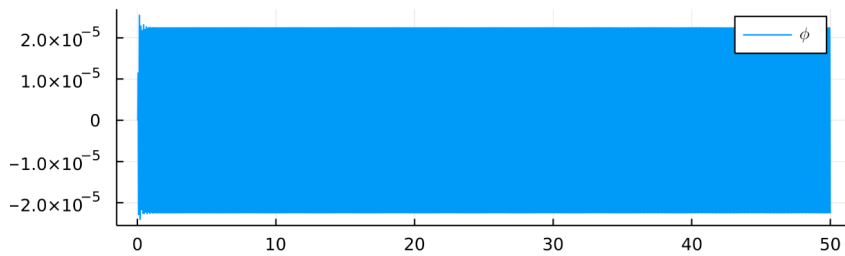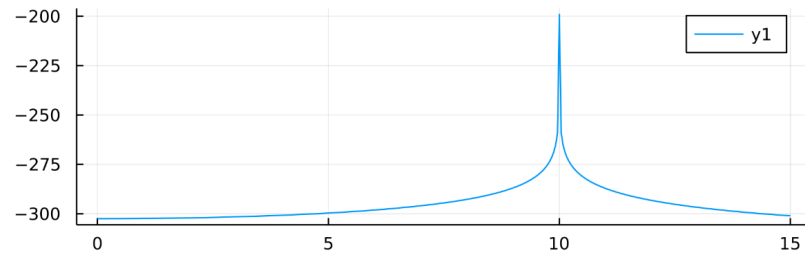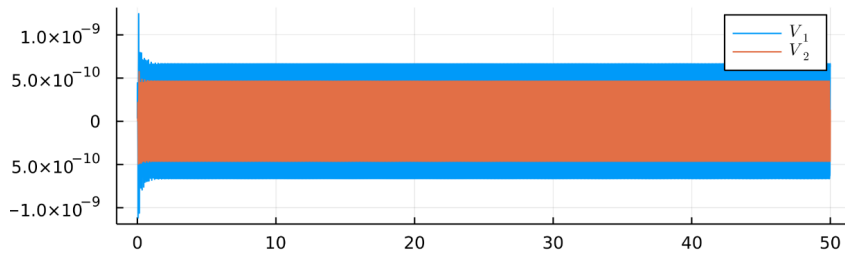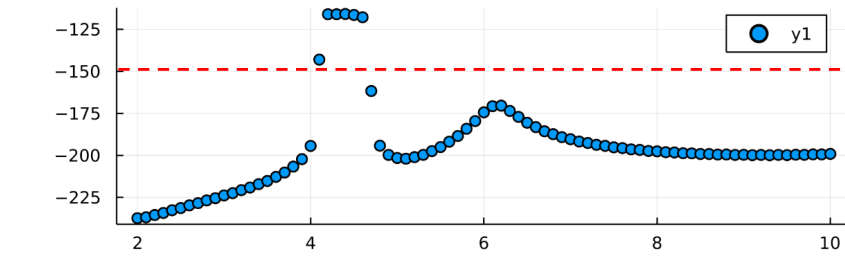

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   $I_0 = 1.0 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$

$F_{\text{plasma}} = 77.95525848081317 \text{ GHz}$

$\text{Lambda}/4 \text{ Resonator frequency} = 11.3 \text{ GHz}$   $\text{Time delay} = 22.123893805309738 \text{ ps}$

$\text{input RF signal} = 0.01 \text{ uV} = -150.0 \text{ dBm}$

$F_{\text{start}} = 2.0 \text{ GHz}$   $F_{\text{end}} = 10.0 \text{ GHz}$   $F_{\text{step}} = 100.0 \text{ MHz}$





**Magnetic flux amplitude DC = 0.30  $\Phi_0$  RF = 0.25  $\Phi_0$  Frequency = 11.3 GHz**

$\text{Integration time} = 50.0 \text{ ns}$   $\text{time step} = 0.1 \text{ ps}$

$\text{integrating } 500000 \text{ time steps with } 221 \text{ lag steps}$

# Effect of increasing the dc magnetic flux

$F_{dc} = 0.31$

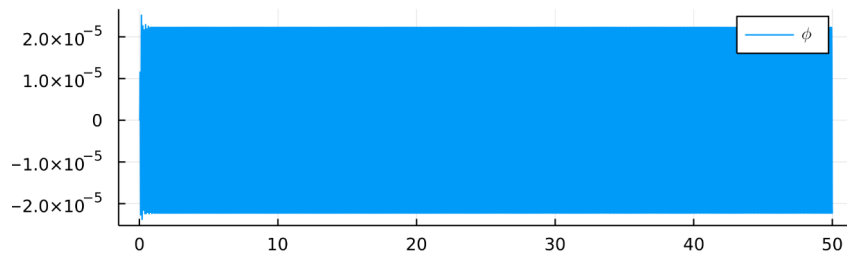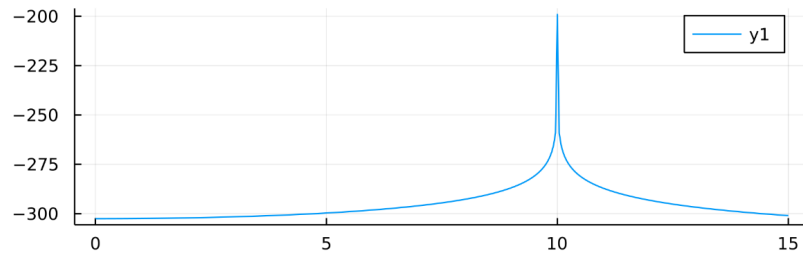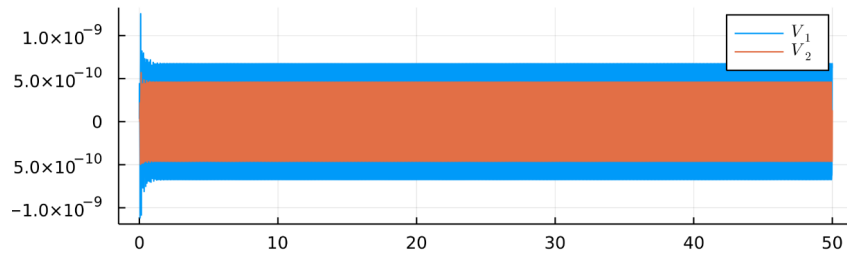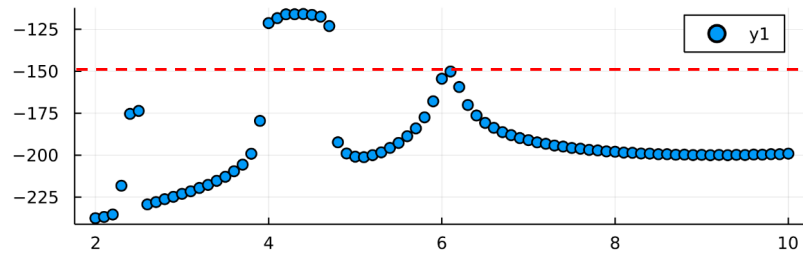

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   $I_0 = 1.0 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$

$F_{\text{plasma}} = 77.95525848081317 \text{ GHz}$

$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.123893805309738 ps

input RF signal = 0.01 uV = -150.0 dBm

$F_{\text{start}} = 2.0 \text{ GHz}$   $F_{\text{end}} = 10.0 \text{ GHz}$   $F_{\text{step}} = 100.0 \text{ MHz}$





**Magnetic flux amplitude DC = 0.31  $\Phi_0$  RF = 0.25  $\Phi_0$  Frequency = 11.3 GHz**

Integration time = 50.0 ns time step = 0.1 ps

integrating 500000 time steps with 221 lag steps

## Effect of increasing the dc magnetic flux

$F_{dc} = 0.32$

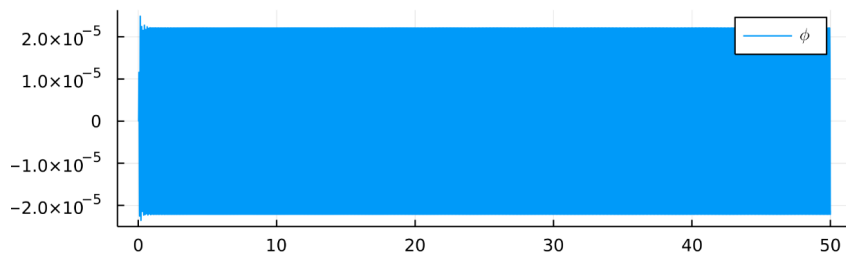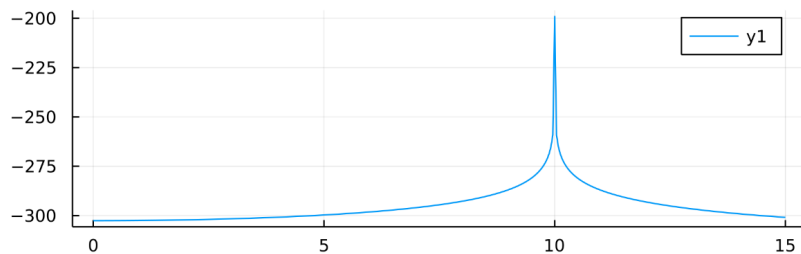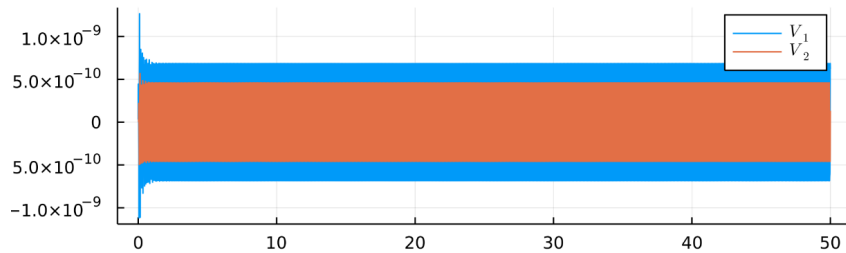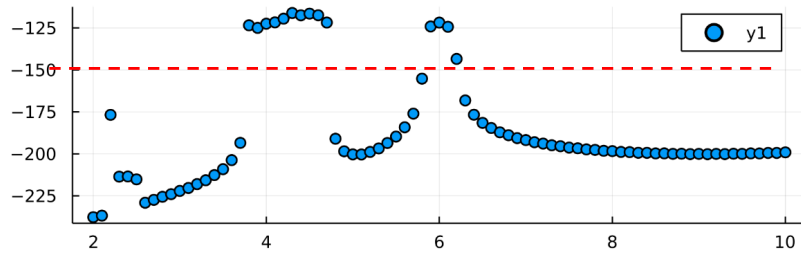

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   
 $I_0 = 1.0 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$   
 $F_{\text{plasma}} = 77.95 \text{ GHz}$

$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.123893805309738 ps

input RF signal = 0.01 uV = -150.0 dBm

Fstart = 2.0 GHz Fend = 10.0 GHz Fstep = 100.0 MHz





**Magnetic flux amplitude DC = 0.32  $\Phi_0$  RF = 0.25  $\Phi_0$  Frequency = 11.3 GHz**

Integration time = 50.0 ns time step = 0.1 ps

integrating 500000 time steps with 221 lag steps

# Effect of increasing the dc magnetic flux

$F_{dc} = 0.33$

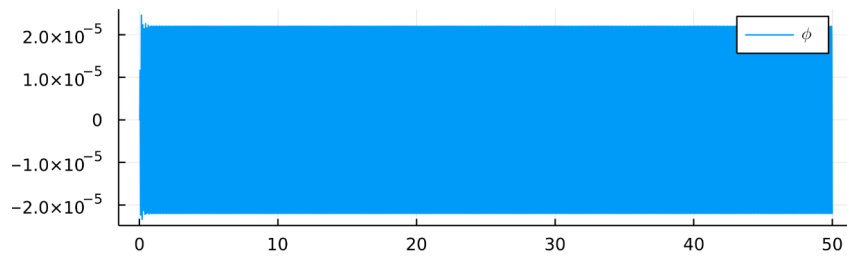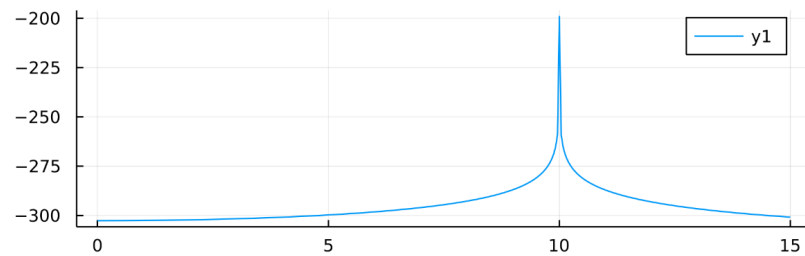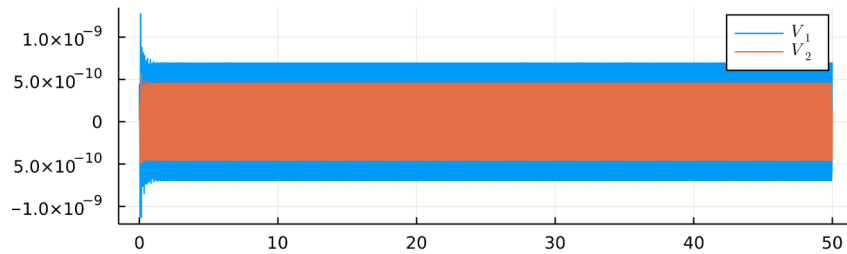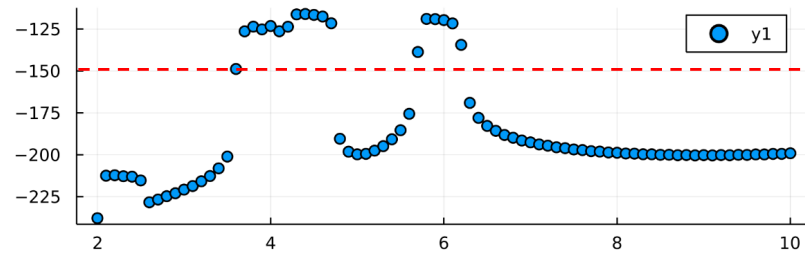

$Z_i = 50 \text{ Ohm}$   $C_c = 0.015 \text{ pF}$   $Z_0 = 50 \text{ Ohm}$   
 $I_0 = 1.0 \text{ uA}$   $C_j = 0.5 \text{ pF}$   $R_j = 100000 \text{ Ohm}$

$F_{\text{plasma}} = 77.95 \text{ GHz}$

$\lambda/4$  Resonator frequency = 11.3 GHz Time delay = 22.123893805309738 ps

input RF signal = 0.01 uV = -150.0 dBm

$F_{\text{start}} = 5.0 \text{ GHz}$   $F_{\text{end}} = 7.0 \text{ GHz}$   $F_{\text{step}} = 100.0 \text{ MHz}$

**Magnetic flux amplitude DC = 0.33  $\Phi_0$  RF = 0.25  $\Phi_0$  Frequency = 11.8 GHz**


Integration time = 50.0 ns time step = 0.1 ps

integrating 500000 time steps with 221 lag steps

# Scan of signal frequency for fixed pump

Scan of signal frequency


Fpump=12.4 GHz Asignal = -150 dBm

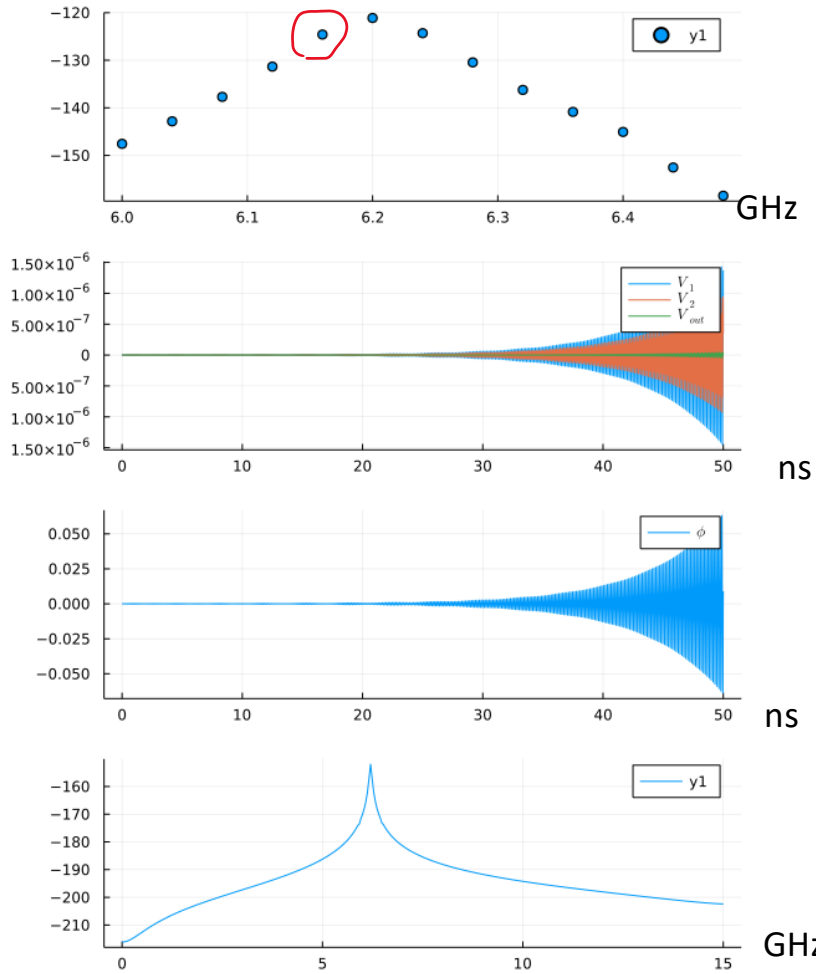

# Detail of dynamics

fixed signal frequency at 6.18 GHz

Fpump=12.4 GHz Asignal = -150 dBm

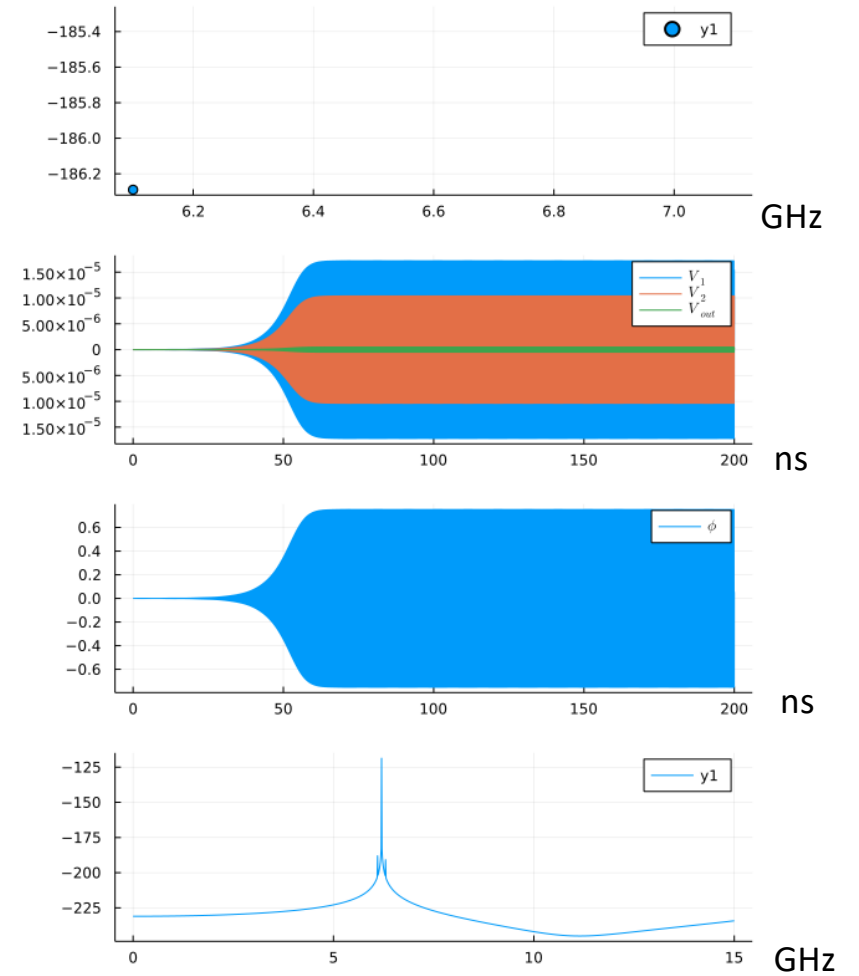

## Conclusions (for now)

- 1) the numerical model seems to work
- 2) Extension to a real SQUID is in progress
- 3) The value of experimental parameters are important ( $C_c$  and  $I_0$ )
- 4) The JPA simulation show expected responses but not amplifications
- 5) Self oscillations are triggered by input signal
- 6) More tests are necessary to fully validate the model
- 7) The role of circulator needs to be clarified