
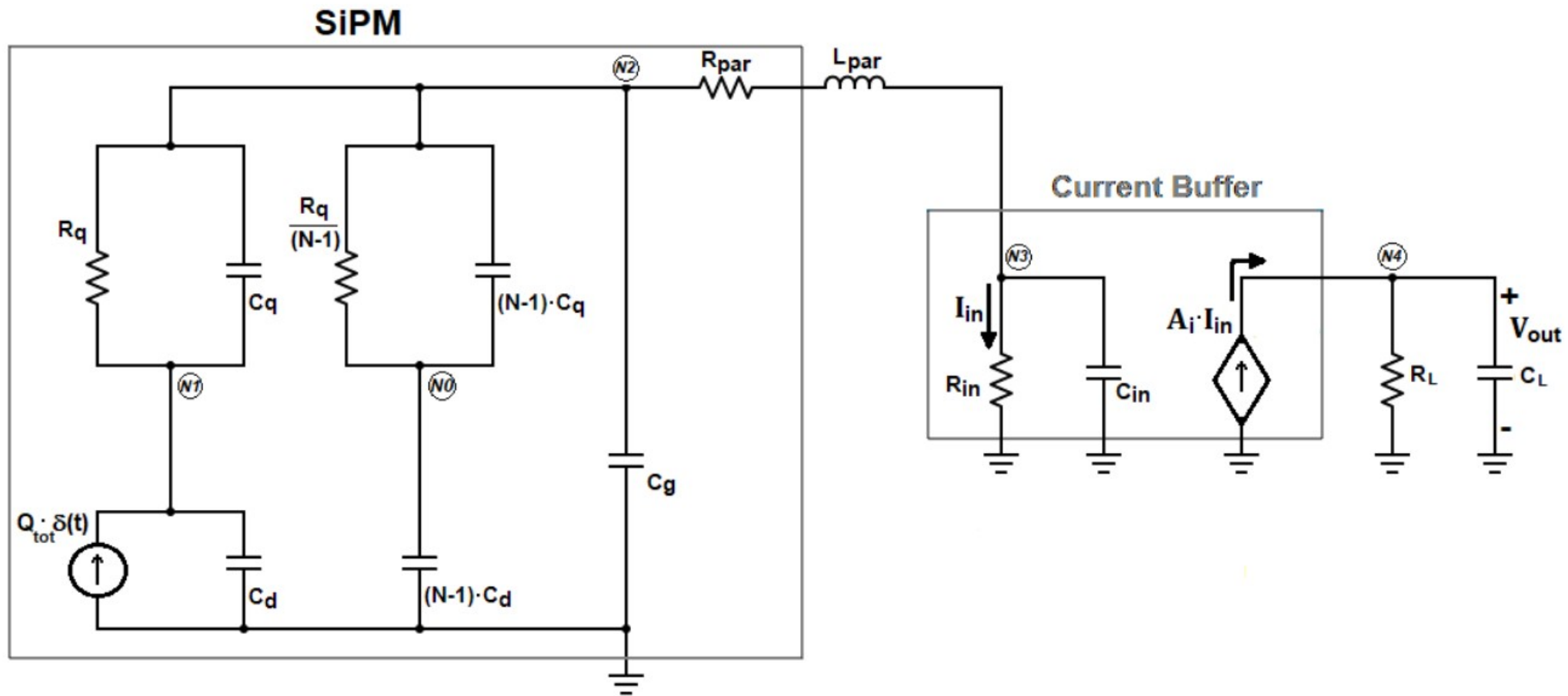



SiPM model

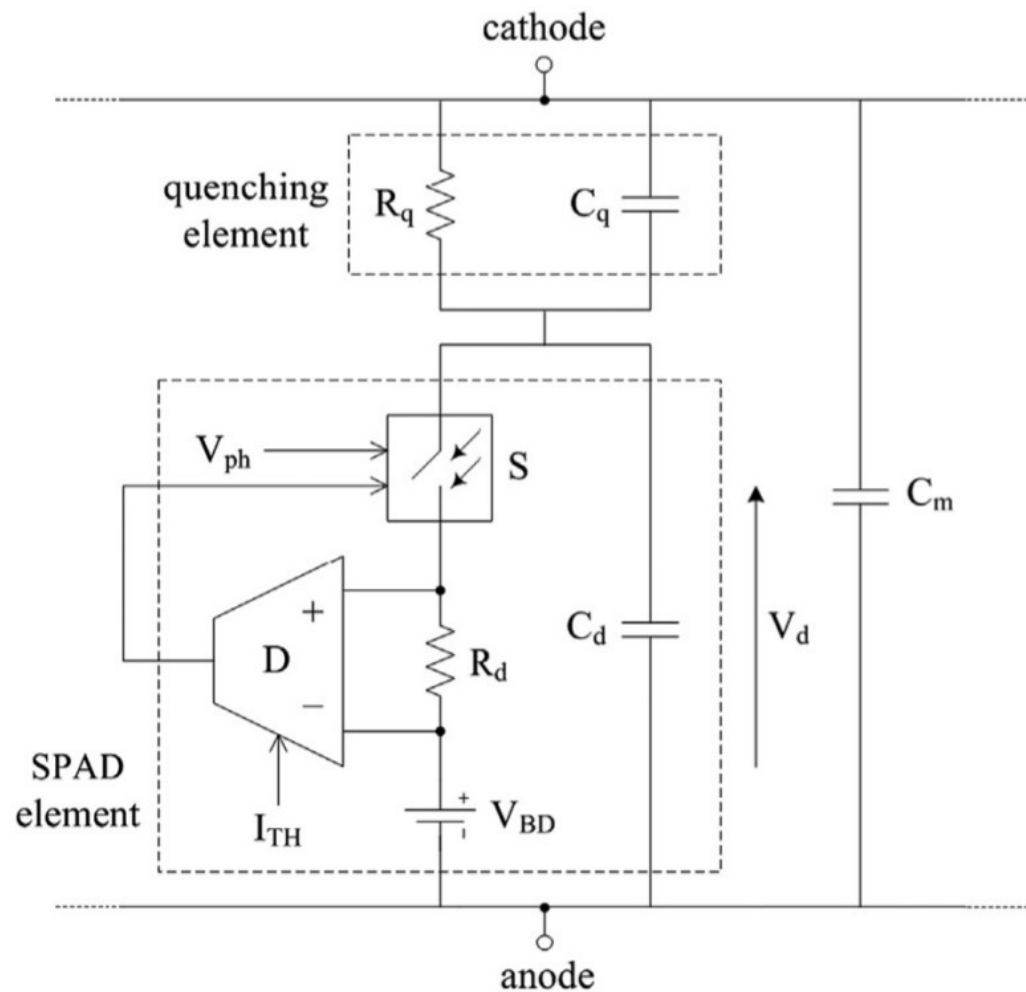

**Figure 1.** Equivalent electrical model of the silicon photomultiplier (SiPM) coupled to a current-mode front-end.



**Fig. 3.** Simplified block diagram of the improved equivalent electrical model of a single SPAD microcell.

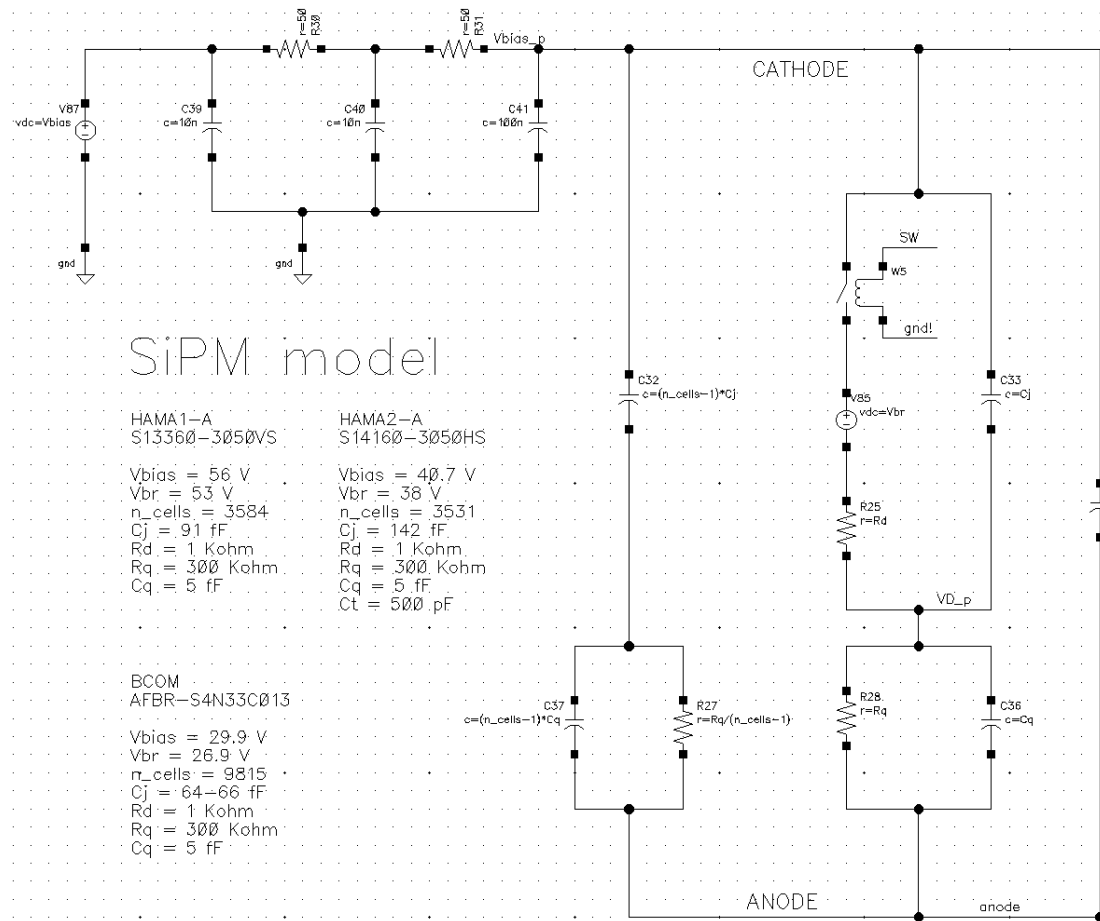

## SiPM model

HAMA1-A  
S13360-3050VS


$Vbias = 56\text{ V}$   
 $Vbr = 53\text{ V}$   
 $n\_cells = 3584$   
 $Cj = 91\text{ fF}$   
 $Rd = 1\text{ Kohm}$   
 $Rq = 300\text{ Kohm}$   
 $Cq = 5\text{ fF}$

HAMA2-A  
S14160-3050HS

$Vbias = 40.7\text{ V}$   
 $Vbr = 38\text{ V}$   
 $n\_cells = 3531$   
 $Cj = 142\text{ fF}$   
 $Rd = 1\text{ Kohm}$   
 $Rq = 300\text{ Kohm}$   
 $Cq = 5\text{ fF}$   
 $Ct = 500\text{ pF}$

BCOM  
AFBR-S4N33C013

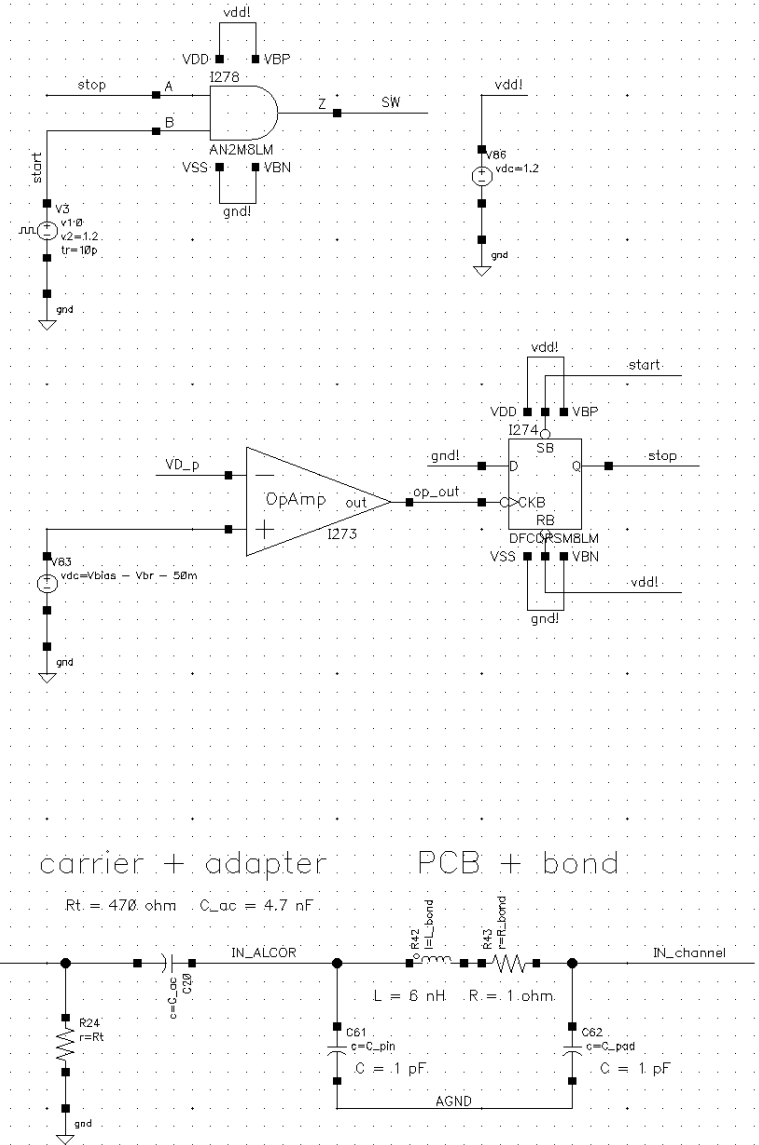$Vbias = 29.9\text{ V}$   
 $Vbr = 26.9\text{ V}$   
 $n\_cells = 9815$   
 $Cj = 64-66\text{ fF}$   
 $Rd = 1\text{ Kohm}$   
 $Rq = 300\text{ Kohm}$   
 $Cq = 5\text{ fF}$



carrier + adapter

$Rt = 470\text{ ohm}$   $C\_ac = 4.7\text{ nF}$


PCB + bond

$L = 8\text{ nH}$   $R = 1.0\text{ ohm}$

$C = .1\text{ pF}$   $C = 1\text{ pF}$


AGND

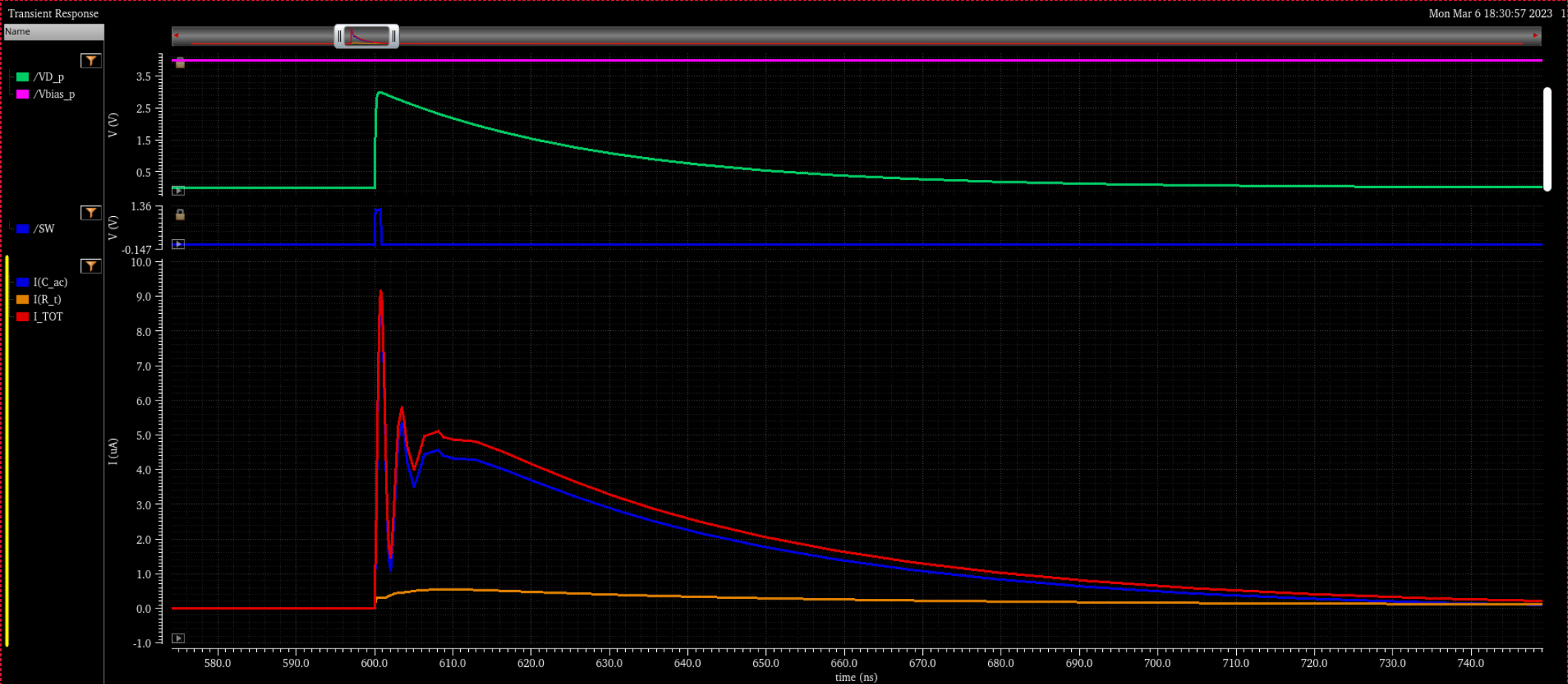$V_{bias} = 4V$ ,  $V_{br} = 1V$ ,  $OV = 3V$




ALCOR v1 sim

# Common gate = 0, boost = 0

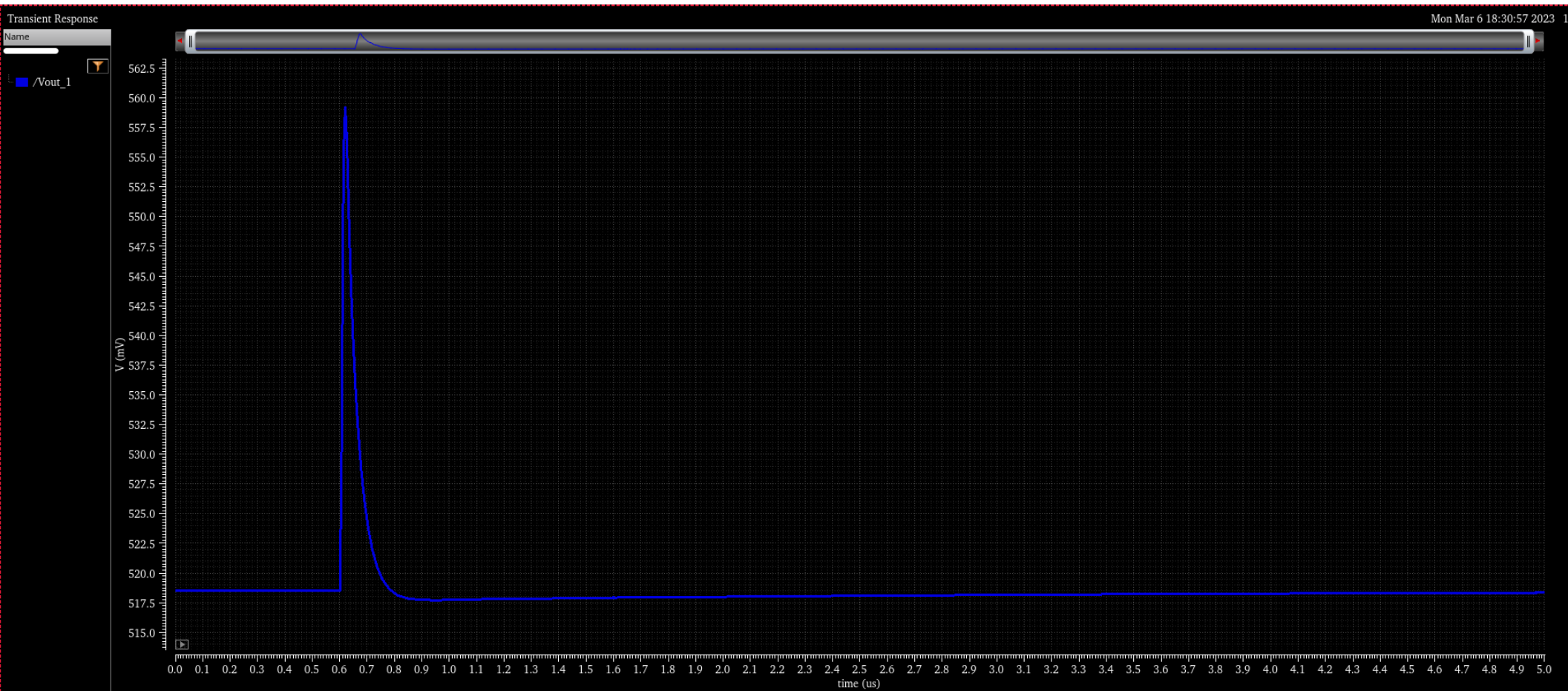


# Common gate = 0, boost = 0

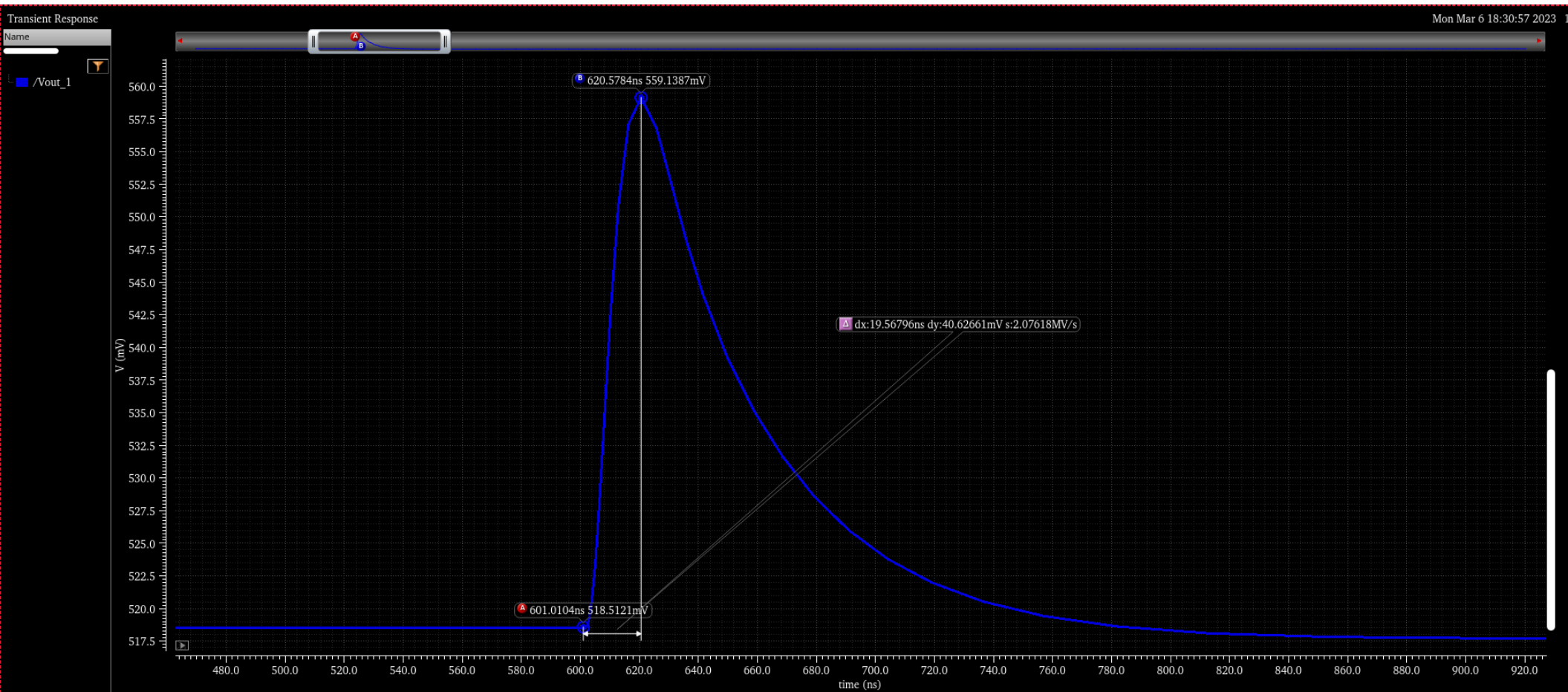



# Common gate scan (0-30)

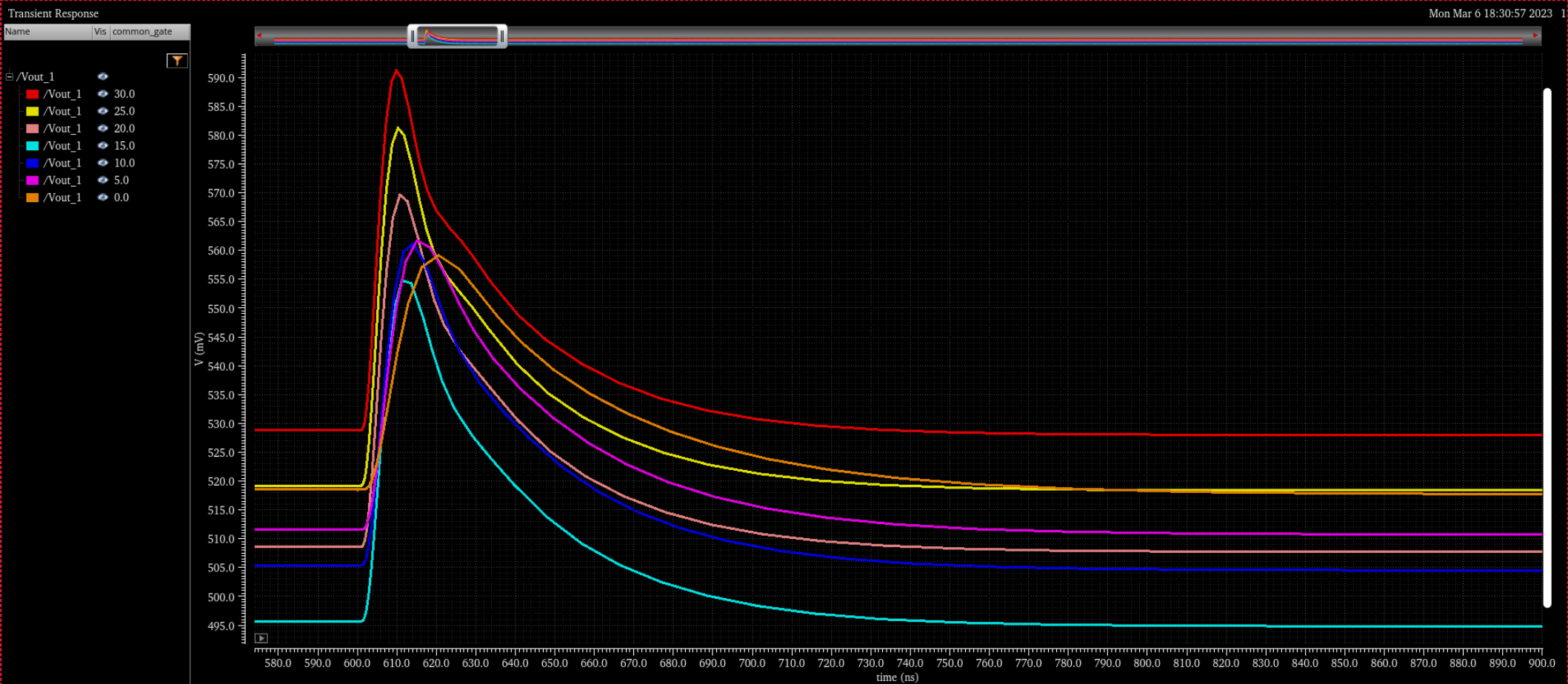

# Common gate scan (0-30)

