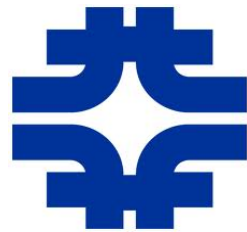


STUDY OF A POWER SUPPLY SYSTEM FOR THE DETECTORS IN MU2E EXPERIMENT




Fermilab summer project 2012

Daniele Ninci

26/09/2012

Mu2e experiment at Fermilab

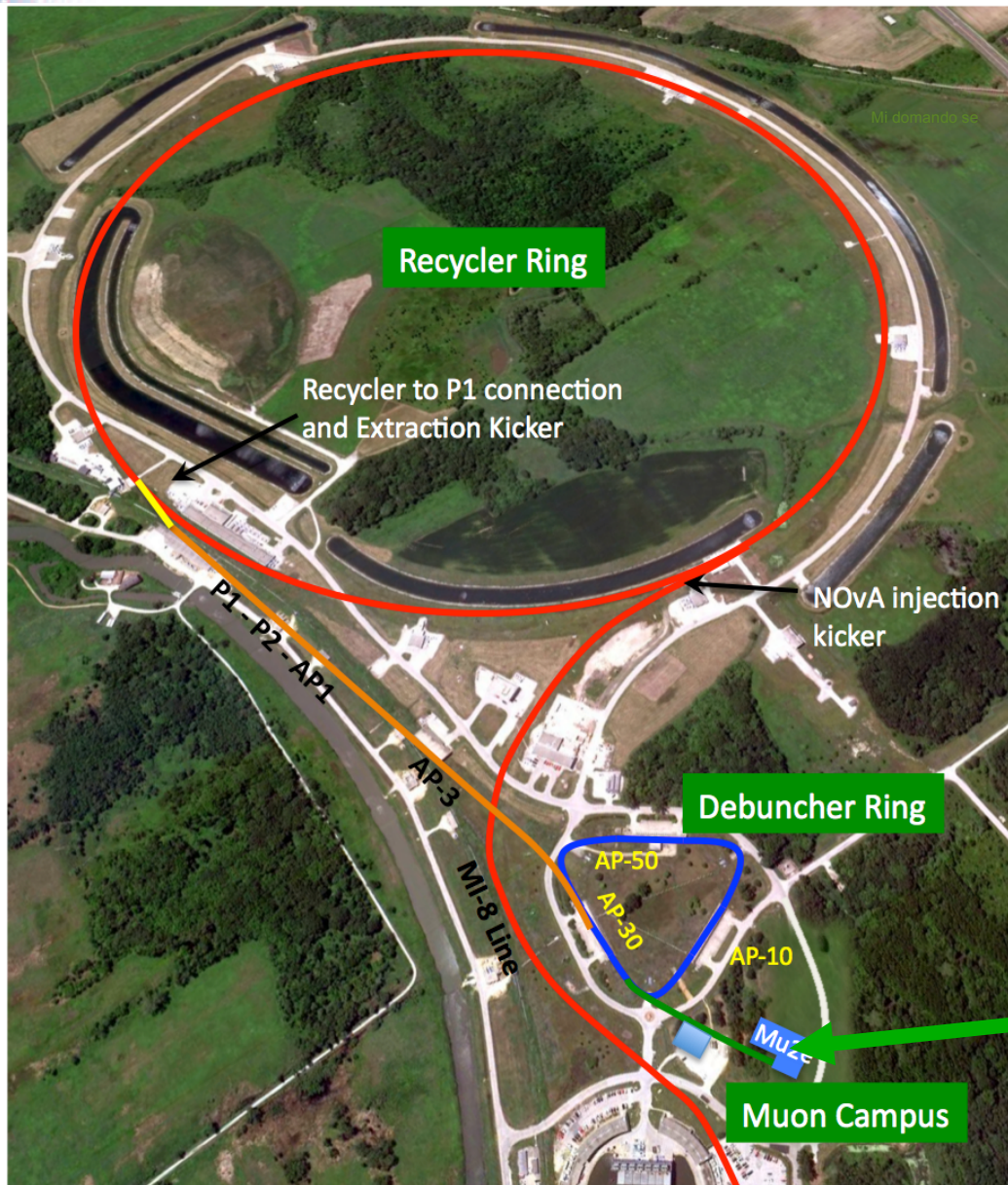


Searching for physics beyond Standard Model, charged lepton flavour violation (CLFV)

Measurement of the B.R. Of coherent conversion of muon into electron into a field of a nucleon, with a sensitivity of $6 \cdot 10^{-17}$



$$R_{\mu e} = \frac{\mu^- + A(Z, N) \rightarrow e^- + A(Z, N)}{\mu^- + A(Z, N) \rightarrow \text{capture}}$$

Mu2e site


Experimental setup

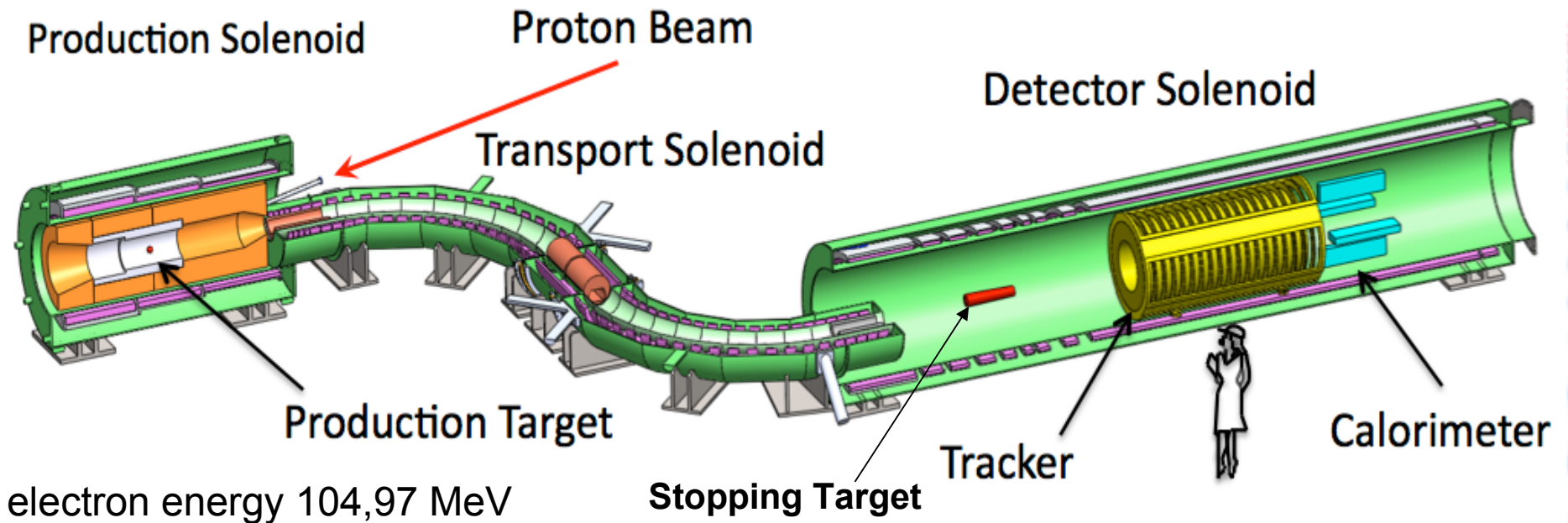

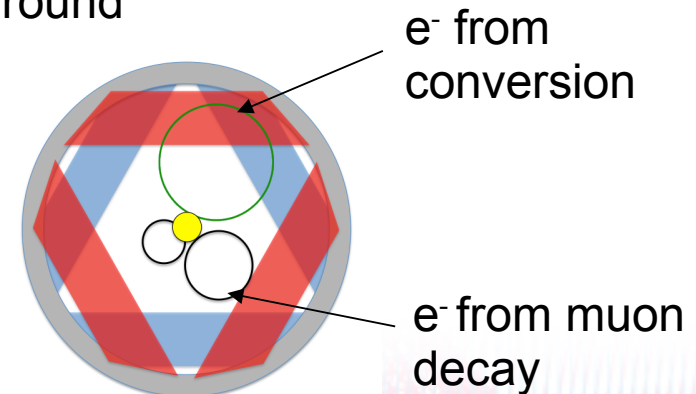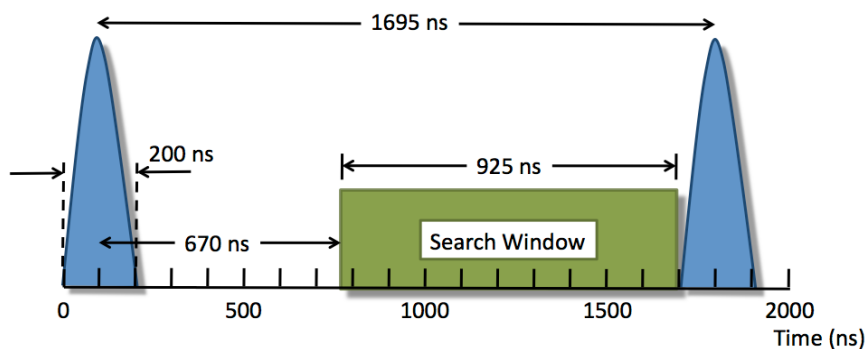Design made in order to suppress lots of the background



Power supply

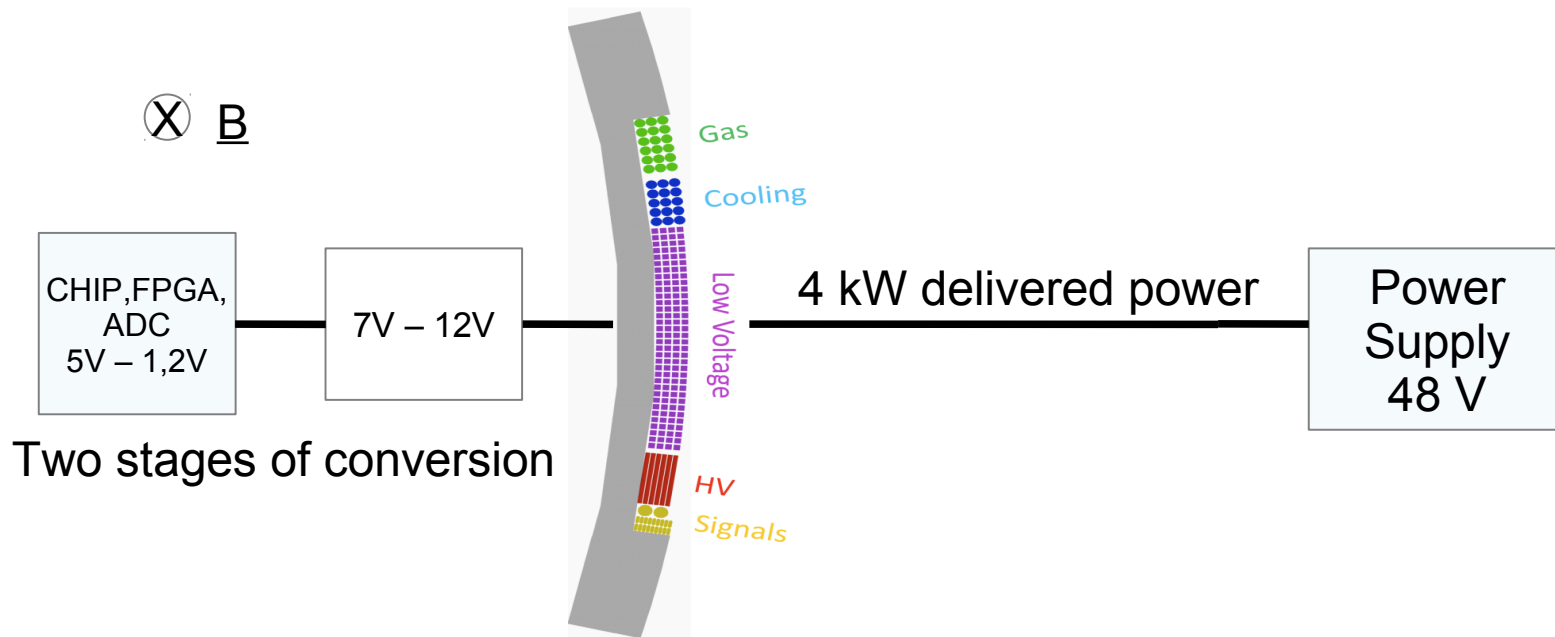

Linear converter (resistive)


- low EMI
- low efficiency ($\approx 50\%$)
- large power dissipation
- large cable cross section and resistive losses

Switch mode dc-dc converter

- higher EMI
- higher efficiency ($>70\%$)
- less power dissipation

dc-to-dc converter

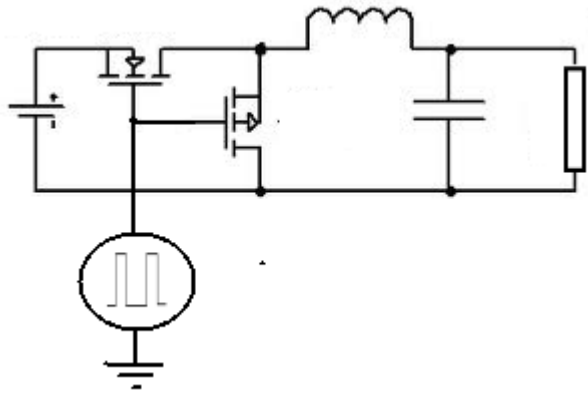
The energy is stored in the inductor and released to the load




Vout depends on the Duty Cycle

i.e. in buck converter $V_{out} = D \cdot V_{in}$


$$T_{on} = DT$$

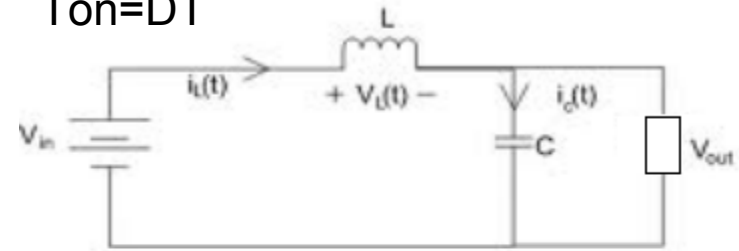


$$T_{off} = (1-D)T$$

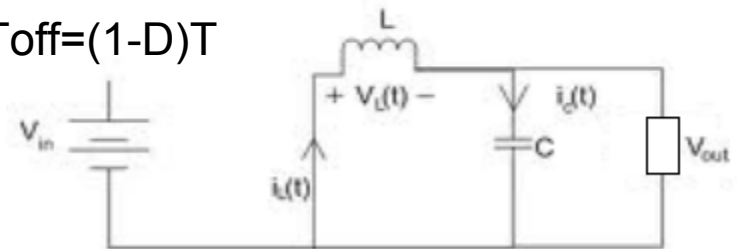

Continuous mode: $T_{off} > \tau_{dump}$

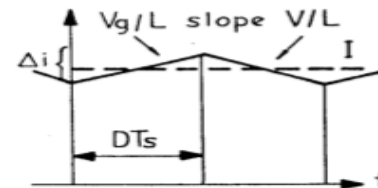


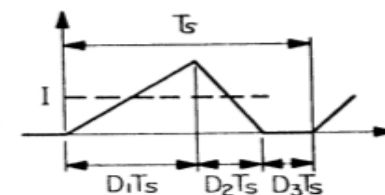Discontinuous mode $T_{off} < \tau_{dump}$




Power supply

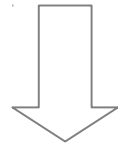Magnetic field in detector stage → inductor without ferromagnetic core to avoid saturation due to the ambient field.



Large inductor to recover the flux density lost due to the μ

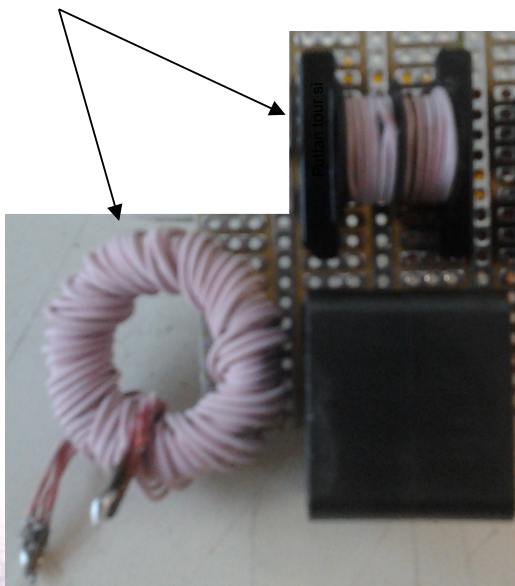Aircore inductors $1\mu\text{H}$ (>20 turns)




Large value of parasitic inductances and capacitances.

Ferromagnetic core
 $200\mu\text{H}$ (6 turns)

Final Conversion Stage


From 10 V to 1,5V - 5V

GaN transistors 2x4 mm

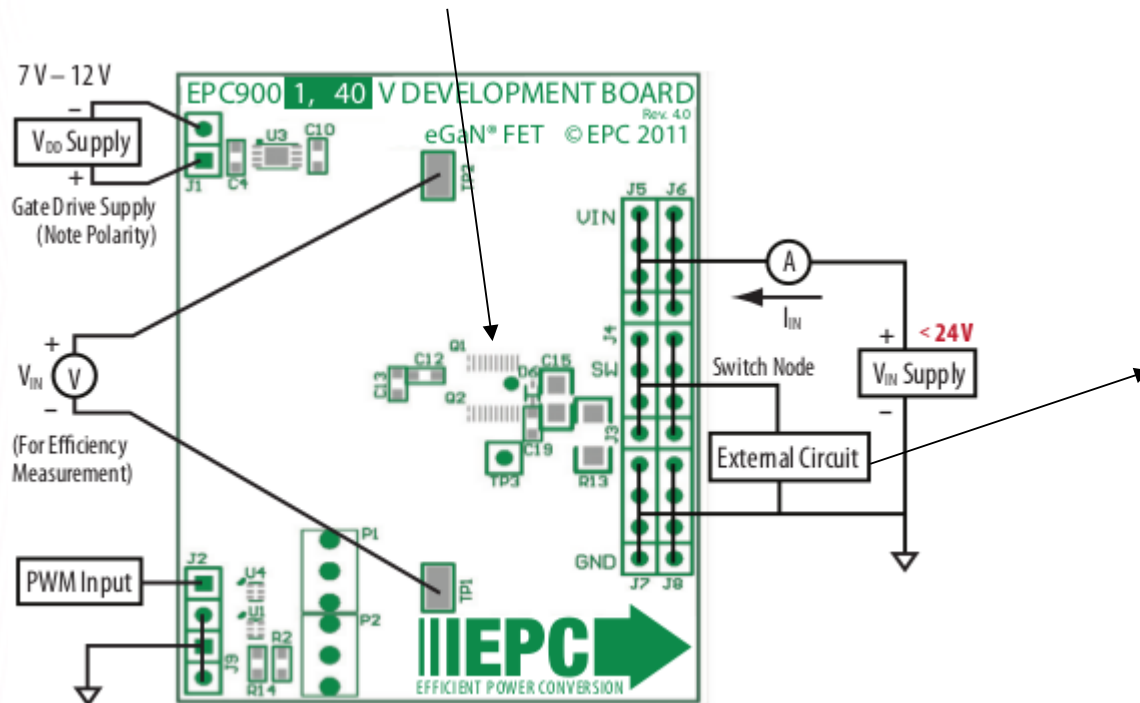

Buck converter

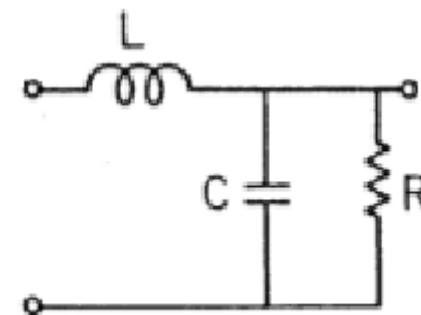- simple implementation
- non-inverting output
- $V_{out} = D \cdot V_{in}$



- R load = 0,3 Ω
- C = 33 μF
- L \approx 1 μH

Resistance to high temperature
Work at higher voltage than Si transistor
Higher switching frequency
Radiation hard (Mrad)

Final Conversion Stage



Buck converter solenoidal inductor (litz wire 24x36) efficiency results

$V_{out}/V_{in} \approx D$, neglecting parasitics resistances and losses during the switching.

Efficiency over 80%, expect higer with finer litz.

PWM and switch signal

Vin (V)	Freq (kHz)	D.C. (%)	Vout (V)	Eff (%)	RMS (%)
12	1000	14,4	1,490	84,5	0,4
	500	14,3	1,492	85,5	0,4
14	1000	12,3	1,488	83,0	0,4
	500	12,3	1,494	85,4	0,4
16	1000	10,9	1,501	82,4	0,4

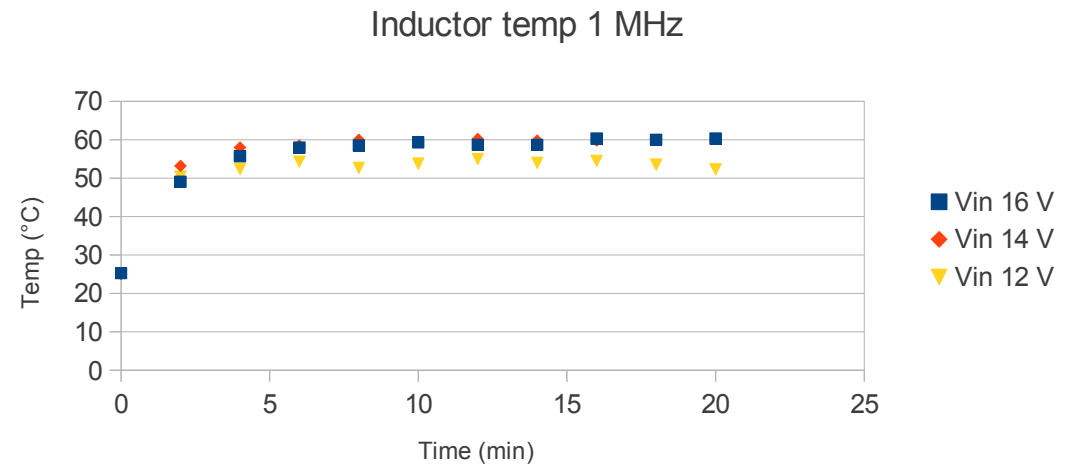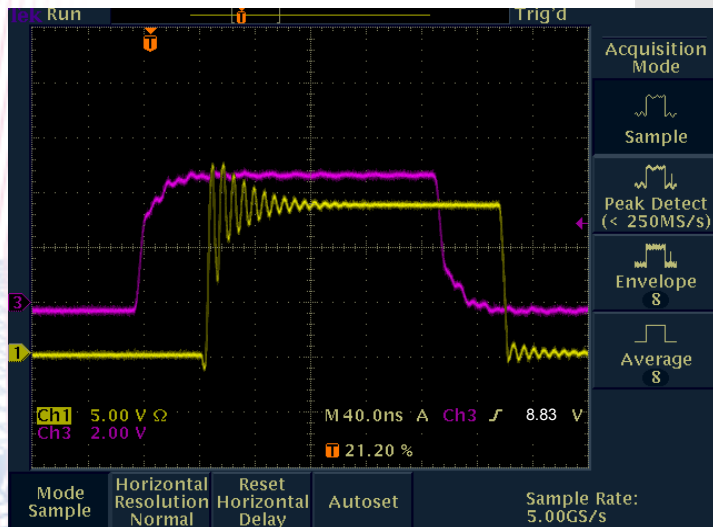


Final Conversion Stage

Trifiler toroidal inductor

Carry high current value dissipating less heat 7,78 A \rightarrow $T < 48^\circ$

Decrease interaction with e.m. external field

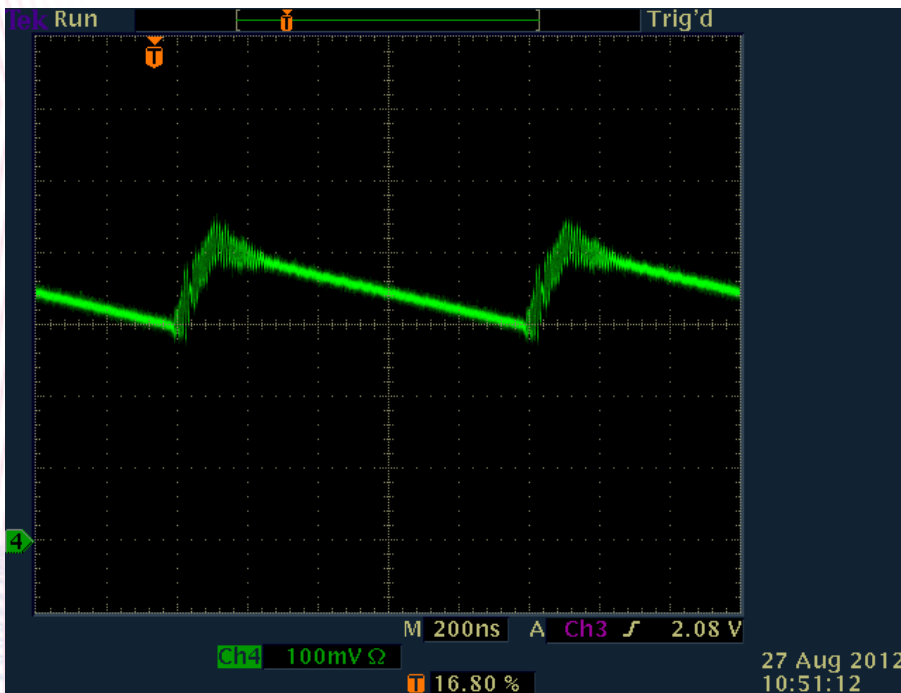Ripple current in inductor $\sim 20\%$ of signal



Vin	Freq	Eff (%)	RMS (%)
12	1MHz	81,0	0,4
12	1MHz	81,7	0,4
20	1MHz	81,5	0,4
24	1MHz	81,6	0,4

Initial Conversion Stage

From 48 V to 10 V

Switch converter with transformer in resonant mode:

- working with 50% duty cycle at higher frequency than buck converter
- isolation between power supply and load, preventing damage due to a transistor fault,
- negative or positive voltage supply,
- less EMI than buck converter.

Turns ratio 3:1

- $L_{\text{primary}} = 18,1 \mu\text{H}$; $L_{\text{leak}} = 3,0 \mu\text{H}$
- $L_{\text{secondary}} = 2,9 \mu\text{H}$; $L_{\text{leak}} = 0,46 \mu\text{H}$
- $C_{\text{coupling}} = 0,71 \text{ nF}$
- $R = 0,1 - 0,3 \Omega$
- $R_{\text{ac}} = 3,6 \Omega$ (600kHz)
- $\varnothing = 4 \text{ cm}$



Turns ratio 4:1

- $L_{\text{primary}} = 31,4 \mu\text{H}$; $L_{\text{leak}} = 3,81 \mu\text{H}$
- $L_{\text{secondary}} = 1,9 \mu\text{H}$; $L_{\text{leak}} = 0,23 \mu\text{H}$
- $C_{\text{coupling}} = 1,6 \text{ nF}$
- $R = 0,1 - 0,3 \Omega$
- $R_{\text{ac}} = 4,8 \Omega$ (600kHz)
- $\varnothing = 4 \text{ cm}$



Initial Conversion Stage

Resonant capacitance: 13 nF
Silicon instead of the GaN mosfet


Resonance frequency \approx 500 kHz

Without rectification

3:1

F(kHz)	Vin (V)	Vout (V)	Eff(%)	RMS (%)
600	48	7,00	80,0	0,5
700	48	7,64	84,2	0,5
800	48	6,08	74,4	0,5

With half bridge diodes rectification

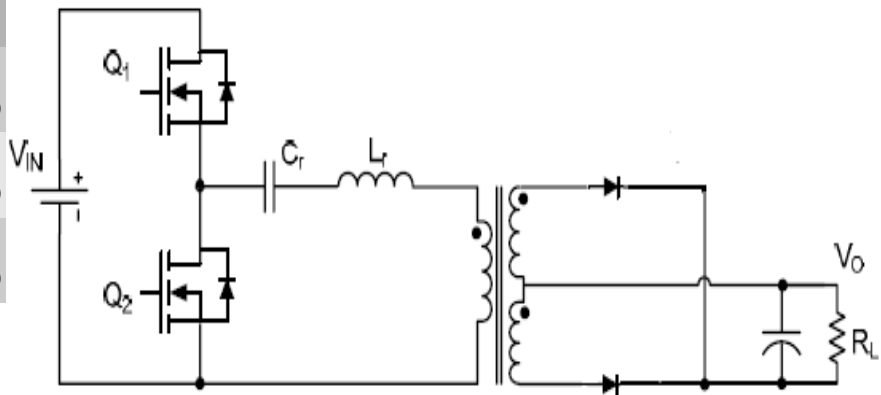

4:1


F(kHz)	Vin (V)	Vout (V)	Eff (%)	RMS (%)
500	48	5,8	83,4	0,7
600	48	5,16	82,2	0,8
700	48	4,48	79,5	1,0
760	48	4,24	82,4	1,0

F(kHz)	Vin (V)	Vout (V)	Eff (%)	RMS (%)
480	48	5,74	70,7	0,5
600	48	5,38	74,3	0,7
700	48	4,94	74,8	0,7
800	48	4,52	73,1	0,8

Initial Conversion Stage




Significant ringing on the diode anodes

Efficiency 74% @ 600kHz

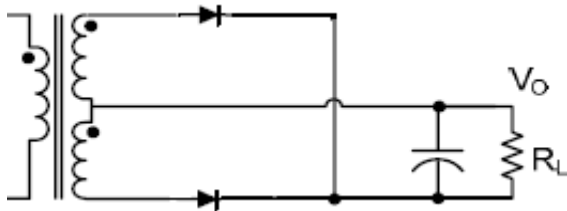

Ringing reduced by adding a snubber.

Efficiency 76% @ 600kHz

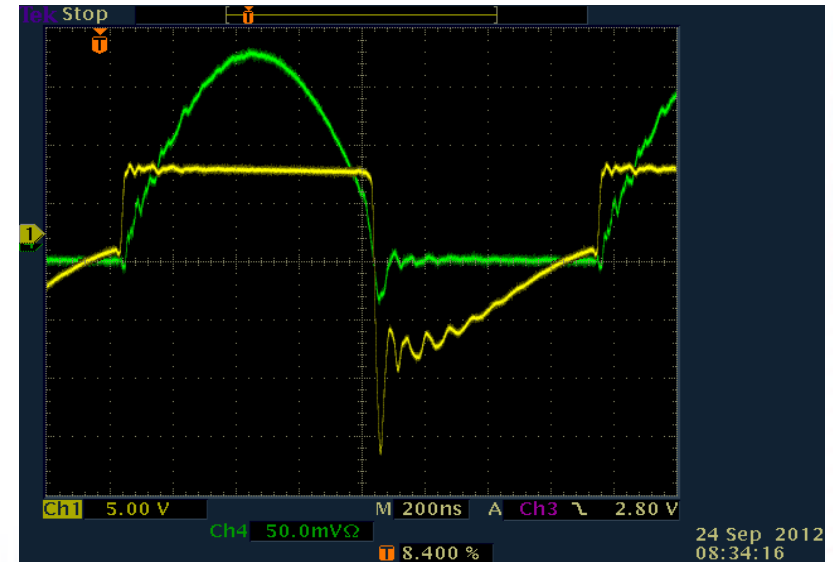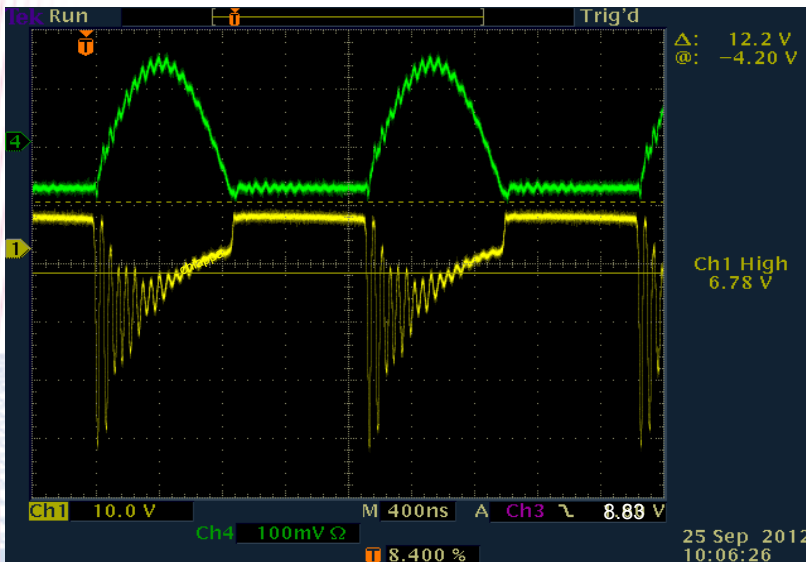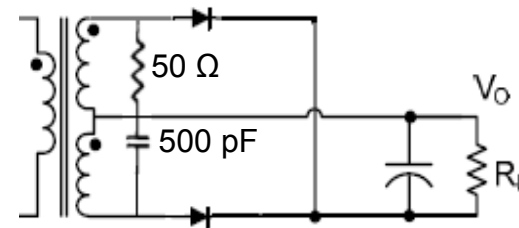

Initial Conversion Stage

Using a finer litz wire (660x45) is possible to reduce AC resistance and increase in efficiency

4:1 transformer fine litz wire

- $L_{\text{primary}} = 7,02 \mu\text{H}$; $L_{\text{leak}} = 3,2 \mu\text{H}$
- $L_{\text{secondary}} = 0,88 \mu\text{H}$;
- $C_{\text{coupling}} = 0,2 \text{ nF}$
- $R = 0,2 \Omega$
- $\varnothing = 5 \text{ cm}$



Tested with a resonant capacitance of 13 nF

Freq (kHz)	Vin (V)	Vout (V)	Iout (A)	Pout (W)	Eff (%)	RMS (%)
790	48	8,5	4,25	36,125	81,5	0,2
850	48	7	3,5	24,5	83,0	0,3

Conclusions

- buck converter is a good choice for a final stage;
- rectification with diodes cause a drop in efficiency;
- aircore transformers appear to be promising for the first level converters.

Future plans

- implementation of half bridge and full bridge converters with synchronous rectification;
- optimization of transformer;
- introduce closed loop operation;
- test the interaction between the two stages of converter;
- measure EMI.

The background features a complex, abstract pattern of thin, overlapping lines in red and blue. These lines form a series of interconnected, slightly offset rectangular and polygonal shapes, creating a 3D wireframe effect. The lines are most dense and visible in the corners and along the edges, fading towards the center. The overall color palette is a mix of vibrant red and a bright, slightly cyan blue, set against a plain white background.

THANK YOU