

# Front-end electronics For FD2 X-Arapuca tests

April 2023

P. Carniti, C. Gotti, E. Cristaldo, G. Pessina, F. Terranova  
INFN/Univ. Milano-Bicocca






# Membrane cold electronics

**DMEM 1.0** 4-channel motherboard designed at FNAL [EDMS 2795424](#)

- **3@CERN** (in use), **7@MiB** (of which 2 in use)
- Changes w.r.t. EDMS schematic:  $R_f=1.2k$  instead of  $2k$  (2 resistors per channel)
- Change propagated to all boards (except M1 M2 in module 0)

**HD-style amplifiers:** same as horizontal drift [EDMS 2805804](#)

     - **8(new)@MiB** (of which 4 in use),  **$\approx 15$ (old)@CIEMAT**, a few(?)@CERN (not all in use)
- 50 ohm resistors must be added in series with the THS4531 outputs to prevent instabilities with large (>390 ohm) feedback resistors; likely not necessary with old amplifiers (old batch of THS4531)



# Cables

Between flex and DMEM: [EDMS 2815448](#)



- White «coaxial» cables (actually 2 conductors + shielding), about 1m long
- Made/ordered by FNAL
- Included in mounted Arapucas (?)

Between DMEM and warm: [EDMS 2815464](#)

- Blue superior essex cable (same as HD)
- DSUB15 connectors at both ends (differs from HD)
- Cold side: female/female
- Warm side: female/male

NIOBE-VD flange: [EDMS 2802472](#)

  
- Male DSUB15 connectors on both sides
- Designed by Jon Ameel (UMich), in use at CERN
- Don't know if available for other labs





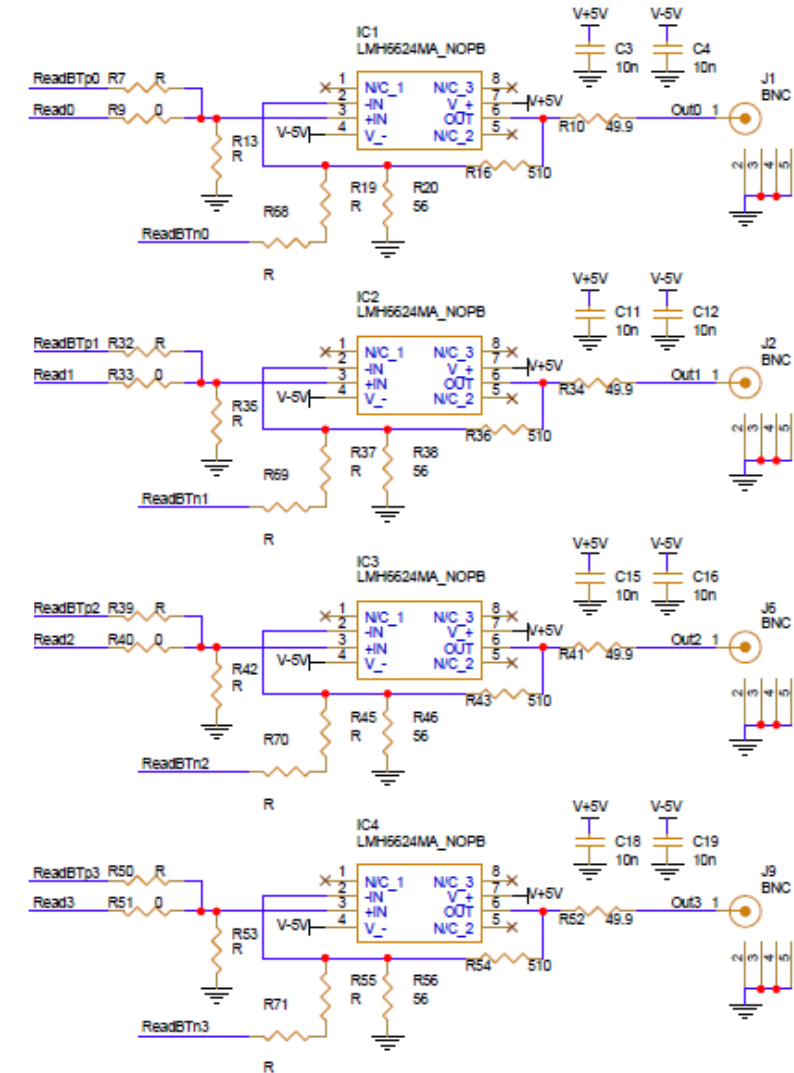
# Warm second stage v1

- «Sold out» (a few boards in some labs, but we don't have anymore)
- Undershoot  $\approx 25\%$  mainly due to input transformer
- Same as unmodified DAPHNE V2A
- There are ways to reduce undershoot with the transformer, studied by Esteban, not applied here

Buffers with gain  
(before or after the transformer)



To/from the cold amp



 
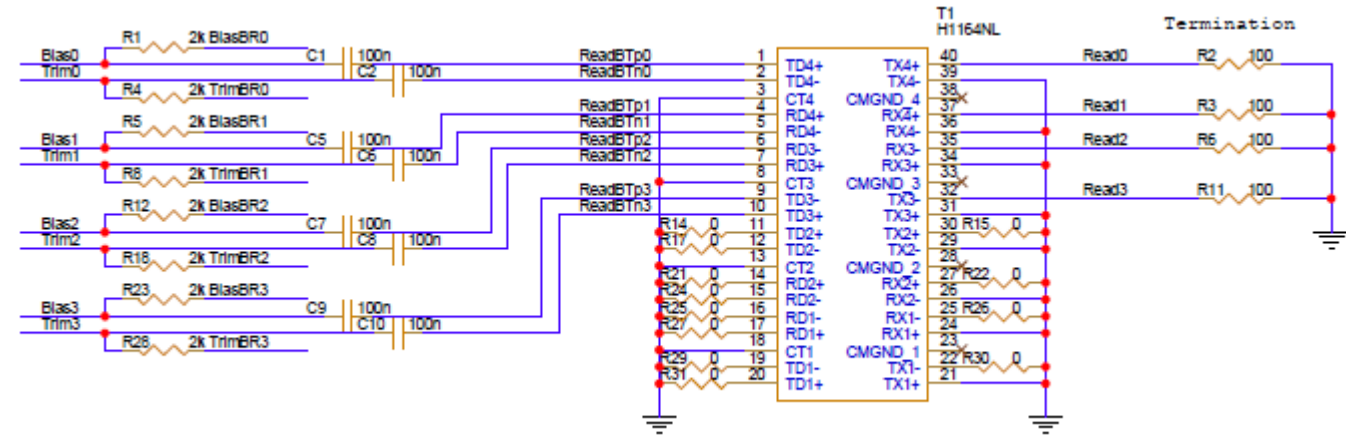
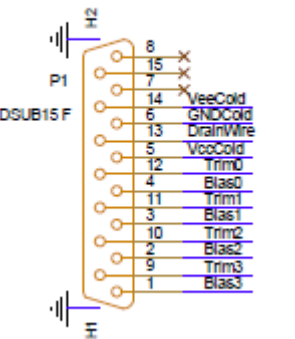




# Warm second stage v2


- 10 populated boards ordered, expected by mid may
- Two options:
  - Transformer as DAPHNE v3 (undershoot down to  $\approx 8\%$ )
  - Transformer bypassed, AC coupled w large caps, undershoot  $\approx 3\%$

DUNE\_warm\_interface v2.0 202303

 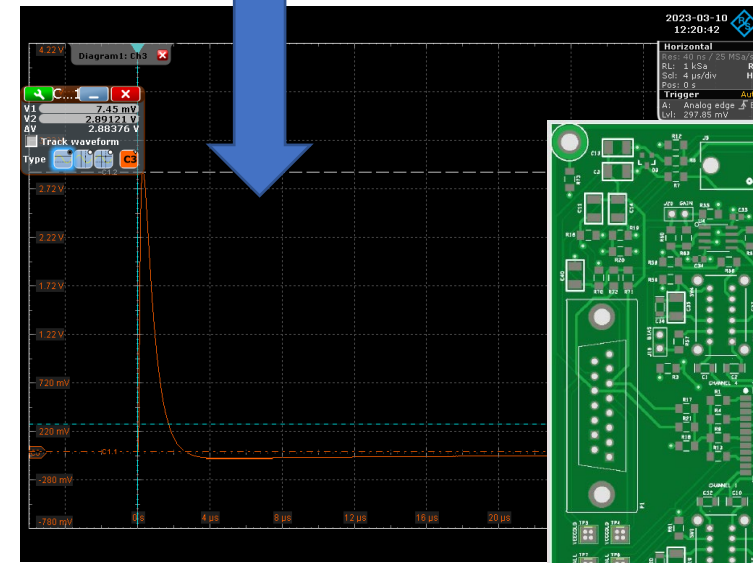  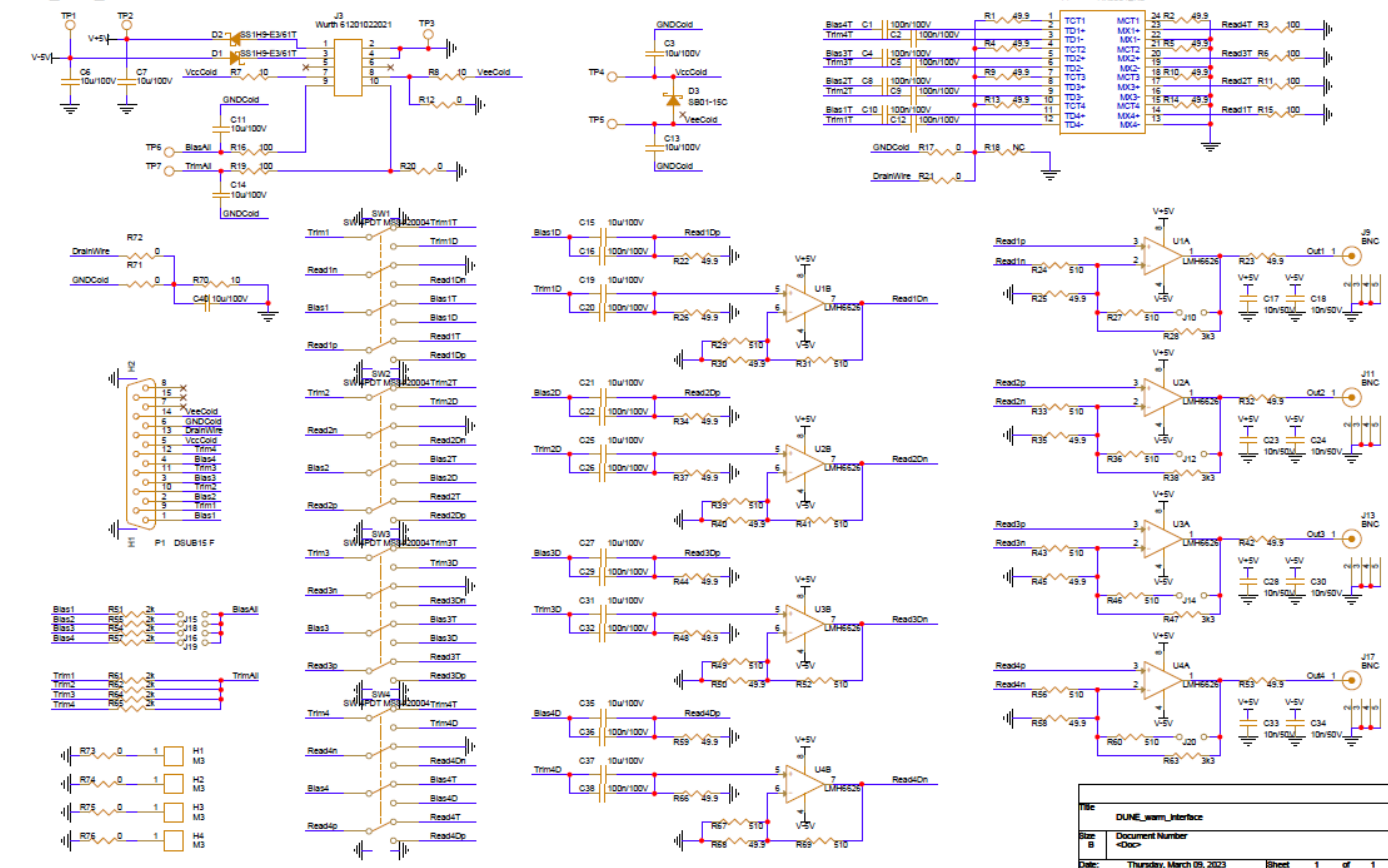
 
# Expected performance

- $S/N \approx 8$  with HPK SiPMs at 45V in LN2 (+3Vov)



# Lab instruments

- 0-60 V power supply for SiPM bias (current  $\approx$  negligible; better if low noise)
- 3.3V power supply for the cold amplifier (current  $\approx$  1mA / cold amplifier)
- +5V/-5V supply for the warm amplifiers (current  $\approx$  100 mA for the warm second stage v2)
- Oscilloscope or digitizer
- Pulsed LED

# Other readout options?

## DAPHNE

- Needs effort to setup and operate
- Limited availability
- Less flexible than oscilloscope
- Makes sense only if one needs to acquire more than 4 channels at a time

## Cathode electronics

- DCEM motherboard (several versions exist)
- Power over fiber (source+receiver)
- Signal over fiber (source+receiver)
- DCDC for SiPM bias voltage → fixed bias voltage (in most cases)