

Understanding performance of analog-to-digital converters for radiation detector systems

Gianni Mazza

INFN sez. di Torino

mazza@to.infn.it

October 10th, 2023

Outline

- Basic concepts on data conversion - a reminder
- Main ADC architectures
- Test of high performances ADC
- Case study

Outline

- Basic concepts on data conversion - a reminder
- Main ADC architectures
- Test of high performances ADC
- Case study


Motivations

- Detector outputs are typically analog signals
→ *however, they are processed digitally*
- A/D conversion is a critical processing step :
 - Several ADC architectures
 - Sampling frequency vs resolution trade-off
 - Converter maximum input frequency
 - Several ADC metrics (*INL, DNL, ENOB, SNR, SFDR, SNDR, ...*)
 - ADC complexity increases exponentially with resolution
- No "one fits all" solution
- Many ADCs concepts apply to TDCs as well

Analog-to-digital conversion

- Analog signals :
 - Infinite number of values in time (in a specific time range)
 - Infinite number of values in amplitude (in a specific amplitude range)
 - "Real life signals"
- Digital signals :
 - Finite number of values in time.
 - Finite number of values in amplitude.
 - Numerical representation of real life signals.
- Converting from analog to digital requires taking a limited number of samples of the signal with a limited amplitude resolution :
 - Time conversion \rightarrow sampling
 - Amplitude conversion \rightarrow quantization

Sampling

 

$$F_S = \frac{1}{T_S}$$

Sampling theorem

Question : what is the minimum sampling frequency F_S required to correctly represent a given signal ?


Answer (*Sampling theorem*) : for a signal with limited bandwidth B the minimum sampling frequency is given by :

$$F_S = 2 \times B$$


$\frac{F_S}{2}$ is called the Nyquist frequency of the converter.

Important : the Nyquist frequency is a theoretical limit !

Aliasing

 

 - The signal bandwidth must not exceed the $\frac{f_s}{2}$ limit
- Higher frequencies are mirrored on the baseband at different frequencies




- This is also true for disturbances entering in the ADC at the sampling switch

Quantization

For a converter with N bits and input range FS the quantization error (or quantization noise) is

$$Q_E = FS/2^N$$

$$\sigma = FS/(\sqrt{12} \times 2^N)$$

 


Power supply voltage and LSB

Modern CMOS technologies work with low power supply → ADC maximum full scale is reduced accordingly

Resolution	Voltage levels	LSB	
		(4 V FS)	(1 V FS)
2	4	1 V	250 mV
4	16	250 mV	62.5 mV
8	256	15.6 mV	3.9 mV
10	1024	3.91 mV	976.6 μ V
12	4096	976 μ V	244.1 μ V
16	65536	61.0 μ V	15.3 μ V
24	16777216	238 nV	59.6 nV



ADC performances vs process node

 


$$SNDR = 6.02 \times N + 1.78$$

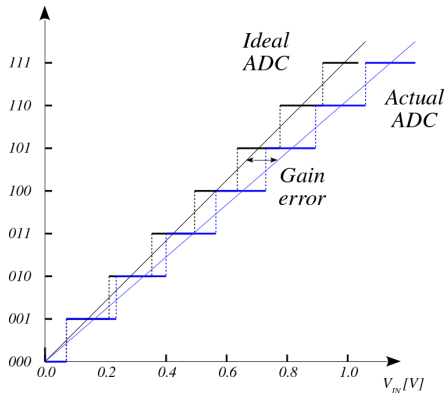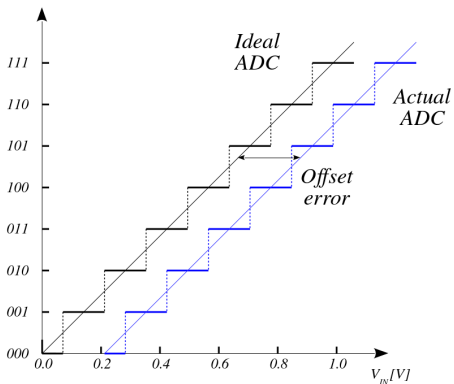B. Murmann, "ADC Performance Survey 1997-2023," [Available Online]


Errors in data conversion : offset and gain



Errors in data conversion : INL and DNL

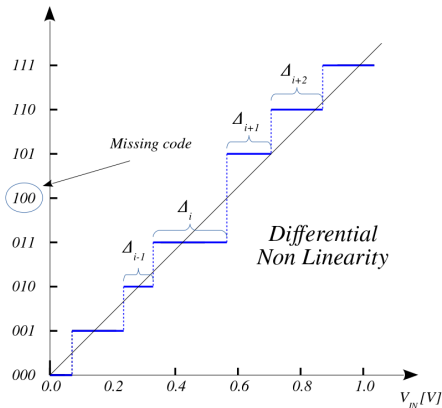

$$DNL(i) = \Delta_i - 1 \text{ LSB}$$

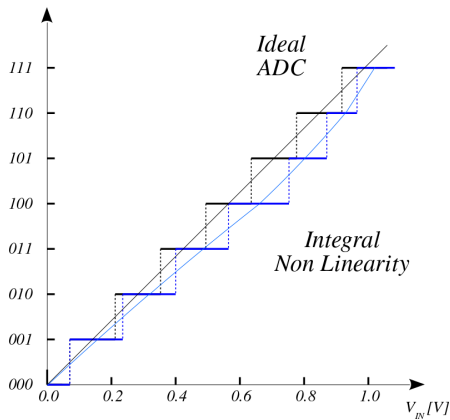

$$INL(i) = \sum_{j=0}^i DNL_j$$


Outline

- Basic concepts on data conversion - a reminder
- **Main ADC architectures**
- Test of high performances ADC
- Case study

Main ADC architectures



- Parallel converters
- Successive approximation converters
- Single and double ramp converters
- Δ - Σ converters
- Mixed techniques :
 - Dual stage converters
 - Pipelined converters
 - Time interleaved converters

Parallel (flash) converter

 

- Very fast : single step conversion
- Requires 2^N-1 (or $+1$) comparators
- Thermometric encoding
- Intrinsically monotonic ? *Not necessarily*
- S/H non required ? *Only at low signal frequencies*
- Typically limited to < 8 bits


Successive approximation converter

  

- Conversion time : $T_S + N \times T_{CK}$
- Requires 1 comparator and 1 N-bits DAC
- Binary encoding

- Strong dependence on the DAC quality
- Typical resolution 8-12 bits

Single slope converters

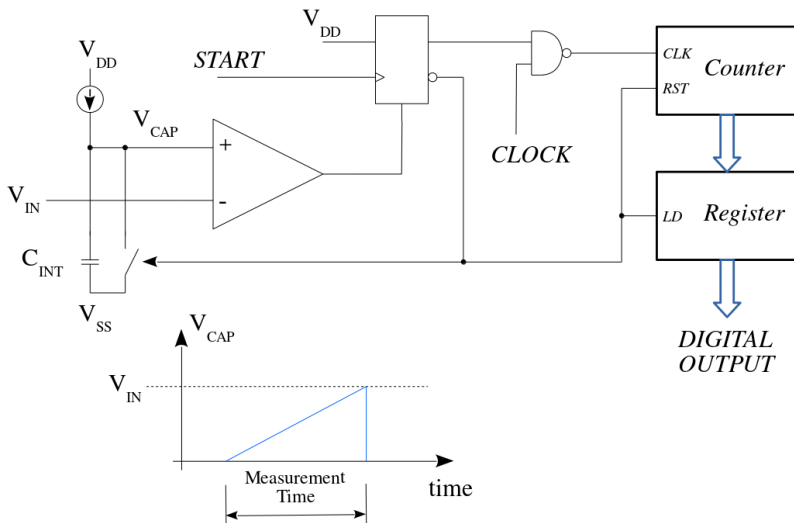

Single slope converter main points


- Signal dependent conversion time :

$$T_C = T_S + \frac{C V_{IN}}{I}$$

- Max conversion time : $T_S + 2^N \times T_{CK}$
- Very simple : requires 1 comparator and 1 precise integrator
- Binary encoding
- Depends on C and I absolute values
 - Calibration is mandatory in multi-channel systems
- High resolution, low sampling rate

→ *Can be very interesting in HEP applications where most samples are baseline ones*

Dual slope converters

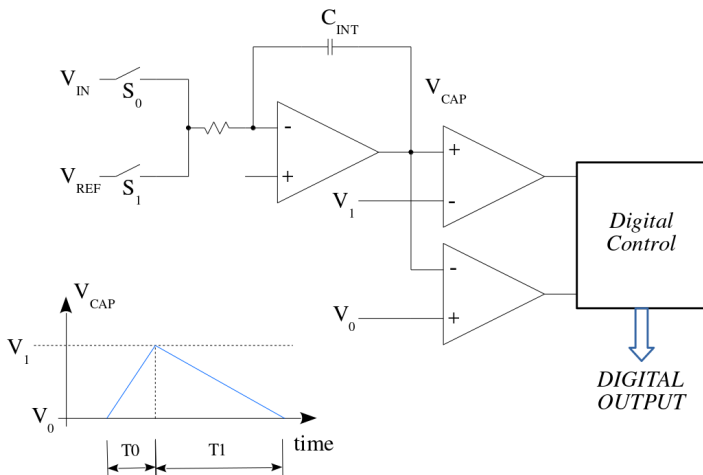



$$\frac{V_{IN} T_0}{RC_{INT}} = \frac{V_{REF} T_1}{RC_{INT}}$$
$$V_{IN} = V_{REF} \frac{T_1}{T_0}$$

Dual slope converter main points


- Signal dependent conversion time
- Max conversion time : $T_S + 2^{N+1} \times T_{CK}$
- Very simple : requires 1 comparator and 1 precise integrator
- Binary encoding
- Independent from C and R absolute values
- High resolution, low sampling rate

Oversampling

  
- Noise power is constant and distributed from 0 to $\frac{f_s}{2}$
- By oversampling and digitally filter the output part of the quantization noise can be removed
- The number of samples can be then reduced to f_s (decimation)
- $K = 2 \rightarrow 3$ dB gain
- $K = 4 \rightarrow 6$ dB gain (1 bit)



Noise shaping


 

 
$$V_{out} = \frac{A}{1+A} V_{in} + \frac{1}{1+A} e_n$$



- Continuous system : noise reduced by the open loop gain
- Discrete system : stable loop for $A < 1$ only
- $A < 1$ required for high frequency only
→ an integrator can be added to the loop


$\Delta - \Sigma$ converter

  

- First-order $\Delta - \Sigma$ converter
- $K=2$ oversampling ratio \rightarrow 6 dB noise reduction


- High order further improves noise shaping
- Typically orders above 2 are difficult to compensate

Comparison between architectures - 1

 


B. Murmann, "ADC Performance Survey 1997-2023," [Available Online]

Two-stages converter

 


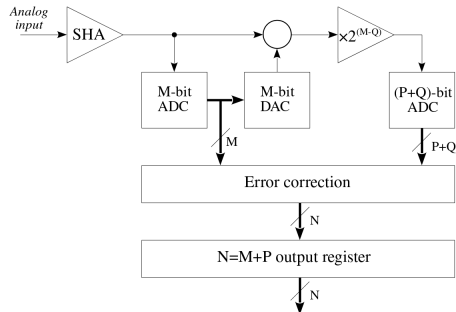- Conversion performed in two phases
- First ADC INL and DNL must be at N-bit level
- Residue amplifier design critical




- Q-bit redundancy can be added

Pipeline converter

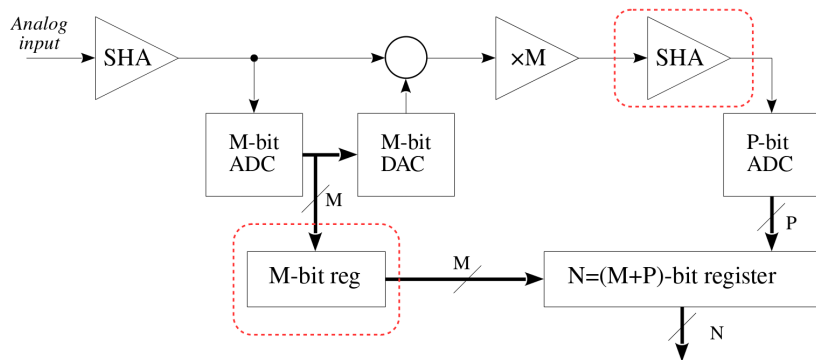


- With an extra S/H the two phases can be superimposed
- Max sampling rate is equal to the slowest of the two ADCs
- A latency is introduced
- Error correction techniques are usually implemented

Comparison between architectures - 2

 


B. Murmann, "ADC Performance Survey 1997-2023," [Available Online]

Time interleaved converters

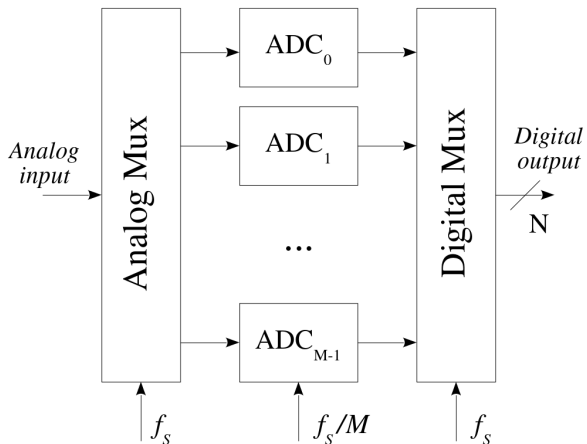

- Widely used in DSO
- Analog mux performances critical
- ADC intercalibration required

Comparison between architectures - 3

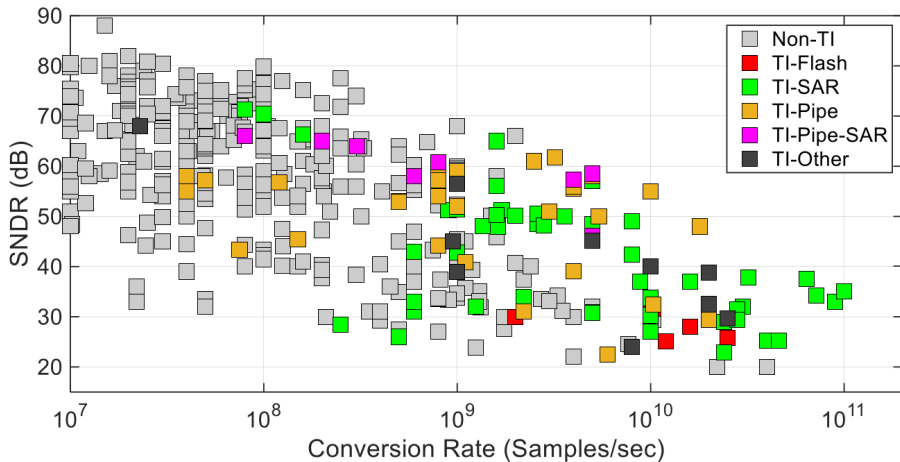


B. Murmann, "ADC Performance Survey 1997-2023," [Available Online]

Outline


- Basic concepts on data conversion - a reminder
- Main ADC architectures
- Test of high performances ADC
- Case study

Test with a higher resolution ADC

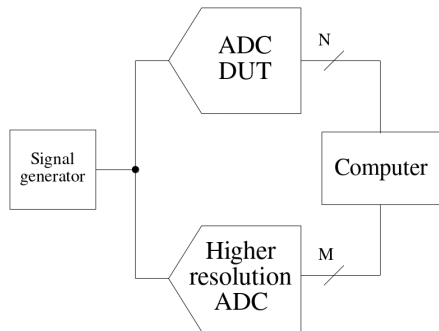


- Input signal split to the DUT and a reference ADC
- Reference ADC resolution :
 $M \geq N + 2$
- Requires a much better ADC for full speed testing
- Requires a proper input signal: must cover all codes

Test with a higher resolution DAC

 

- Input signal provided by a reference DAC - no need of a precise signal source
- Reference DAC resolution : $\geq N + 2$
- DAC performances are typically better than ADC ones

Histogram (Code Density) Test

 

- Collect M_T total samples for codes 1 to $2^N - 2$
- Count number of occurrences of each code, $h(n)_{ACTUAL}$
- The theoretical number of occurrences is :


$$h(n)_{THEOR} = \frac{M_T}{2^N - 2}$$

- Calculate DNL of each code as :

$$DNL(n) = \frac{h(n)_{ACTUAL}}{h(n)_{THEOR}} - 1$$

- Integrate DNL to obtain INL



Histogram for Linear Ramp Test

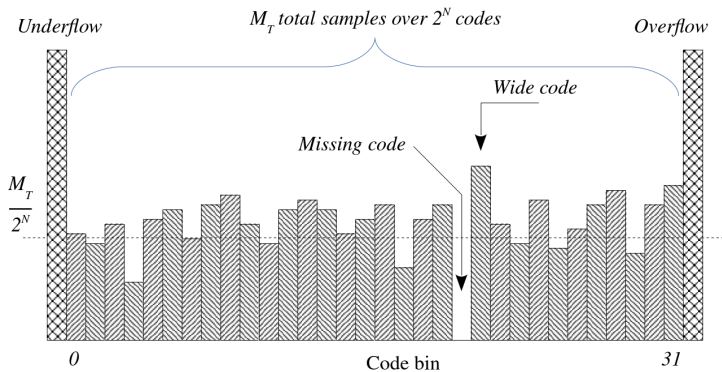

Practical considerations

- **Number of samples :**
 - With M hits per code bin, DNL resolution is $1/M$
 - For a N -bits ADC, $M_T = 2^N \times M$
 - Example : 8 bits, 50 MS/s, $M = 20$ (5% error on LSB) : $M_T=5120$,
 $T_{measure}=102.4 \mu s$
 - Example : 12 bits, 1 MS/s, $M = 20$ (5% error on LSB) : $M_T=81920$,
 $T_{measure}=81.92 \text{ ms}$
- For high performances ADCs is very difficult to generate a ramp with the required performances → A **sinewave** is normally used
 - High quality passive filters to improve the signal
 - Code distribution is not constant anymore
- **Important** : frequency of the input wave must not be a sub-harmonic of the ADC sampling clock


Histogram for Sinewave Test

  

$$V_{IN} = A \sin(\omega t)$$

$$p(n) = \frac{1}{\pi} \left\{ \sin^{-1} \left[\frac{V_{FS}(n - 2^{N-1})}{A \cdot 2^N} \right] - \sin^{-1} \left[\frac{V_{FS}(n - 1 - 2^{N-1})}{A \cdot 2^N} \right] \right\}$$

Sinewave Test setup

 

- Key points :
 - Input signal specs
 - Clock specs
 - Data transmission

Methodology for ADC characterisation

- Histogram method :
 - The ADC codes distribution is obtained by non-coherently sampling the sinewave input
 - From this distribution, the transition voltages can be derived, and with them the DNL, INL and missing codes
- FFT method :
 - The Fast Fourier Transform of the signal is computed.
 - ENOB, SNDR, SFDR and other noise-related parameters in the frequency domain can be measured
- Fit method :
 - A 4 parameters sinewave fit is applied to the ADC samples
 - The fit-sample residuals distribution is reconstructed and used to calculate the noise-related parameters ENOB and SNDR

Sinewave Test calculations

$$V_O = \frac{\pi}{2} \sin \frac{N_P - N_N}{N_T}$$

$$CH(i) = \sum_{j=0}^i H(j)$$

$$V(i) = \cos\left(\frac{\pi CH(i)}{N_T}\right)$$


$$INL(i) = \frac{V(i) - V(1)}{1 \text{ LSB}} - (i - 1)$$

$$DNL(i) = \frac{V(i+1) - V(i)}{1 \text{ LSB}}$$

- N_P, N_N : number of samples above/below midrange
- $N_T = N_P + N_N$
- V_O : offset voltage

Reference : *J. Doenberger et al.*
Full-Speed Testing of A/D Converters
IEEE J. Solid-State Circuits, vol 19, n. 6, Dec 1984

ENOB measurement - from FFT

 


- SNDR or SINAD : Signal to Noise and Distorsion Ratio
- SNR : Signal to Noise Ratio
- ENOB : Effective Number of Bits

$$ENOB = \frac{SNDR - 1.78dB}{6.02}$$

- THD : Total Harmonic Distorsion

ENOB	SNDR	ENOB	SNDR	ENOB	SNDR
4 b	25.86 dB	8 b	49.94 dB	12 b	74.02 dB
6 b	37.90 dB	10 b	61.98 dB	16 b	98.10 dB

ENOB measurement - from fit

 

$$ND = \sqrt{\frac{1}{M} \sum_{n=1}^M (x[n] - x'[n])^2}$$

$$SNDR = \frac{A_{rms}}{ND} = \frac{A_p}{ND\sqrt{2}}$$

$x[n]$: sample data set

$x'[n]$: best fit data set

M : number of samples

Relations between INL, DNL, SFDR and SNR

INL and SFDR

- Type of distortion depend on the INL shape
- Rule of thumb

$$SFDR = 20 \log \left(\frac{2^N}{INL} \right)$$

DNL and SNR

Assuming:


- Uniform DNL distribution
- No missing codes

$$SNR = \frac{\frac{1}{2} \left(\frac{2^N LSB}{2} \right)^2}{\frac{LSB^2}{12} + \frac{DNL^2}{3}}$$

Please do not forget that...

- A converter does not just have one input pin but also :
 - Clock
 - Power supply and ground
 - Reference Voltage
- For good practices on how to avoid issues see e.g.:
 - Analog Devices Application Note 345: *Grounding for Low-and-High-Frequency Circuits*
 - Maxim Application Note 729: *Dynamic Testing of High-Speed ADCs*
- More details in:
 - IEEE Standard for Terminology and Test Methods for Analog-to-Digital Converters - *IEEE Std 1241TM - 2010*


Effects of jitter on the sampling clock

 

Jitter on the sampling clock adds an error voltage proportional to the product between the time jitter and the input signal slope

$$\sigma_V = \sigma_T \frac{\Delta V}{\Delta t}$$

Maximum SNR vs input frequency

 

$$SNR_{max} = 20 \log_{10} \left(\frac{1}{2\pi f_{sig} t_j} \right)$$

$$ENOB_{max} = \frac{SNR_{max} - 1.76}{6.02}$$

f_{sig} : signal frequency

t_j : r.m.s. jitter

N : number of bits

- Note 1 : here we have the **signal** (not the **sampling**) frequency
- Note 2 : this is a worst case. Typical signals have a frequency spectra

How to readout the bits

- Full swing CMOS signaling works well for $f_{CLK} < 100\text{MHz}$. For higher frequencies:
 - Uncontrolled characteristic impedance
 - High swing \rightarrow higher level of spurious coupling to other signals
 - High power consumption
- Alternative to CMOS: LVDS (Low Voltage Differential Signaling)
- LVDS vs CMOS:
 - Higher speed, more power efficient at high speed
 - Two pins/bit


Typical ADC metrics

- 1 Gain error : difference between the expected and actual slope of the transfer function
- 2 Offset error : difference between the expected and actual intercept of the transfer function
- 3 DNL (Differential Non-Linearity) : difference between an actual step width and the ideal value of 1 LSB.
- 4 INL (Integral Non-Linearity) : deviation of the values on the actual transfer function from the ideal linear fit.
- 5 SNDR or SINAD (Signal to Noise and Distorsion Ratio) : ratio of the rms signal amplitude to the mean value of the root sum square of the other spectral components, excluding DC.
- 6 SNR (Signal to Noise Ratio) : the same as SNDR but without signal harmonics
- 7 ENOB (Effective Number Of Bits) : equivalent to SNDR.
- 8 SFDR (Spurious Free Dynamic Range) : ratio between the rms signal amplitude to the rms amplitude of the highest harmonic.
- 9 THD (Total Harmonic Distorsion) : ratio between the rms value of the signal amplitude to the mean value of the root sum square of its harmonics.

Outline


- Basic concepts on data conversion - a reminder
- Main ADC architectures
- Test of high performances ADC
- **Case study**

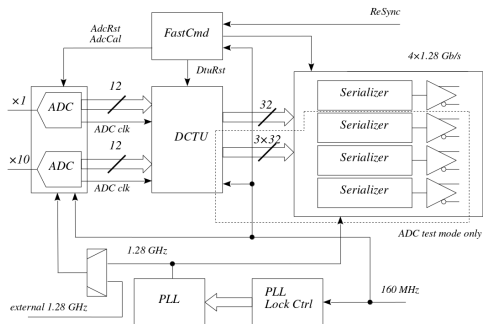Case study : LiTE-DTU - Data Conversion, Compression and Transmission ASIC for the CMS ECAL




- Two 12 bits, 160 MS/s ADCs
- Clock multiplication PLLs
- I²C interface for slow control (*not shown*)
- Technology : CMOS 65 nm

- Data Compression and Transmission Unit
- Fast command and lock control units
- 1.28 Gb/s serializers

 


ADC IP

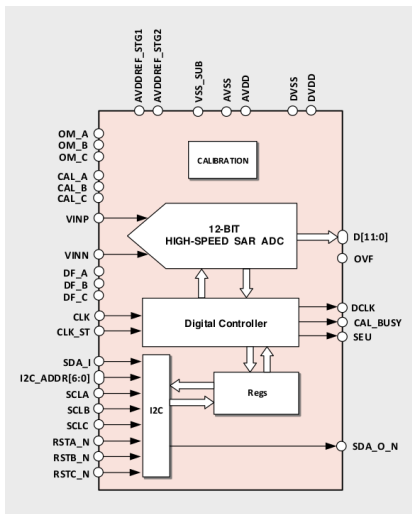

- Designed by Dialog Semiconductor
- 12 bits, 160 Mb/s
- Two 80 MS/s cores in time interleaving
- Cores based on the successive approximation technique
- Foreground calibration, calibration time 167.3 μ s
- Working frequency 1.28 GHz
- Sampling frequency 160 MHz
- Triplicated digital control signals
- SEU-protected I²C interface and registers
- ENOB \geq 10.1
- Power \leq 10.5 mW (\sim 9 μ W in power down mode)

ADC test mode

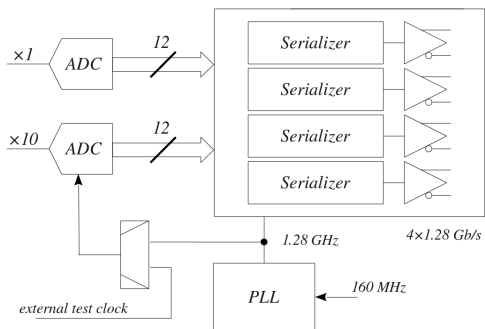


In ADC test mode :


- bypass of the compression logic
- Four 1.28 Gb/s links active
- Samples packed in 32 bit words
- 4 bit patterns in fixed position to simply word alignment
- Allows independent test of ADCs
- Activated by the ATM CMOS input

Bits	31:28	27:16	15:12	11:0
Dout0	0011	ADC H (i+3)	1001	ADC H (i+1)
Dout1	0110	ADC H (i+2)	1100	ADC H (i)
Dout2	1100	ADC L (i+3)	0110	ADC L (i+1)
Dout3	1001	ADC L (i+2)	0011	ADC L (i)


Test Set-up

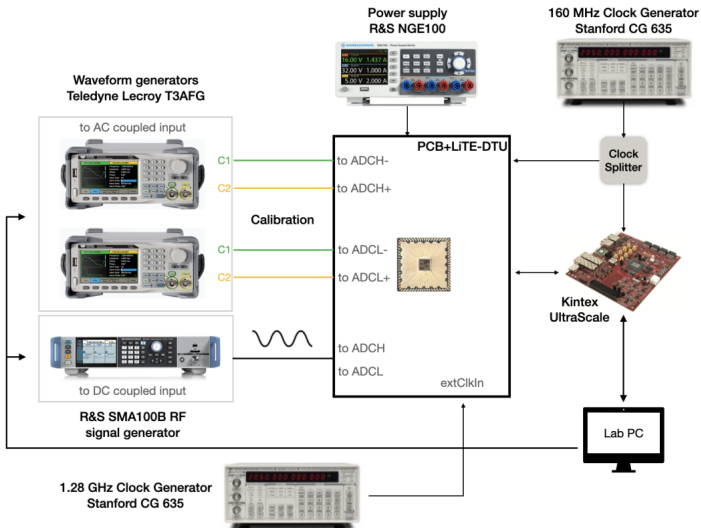

Interleaving errors

 


FFT - 500 kHz

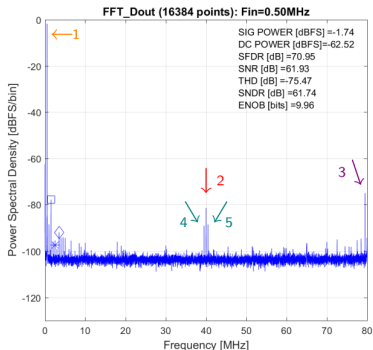

500 kHz FFT with internal clock

 
- 1: $f_{in} = 500$ kHz
- 2: 40 MHz spurs
- 3: $f_S/2 \pm f_{in}$
- 4 and 5: 40 MHz $\pm f_{in}$



500 kHz FFT with external clock


- 1: $f_{in} = 500$ kHz
- 2: 40 MHz spurs
- 3: $f_S/2 \pm f_{in}$

FFT - 10.7 MHz

 

10.7 MHz FFT with internal clock

 
- 1: $f_{in} = 10.7$ MHz
- 2: 40 MHz spurs
- 3: $f_S/2 \pm f_{in}$
- 4 and 5: $40 \text{ MHz} \pm f_{in}$



10.7 MHz FFT with external clock


- 1: $f_{in} = 10.7$ MHz
- 2: 40 MHz spurs
- 3: $f_S/2 \pm f_{in}$

FFT - 40 MHz

 

40 MHz FFT with internal clock

 
- 1: $f_{in} = 40$ MHz
- 2: 40 MHz spurs
- 3: $f_S/2 \pm f_{in}$
- 4 and 5: 40 MHz $\pm f_{in}$



40 MHz FFT with external clock


- 1: $f_{in} = 40$ MHz
- 2: 40 MHz spurs
- 3: $f_S/2 \pm f_{in}$

FFT - 50 MHz

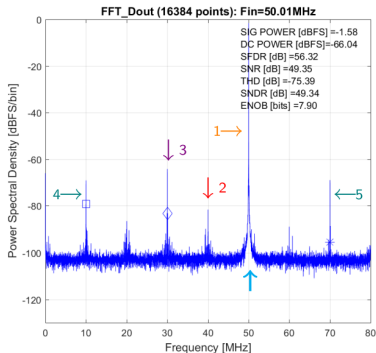

50 MHz FFT with internal clock

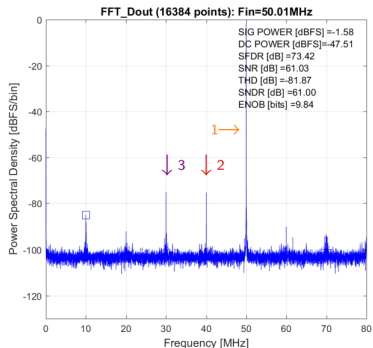
- 1: $f_{in} = 50$ MHz
- 2: 40 MHz spurs
- 3: $f_S/2 \pm f_{in}$
- 4 and 5: 40 MHz $\pm f_{in}$



50 MHz FFT with external clock


- 1: $f_{in} = 50$ MHz
- 2: 40 MHz spurs
- 3: $f_S/2 \pm f_{in}$

FFT @ 50 MHz : TPS78601 vs ADP7158

 

TPS78601 → blue curve, ADP715 → red curve

ADC test : ENOB vs F_{IN}

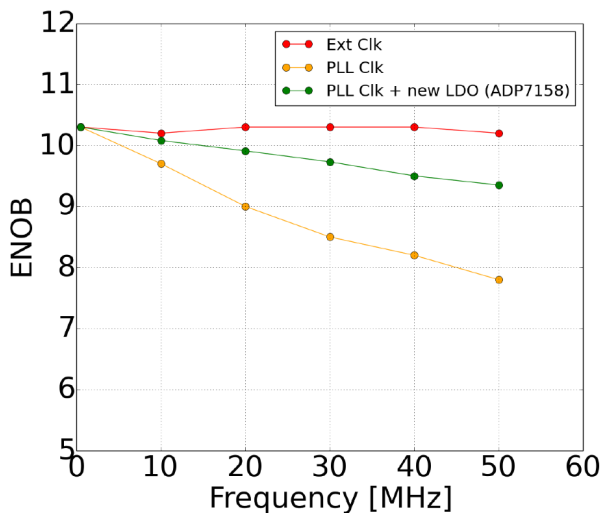

- Strong dependence on voltage regulator on PIIVddRF

Conclusions

- High-performances A/D converters are an essential component of an integrated readout electronics
- In HEP experiments, calorimeters are typically the more demanding application for ADCs.
- Modern converters can provide both high resolution and high sampling frequencies
- Modern technologies are powered at ~ 1 V voltages \rightarrow LSB can in the μV range \rightarrow noise is critical
- Clock jitter requirements can be very challenging to obtain

- **J. Doenberger et al., Full-Speed Testing of A/D Converters**
IEEE J. Solid-State Circuits, vol 19, n. 6, Dec 1984
- **Defining and Testing Dynamic Parameters in High-Speed ADCs**
Maxim Tutorial 728
- **Dynamic Testing of High-Speed ADCs**
Maxim Tutorial 729
- **IEEE Standard for Terminology and Test Methods for Analog-to-Digital Converters**
IEEE Std 1241TM - 2010