



AKADEMIA GÓRNICZO-HUTNICZA
IM. STANISŁAWA STASZICA W KRAKOWIE
AGH UNIVERSITY

Low power, high accuracy ADCs and TDCs

Jakub Moroń^A

M. Firlej^A, T. Fiutowski^A, M. Idzik^A, S. Kulis^B, A. Molenda^A, K. Świentek^A

A) AGH University of Krakow, Poland

B) CERN


This research was funded by the National Science Centre, Poland, under the grant no. 2021/43/B/ST2/01107

XII Front-End Electronics Workshop, 12-16 June 2023, Torino, Italy

- 10b ADC in CMOS 130nm and 65nm
 - Motivation
 - Architecture considerations
 - ADC design
 - Measurement results
 - Static and dynamic metrics
 - Power consumption
 - Radiation hardness
- TAC (Time to Analogue Converter)-based TDC
 - Architecture and design
 - Post-layout simulation results
 - ~~Measurement results~~ (*no data yet...*)
- Summary

Demands for readout electronics in high energy physics experiments are constantly rising:

 - Higher luminosity – more events – more data
- Calorimetry – needs amplitude measurement and digitization:
 - ADC (FE pulse maximum)
 - TDC (FE pulse time over threshold)



- Increasing complexity of event reconstruction starts to require:
 - Amplitude measurements in trackers (e.g. Upstream Tracker in LHCb)
 - 4-D detectors (pixel detector with precise timing measurement) *not in scope of this talk*
- Putting an ADC in each readout channel fairly not possible in the past:
 - Large power consumption (much higher than analogue FE)
 - Large die area


ADC

Various features/parameters are important in ADC design/applications: effective resolution (ENOB), power, sampling frequency, area, etc... and can be used to create the “Figure Of Merit” (FOM) for ADC



- Walden FoM [Walden, 1999] $FoM_W = \frac{P}{f_s \cdot 2^{ENOB}}$
- Schreier FoM (DR) [Schreier, 2005] $FoM_{S,DR} = DR + 10 \log \left(\frac{BW}{P} \right)$
- Schreier FoM (SNDR) [Ali, 2010] $FoM_S = SNDR + 10 \log \left(\frac{f_s/2}{P} \right)$

FoM_W is often given as:

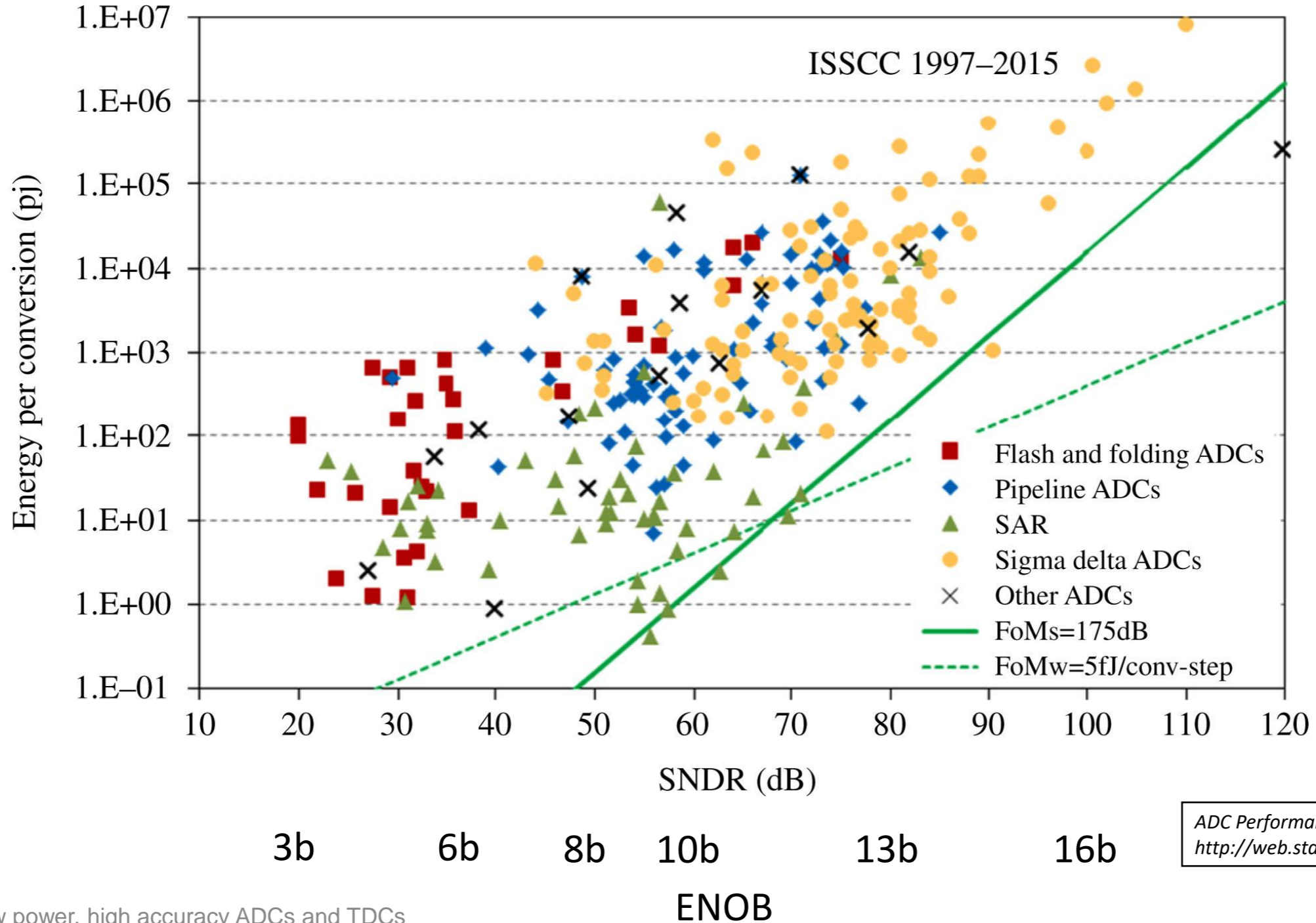- FoM_W^{hf}, measured at input sine with almost Nyquist frequency
- FoM_W^{lf}, measured at lower input frequency




 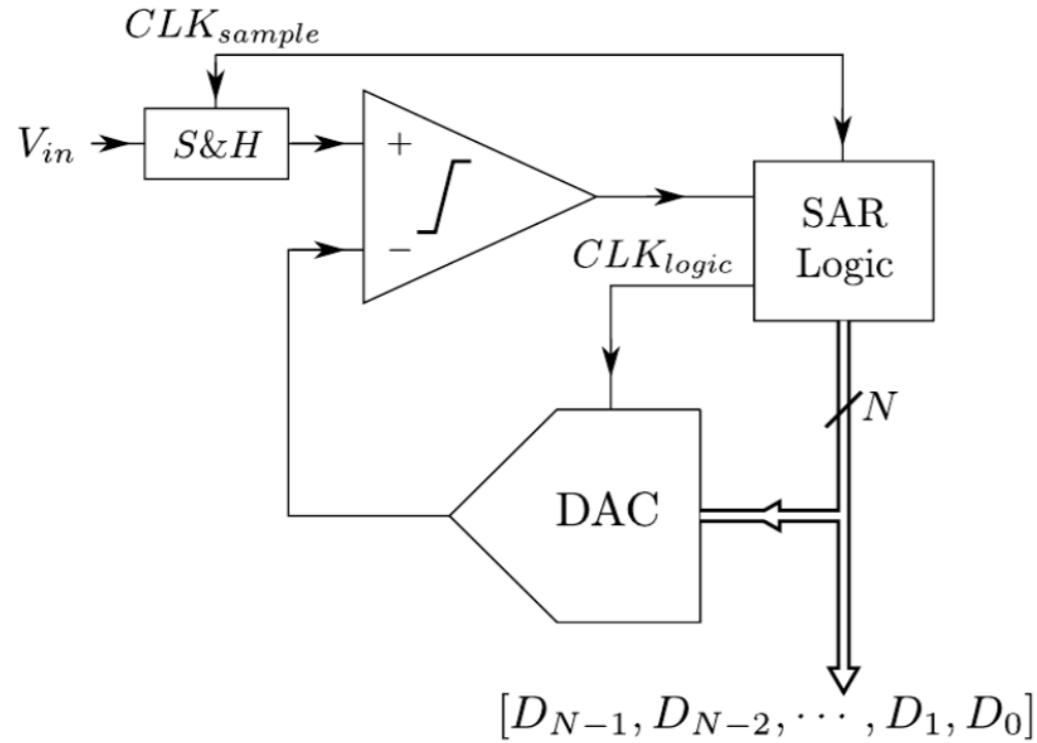ADC Performance Survey 1997-2015, B. Murmann
<http://web.stanford.edu/~murmann/adcsurvey.html>



- Comparison between sampled input voltage and DAC output voltage
- Comparison result → changes DAC output voltage closer to the input sample
- Each consecutive voltage change is half of the previous one
- Operation repeated N times for N-bit ADC

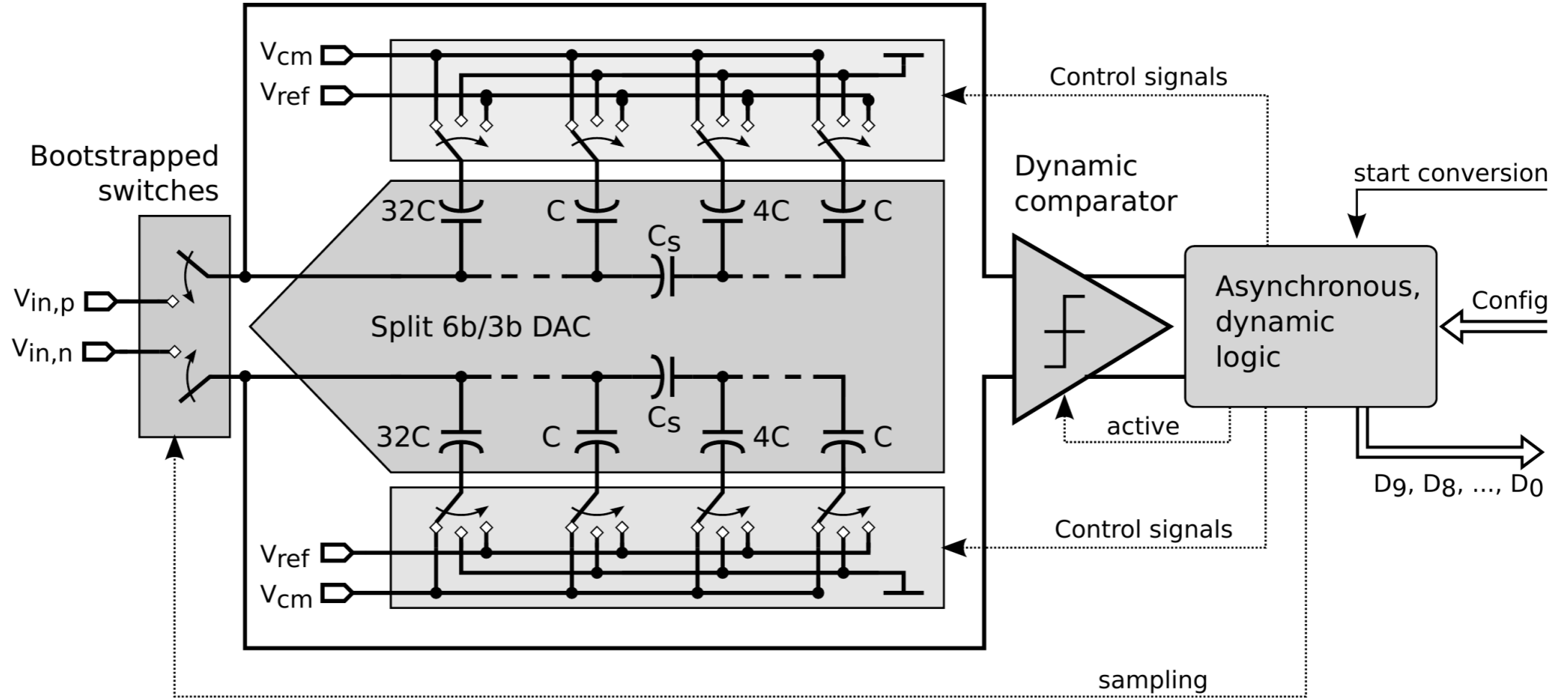- + Power and area-efficient architecture – same circuitry used in loop N-times
- + Contains: one comparator, two DACs (differential) and SAR logic – fits well to modern digital CMOS
- + DAC network usually capacitive - no static power, serves also as S/H circuit
- Limited conversion rate




Architecture of 10-bit ADC

Differential segmented/split DAC with MCS switching scheme – ultra low power

Dynamic comparator – no static power consumption, power pulsing for free


Asynchronous logic – no clock tree – power saving, allows asynchronous sampling

Planar capacitor – MIMcap

 

- Available in both technologies
- Lower capacitance density
- Well defined matching parameters
- Smaller parasitics (especially to bulk)
- Minimal capacitance
 - 26.2 fF in CMOS 130 nm
 - 9.9 fF in CMOS 65 nm

Vertical capacitor – MOM

 

- Available only in CMOS 65 nm
- Higher capacitance density
- Matching given by MC simulations
- Large parasitics (especially to bulk)
- Minimal capacitance of 2.5 fF

Two subjects have to be considered in terms of capacitive DAC design:

- Thermal noise
- Matching


Thermal noise is given by

$$\frac{kT}{C_{total}} < \frac{\sigma^2}{12}, \quad \sigma = \frac{V_{ref}}{2^N} \Rightarrow C_{total} > 12kT \left(\frac{2^N}{V_{ref}} \right)^2$$

For $V_{ref} = 1 \text{ V}$, $T = 293 \text{ K}$

- $N = 6\text{b}$, $C > 0.2 \text{ fF}$
- $N = 8\text{b}$, $C > 3.2 \text{ fF}$
- $N = 10\text{b}$, $C > 51 \text{ fF}$
- $N = 12\text{b}$, $C > 815 \text{ fF}$
- $N = 16\text{b}$, $C > 209 \text{ pF}$

 Thermal noise is negligible
for medium resolution ADC



To reduce total capacitance, N-bit DAC can be split into two sub-DACs, connected via series unit capacitor

$$C_u > \frac{9}{2\sqrt{2}\sigma_{Limit}^2} 2^{2L}(2^M - 1)K_\sigma^2 K_C$$

K_σ [% μm] Matching parameter

K_C $\left[\frac{fF}{\mu m^2} \right]$ Capacitance density



C_u – minimal unit capacitance ensuring $3\sigma_{DNL} < \sigma_{Limit}$ (0.5 LSB assumed)

C_u cannot be smaller, than the technology limit


65 nm offers ~2.5 smaller minimal capacitance (9.9 fF vs 26.2 fF)

130 nm offers a slightly better matching

  - 6-1-3 and 5-1-4, both with minimal 26.2 fF capacitor as C_u configurations selected for 130 nm
- 6-1-3 with minimal 9.9 fF capacitor as C_u selected for 65 nm




 - DAC 613 MIMcap**
130nm / 65nm
 $C_u = 26.2 / 9.9 \text{ fF}$
 $C_{in} = 1.68 / 0.64 \text{ pF}$




6-1C-3

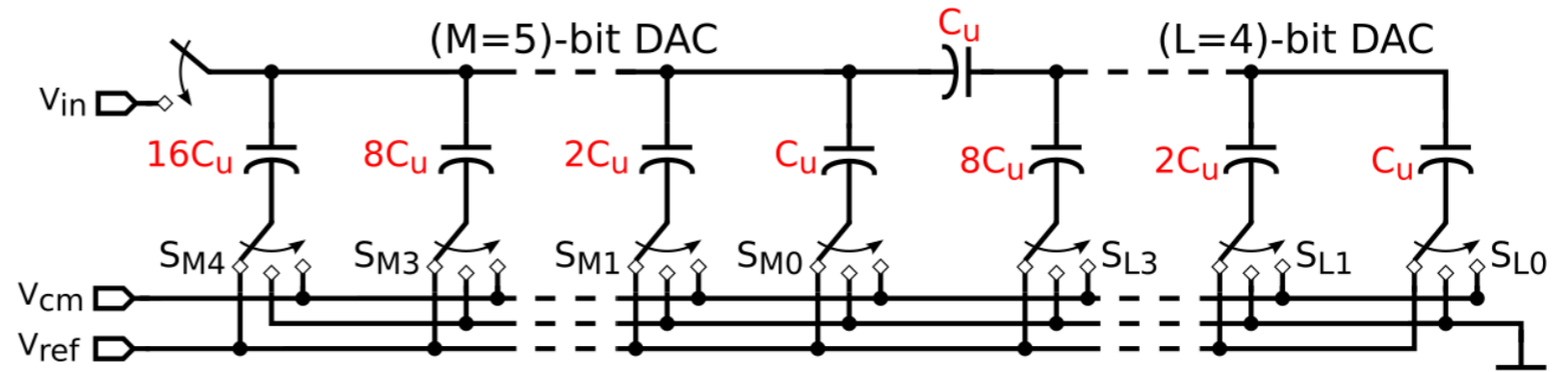- DAC 514 MIMcap**
130nm only
 $C_u = 26.2 \text{ fF}$
 $C_{in} = 0.84 \text{ pF}$



5-1C-4

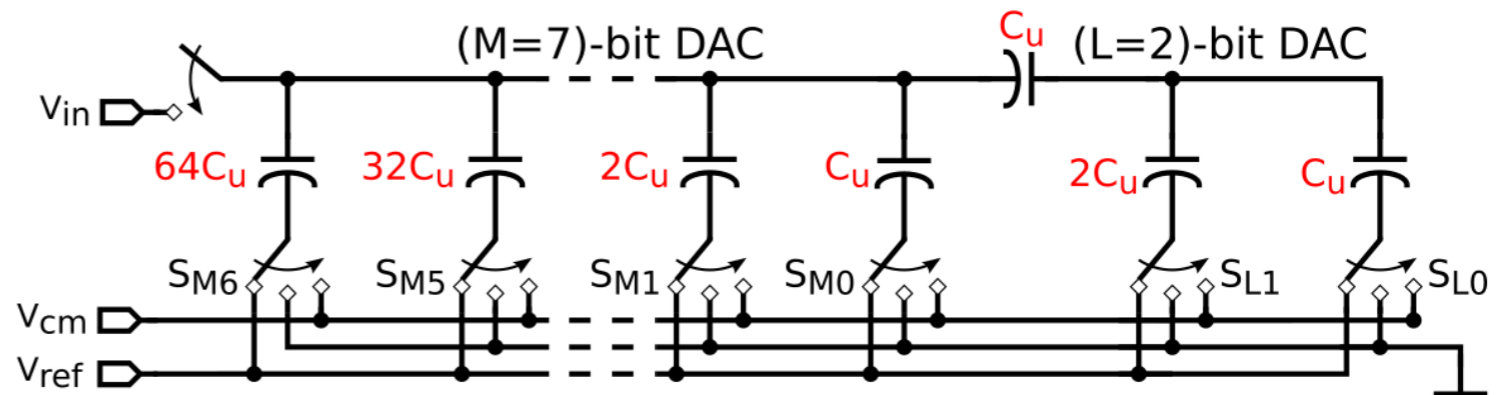- DAC 712 MOMcap**
65nm only
 $C_u = 4.6 \text{ fF}$
 $C_{in} = 0.59 \text{ pF}$



7-1C-2

“Typical” SAR ADC requires bit cycling clock

- For 10b ADC working at 50 MSps, at least 500 MHz (1 GHz in reality) needed


Such bit cycling clock have to be generated (PLL) and distributed in the ASIC – large power consumption.



Asynchronous, “event-driven” logic does not need bit cycling clock, so can save a lot of power.

Additionally, asynchronous logic requires a “start conversion” signal, not a sampling clock, so ADC can sample input signal asynchronously.

There are two downsides of the asynchronous logic:

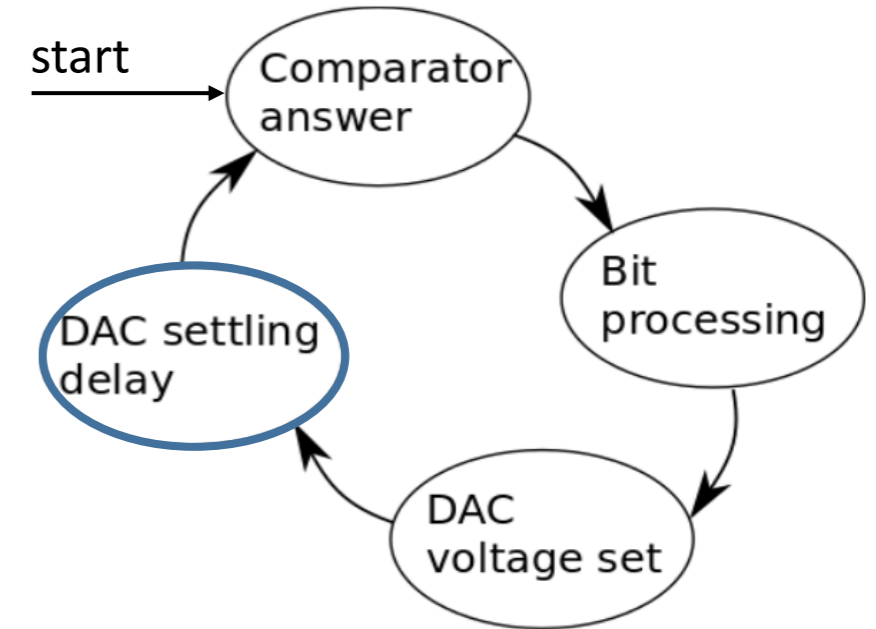- It have to be designed and simulated manually (no automatic synthesis and implementation)
- It needs to have a “settling delay” (see next slide) implemented




  

- Making settling time equal for each bit almost impossible
- Constant settling delay for each bit → a lot of time wasted...
- Variable (and configurable) settling delay implemented


Bit no.	9	8	7	6	5	4	3	2	1
Group	D9	D87		D65		D41			

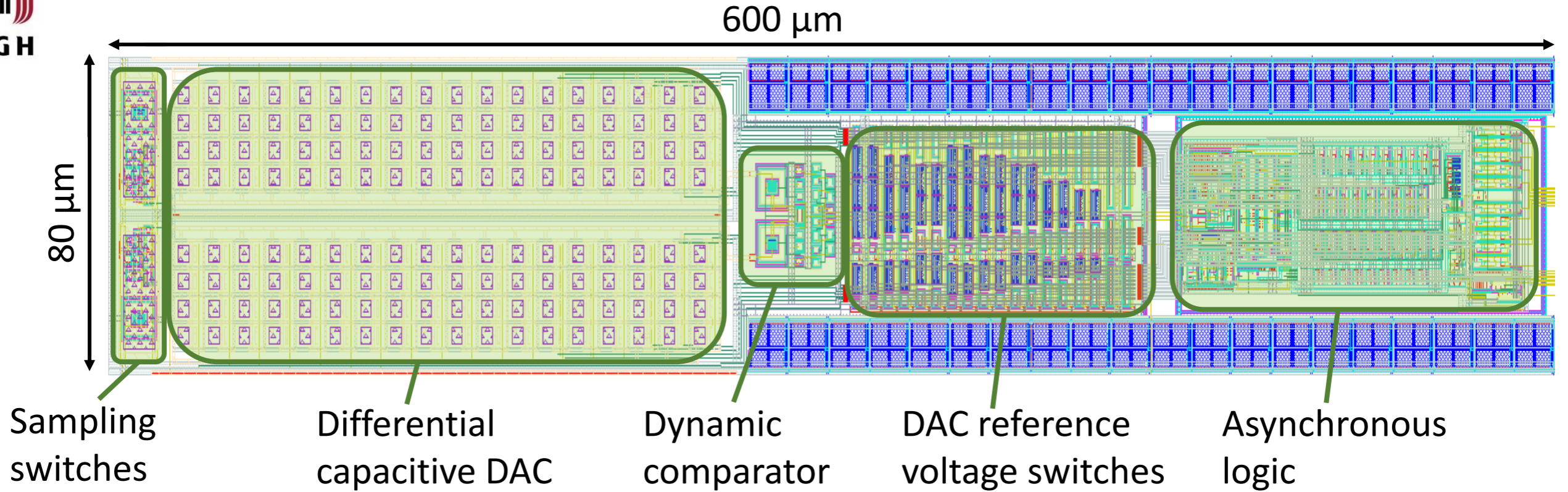Delay for each group set individually via slow control 3-bit register, with 175 ps/bit resolution in 130nm, ~120 ps/bit in 65nm




MIM 613 (514 is nearly identical) layout in 130 nm

 - Designs ready for multichannel ASIC with pitch 160 μm (80 μm ADC core + 80 μm decoupling)



335 μm

60 μm

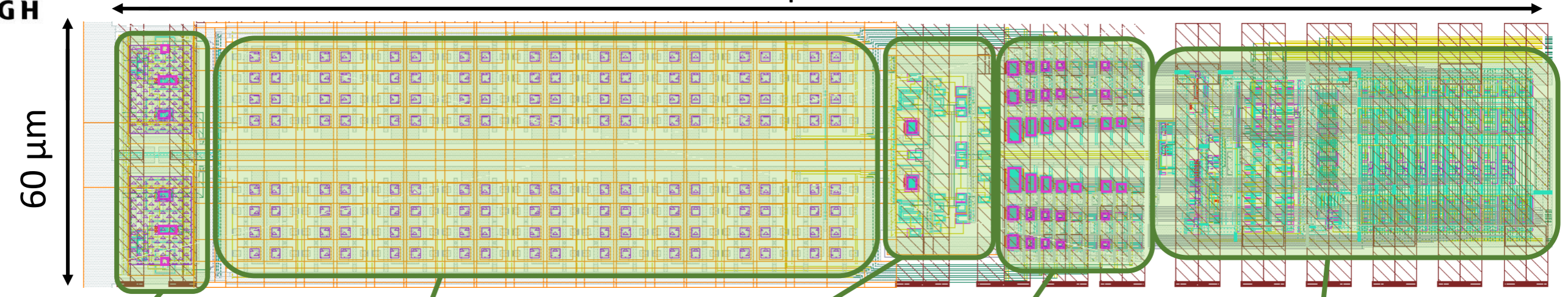

Sampling switches

Differential capacitive DAC

Dynamic comparator


DAC reference voltage switches

Asynchronous logic

MIM (top) and MOM (bottom) layouts in 65 nm


- Multichannel ready

60 μm

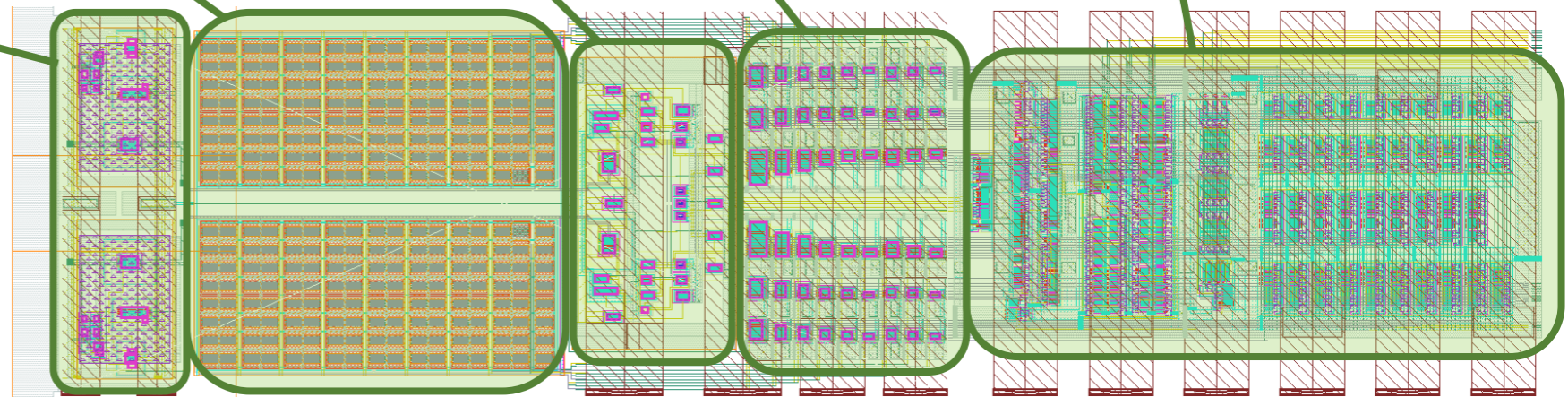


240 μm

ADC measurement setup

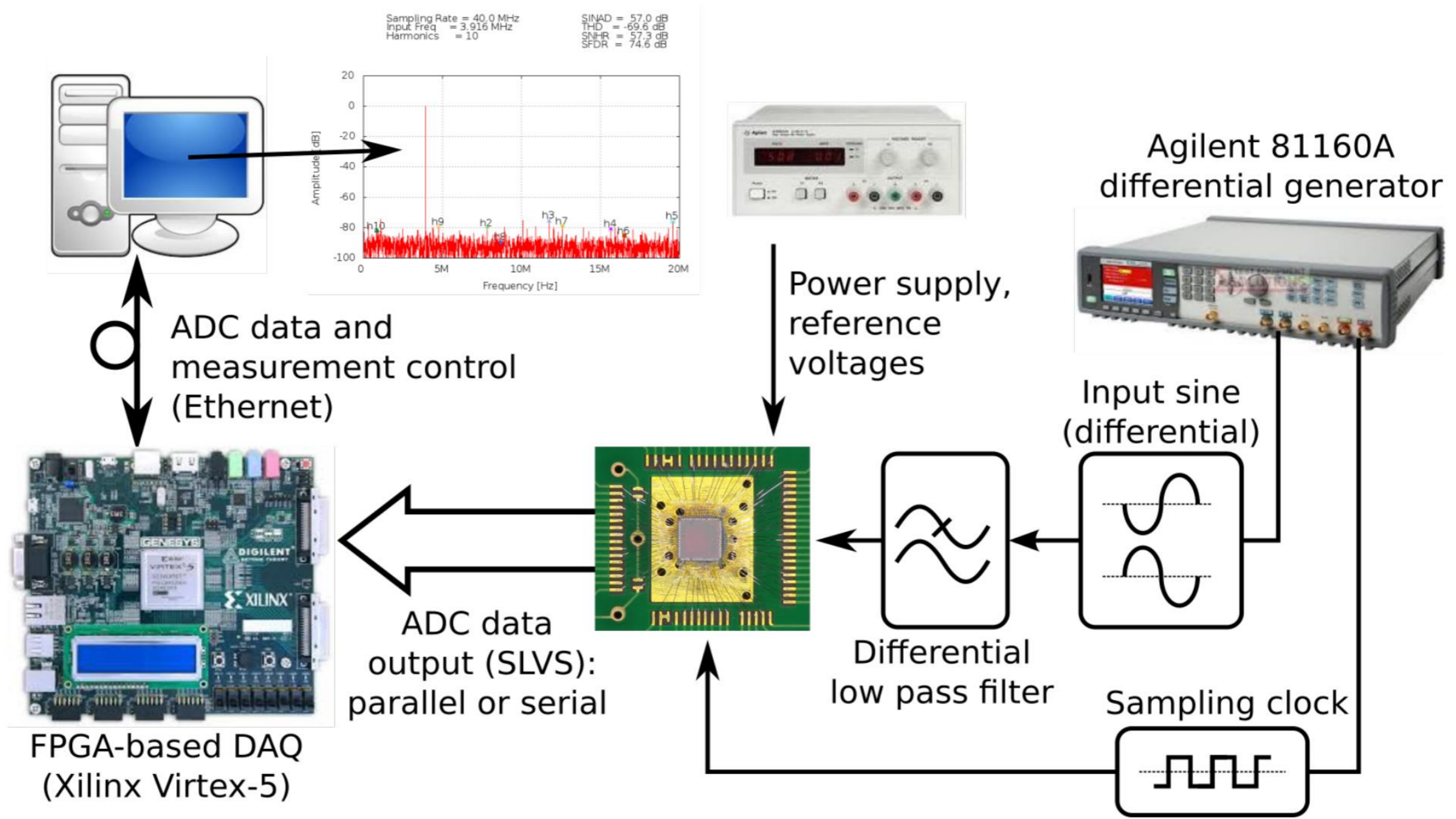


130 nm MIM 613

 


$-0.22 < \mathbf{DNL} < 0.20$
 $-0.30 < \mathbf{INL} < 0.40$
 Static **ENOB** = 9.92

130 nm MIM 514

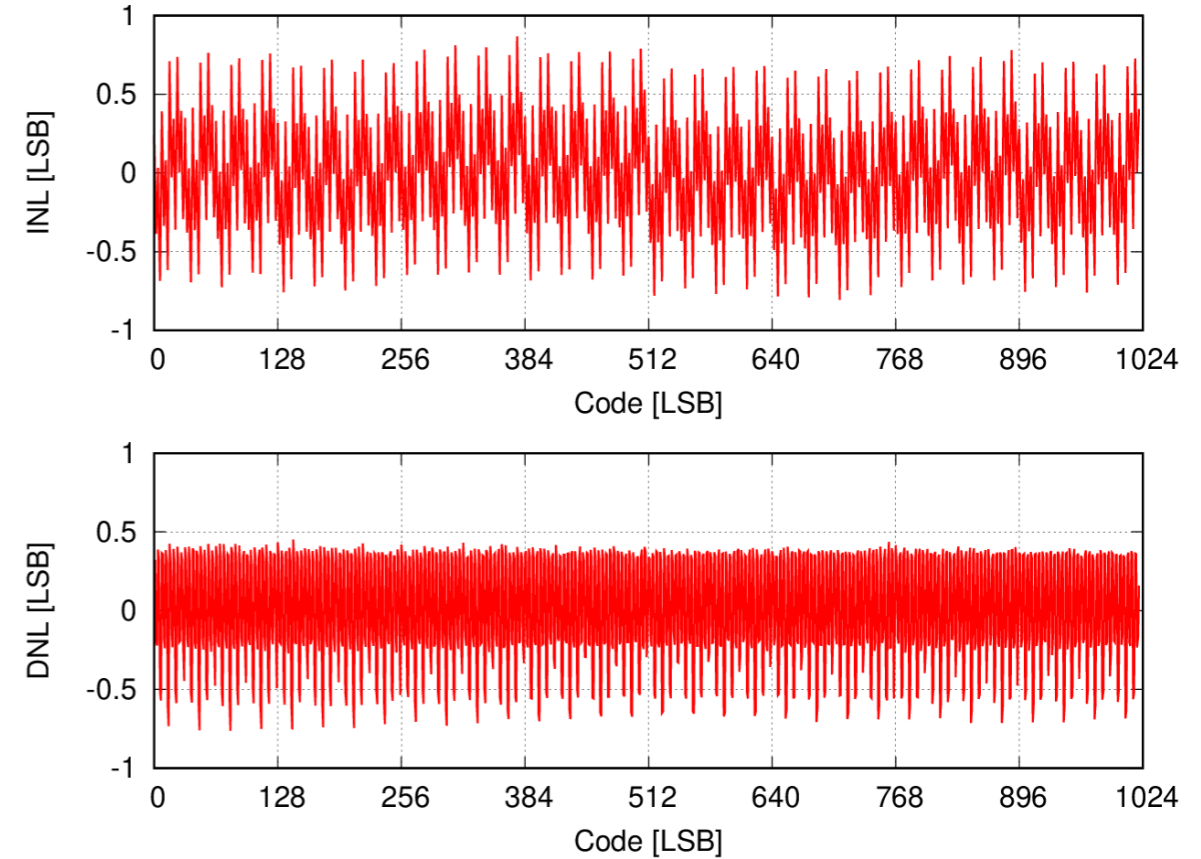

$-0.70 < \mathbf{DNL} < 0.44$
 $-0.87 < \mathbf{INL} < 0.81$
 Static **ENOB** = 9.37


65 nm MIM 613

 

$-0.75 < \mathbf{DNL} < 0.40$
 $-0.80 < \mathbf{INL} < 0.82$
 Static **ENOB** = 9.40

Unexpected large INL step in the middle due to the overlooked parasitic capacitance

65 nm MOM 712

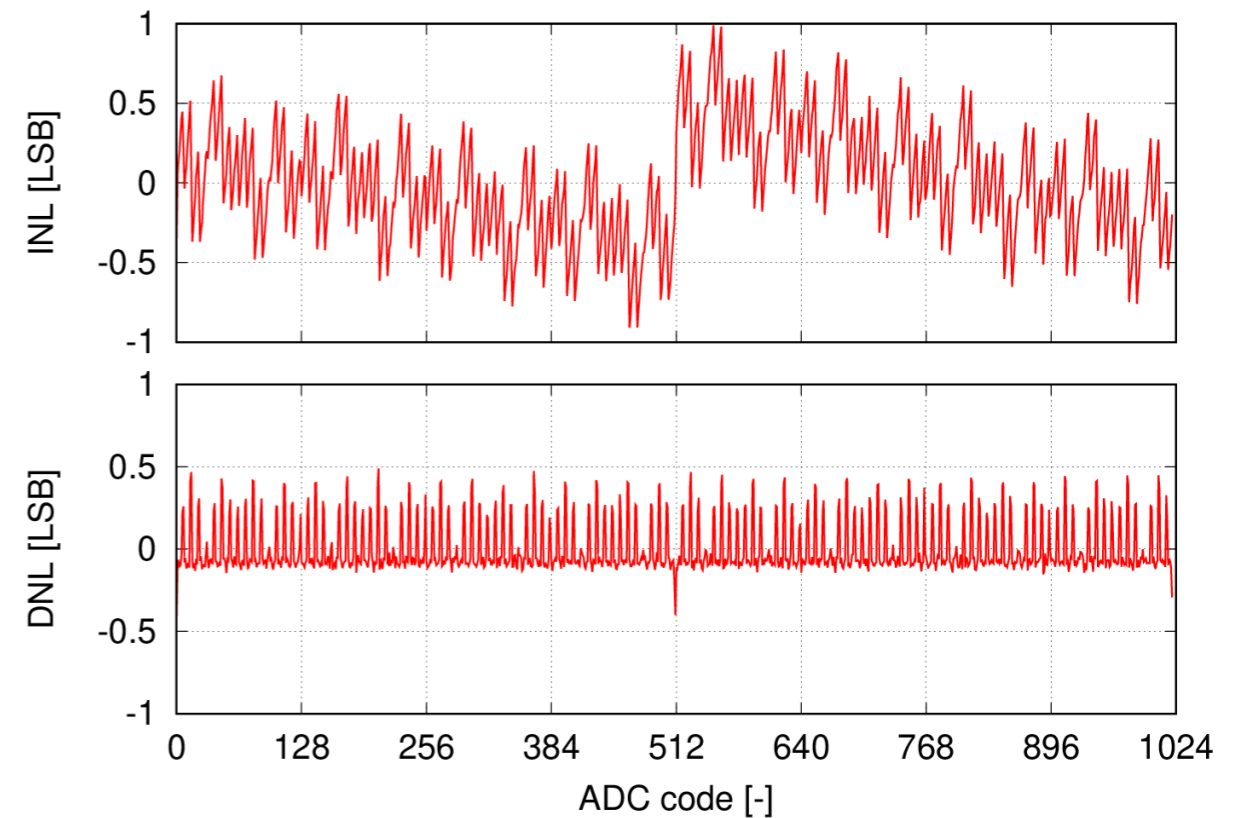

$-0.42 < \mathbf{DNL} < 0.52$
 $-0.98 < \mathbf{INL} < 0.94$
 Static **ENOB** = 9.35



Result somehow expected due to the large parasitics and lack of matching parameters

130 nm MIM 613

130 nm MIM 514

—+ SINAD —* SFDR —● ENOB
—x |THD| —□ SNHR

—+ SINAD —* SFDR —● ENOB
—x |THD| —□ SNHR

 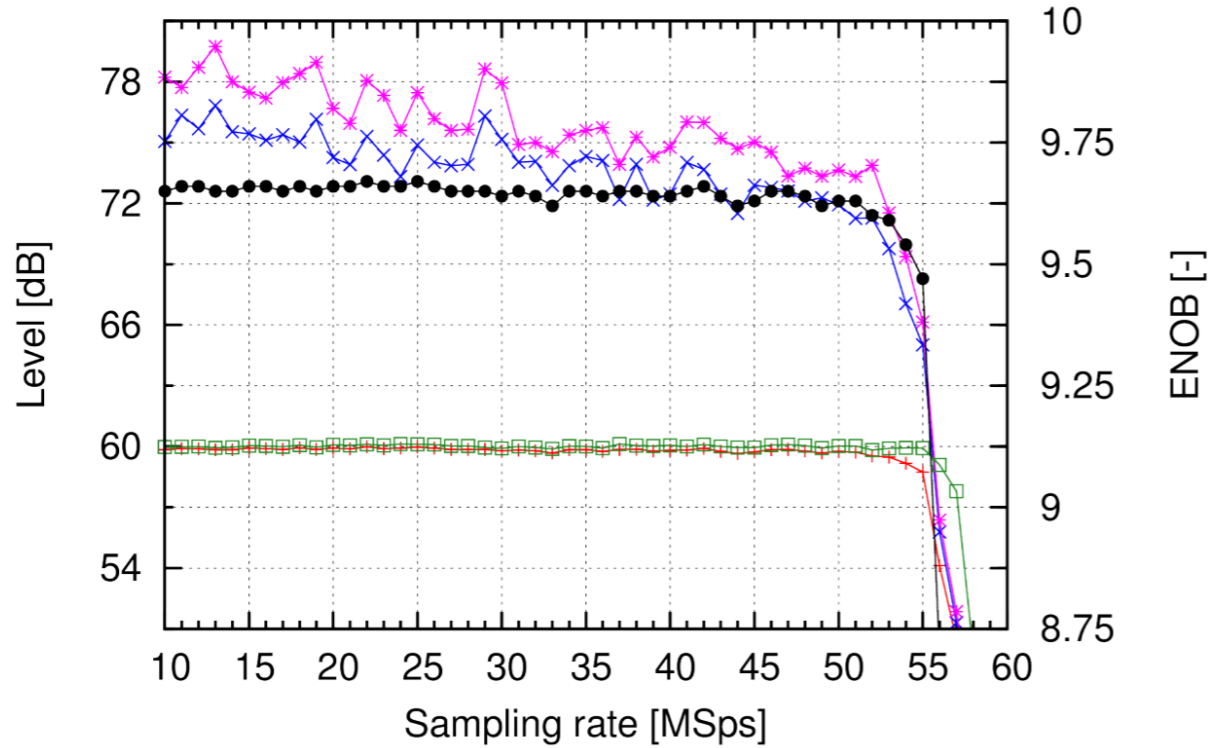

Sampling rate \leq **55 MSps**

Sampling rate \leq **50 MSps**


ENOB $>$ 9.65 up to 50 MSps

ENOB $>$ 9.2 up to 45 MSps

ENOB \approx 9.5 at 55 MSps

ENOB \approx 9.0 at 50 MSps

65 nm MIM 613

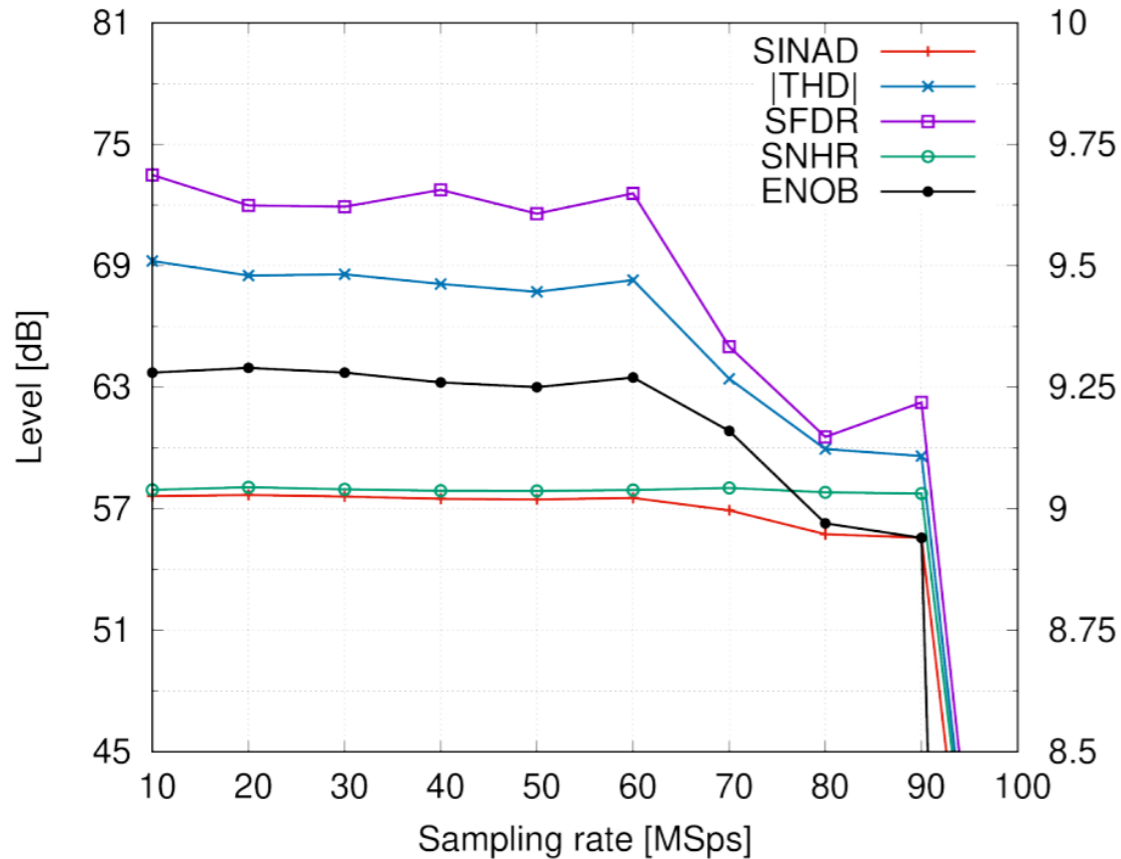


Sampling rate ≤ 90 MSps

ENOB > 9.3 up to 60 MSps

ENOB ≈ 8.9 at 90 MSps


65 nm MOM 712

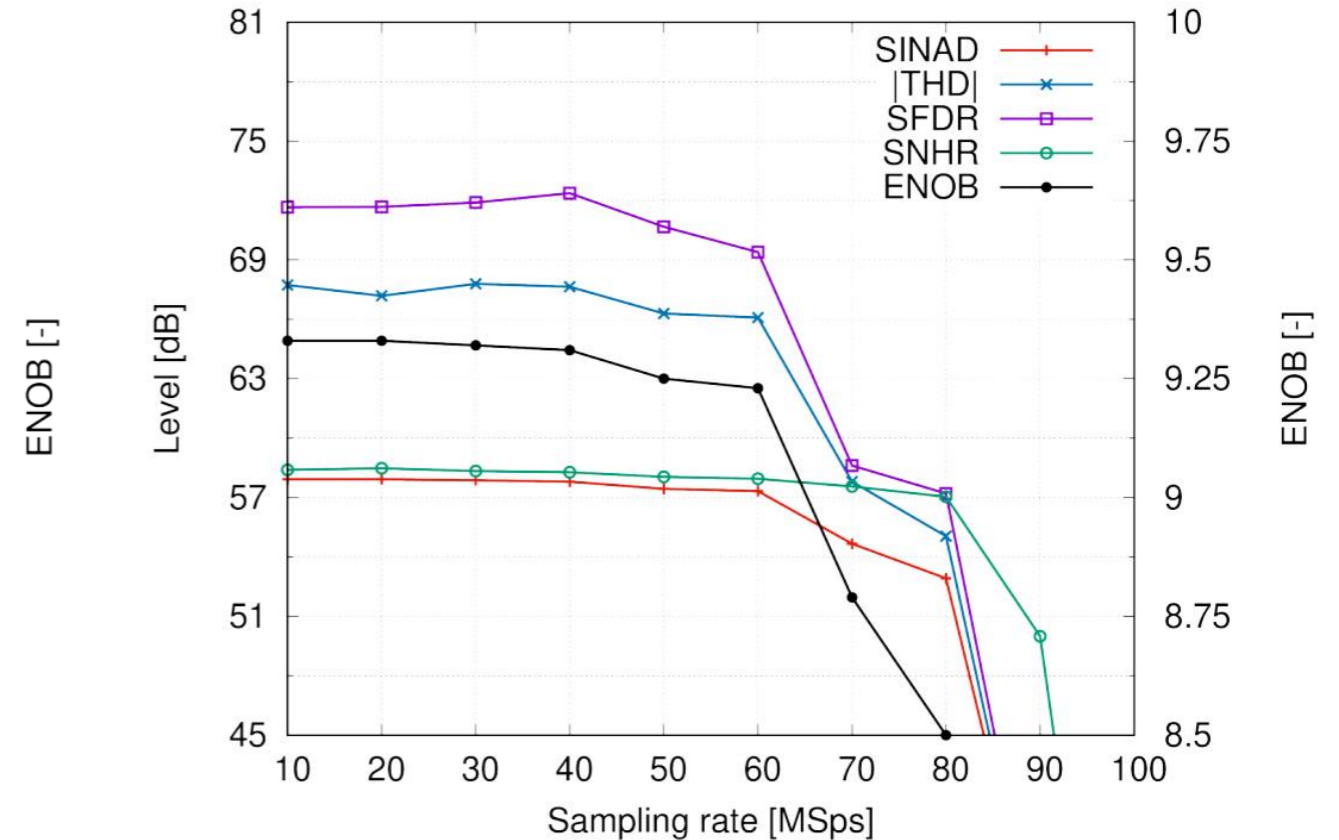


Sampling rate ≤ 70 MSps

ENOB > 9.3 up to 60 MSps

ENOB ≈ 8.7 at 70 MSps

 




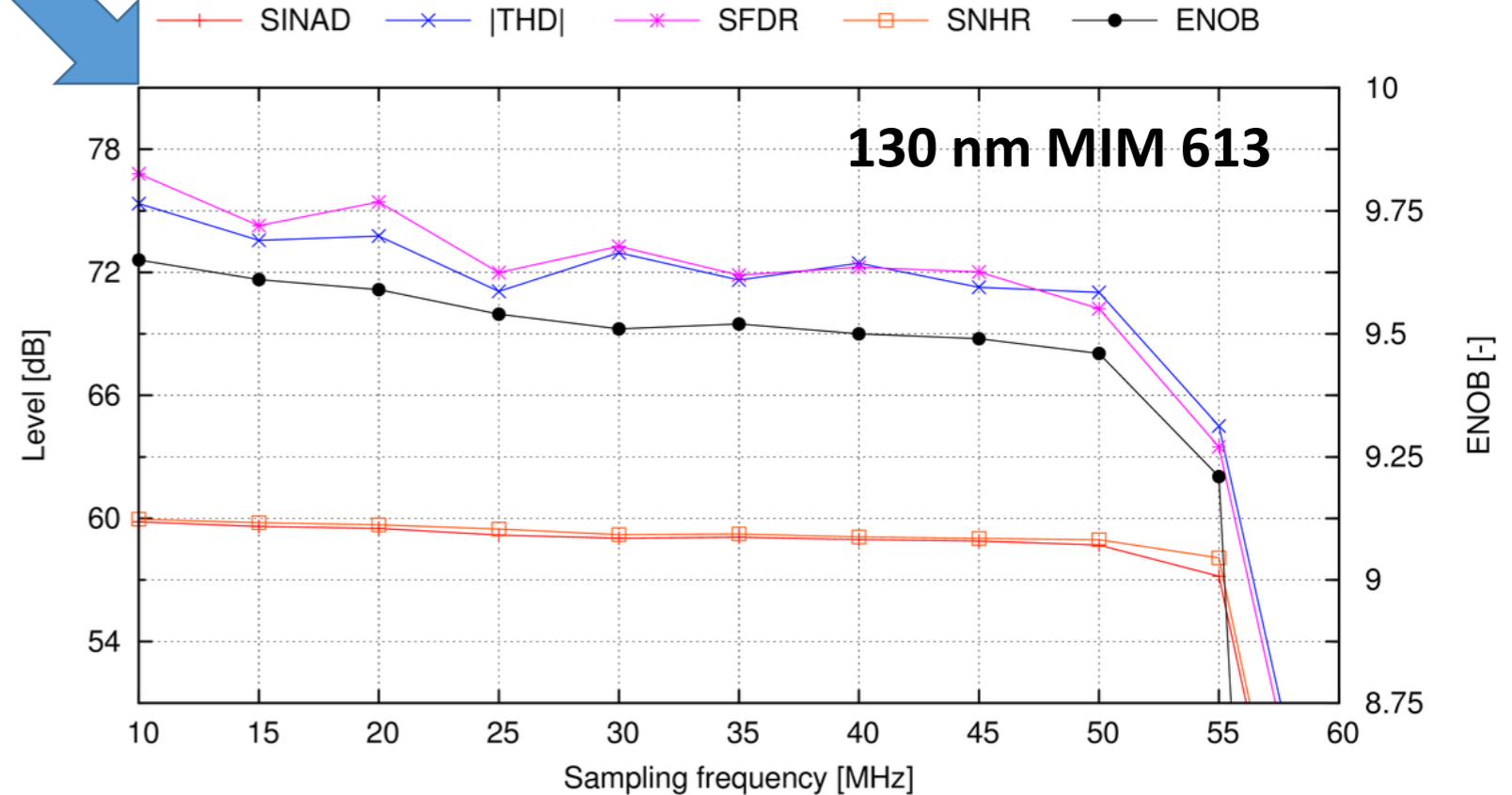
Measurements at Nyquist are challenging...



Sampling rate ≤ 55 MSps

ENOB > 9.5 up to 40 MSps


ENOB ≈ 9.2 at 55 MSps

    

(digital + analogue + reference)

130nm power consumption at 40 MSps: • 613: **680 μW** (440 + 160 + 80) μW


• 514: **635 μW** (425 + 160 + 50) μW

 

Power consumption at 40 MSps:

- 130nm 613: **680 μ W**
- 130nm 514: **635 μ W**
- 65nm MIM : **550 μ W**
- 65nm MOM: **600 μ W**


130 nm MIM 613

 


FoM_{If} ≤ **21** fJ/conv up to 50 MSps
 FoM ≤ **24** fJ/conv up to 50 MSps

One of the best results so far among State of the Art ADCs in similar technology


130 nm MIM 514

 

FoM_{If} ≤ **27** fJ/conv up to 45 MSps

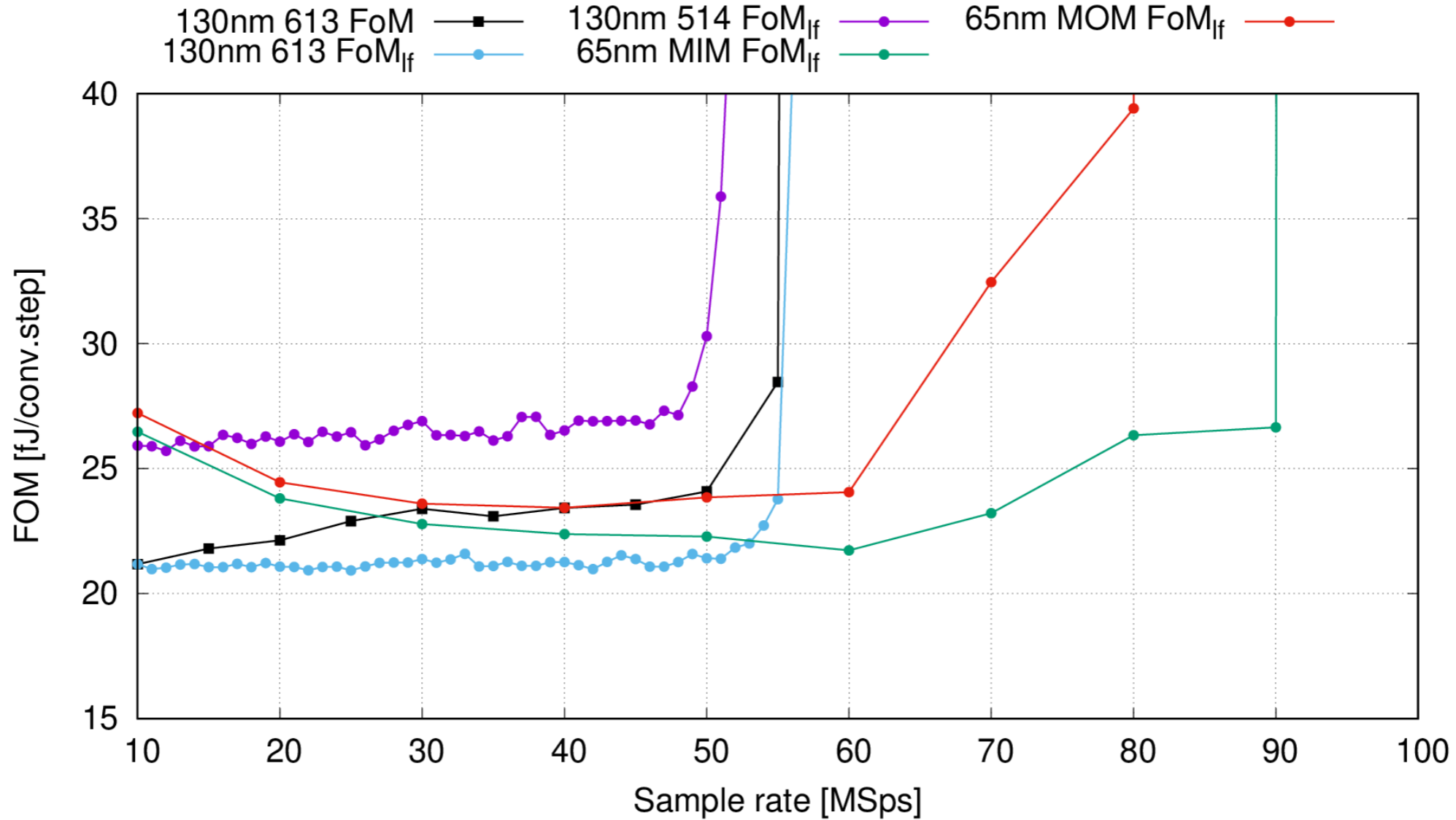

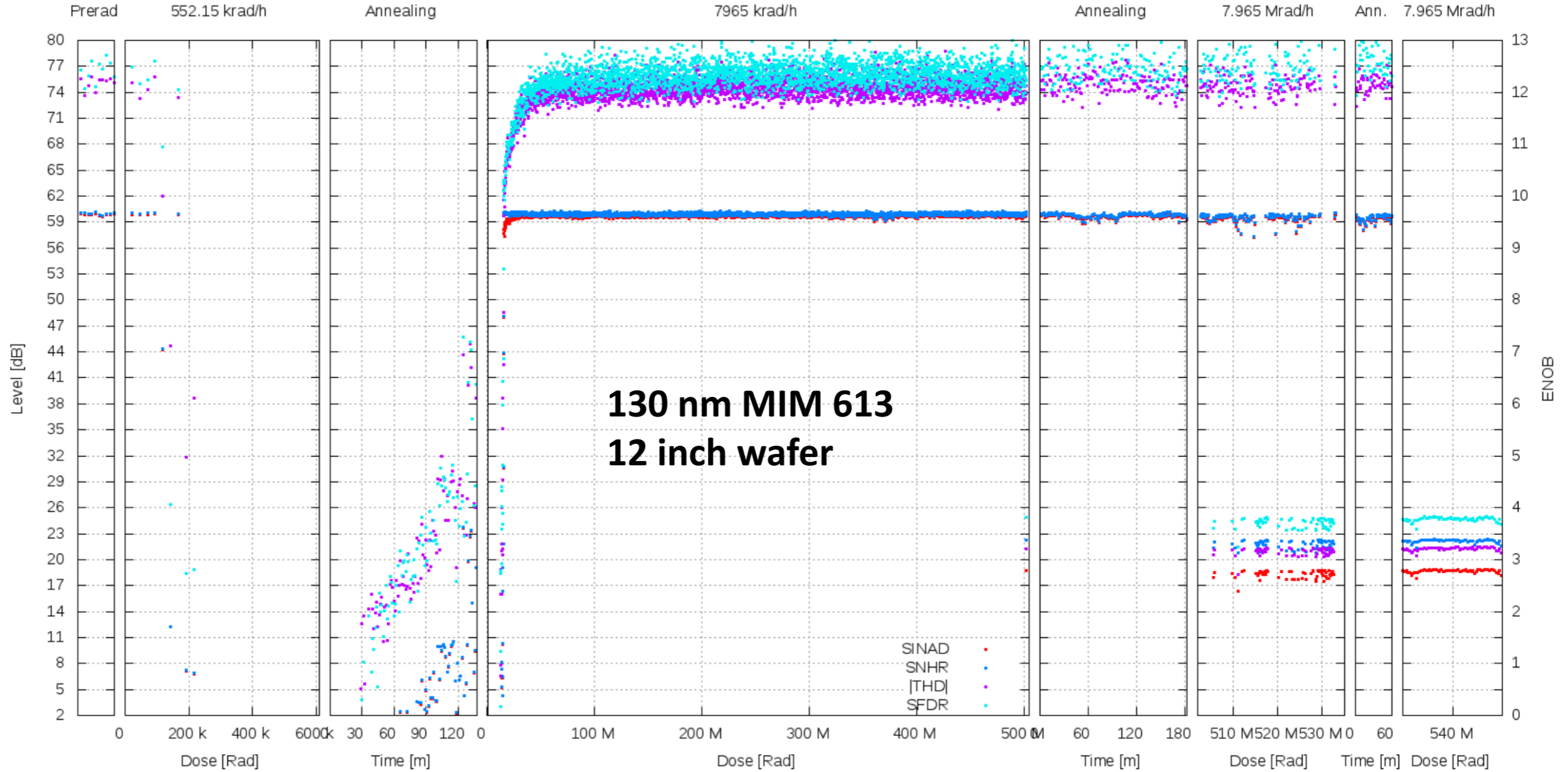- 65nm – $FoM_{lf} \leq 23$ for sampling rates < 60 MSps (MOM) and < 80 MSps (MIM)
For lower sampling rates, FoM_{lf} increases due to decoupling leakage current
- 130nm achieves similar FoM (even at Nyquist) – larger power but better ENOB



Resolution drops after few hundred krad but recovers in few hours and stays good up to 500 Mrad


TDC

General idea: take advantage of the excellent ADC we have (130nm 613) and build analogue interpolation TDC around it.

- Time-to-Analog Converter (TAC) – converts time into voltage (proportional to time)
- ADC converts TAC output voltage to binary number


TAC operation:

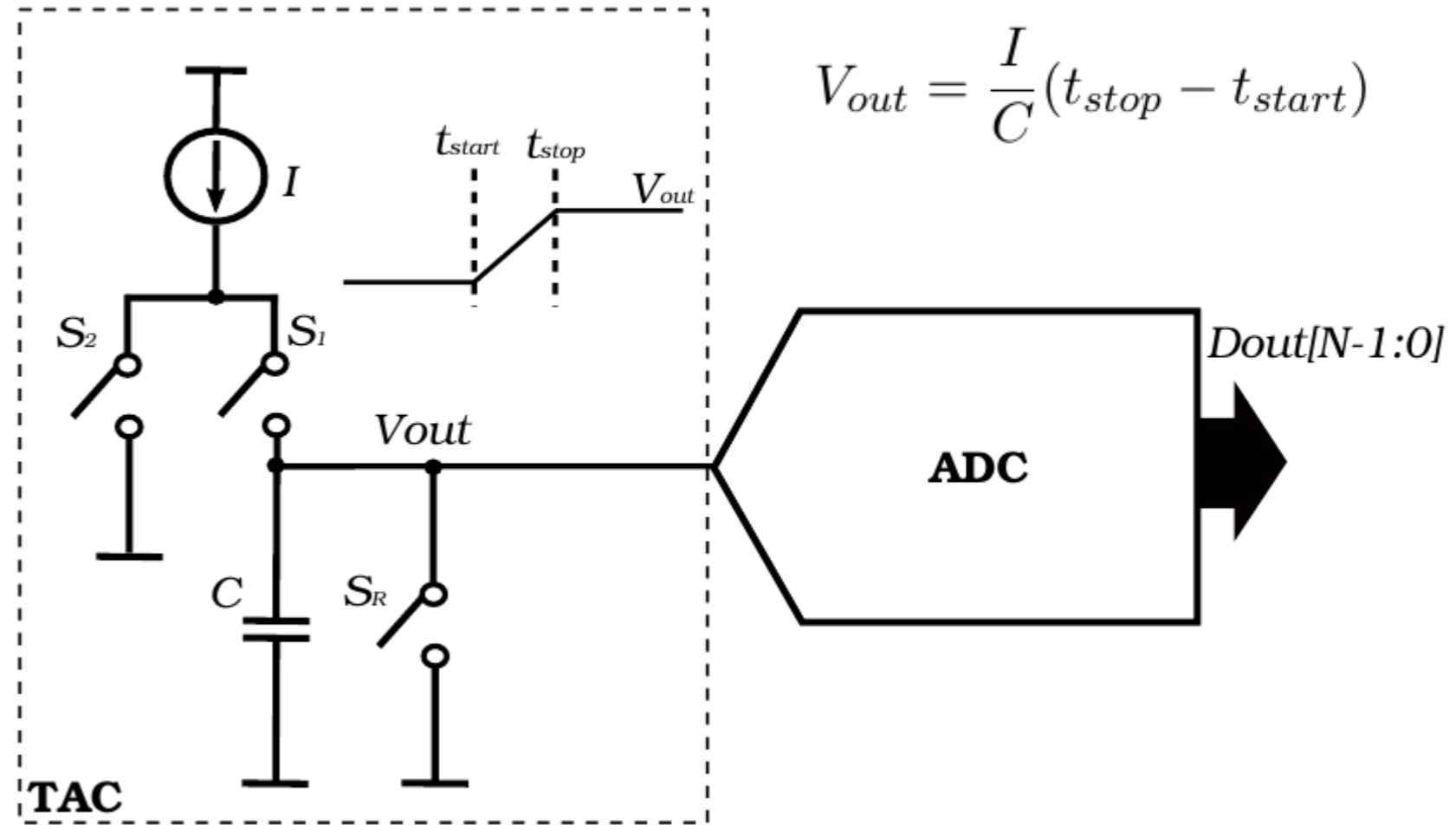1. Reset sampling capacitor to constant, known voltage
2. Charge it with constant current between “Start” and “Stop” signals




Since ADC comprises capacitive DAC, an additional sampling capacitor in TAC is not really needed, and constant current can directly charge capacitive DAC in the ADC

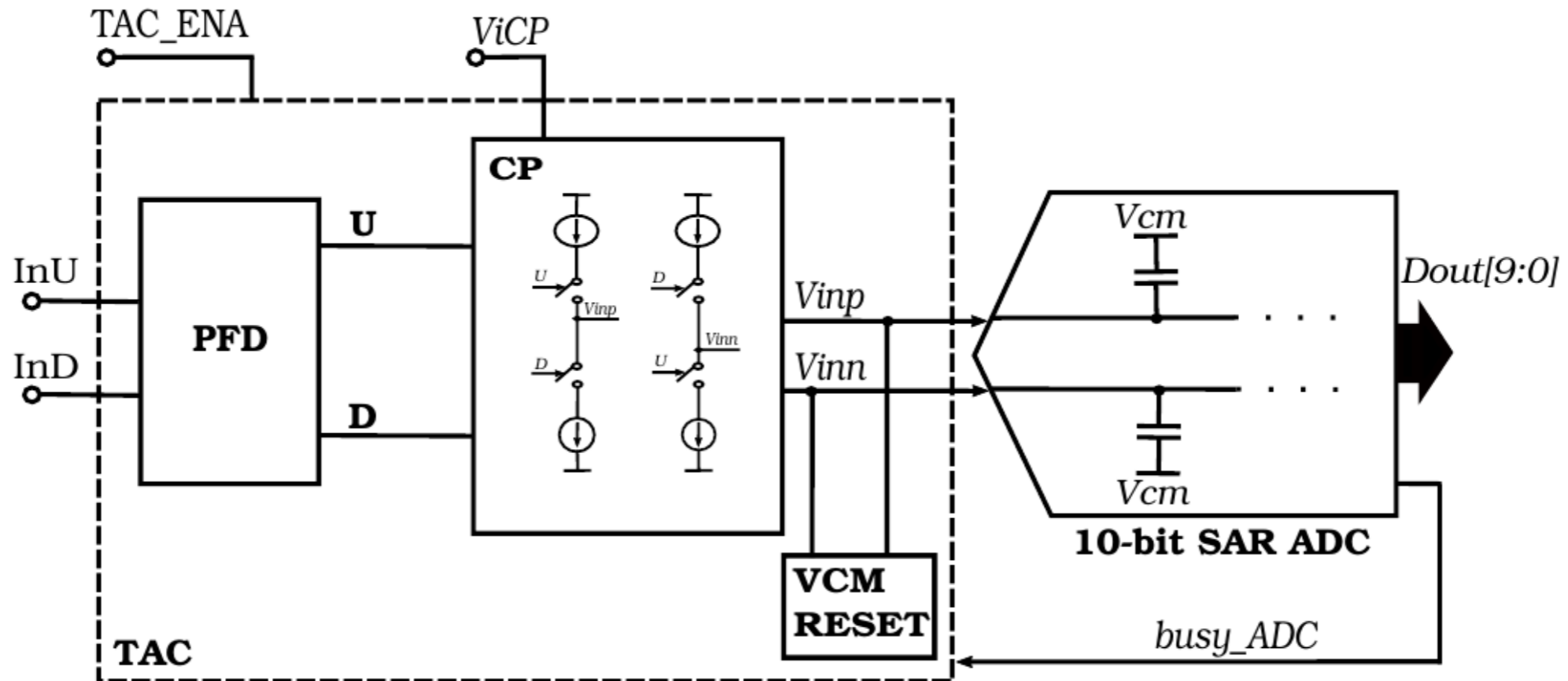- Phase Frequency Detector (PFD) – converts time difference between rising edge on InU and InD inputs into current source control signals U, D
- Charge Pump (CP) – charges (U) or discharges (D) capacitive DAC in the ADC. Charging current is determined by the bias voltage ViCP




TAC layout


120 μm

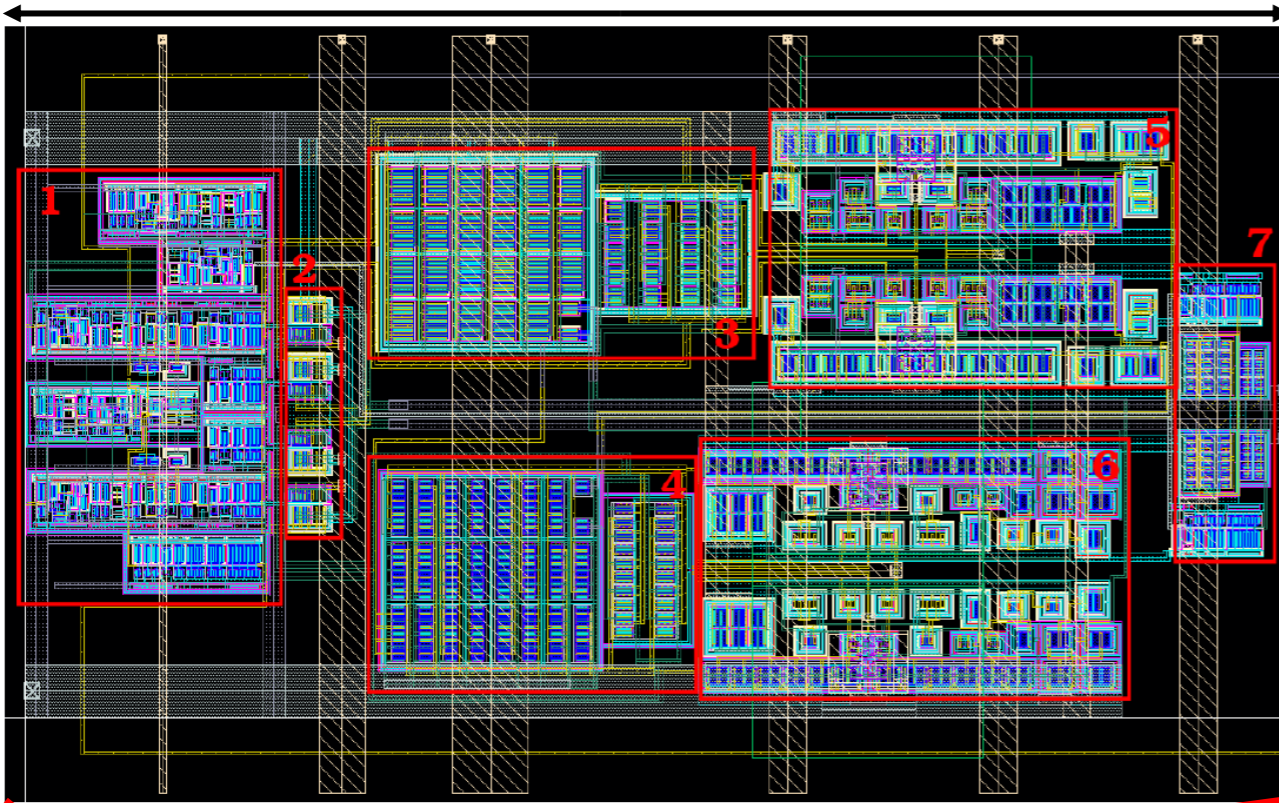

 
Time resolution in function of ViCP bias voltage DAC (7-bit) setting



100 μm

 

740 μm

 


Post-layout, 10ps resolution:
INL within ± 0.5 LSB in range:

 - -4.29ns (-365 LSB)
- +4.42ns (+375 LSB)



Post-layout, 100ps resolution:
INL within ± 3 LSB in range of
 ± 53 ns (± 480 LSB)

*TDC was optimized for 10ps resolution, so
100ps performance is much worse*



Time resolution dispersion
for 100 MC simulations

  Linear range dispersion for
100 MC simulations



Simulation results

ΔT (resolution) = 10ps


Summary

- Two ADC prototypes in 130nm CMOS technology designed and tested:
 - 613 split DAC:
 - Excellent resolution (**$ENOB_{lf} > 9.65$** , **$ENOB_{Nyq} \approx 9.5$** up to **50 MSps**)
 - **680 μ W** at 40 MSps with excellent **$FoM_{lf} = 21$** and **$FoM = 24$ fJ/conv.**
 - One of the best State of the Art ADC till now
 - Multichannel ready – in fact already used in:
 - HGCROC (*see D. Thienpont talk, Thursday 9:30*)
 - FLAME and FLAXE (*see M. Idzik talk, Thursday 10:30*)
 - Radiation hardness (with annealing) up to 500 Mrad
 - 514 split DAC:
 - Slightly lower power consumption, but also lower resolution than 613

- Two ADC prototypes in 65nm CMOS technology designed and tested:
 - MIM-based, 613 split DAC:
 - Good resolution (ENOB_{lf} ≈ **9.3** up to **60 MSps**, ENOB_{lf} ≈ 8.9 at 90 MSps)
 - Power consumption around 80% of 130nm technology
 - Modified version (not shown here) used in IpGBT in monitoring circuitry
 - MOM-based, 712 split DAC:
 - Smaller than MIM-based (70% area), similar resolution but slower
- ADC-based TDC designed, simulated and fabricated.
Post-layout simulation results shows resolution < 12ps in range up to 4ns with good linearity
Due to unexpected delays in test setup preparation measurement results not ready yet

Thank you for the attention

Backup slides

 


$$SNR = SNHR = \frac{P_{Sig}}{\sum P_{Noise}}$$


$$SNDR = SINAD = \frac{P_{Sig}}{\sum P_{Noise} + P_{HD}}$$

$$THD = \frac{P_{Sig}}{P_{HD}}$$

$$ENOB = \frac{SINAD - 1.76}{6.02}$$

 
ADC dynamic metrics: DFT of the samples of the pure sine input signal



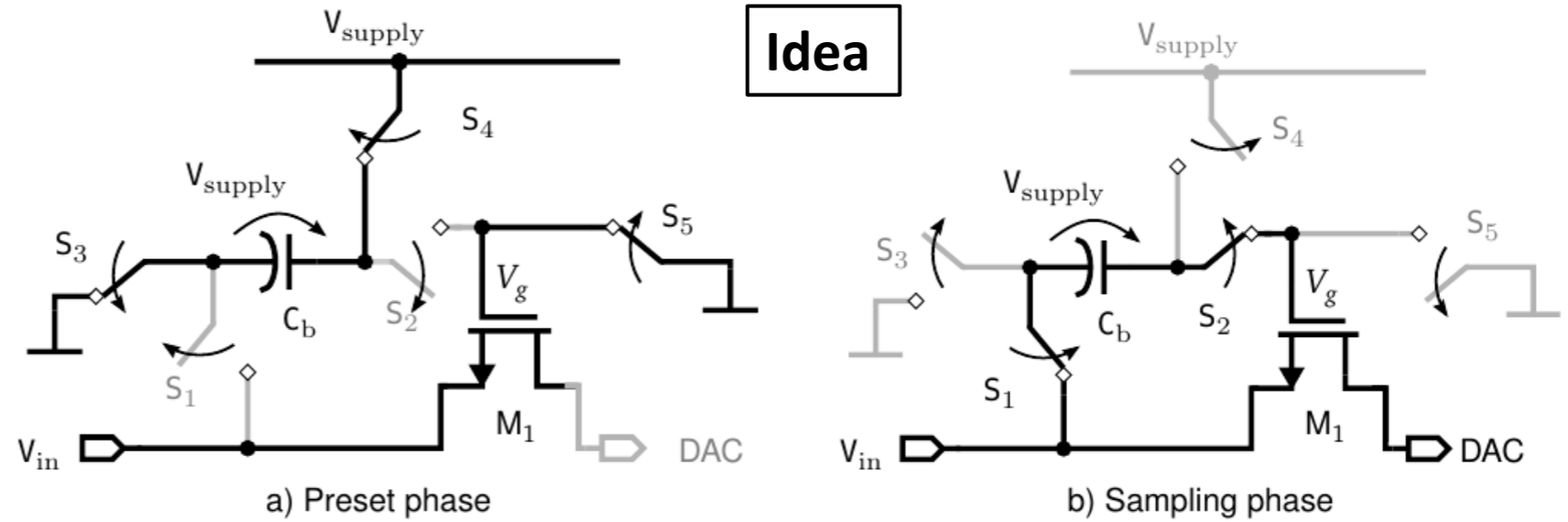

To minimize distortions during sampling, a bootstrap switches implemented.

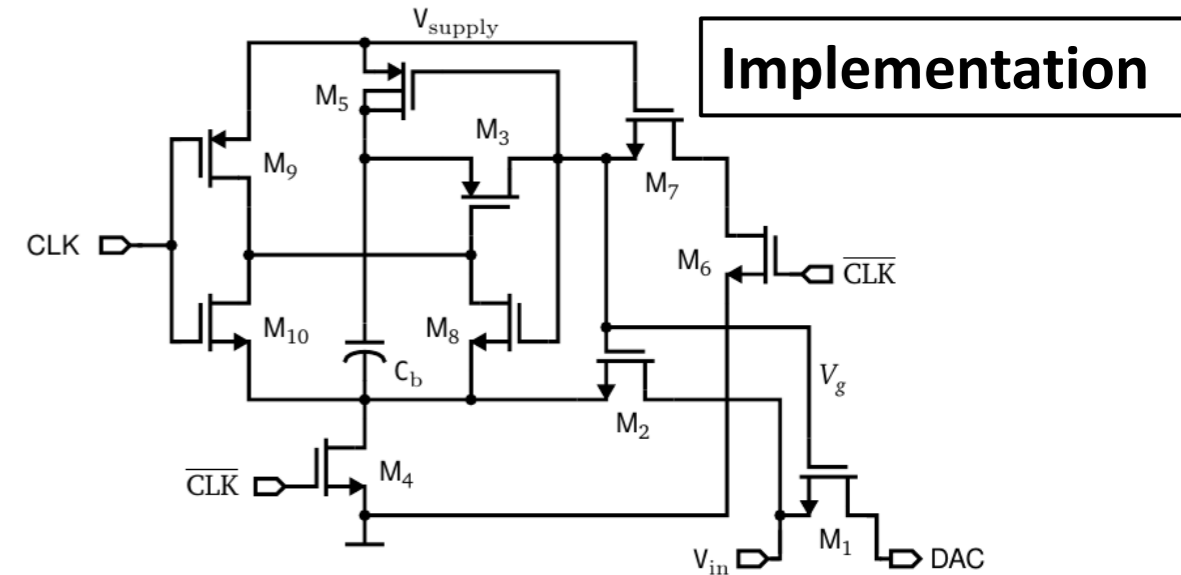General idea: keep V_{gs} equal to power supply voltage, regardless the V_s (input) voltage.




M. Dessouky and A. Kaiser, "Input switch configuration for rail-to-rail operation of switched opamp circuits," *Electronics Letters*, vol. 35, no. 1, pp. 8–10, 1999

Dynamic comparator

- Comparison performed on rising edge of “active” signal
- Reset (“active” low level) needed before next comparison


Pros and cons:

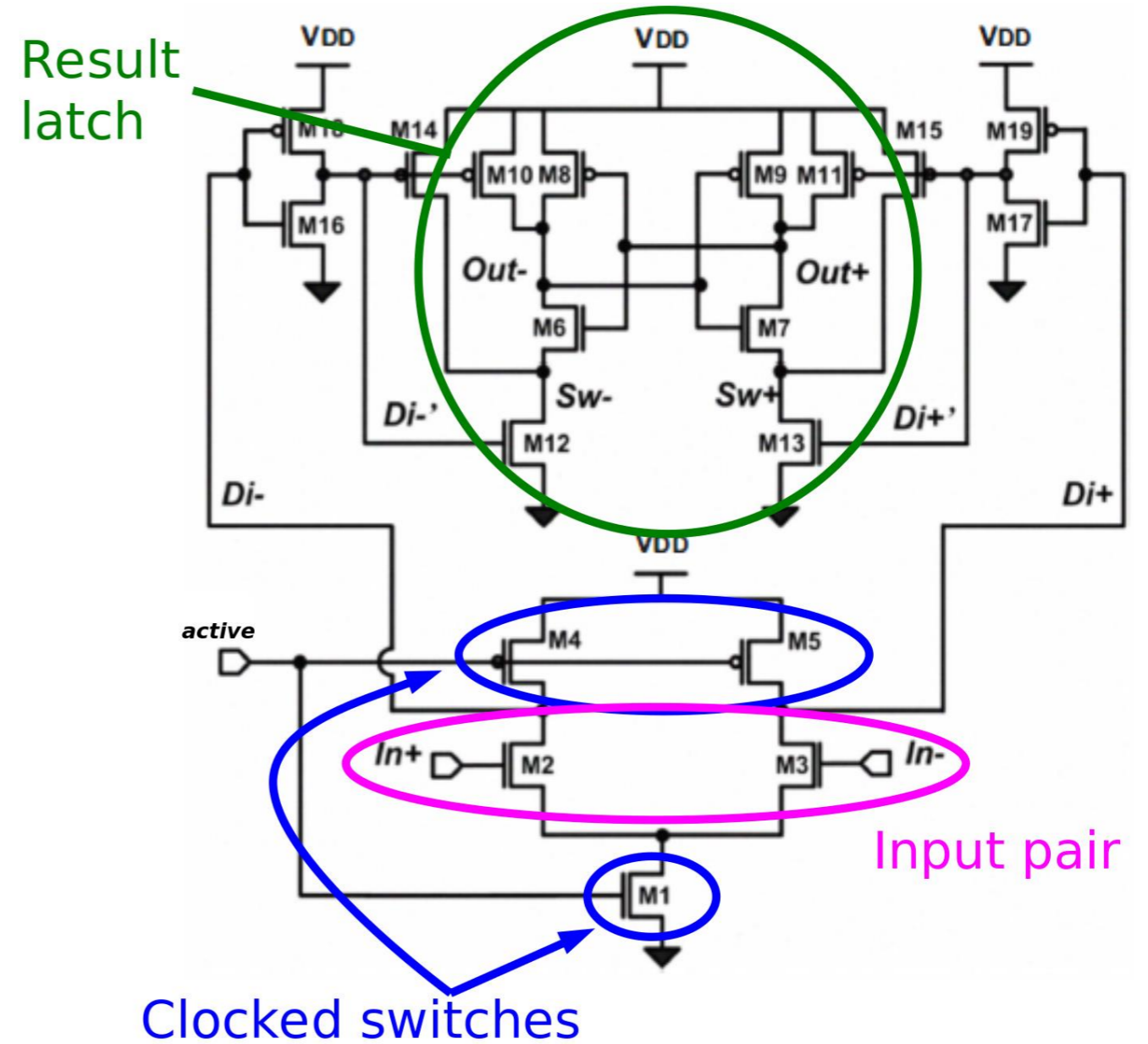- + No direct path current
- + Low power consumption
- Dead time needed for reset
- Response time depends on input voltage difference




H.J. Jeon, Y-B. Kim, M. Choi “Offset voltage analysis of dynamic latched comparator”, IEEE 54th Int. Midwest Symp. On Circuits and Systems, 2011

 With CMOS technology scaling digital power consumption is decreasing rapidly, so minimizing analog power (DAC, comparator) is of main interest. Huge progress has been obtained in the last ~10 years in optimizing capacitive DAC configurations and their switching schemes





- Conventional – 100%
- Energy saving – 44%
- Switchback (SBA) – 18%
- Monotonic – 18%
- Improved SBA – 13%
- **Merge Capacitor Switching (MCS) – 7%**
- (...)
- Tri-level switching – 3.1%
- V_{cm}-based – 2.3%

MCS (Merge Capacitor Switching) scheme


 


 First comparison done before any switching – (N-1) capacitors needed




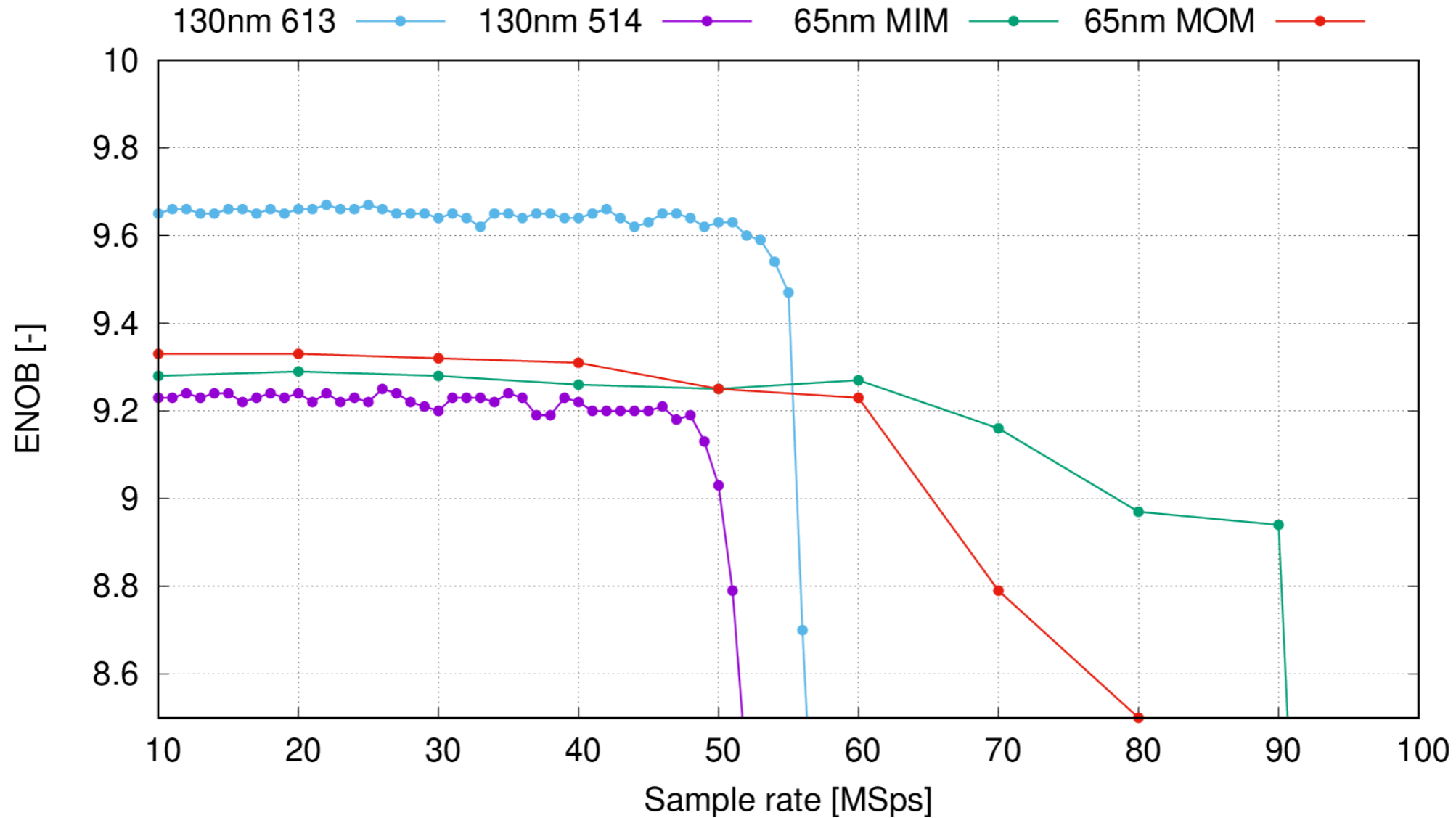



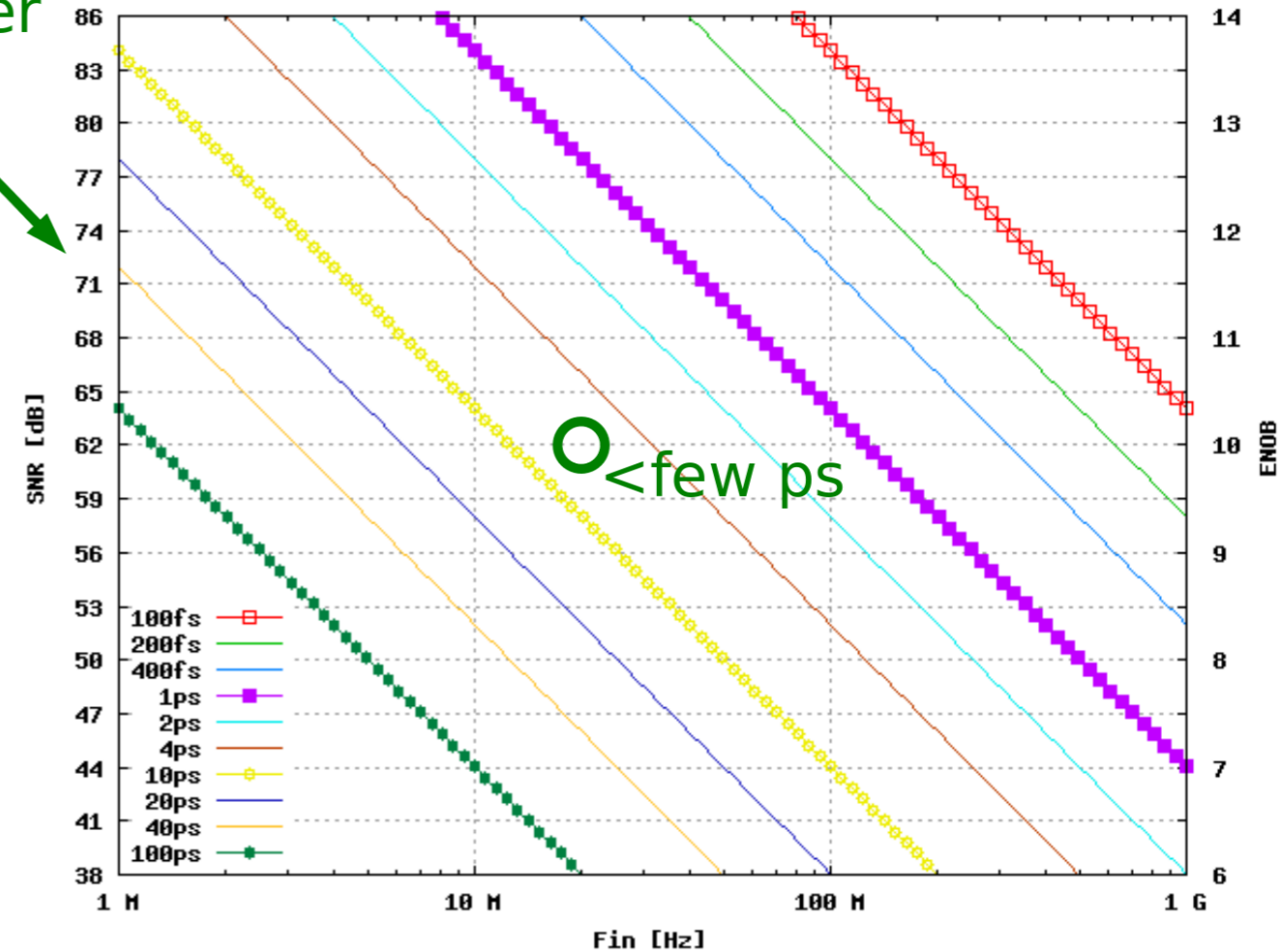
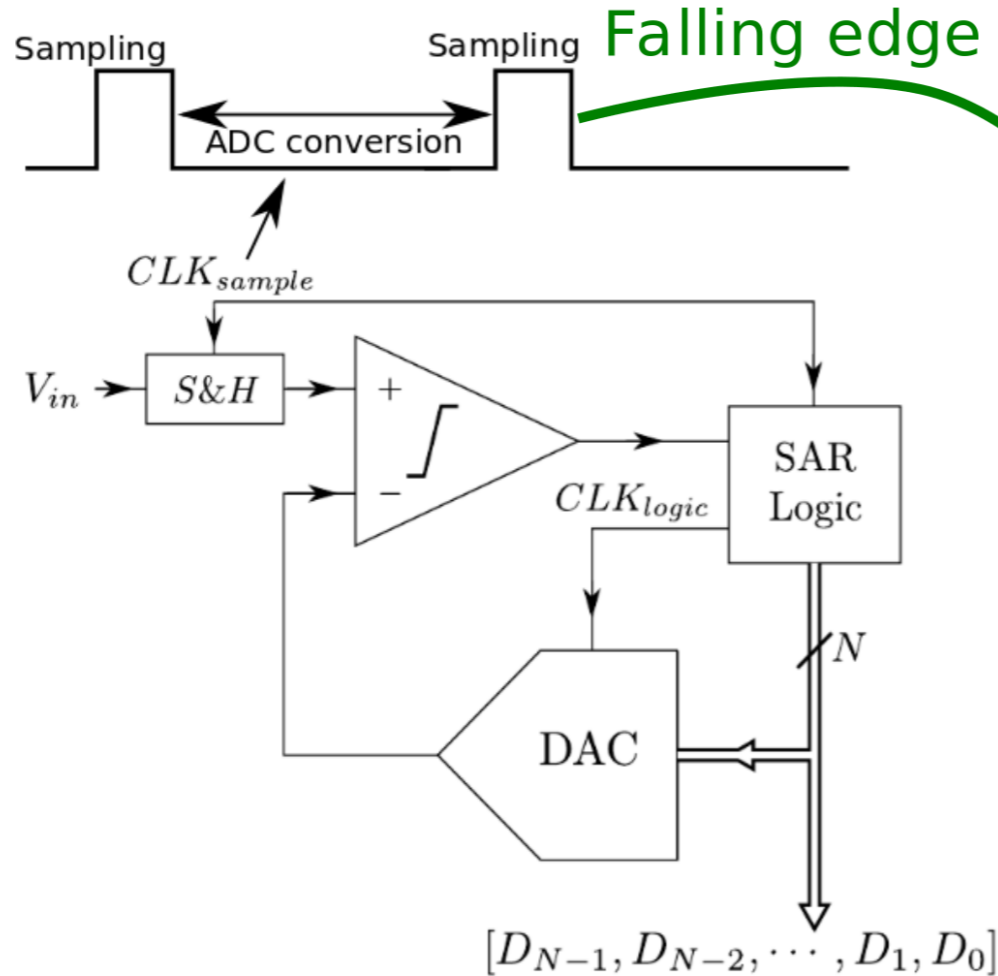
- 130nm 613 – excellent performance up to 55 MSps
- 130nm 514 and 65nm – similar, with 65nm being faster (MIM version up to 90 MSps)



 - To achieve 10b resolution (SNR = 61.96 dB), jitter of the end of the sampling phase, for 20 MHz input frequency, have to be lower than few ps.
- If the sampling clock provided to the ADC (in reference to the input sine wave) has already higher jitter, it will artificially degrade ADC performance...




    We have also made “low power” version of control logic in 65nm, but the performance is not the best – ENOB similar to the “regular” version, but sampling rate limit as in 130nm




- **DAC 613 – maximal delay**
- $-0.32 < \mathbf{DNL} < 0.20$
- $-0.40 < \mathbf{INL} < 0.54$
- Static **ENOB** = 9.92
- Max sampling rate \sim **30 MSps**

 - **DAC 613 – shorter delay**
- $-0.96 (-0.35) < \mathbf{DNL} < (0.20) 1.15$
- $-0.70 (-0.40) < \mathbf{INL} < (0.55) 1.15$
- Static **ENOB** = 9.9
- Max sampling rate \geq **40 MSps**



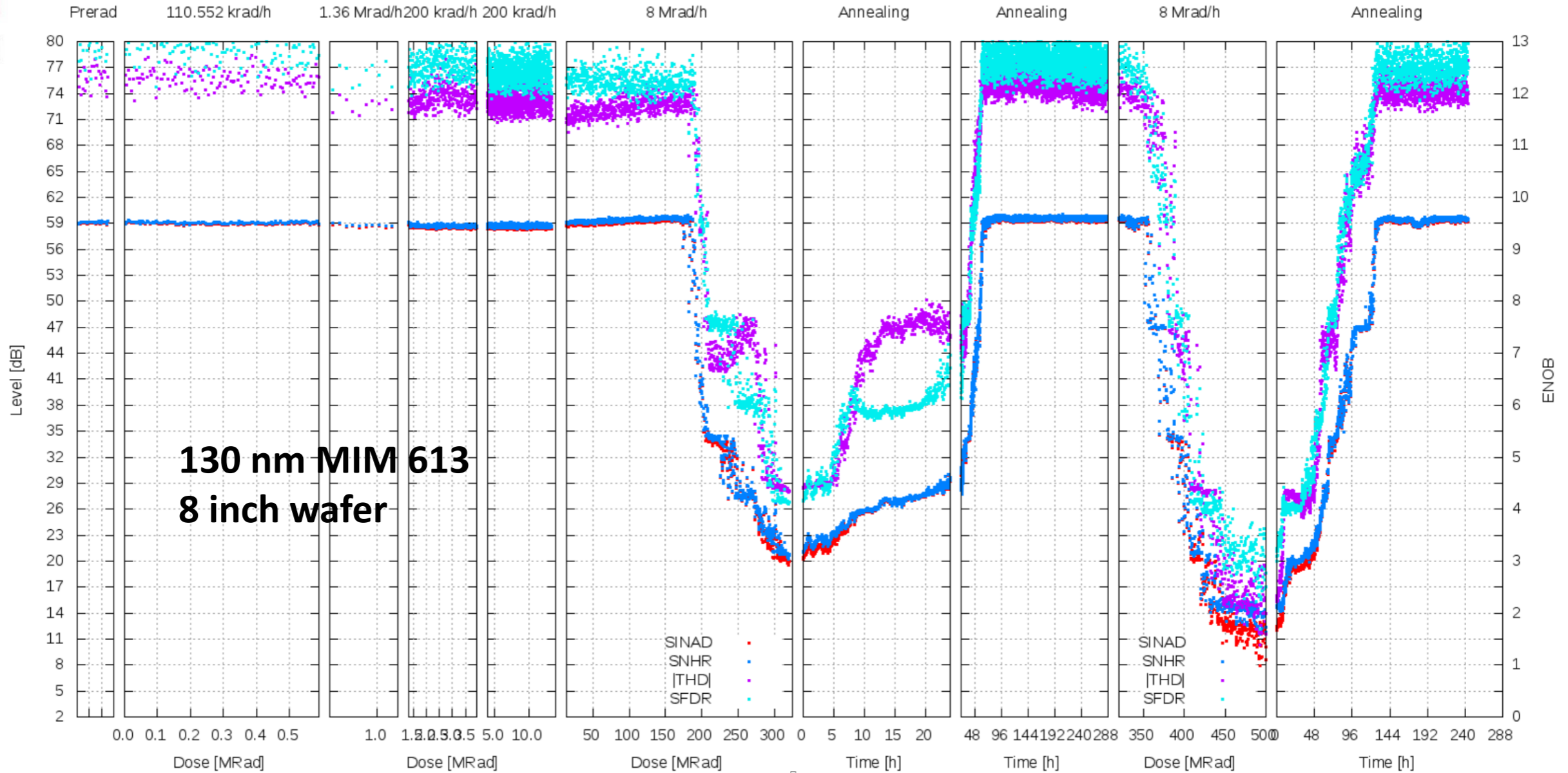1. Measure static metrics, scanning delay for each group (4 groups x 8 settings = 32 meas.)
2. Get minimal and maximal value of the DNL and calculate static ENOB
3. Choose smallest delay providing similar performance to the longest one



No effect up to 200 Mrad. Resolution degradation above (high dose intensity), recovered after annealing even above 500 Mrad