

# DUNE

## Power over Fiber

Meeting Annuale della Collaborazione Nazionale DUNE-Italia  
Lecce 2023-11-07

*Alessandro Andreani<sup>1,2</sup>, Marco Bassani<sup>1,3</sup>, Paolo Cova<sup>1,3</sup>, Nicola Delmonte<sup>1,3</sup>, Massimo Lazzaroni<sup>1,2</sup>, Danilo Santoro<sup>1,3</sup>, Valeria Trabattoni<sup>1,2</sup>, Andrea Zani<sup>1</sup>*

<sup>1</sup>INFN Sezione di Milano

<sup>2</sup>Università degli Studi di Milano

<sup>3</sup>Università degli Studi di Parma



UNIVERSITÀ  
DEGLI STUDI  
DI MILANO




UNIVERSITÀ  
DI PARMA



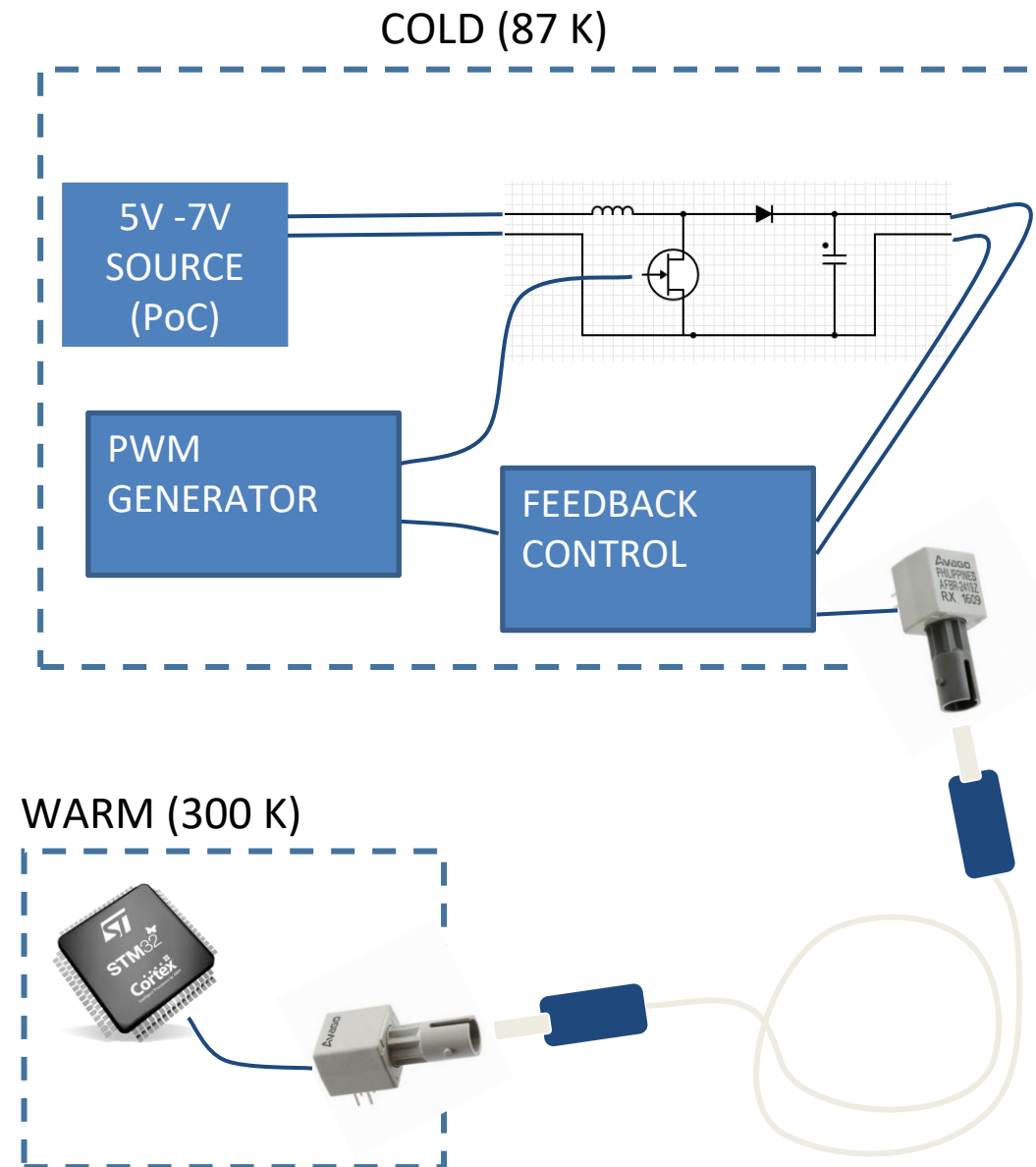
# System overview

- DC-DC boost converter: HV for SiPM bias at cold
- Power supply provided by PoC (Power optical Converter): 5 V to 7 V range
- PWM generation with two possible controls:
  - Inner feedback setting output voltage at nominal point (e.g. 48 V)
  - Optical input to change the setting voltage within few volts
- Analog feedback control loop circuit



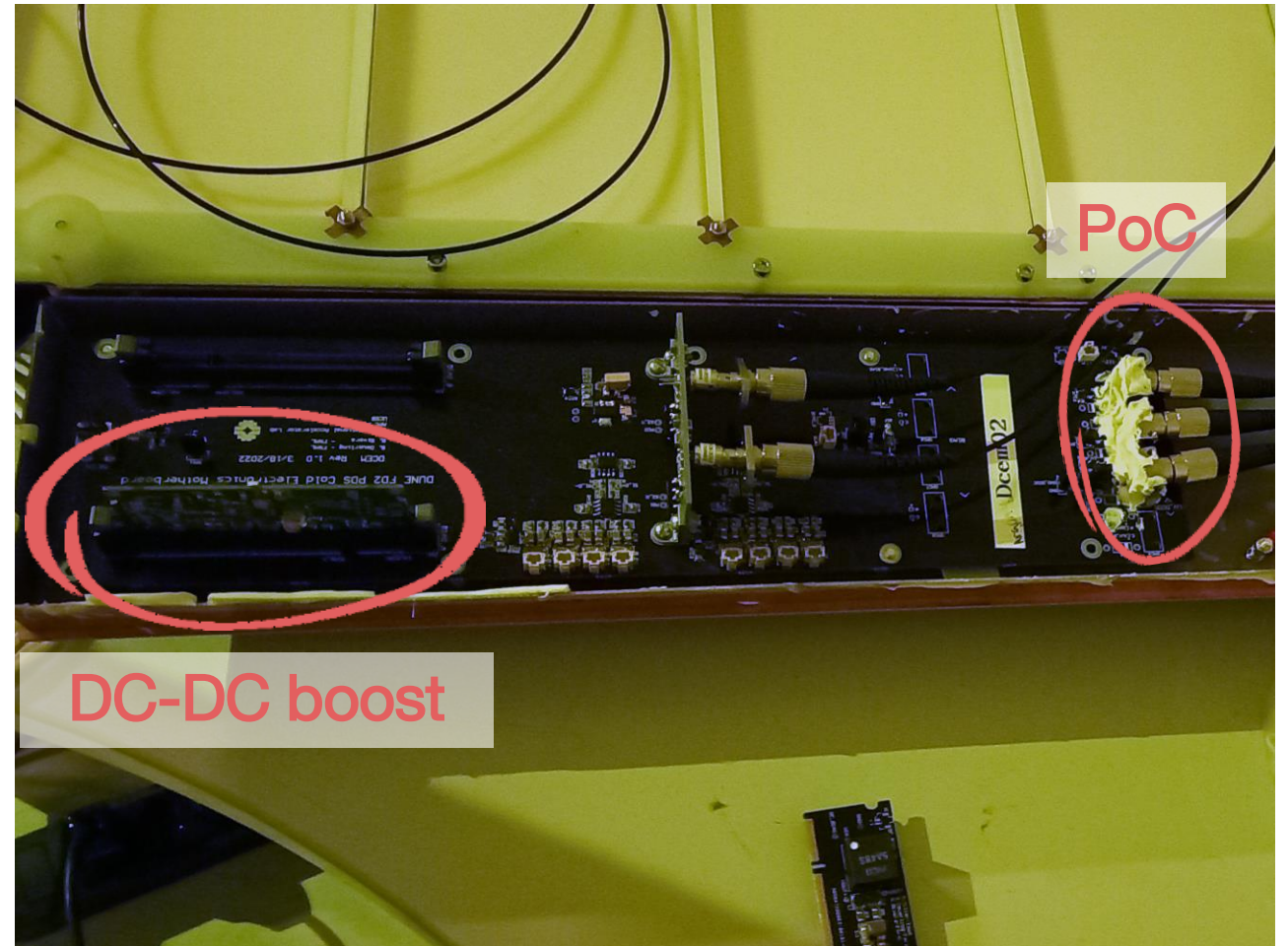
# Content

- DC-DC boost design
  - Performance
  - External PWM control
- Control design
- Operational Amplifier characterization for analog feedback control loop
- Conclusions



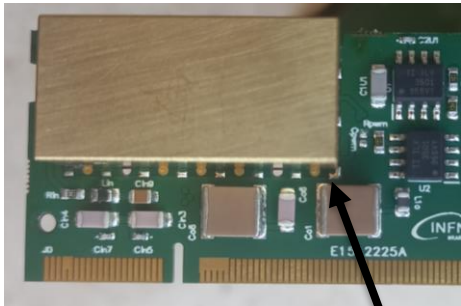
# DC-DC boost prototype, version 2

- Improved input and output filters
- Optimized analog feedback control circuitry
- Tests with external PWM control




With EMI shield

With EMI shield

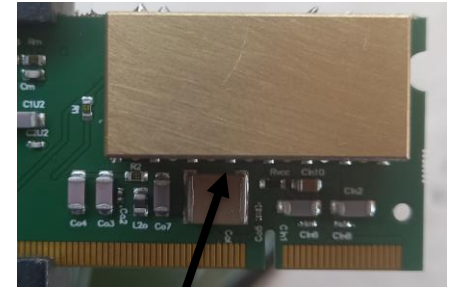



a) DC-DC prototype top layer

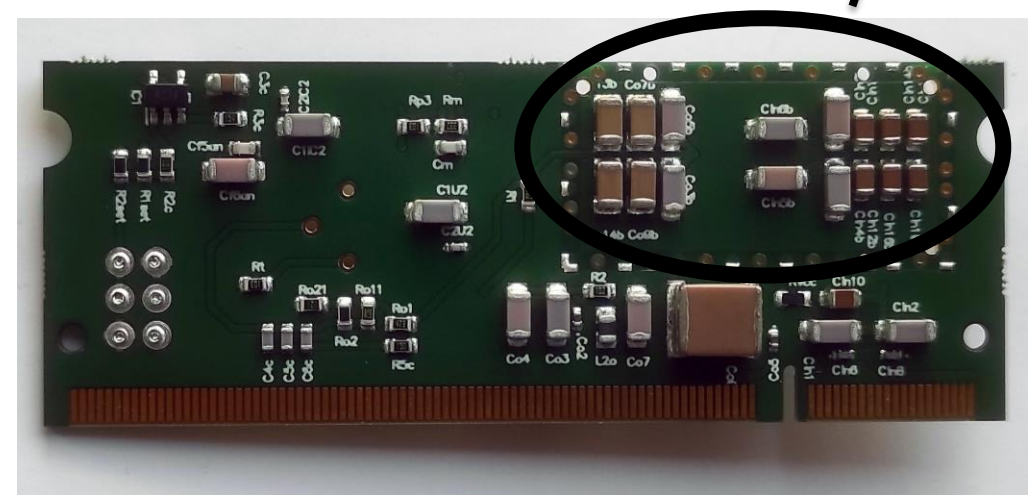

b) DC-DC prototype bottom layer





# DC-DC prototype results

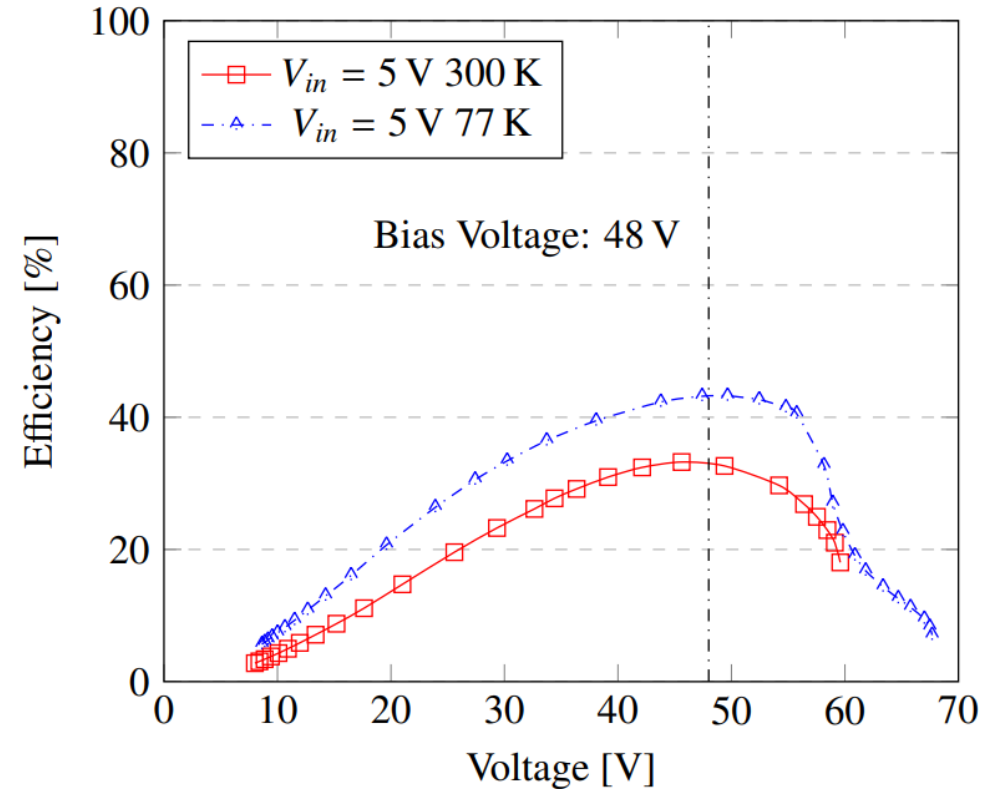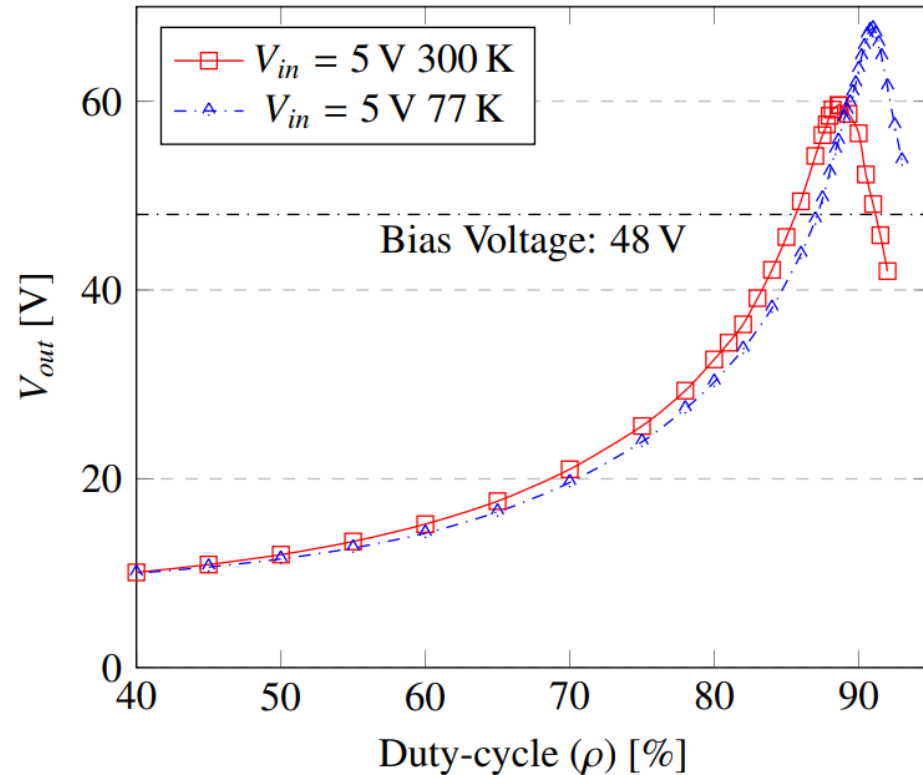

- **Output voltage** at RoomT limited by the inductor series resistor. At LN2 T, it is possible to reach 68 V at 91% of Duty Cycle
- The **efficiency** at LN2 at 48 V is **greater than 40%**

# DC-DC prototype results

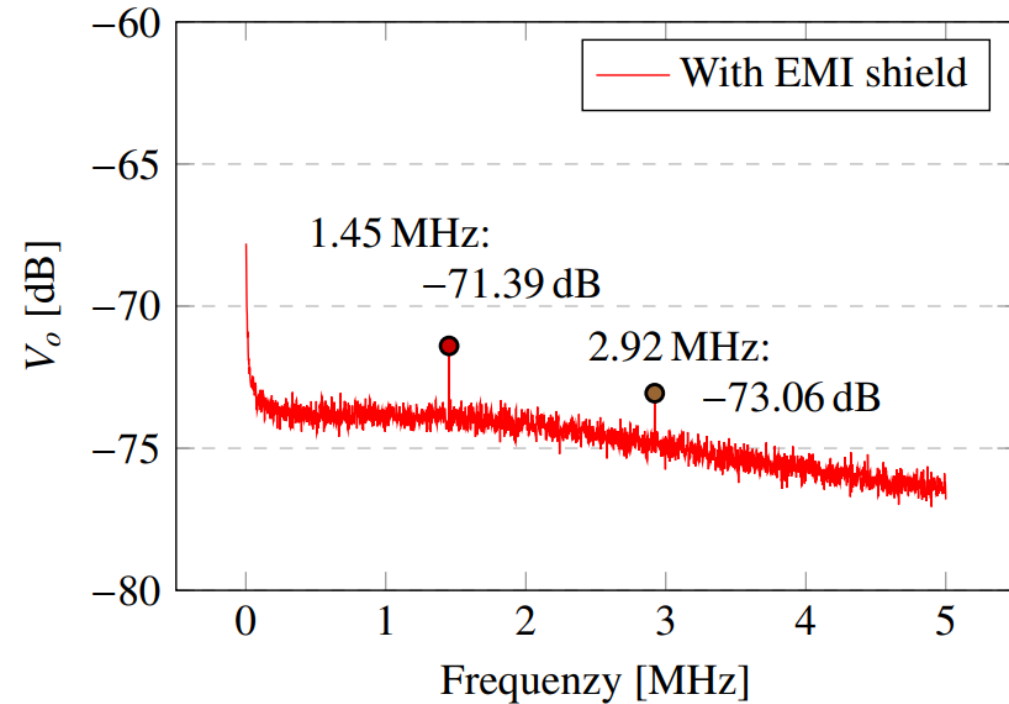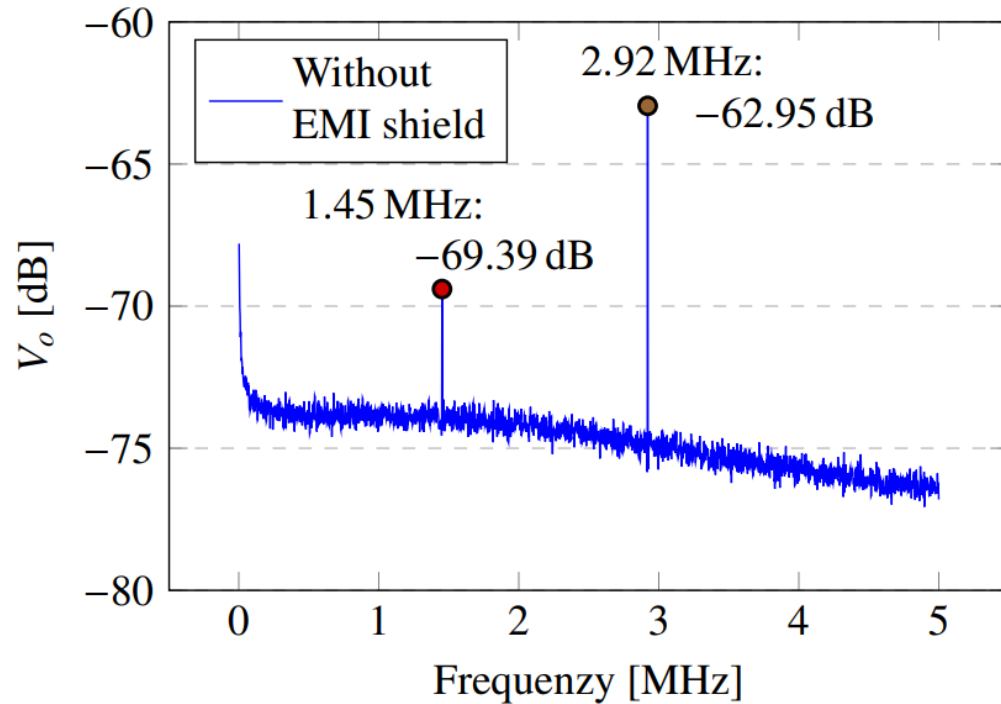


- Output voltage FFT measurements at 77K without EMI shield (blue) and with EMI shield (red)

# Control design



**Internal feedback:** output voltage control at desired set point

The **set point** can be:

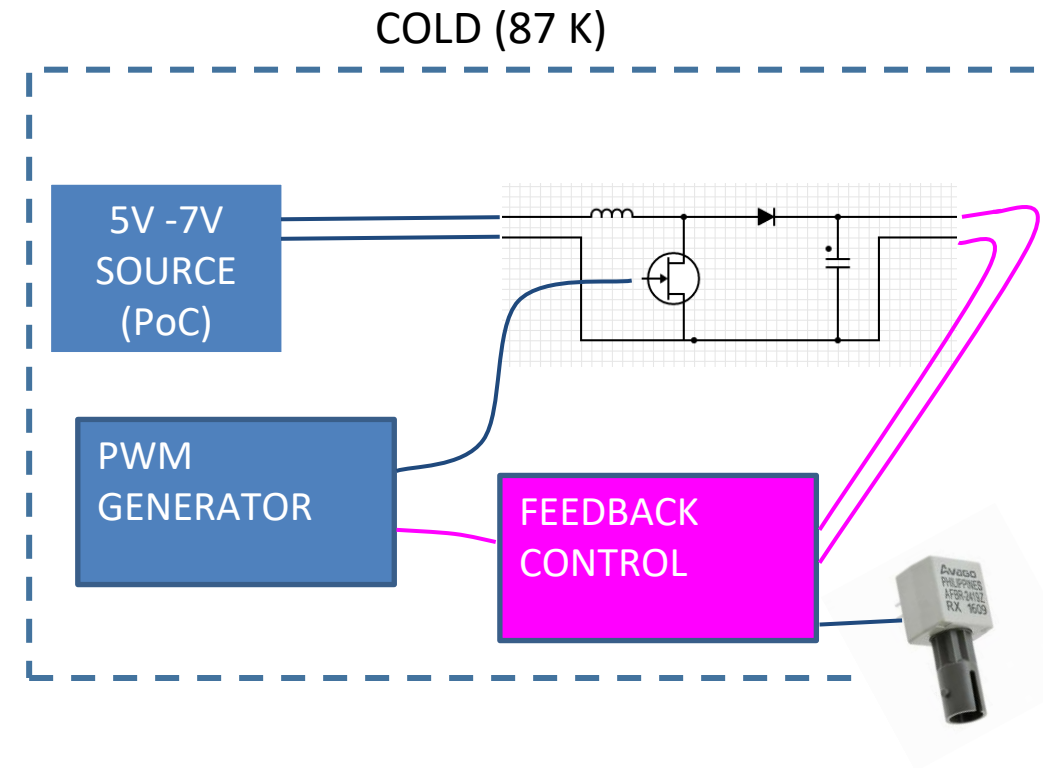- **Nominal:** set at design stage and fixed throughout the entire run (standalone mode)
- **External:** set point adjusted through external communication (in case of failure, nominal set-point)


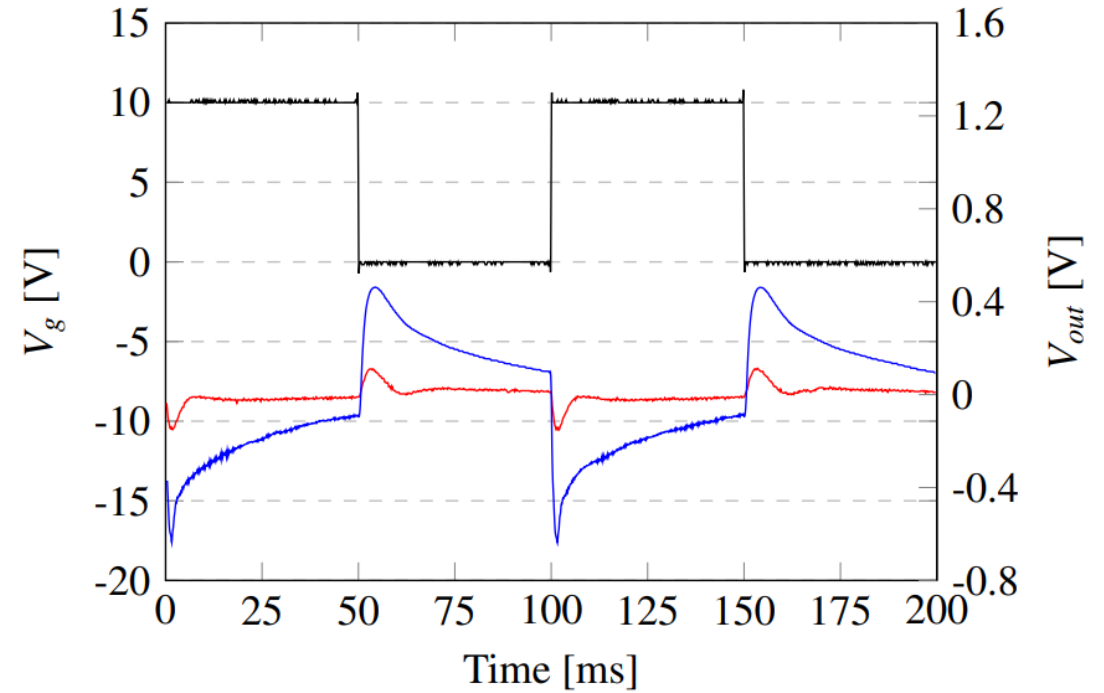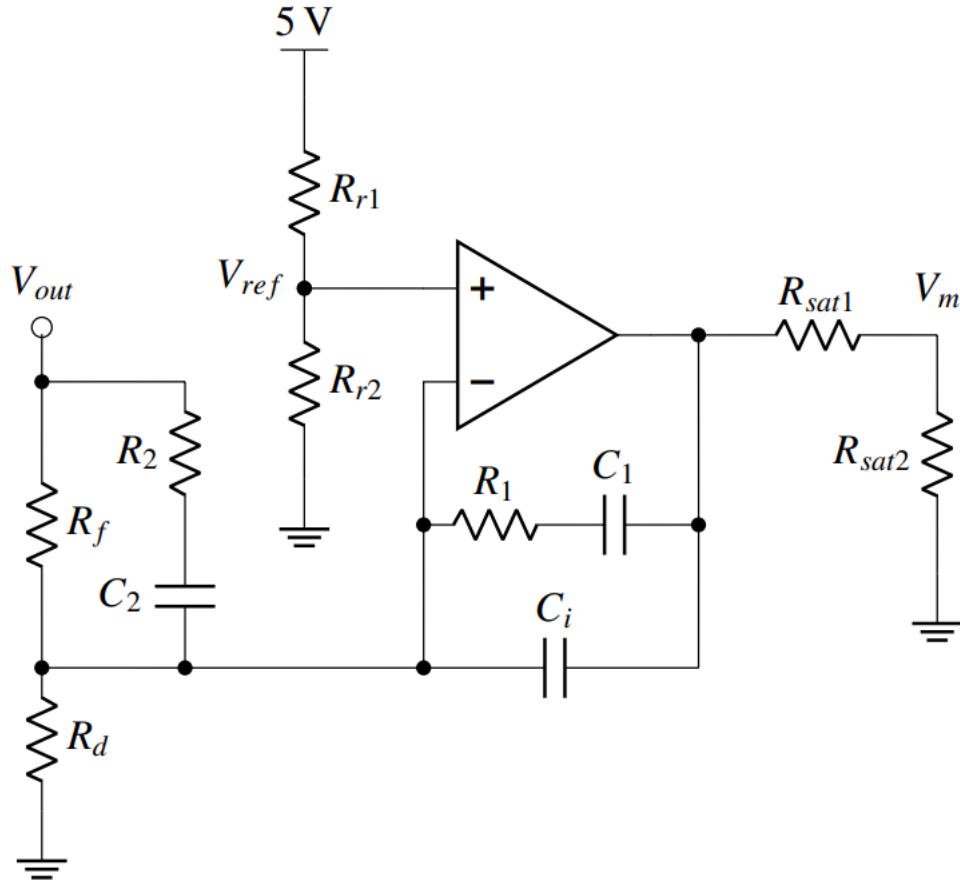
# Control design: analog feedback circuit





Experimental results of the **output step rejection response**, with a **load change from 50 k $\Omega$  to 8.33 k $\Omega$**

$V_{out} = 48$  V,  $V_{in} = 5$  V, output voltage measured with AC coupling at 300 K (red trace) and at 77 K (blue trace)


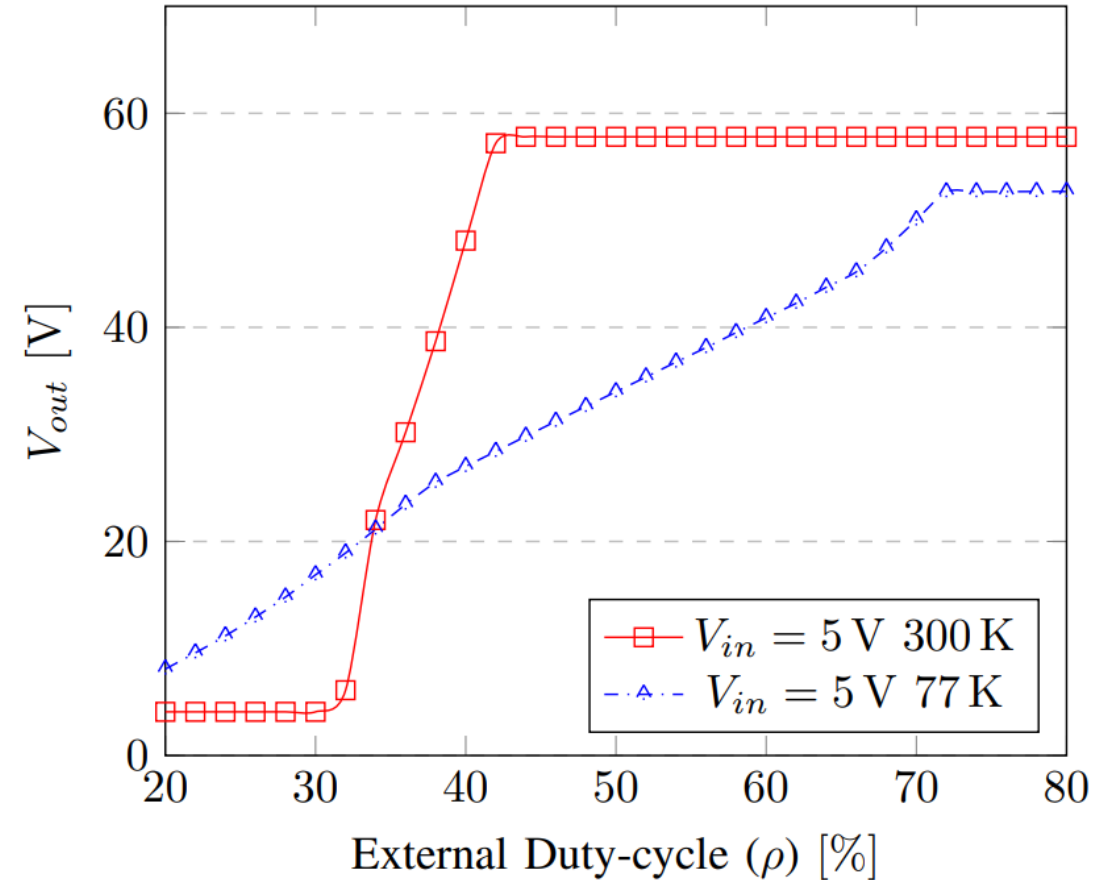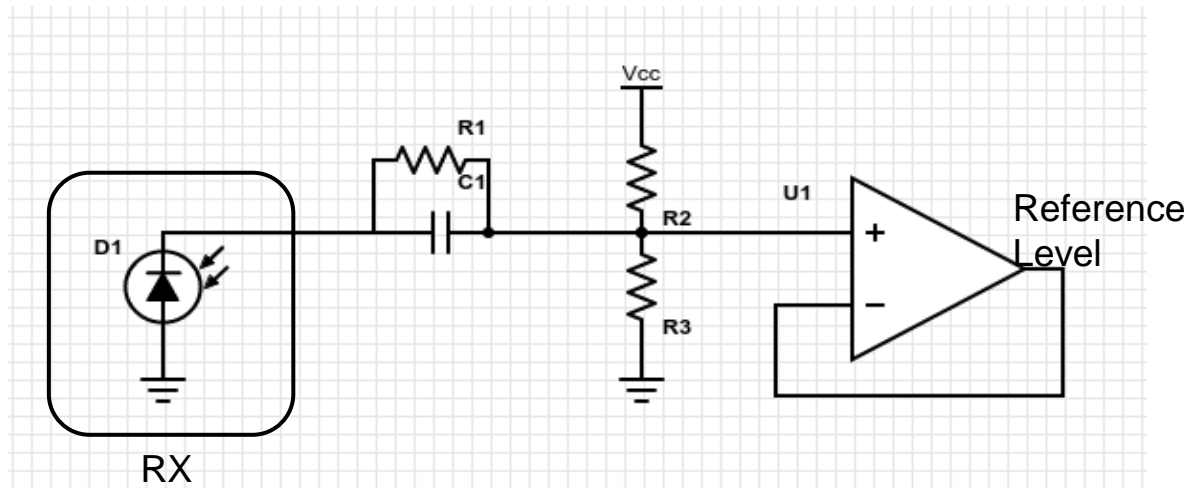
# Control design: external set point

- External PWM signal drove through optical fiber: **external set point**
- Reference level changes
- AC-coupling in case of external PWM, otherwise reference set by voltage divider




\*Test with electrical connection (waveform generator)

# Component characterization: OpAmps
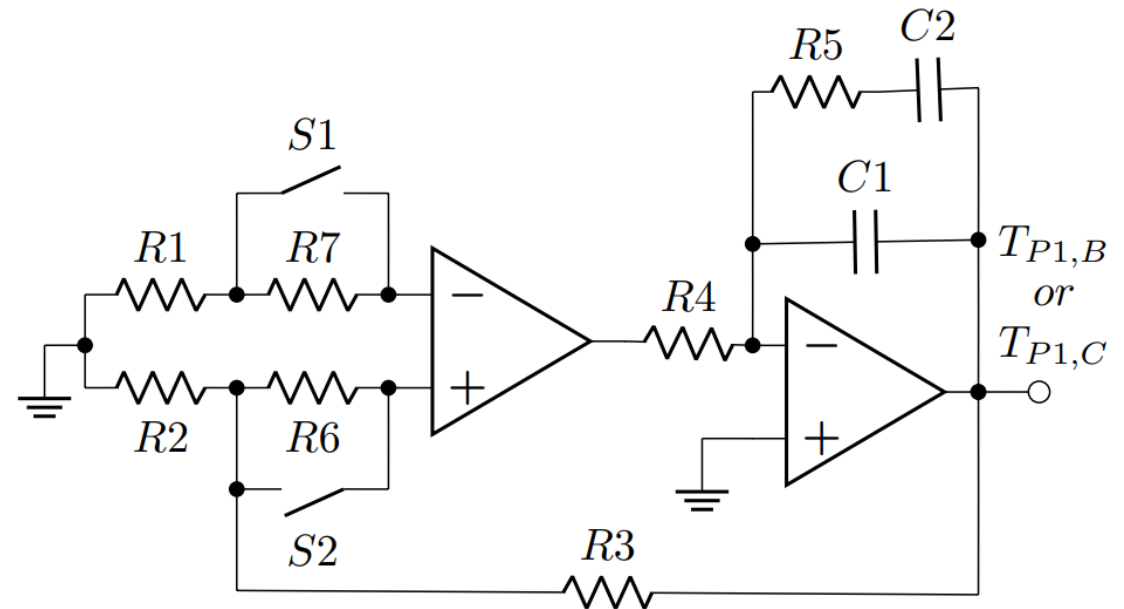
## Characterization circuit for OpAmps

- Offset voltage, quiescent current, offset and bias currents
- First test with DUT: OpAmp LMV321
- Auxiliary OpAmp: OP27G
- DUT in climate chamber with LN2 injection
- Data recovery at each temperature step
- Automatic test bench control



# Characterization testbed

- DUT in climate chamber with LN2 injection

Climatic chamber






Data acquisition unit

Auxiliary OpAmps at ambient temperatures

Semiconductor analyzer for quiescent current measurements
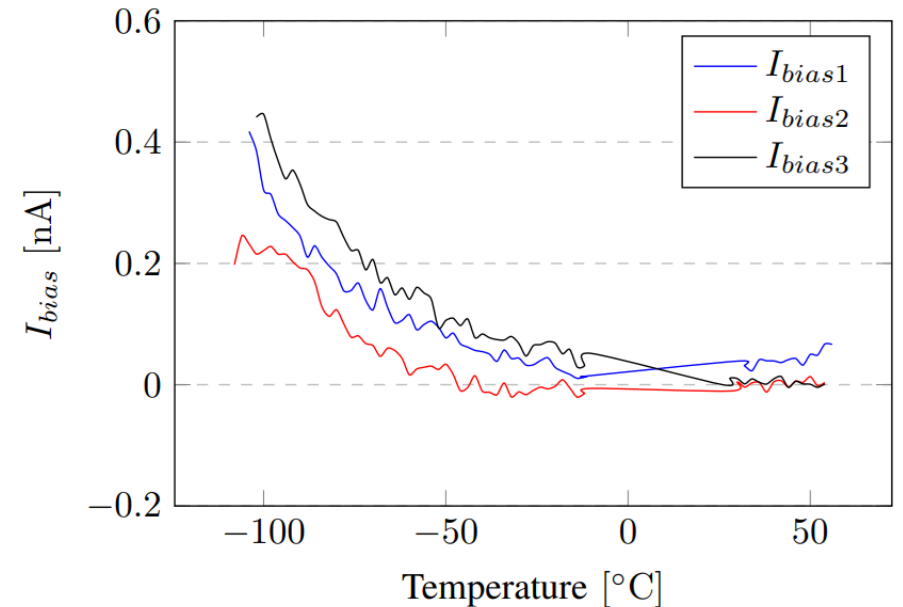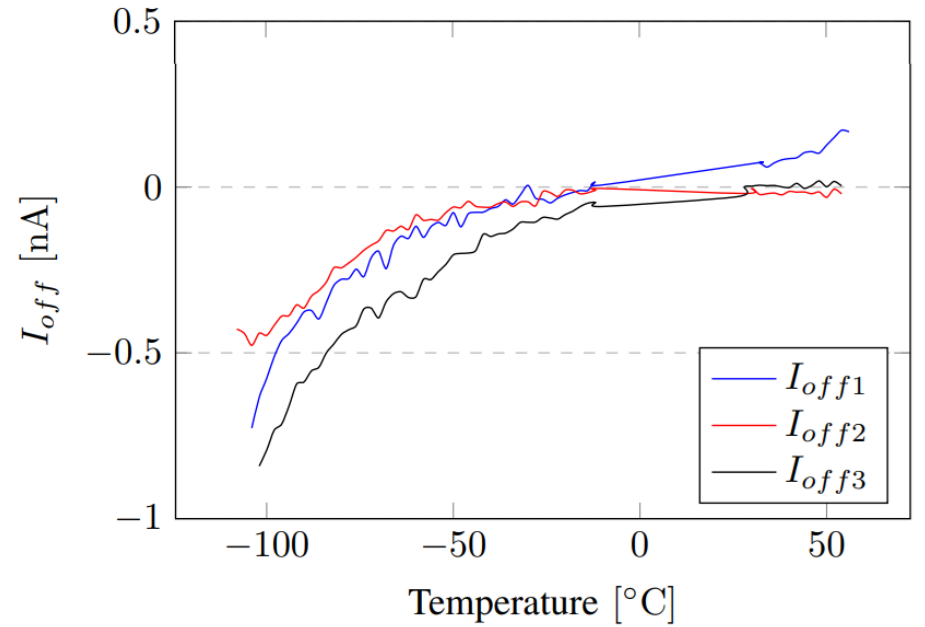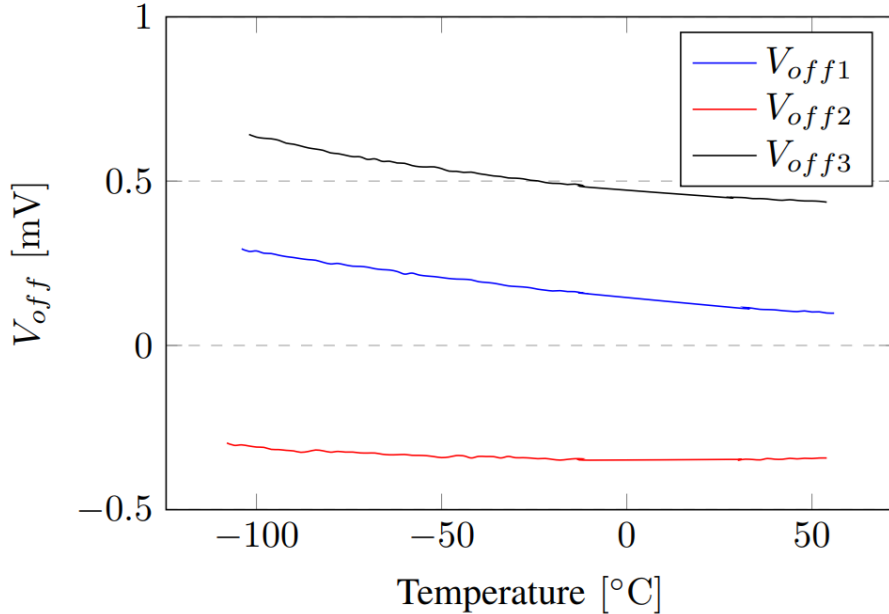
# Experimental results: OpAmp characterization




# Future developments

- Test of DC-DC external control through **optical fiber**
- Characterization of **different OpAmps**:
  - MCP6291
  - MCP6N11
  - LMV321
  - TLC271
  - AD8293
- Use of automated test bench for reliability tests for **active and passive devices**
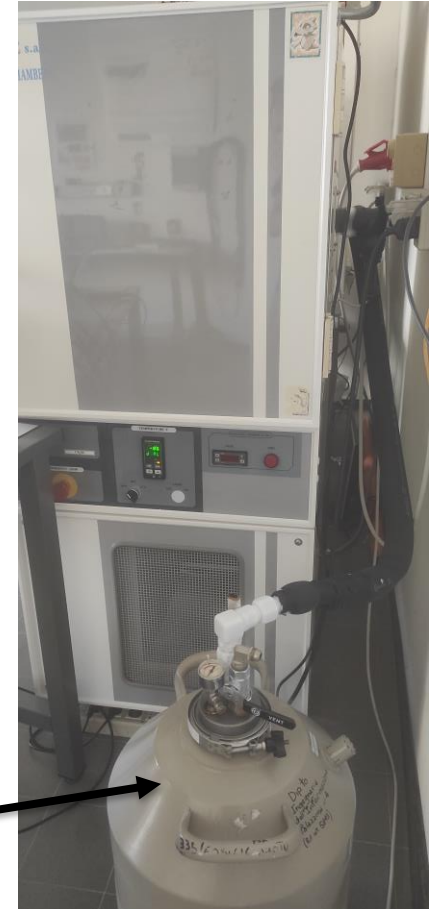
## Issues:

- **Dewar** with more capacity necessary
- **High-rate multiplexer** for data acquisition unit necessary



# Cryo PoF



1  
UNIVERSITÀ  
DI MILANO




Istituto Nazionale di Fisica Nucleare

MILANO MILANO DI PARMA








# From laser to SiPM – Cryo-PoF setup

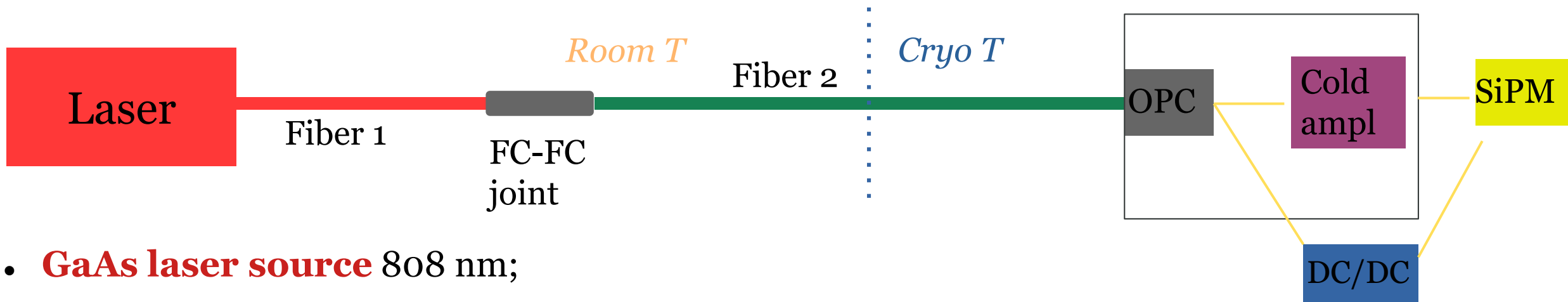

- **GaAs laser source** 808 nm;
- **Graded index multi mode optical fiber** with black plastic sheath;
- **Optical power converter**,  $V_{\max} = 6 \text{ V}$ , 30% efficiency in LN;
- **Cold amplifier** MiB for DUNE HD,  $V_{\text{in}} = 3.3 \text{ V}$ ;
- **DC/DC** boost converter **V1** INFN Mi → placed in a metallic box to reduce noise, possibility to tune SiPM bias as a function of laser power;
- **Hamamatsu SiPM**, 1 flexi board with **20 SiPMs** in parallel.

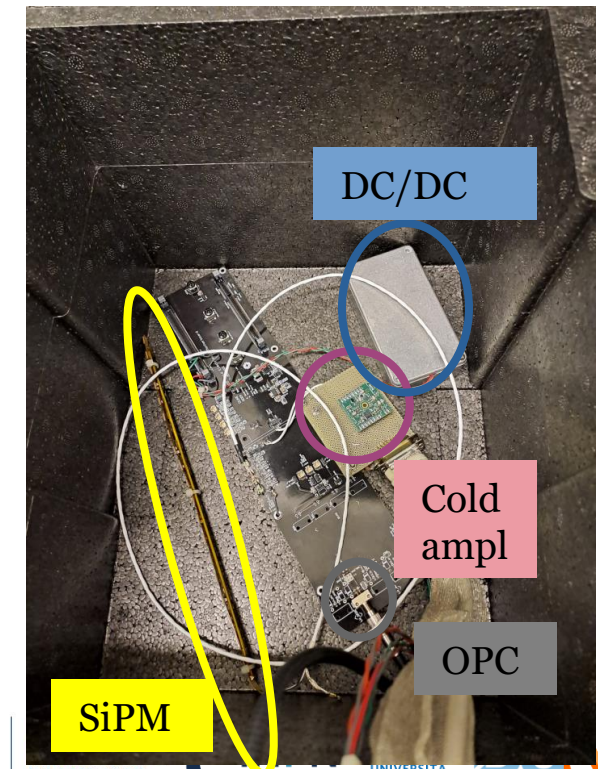


# From laser to SiPM - Results

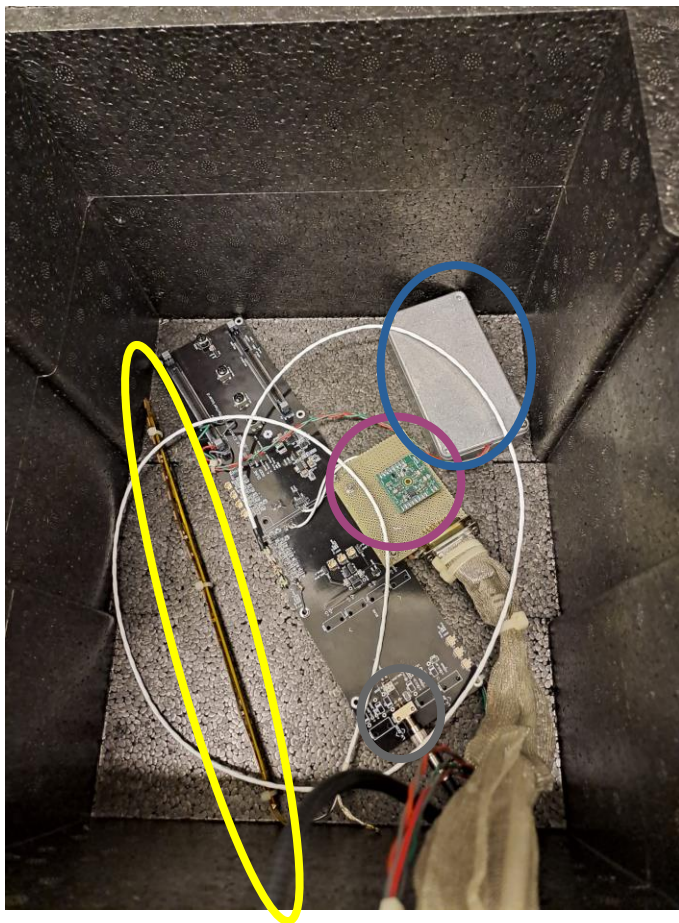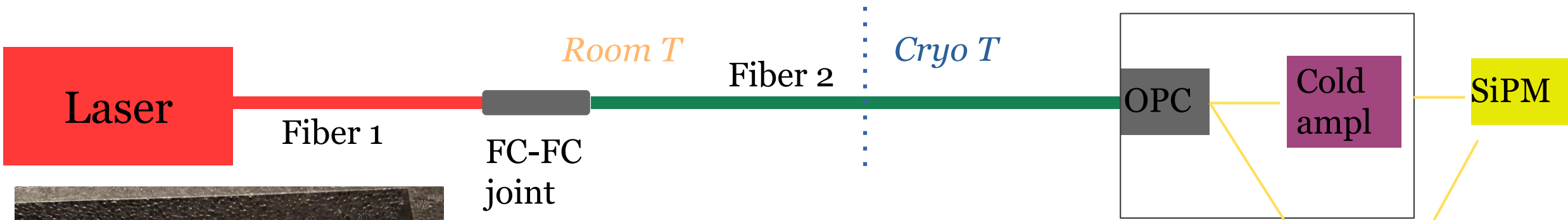

- Tests in LN ( T = 77 K);
- **20 SiPMs** in parallel ( 1 flexi board);
- **three SiPM bias** tested : 45 V, 46 V, 47 V (3, 4, 5 V ov);
- evaluation of the **Signal to Noise Ratio** (SNR);
- comparison of the results: PoF vs copper line.





# From laser to SiPM – PoF Results

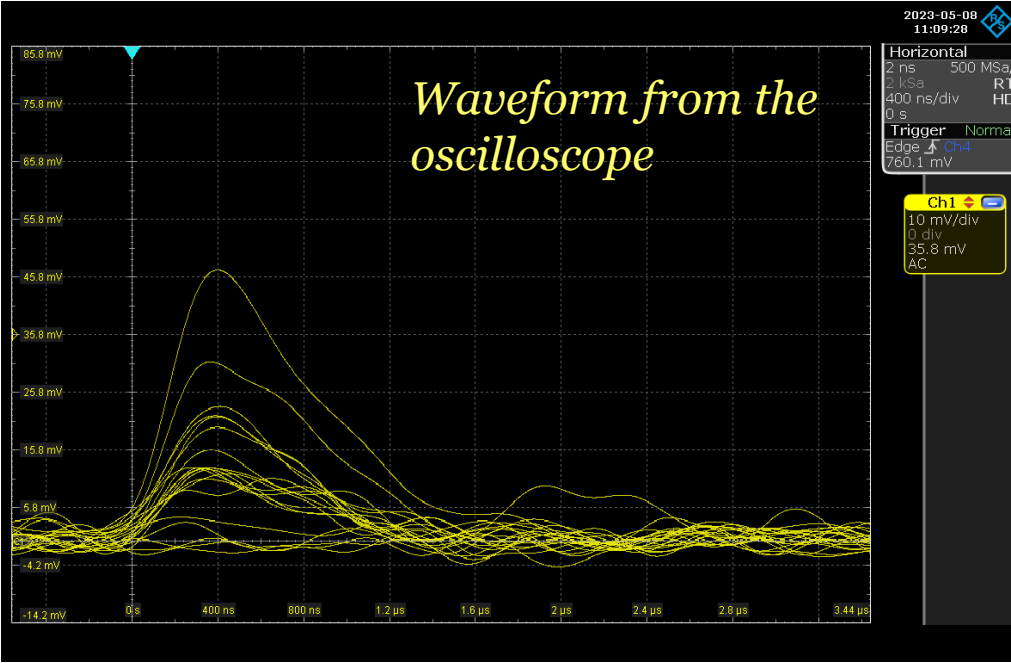

$$V_{in \text{ laser}} = -2.83 \text{ V}$$

$$V_{bias} = 46 \text{ V} - 4 \text{ V ov}$$

Charge integral

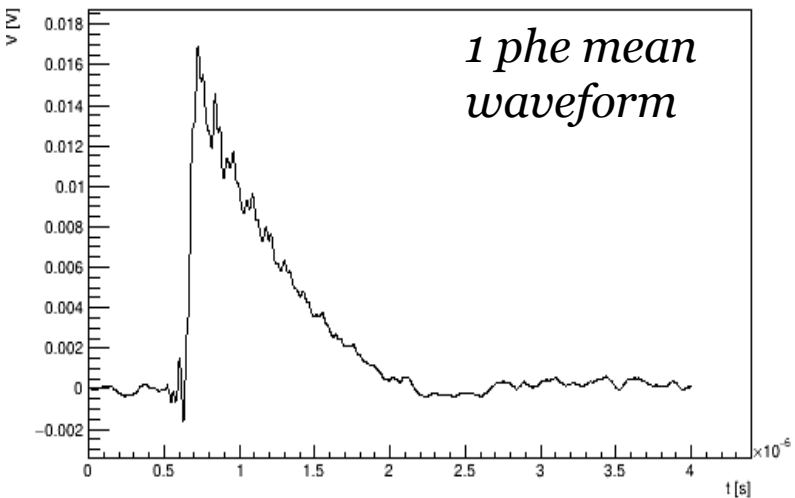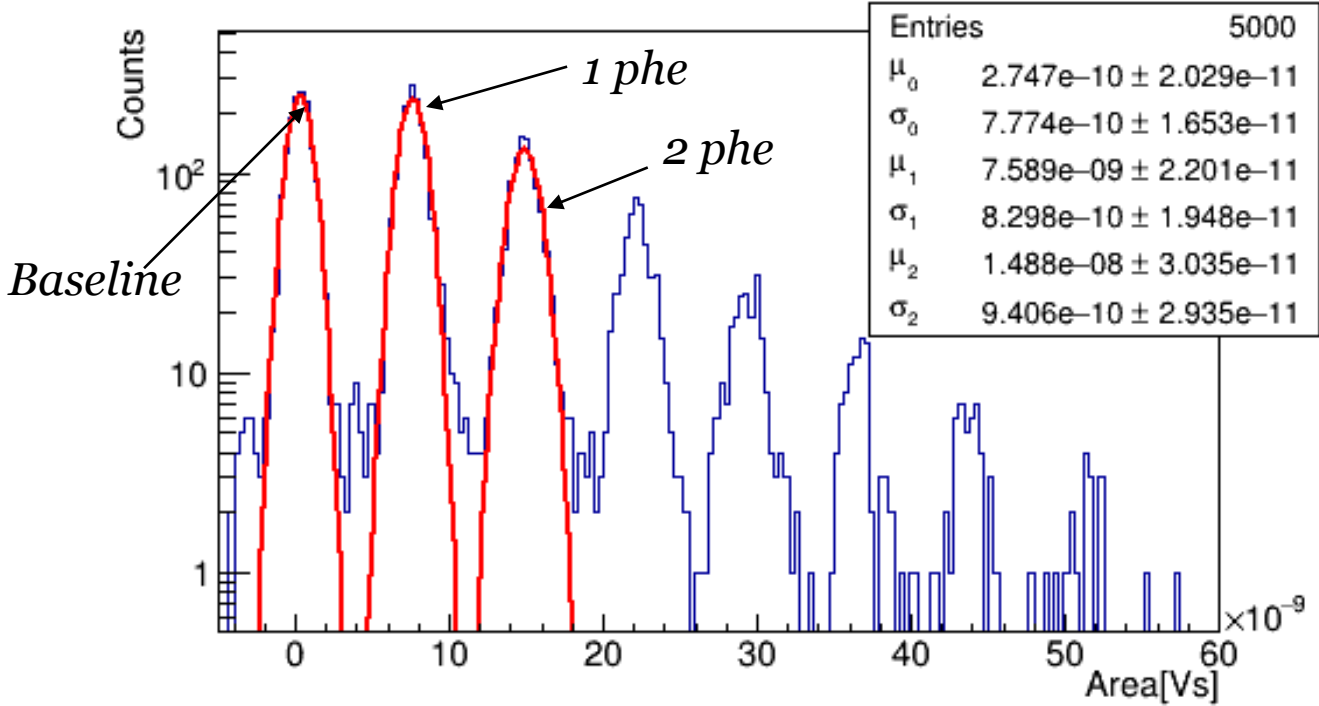

**SNR = 9.409**


SNR is calculated for each SiPM bias tested.

		<b>SNR</b>	
<b>SiPM bias</b>	<b>Overvoltage</b>	<i>Copper cable</i>	<i>PoF</i>
45 V	3 V	7.830	7.520
46 V	4 V	10.665	9.409
47 V	5 V	13.004	11.070

The performances of the PoF are comparable with the copper cable ones.

# Back up

# DC/DC boost converter

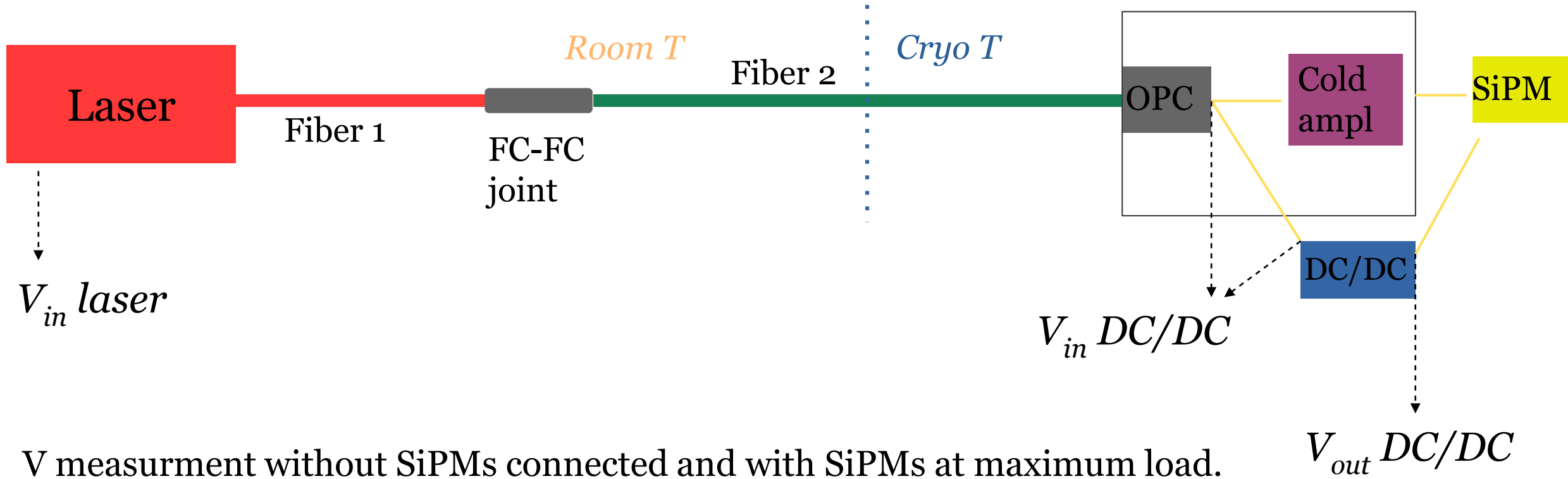

V measurment without SiPMs connected and with SiPMs at maximum load.




$V_{in} \text{ laser}$  → V laser source input, proportional to the laser power;

$V_{in} \text{ DC/DC}$  → V output from the OPC, that is the DC/DC input ;

$V_{out} \text{ DC/DC}$  → V output from the DC/DC, that is the SiPMs bias voltage.









# DC/DC boost converter

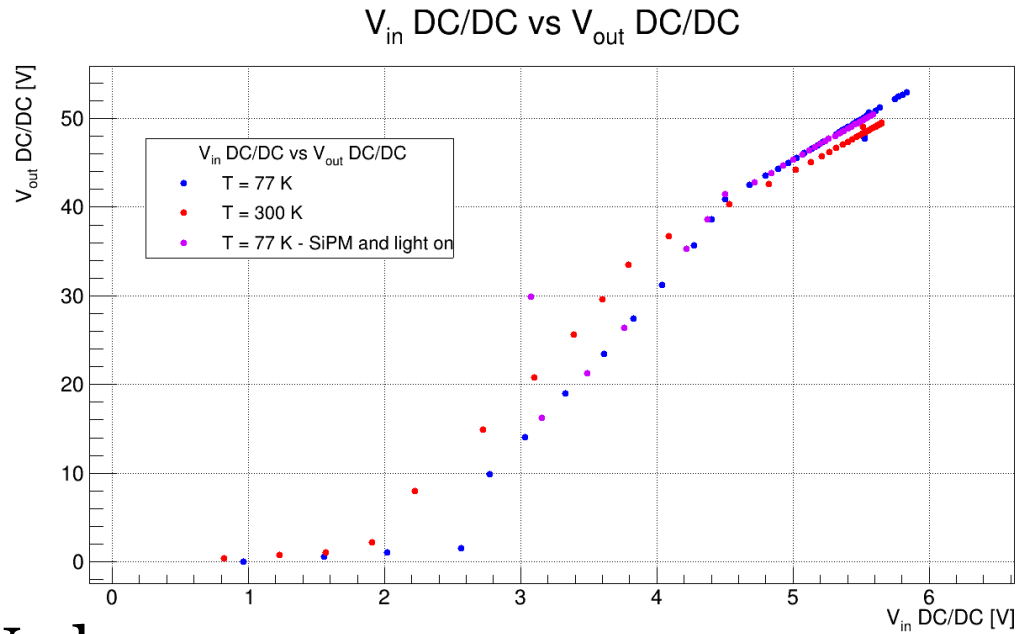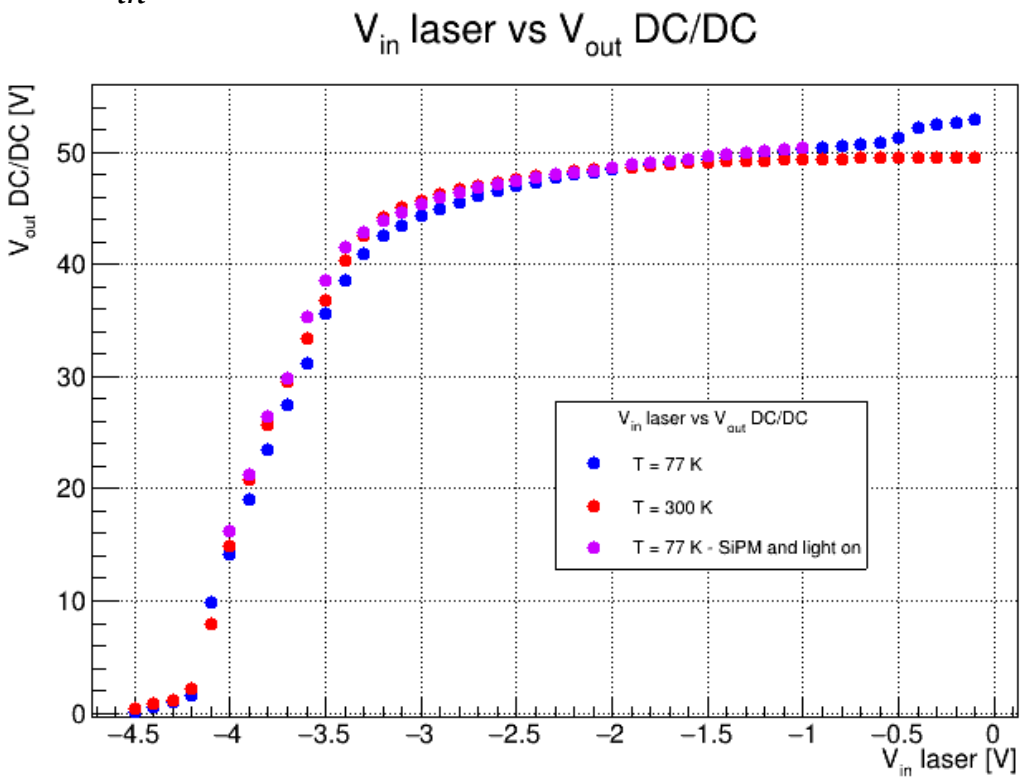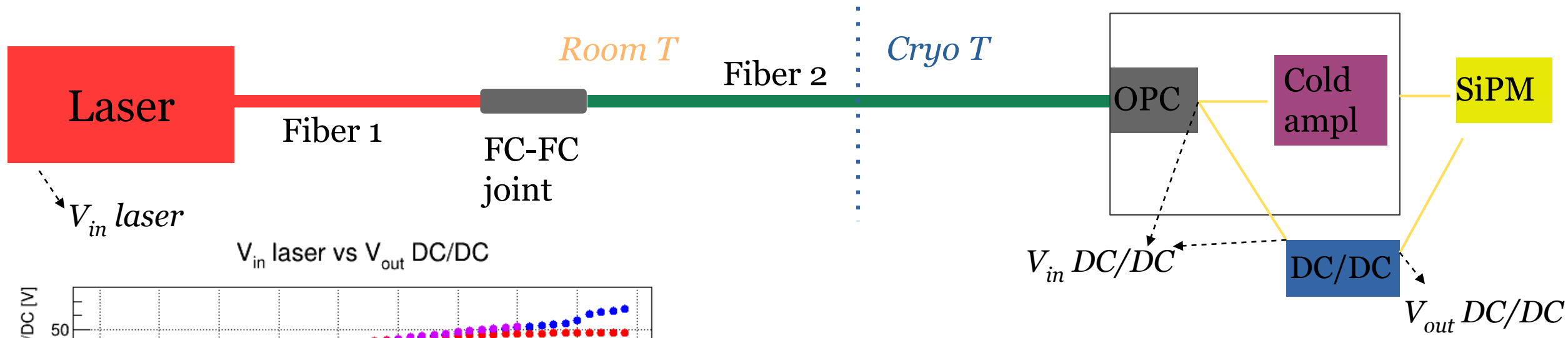


$V_{out\ DC/DC}$  increases as a function of  $V_{in\ laser}$ .

Waveform from the oscilloscope

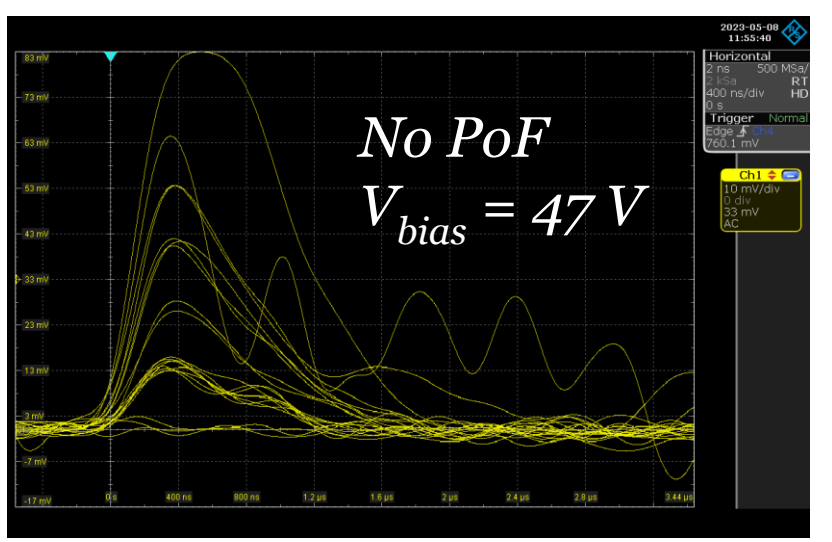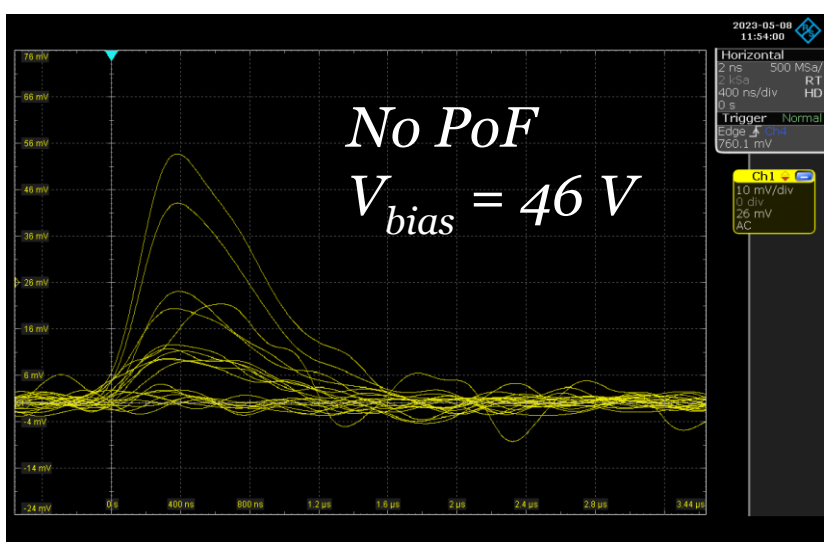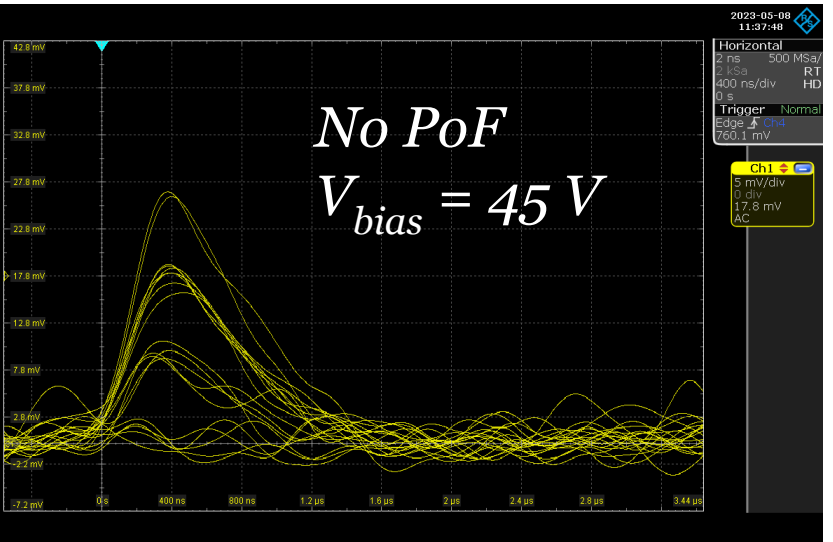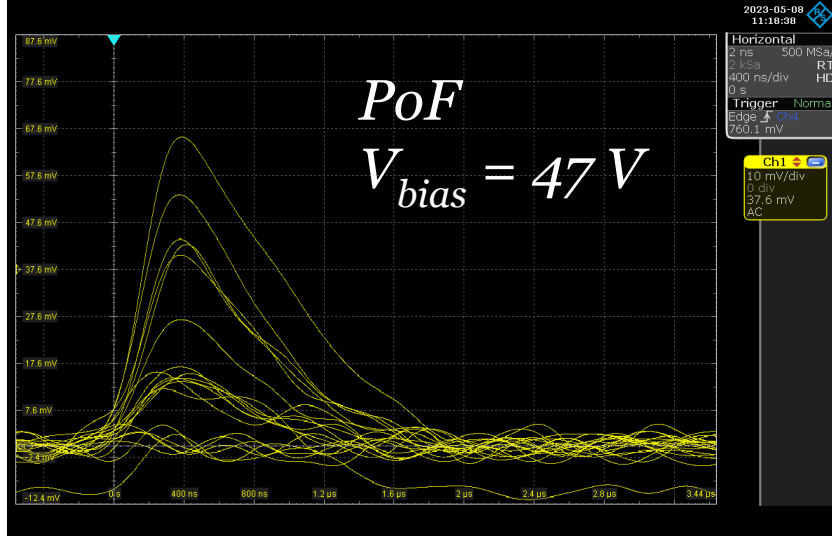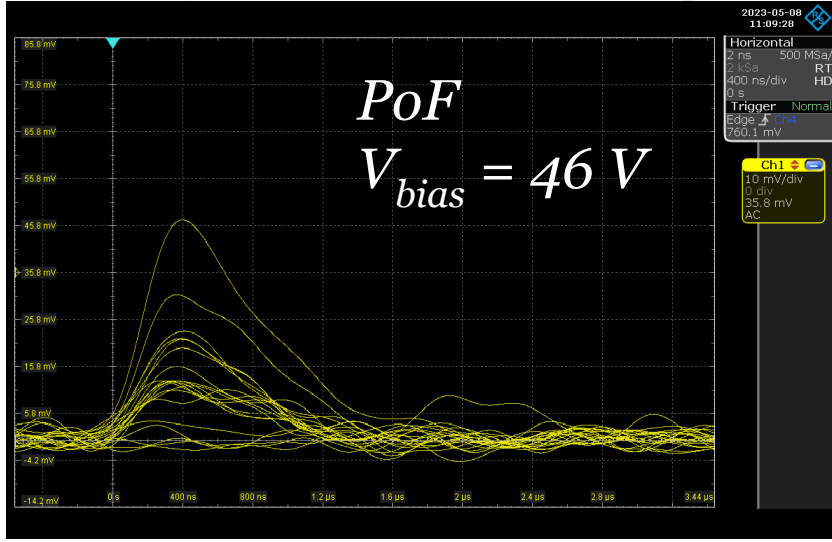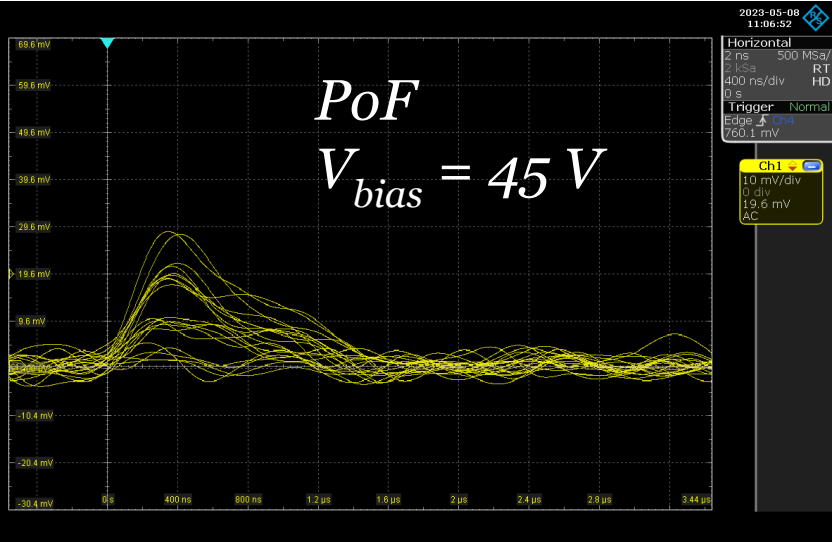


## Copper cable

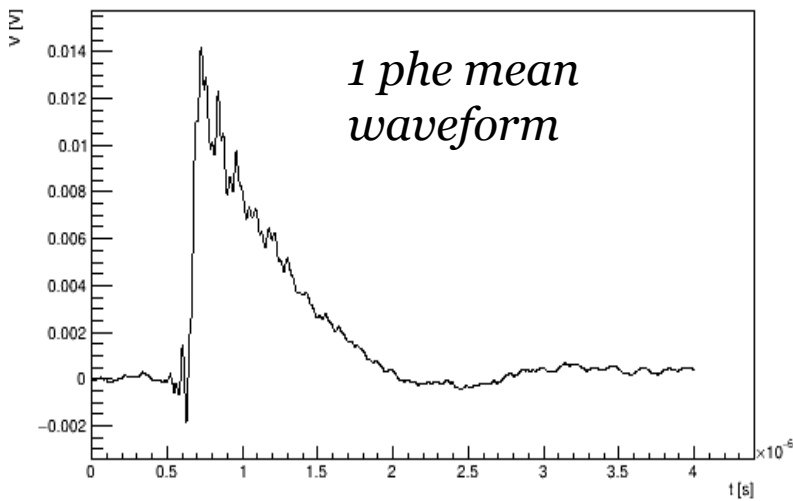


$$V_{\text{bias}} = 45 \text{ V} - 3 \text{ V ov}$$

**SNR = 7.830**

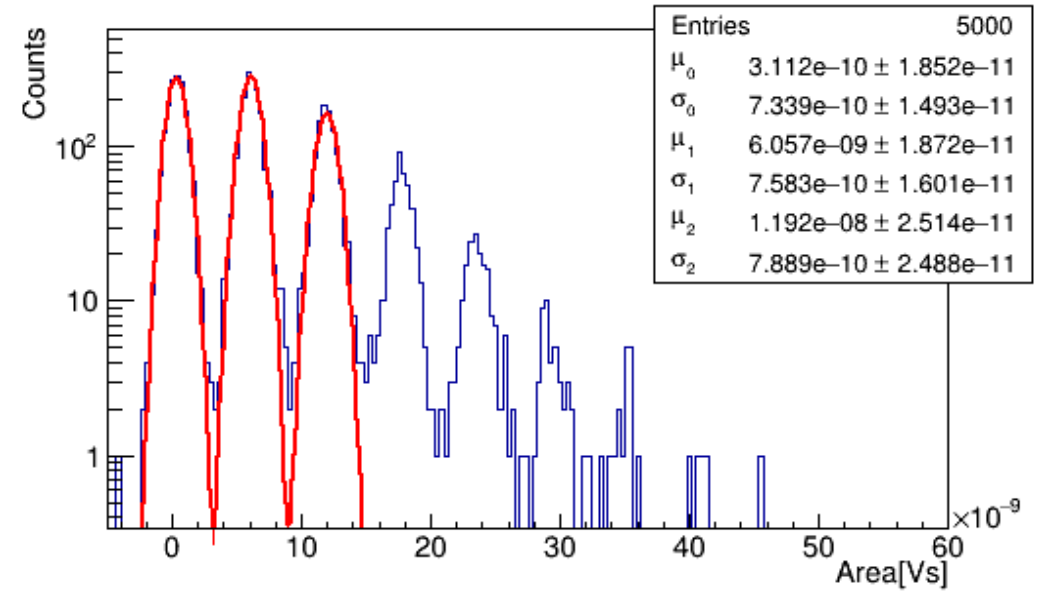


## PoF

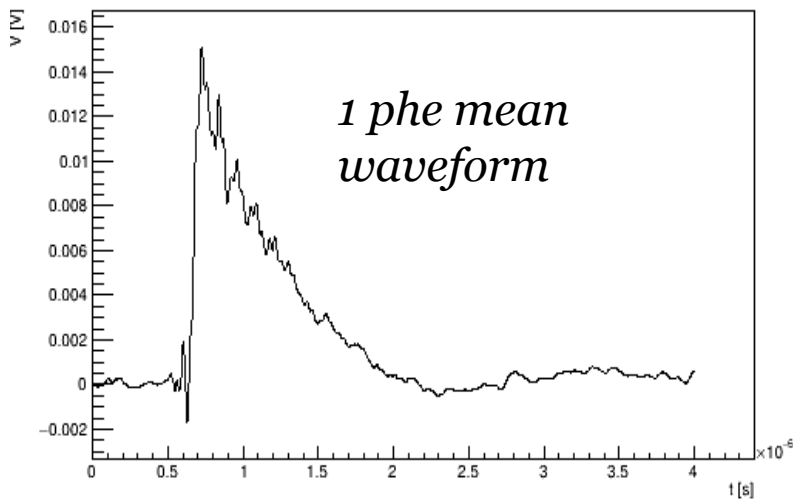


$$V_{\text{in laser}} = -2.97 \text{ V}$$
$$V_{\text{bias}} = 45 \text{ V} - 3 \text{ V ov}$$

**SNR = 7.520**

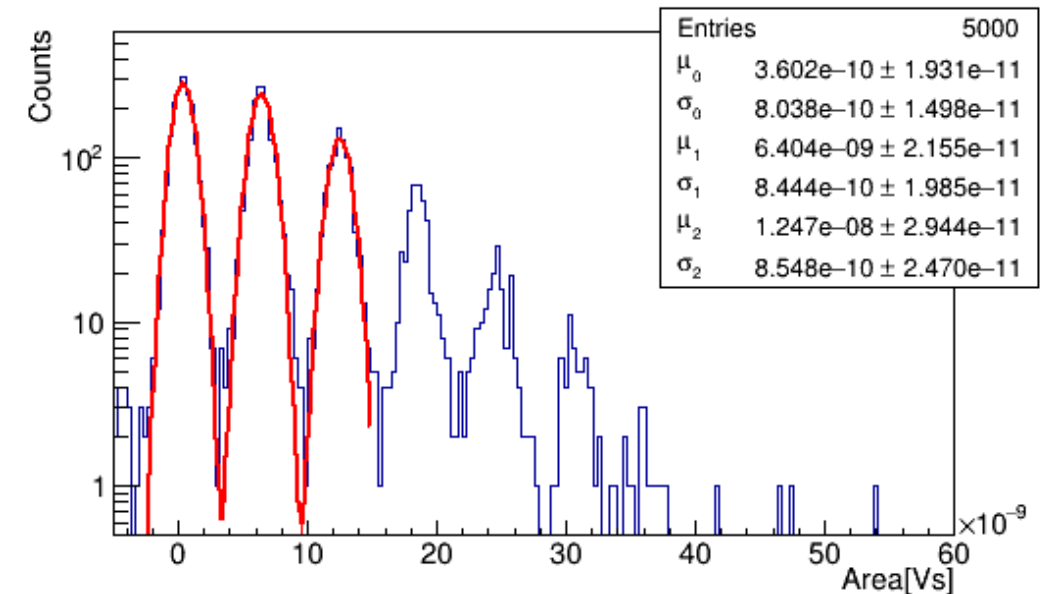


## Copper cable

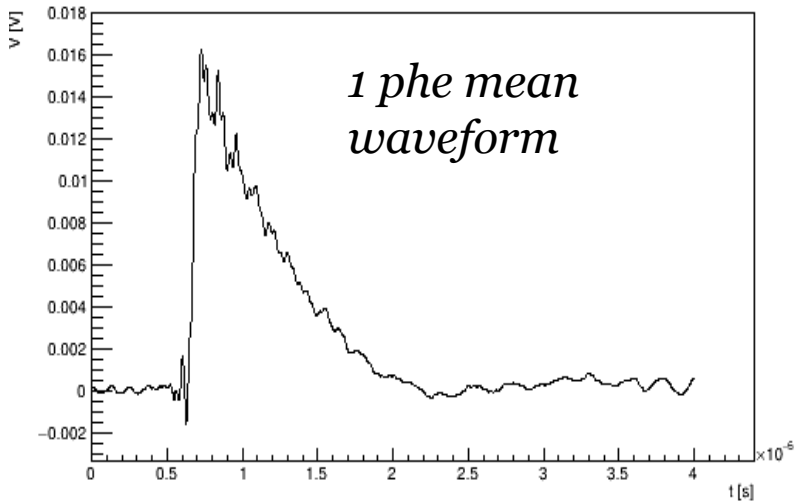


$$V_{\text{bias}} = 46 \text{ V} - 4 \text{ V ov}$$

**SNR = 10.665**

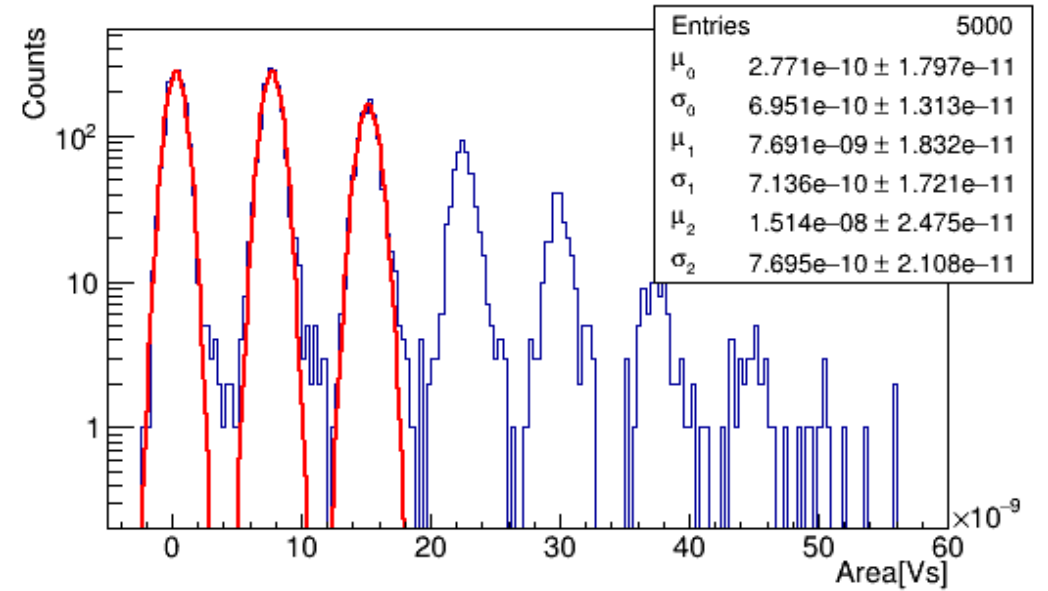


## PoF

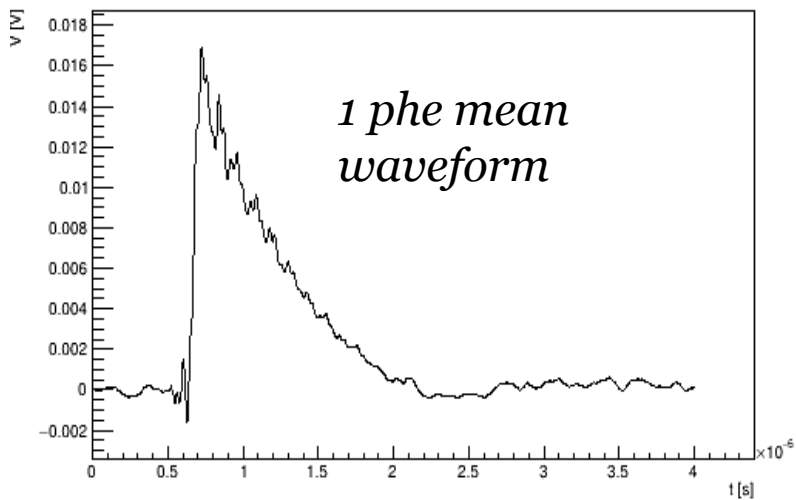


$$V_{\text{in laser}} = -2.83 \text{ V}$$
$$V_{\text{bias}} = 46 \text{ V} - 4 \text{ V ov}$$

**SNR = 9.409**

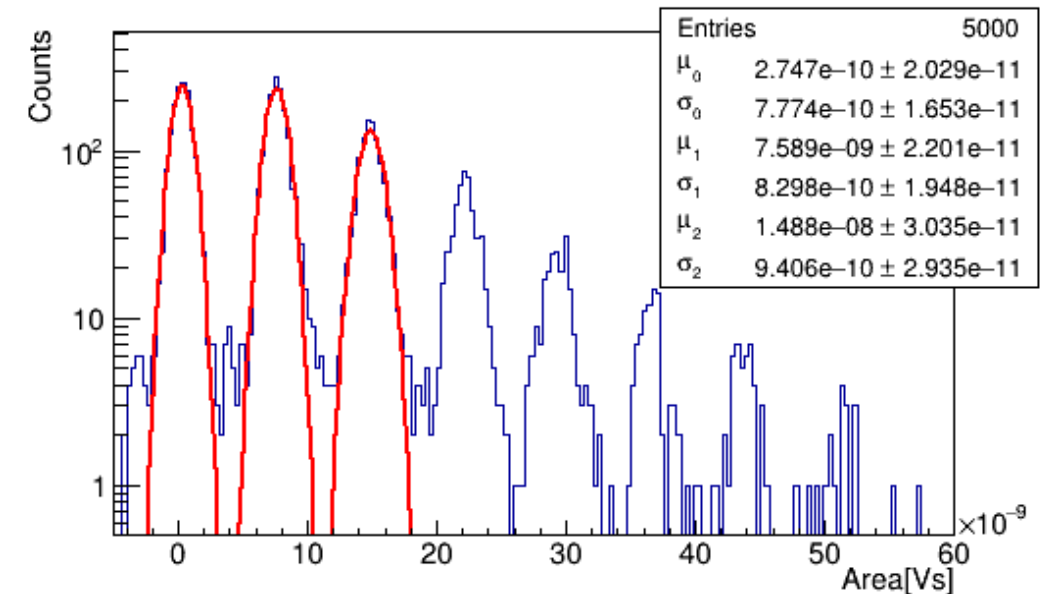


## Copper cable

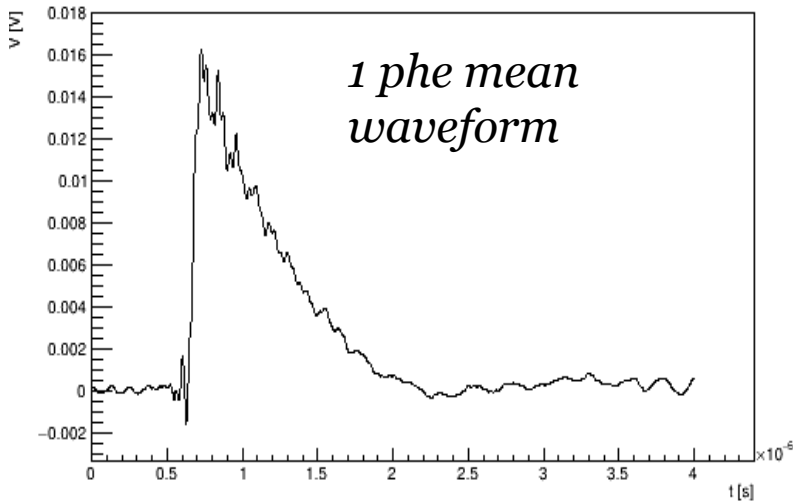


$$V_{\text{bias}} = 47 \text{ V} - 5 \text{ V ov}$$

**SNR = 13.004**

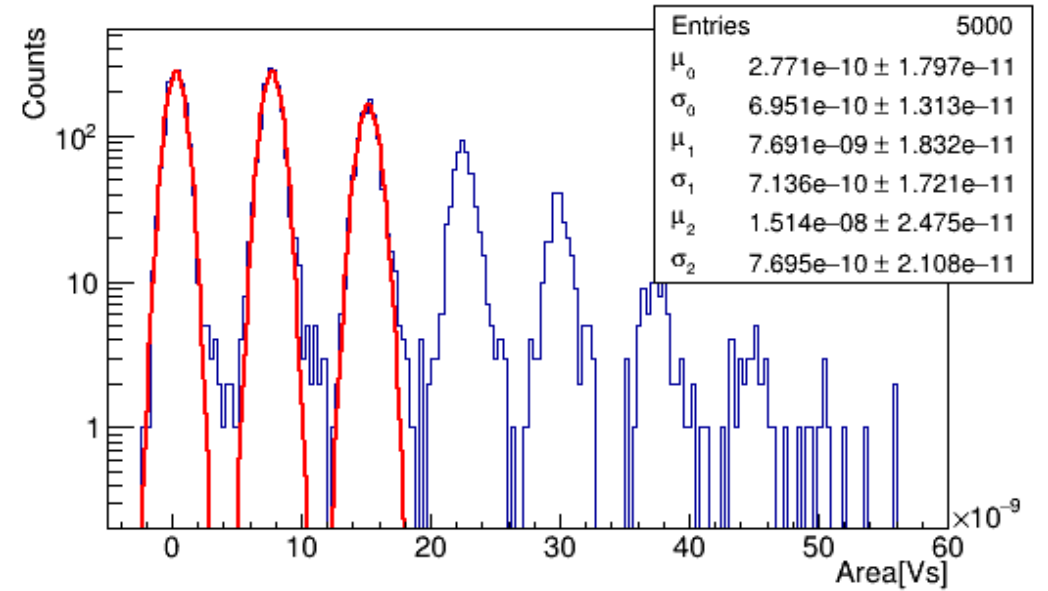

## PoF

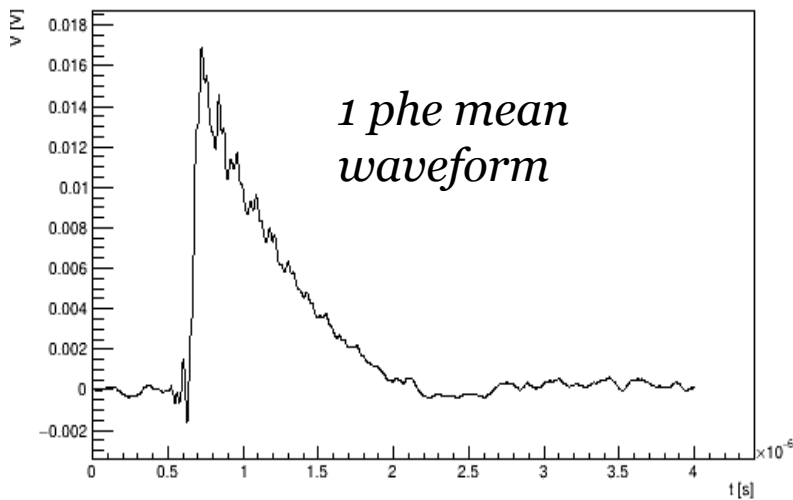

$$V_{\text{in laser}} = -2.61 \text{ V}$$
$$V_{\text{bias}} = 47 \text{ V} - 5 \text{ V ov}$$

**SNR = 11.070**

