

Prototype of a Gigabit Data Transmitter in 65-nm CMOS for DEPFET Pixel Detectors at Belle-II

Tetsuichi Kishishita



H. Krüger, T. Hemperek, M. Lemarenko, M. Koch, M. Gronewald, N. Wermes

University of Bonn

Outline

- ◆ Pixel Detector (PXD) at Belle-II
- ◆ Data Handling Processor (DHP)
- ◆ Gbit Data Transmitter
- ◆ Measurement Results
- ◆ Summary

Belle-II Experiment at Super-KEKB

 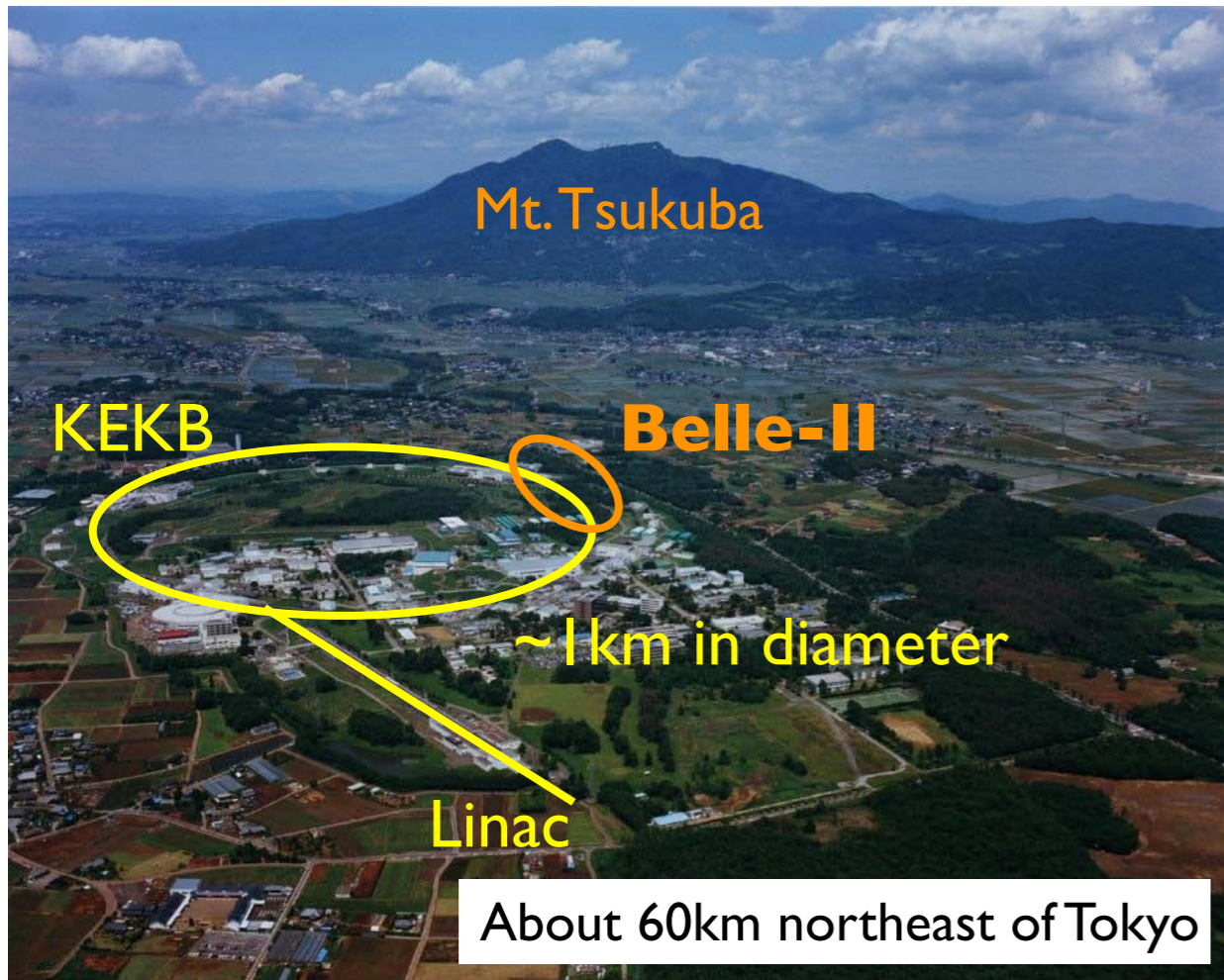


KEKB/Belle upgrade (2010–2013)

- study CP violation via $B^0/B^0\text{-bar}$ decays
- rare decay modes → more statistics

- ◆ Super-high luminosity $\sim 8 \times 10^{35} \text{ cm}^{-2}\text{s}^{-1}$ (**x40 higher**)
- ◆ Radiation environment: **~1 Mrad per year**
- ◆ Refurbishment of accelerator and detector required

Pixel Detector with DEPFET sensor

 - ◆ p-FET (MOSFET) on a **fully depleted bulk** (sideward depletion)
- ◆ signal electrons accumulated in the internal gate modulate the transistor current ($g_q \sim 600 \text{ pA/e}^-$) → **low C_D , low noise**
- ◆ charge collection during external gate being switched off → **low power**
- ◆ integrating device, discharge internal gate with positive pulse applied to the clear contact



→ See posters by Peter Kodys & Christian Koffmane

Front-end ASICs for PXD

- Active pixel area thinned to 50 μm
- Independent read-out from both sides
- ASICs bump bonded onto the DEPFET substrate

◆ SWITCHER

- high voltage (10-20V) pulses for clear and gate lines

◆ DCD (Drain Current Digitizer)



- receive drain current signals from DEPFET
- sample and subtract pedestal currents
- digitize signals

- 4:1 multiplex ADC outputs

◆ DHP (Data Handling Processor)

- data reduction
- sending data off the module to the backend

“All-silicon” DEPFET module

  


Data Handling Processor (DHP)

◆ **Functionality**

- Module controller
 - JTAG bus to DCD and SWITCHER chips
 - Clock & timing generation & distribution
- Data reduction (1/20)
 - 0-suppression
 - triggered r/o

◆ **Data processing**

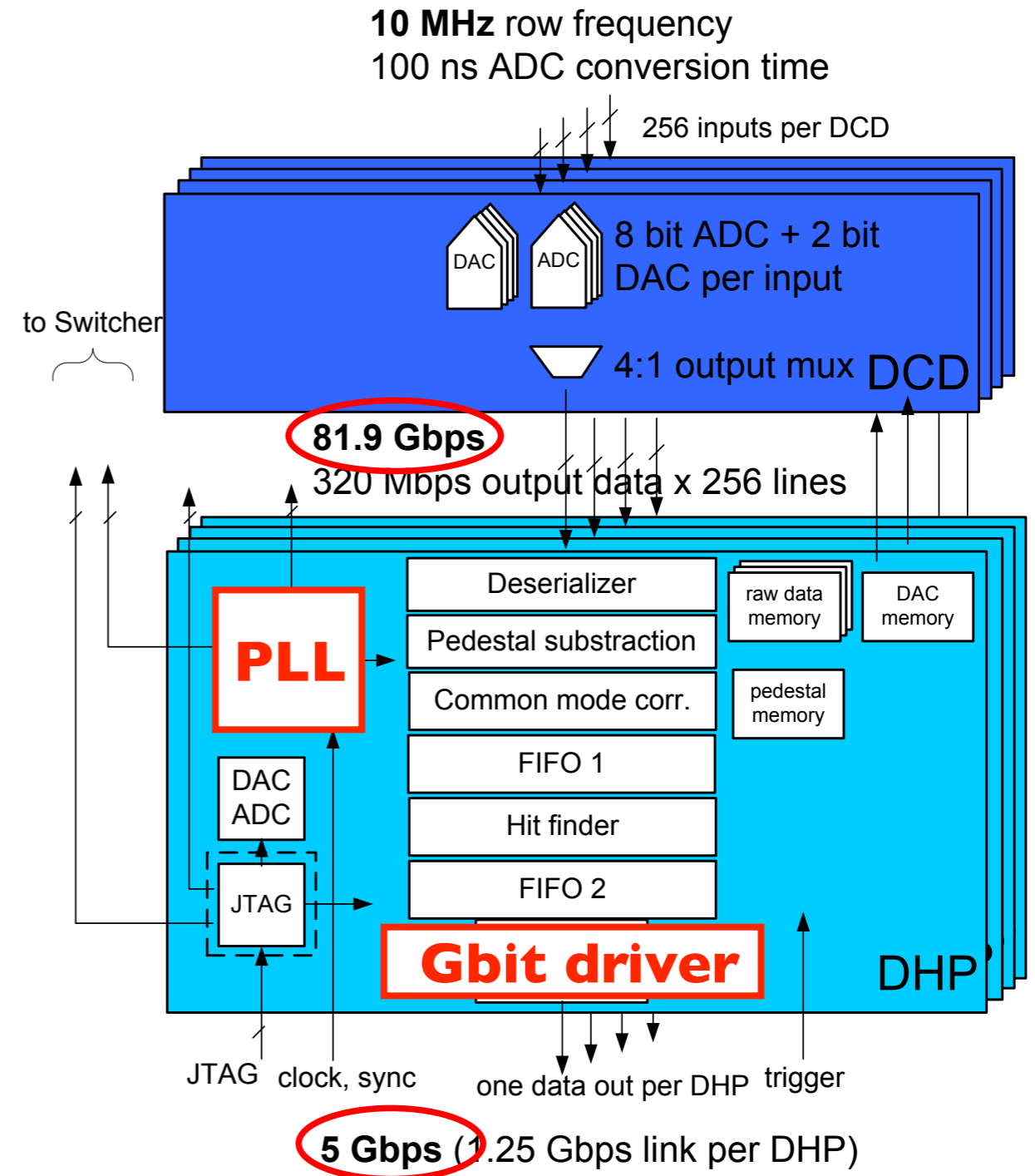- Raw data buffer
- Fixed pattern noise correction
- Hit finder (FIFO1 + FIFO2)
- Framing (AURORA)
- Serializer + Gbit link driver




Synchronized clock generation (PLL) + Gbit link driver

DHP Data Link Specifications

- ◆ 1.6 Gbps per DHP chip, four links per module (incl. 20 % overhead)
- ◆ Electrical link (optical data transmission not feasible due to radiation tolerance requirements)
- ◆ **40 cm flex-cable** up to patch panel (PP)
- ◆ **12-15m twisted pair** (TWP) cable to DHH (Data Handling Hybrid)

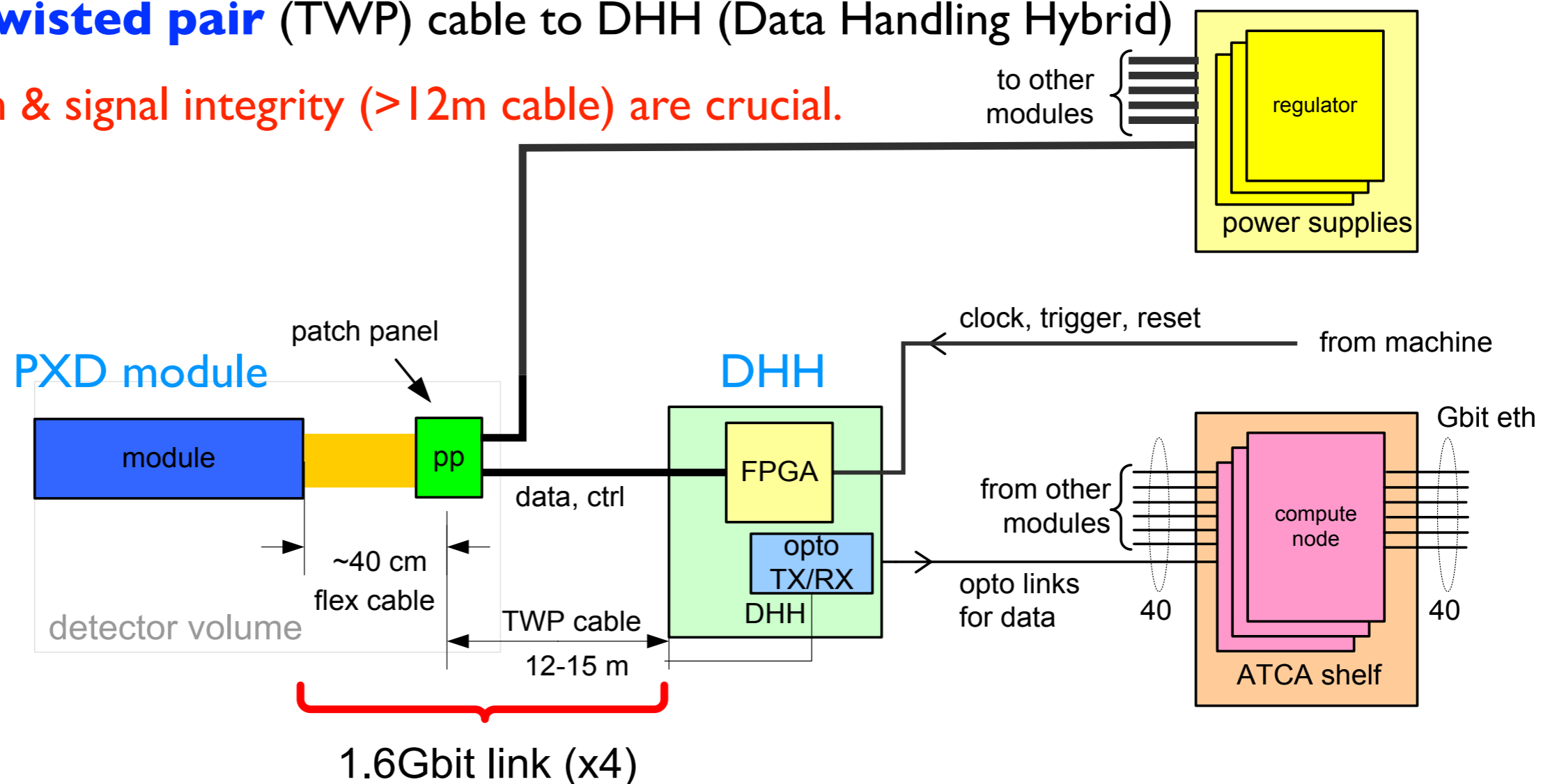
Link bandwidth & signal integrity (> 12m cable) are crucial.



Test Chips



- ◆ DHP 0.1, **IBM 90nm**, submitted March 2010
 - C4 bumps
 - **half size** chip (32 inputs)
 - Full data processing
(1.6 GHz PLL , Gbit link driver)
- ◆ DHP 0.2, **IBM 90nm**, submitted July 2011
 - **full size** chip (64 inputs)
 - improved data processing & hit finder
 - CML driver with programmable pre-emphasis
 - Bias DACs & temperature sensor
- ◆ **DHPT 0.1, TSMC 65nm**, submitted Oct 2011
 - 4 separate chiplets:

Analog designs are challenging.

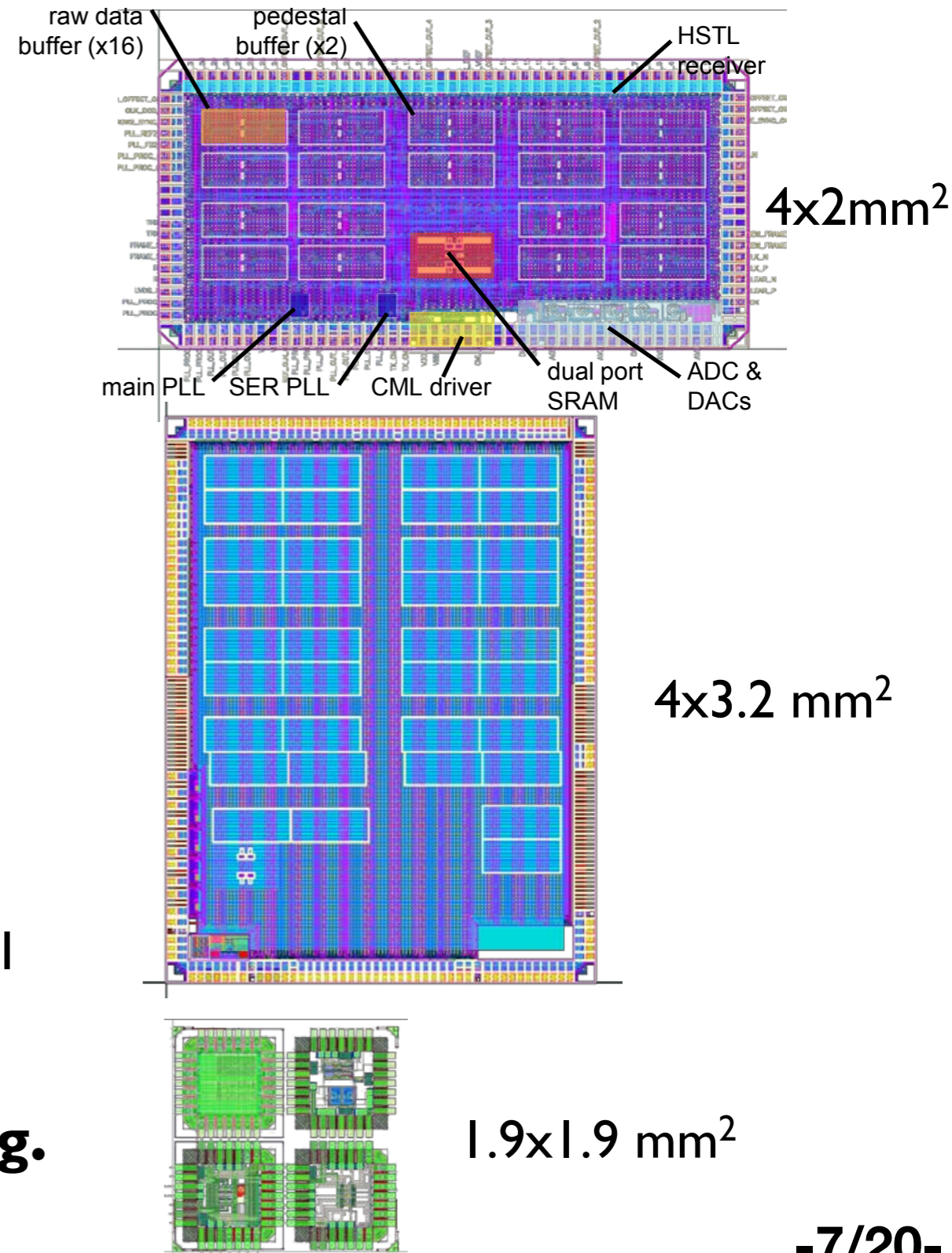

DHPT0.1 with TSMC 65-nm CMOS

 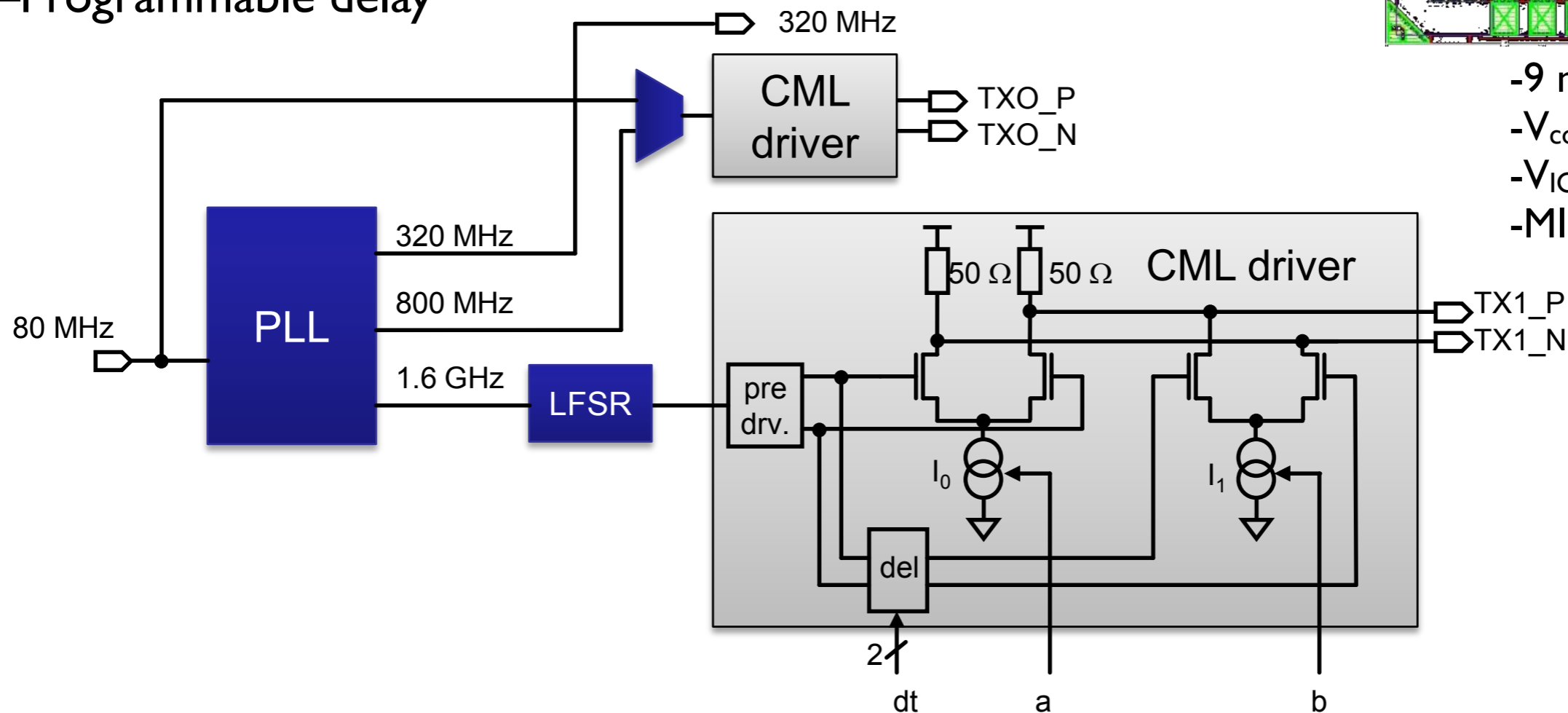
- ◆ **PLL (Phase-Locked Loop)**
 - 80 MHz reference clock
 - 1.6 GHz, 800MHz & 320 MHz outputs
- ◆ **Pseudo random bit sequence generator**
 - 8 bit LFSR
- ◆ **CML link driver** with programmable pre-emphasis
 - Two differential pairs with adj. bias currents
 - Programmable delay





- 9 metal layers
- $V_{\text{core}}=1.2\text{V}$
- $V_{\text{IO}}=1.8\text{V}$
- MIM option

Charge-pump PLL

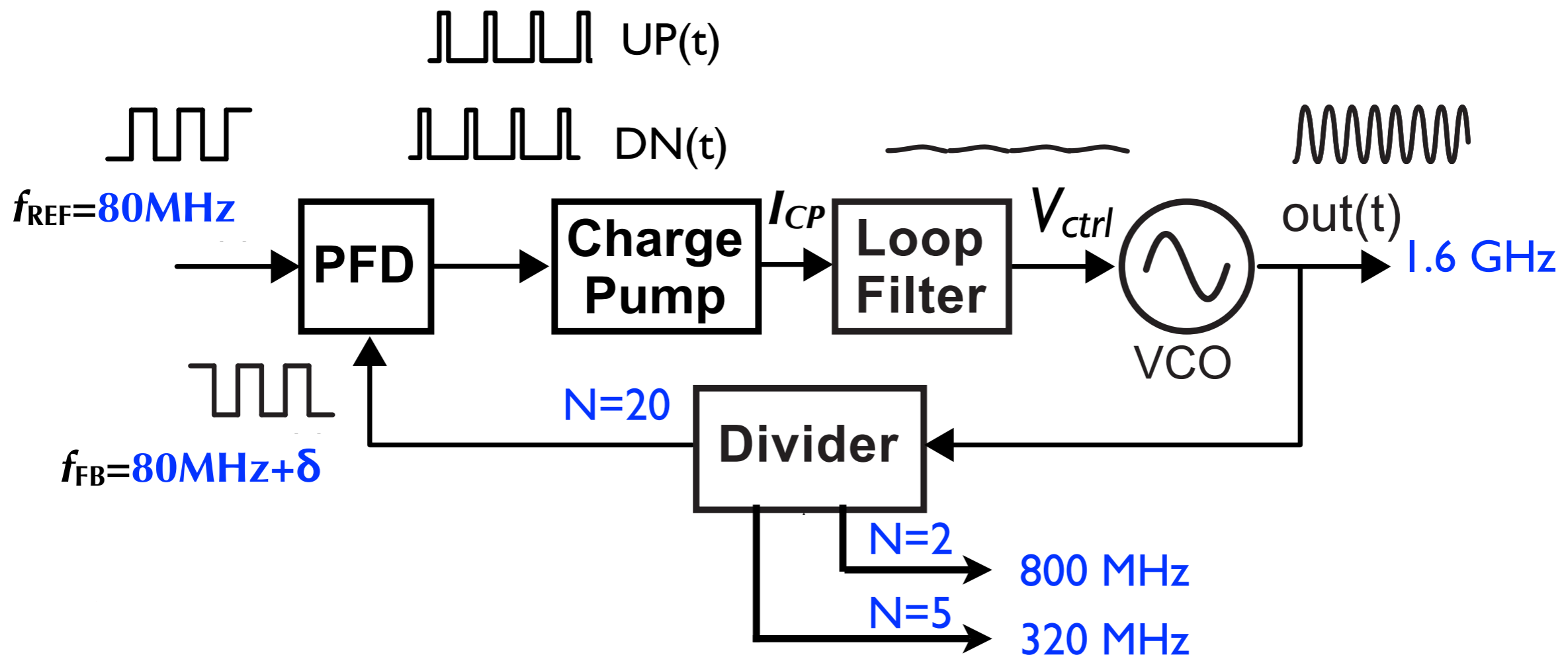- ◆ Voltage Controlled Oscillator (VCO) provides oscillating waveform with variable frequency
- ◆ PLL synchronizes VCO frequency to input reference freq. through feedback
- ◆ Use digital counter structure to divide VCO frequency





more schematic details...

 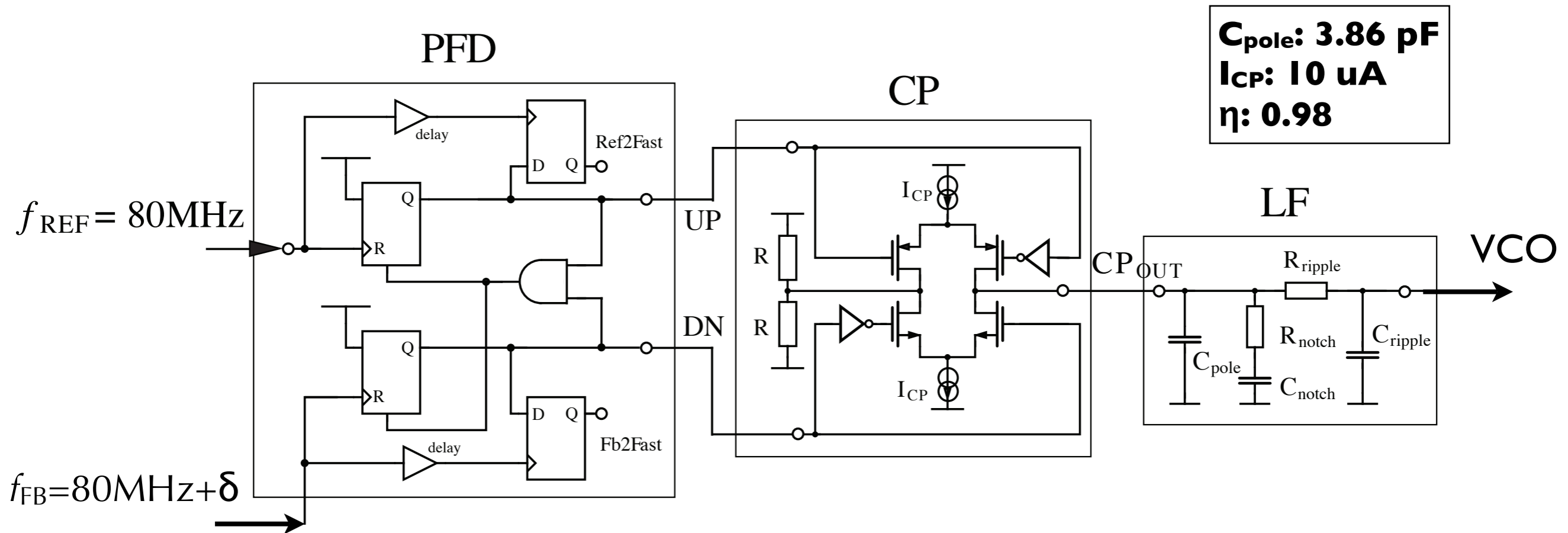


- ◆ Phase-Frequency Detector (PFD): classical two flipflops structure, additional error detection circuit
- ◆ Charge-pump (CP): differential structure with dummy branch
- ◆ Loop-filter (LPF): MIM structures, well-tuned parameters for PLL stability

more schematic details...

 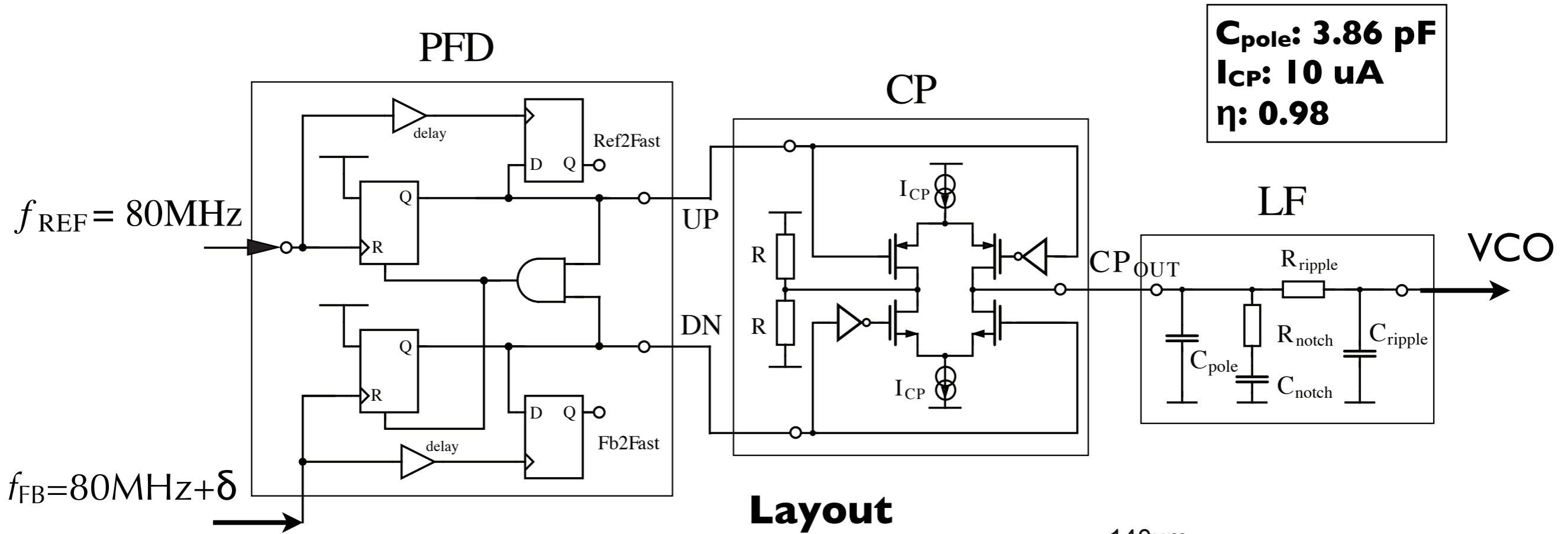


Layout

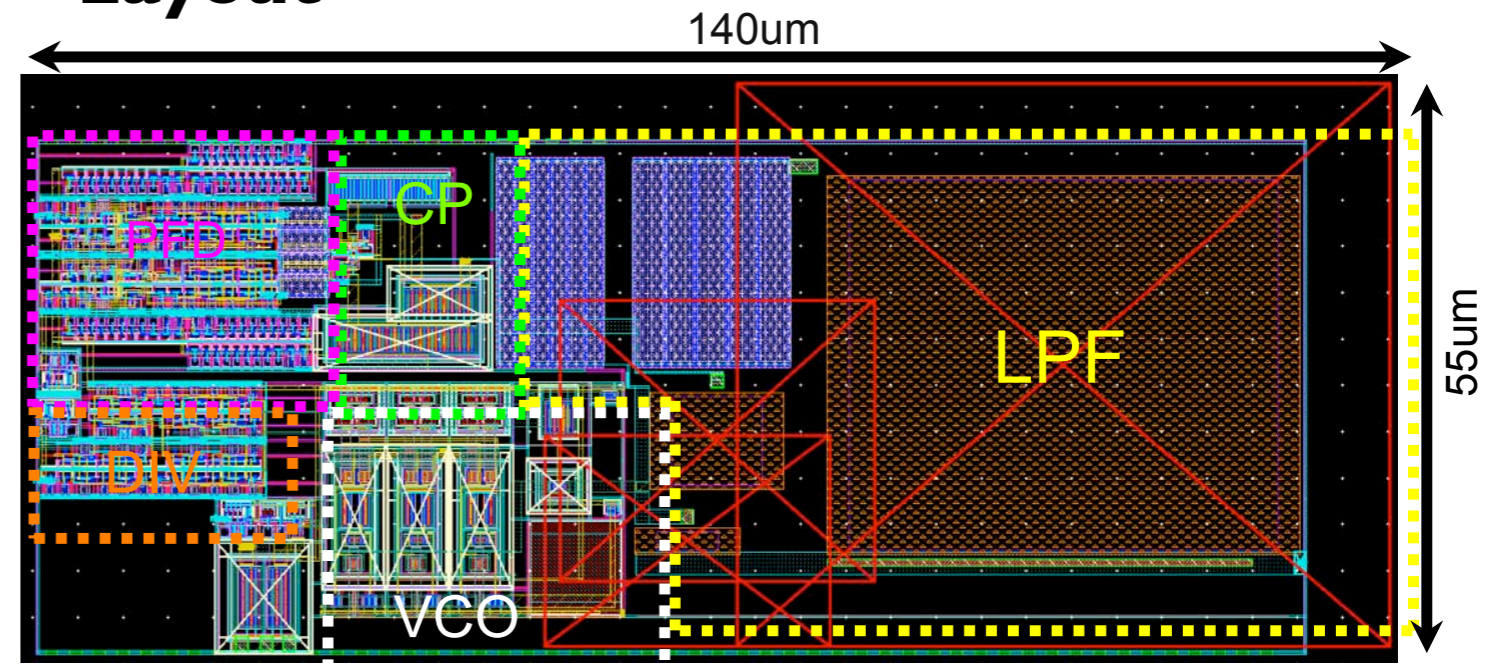


Voltage-Controlled Oscillator (VCO)

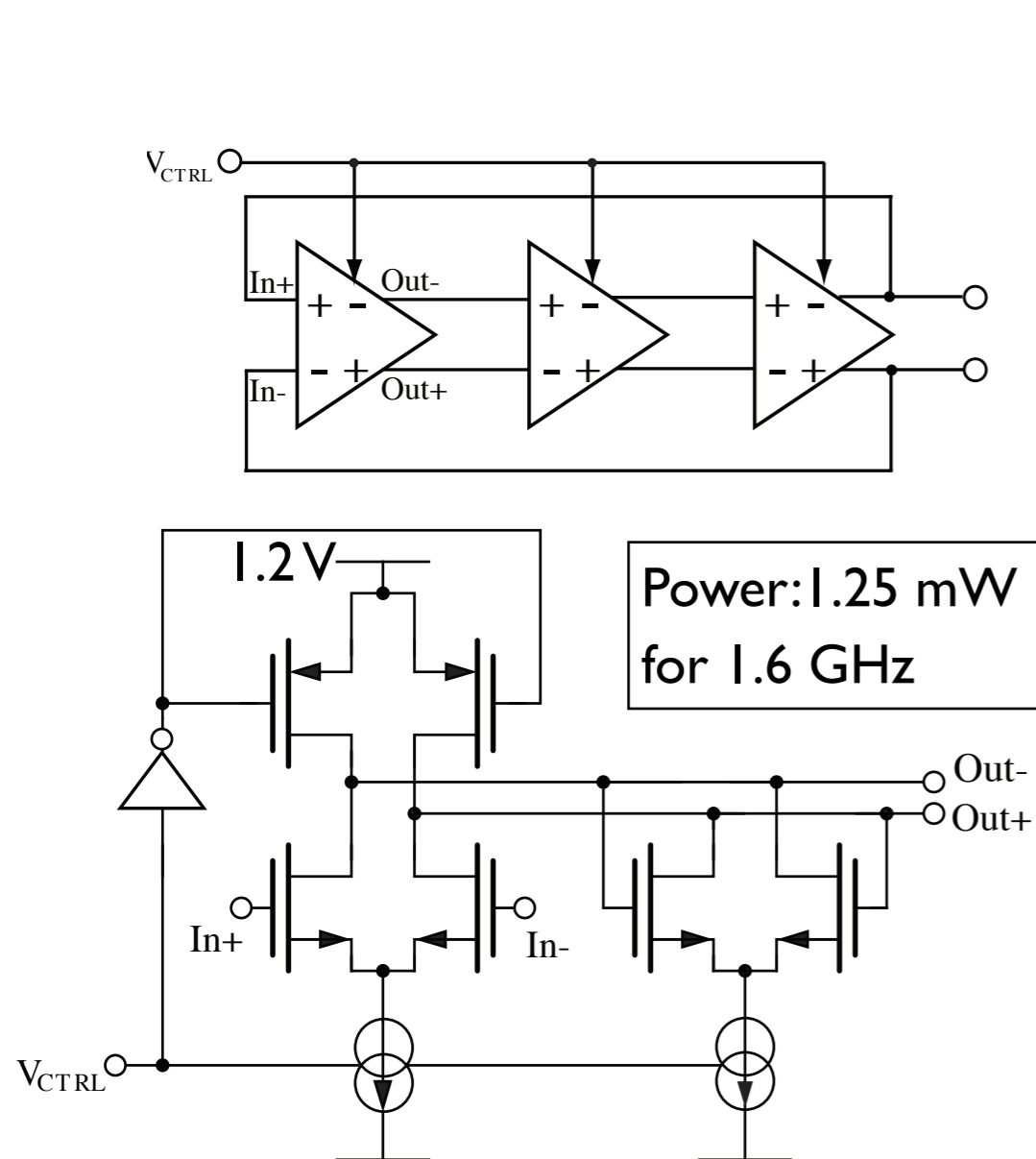- ◆ three inverters connected as a ring oscillator
- ◆ differential pairs with PMOS loads with cross-coupled stages for rail-to-rail switching




[800 MHz vs. V_{ctrl}]

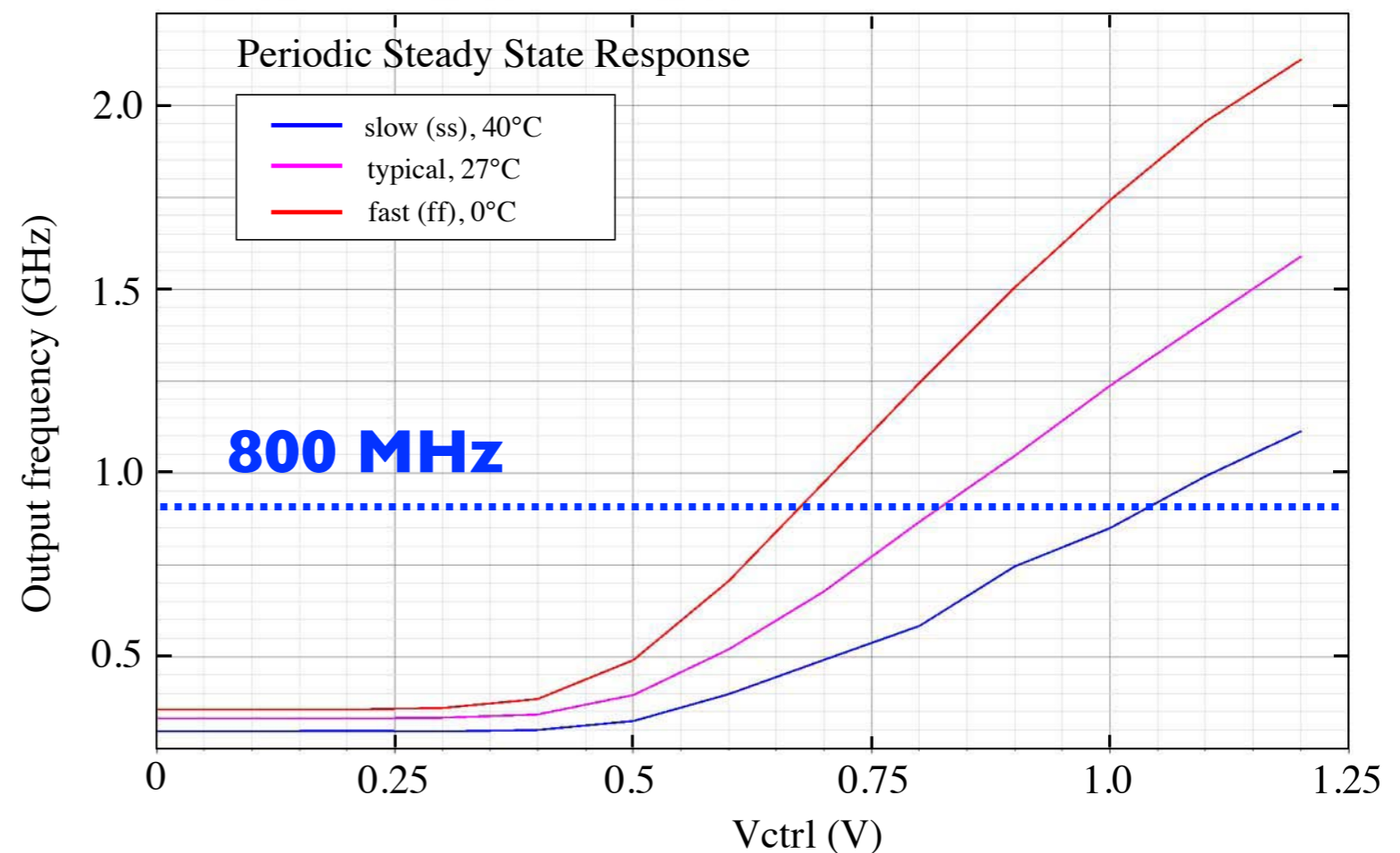

- ◆ wide tuning range of the output frequency
- ◆ oscillation freq. of 1.6 GHz is secured under 3σ process variations.




PLL Settling Behavior

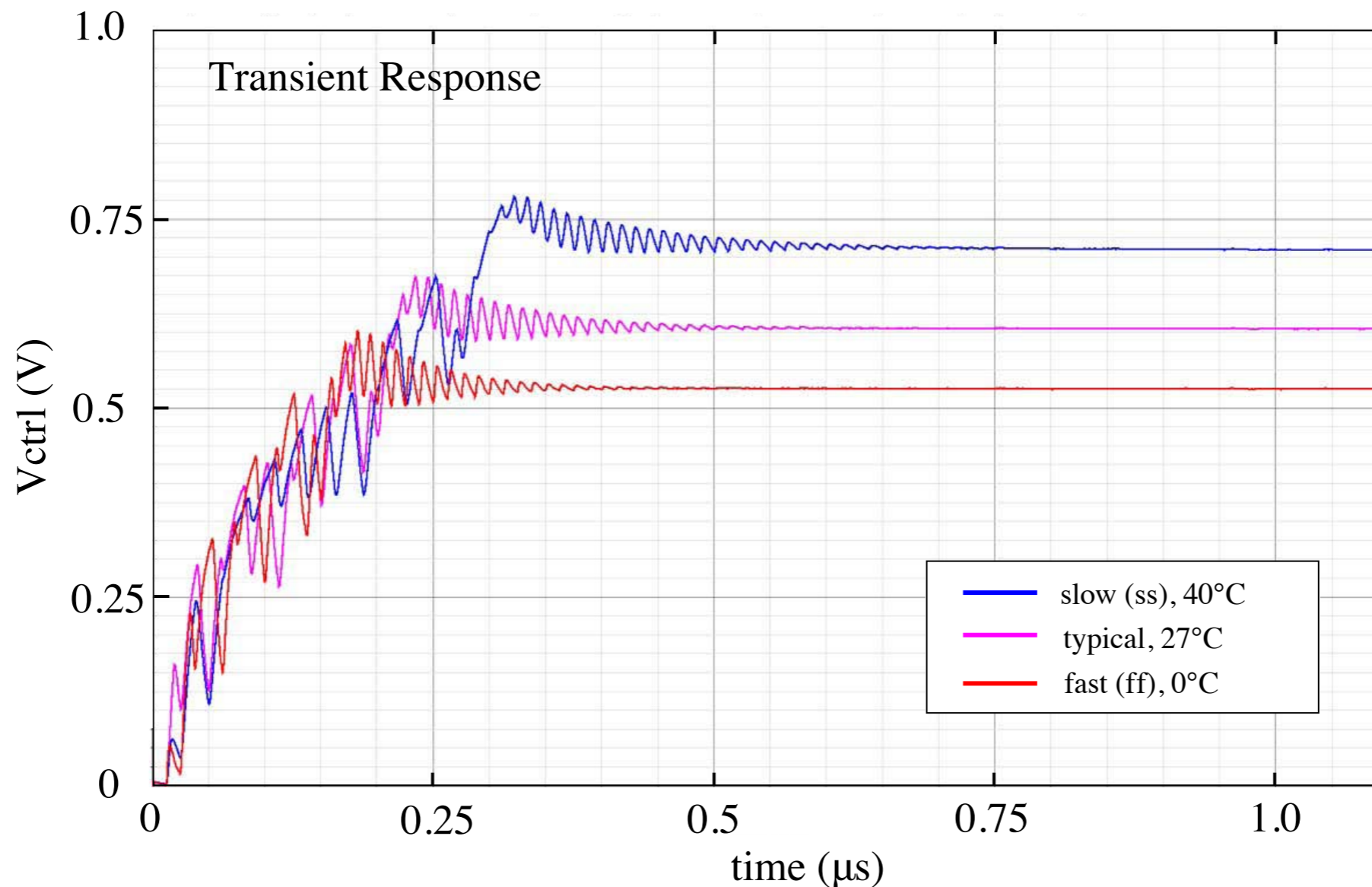- ◆ The V_{ctrl} settles to the final value in $t_{settle} \sim 750$ ns within accuracy of 2%.
- ◆ Stable behavior for all process corners.
- ◆ Layout parasitics are included in the simulation.



CML Driver with pre-emphasis

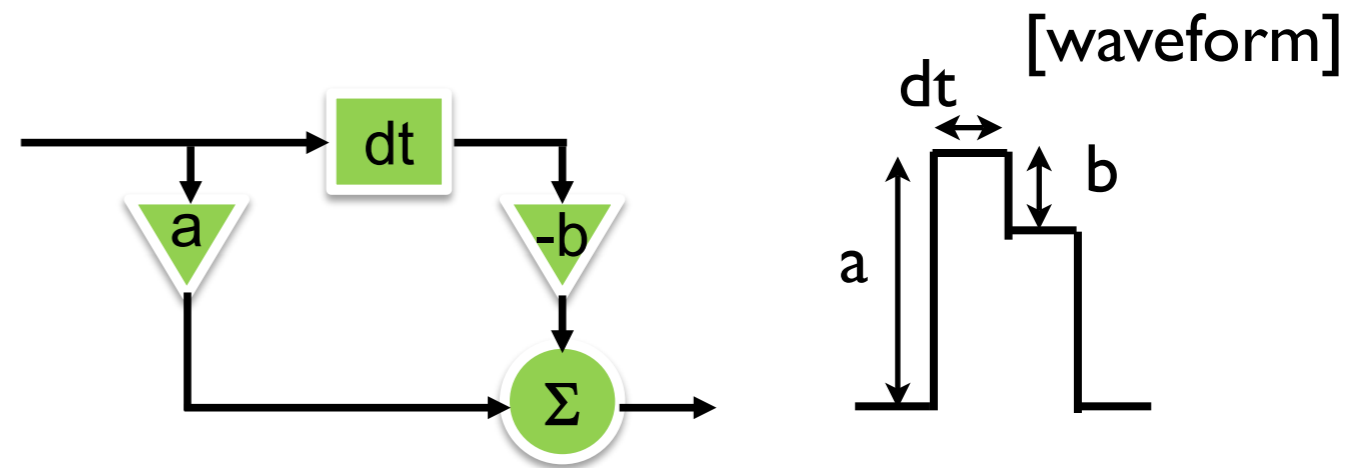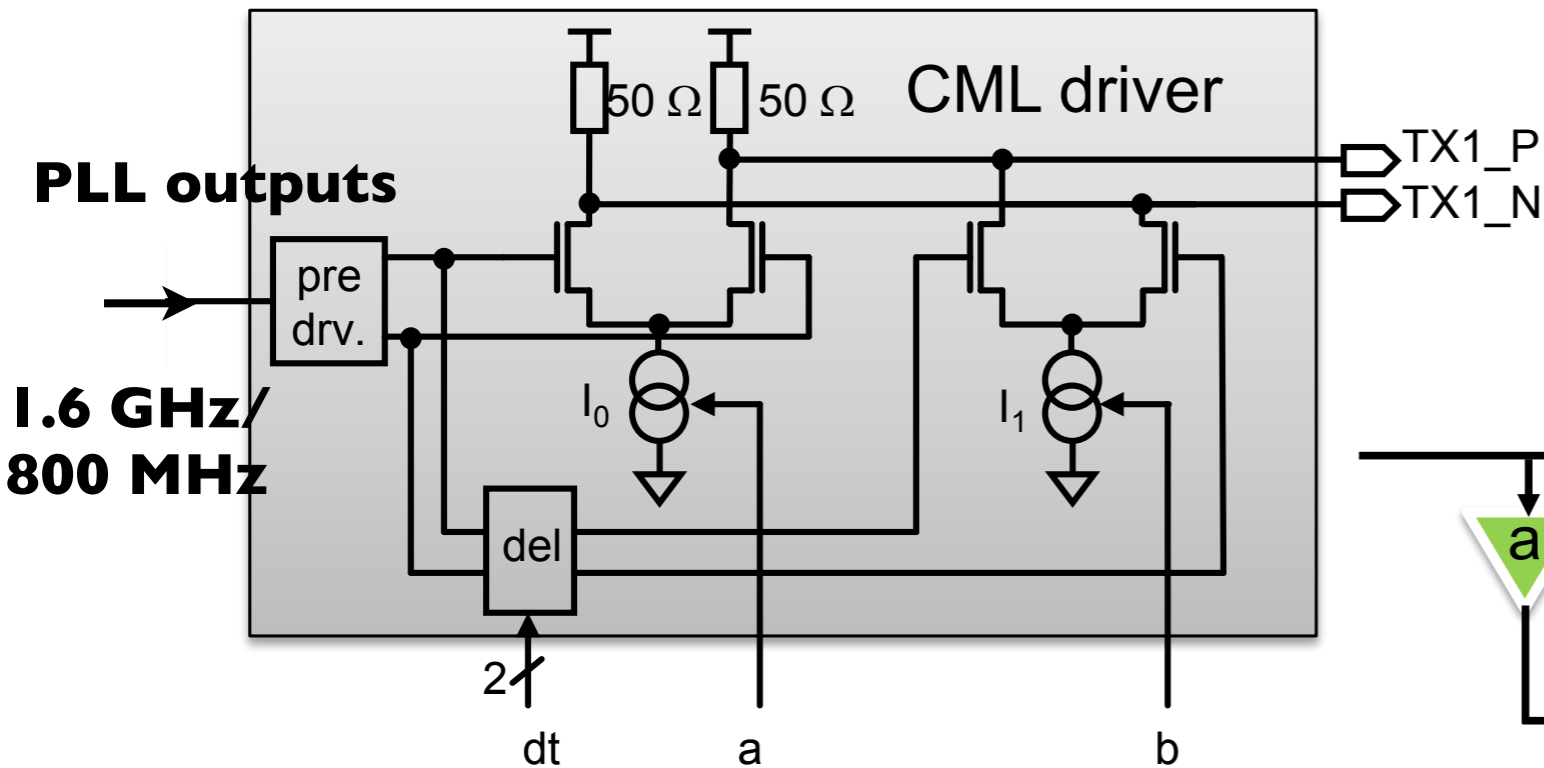 
- ◆ Differential current mode logic (CML):
 - driver (phase control) + differential pair post driver
- ◆ Two differential pairs: adj. bias currents:
 - tap weights (a & b),
 - delay (dt) upto 600ps with 4 fixed steps
- ◆ Dummy poly layout for impedance matching



Why pre-emphasis is necessary?

Signal integrity is affected by

 - ◆ Driver
 - PLL jitter → phase noise
 - signal rise time
- ◆ Cable (12-15m long → high frequency attenuation)
 - resistive loss (skin effect) → large cable diameter
 - dielectric loss → low ϵ_r
- ◆ Cross-talk → shielding




Compensate signal losses by shaping the transmitted pulse response
(boosting high frequency component) → **necessary for Gbit driver**

Measurement setup

800 MHz output connected to the oscilloscope

 1.6 GHz LFSR output connected with flex & twisted cables




Measurement setup

800 MHz output connected to the oscilloscope

1.6 GHz LFSR output connected with flex & twisted cables


800 MHz output clock

 


→ precise clock generation

Pre-emphasis Measurements

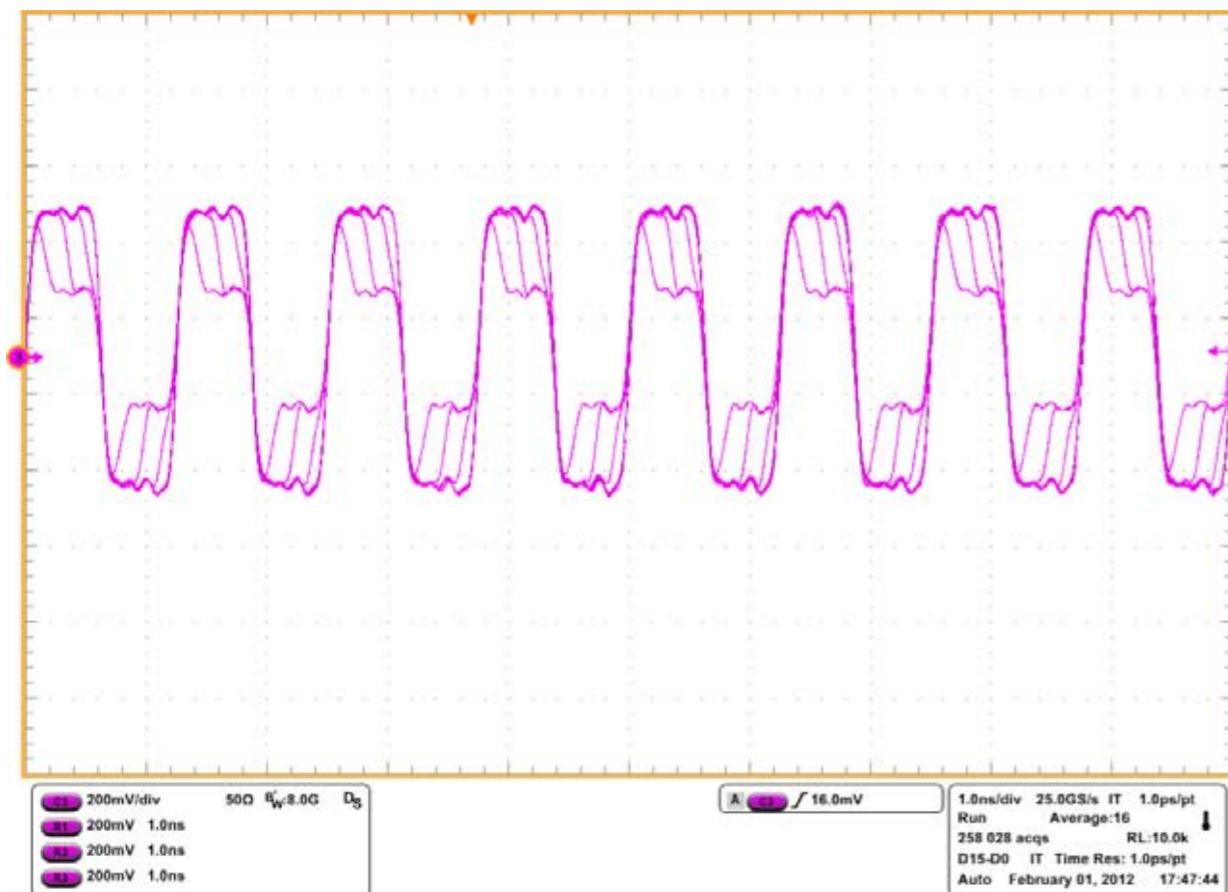Check 800 MHz output with CML pre-emphasis on
(directly connected to the oscilloscope) → pre-emphasis works as expected




variable delay settings

 

variable tap weight settings

Signal Integrity Analysis

 - ◆ Measure vertical & horizontal **eye opening**
- ◆ Pseudo random bit sequence as a signal source
- ◆ 1.6 Gbps, 8bit LFSR sequence
- ◆ **10m** Infiniband cable (LEONI, AWG 26)




← **bad eye opening**


Pre-emphasis: off

Signal Integrity Analysis

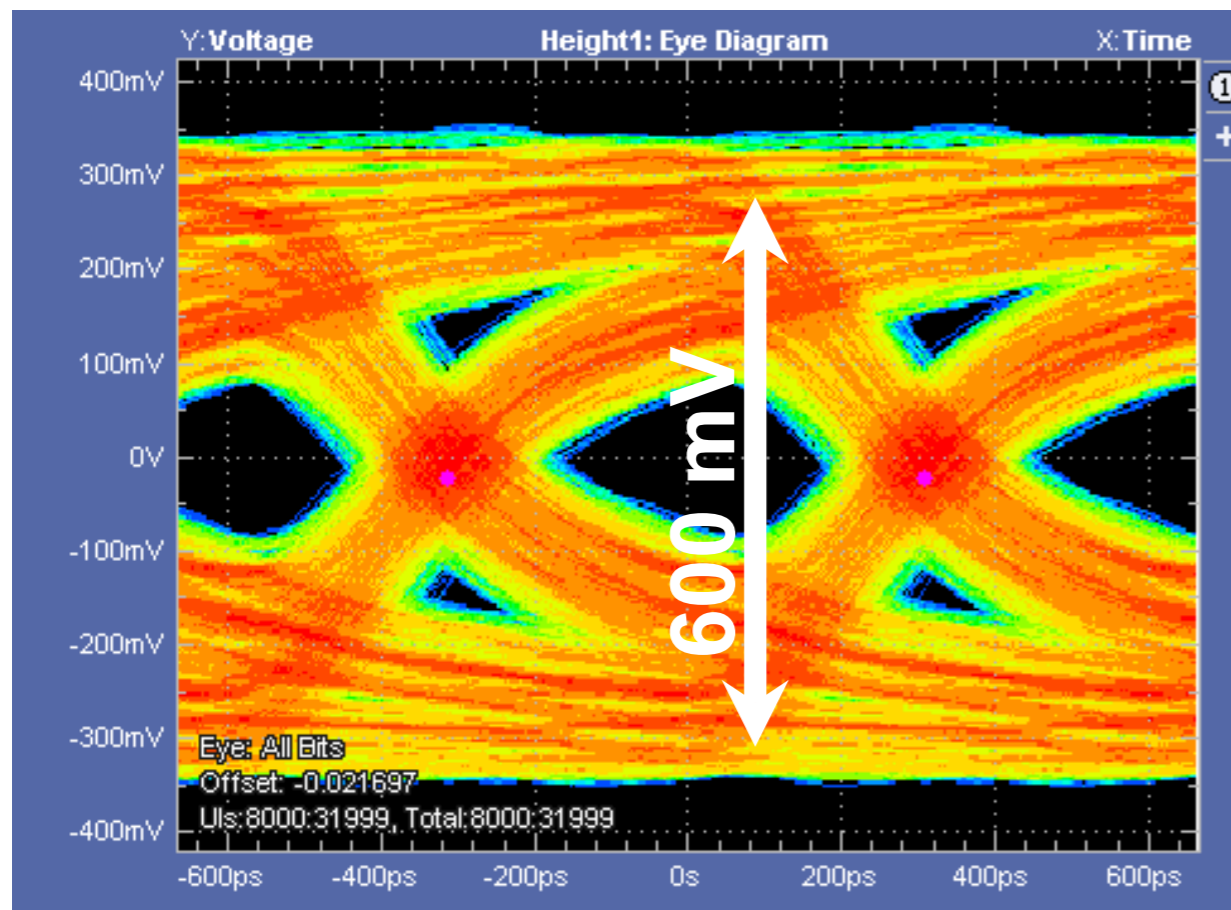- ◆ Measure vertical & horizontal **eye opening**
- ◆ Pseudo random bit sequence as a signal source
- ◆ 1.6 Gbps, 8bit LFSR sequence
- ◆ **10m** Infiniband cable (LEONI, AWG 26)



Pre-emphasis: off

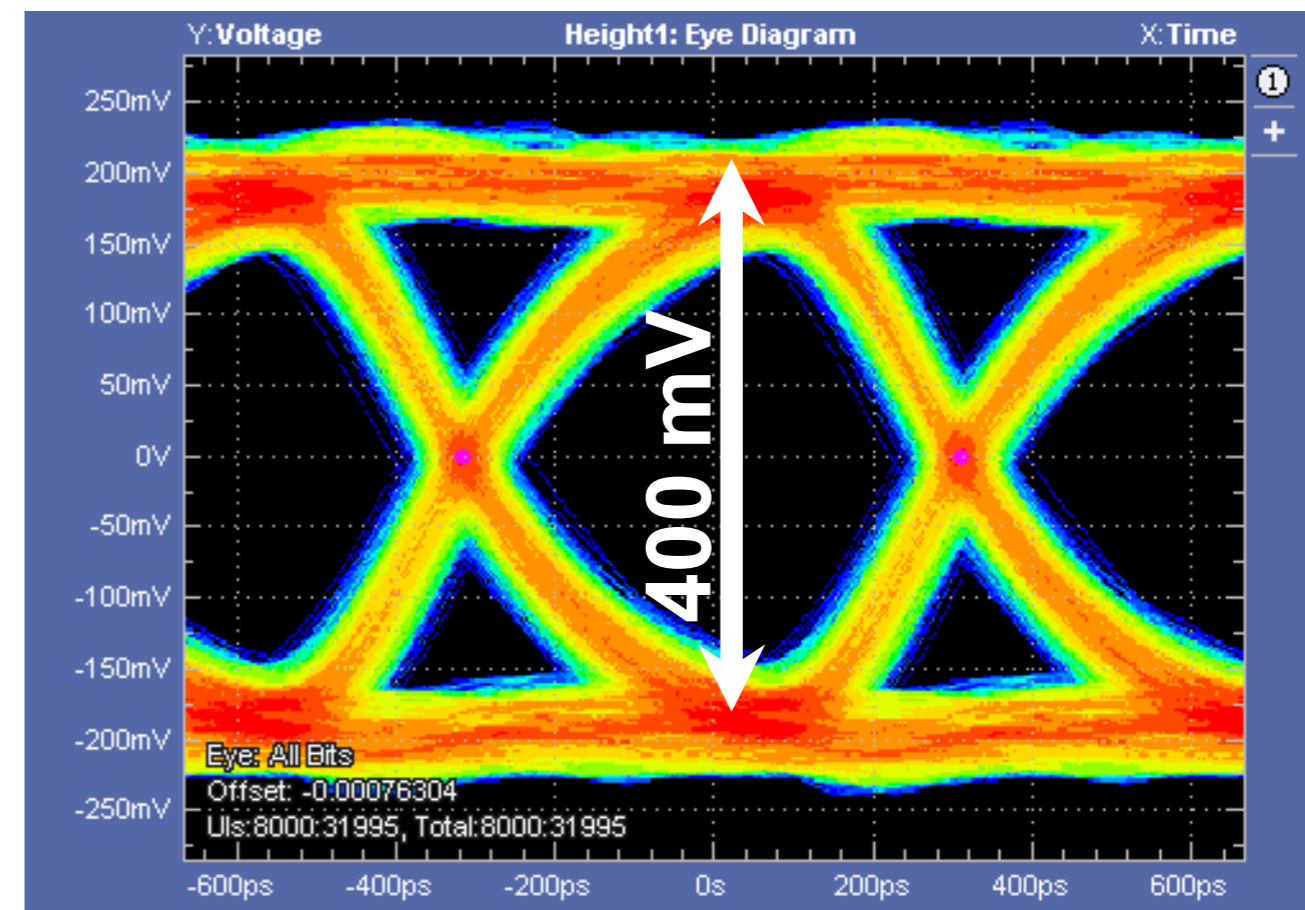


Pre-emphasis: on

(dt=600 ps & max. tap weight)


Signal Integrity Analysis

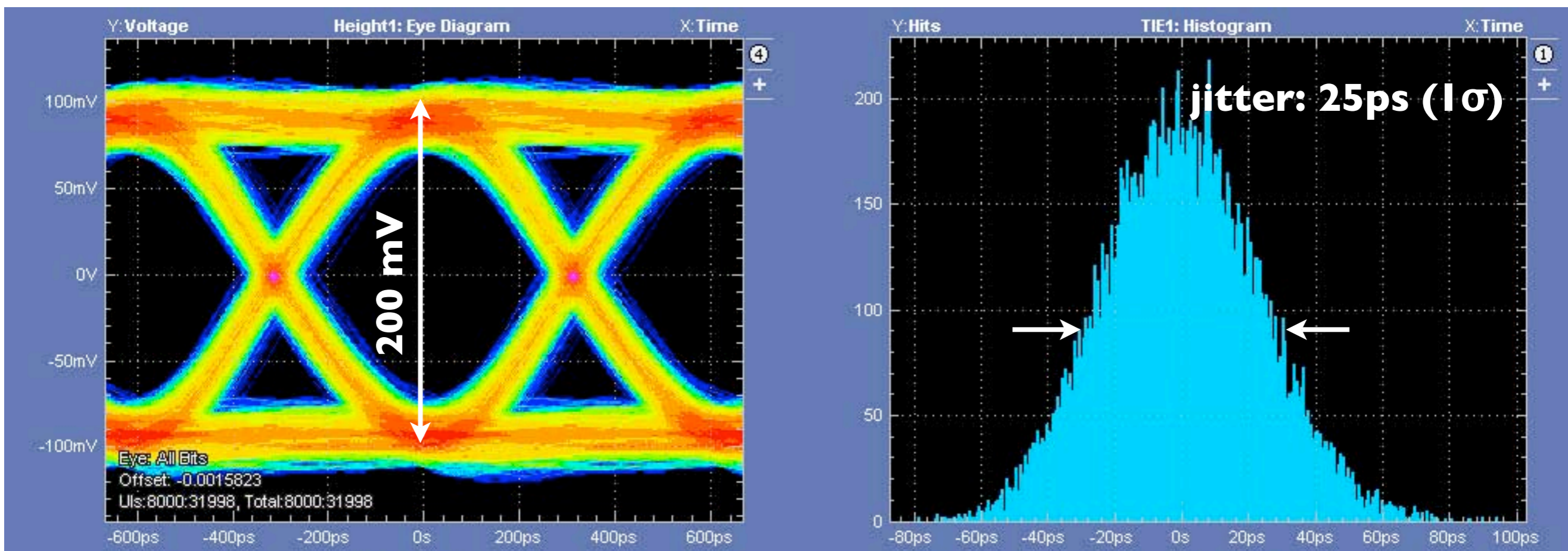- ◆ 1.6 Gbps, 8bit LFSR sequence **38 cm flex** (I.V.) + **10m** Infiniband cable (LEONI, AWG 26)
- ◆ Max. pre-emphasis settings



Signal Integrity Analysis

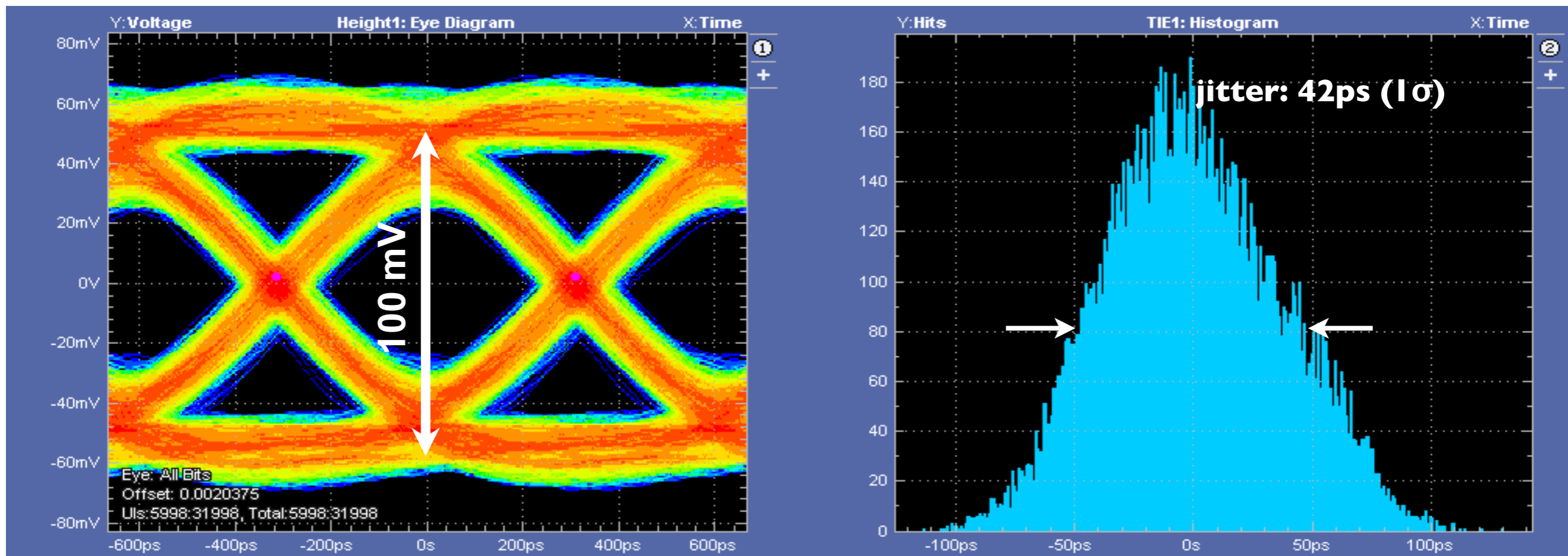1.6 Gbps, 8bit LFSR sequence **38 cm flex** (I.V.) + **20m** Infiniband cable (LEONI, AWG 26)
Max. pre-emphasis settings



Intrinsic rad. hardness ($t_{ox} \sim 1-2$ nm) is attractive for future high-energy experiments.



Summary

- ◆ DHPT 0.1, test chip, TSMC 65nm, shipped Jan. 2012, full custom blocks
 - good signal integrity for 1.6 Gbps with flex + 10m (20m) Infiniband cables
 - Irradiation tests (TID for PLL & Gbit driver) under way
- ◆ Another 65nm test chip was submitted in Mar. 2012
 - LVDS RX/TX for JTAG
- ◆ Full size chip (DHPT 1.0, TSMC 65nm) to be designed & submitted by fall 2012

Thank you for your attention.

Backup slides

DEPFET Pixel Vertex Detector – PXD

  

- occupancy: ~ 0.2 hits/ $\mu\text{m}^2/\text{sec}$ (estimated for 1×10^{35} $\text{cm}^{-2}\text{sec}^{-1}$, @ 1.8cm radius)
- spatial resolution : $< 10 \mu\text{m}$ (r-phi) (can be less in z)
- pixel size: $50 \mu\text{m}$ (r-phi) x $\sim 90 \mu\text{m}$ (z-axis)
- material budget $< 0.15 \% X_0$ per layer
- **read-out time: 10 μs**
- radiation level: **~ 1 Mrad per year**

- $17^\circ - 150^\circ$ acceptance ($\eta = [0.55 .. 0.3]$)
- layer 1: 10 modules at 1.8 cm radius
- layer 2: 12 modules at 2.2 cm radius
- optional layer 0 at 1.3 cm radius with beam pipe upgrade
- half-module active area: 4.9 cm x 1.2 cm (layer1)
- #pixels: 240 x 512
- r/o channels: 960 x 128 (4-fold parallel)
- **sample (row) rate: 12 MHz**