

# MasterPanel

SiPM elettronica, 23 settembre 2024

# The work of the MasterPanel

- **patch panel for the front-end electronics**


- MP receives the input LV from the PS
  - 1.4 V analog, 1.4 V digital low, 2.7 V digital high
- MP distributes the LV to the connectors to the FEE
  - 1 MP / 8 PDU scheme = 32 FEB + 8 RDO connectors on the MP output side
- space considerations
  - 1 MP can not be bigger than  $100 \times 200 \text{ mm}^2$  ( $2 \times 4 \text{ PDU}$ ) =  $20000 \text{ mm}^2$
  - one FEB/RDO connectors is  $\sim 150 \text{ mm}^2 \rightarrow 150 \times 40 = 6000 \text{ mm}^2$
  - assume similar space is taken by the input connectors
  - there are  $8000 \text{ mm}^2$  for services:  $100 \times 80 \text{ mm}^2$

- **PDU services: NTC, Vbias, Vannealing**

- MP receives 32 NTC voltages from PDU and converts into ADC
  - 1 32-channel ADC? 1 ADC + 32-channel multiplexer?
- MP receives one input Vbias-in (64 V) from PS and generates 8 output regulated Vbias-out (40-60 V)
  - Vbias-out, one for each PDU
- MP receives 8 input Vann-in (-12 V)
 
# MasterPanel

$X = 0 \dots 7$   
8 linear regulators  
8 output stages



# Vbias distribution

## summary table

ne avevamo discusso tempo fa, anche a riunione ePIC-DAQ  
 avevo mostrato possibili opzioni, ma quella che troverei più appetibile / realizzabile è quella in cui abbiamo un regolatore Vbias MasterPanel per ogni PDU assumendo che una scheda MasterPanel serve 8 PDU = 8 regolatori per scheda MasterPanel (che è quello che abbiamo nella scheda MasterLogic v2)

	<b>1 main 4 PDU</b>	<b>1 main 52 CAEN 4 PDU</b>	<b>1 main 52 ML3 4 PDU</b>	<b>1 main 208 ML3 4 PDU</b>
<b>N<sub>primary</sub></b>	312	6	6	6
<b>N<sub>primary</sub> / sector</b>	52	1	1	1
<b>V<sub>primary</sub> (V)</b>	64	12	64	64
<b>I<sub>primary</sub> (A)</b>	< 1 mA	2	2	1
<b>Granularity</b>	1024	1024	1024	256
<b>uController</b>	no	yes	yes	yes

# Vbias distribution





64 V  
1.5 A

30 mA



MasterPanel board

  

1 MasterPanel  
8 PDU

per ogni PDU

- 1 regolatore lineare
- 8 MOSFET per capacità di spegnere indipendentemente

regolazione Vbias comune a 256 SiPM  
capacità di spegnere a 32 SiPM

quindi in totale sulla MasterPanel

- 8 regolatori lineari
- 64 MOSFET


# Vbias distribution



64 V  
1.5 A

30 mA


MasterPanel board

 

sulla MasterLogic v2 i regolatori consumano ognuno  
3.3 mA quando l'uscita è a 50 V

8 canali sono circa 30 mA

# Vbias distribution

 

una MasterPanel per 8 PDU  
in un settore ci sono 208 PDU

→ in un settore ci sono 26 MasterPanel

se ogni MasterPanel consuma 30 mA

30 mA per 26 MasterPanel  
= 0.8 A dal canale primario

al momento la CAEN una scheda così non ce l'ha,  
ma sta facendo una scheda 64 V 1.5 A

esistono  
8 V 12 A  
16 V 6 A  
32 V 3 A  
quindi la prossima è la 64 V 1.5 A



# Vannealing distribution

2 Vbias input lines for each FEB

32 SiPM / Vbias input line

= 3.2 A for each line during annealing (max)

MasterPanel board

  


but, 1248 8-channel CAEN boards are a bit too much and are not needed given that we do not do annealing all at the same time  
(that would be 150-300 kW)

fan-out to 8 PDUs

# Vannealing distribution

MasterPanel board

 

fan-out to 8 PDUs with MOSFETs to select which PDU is doing annealing  
note: we want to do annealing of a full PDU

# MasterPanel




64 V  
1.5 A

1 Vbias input





8 Vann inputs

 

for each PDU

  - 1 linear regulator for Vbias
- 1 output stage with 8 bias lines with individual ON/OFF control



cable

NORMAL operation  
Vbias-in → regulator → 8x V-out

ANNEALING operation  
8x Vann-in → 8x V-out