


PTOLEMY

HV stabilization system

N. Rossi, A. Cocco, N. D'Ambrosio,
M. D'Incecco, G. Korga, M. Messina, F. Pofi
and F. Virzi (*LNGS Group*)



PTOLEMY Collaboration Meeting
Genova, 20-22 November 2024

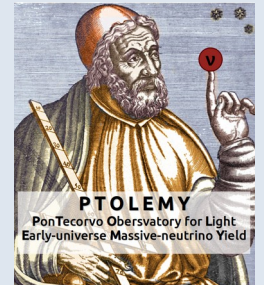

Part I

Static voltage reference

Motivations and goals

Resolution $\Delta E \sim \Delta V$:

$\Delta E < 50$ mV at the tritium end point (18600 keV)


@ 20 kV $\rightarrow \Delta V/V \sim 2.5$ ppm

High precision
reference diode chain



Non invasive
measurement with a
field mill


Accuracy and Precision

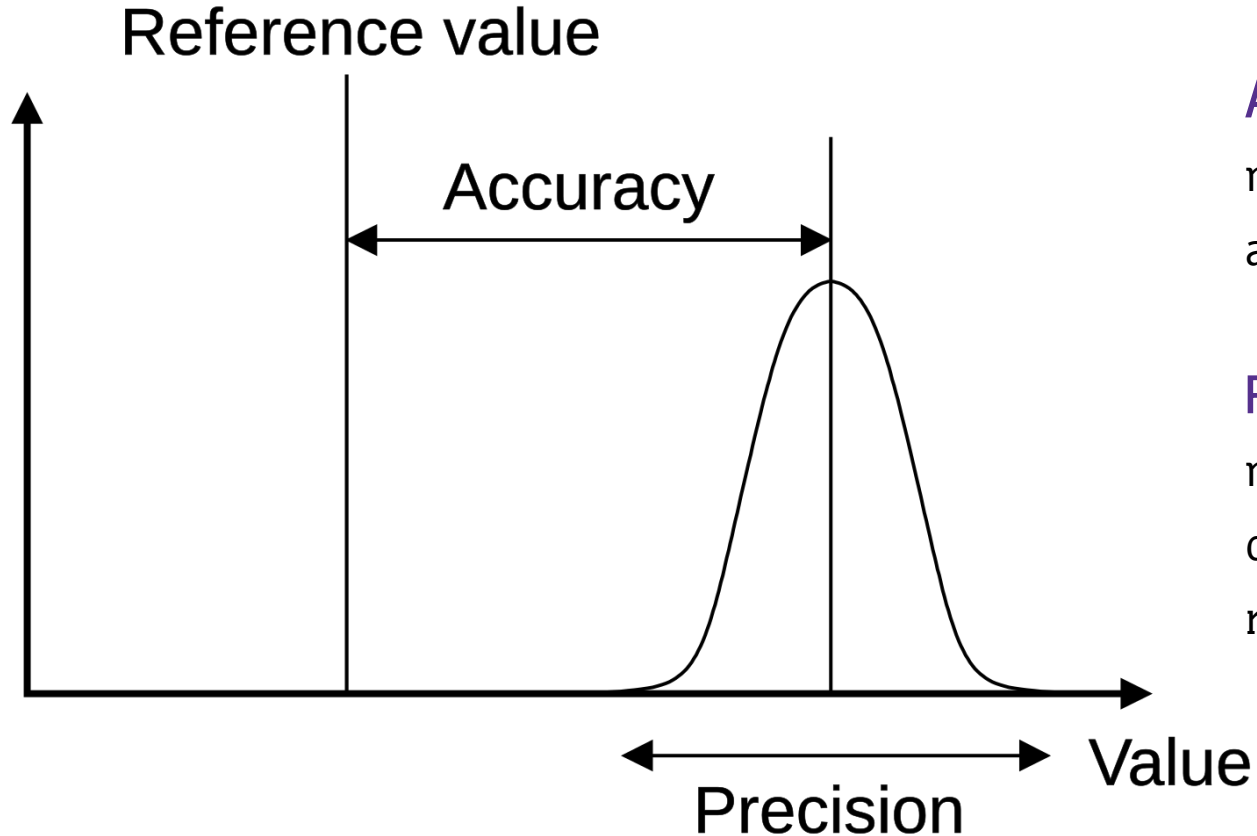


Accuracy: proximity of measurement results to the accepted value

Precision: degree to which measurements under unchanged conditions show the same results.

Setup scheme (baseline)

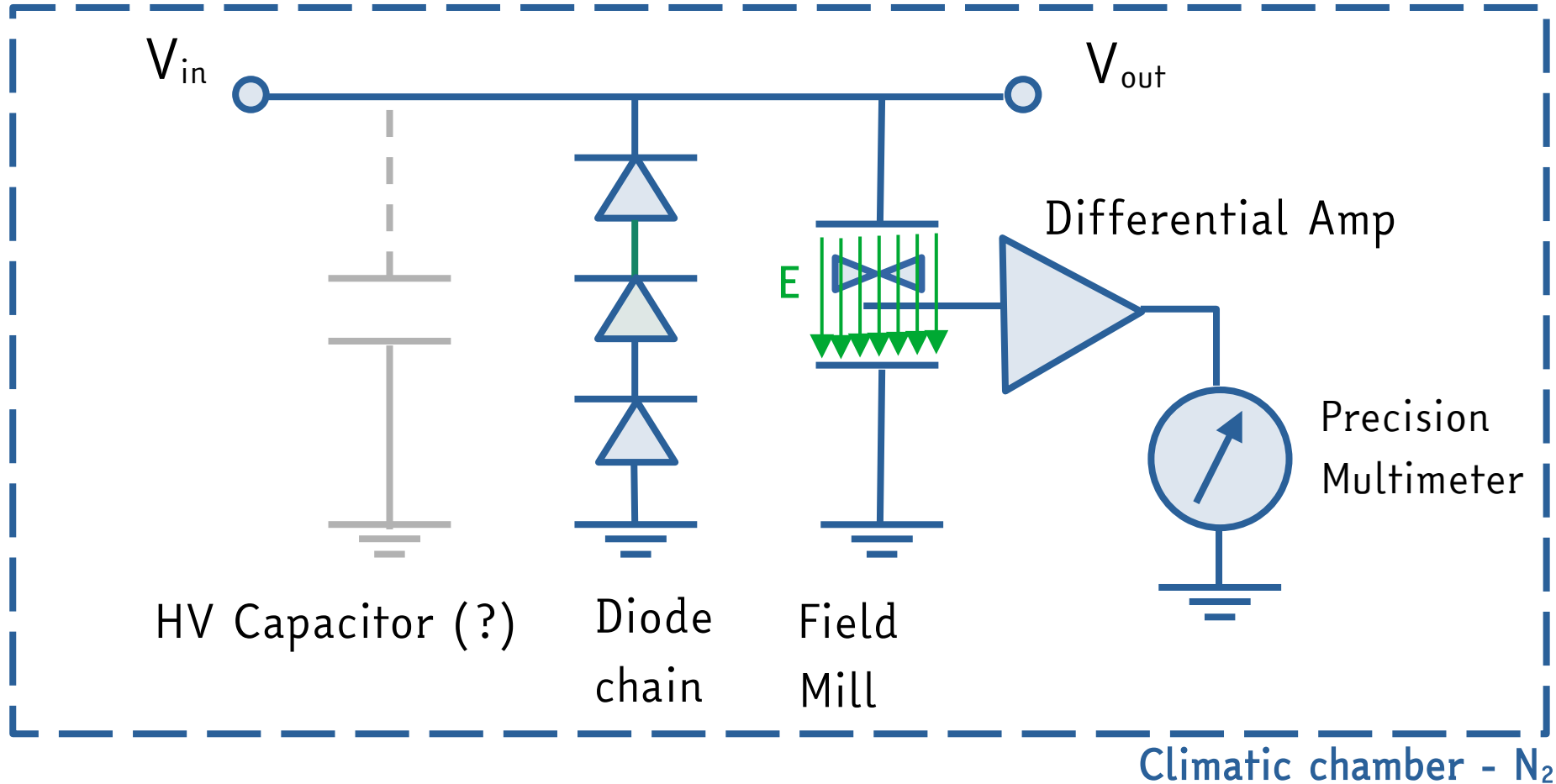

Amplification chain

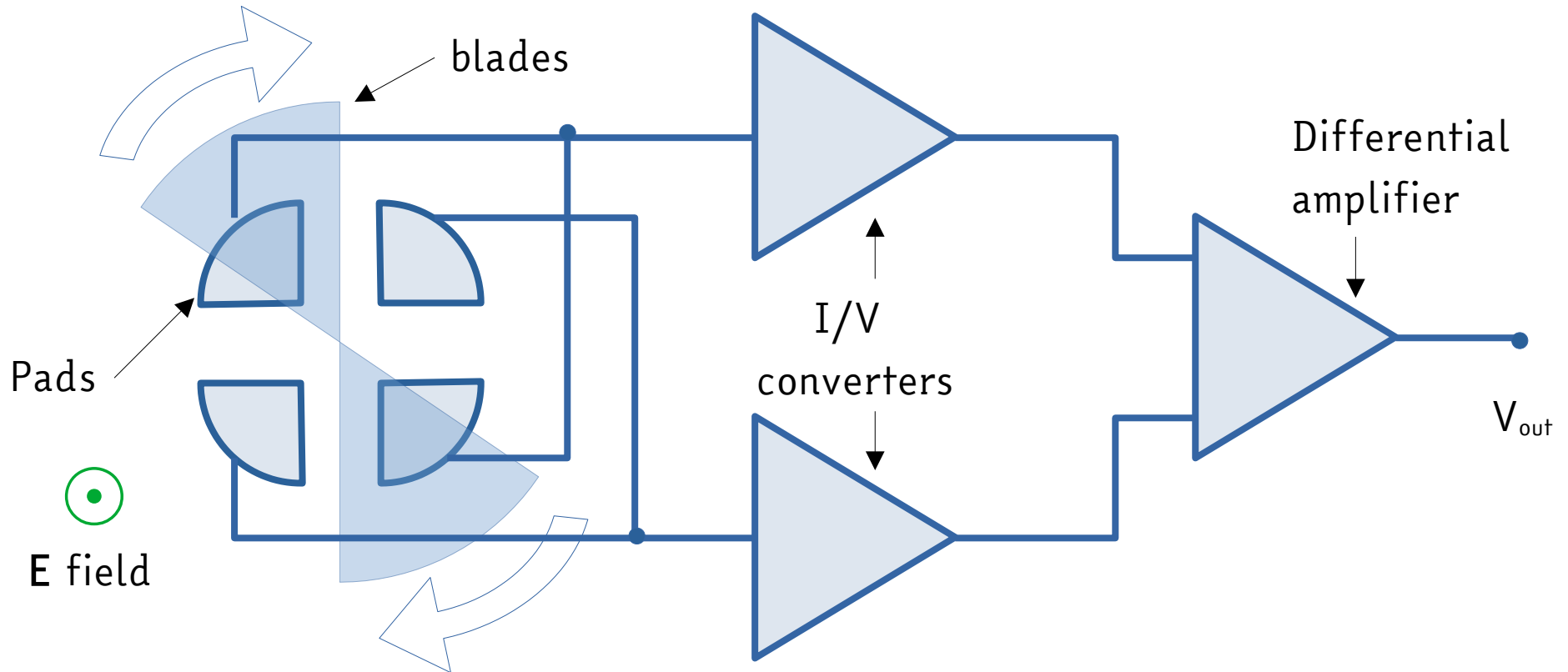

High precision reference voltage regulators (slang *diode*) - REF50xx

$$V_0 = 10V$$

$$V_{in} = 10.2 - 18 V$$

$$I_q = 0.8 \text{ mA}$$



Low temperature drift: 2.5 ppm/°C

High accuracy: 0.025%



Low noise: 0.5 $\mu\text{V}_{pp}/\text{V}$

Excellent long term stability: 22 ppm/1000h

Temperature range: -40 ÷ 125°C

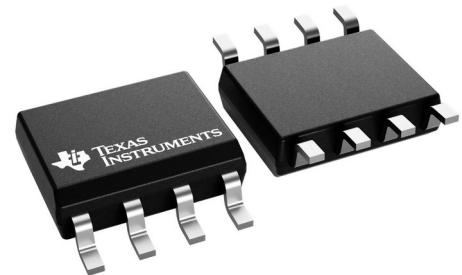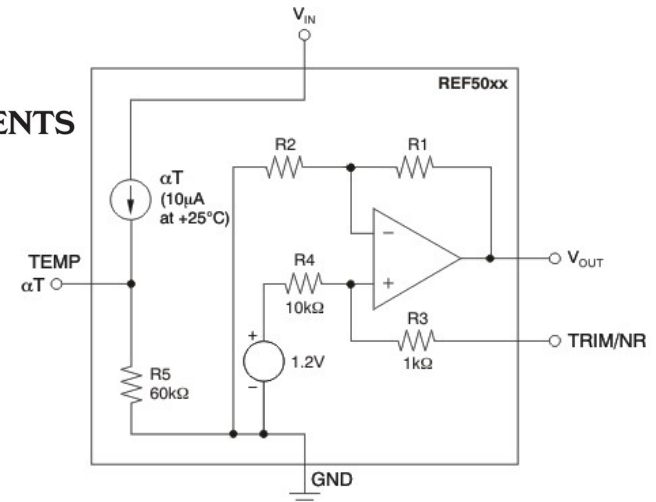


Diode chain configuration

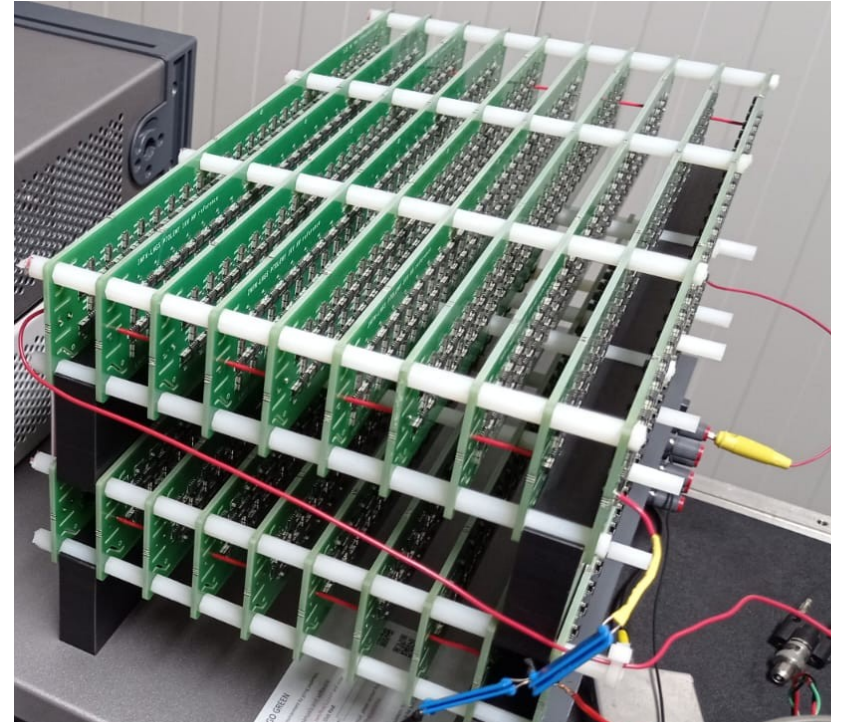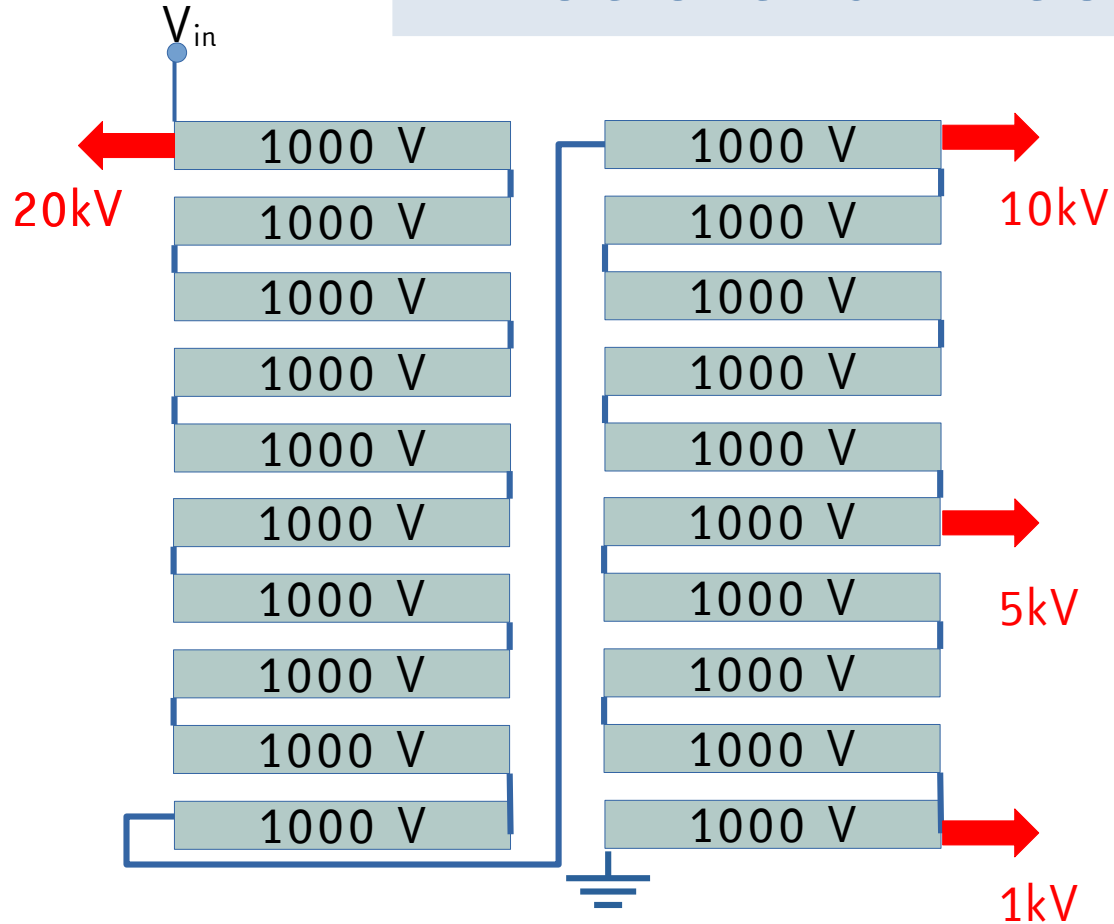


Precision
Multimeters
6.5 and 7.5 digits

Old set-up

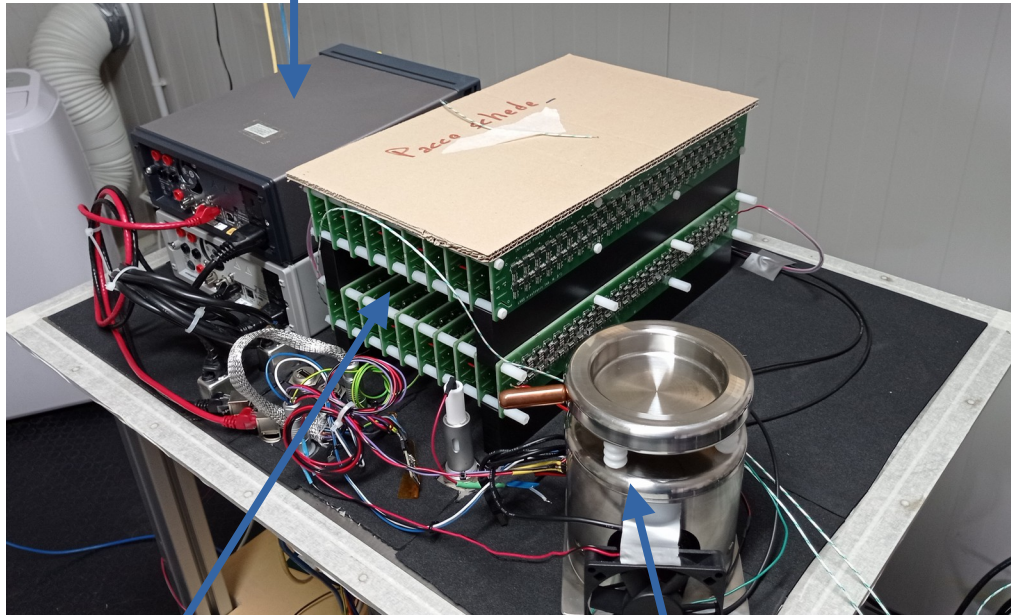




Diode chain

Field mill

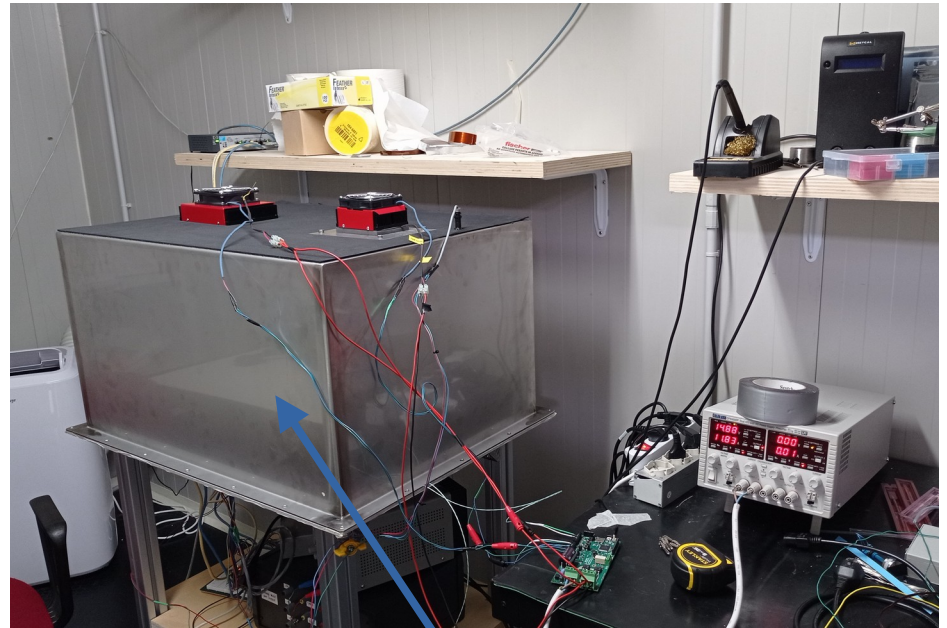




Climatic chamber

Old results (baseline)

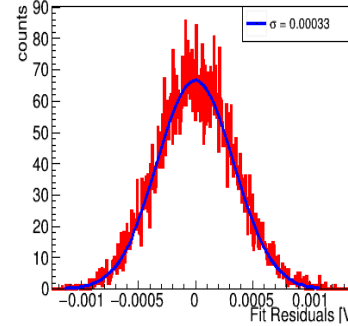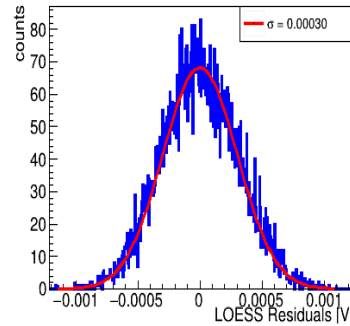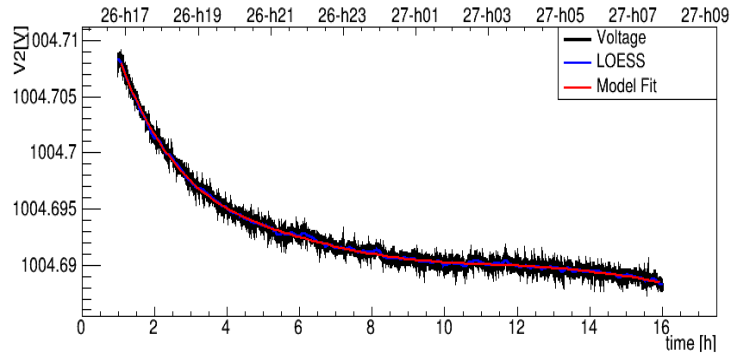

Single board
(1 kV)

$$\sigma = 0.3 \text{ mV}$$

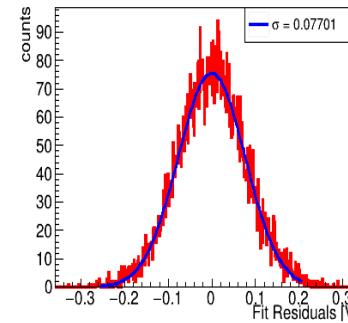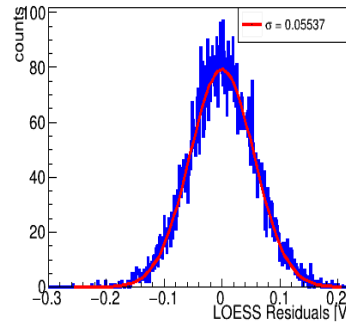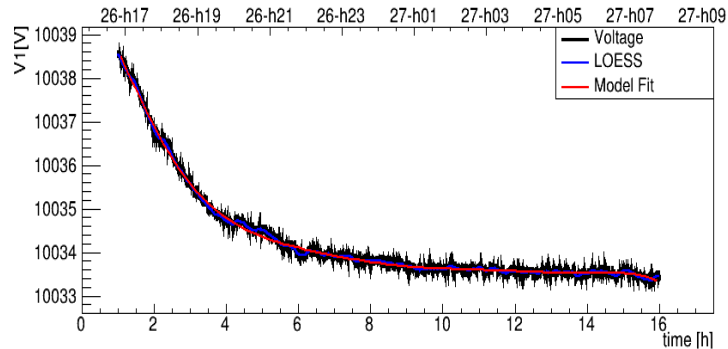

10 board series
(10 kV)

$$\sigma = 55 \text{ mV}$$

$$\sigma(\text{intrinsic, 10kV}) = \text{sqrt}(10) \times 0.3 \sim 1 \text{ mV}$$

$$\sigma(\text{intrinsic, 20kV}) = \text{sqrt}(20) \times 0.3 \sim 1.4 \text{ mV}$$

($\ll 55 \text{ mV} !!!$)
[I wish!!!]

New set-up

- New climatic chamber ✓
- New motor ✗⚠
- New mill blade ✓
- New motor driver ⚠
- Modified differential amplifier ⚠
- Additional precision multimeter ✓
(8.5 digits)
- HV slow switch ✓

Make a change
at a time!




New set-up

Multimeter
7.5 digits
(Field mill)

Multimeter
6.5 digits
Temp. board

Motor driver

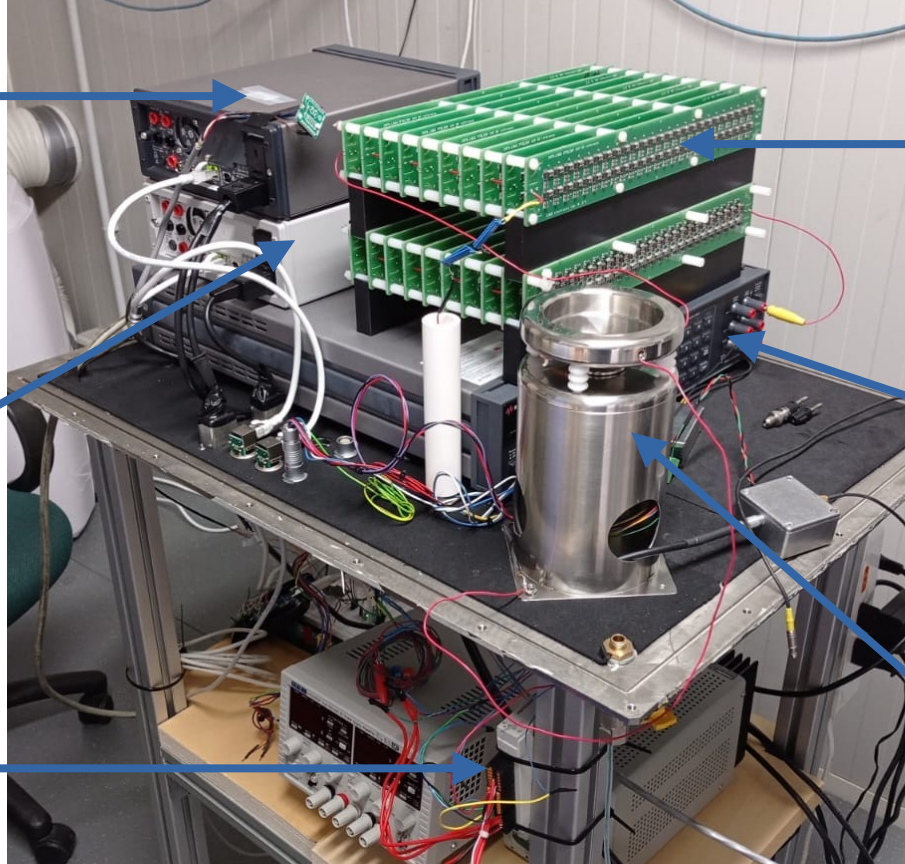






Diode
chain

Multimeter
8.5 digits
(1kV board)

Field mill


New climatic chamber

Room
conditioning

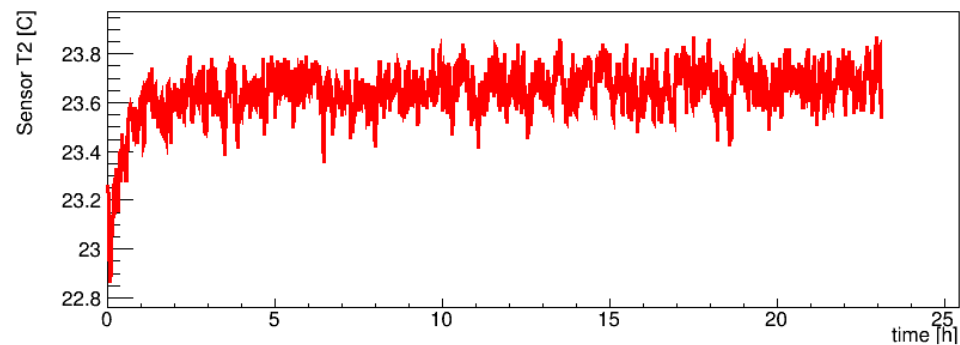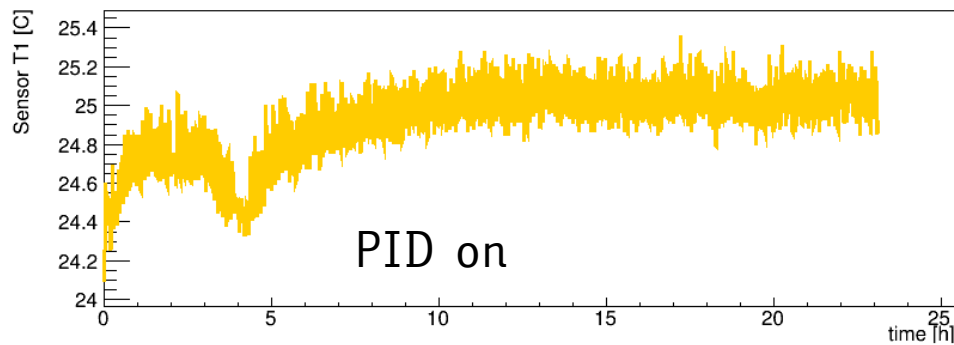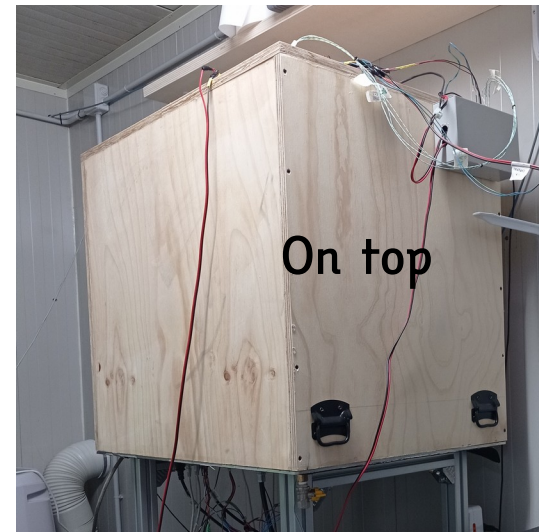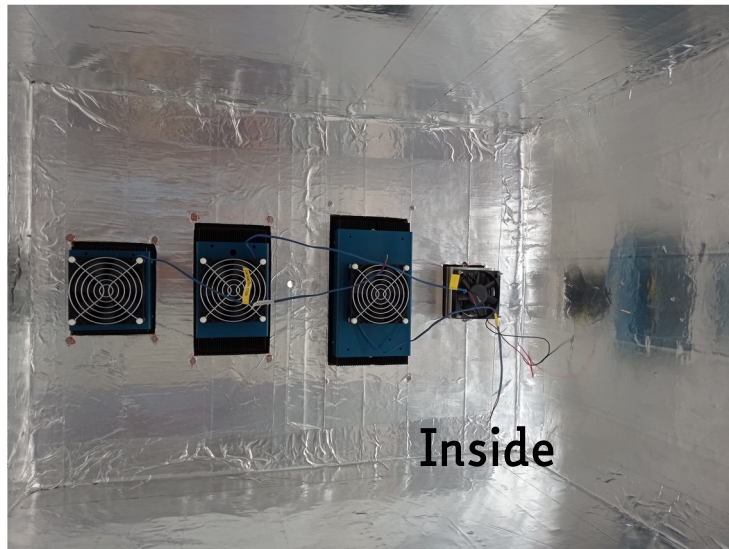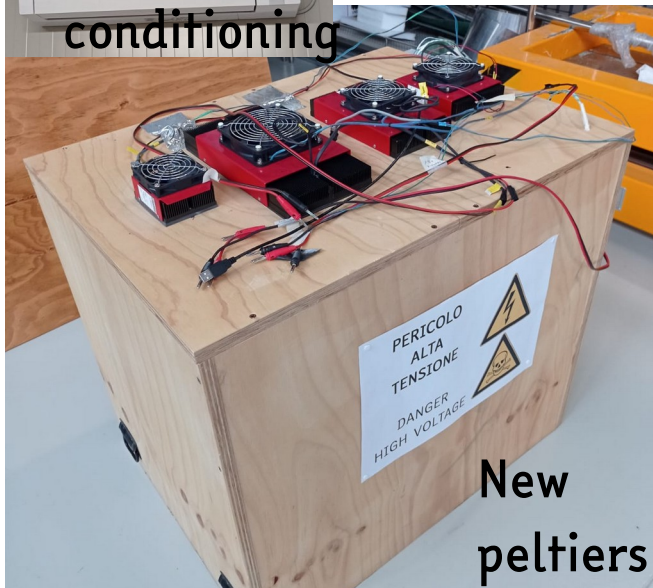

HV slow switch

Horizontal
movement

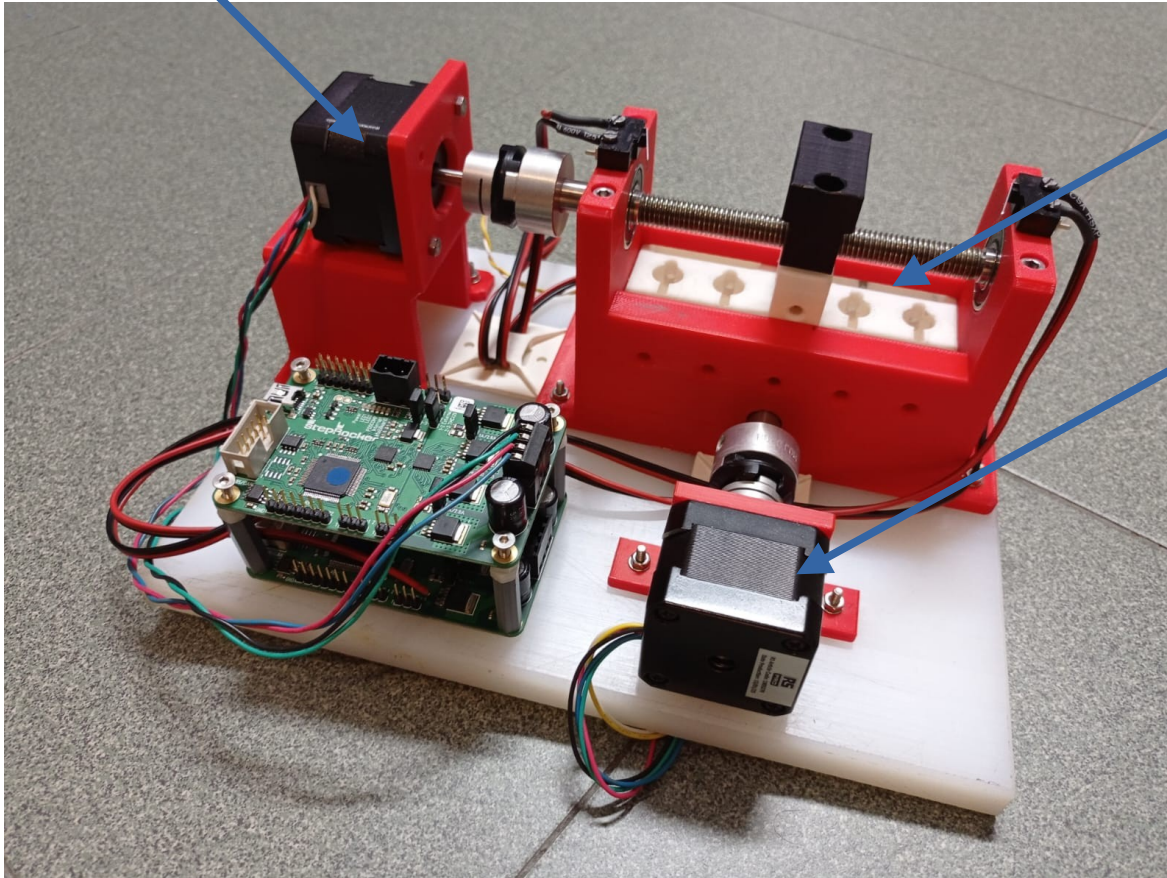

Electrode
holes

Lateral
movement

Switching between
different partition of the
diode chain without
opening the climatic
chamber


Ready to be tested

New mill blade



New mill blade
LIGHT
(height adjustable)

Mechanical Spectrum

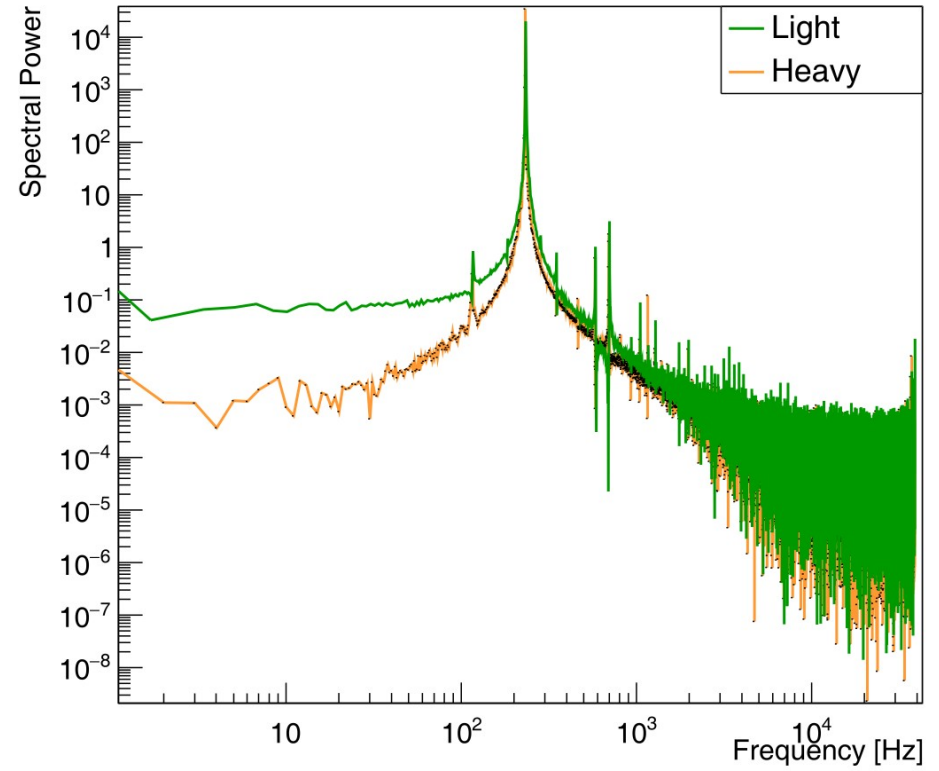


New mill blade
HEAVY

High stability in frequency

New motor



New brush-less motor

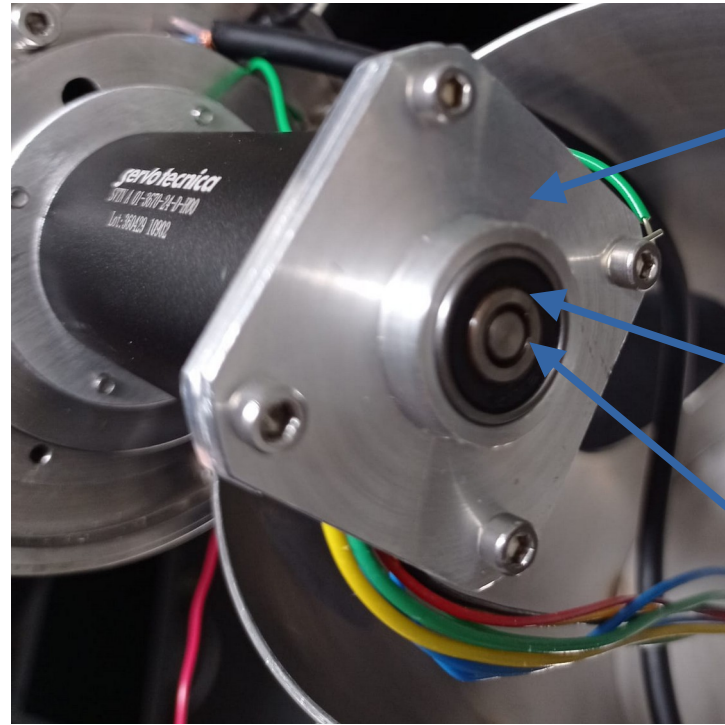



Aluminum
plate

Ball
bearing



Motor axis

Grounding problem between the axis
and the aluminum plate ($> 10 \text{ k}\Omega$) ⚠

New results

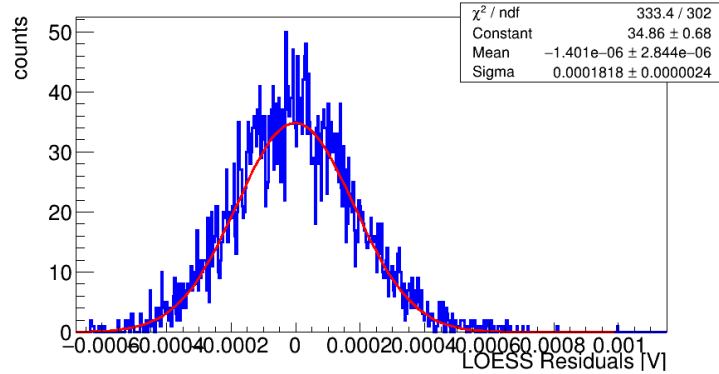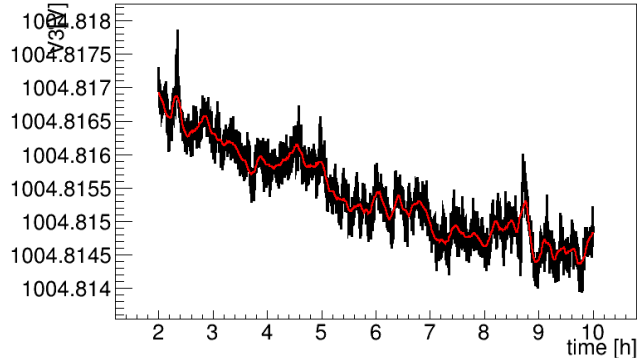

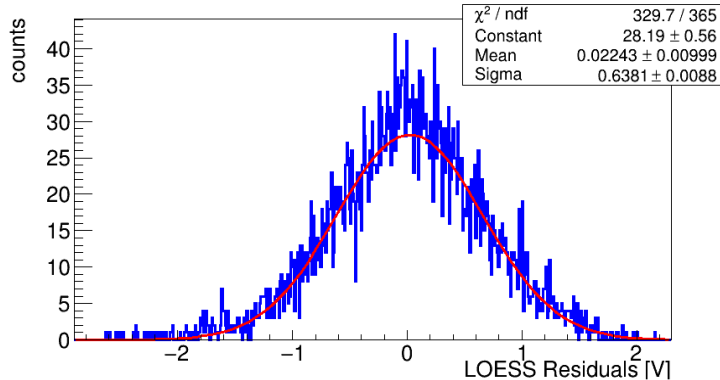
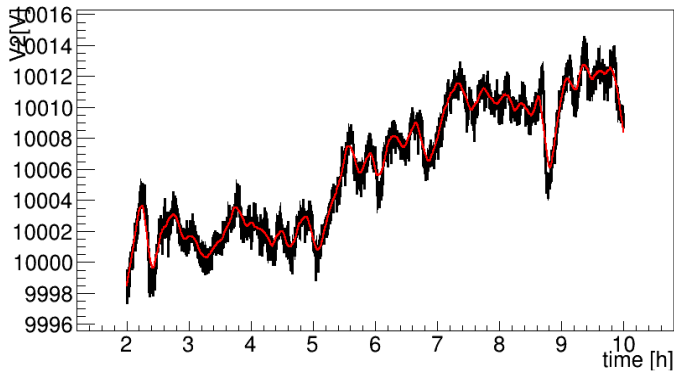
Single board
(1 kV)
 $\sigma = 0.18 \text{ mV}$
[IMPROVED]
 $\Delta V/V = 0.18 \text{ ppm}$



10 board series
(10 kV)
 $\sigma = 638 \text{ mV}$





Origin of the noise

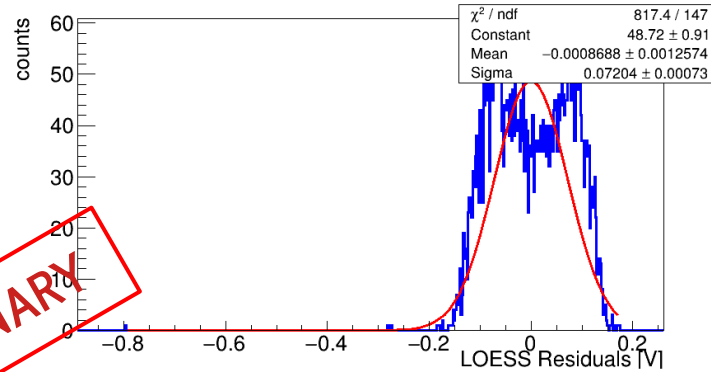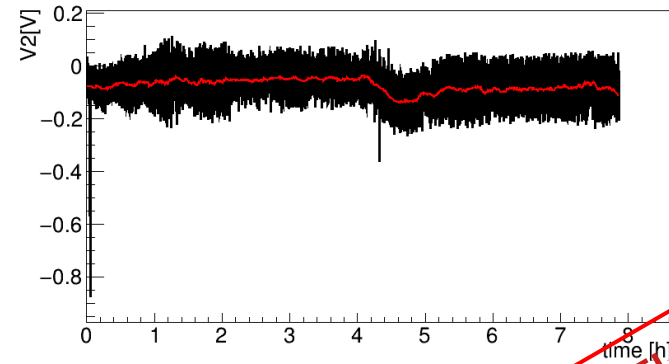

Field mill off
Plate grounded

$$\sigma = 72 \text{ mV (10 kV eq.)}$$

PRELIMINARY

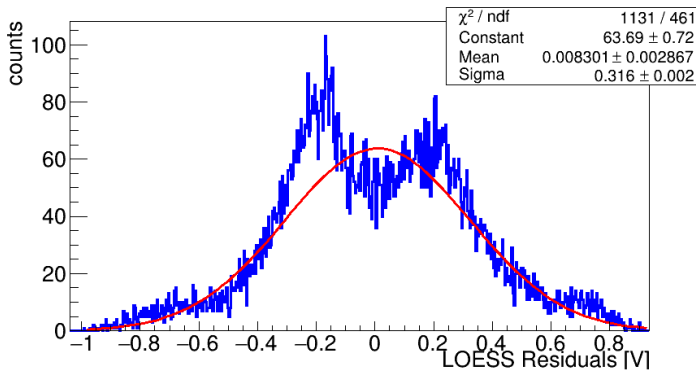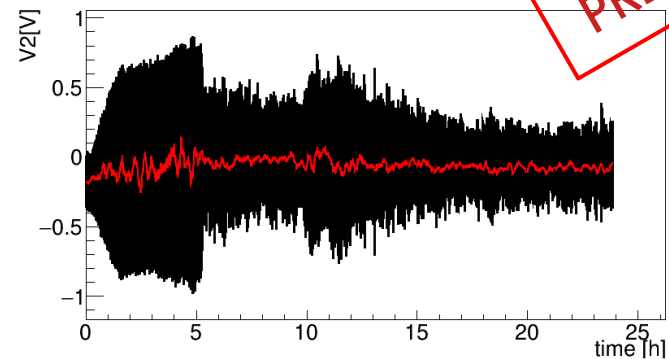

Field mill on
Plate grounded

$$\sigma = 300 \text{ mV (10kV eq.)}$$

Next actions

- Motor **grounding** fix
- Optimization of the field mill signal **amplifier**
- Test on **mechanical stability**
- Tests with the new motor **driver**

Publication of preliminary results [in preparation]

- 0.18 ppm precision on the single board 1kV and extrapolation at 0.8 ppm
- Preliminary 5.5 ppm on 10kV and field mill technology


Part. II

Dynamic voltage reference

Dynamic filter electrode switch

- Change the reference voltage over a **wide range** from 0 to 20 kV
- Change in a **very short time** ($\sim 1\text{ms}$)
- Avoid **electromagnetic noise emission**
- Avoid **leakage current** in switches
- Minimize the **reference diode divider** complexity

Zero level switch

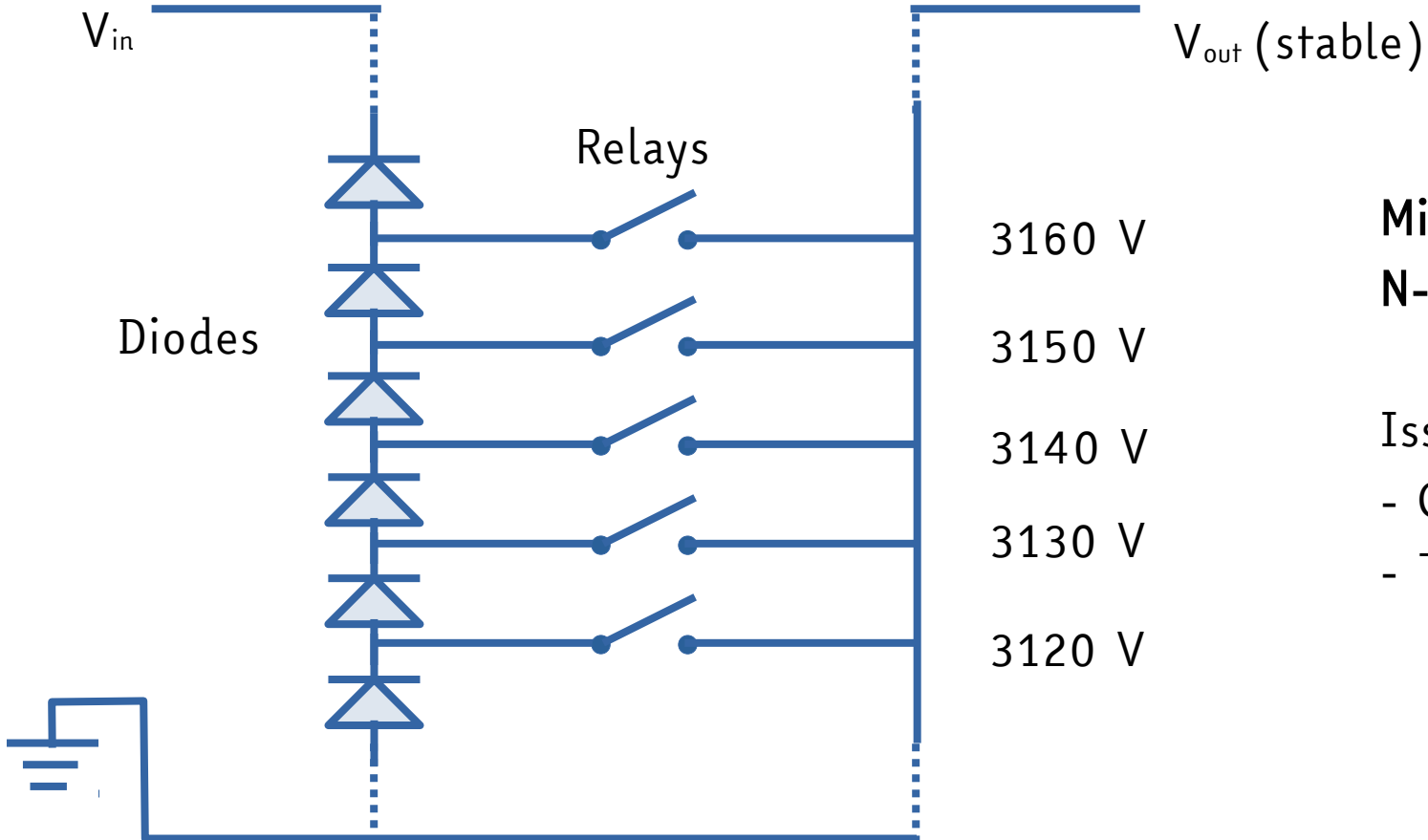


Millipede
N-way switch


Issues:

- Complex system
- Too many components



Multiple switch problem

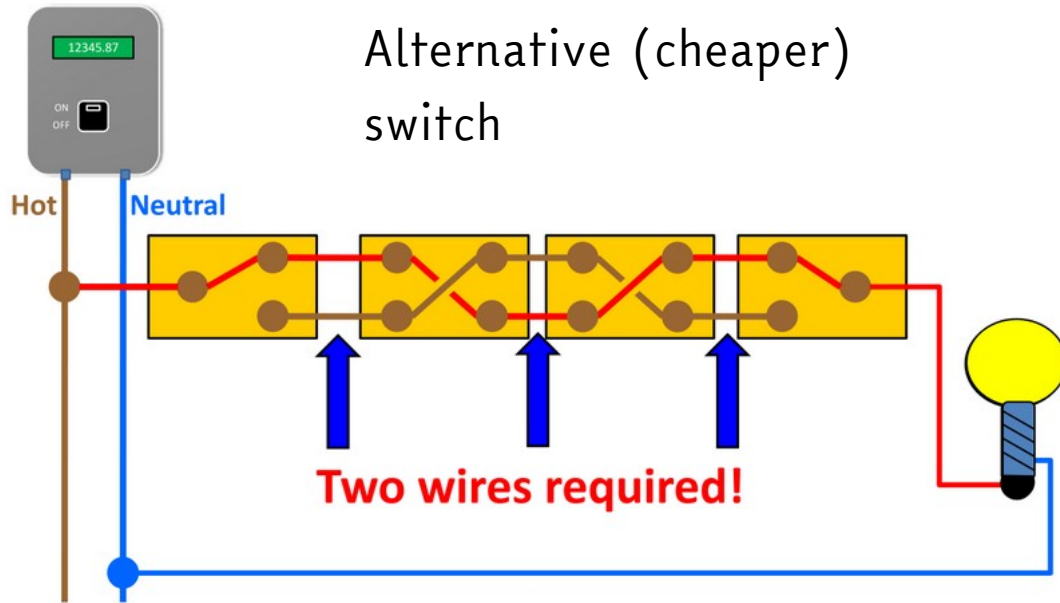

Diverter (3 ways)

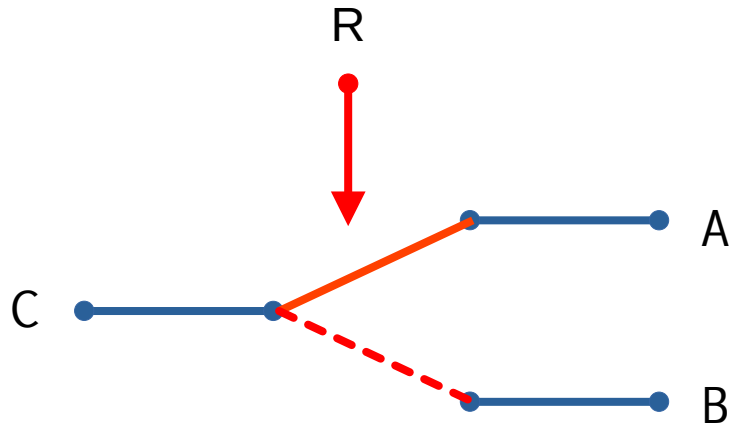

Three
way
witch

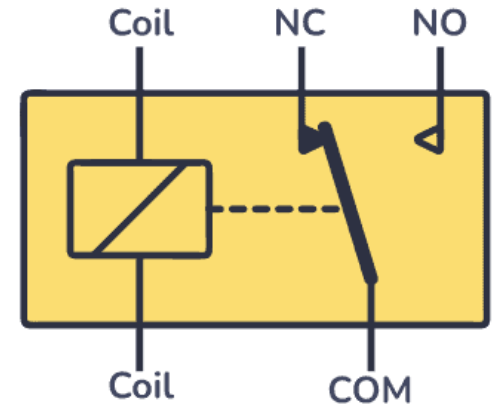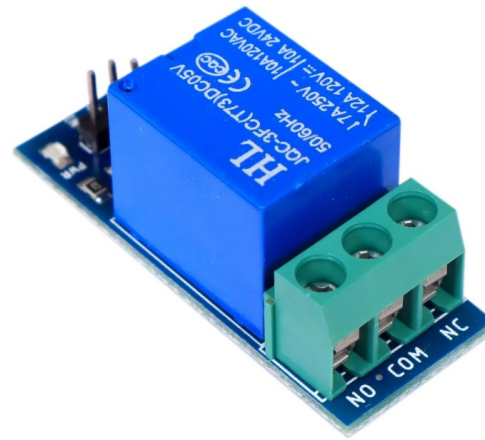


Common coil relay


NC = normally closed

NO = Normally open

Inverter (4 ways)

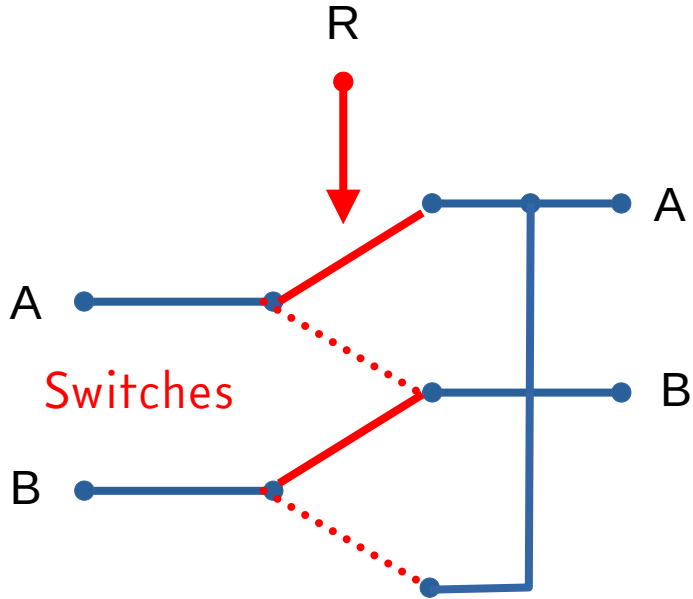

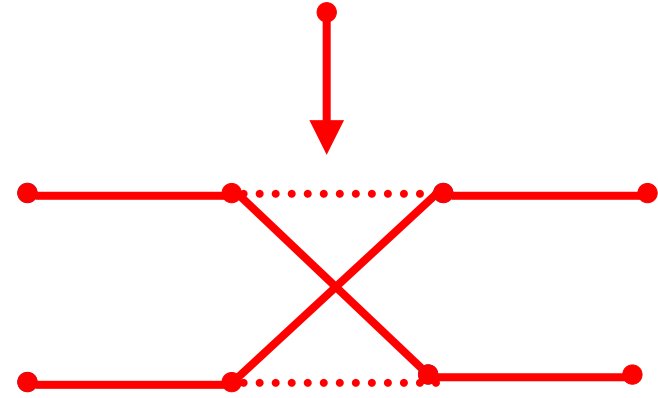
Made of two relays
switching
Simultaneously




Simplified scheme

- I. parallel (direct)
- II. Crossed (inverted)


Encoding

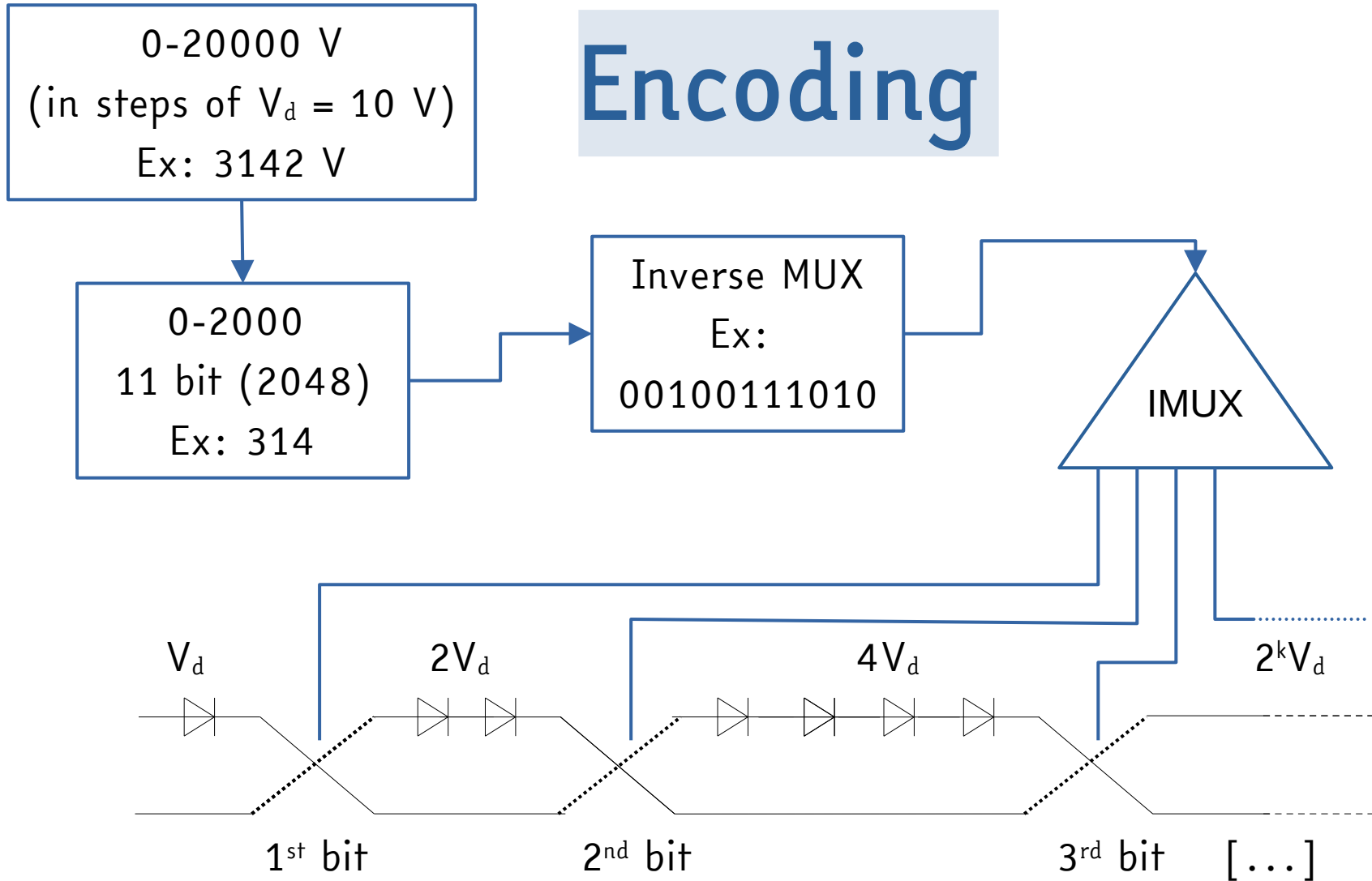


Divider

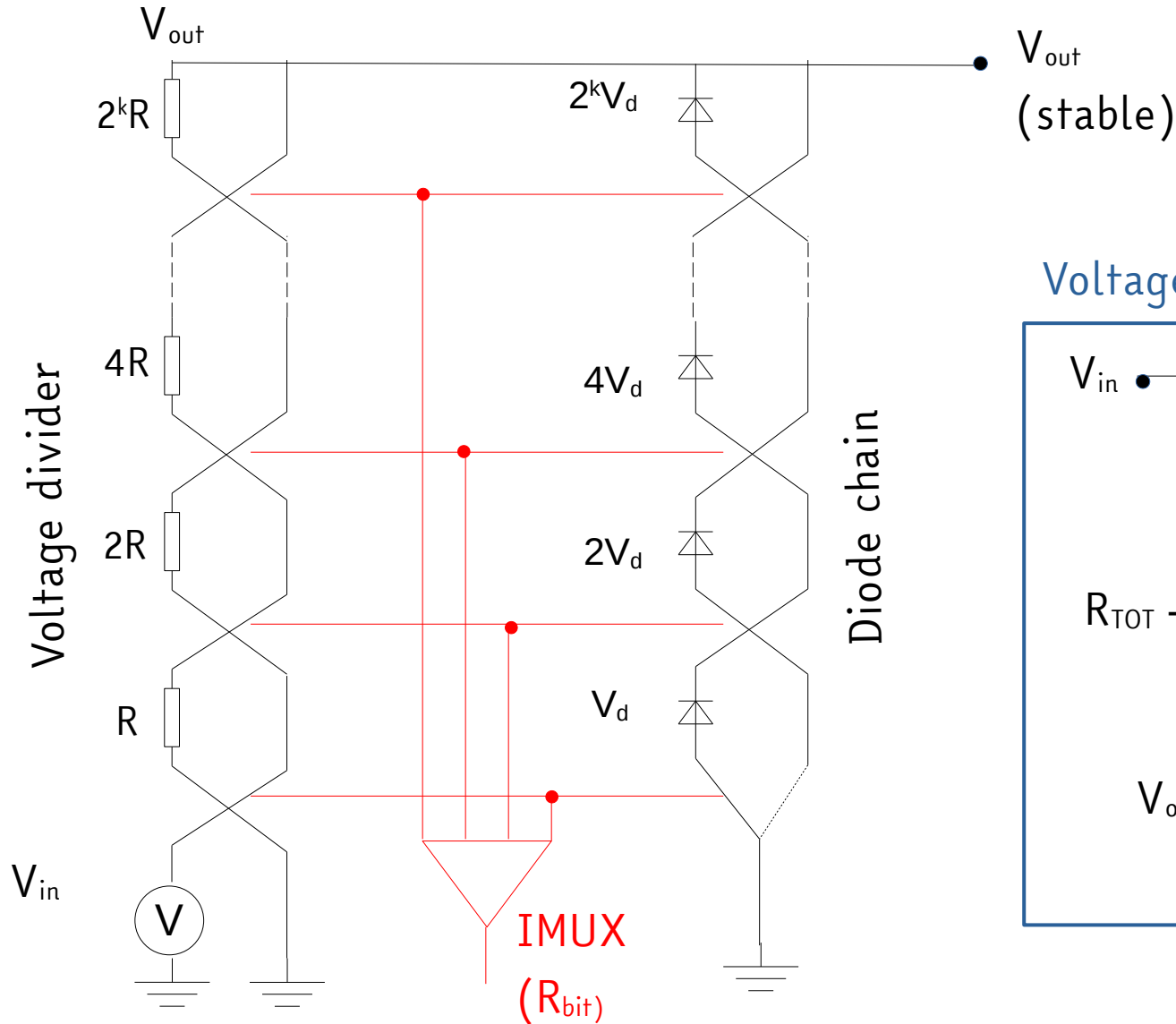

Voltage divider equivalent

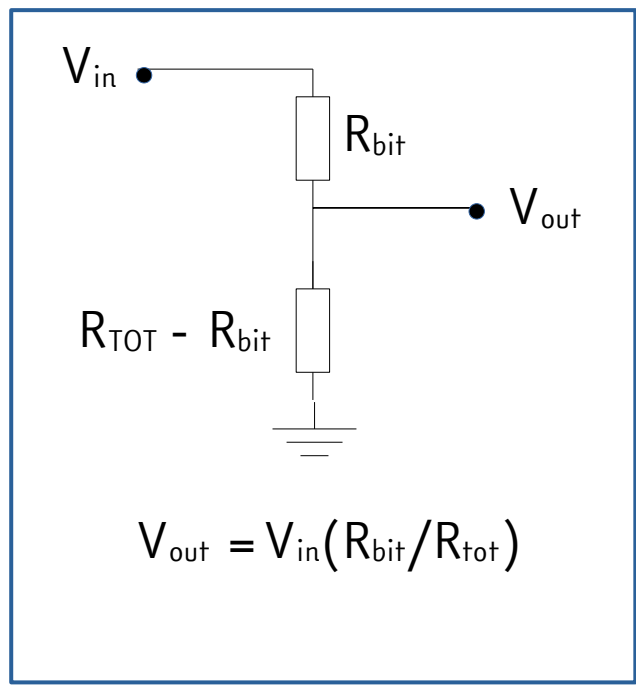


"4 bit" example

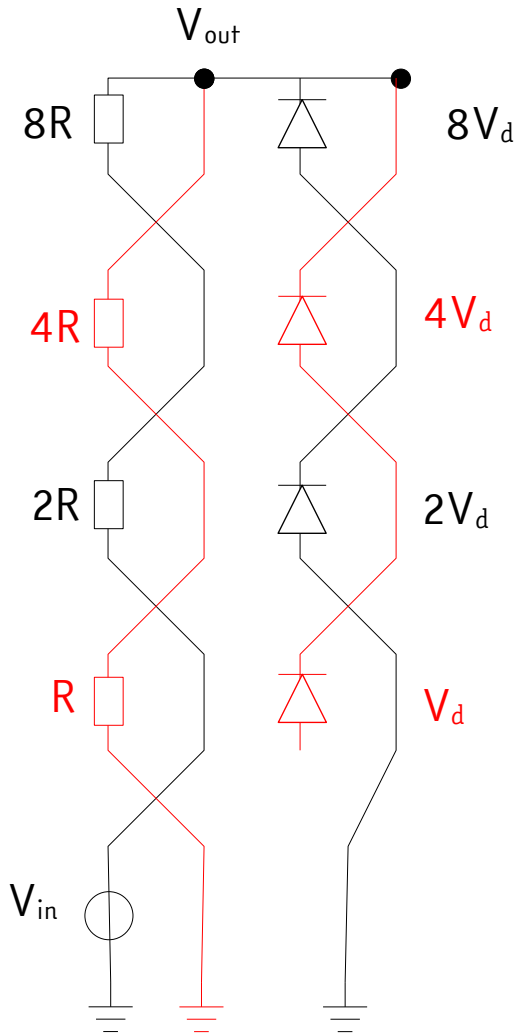

$$1 + 2 + 4 + 8 = 15 \rightarrow V_{in} = 150 \text{ V}$$

$$\text{Ex: } V_{out} = 100 \text{ V}$$
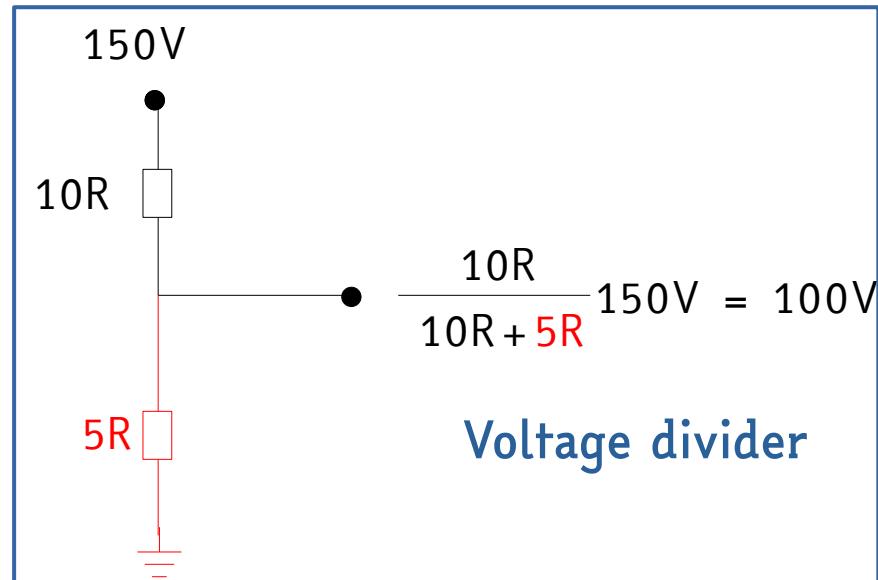
$$100 \rightarrow N = 10 \rightarrow \text{bit} = 1010$$






Diode Chain

$$8V_d + 2V_d \rightarrow 100 \text{ V}$$

High Voltage Relay

On the market...

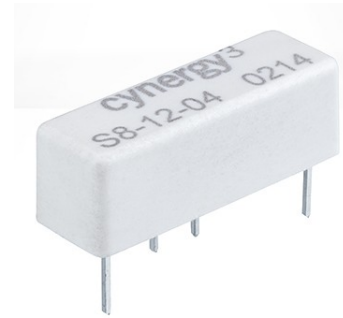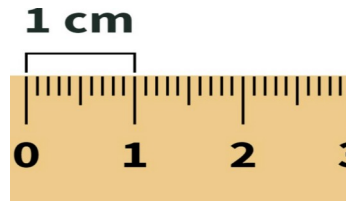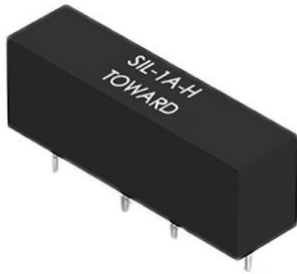

A. Low noise
Solid-state relay (SSR)
(up to 2 kV)

B. Low noise
Reed switch relay
(up to tens of kV)

Next actions

Problem to face

- Fast output
- Leakage current
- Electromagnetic emission
- Field mill inertia

Test bench

- Realization of a small prototype < 1 kV with SSR
- Preliminary test with precision multimeter

Thank you very much!