 


Update on in-strip logic design


Description of actual code

Present pixel readout



Design is strongly based on presently available blocks.
Architecture suited for reading out a Pixel matrix.

Proposed strip readout

 

Design is strongly based on presently available blocks.

Architecture suited for reading out a Pixel matrix.

The idea is to replace the "Pixel matrix" with a Strip matrix.

the size is $128 * \text{MEM_SIZE}$ buffers, subdivided in four submatrices, as before.

The sweeper logic requests a particular TimeStamp (TS)

The Matrix presents all Hits with that specific TS and clears unread data.

Strips module interface

There is only one module that interfaces with:

Readout Block on one side and with the Detector on the other side

```
module Strips(  
  // Outputs  
  output reg [(TOT_SIZE*N_STRIP)-1:0] StripData, // Data to be read (1024 bits)  
  output reg [N_SUBMAT-1:0] FastOr, // Active if one submatrix has data  
  // Inputs  
  input wire [N_STRIP-1:0] HIT, // Inputs coming from the Strip Detector  
  GlobalReset_b, // Allows to reset single strip circuitry  
  StripEnable, // If true corresponding strip is enabled  
  input wire [TS_SIZE-1:0] TSCnt, // Time Stamp Counter  
  input wire [(N_SUBMAT*TS_SIZE)-1:0] TSReq, // Time Stamp Request.  
  // There is one for each submatrix  
  input wire [N_SUBMAT-1:0] ColClearData_b, // Reads data if TS matches  
  ColReadData_b, // Clears data if TS matches  
  input wire RDclk, // System clock  
  BCclk); // BC clock
```

HIT signal is connected to the MC generator that provides the hits

FastOr initiates the readout process and after a TSReq, StripData is set.

Two clock signals (RDclk and BCclk) are used within this module.

Strips module architecture

The main module is divided in two blocks: `StripAnalog` and `StripDigital`

```
StripAnalog Analog(// Inputs
    .StrIn(HIT),           // N_STRIP wide signal
    .BCK(BCK),.CK(CK),     // Clocks used by the design
    // Outputs
    .StripData(IntStripData) // N_STRIP wide signal
);

StripDigital Digital( // Inputs
    .HitData(IntStripData), // N_STRIP wide signal
    .ColClearData_b(ColClearData_b), // N_SUBMAT wide signal
    .ColReadData_b(ColReadData_b), // N_SUBMAT wide signal
    .TSCnt(TSCnt), // TS_SIZE wide signal
    .TSReq(TSReq), // (N_SUBMAT*TS_SIZE) wide signal
    //
    .CK(CK),.BCK(BCK), // Clocks used by the design
    .GlobalReset_b(GlobalReset_b), // N_STRIP wide signal
    // Outputs
    .StripData(StripData), // DATA_SIZE wide signal
    .FastOr(FastOr) // N_SUBMAT wide signal
);
```

`StripAnalog` presently just samples data coming from the MC generator and provides a “fake” `ToT`. It will be replaced with the real Analog model (`FrontEnd + ToT logic`) as soon as it will be available.

StripDigital

StripDigital contains 128 copies of SingleStrip, which stores Data in buffers.

```
module SingleStrip(// Inputs
    input wire [TS_SIZE-1:0] TSCnt,    // TimeStamp Counter
    input wire [TS_SIZE-1:0] TSReq,    // Requested Time Stamp
    input wire [TOT_SIZE-1:0] ToT,     // ToT coming from the analog part
    input wire Read,                  // If 1 we read out the strip memory data
    input wire Clear,                // If 1 we clear the strip memory data
    input wire Write,                // If true we have to write data
    input wire CK,                   // System clock
    input wire BCK,                  // BC clock
    input wire Reset,                // Active high Reset

    // Outputs
    output reg [DATA_SIZE-1:0] StripData, // Data to be read (DATA_SIZE Data words)
    output reg HasData,                  // True if the strip has data
);
DataWord [MEM_SIZE-1:0] Data;          // Data to store Hits
WritePointer WrPtr;                    // Write pointer
ReadPointer RdPtr;                     // Read pointer
...
```

DataWord is the buffer and is addressed by a RdPtr and a WrPtr.

MEM_SIZE is the depth of the buffer (16, 32, ..., bit deep)

DATA_SIZE is the width of each output word. (10 TS bit + 4 ToT bit wide)

Conclusions

- We presently have a working framework for simulating the entire chip:
 - Digital In-strip logic has been implemented.
 - Interfaces correctly with existing Digital output logic.
- Ongoing simulations will provide the depth of buffers with 100% efficiency.

Still to be done

- Implement “correct” Analog section, with chosen ToT generation.
- Investigate some crucial design parameters:
 - Area of the Buffers in function of their depth.
 - Possible power consumption.

Need to perform some preliminary synthesis with chosen technology.