

MARIE CURIE IAPP: FAST TRACKER FOR HADRON COLLIDER EXPERIMENTS

1ST SUMMER SCHOOL: VHDL BOOTCAMP


PISA, JULY 2013

Finite State Machines (FSMs)

Calliope-Louisa Sotiropoulou

PhD Candidate/Researcher

Aristotle University of Thessaloniki

 

AUTH e-LAB

Aristotle University of Thessaloniki-Electronics Laboratory




UNIVERSITÀ DI PISA

Finite State Machines

Finite State Machines

- A **finite state machine (FSM)** is a sequential logic circuit which moves between a finite set of states, dependent upon the values of the inputs and the previous state. The state transitions are synchronized on a clock.
- FSMs are used for designs who require a defined sequence of events (e.g. **control modules**)
- They consist of two parts:
 - Combinational Logic
 - Memory elements


Finite State Machines

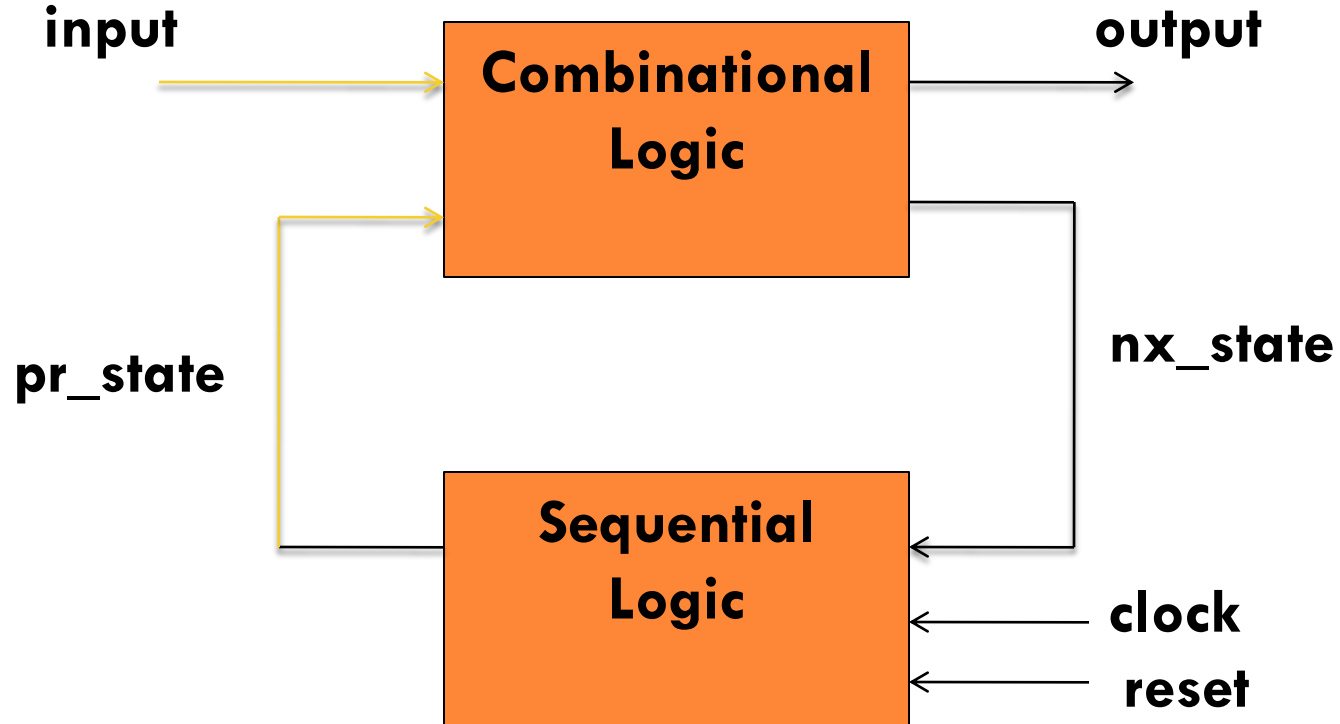


Finite State Machines

- There are two different types of FSMs **Mealy** vs **Moore**
- **Moore Machines:**
 - Outputs are a function of current state
 - Outputs change synchronously with state changes
- **Mealy machine:**
 - Outputs depend on state and on inputs
 - Input changes can cause immediate output changes (asynchronous)

Moore vs Mealy Machines

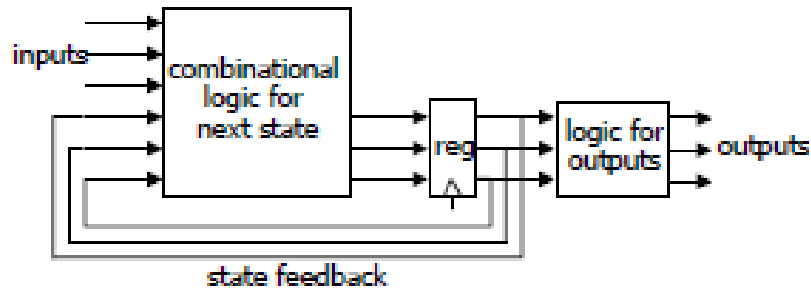

Moore Machine

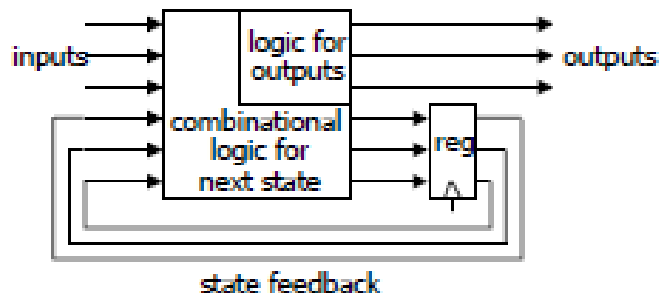

Mealy Machine

How to write an FSM – Style 1

- Using two processes: One for the combinational part and one for the FSM state
- For the different states a new enumerated type of signal is usually defined

Process (reset, clock)

Begin

if (reset='1') then

pr_state <= state0;

elsif (clock'event and clock='1') then

pr_state <= nx_state;

end if;

End process;

How to write an FSM – Style 1

Process (input, pr_state)

Begin

```
    case pr_state is
        when state0 =>
            if (input = ...) then
                output <= <value>;
                nx_state <= state1;

            else ...
            end if;

        when state1 =>
            if (input = ...) then
                output <= <value>;
                nx_state <= state2;

            else ...
            end if;

        when state2 =>
            if (input = ...) then
                output <= <value>;
                nx_state <= state1;

            else ...
            end if;
```

...

end case;


End process;

The use of **CASE** is very common

All the input signals must be in the sensitivity list

All the possible outputs must be defined

How to write an FSM – Style 1

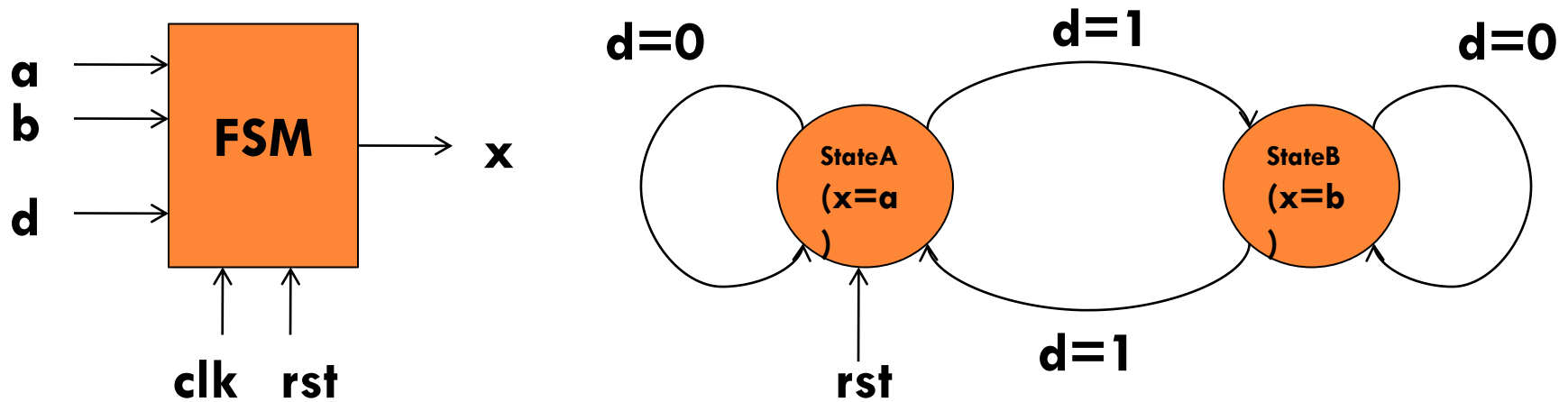

Entity simple_fsm is

```
port (a, b, d, clk, rst: in bit;  
      x: out bit);
```

End simple_fsm;

Architecture simple_fsm of simple_fsm is

```
type state is (stateA, stateB);  
signal pr_state, nx_state: state;
```

Begin

How to write an FSM – Style 1

----- sequential part -----

```
Process (rst, clk)
Begin
    if (rst='1') then
        pr_state <= stateA;
    elsif (clock'event and clk='1') then
        pr_state <= nx_state;
    end if;
End process;
```

----- combinational part-----

```
Process (a, b, d, pr_state)
Begin
    case pr_state is
        when stateA =>
            x <= a;
            if (d='1') then nx_state <= stateB;
            else nx_state <= stateA;
            end if;
        when stateB =>
            x <= b;
            if (d='1') then nx_state <= stateA;
            else nx_state <= stateB;
            end if;
    end case;
End process;
End simple_fsm;
```

How to write an FSM – Style 2

- The output is assigned on clock change
- Only one process is used

Architecture <arch_name> of <ent_name>

type states is (state0, state1, state2, state3, ...);

signal pr_state: states;

signal temp: <data_type>

Begin

Process (reset, clock, pr_state)

Begin

if (reset='1') then

pr_state <= state0;

elsif (clock'event and clock='1') then

case pr_state is

when state0 =>

output<= <value>;

if (condition) then pr_state <= state1;

...

end if;

when state1 =>

output<= <value>;

if (condition) then pr_state <= state2;

...

end if;

.....

end case;

end if;

end process;

End <arch_name>;

Example – BCD counter

```
library ieee;
use ieee.std_logic_1164.all;

-----
entity counter is
    port ( clk, rst: in std_logic;
          count: out std_logic_vector (3 downto 0));
end counter;

-----
architecture state_machine of counter is
    type state is (zero, one, two, three, four,
                  five, six, seven, eight, nine);
    signal pr_state, nx_state: state;
begin
    -----
    process (rst, clk)
    begin
        if (rst='1') then
            pr_state <= zero;
        elsif (clk'event and clk='1') then
            pr_state <= nx_state;
        end if;
    end process;
end;
```

Example – BCD counter

```
-----
process (pr_state)
  begin
    case pr_state is
      when zero =>
        count <= "0000";
        nx_state <= one;
      when one =>
        count <= "0001";
        nx_state <= two;
      when two =>
        count <= "0010";
        nx_state <= three;
      ....
      when eight =>
        count <= "1000";
        nx_state <= nine;
      when nine =>
        count <= "1001";
        nx_state <= zero;
    end case;
  end process;
end state_machine;
```

FSM

- So...

What does our FSM do?